

Computer Architecture
CPSC 32, Fall Semester 2003

Lab Assignment #4

Due: Week of November 3– November 7, demonstrate in your lab,
complete by yourself

1 Assignment

Problem 1 [15 points] Write Verilog code that represents a JK flip-flop. Use behavioral code rather than structural code. Recall that a JK flip-flop has the truth table

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\overline{Q}(t)$

Assume that the state changes on a positive edge.

Problem 2 [15 points] Write Verilog code that represents a T flip-flop with an asynchronous clear input. Use behavioral code, rather than structural code.

```
module TFF(clk, T, clr, Q);
  input clk, T, clr;
  output Q;
  ...
endmodule
```

A T flip-flop has the following behavior

clr	T	$Q(t+1)$
0	x	0
1	0	$Q(t)$
1	1	$\overline{Q}(t)$

Problem 3 [25 points] Write a three-bit up/down-counter `updown` using the T flip-flops from the previous exercise. It should have a control input `down` such that if `down=0` then it should behave as an up-counter, and if `down=1` then it should behave as a down-counter.

```

module updown(clk, clr, Q);
    input clk, clr;
    output [2:0] Q;
    ...
endmodule

```

Write a testbench that lets `updown` count 15 cycles up, and then 5 cycles down, and then finishes the simulation. Use `$monitor` to trace the output of the updown counter. You can use the `m555` module discussed in the lecture to create the clock signal.

Problem 4 [15 points] A sequential circuit has two inputs w_1 and w_2 , and an output z . Its function is to compare the input sequences on the two inputs. If $w_1 = w_2$ during any four consecutive clock cycles, the circuit produces $z = 1$; otherwise $z = 0$. For example

```

w1: 0110111000110
w2: 1110101000111
z: 0000100001110

```

Derive a suitable circuit.

Problem 5 [20 points] Write a finite state machine in Verilog for the previous problem. Is this a Moore machine?

Problem 6 [10 points] The following code checks for adjacent ones in an n -bit vector.

```

always @(A)
begin
    f = A[1] & A[0];
    for(k = 2; k<n; k=k+1)
        f = f | (A[k] & A[k-1]);
end

```

With blocking assignments this code produces the desired logic function $f = a_1a_0 + \dots + a_{n-1}a_{n-2}$. What logic function is produced if we change the code to use non-blocking assignments? Explain.

Demonstrate your solutions in your lab sessions, and turn in written solutions for Problems 4 and 6 at the same time.

Reading Assignment Read chapter 7 of the book by Brown and Vranesic. This chapter is freely available from the McGraw-Hill website (use google: mcgraw-hill brown vranesic).