

# Model Neurons: Neuroelectronics

## (Part I)


Dayan and Abbott (2001) Chapter 5 and Appendix A.4.

- Basic electrical circuits.
- Passive membrane model.
- Single compartment model.
- Integrate-and-fire neurons.
- Hodgkin-Huxley model.
- Synaptic conductances.

Instructor: Yoonsuck Choe; CPSC 644 Cortical Networks

1

### Electrical Circuits

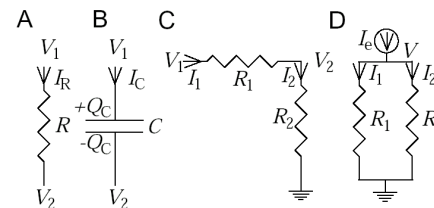

- Ohm's law:

$$V_R = I_R R,$$

V: voltage, I: current, R: resistance.

- Charge across a capacitor:


$$C V_C = Q_C$$

$$C \frac{dV_C}{dt} = \frac{dQ_C}{dt} = I_C,$$

V: voltage, Q: charge, I: current.

2
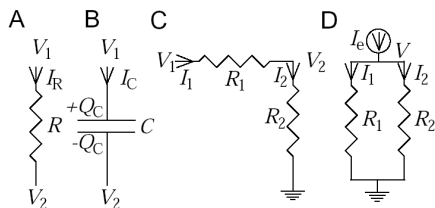
### Electrical Circuits: Serial Resistors



Kirchhoff's current law: At a node, all currents sum to zero (or, sum of incoming = sum of outgoing currents).

- Example C: at node next to  $V_2$ ,  $I_1 = I_2$ . Thus:


$$V_1 - V_2 = I_1 R_1, V_2 - 0 = I_2 R_2$$

$$V_1 = I_1(R_1 + R_2), V_2 = I_2 R_2 = I_1 R_2$$

$$V_2 = \frac{V_1 R_2}{R_1 + R_2}.$$

3
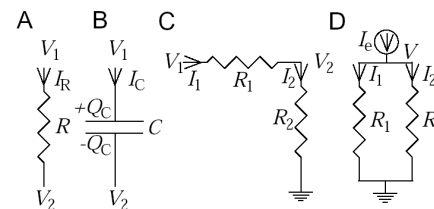
### Electrical Circuits: Parallel Resistors



At the node next to  $V$ ,  $I_e = I_1 + I_2$ .


$$I_1 = \frac{V}{R_1}, I_2 = \frac{V}{R_2}$$

$$I_e = \frac{V}{R_1} + \frac{V}{R_2} = \frac{R_1 + R_2}{R_1 R_2} V$$

Thus, total resistance of parallel resistors is  $\frac{R_1 R_2}{R_1 + R_2}$ .

4

## Resistor-Capacitor Circuit (I)

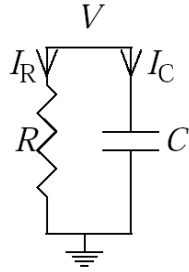

Case A: No external current source:  $I_R + I_C = 0$ .


$$I_R + I_C = \frac{V - 0}{R} + C \frac{dV}{dt} = 0$$

$$C \frac{dV}{dt} = -\frac{V}{R}$$

which is a homogeneous linear differential equation, and the general solution is (straight-forward integration after separating the variables):  $V(t) = V(0) \exp(-t/RC)$ .

5

## Resistor-Capacitor Circuit (II)

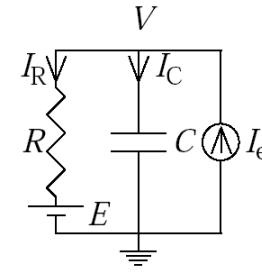

Case B: With external current source:  $I_R + I_C = I_e$ .


$$I_R + I_C = \frac{V - E}{R} + C \frac{dV}{dt} = I_e$$

$$C \frac{dV}{dt} = \frac{E - V}{R} + I_e$$

which is a nonhomogeneous linear differential equation, and the general solution is:  $V(t) = V_\infty + (V(0) - V_\infty) \exp(-t/\tau)$ .

6
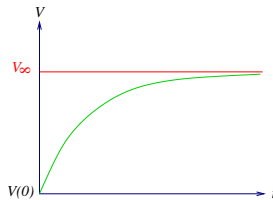
## Resistor-Capacitor Circuit (II, Cont'd)



The steady state of the membrane equation is:

$$C \frac{dV}{dt} = \frac{E - V}{R} + I_e = 0,$$

$$V = E + I_e R,$$


which we define as  $V_\infty = E + I_e R$ , and the time constant is  $\tau = RC$ , which gives the equation in the previous page:

$$V(t) = V_\infty + (V(0) - V_\infty) \exp(-t/\tau).$$

For the solution, first get the general solution  $V_h$  for the homogeneous case and set  $V = V_h \cdot u$ , where  $u$  is a dummy variable. Solve for  $V$ .

7


## Single Compartment Model

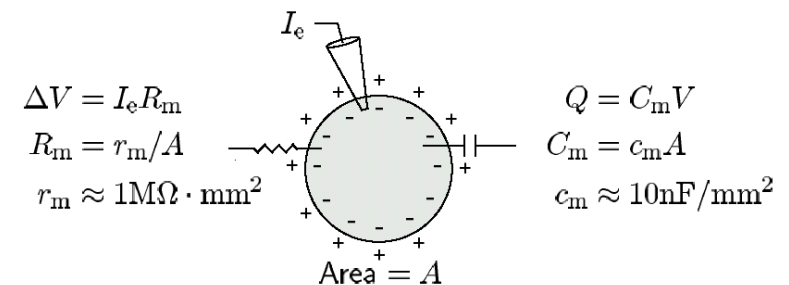

- $V$ : membrane potential
- $r_m$ : specific membrane resistance
- $c_m$ : specific membrane capacitance
- $I_e$ : input current
- Conductance: reciprocal of resistance, denoted  $g$ .

8

## Single Compartment Model: Circuit

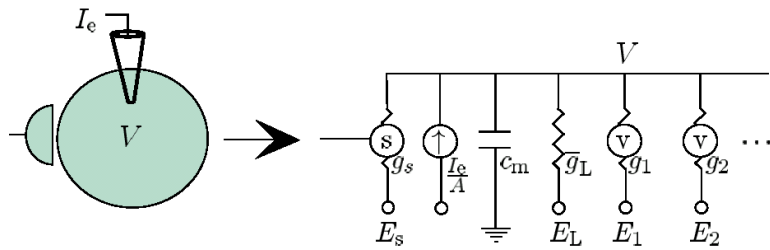

- Leakage current:  $i_L = \bar{g}_L(V - E_L)$ .
- Membrane current:  $i_m = \sum_i g_i(V - E_i)$ .
- Input current:  $I_e/A$ .
- Current across capacitor:  $c_m \frac{dV}{dt} = I_C$ .

9

## Integrate and Fire Models

- Basically an RC circuit with the R-part serving as the leakage:

$$c_m \frac{dV}{dt} = -\bar{g}_L(V - E_L) + \frac{I_e}{A}.$$

- Multiplying both sides with  $r_m$  gives  
( $r_m = 1/\bar{g}_L$ ,  $\tau_m = r_m c_m$ ,  $R_m = r_m/A$ ):


$$\tau_m \frac{dV}{dt} = E_L - V + R_m I_e.$$

When  $I_e = 0$ , steady state voltage becomes  $V = E_L$ , which is the resting membrane potential ( $V_{rest}$ ).

- When  $V$  reaches a threshold  $V_{th}$ , generate a spike and reset the membrane potential to  $V_{rest}$ .

11

## Single Compartment Model: Equation

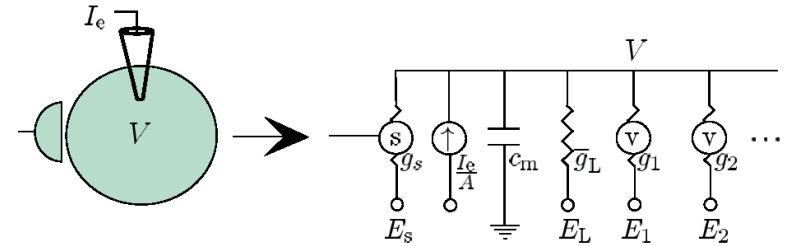

Incoming:  $I_e/A$ ; Outgoing: all the rest. So, we get:

$$\frac{I_e}{A} = c_m \frac{dV}{dt} + \sum_i g_i(V - E_i),$$

which becomes:

$$c_m \frac{dV}{dt} = -i_m + \frac{I_e}{A}.$$

10

## Integrate and Fire Models: Analytic Solution

- Exact solution gives:

$$V(t) = E_L + R_m I_e + (V(0) - E_L - R_m I_e) \exp(-t/\tau_m),$$

which is the same as in page 7.

- $V_\infty = E_L + R_m I_e$ , and this value should be greater than the threshold  $V_{th}$  for the neuron to fire at all. Given a fixed  $E_L$  and  $R_m$ , the only thing that can change  $V_\infty$  is then the input current  $I_e$ .
- Given a constant input current  $I_e$  that allows spiking, the spiking frequency can be analytically calculated.
- First, calculate the time to first spike, when  $V(t) = V_{th}$  with  $V(0) = V_{rest}$ , and solve for  $t$ .

12

## Integrate and Fire Models: Firing Rate


- The calculation comes out to:

$$t_{\text{isi}} = \tau_m \ln \left( \frac{R_m I_e + E_L - V_{\text{rest}}}{R_m I_e + E_L - V_{\text{th}}} \right).$$

- Since the neuron will fire every  $t_{\text{isi}}$  time units, this gives the “inter-spike interval” (or ISI).
- Thus, firing occurs with a period of  $t_{\text{isi}}$ , and so the firing frequency is  $r_{\text{isi}} = 1/t_{\text{isi}}$ .
- Note again that  $V_{\text{th}} < V_{\infty} = E_L + R_m I_e$  must hold. Otherwise, no spikes.

13

## Integrate and Fire Model

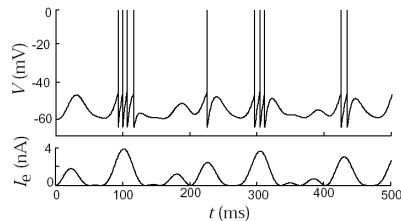


- INF model with a fluctuating driving input is shown.
- The spikes (the long peaks) are shown just as a visualization, and they are not represented in the equation.
- Usually simple numerical integration is used for the simulation (use Taylor series expansion and drop higher-order terms):

$$\tau_m \frac{\Delta V}{\Delta t} = E_L - V(t) + R_m I_e(t)$$

$$\Delta V = \frac{(E_L - V(t) + R_m I_e(t))}{\tau_m} \Delta t$$

$$V(t + \Delta t) \approx V(t) + \Delta V.$$

## Integrate and Fire Model: Firing Rate

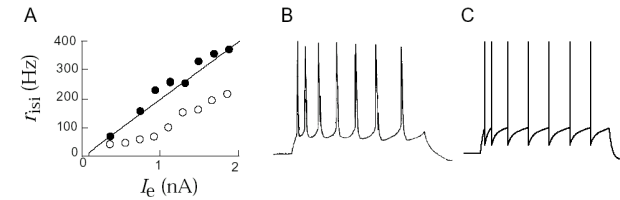

- Plot shows  $r_{\text{isi}}$  dependent on the input current (in INF vs. real data), and real neuron vs. INF firing.
- Without spike adaptation, INF fits the real data well (black dots).
- Spike adaptation means dynamic change in firing rate as a neuron keeps firing.

14