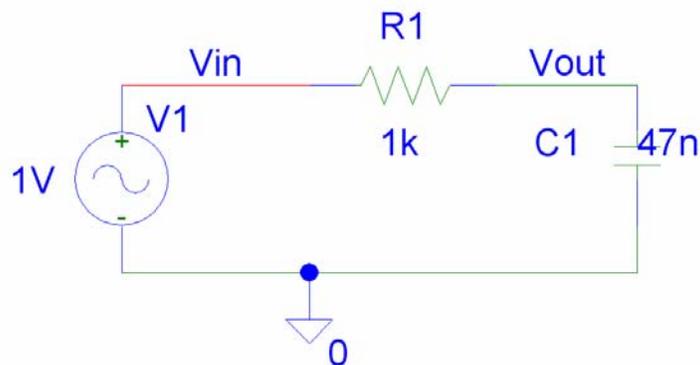


ELEN 325 – Fall 2007

RC Filter Simulation

1. Open PSPICE/Schematics
2. Place components for your circuit
 - a. Go to “Draw” menu
 - b. Get new part...
 - c. Click on Libraries if you can't see the component you are looking for
 - d. Search within the libraries listed on right column
 - e. Place components on schematic window
3. Connect components
 - a. Go to “Draw” menu
 - b. Wire
 - c. Connect nodes by clicking on them and wiring as desired
4. Edit component values
5. Label nodes by double-clicking on wire and entering name (ex: vin, vout, v1, etc)



6. Setup analysis
 - a. Go to “Analysis” menu
 - b. Setup
 - c. AC Sweep
 - d. AC Sweep Type = Decade
7. Save Schematic
8. Run simulation
 - a. Go to “Analysis” menu
 - b. Simulate
 - c. Plotting window will open automatically (**remaining steps 9-12 should be done in this window**)
9. Add plot to window so that you can plot the magnitude and phase separate
 - a. Go to “Plot” menu
 - b. Add plot to window
10. Plot Magnitude in dB (**use top window**)

- a. Go to "Trace" menu
- b. Add Trace
- c. Deselect "Currents" and "Alias Names" boxes
- d. Click on "DB()" in functions and macros column on the right
- e. Click on node name you want to plot on simulation output variables list
- f. OK
- g. Adjust Y-axis if desired by double-clicking on it and setting the range for min and max values you want to display

11. Plot Phase in degrees (**in bottom window**)

- a. Go to "Trace" menu
- b. Add Trace
- c. Click on "P()" in functions and macros column on the right
- d. Click on node name you want to plot on simulation output variables list
- e. OK
- f. Adjust Y-axis if desired by double-clicking on it and setting the range for min and max values you want to display

12. Measure corner (-3 dB) frequency

- a. Go to "Trace" menu
- b. Cursor
- c. Display
- d. Click on magnitude plot
- e. Drag cursor with your mouse until you get to - 3dB
- f. Click on "Mark Label" button to mark the -3 dB point on the plot

