

ECEN474: (Analog) VLSI Circuit Design

Fall 2011

Lecture 19: Fully Differential Amplifiers & CMFB




Sebastian Hoyos
Analog & Mixed-Signal Center
Texas A&M University

Agenda

- Feedback amplifier examples
- Fully differential circuits
- Common-mode feedback introduction

Non-Inverting Amplifier Example

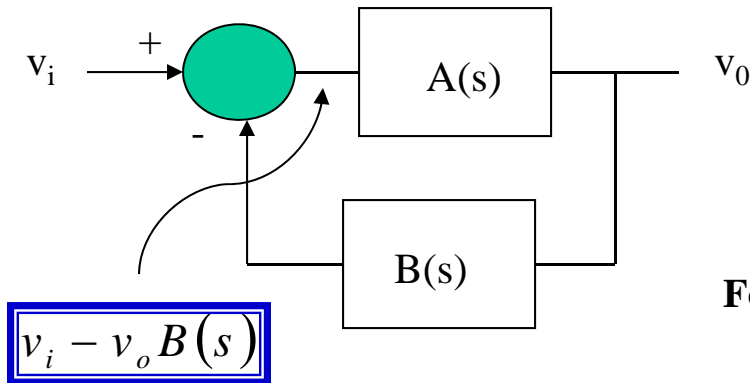

$$\frac{v_o}{v_i} = \frac{A(s)}{1 - (-T(s))}$$

If $T(s) \gg 1$, then $\frac{v_o}{v_i} \cong \frac{A(s)}{T(s)} = \frac{1}{B(s)}$

For Error, can write: $\frac{v_o}{v_i} = \frac{1}{B(s)} \left[\frac{T(s)}{1+T(s)} \right] = \frac{1}{B(s)} \left[\frac{1}{1 + \frac{1}{T(s)}} \right]$

Error $\propto -\frac{1}{T(s)}$


Key points:

If you want to amplify your signal: B(s) must be an attenuator (voltage divider!!)


The error is determined by the overall loop gain: T(s)=A(s)B(s)

$$B(s) = \frac{Z_1}{Z_1 + Z_2} = \frac{1}{1 + \frac{Z_2}{Z_1}}$$
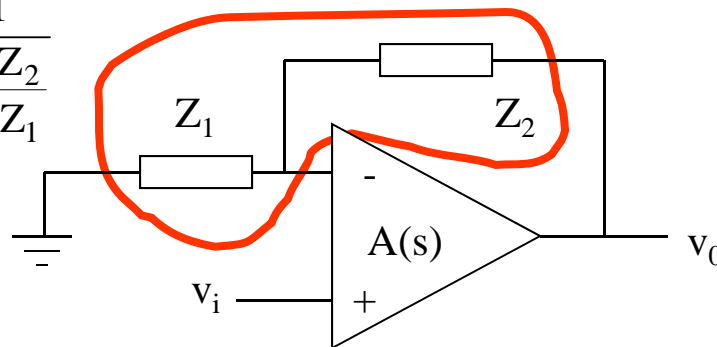
$$\frac{v_o(s)}{v_i(s)} \cong 1 + \frac{Z_2}{Z_1}$$






A(s) is amplifier response only

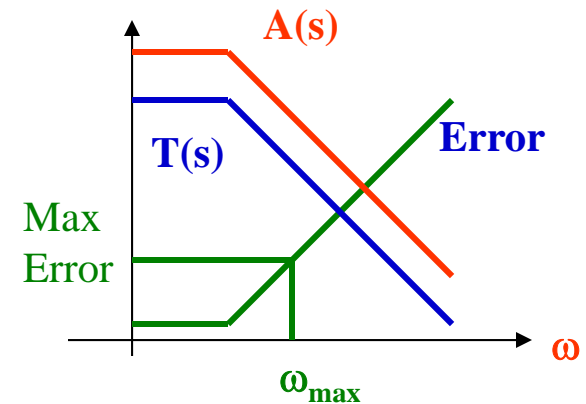

Inverting Amplifier: Apply superposition

A(s) and B(s) are sharing some elements!!

A(s) = ? B(s) = ? T(s) = ?

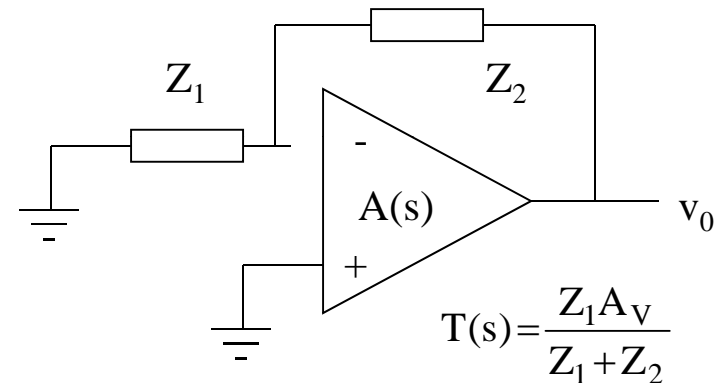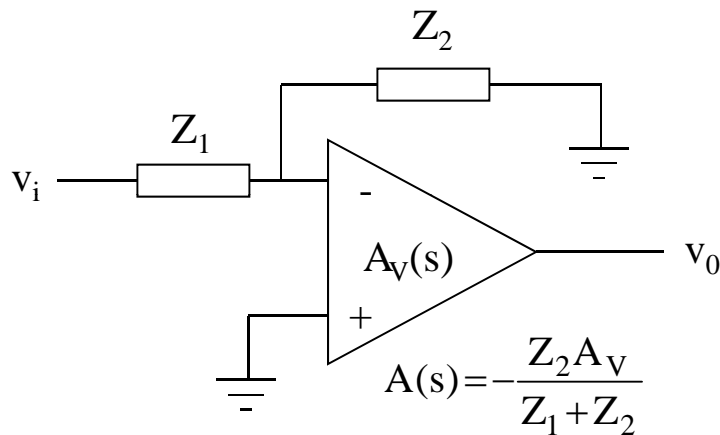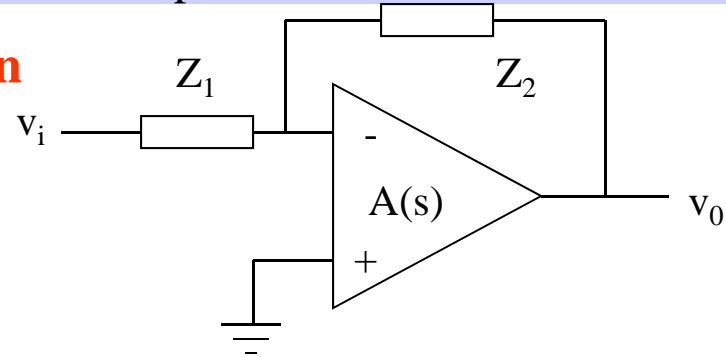



From $T(s) = A(s)B(s)$

$$B(s) = \frac{T(s)}{A(s)} = -\frac{Z_1}{Z_2}$$

$$\frac{v_o(s)}{v_i(s)} \cong \frac{1}{B(s)} = -\frac{Z_2}{Z_1}$$

$$\frac{v_0}{v_i} = \frac{A(s)}{1+T(s)} = -\frac{\frac{Z_2 A_V}{Z_1 + Z_2}}{1 + \frac{Z_1 A_V}{Z_1 + Z_2}} = -\frac{Z_2}{Z_1} \left(\frac{1}{1 + \frac{Z_2}{Z_1} \frac{1}{A_V}} \right)$$

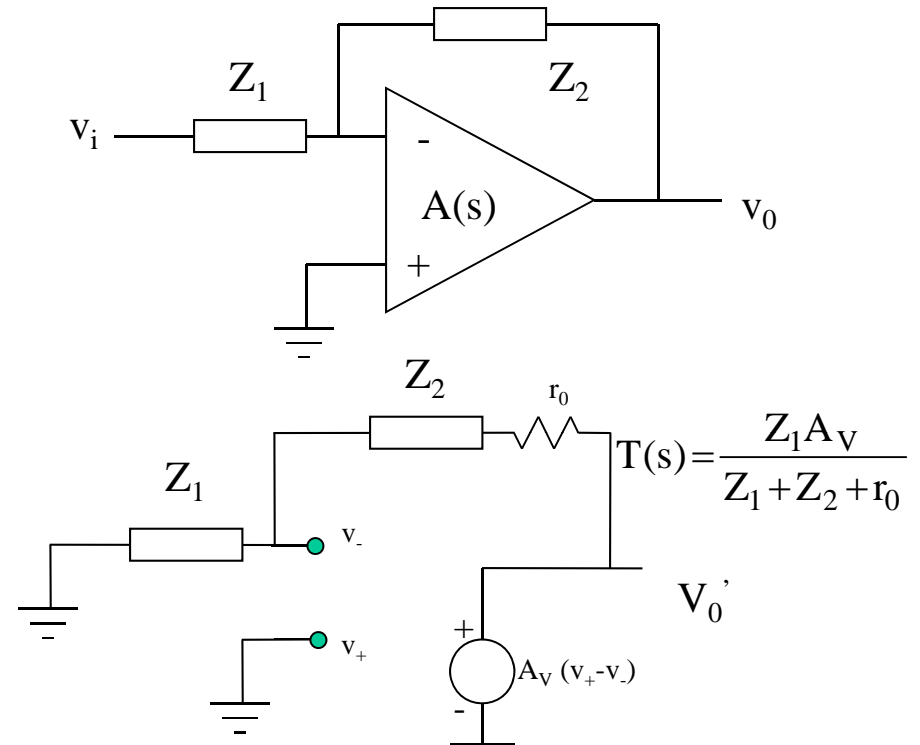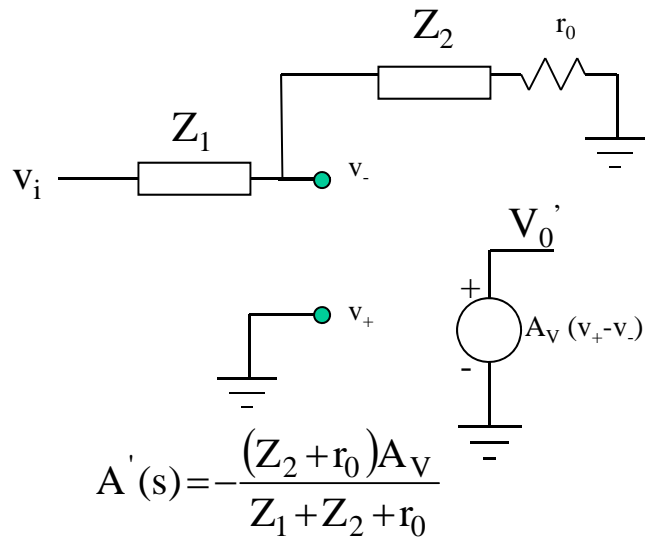Inverting Amplifier: consider the non-zero output impedance!!




$$\frac{v_o'(s)}{v_i} = -\frac{\frac{(Z_2 + r_0)A_V}{Z_1 + Z_2 + r_0}}{1 + \frac{Z_1 A_V}{Z_1 + Z_2 + r_0}}$$

$$\frac{v_o}{v_i}(s) = \left(\frac{v_o'}{v_i} \right) \frac{Z_1 + Z_2}{Z_1 + Z_2 + r_0} = -\frac{Z_2}{Z_1} \left[\frac{1 - \frac{r_0}{A_V Z_2}}{1 + \frac{Z_2 + r_0}{Z_1}} \right]$$

Inverting Amplifier: consider the non-zero output impedance!!
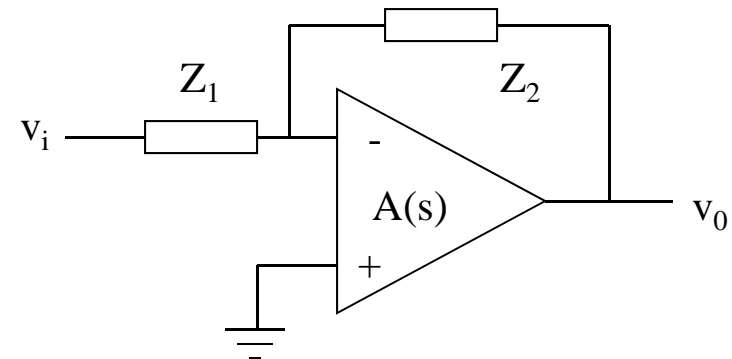
$$\frac{v_o}{v_i}(s) = -\frac{Z_2}{Z_1} \left[\begin{array}{c} 1 - \frac{r_0}{A_V Z_2} \\ 1 + \frac{Z_2 + r_0}{Z_1} \\ 1 + \frac{Z_1}{A_V} \end{array} \right]$$



The error can be approximated as:

$$\text{Error} \cong \frac{r_0}{A_V Z_2} - \frac{1 + \frac{Z_2 + r_0}{Z_1}}{A_V}$$

IDEAL GAIN

Determined by the OPAMP open-loop gain

Determined by the OPAMP output impedance




Common-Mode Feedback Techniques for Analog Circuits

Jose Silva-Martinez


Texas A&M University

Department of Electrical and Computer Engineering

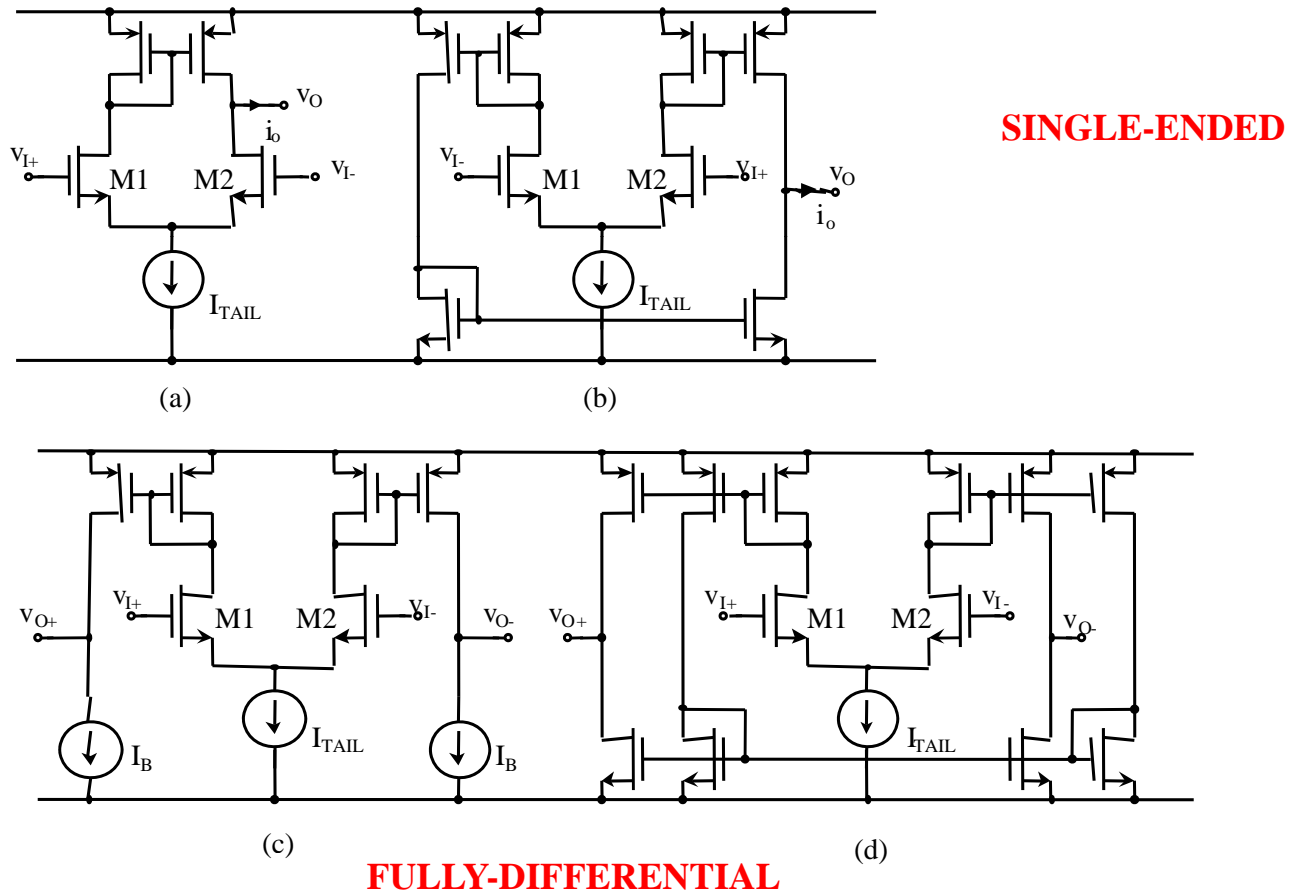Basic Operational Transconductance Amplifier Topologies



Fully-Differential Circuits

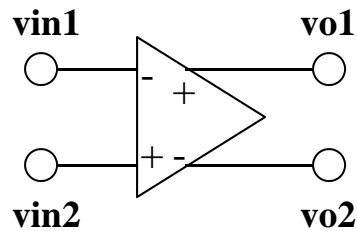

In general:

$$v_{o1} = \frac{v_{o1} - v_{o2}}{2} + \frac{v_{o1} + v_{o2}}{2} = \frac{v_{od}}{2} + v_{oc}$$

$$v_{o2} = \frac{v_{o2} - v_{o1}}{2} + \frac{v_{o1} + v_{o2}}{2} = -\frac{v_{od}}{2} + v_{oc}$$

➤ Hence

$$\begin{bmatrix} v_{od} \\ v_{oc} \end{bmatrix} = \begin{bmatrix} A_{dd} & A_{dc} \\ A_{cd} & A_{cc} \end{bmatrix} \begin{bmatrix} v_{id} \\ v_{ic} \end{bmatrix}$$

Differential-mode output

$$A_{dd} = \left. \frac{v_{od}}{v_{id}} \right|_{v_{ic}=0}$$


$$A_{dc} = \left. \frac{v_{od}}{v_{ic}} \right|_{v_{id}=0}$$

Common-mode output

$$A_{cd} = \left. \frac{v_{oc}}{v_{id}} \right|_{v_{ic}=0}$$

$$A_{cc} = \left. \frac{v_{oc}}{v_{ic}} \right|_{v_{id}=0}$$

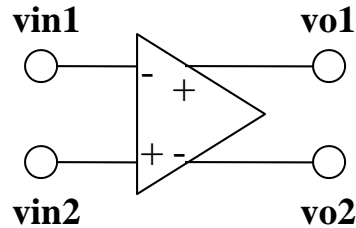Fully-Differential Filters: Effects of current source impedance and mismatches




A very important parameter:

$$CMRR = \frac{A_{dd}}{A_{dc}}$$

w/ $v_{id} = v_{i2} - v_{i1}$ and $v_{ic} = \frac{v_{i2} + v_{i1}}{2}$

Solving the circuit:

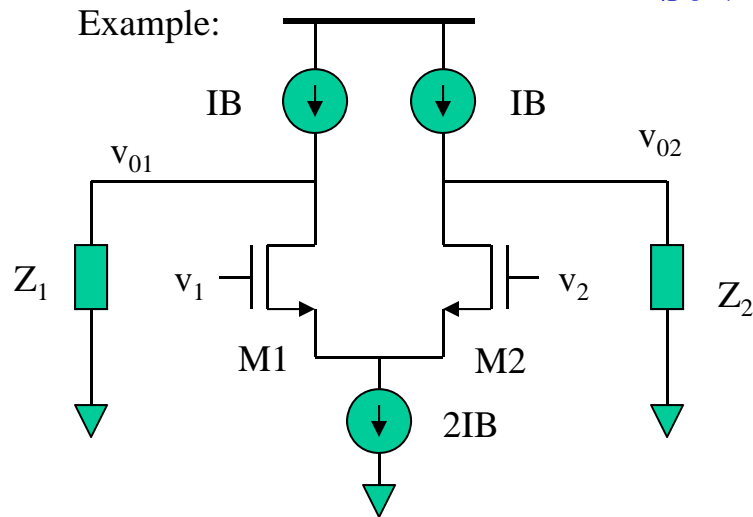


$$v_{01} = \frac{g_{m1}g_{m2}Z_1}{g_{m1} + g_{m2} + Y_s} \left[\left(1 + \frac{Y_s}{2g_{m2}} \right) v_{id} - \left(\frac{Y_s}{g_{m2}} \right) v_{ic} \right]$$

$$v_{02} = \frac{g_{m1}g_{m2}Z_2}{g_{m1} + g_{m2} + Y_s} \left[- \left(1 + \frac{Y_s}{2g_{m1}} \right) v_{id} - \left(\frac{Y_s}{g_{m1}} \right) v_{ic} \right]$$

Y_s is the admittance associated with the current source $2IB$

Fully-Differential Filters: Non-idealities

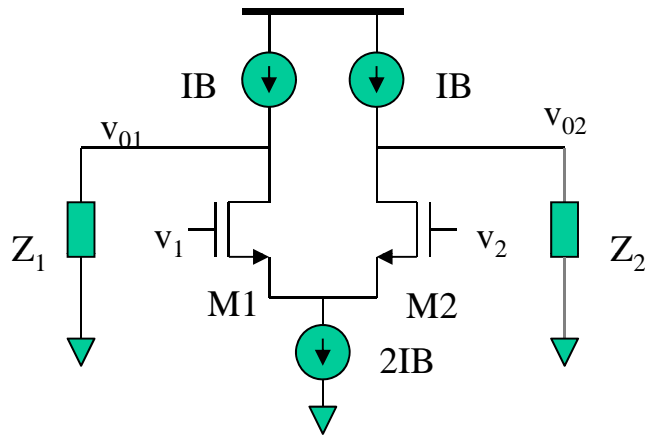Voltage gain: Note the effects of the mismatches, especially in A_{dc} and A_{cd}



$$CMRR = \frac{A_{dd}}{A_{dc}} \cong \frac{g_{m1} \left(1 + \frac{Z_1}{Z_2} \right)}{Y_s \left(1 - \frac{g_{m1} Z_1}{g_{m2} Z_2} \right)}$$


$$A_{dd} = \left. \frac{v_{o1} - v_{o2}}{v_{i2} - v_{i1}} \right|_{v_{ic}=0} = \frac{g_{m1} g_{m2}}{g_{m1} + g_{m2} + Y_s} \left[Z_1 + Z_2 + \frac{Y_s}{2} \left(\frac{Z_1}{g_{m2}} + \frac{Z_2}{g_{m1}} \right) \right]$$

$$A_{dc} = \left. \frac{v_{o1} - v_{o2}}{(v_{i2} + v_{i1})/2} \right|_{v_{id}=0} = \frac{g_{m1} g_{m2}}{g_{m1} + g_{m2} + Y_s} \left[Y_s \left(\frac{Z_2}{g_{m1}} - \frac{Z_1}{g_{m2}} \right) \right]$$

$$A_{cd} = \left. \frac{(v_{o2} + v_{o1})/2}{v_{i2} - v_{i1}} \right|_{v_{ic}=0} = \frac{g_{m1} g_{m2}}{g_{m1} + g_{m2} + Y_s} \left(\frac{1}{2} \right) \left[Z_1 - Z_2 + \frac{Y_s}{2} \left(\frac{Z_1}{g_{m2}} - \frac{Z_2}{g_{m1}} \right) \right]$$

$$A_{cc} = \left. \frac{(v_{o2} + v_{o1})/2}{(v_{i2} + v_{i1})/2} \right|_{v_{id}=0} = -\frac{g_{m1} g_{m2}}{g_{m1} + g_{m2} + Y_s} \left(\frac{1}{2} \right) \left[Y_s \left(\frac{Z_2}{g_{m1}} + \frac{Z_1}{g_{m2}} \right) \right]$$

Fully-Differential Circuits

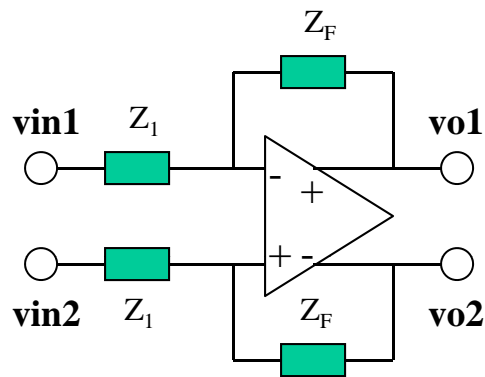

➤ **Ideal voltage gain**


$$A_{dd} = \frac{v_{o1} - v_{o2}}{v_{in2} - v_{in1}} = \frac{Z_f}{Z_1}$$

➤ **Ideally even-order distortions are cancelled**

➤ **Ideally common-mode signals are rejected**

➤ **What sets the output common-mode of these circuits?**

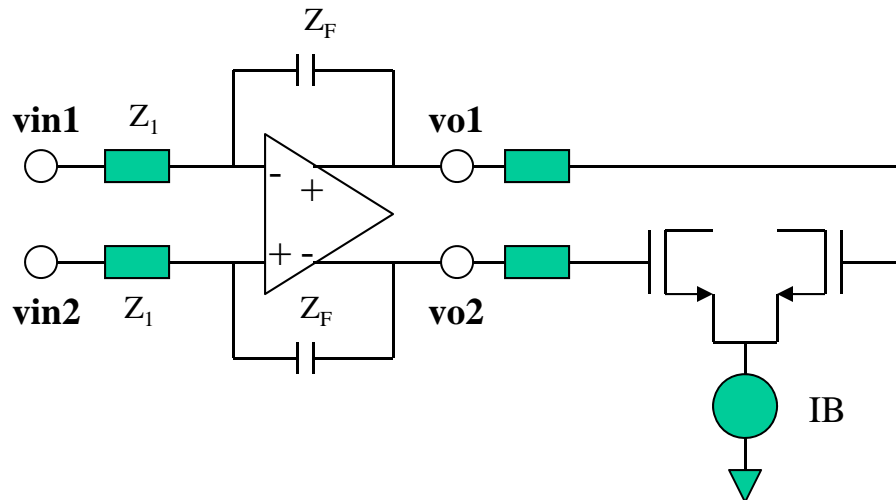
➤ **Function of the amplifier output resistance**



Common-mode offsets can impact the performance of the following stages

- **Can exceed the common-mode input range of preceding stages**
- **With finite A_{cc} can accumulate in a multi-stage amplifier circuit**

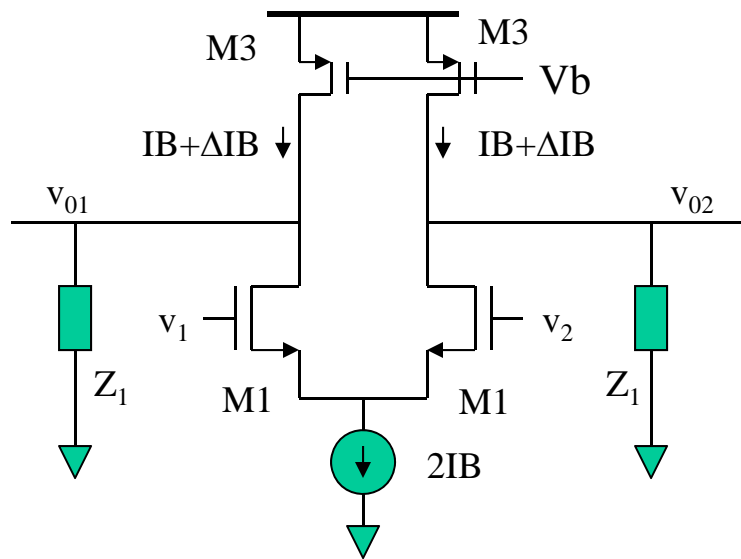Fully-Differential Amplifiers: COMMON-MODE DC offset



✓ If ΔI_B is positive transistors M3 eventually will be biased in triode region (small resistance)

✓ dc gain reduces drastically

✓ Linear range is further minimized


✓ THD increases

✓ The common-mode output impedance is the parallel of the equivalent output resistance (M1 and M3) and the parasitic capacitors.

✓ For large dc gain, the output impedance at nodes v_{01} and v_{02} are further increased and ΔI_B produces a dc offset = $R_{out}\Delta I_B$.
Large common-mode offsets!

✓ How this issue can be fixed?

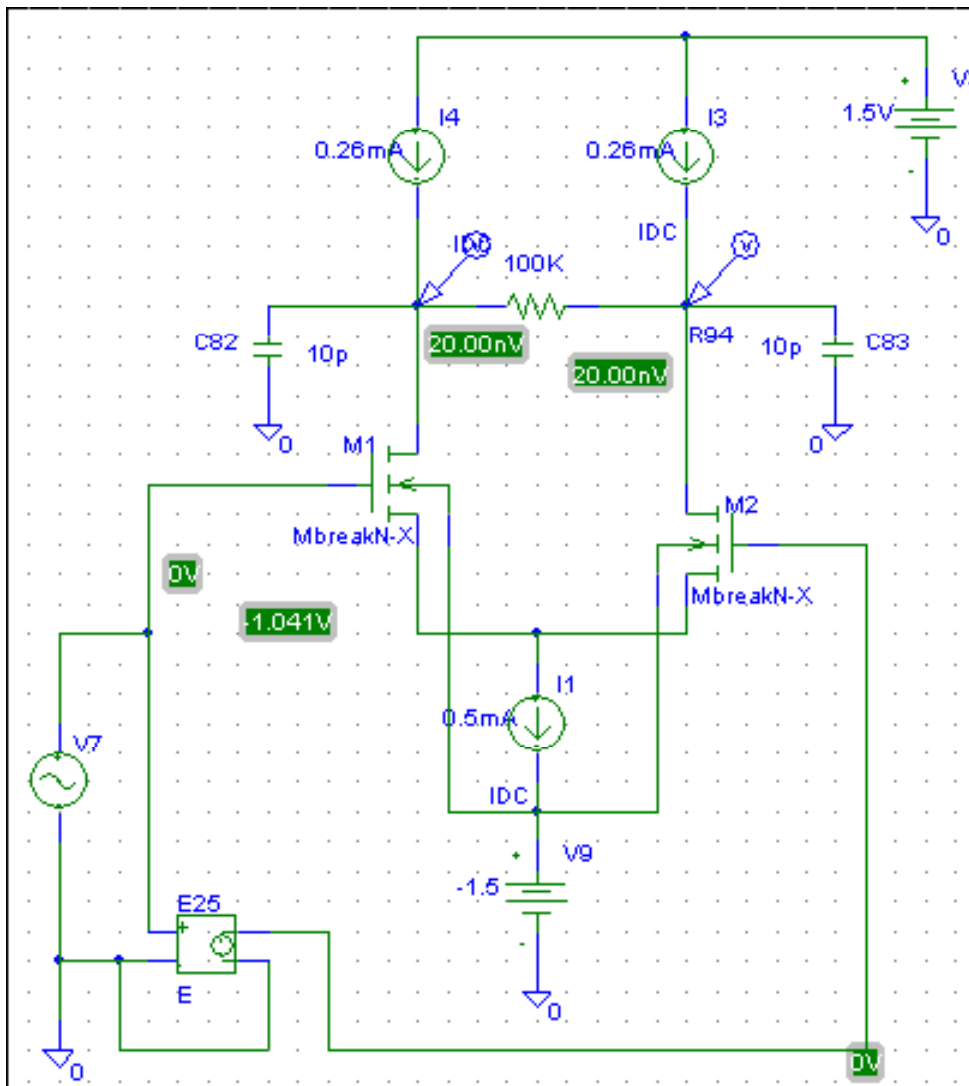Fully-Differential Amplifiers: Characterization





✓ Common-mode current offset of 0.01 mA per side is added on purpose

Tail current is 0.5 mA while the current sources on top are 0.26 mA!

✓ Differential input voltage is set at 0

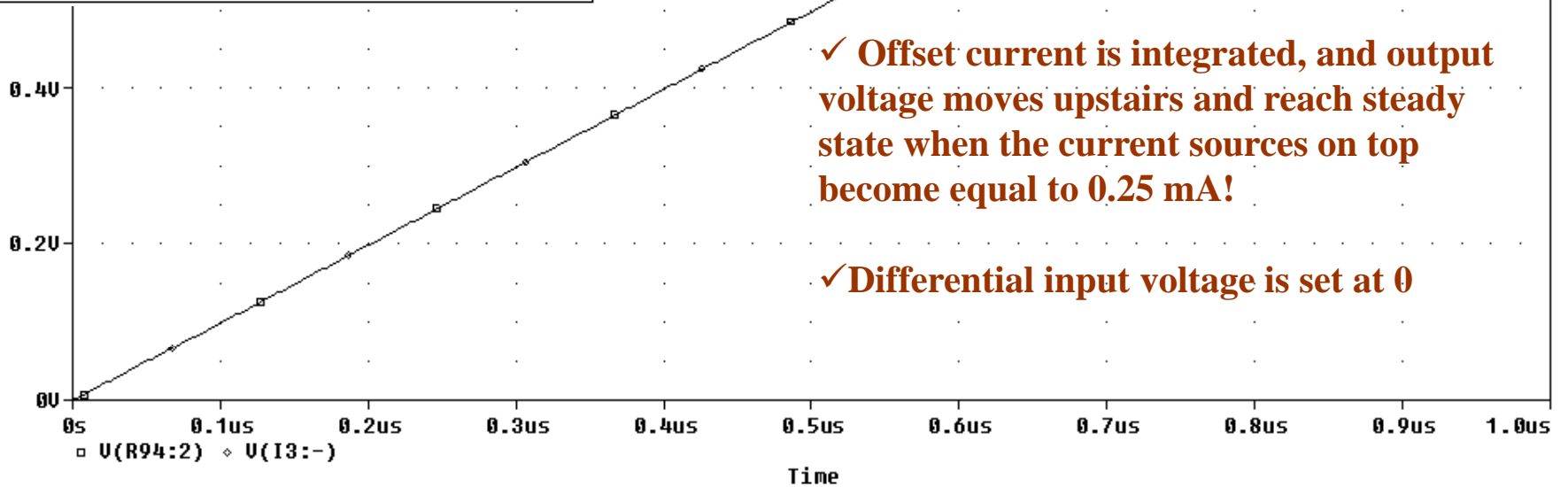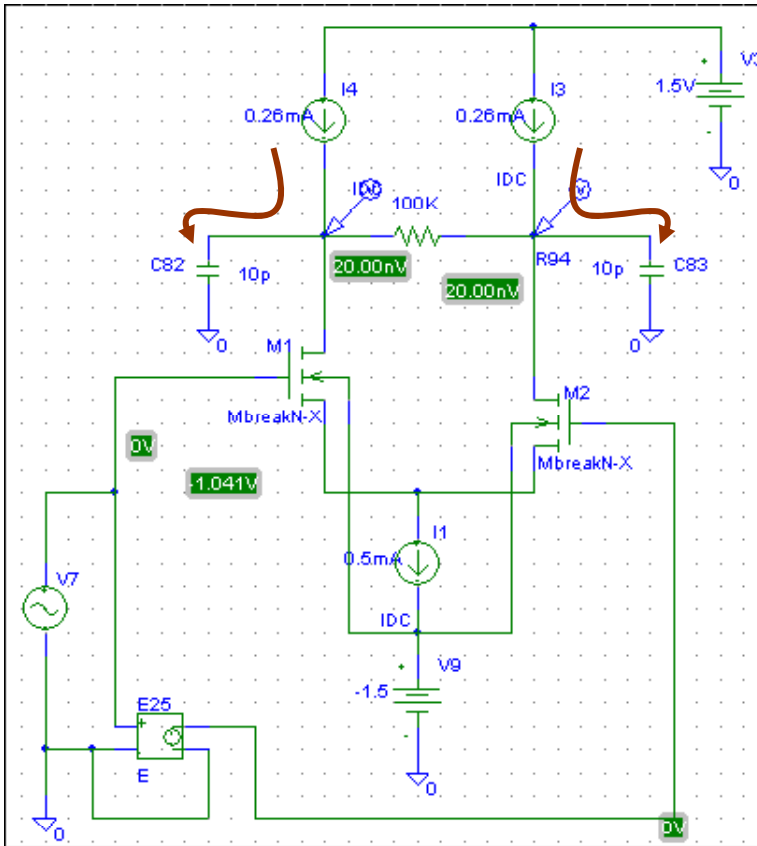
Differential Amplifiers: Characterization



✓ Offset current is integrated, and output voltage moves upstairs and reach steady state when the current sources on top become equal to 0.25 mA!

✓ Differential input voltage is set at 0

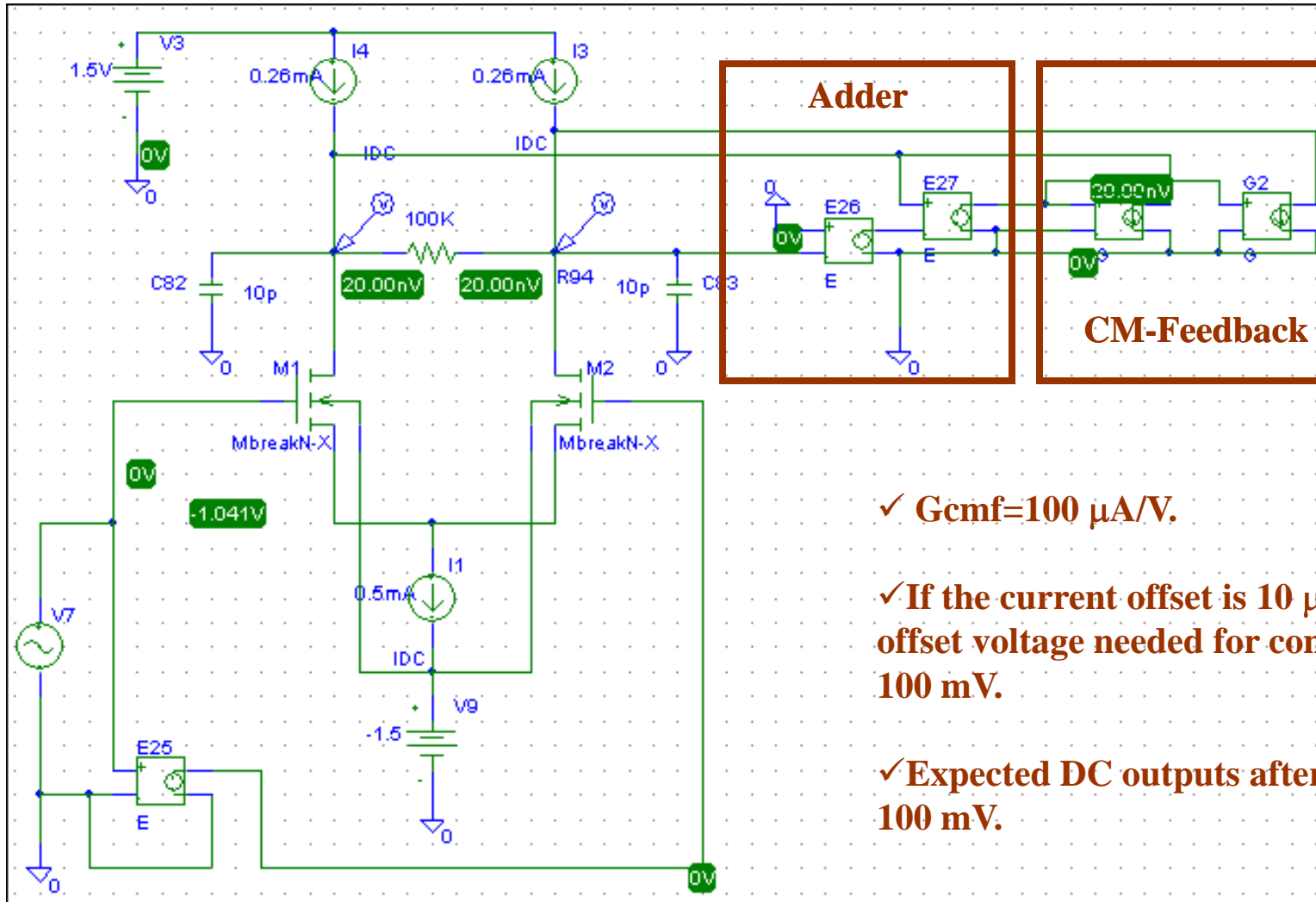Fully-Differential Amplifiers: Common-mode Feedback




✓ $G_{cmf} = 100 \mu A/V$.

✓ If the current offset is $10 \mu A$, then the offset voltage needed for compensation is 100 mV.

✓ Expected DC outputs after settling are 100 mV.

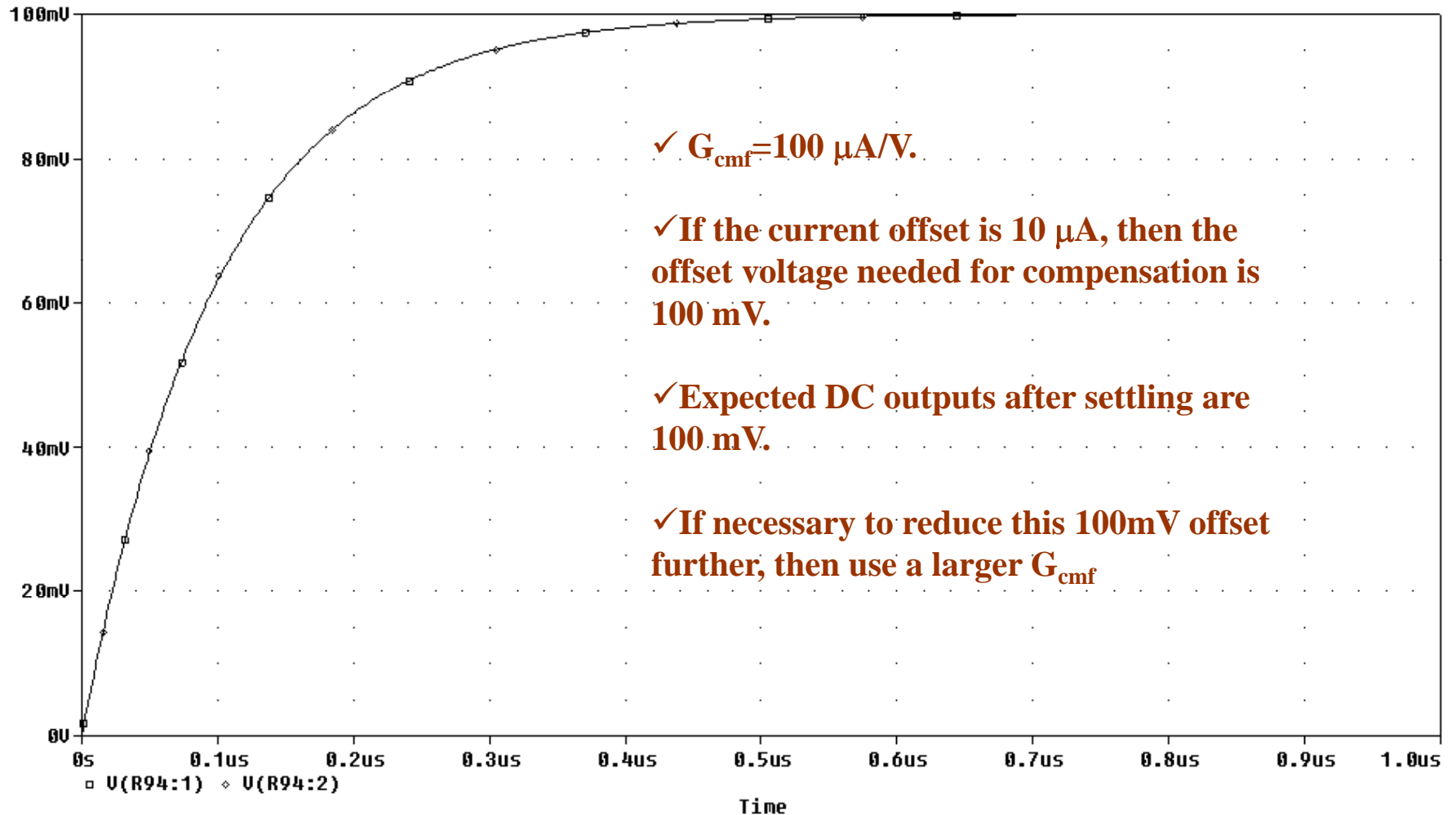Fully-Differential Amplifiers: Common-mode Feedback




A photograph of a multi-pin connector, possibly a ribbon cable connector, with a white label overlaid on it. The label contains text about common-mode feedback circuits. The background shows the metal pins and the green printed circuit board (PCB) of the connector.


What is a common-mode feed-back correction circuit ?

A common mode **feed-back** circuit is a circuit sensing the common-mode voltage, comparing it with a proper reference, and feeding back the correcting common-mode signal (both nodes of the fully-differential circuit) with the purpose to cancel the output common-mode current component, and to fix the dc outputs to the desired level.

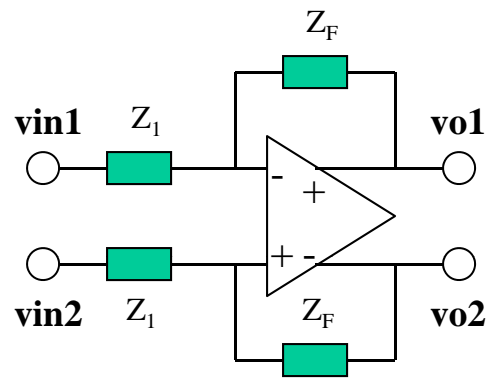Fully-Differential Filters: CMFB Principle



Simplest common-mode detector

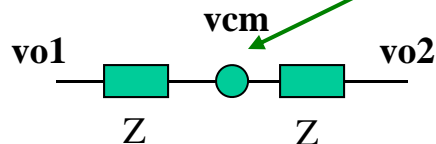

$$v_{cm} = \frac{v_{o1} + v_{o2}}{2}$$

➤ A common-mode feedback loop must be used: Circuit must operate on the common-mode signals only!

➤ BASIC IDEA: CMFB is a circuit with very small impedance for the common-mode signals but transparent for the differential signals.

➤ Use a common-mode detector (eliminates the effect of differential signals and detect common-mode signals)

➤ Analyze the common-mode feedback loop: Large transconductance gain and enough phase margin

➤ Minimum power consumption

Next Time

- Common-Mode Feedback Techniques