

# ECEN474: (Analog) VLSI Circuit Design

## Fall 2011

---

### Lecture 24: Variable Gain Amplifiers (VGAs)



Sebastian Hoyos  
Analog & Mixed-Signal Center  
Texas A&M University


# Agenda

---

- Variable Gain Amplifiers
- Material is related primarily to Project #4
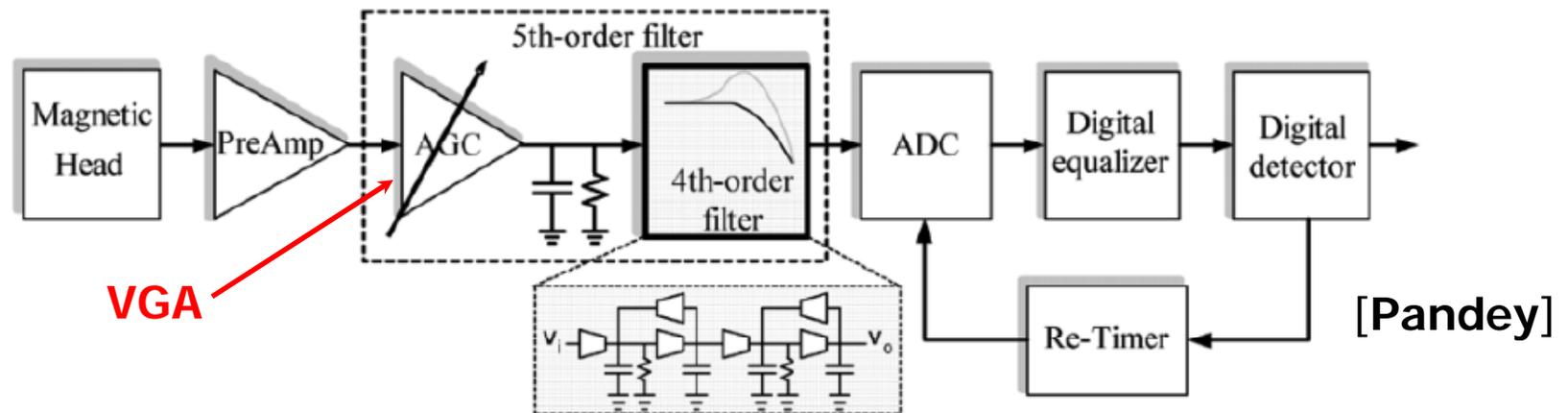
# Variable Gain Amplifier (VGA) Applications

- Variable gain amplifiers (VGAs) are employed in many applications in order to maximize the overall system dynamic range
- Critical component of automatic-gain control (AGC) systems




Hard-Disk Drive Receiver Front-End

# Typical VGA Design Goals


- Constant bandwidth across wide gain range
- Exponential gain control ("linear in dB") preferred in many applications
- Low noise, low distortion, low power

[Gilbert]

Poor Performance

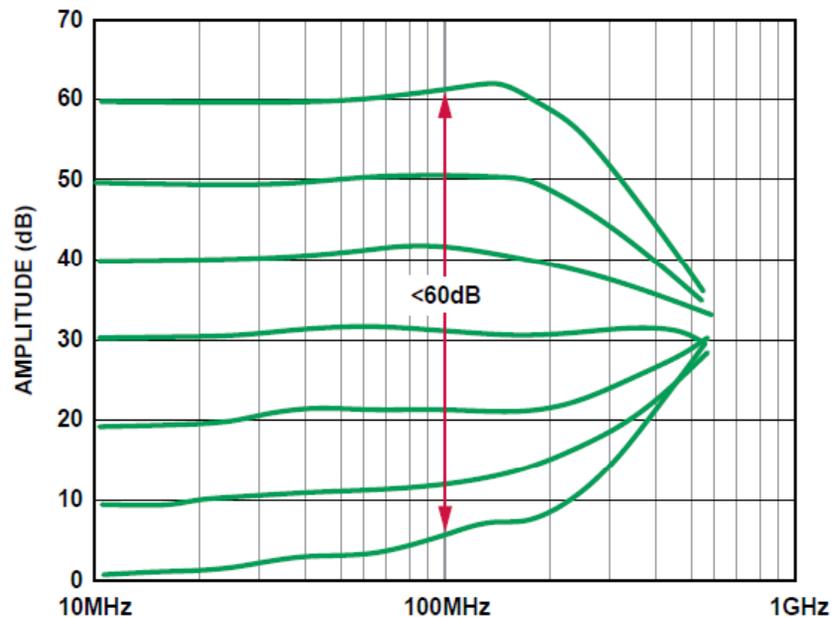

Desired Performance

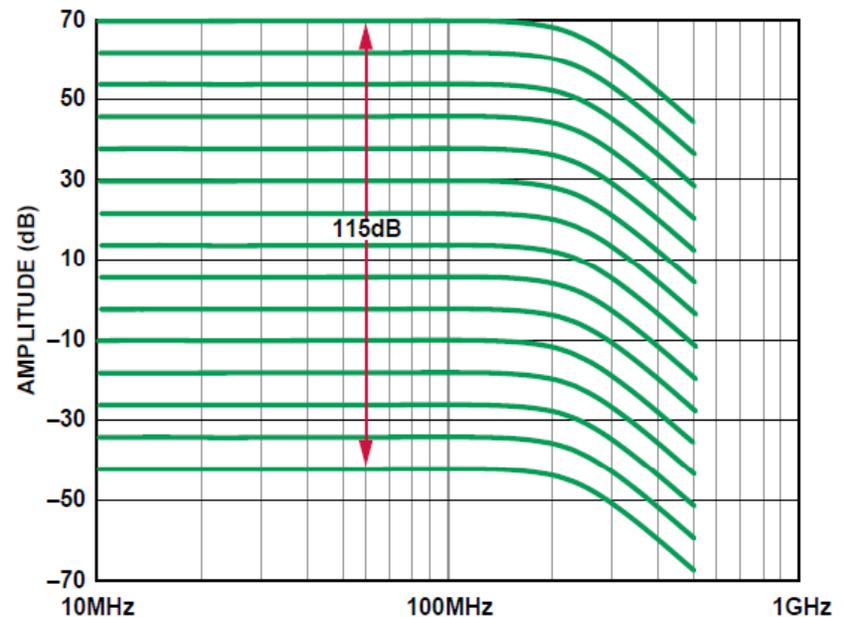

# VGA Techniques


---

- Multipliers
- Transconductance ratio amplifiers
- Source degeneration




# 4-Quadrant Multiplier

[Razavi]

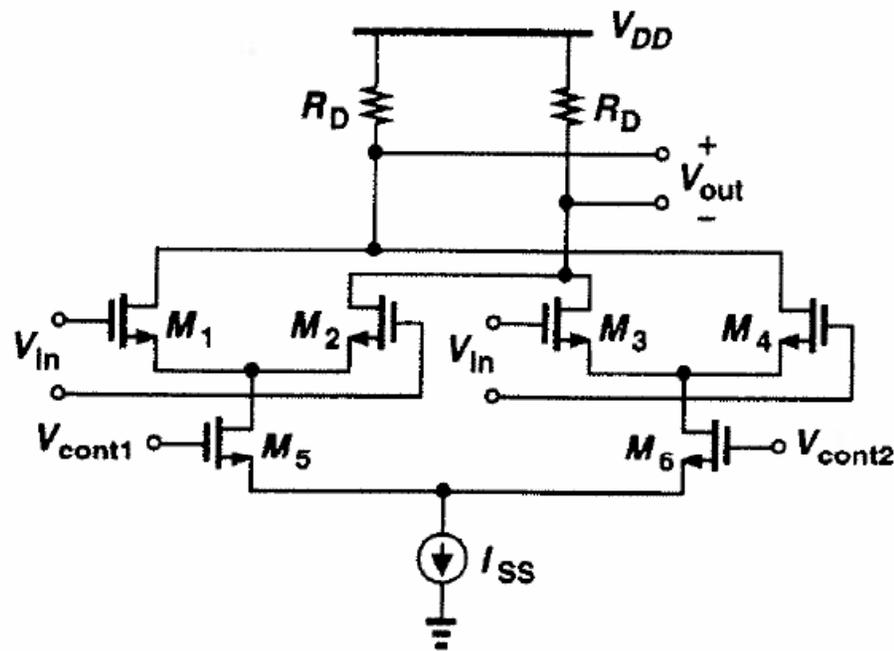

- Allows multiplication in all 4-quadrants
- Differential  $V_{cont}$  allows the sign of the gain to be inverted
- Can also use for VGAs, although 4-quadrant operation is not necessary
- Often used in RF transceivers as a frequency translator (mixer)
- Also called the "Gilbert Cell", after Barrie Gilbert who is the inventor of the bipolar version

# Transconductance Ratio VGA #1

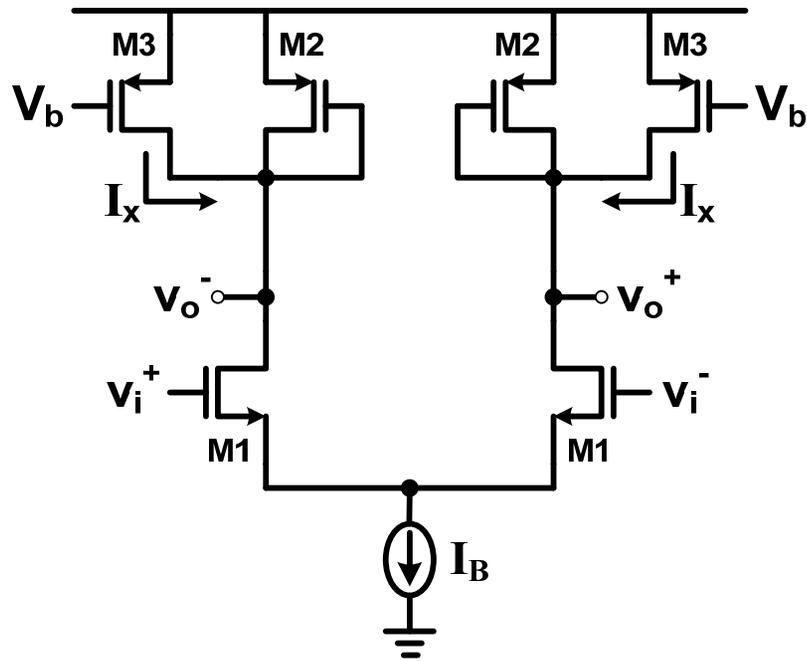

$$A_v \approx \frac{g_{m1}}{g_{m2}}$$


- Diode-load transconductance ( $g_{m2}$ ) can be altered by stealing current with a parallel current source M3, thus altering the gain
- Issues
  - Gain is a ratio of nmos and pmos transconductance, which can be sensitive to process variations
  - Bandwidth changes with gain

# Transconductance Ratio VGA #2

TP 5.1: A 2mA/3V 71MHz IF Amplifier in 0.4 $\mu$ m CMOS  
Programmable over 80dB Range


ISSCC 1997

Francesco Piazza, Paolo Orsatti, Qiuting Huang, Hiroyuki Miyakawa<sup>1</sup>

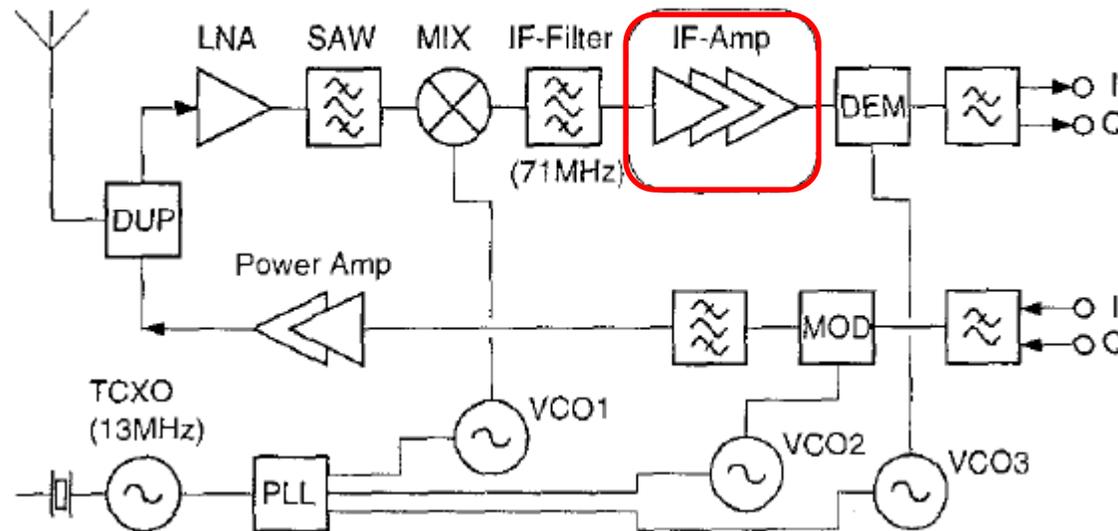



**Figure 1: Block diagram of the GSM handset.**

# Transconductance Ratio VGA #2

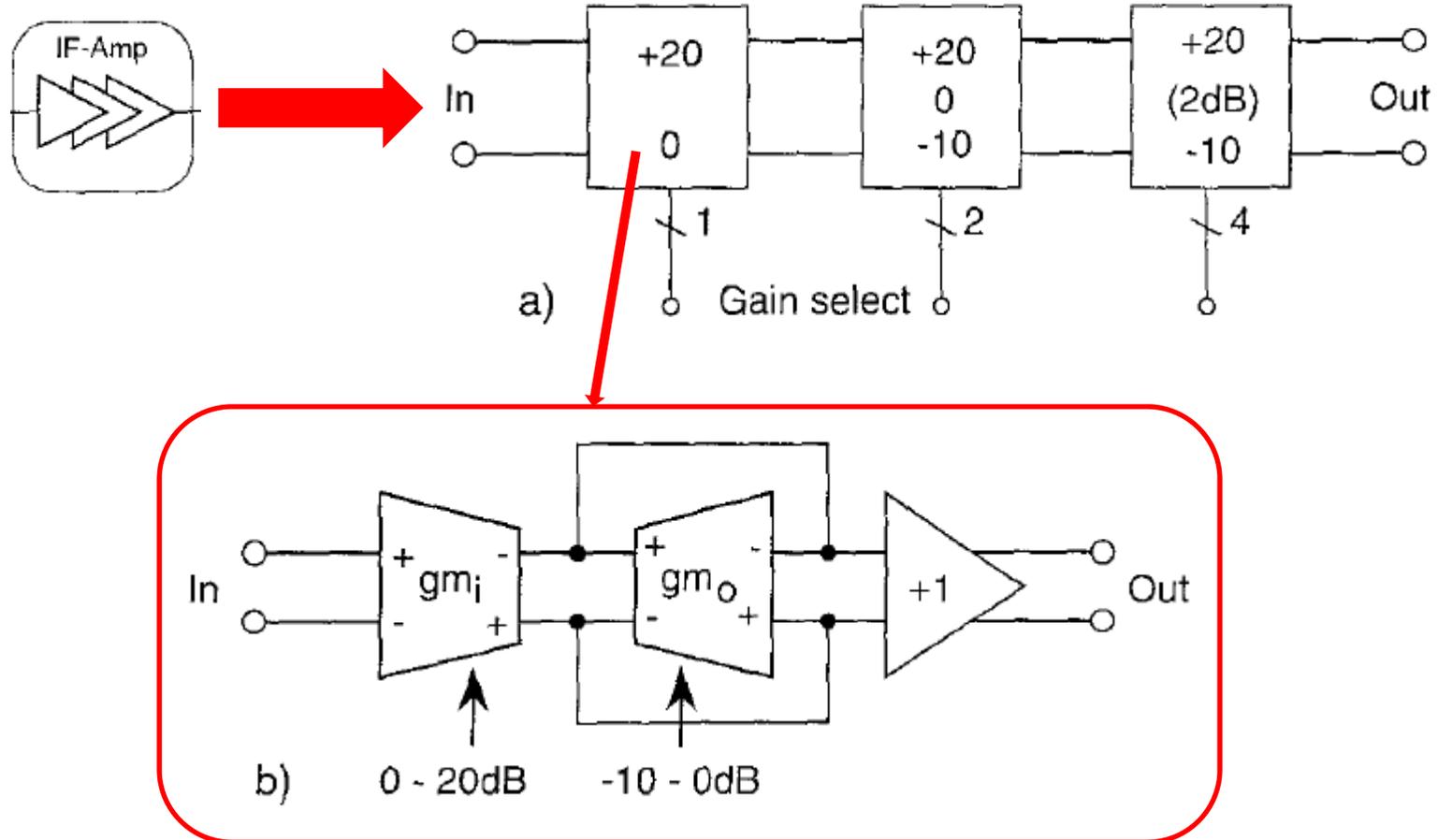

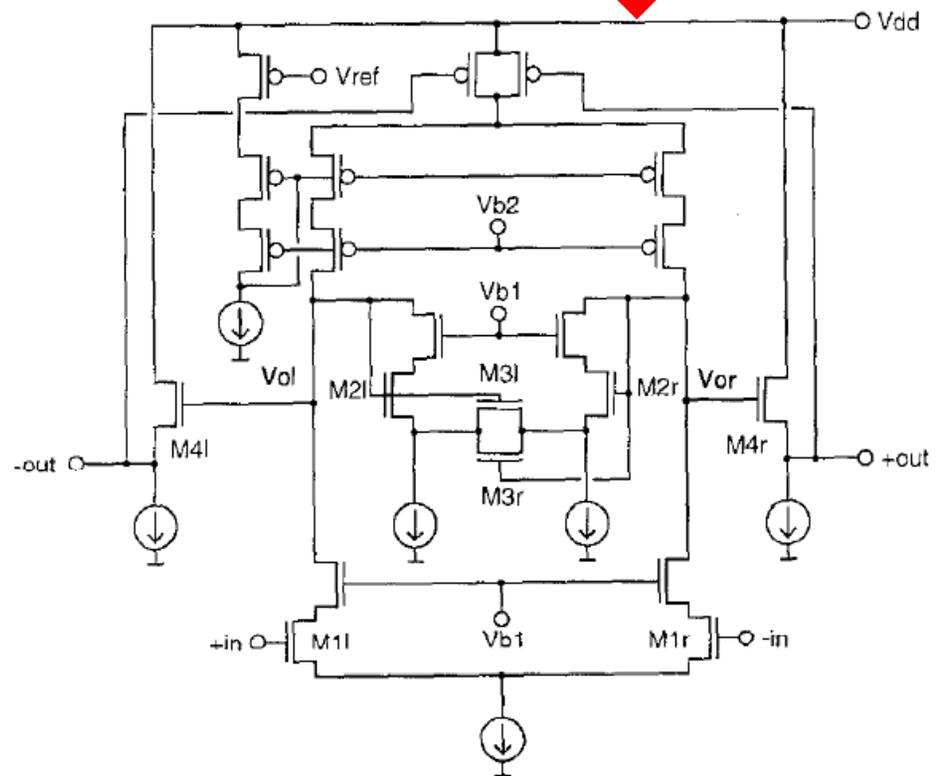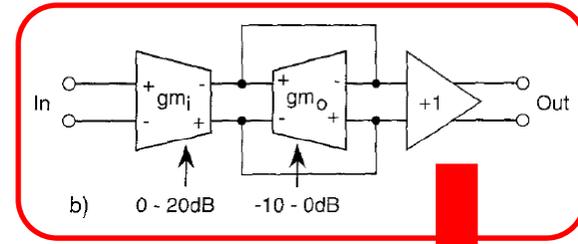
# Transconductance Ratio VGA #2

- $g_{mi}$  is from M1
- $g_{mo}$  is from M2
- M4 source-follower output buffers
- Both the  $g_{mi}$  and  $g_{mo}$  transistors are segmented into multiple parallel transistors
- Gain is controlled by switching off bias current to these segments



# Transconductance Ratio VGA #2

---

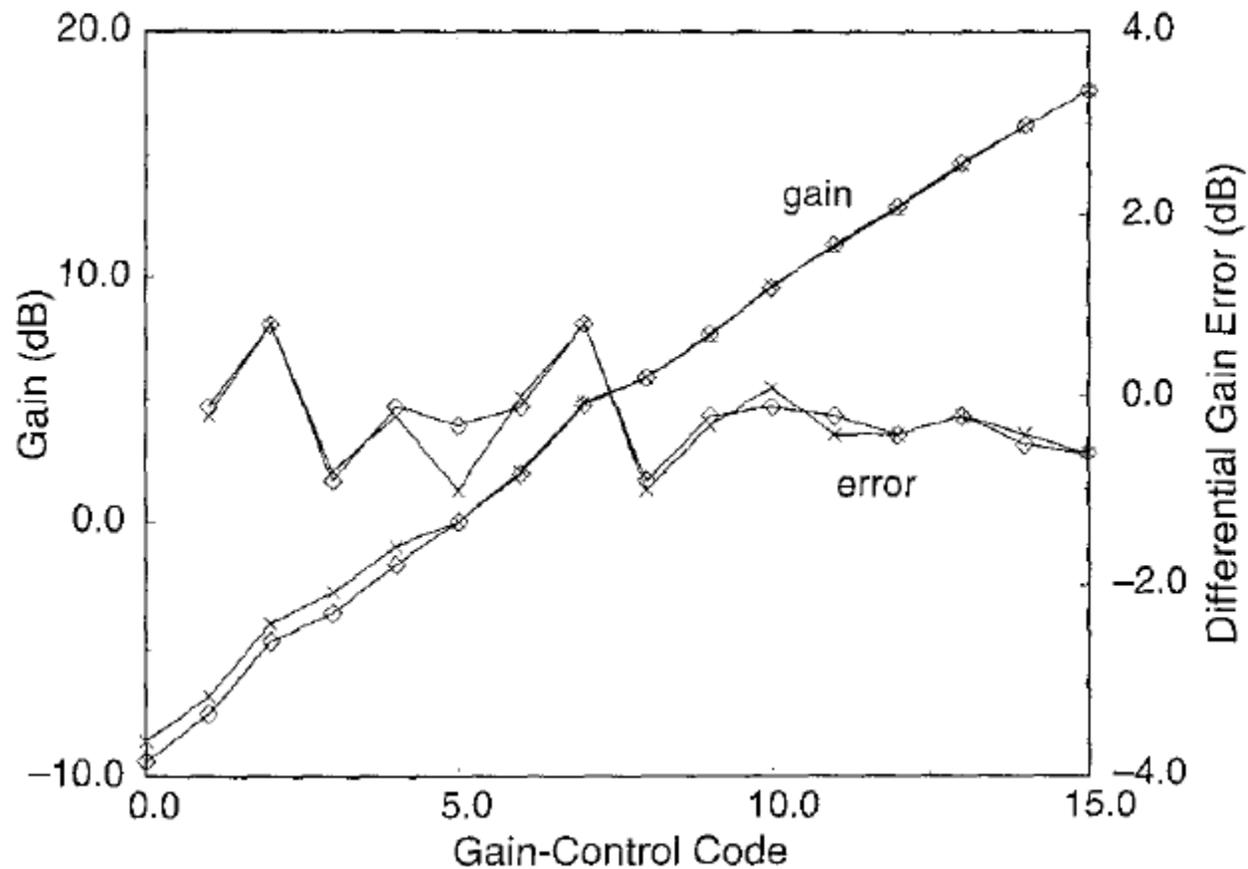


**Figure 4: Amplifier gain and gain error.**

# Source Degeneration VGA

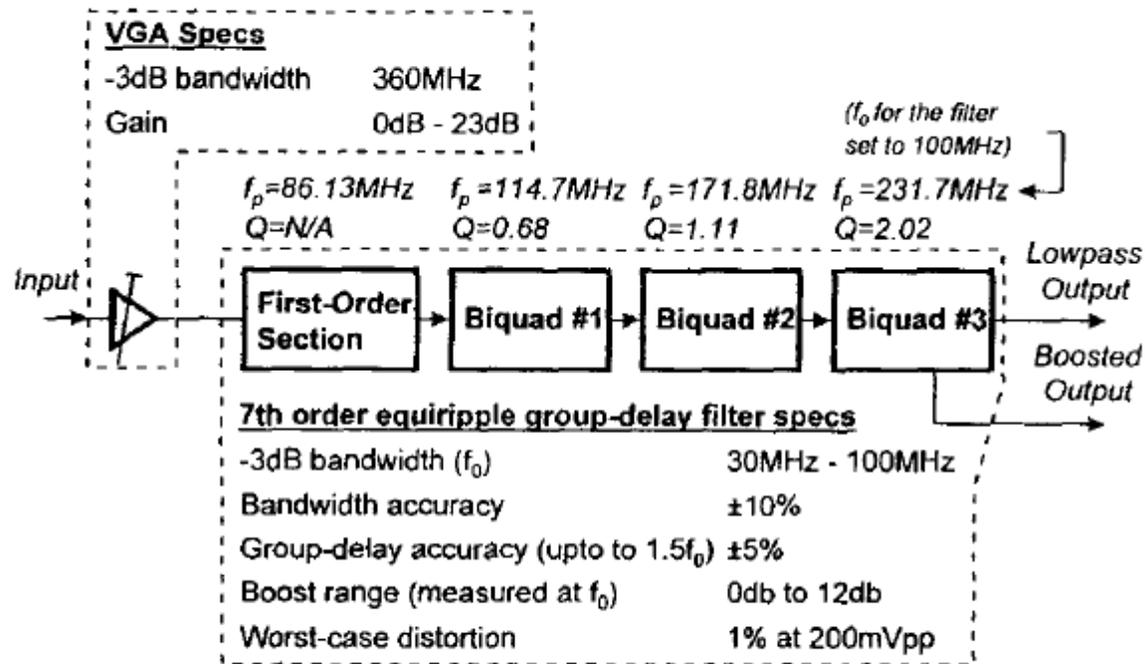**WA 23.2 A 2.5V, 30MHz-100MHz, 7th-Order, Equiripple Group-Delay Continuous-Time Filter and Variable-Gain Amplifier Implemented in 0.25 $\mu$ m CMOS**

ISSCC 1999

Venu Gopinathan<sup>1</sup>, Maurice Tarsia<sup>1</sup>, Davy Choi



# Source Degeneration VGA

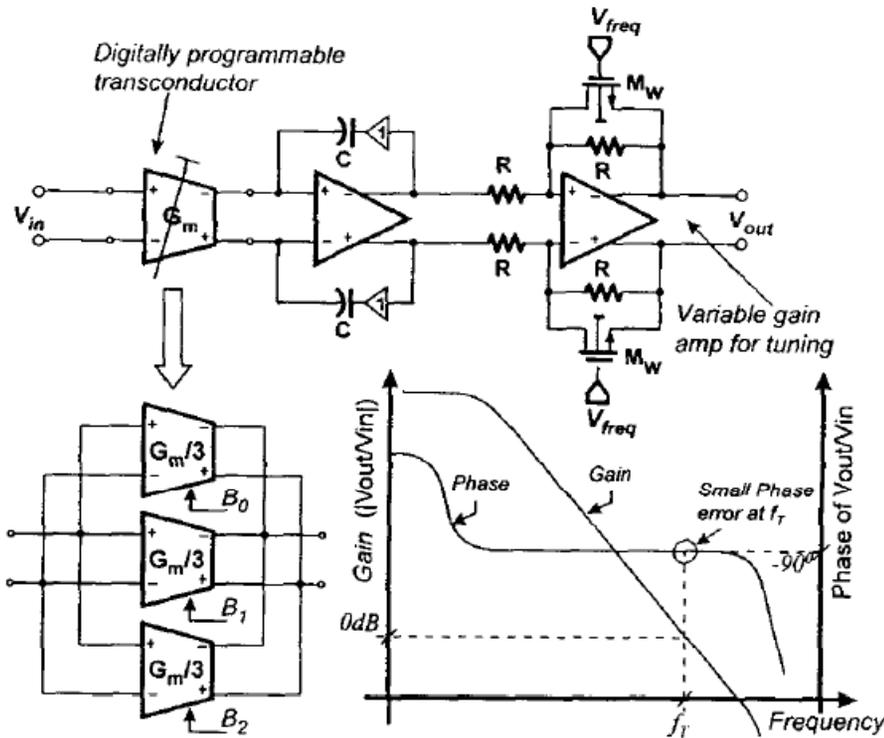


Figure 23.2.2: Programmable integrator.

Gm-OpAmp-C Integrator

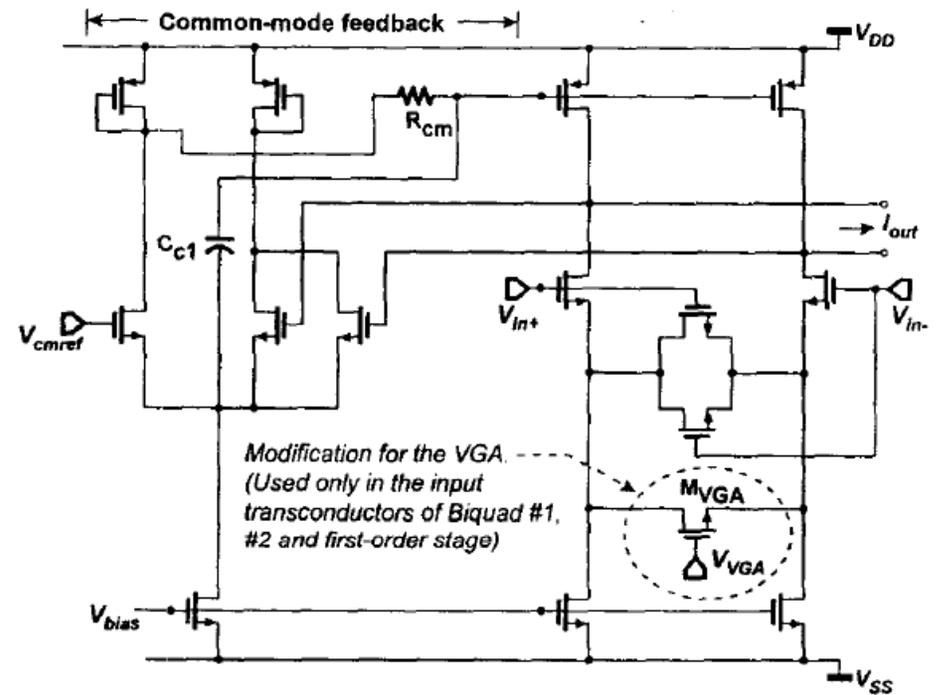


Figure 23.2.3: Complete transconductor.

# Source Degeneration VGA

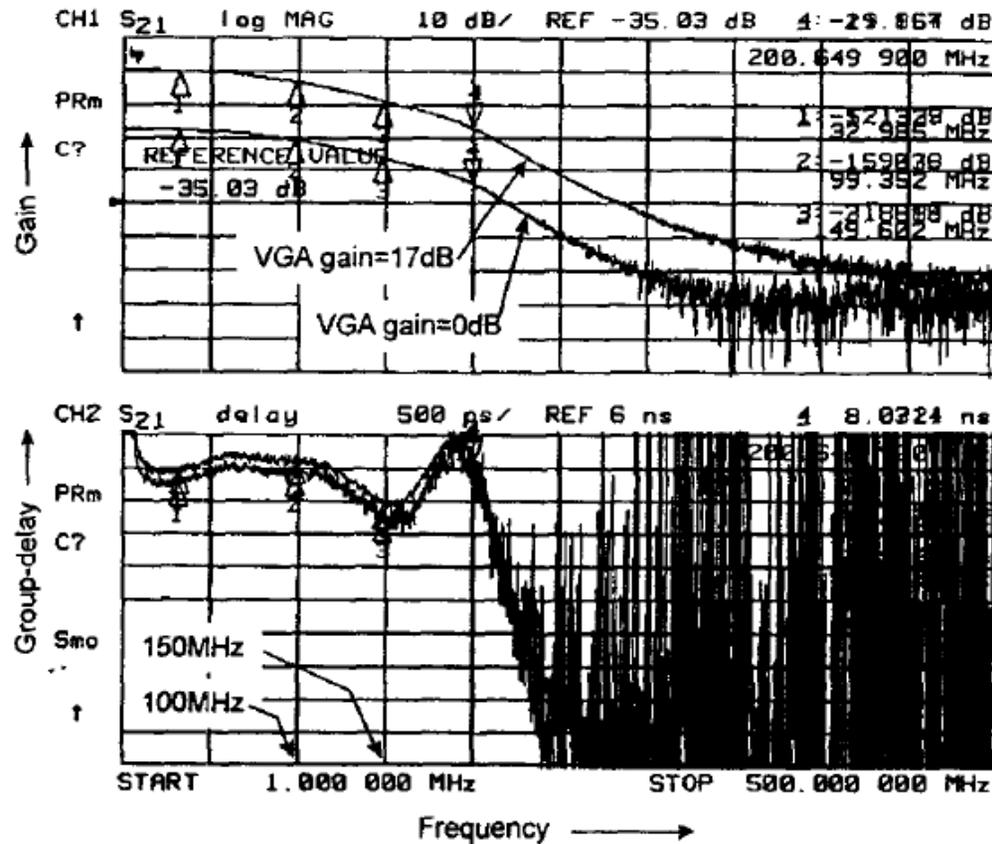


Figure 23.2.5: VGA operation.

- Bandwidth and group delay display consistent performance over gain range


# Digitally Controlled VGA




Analog Integrated Circuits and Signal Processing, 38, 149–160, 2004  
© 2004 Kluwer Academic Publishers. Manufactured in The Netherlands.

**A 270 MHz, 1 V<sub>pk-pk</sub>, Low-Distortion Variable Gain Amplifier  
in a 0.35 μm CMOS Process**

SIANG TONG TAN\* AND JOSÉ SILVA-MARTÍNEZ

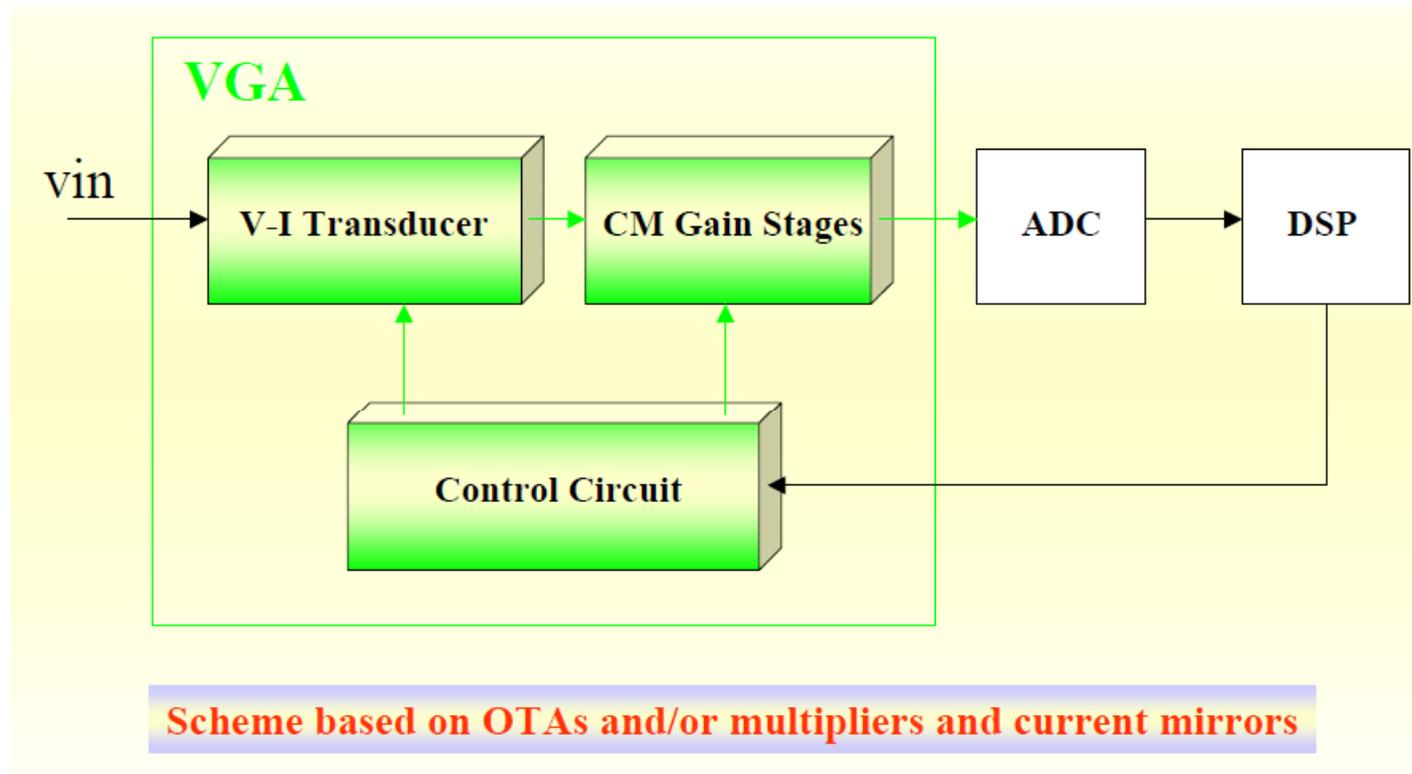

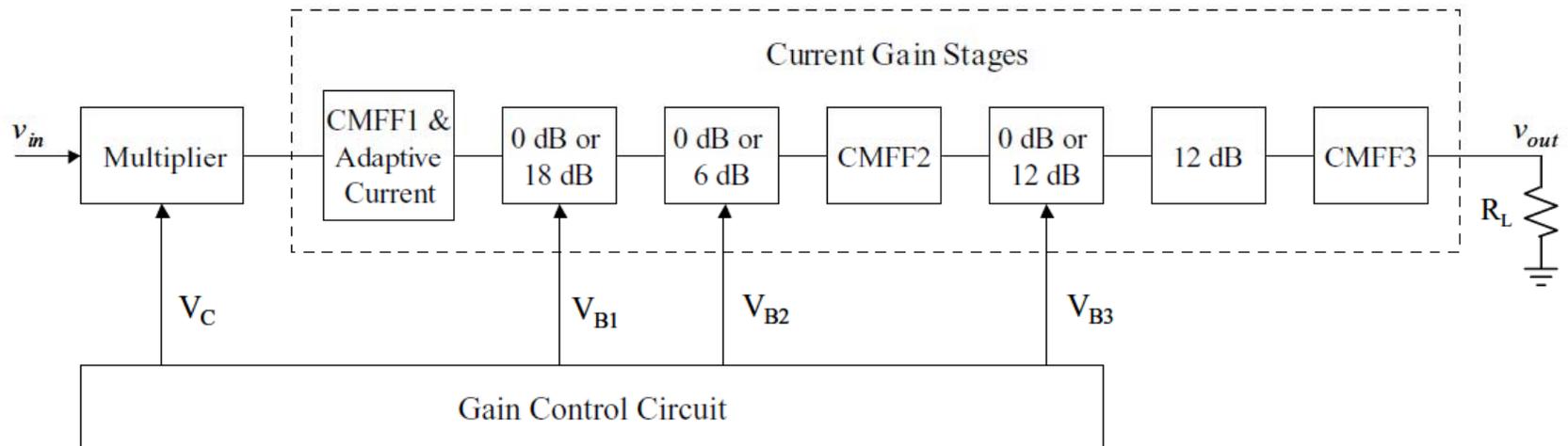
# VGA Based on Analog Multiplier & Current Mirror Amplifiers


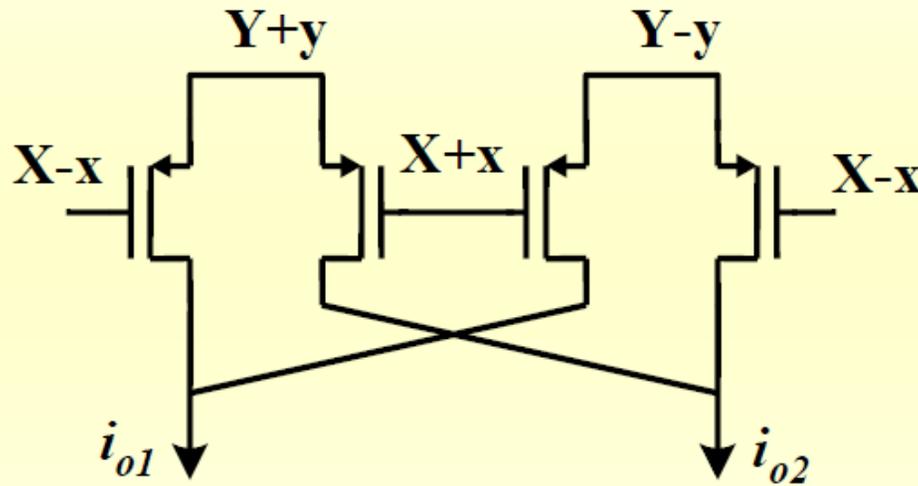
# Analog Multiplier

Transistors operate in saturation region: Linearized



$$i_{out} = 4\mu C_{ox} \frac{W}{L} v_y v_x$$


## Advantages:

- ⇒ Very fast
- ⇒ Relative good linearity
- ⇒ Easy to program

## Drawbacks:

- Requires low impedance Y drivers
- Large swing requires large X and Y
- Mobility degradation effects
- Poor accuracy (calibration is required)
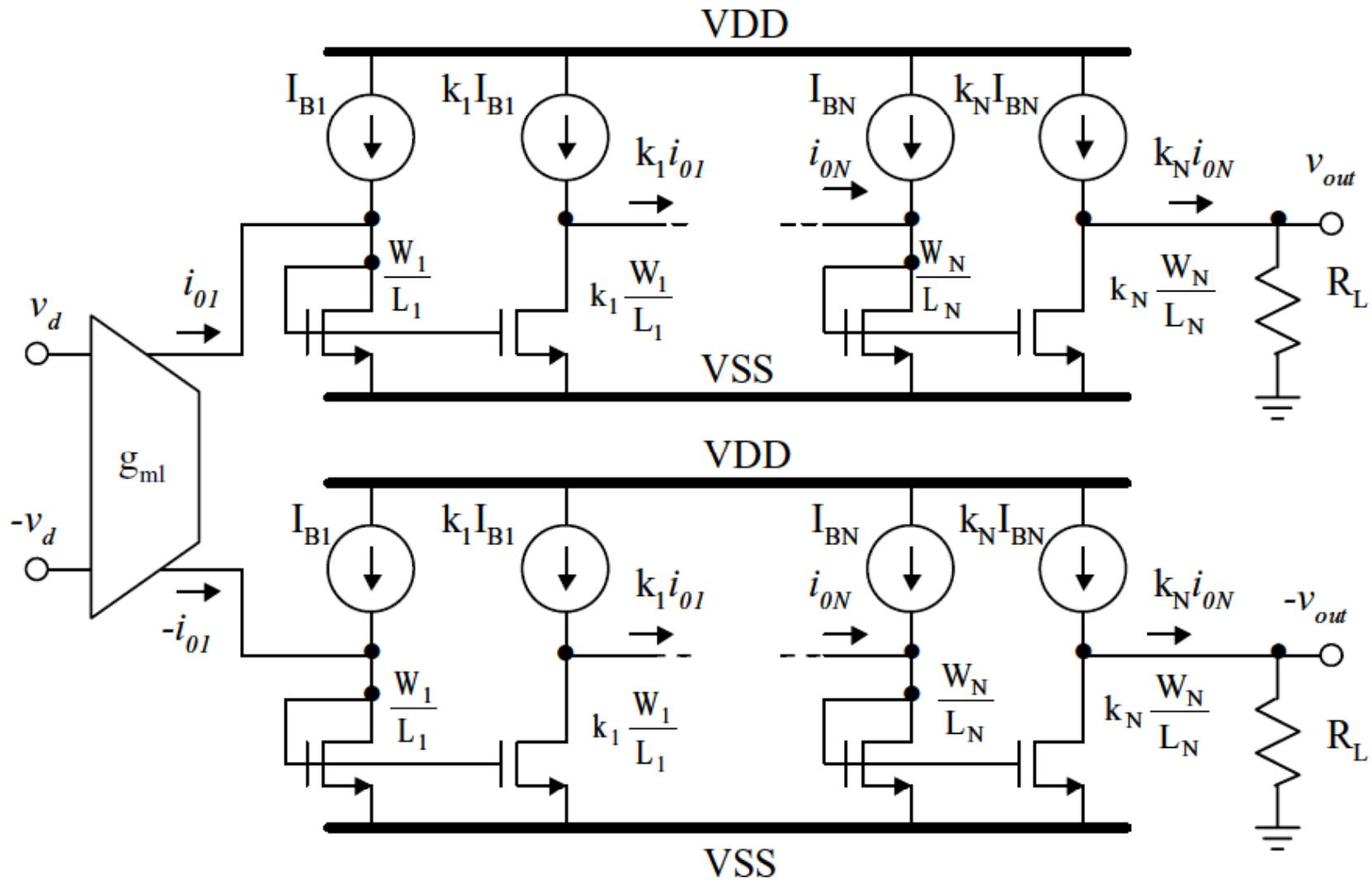
# VGA Based on Analog Multiplier & Current Mirror Amplifiers




# Low-Voltage Cascode Current Mirrors

---

## Cascode Current Mirrors are used

- High bandwidth
- High output impedance and low input impedance
- More accurate, because  $V_{ds}$  are always fixed
- Low voltage headroom
- 2nd order loop, bandwidth can be improved
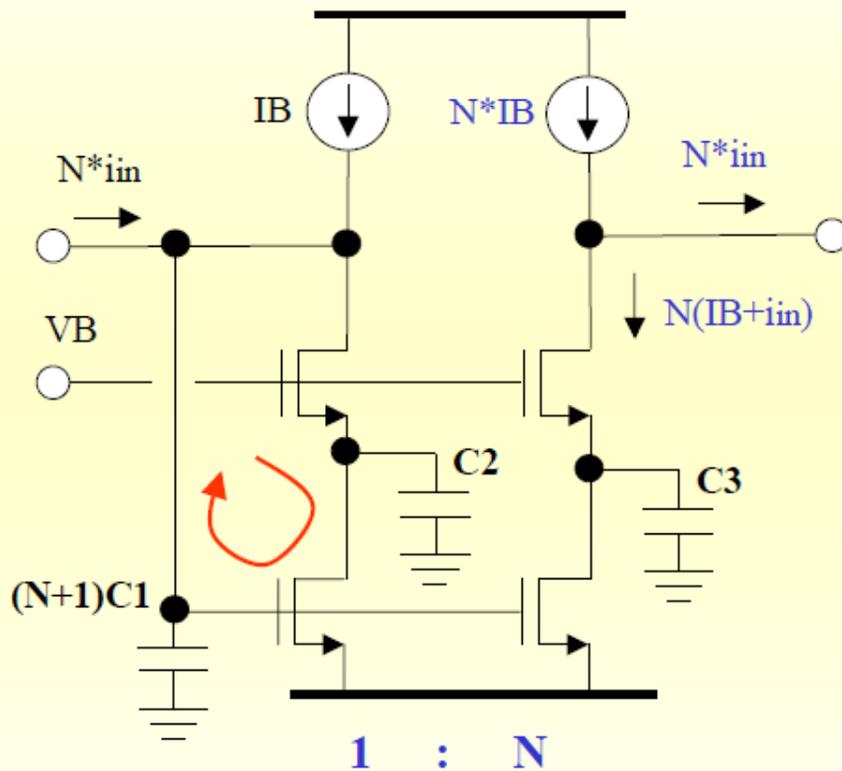
# Basic Current Amplifier Frequency Response



$C_1 \sim C_{GS1}$

$$\frac{i_{out}}{i_{in}} \cong \frac{N g_{m1} g_{m2}}{(N+1) C_1 C_2} \frac{1}{s^2 + \frac{g_{m2}}{C_2} s + \frac{g_{m1} g_{m2}}{(N+1) C_1 C_2}}$$

$$\omega_0 = \sqrt{\frac{g_{m1} g_{m2}}{(N+1) C_1 C_2}}$$


$$Q = \sqrt{\frac{g_{m1}}{g_{m2}}} \sqrt{\frac{C_2}{(N+1) C_1}}$$

**Peaking?**


**Best bandwidth for  $N \sim 2 - 3$**

**$C_3$  introduces an additional pole**

# Frequency Compensation Scheme

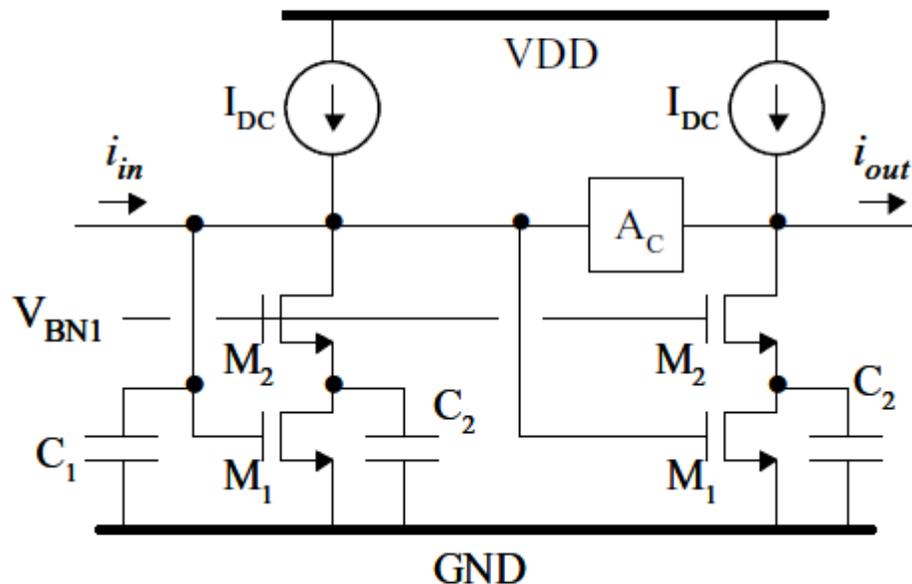

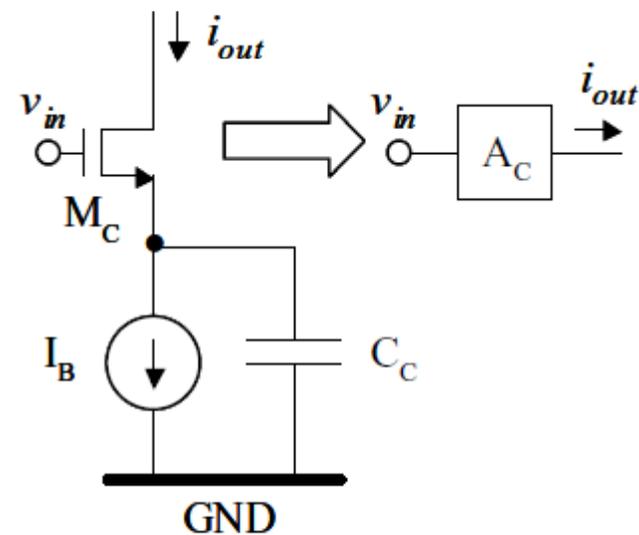- Parallel transconductance transistor  $M_C$  with capacitive degeneration introduces a zero which provides frequency compensation



# Measurement Results

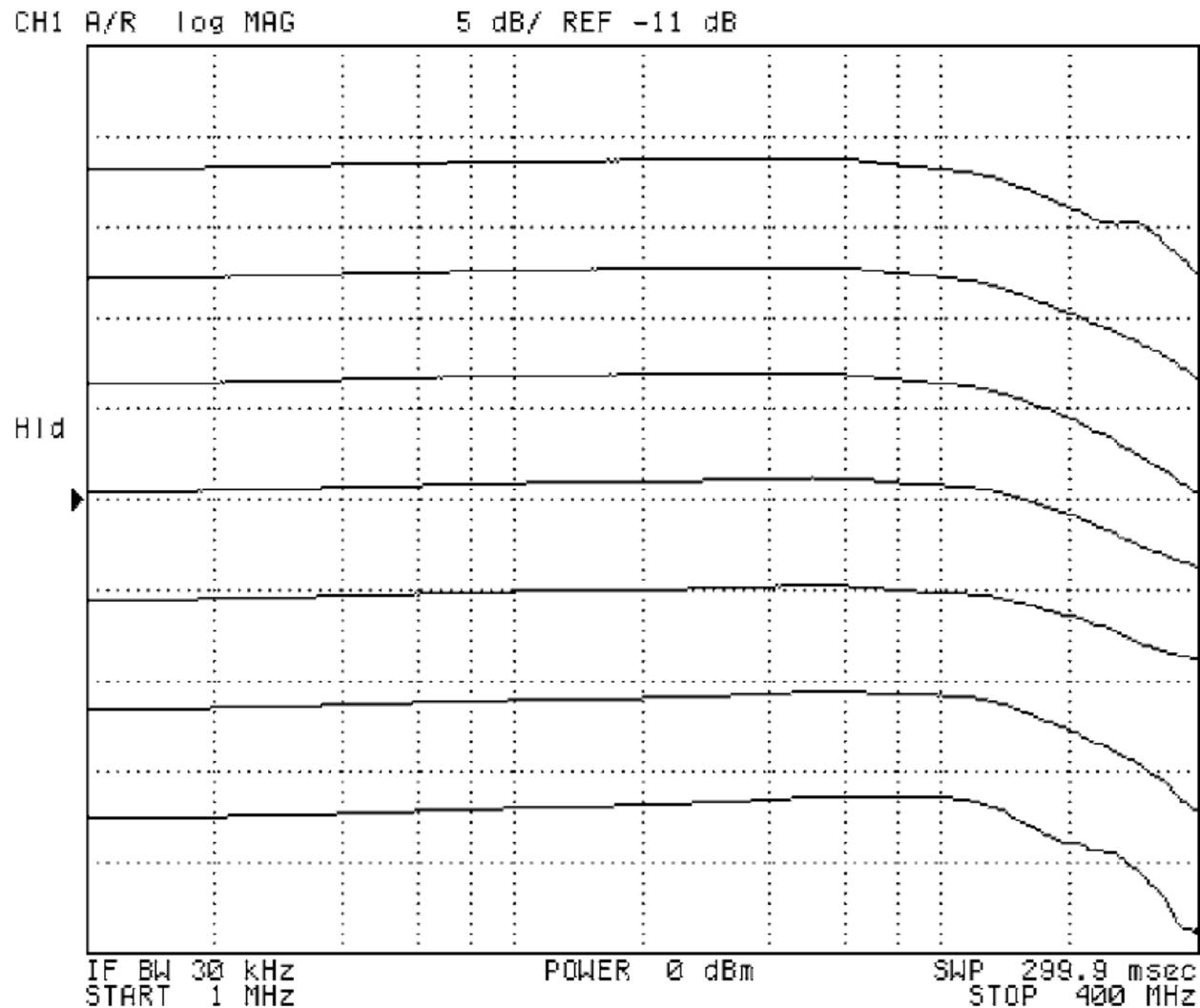


Fig. 10. Experimental frequency response of the VGA for several gain settings.

# Next Time

---

- Analog Applications
  - Switch-Cap Filters, Broadband Amplifiers
- Bandgap Reference Circuits
- Distortion