

Lecture 5: The ideal operational amplifier


- **The ideal operational amplifier**
 - Terminals
 - Basic ideal op-amp properties
- **Op-amp families**
- **Operational amplifier circuits**
 - Comparator and buffer
 - Inverting and non-inverting amplifier
 - Summing and differential amplifier
 - Integrating and differentiating amplifier
 - Current-voltage conversion



The ideal op-amp

■ Primary op-amp terminals

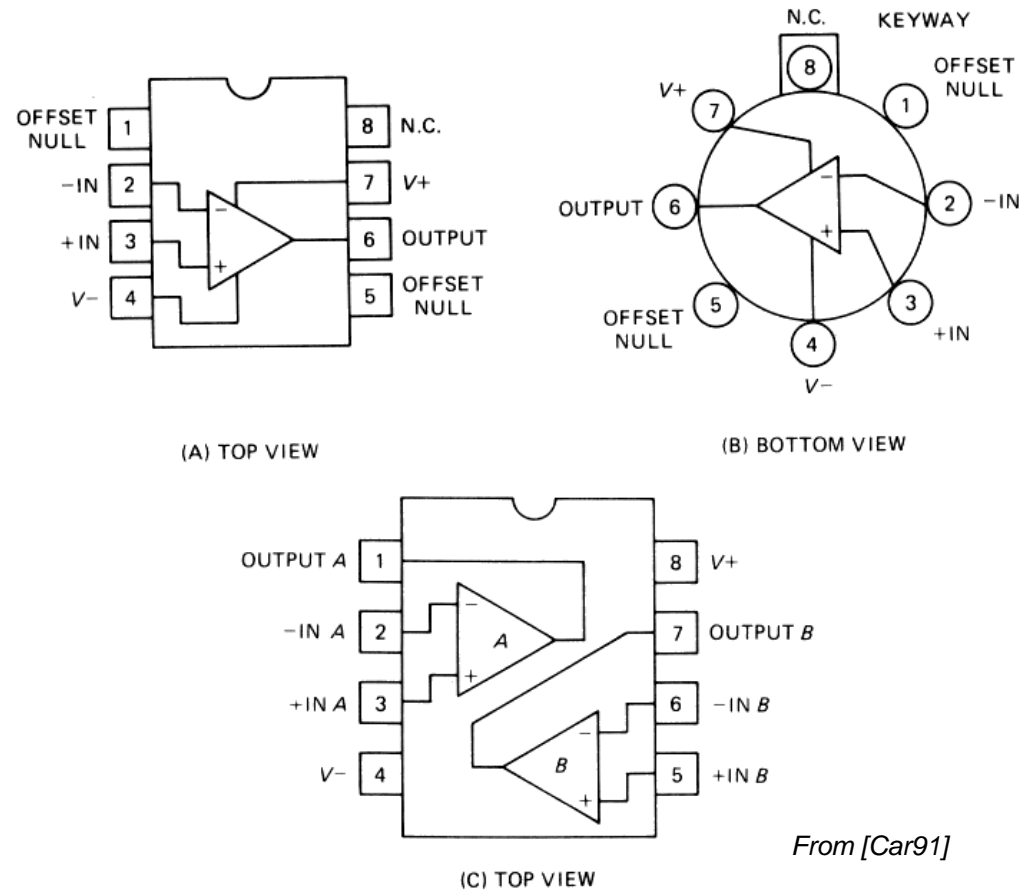- Inverting input
- Non-inverting input
- Output
- Power supply



From [Car91]

Fig. 12-6 Packaging for industry standard op-amp (741) in (A) DIP and (B) metal can packages; (C) dual op-amp such as 1458 device.



Ideal op-amp characteristics

- **The ideal op-amp is characterized by seven properties**
 - Knowledge of these properties is sufficient to design and analyze a large number of useful circuits
- **Basic op-amp properties**
 - Infinite open-loop voltage gain
 - Infinite input impedance
 - Zero output impedance
 - Zero noise contribution
 - Zero DC output offset
 - Infinite bandwidth
 - Differential inputs that stick together



Ideal Op-Amp Properties

■ Property No.1: Infinite Open-Loop Gain

- Open-Loop Gain A_{vol} is the gain of the op-amp without positive or negative feedback
- In the ideal op-amp A_{vol} is infinite
 - Typical values range from 20,000 to 200,000 in real devices

■ Property No.2: Infinite Input Impedance

- Input impedance is the ratio of input voltage to input current

$$Z_{in} = \frac{V_{in}}{I_{in}}$$


- When Z_{in} is infinite, the input current $I_{in}=0$
 - High-grade op-amps can have input impedance in the T Ω range
 - Some low-grade op-amps, on the other hand, can have mA input currents



Ideal Op-Amp Properties

■ Property No. 3: Zero Output Impedance

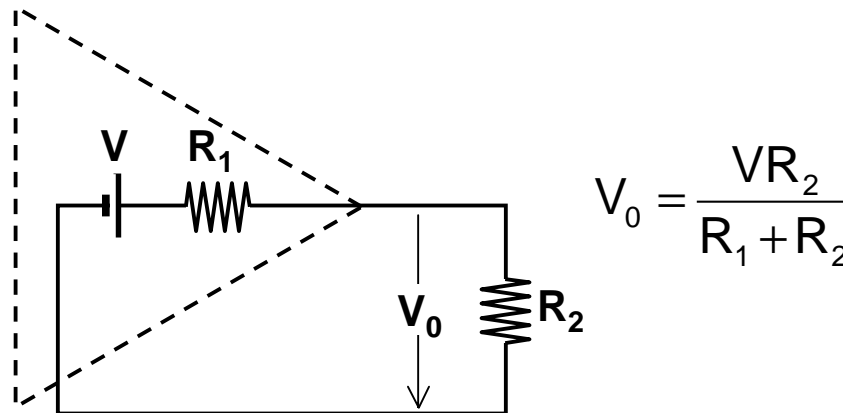- The ideal op-amp acts as a perfect internal voltage source with no internal resistance
 - This internal resistance is in series with the load, reducing the output voltage available to the load
 - Real op-amps have output-impedance in the 100-20Ω range
- Example




Ideal Op-Amp Properties

■ Property No.4: Zero Noise Contribution

- In the ideal op-amp, zero noise voltage is produced internally
 - This is, any noise at the output must have been at the input as well
- Practical op-amp are affected by several noise sources, such as resistive and semiconductor noise
 - These effects can have considerable effects in low signal-level applications

■ Property No. 5: Zero output Offset

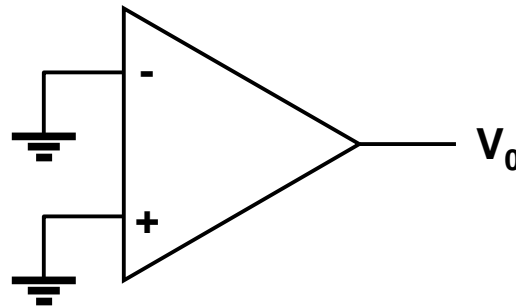- The output offset is the output voltage of an amplifier when both inputs are grounded
- The ideal op-amp has zero output offset, but real op-amps have some amount of output offset voltage



Ideal Op-Amp Properties

■ Property No. 6: Infinite Bandwidth

- The ideal op-amp will amplify all signals from DC to the highest AC frequencies
- In real opamps, the bandwidth is rather limited
 - This limitation is specified by the Gain-Bandwidth product (GB), which is equal to the frequency where the amplifier gain becomes unity
 - Some op-amps, such as the 741 family, have very limited bandwidth of up to a few KHz

■ Property No. 7: Differential Inputs Stick Together

- In the ideal op-amp, a voltage applied to one input also appears at the other input



Operational amplifier types

■ General-Purpose Op-Amps

- These devices are designed for a very wide range of applications
 - These op-amps have limited bandwidth but in return have very good stability (they are called frequency compensated)
 - Non-compensated op-amps have wider frequency response but have a tendency to oscillate

■ Voltage Comparators

- These are devices that have no negative feedback networks and therefore saturate with very low (μV) input signal voltages
 - Used to compare signal levels of the inputs

■ Low Input Current Op-Amps

- Op-amps with very low (pico-amp) input currents, as opposed to μA or mA input currents found in other devices

■ Low Noise Op-Amps

- Optimized to reduce internal noise
 - Typically employed in the first stages of amplification circuits

■ Low Power Op-Amps

- Optimized for low power consumption
 - These devices can operate at low power-supply voltages (i.e., $\pm 1.5\text{VDC}$)

■ Low Drift Op-Amps

- Internally compensated to minimize drift caused by temperature
 - Typically employed in instrumentation circuits with low-level input signals



Operational amplifier types

■ Wide Bandwidth Op-Amps

- These devices have a very high GB product (i.e., 100MHz) compared to 741-type op-amps (0.3-1.2MHz)
 - These devices are sometimes called **video op-amps**

■ Single DC Supply Op-Amps

- Devices that operate from a monopolar DC power supply voltage

■ High-Voltage Op-Amps

- Devices that operate at high DC power supply voltages (i.e. $\pm 44\text{VDC}$) compared to most other op-amps ($\pm 6\text{V}$ to $\pm 22\text{V}$)

■ Multiple Devices

- Those that have more than one op-amp in the same package (i.e., dual or quad op-amps)


■ Instrumentation Op-Amps

- These are DC differential amplifiers made with 2-3 internal op-amps
 - Voltage gain is commonly set with external resistors



Families of operational amplifiers

Table 12-1
Families of Operational Amplifiers

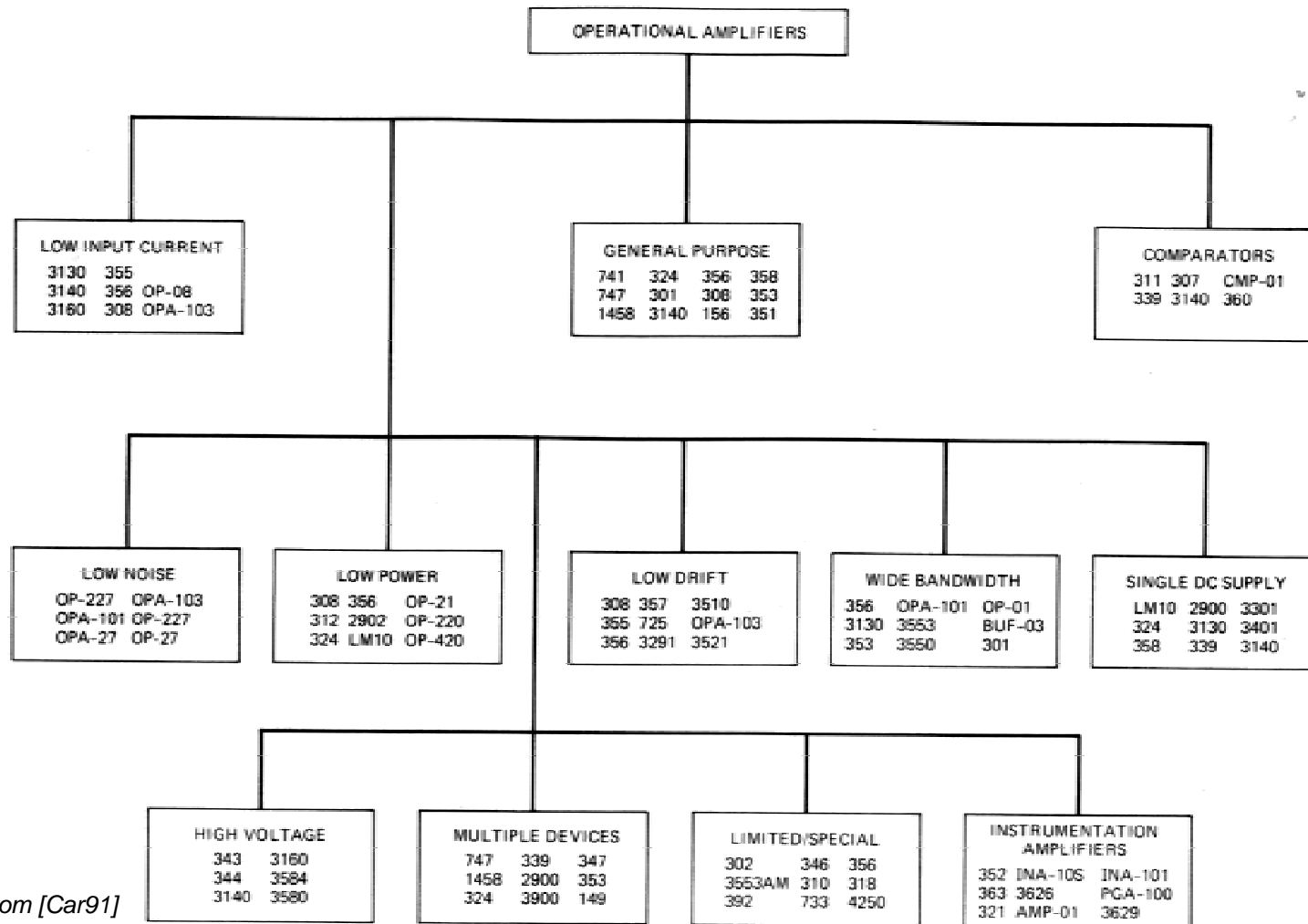


From [Car91]




Op-amp practical circuits

■ Voltage comparator

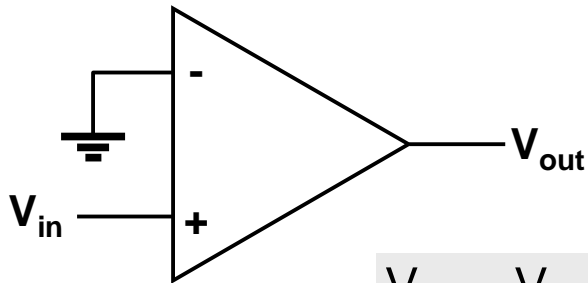


$$V_{out} = V_{CC} \text{sign}(V_{in})$$

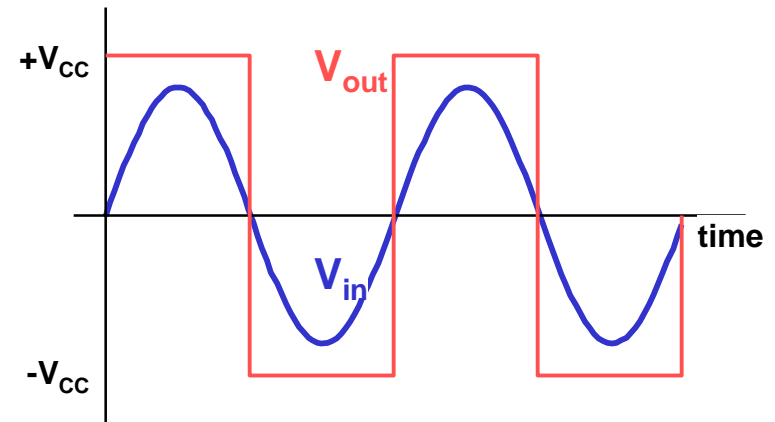

■ Voltage follower

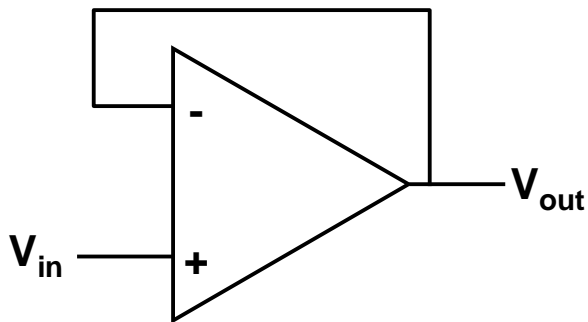- What is the main use of this circuit?
 - Buffering




$$V_{out} = V_{in}$$




Inverting and non-inverting amplifiers

■ Non-inverting amplifier

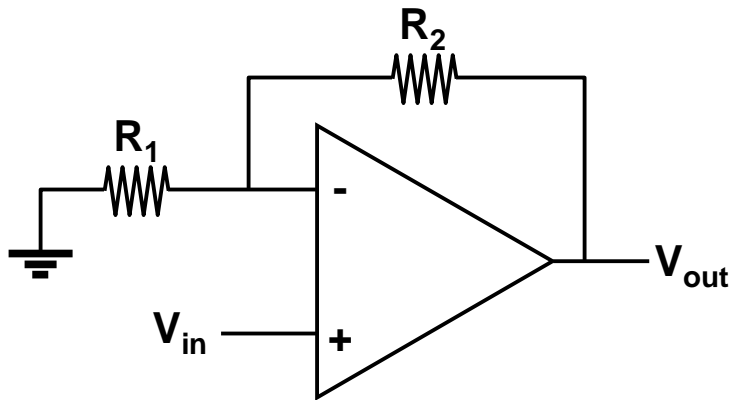

$$V_{\text{out}} = \left(1 + \frac{R_2}{R_1}\right) V_{\text{in}}$$

■ Inverting amplifier

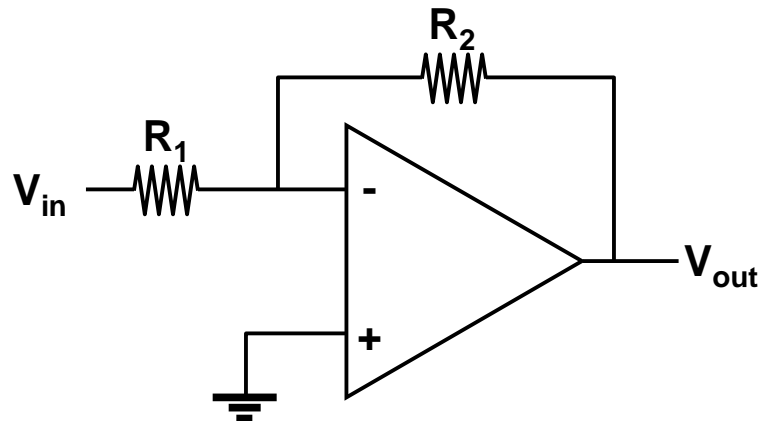


$$V_{\text{out}} = -\frac{R_2}{R_1} V_{\text{in}}$$




Summing and differential amplifier

■ Summing amplifier

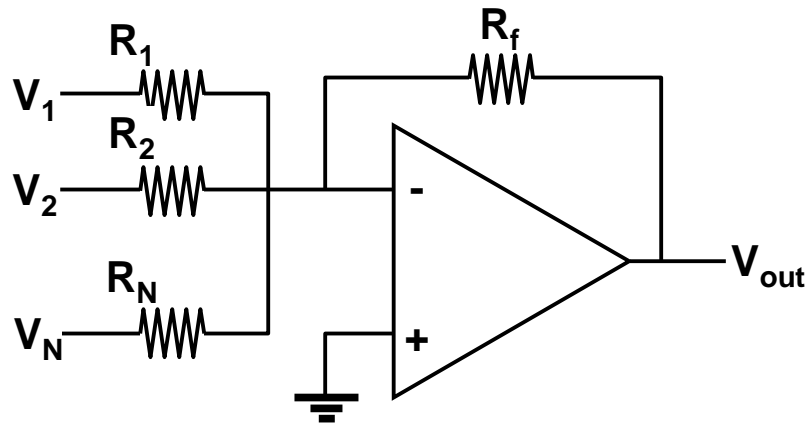

$$V_{\text{out}} = - \left(V_1 \frac{R_f}{R_1} + V_2 \frac{R_f}{R_2} + \dots + V_N \frac{R_f}{R_N} \right)$$

■ Differential amplifier

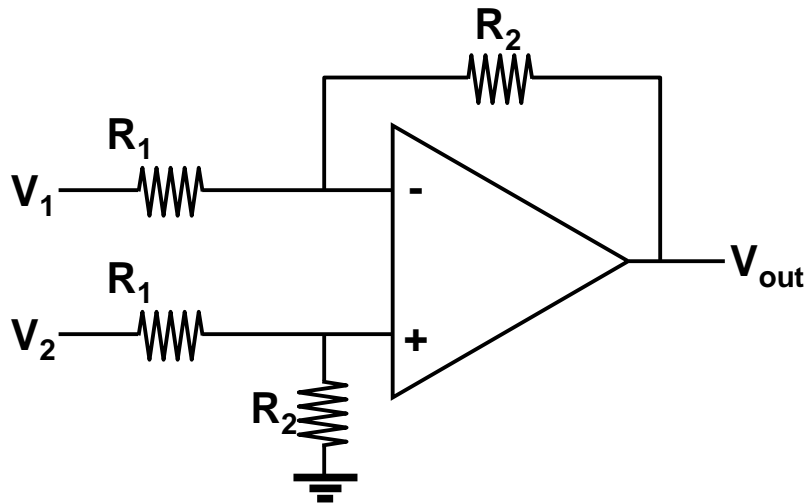


$$V_{\text{out}} = \frac{R_2}{R_1} (V_2 - V_1)$$




Integrating and differentiating amplifier

■ Integrating amplifier

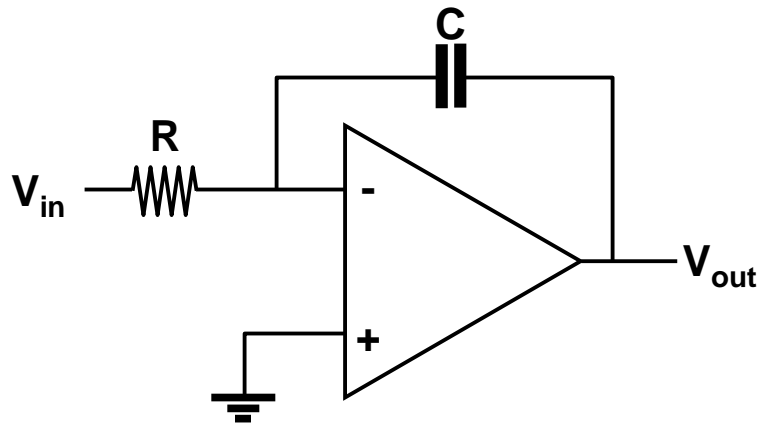

$$V_{out} = -\frac{1}{j\omega CR} V_{in} = -\frac{1}{RC} \int V_{in} dt$$

■ Differentiating amplifier

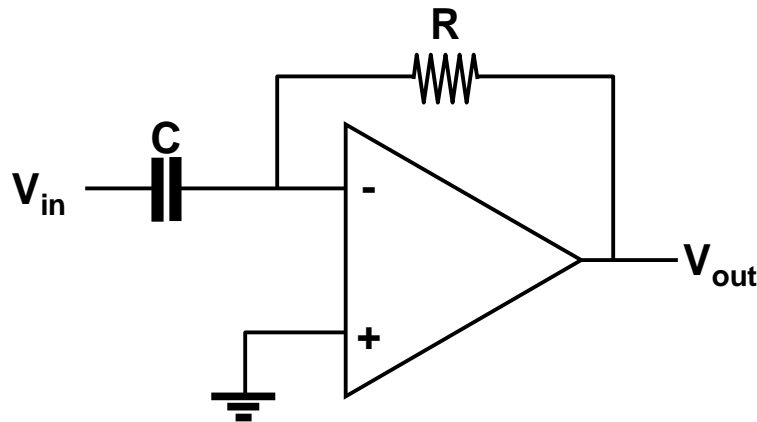


$$V_{out} = -\frac{R}{\frac{1}{j\omega C}} V_{in} = -RC \frac{dV_{in}}{dt}$$




Current to voltage conversion

■ Current-to-voltage

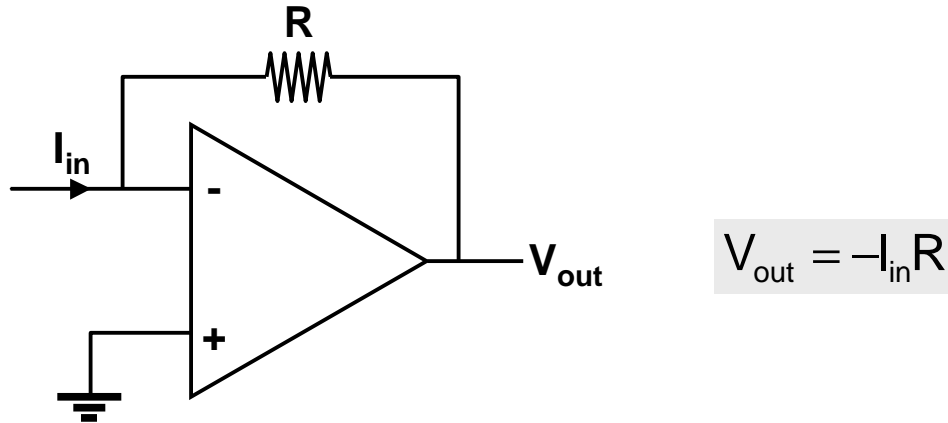

■ Voltage to current

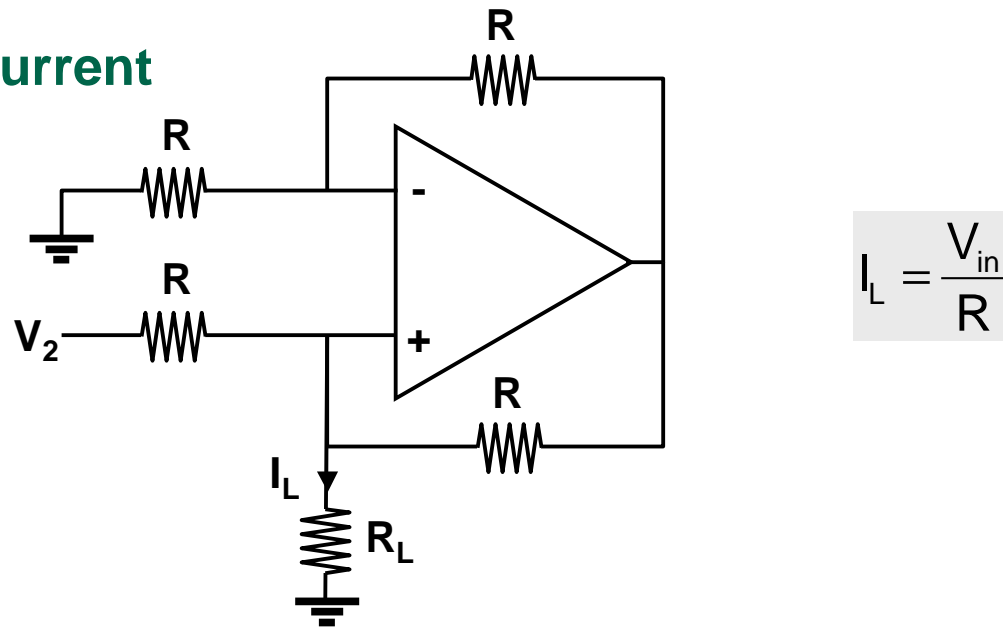

References

- [Car91] J. J. Carr, 1991, *Designer's Handbook of Instrumentation and Control Circuits*, Academic Press, San Diego, CA.
- [Whi96] J. C. Whitaker, 1996, *The Electronics Handbook*, CRC Press
- [Elg98] P. Elgar, 1998, *Sensors for Measurement and Control*, Addison Wesley Longman, Essex, UK.
- [PAW91] R. Pallas-Areny and J. G. Webster, 1991, *Sensors and Signal Conditioning*, Wiley, New York

