
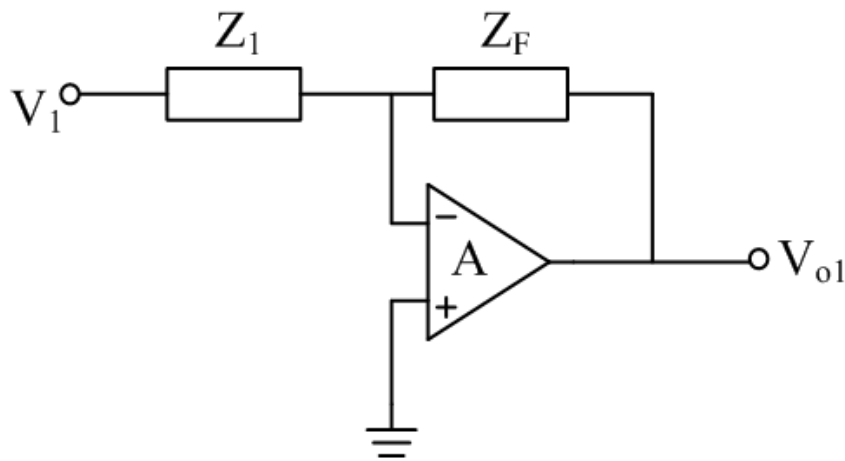


ACTIVE-RC FILTER ARCHITECTURES

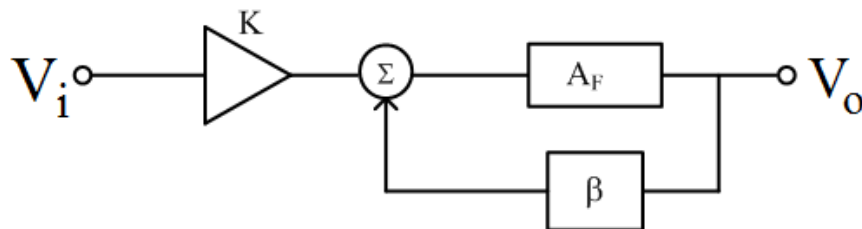- We will discuss first-order and second-order filters based on general inverter configurations.
- This approach will be based on two key building blocks.



$$\frac{V_{o1}}{V_i} = \frac{-\frac{Z_F}{Z_1}}{1 + \frac{1}{A} \left(1 + \frac{Z_F}{Z_1} \right)} \quad (1)$$



$$\frac{V_o}{V_i} = \frac{KA_F}{1 + \beta A_F} \quad (2)$$


Z_1
 or
 Z_F
 Can be:

$$\left\{ \begin{array}{ll}
 \begin{array}{c} \text{---} \text{R} \text{---} \\ | \\ \text{---} \text{C} \text{---} \\ | \\ \text{---} \end{array} & \frac{R}{sC} \\
 \begin{array}{c} \text{---} \text{R} \text{---} \\ | \\ \text{---} \text{C} \text{---} \\ | \\ \text{---} \end{array} & \frac{1 + sRC}{sC} \\
 \begin{array}{c} \text{---} \text{C} \text{---} \\ | \\ \text{---} \text{R} \text{---} \\ | \\ \text{---} \end{array} & \frac{R}{1 + sRC}
 \end{array} \right. \quad (3)$$

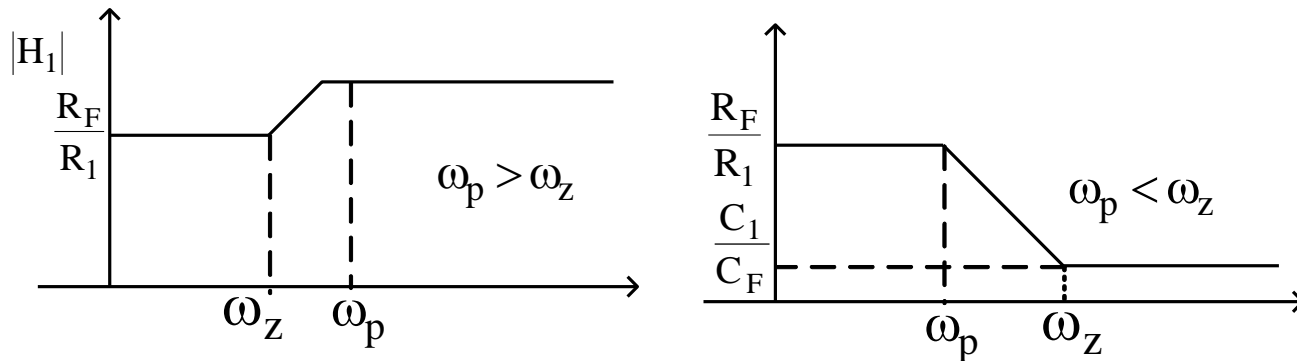EXAMPLE: Let $Z_1 = \frac{R_1}{1 + sR_1C_1}$, $Z_F = \frac{R_F}{1 + sR_FC_F}$

Assuming ideal op amp A $\rightarrow \infty$. Then using (1)

$$H_1 = \frac{V_{01}}{V_1} = -\frac{R_F/R_1(1 + sR_1C_1)}{(1 + sR_FC_F)} = -\frac{K_n(1 + s/\omega_z)}{(1 + s/\omega_p)} \quad (4)$$



Particular cases are easily derived from (3) and (4)

— Integrator: $C_1 \rightarrow 0$, $R_F \rightarrow \infty$

$$H_1 \cong -\frac{R_F}{R_1} \frac{1}{sR_FC_F} = -\frac{1}{sC_FR_1}$$

— Differentiator ; $R_1 \rightarrow \infty$, $C_F \rightarrow 0$

$$H_1 \cong -\frac{R_F}{R_1} sR_1C_1 = -sR_FC_1$$


— Low-Pass: $C_1 = 0$

$$H_1 = \frac{-\frac{R_F}{R_1}}{1 + sR_FC_F}$$

— High-Pass: $R_1 \rightarrow \infty$

$$H_1 \cong -\frac{R_F}{R_1} \frac{sR_1C_1}{1 + sR_FC_F}$$


— One pole and one zero

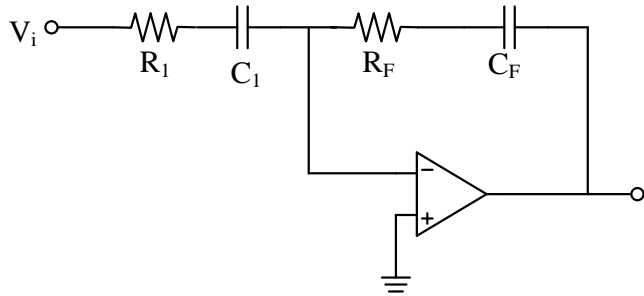

$$\frac{V_o}{V_i} = -\frac{1 + sR_F C_F}{sC_F} \frac{sC_1}{1 + sR_1 C_1} = -\frac{C_1}{C_F} \frac{1 + sR_F C_F}{1 + sR_1 C_1} \quad (5)$$


What are the key differences between Eqs. (4) and (5)?

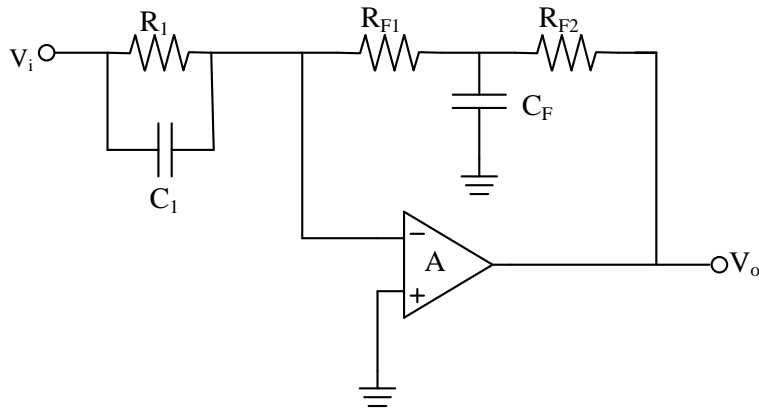Exercise 1. Obtain the transfer function of the following circuit.



Second-Order Filters Based on a Two-Integrator Loop.

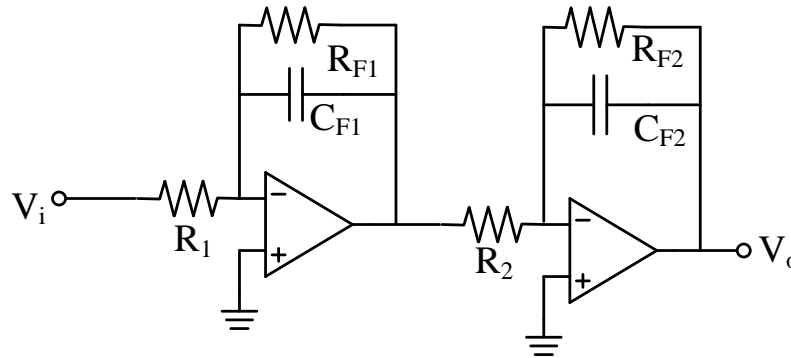- We can design a second-order filter by cascading two inverters. i.e.



$$\frac{V_o}{v_i} = \frac{-\frac{R_{F1}}{R_1} \left(-\frac{R_{F2}}{R_2} \right)}{(1 + sC_{F1}R_{F1})(1 + sC_{F2}R_{F2})} = \frac{\frac{R_{F1}}{R_1} \frac{R_{F2}}{R_2}}{s^2 C_{F1}R_{F1}C_{F2}R_{F2} + s(C_{F1}R_{F1} + C_{F2}R_{F2}) + 1} \quad (6)$$

What are the locations of the poles?


$$s_{p1,2} = \frac{-(C_{F1}R_{F1} + C_{F2}R_{F2}) \pm \sqrt{(C_{F1}R_{F1} + C_{F2}R_{F2})^2 - 4C_{F1}R_{F1}C_{F2}R_{F2}}}{2C_{F1}R_{F1}C_{F2}R_{F2}}$$

To have complex poles it requires that

$$(C_{F1}R_{F1})^2 + (C_{F2}R_{F2})^2 - 2C_{F1}R_{F1}C_{F2}R_{F2} < 0?$$

Which it is impossible to satisfy. Therefore, cascading two first-order filter yield a second-order filter with only real poles.

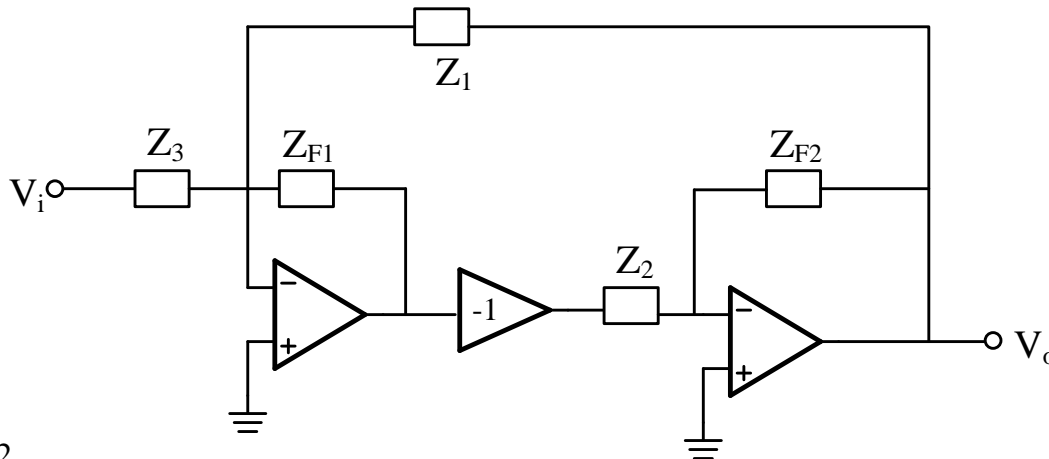The general form of the second order two-integrator loop has the following topology.



$$H = \frac{-\frac{Z_{F1}}{Z_3} \frac{Z_{F2}}{Z_2}}{1 + \frac{Z_{F1}}{Z_1} \frac{Z_{F2}}{Z_2}}$$

(7a)

Note the similarity of Eq. (7a) with (2). Also observe that A “-1” needs to be inserted before or after the second inverter to yield a negative feedback loop.

Let us consider the following filter where


$$Z_3 = R_3, Z_1 = R_1, Z_2 = R_2, Z_{F1} = \frac{1}{sC_{F1}}, Z_{F2} = \frac{R_{F2}}{1 + sC_{F2}R_{F2}}$$

Thus Eq. (7a) yields:

$$H = \frac{-\frac{1}{sC_{F1}R_3} \frac{R_{F2}/R_2}{(1 + sC_{F2}R_{F2})}}{1 + \frac{1}{sC_{F1}R_1} \frac{R_{F2}/R_2}{(1 + sC_{F2}R_{F2})}}$$

$$H = \frac{-\frac{1}{C_{F1}R_3C_{F2}R_2}}{s^2 + \frac{s}{C_{F2}R_{F2}} + \frac{1}{C_{F1}R_1C_{F2}R_2}} = \frac{-\omega_{o1}^2}{s^2 + \frac{\omega_o}{Q}s + \omega_o^2}$$

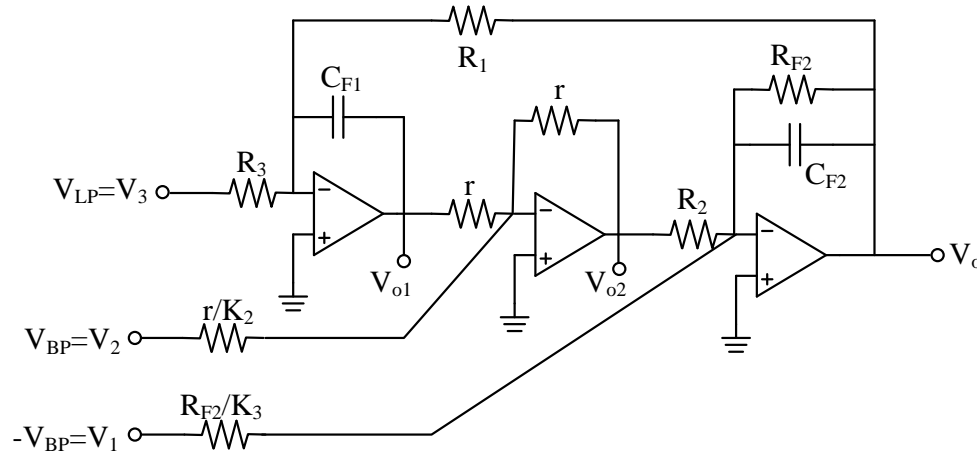By injecting in different current summing nodes a **general biquad filter** can be obtained.




$$V_o = \frac{V_3 \frac{1}{sC_{F1}R_3} \frac{R_{F2}/R_2}{(1 + sC_{F2}R_{F2})} + \frac{-K_2 \frac{R_{F2}}{R_2}}{(1 + sC_{F2}R_{F2})} - \frac{K_3 \frac{R_{F2}}{R_{F2}} V_1}{(1 + sC_{F2}R_{F2})}}{1 + \frac{1}{sC_{F1}R_1} \frac{R_{F2}/R_2}{(1 + sC_{F2}R_{F2})}}$$

$$V_o = \frac{V_3 \frac{1}{C_{F1}R_3C_{F2}R_2} + V_2sC_{F1}R_1K_2 - V_3sC_1R_1K_3}{s^2 + \frac{s}{C_{F2}R_{F2}} + \frac{1}{C_{F1}R_1C_{F2}R_2}}$$

Exercise 2. Obtain the expressions of V_{o1} and V_{o2} .


More general biquad expressions and topologies can be obtained by adding a summer.

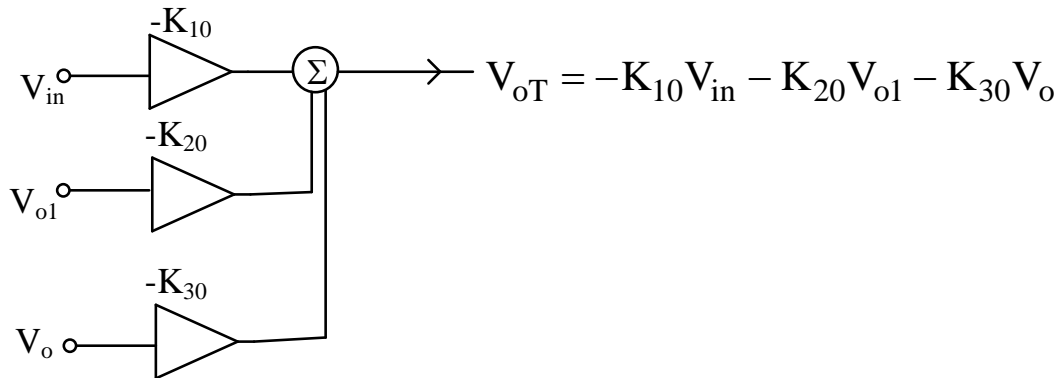

Exercise 3. Draw an active-RC topology of the block diagram show above.

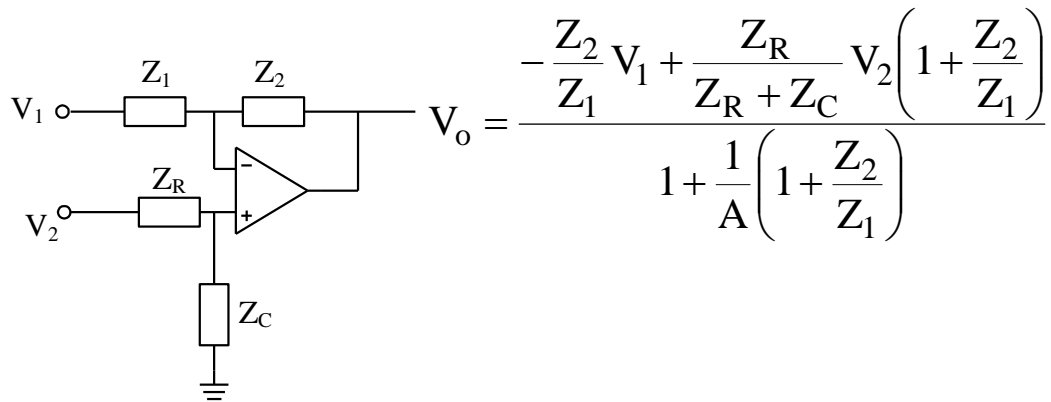Exercise 4 a) For only $V_1 \neq 0$ obtain V_o and V_{o1} when instead of the resistor R_{F2}/K_3 a capacitor $K_4 C_{F2}$ is used. b) For only $V_3 \neq 0$ obtain V_{o1} when the resistor R_3 is replaced by a capacitor $K_{HP} C_{F1}$.

By using also the positive input of the op amp other useful filters can be obtained.




$$V_o = \frac{-\frac{Z_2}{Z_1} V_1 + \frac{Z_R}{Z_R + Z_C} V_2 \left(1 + \frac{Z_2}{Z_1}\right)}{1 + \frac{1}{A} \left(1 + \frac{Z_2}{Z_1}\right)}$$

Example. Phase shifter $Z_2=R_2=R_1$, $Z_1=R_1$, $Z_R=R$ $Z_C = \frac{1}{sC}$ and $A \rightarrow \infty$ with $V_1 = V_2$

$$\frac{V_o}{V_1} = -1 + \frac{sRC}{1 + sRC} \cdot 2 = \frac{-1 - sRC + 2sRC}{1 + sRC} = -\frac{1 - sRC}{1 + sRC}$$

Sallen and Key Bandpass Filter

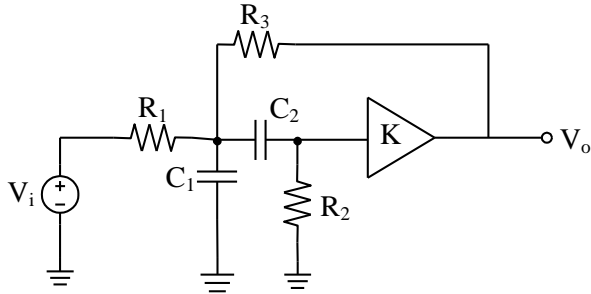

K is a non-inverting amplifier

Using Nodal Analysis

$$V_1 \left(s(C_1 + C_2) + \frac{1}{R_1} + \frac{1}{R_3} \right) - sC_2 V_2 - \frac{V_o}{R_3} = \frac{V_i}{R_1} \quad (1)$$

$$-V_1(sC_2) + V_2 \left(sC_2 + \frac{1}{R_2} \right) = 0 \quad (2)$$

$$V_o = KV_2 \quad (3)$$

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{K \frac{s}{R_1 C_1}}{s^2 + \left[\frac{1}{R_2 C_2} + \left(1 - K + \frac{R_3}{R_1} + \frac{R_3}{R_2} \right) \frac{1}{R_3 C_1} + \frac{R_1 R_3}{R_1 R_3 R_2 C_1 C_2} \right]}$$

A particular case is for $R_1=R_2=R_3=R$, $C_1=C_2=C$


Then

$$\omega_0^2 = \frac{2}{(RC)^2} \quad ; \quad Q = \frac{\sqrt{2}}{4-K}$$

or for a given ω_0 and Q

$$RC = \frac{\sqrt{2}}{\omega_0} \quad \text{and} \quad K = 4 - \frac{\sqrt{2}}{Q}$$

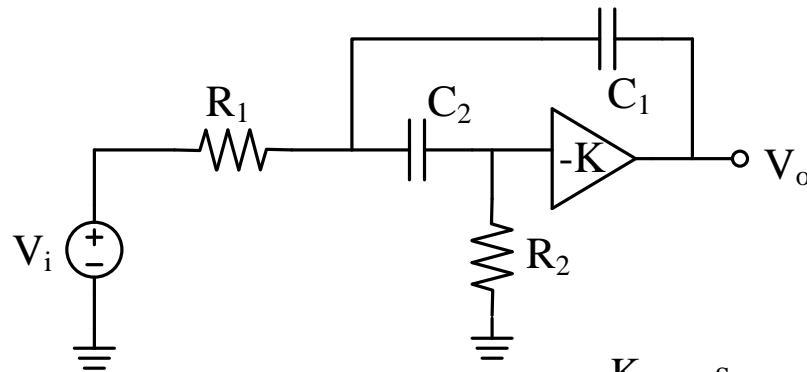
Exercise 5. Prove the transfer function is a BP filter of the following circuit






$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{-K \frac{s}{K+1} \frac{1}{R_1 C_1}}{s^2 + \frac{1}{K+1} \left[\frac{R_1 + R_2}{R_1 R_2 C_1} + \frac{1}{R_2 C_2} \right] s + \frac{1}{(K+1) R_1 R_2 C_1 C_2}}$$

Another technique for analysis and design based on state-variable uses building blocks.



CIRCUIT

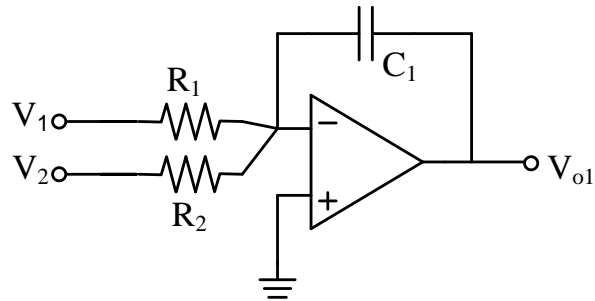

REPRESENTATION

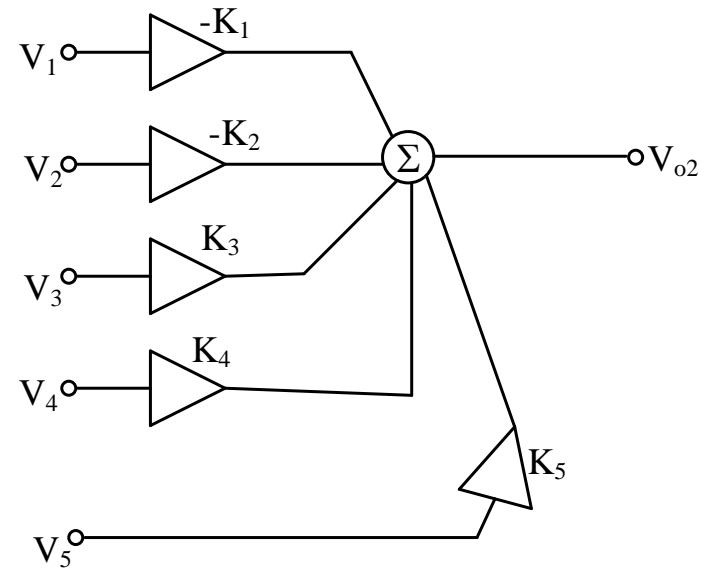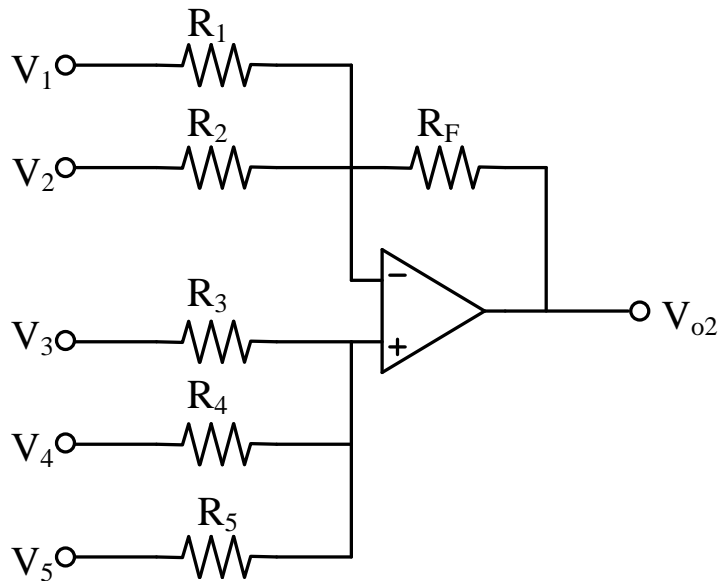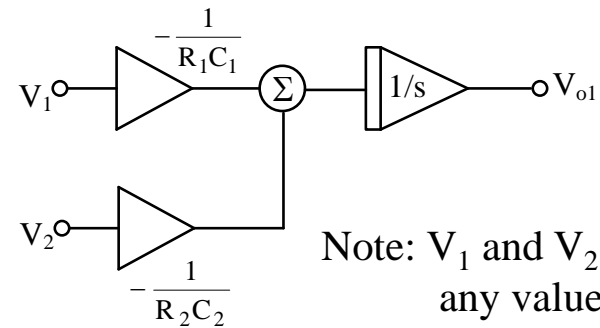

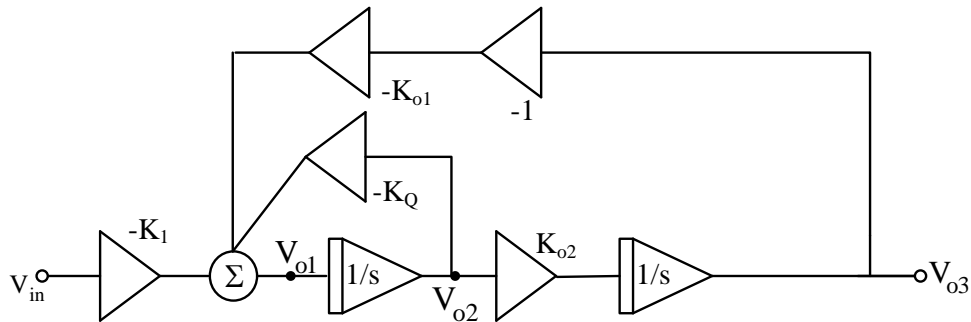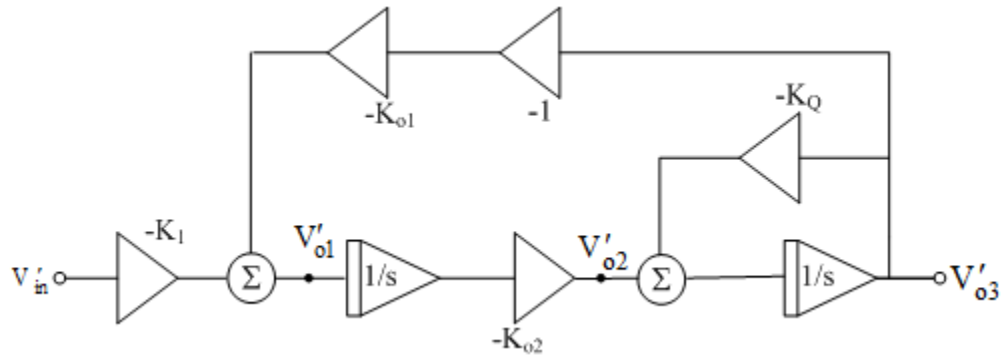Let us apply to a two-integrator loop plus Mason's Rule.




For Second-topology


$$V_{o1} = \frac{-K_1 V_{in}}{1 + \frac{K_Q}{s} + \frac{K_{o1}K_{o2}}{s^2}} = \frac{-K_1 s^2 V_{in}}{s^2 + K_Q s + K_{o1}K_{o2}} \quad \text{HP}$$

$$V_{o2} = \frac{\frac{-K_1}{s} V_{in}}{1 + \frac{K_Q}{s} + \frac{K_{o1}K_{o2}}{s^2}} = \frac{-K_1 s V_{in}}{s^2 + K_Q s + K_{o1}K_{o2}} \quad \text{BP}$$

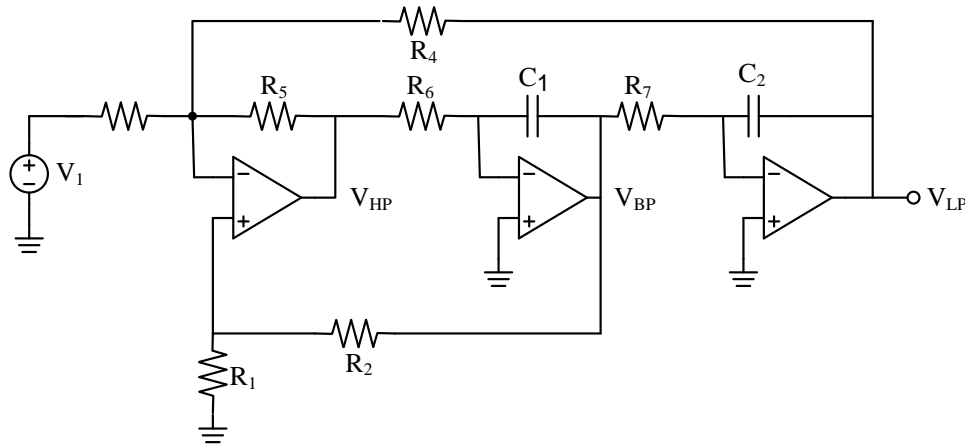Next we show that we can go from an Active-RC representation into a block diagram or vice versa.



KHN Biquad Filter

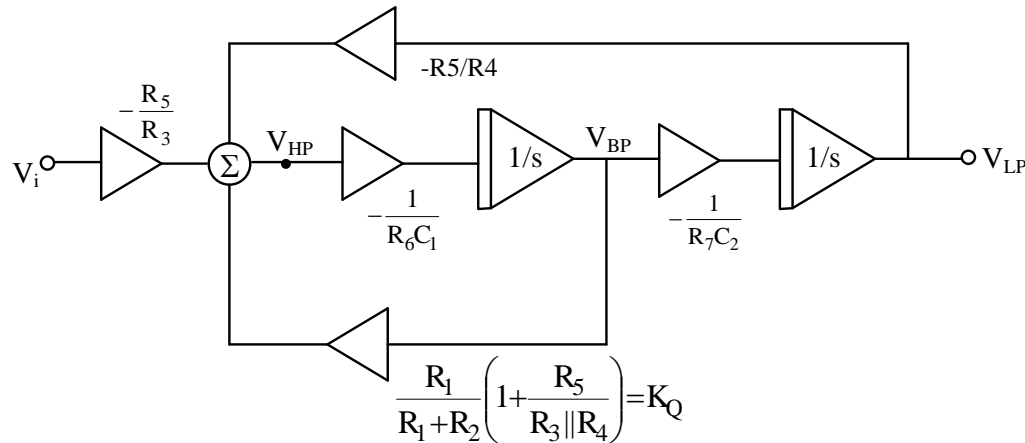

$$\frac{V_{HP}}{V_i} = \frac{-\frac{R_5}{R_3}}{1 + \frac{K_Q}{R_6 C_1} s + \frac{R_5/R_4}{R_6 C_1 R_7 C_2 s^2}} = \frac{-\frac{R_5}{R_3} s^2}{s^2 + \frac{K_Q}{R_6 C_1} s + \frac{R_5/R_4}{R_6 C_1 R_7 C_2}}$$