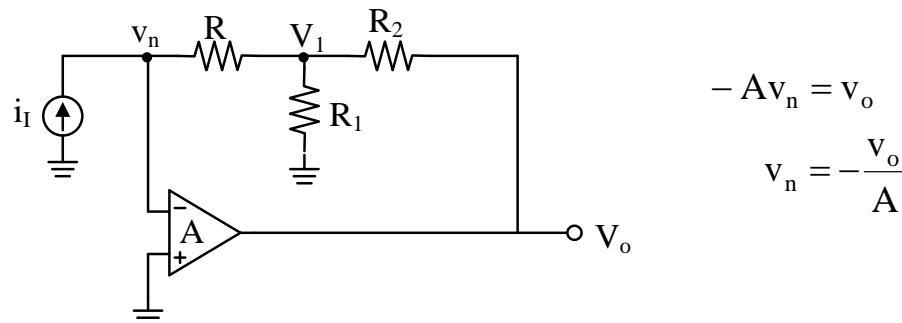


## HIGH SENSITIVITY I-V CONVERTER



$$-Av_n = v_o$$

$$v_n = -\frac{v_o}{A}$$

$$V_1 \left( \frac{1}{R} + \frac{1}{R_2} + \frac{1}{R_1} \right) - \frac{v_n}{R} - \frac{v_o}{R_2} = 0 \quad (1); \quad \frac{v_n}{R} - \frac{V_1}{R} = i_I \quad (2) \quad \text{For } A \rightarrow \infty, \text{ then } v_n = 0. \text{ Thus}$$

$$V_1 \left( \frac{R_2}{R} + 1 + \frac{R_2}{R_1} \right) = V_o \quad (1')$$

$$V_1 = -i_I R \quad (2')$$

(2') into (1')

$$-i_I \left( R_2 + R + \frac{R R_2}{R_1} \right) = V_o = k R i_I = - \left( 1 + \frac{R_2}{R_1} + \frac{R_2}{R} \right) R i_I$$

$$V_o = -i_I \frac{R_2 R_1 + R R_1 + R R_2}{R_1} \leftarrow T - \text{Network}$$

$$V_o = -i_I R \frac{R_1 + R_2 + R_2 R_1 / R}{R_1}$$

$$S_{R_1}^{V_o} = \frac{\partial V_o}{\partial R_1} \frac{R_1}{V_o}$$

$$V_o = -i_I \left( R_2 + R + \frac{R R_2}{R_1} \right)$$

$$\frac{\partial V_o}{\partial R_1} = +i_I \frac{R R_2}{R_1^2} \quad ; \quad \frac{\partial V_o}{\partial R_1} \frac{R_1}{V_o} = i_I \frac{R R_2}{R_1^2} \frac{R_1}{-i_I \left( R_2 + R + \frac{R R_2}{R_1} \right)}$$

$$S_{R_1}^{V_o} = -\frac{R R_2}{R_1} \frac{1}{R_2 + R + \frac{R R_2}{R_1}}$$

$$S_{R_1}^{V_o} = -\frac{R R_2}{R_1 R_2 + R_2 R + R_1 R} = -\frac{R R_2 / R_1}{R_1 R_2 + R_2 R + R_1 R} \frac{R_1}{R_1}$$

$$S_{R_1}^{V_o} = \frac{-R R_2}{R_1 R_T}$$

Example : Let  $R_T = 1M\Omega$

$$R_T = \frac{R R_2 + R R_1 + R_1 R_2}{R_1} = R + R_2 + \frac{R R_2}{R_1}$$

Assume  $R_1 = 100\Omega$

$$\text{Then } R + R_2 + \frac{R R_2}{100} = 10^6$$

and  $R = 100K$  then

$$100K + R_2 \left( 1 + \frac{100K}{100} \right) = 10^6 \Rightarrow R_2 = \frac{10^6 - 10^5}{1 + 10^3} \sim 10^3 - 10^2$$


$$R_2 \approx 900\Omega$$

Thus

$$S_{R_1}^{V_o} = -\frac{R R_2}{R_1 R_T} = \frac{100K \times 0.9K}{100 \times 10^6} = \frac{-90}{100} = -0.9$$

Effects of Input and Output impedance of the Op Amp.

### INVERTING

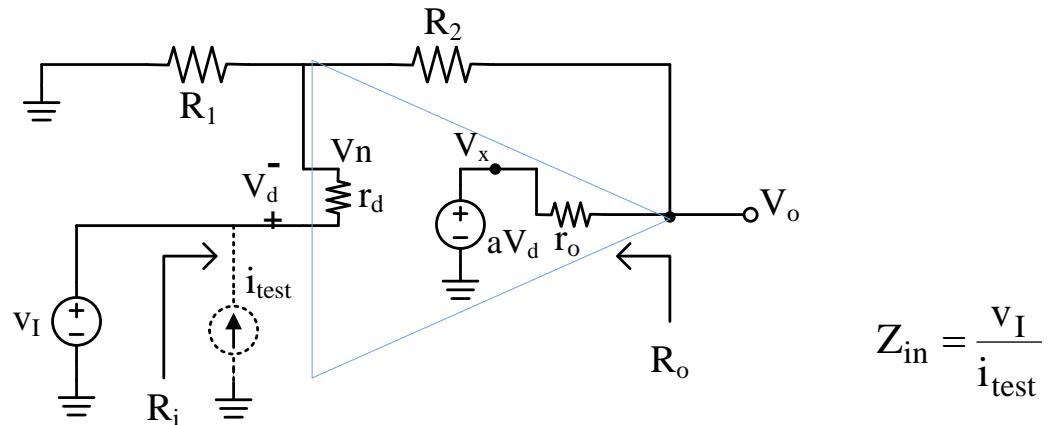

$$Z_{in} = \frac{v_I}{i_{test}}$$

$$v_n \left[ \left( \frac{1}{r_d} \right) + \frac{1}{R_1} + \frac{1}{R_2} \right] - \frac{V_o}{R_2} = \frac{V_I}{r_d} \quad (1)$$

$$v_d = r_d i_{test} \quad (2)$$

$$v_n = v_I - v_d = v_I - r_d i_{test} \quad (4)$$

$$V_o \left( \frac{1}{r_o} + \frac{1}{R_2} \right) - \frac{a V_d}{r_o} - \frac{V_n}{R_2} = 0 \quad (3)$$

(2) into (3)

$$\begin{aligned} V_o \left( \frac{1}{r_o} + \frac{1}{R_2} \right) - \frac{a r_d i_{\text{test}}}{r_o} &= \frac{V_I - r_d i_{\text{test}}}{R_2} \\ V_o = + \frac{r_d i_{\text{test}} a}{1 + \frac{r_o}{R_2}} + \frac{V_I - r_d i_{\text{test}}}{1 + \frac{R_2}{r_o}} \end{aligned} \quad (3')$$

substituting (3') and (4) into (1)

$$\begin{aligned} (v_I - v_d) \left[ \frac{1}{r_d} + \frac{1}{R_1} + \frac{1}{R_2} \right] - \left( \frac{r_d \cdot i_{\text{test}} \cdot a}{1 + \frac{r_o}{R_2}} + \frac{V_I - r_d \cdot i_{\text{test}}}{1 + \frac{R_2}{r_o}} \right) \frac{1}{R_2} &= \frac{v_I}{r_d} \\ (v_I) \left[ \frac{1}{r_d} + \frac{1}{R_1} + \frac{1}{R_2} \right] - r_d i_{\text{test}} \left[ \frac{1}{r_d} + \frac{1}{R_1} + \frac{1}{R_2} + \frac{a}{R_2 + r_o} \right] - r_d i_{\text{test}} \left[ -\frac{1}{1 + \frac{R_2}{r_o}} \cdot \frac{1}{R_2} \right] &= 0 \end{aligned}$$

$$\frac{v_I}{i_{\text{test}}} = \frac{r_d \left[ \frac{a}{R_2 + r_o} + \frac{1}{r_d} + \frac{1}{R_1} + \frac{1}{R_2} - \frac{1}{1 + \frac{R_2}{r_o}} \cdot \frac{1}{R_2} \right]}{\frac{1}{R_1} + \frac{1}{R_2} - \frac{1}{1 + \frac{R_2}{r_o}} \cdot \frac{1}{R_2}}$$

$$Z_{\text{in}} \cong \frac{R_1 R_2}{R_1 + R_2} r_d \left[ \frac{a}{R_2 + r_o} + \frac{1}{r_d} + \frac{R_1 + R_2}{R_1 R_2} \right]$$

$$Z_{\text{in}} \cong \frac{R_1 R_2}{R_1 + R_2} r_d \left[ \frac{a}{R_2} \right] = \frac{r_d a}{1 + \frac{R_2}{R_1}} = r_d \frac{a}{1/\beta} = r_d \beta a = r_d T$$

$$Z_{\text{in}} \cong \frac{R_1 R_2}{R_1 + R_2} \left[ \frac{r_d a}{R_2 + r_o} + 1 + r_d \frac{R_1 + R_2}{R_1 R_2} \right]$$

$$Z_{\text{in}} \cong \frac{R_1 R_2}{R_1 + R_2} \frac{a r_d}{R_2 + r_o} + \frac{R_1 R_2}{R_1 + R_2} + r_d$$

$$Z_{in} \cong \frac{R_1}{R_1 + R_2} ar_d + r_d + \frac{R_1 R_2}{R_1 + R_2}$$

$$Z_{in} \cong r_d \left( 1 + \frac{a}{1 + \frac{R_2}{R_1}} \right) = r_d \left( 1 + \frac{a}{1/\beta} \right) = r_d (1 + \beta a)$$

$$Z_{in} = r_d (1 + T)$$

Exercise. Show that

$$R_o \cong \frac{r_o}{1 + T}$$