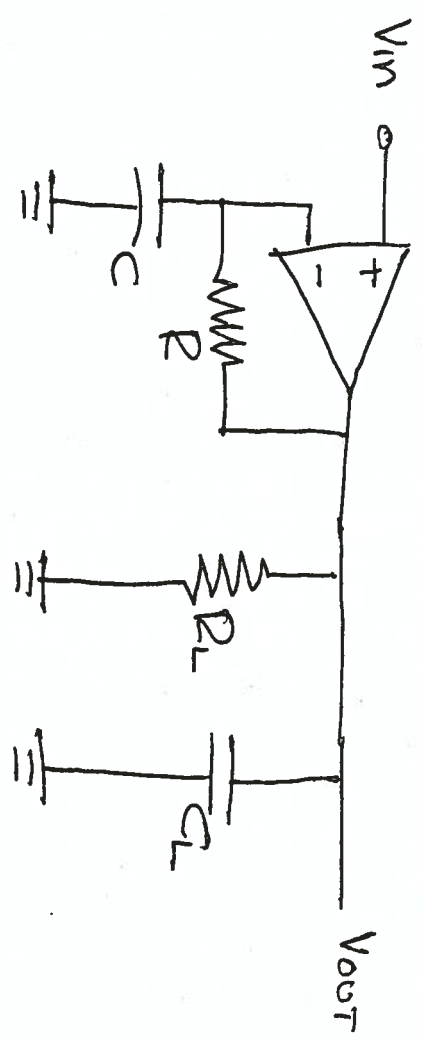


EECE 457 (ess)


SIMULATION AND MEASUREMENTS OF OP AMP.

— OPEN LOOP GAIN



DETERMINE
 $RC < \frac{1}{GB}$

— MEASURING THE INPUT OFFSET VOLTAGE Vos

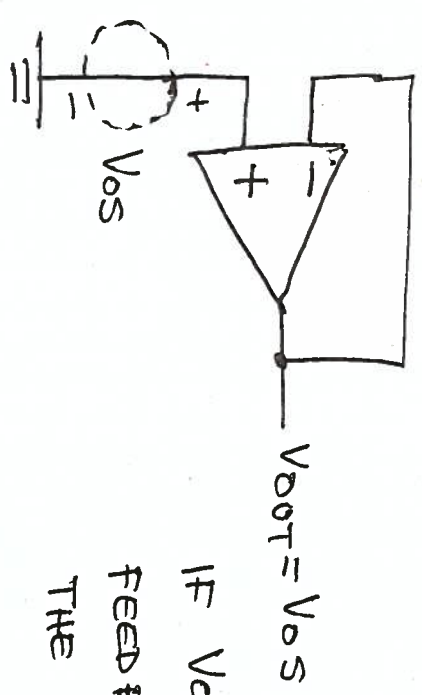

IF Vos IS VERY SMALL USE A FEEDBACK CIRCUIT TO INCREASE THE OUTPUT i.e. $V_{out} = (1 + \frac{R_f}{R_i}) V_{os}$

• PSRR USING PREVIOUS CIRCUIT

FIRST

$$V_{DD} \rightarrow V_{DD} + 1V$$

$$-V_{OUT} \rightarrow -V_{OUT} = 0$$

$$\left. \begin{array}{l} V_{DD} \rightarrow V_{DD} + 1V \\ -V_{OUT} \rightarrow -V_{OUT} = 0 \end{array} \right\} V_{OS3}$$

SECOND

$$V_{DD} \rightarrow V_{DD} - 1V$$


$$V_{OUT} = 0 \rightarrow -V_{OUT} = 0$$

$$\left. \begin{array}{l} V_{DD} \rightarrow V_{DD} - 1V \\ V_{OUT} = 0 \rightarrow -V_{OUT} = 0 \end{array} \right\} V_{OS4} = V_{OFF}$$

FOR PSRR⁻ FIX V_{DD} AND CHANGE V_{SS} WHILE V_{OUT} = 0


$$PSRR^+ = \frac{2000}{|V_{OS3} - V_{OS4}|}$$

- MEASURING CMRR (SIMULATIONS)

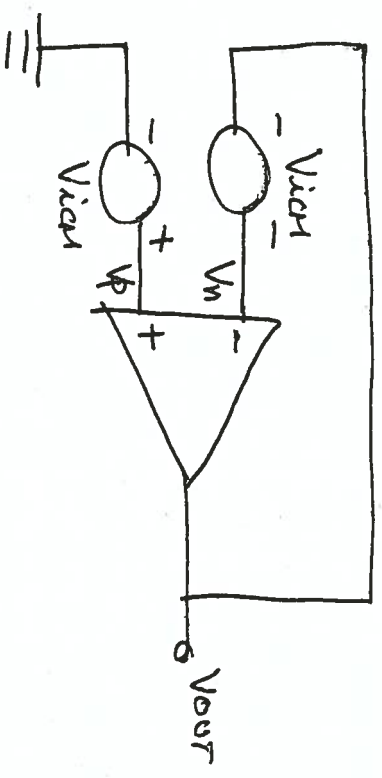

$$\frac{V_{out}}{V_{cm}} = \frac{\pm A_{cm}}{1 + A_{DM} \left(\pm \frac{A_{cm}}{2} \right)}$$

$$\frac{V_{out}}{V_{cm}} \approx \frac{|A_{cm}|}{A_{DM}} = \frac{1}{CMRR}$$

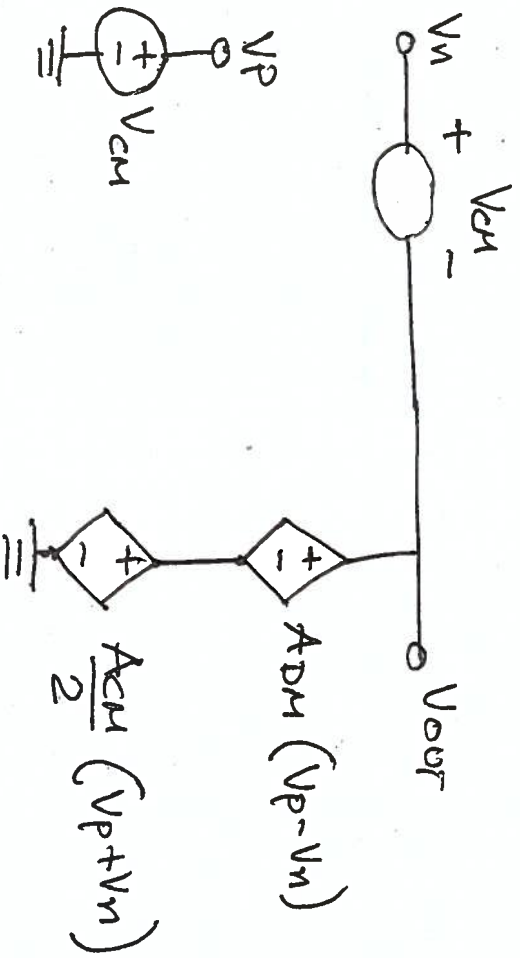


NOTE THAT


$$V_{out} = A_{DM} (V_{cm} - V_{in}) + \frac{A_{cm}}{2} (V_p + V_m)$$

$$V_{in} = V_{cm} + V_{out}$$

— MEASURING DIRECTLY PSPICE

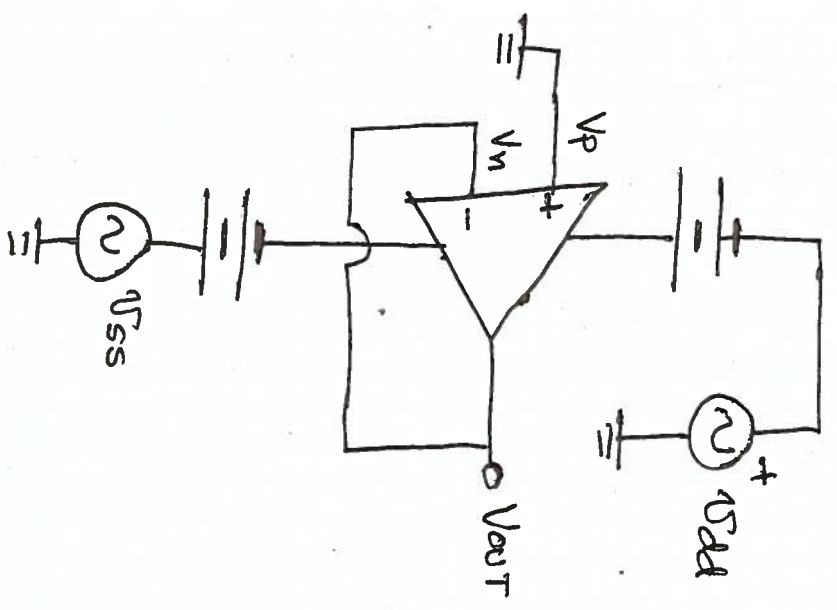

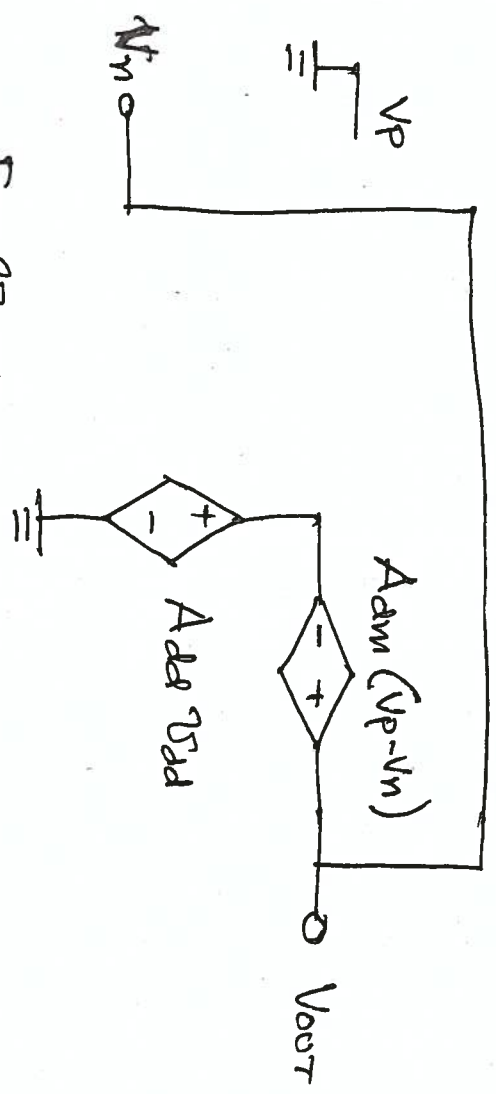NOTE: IN REAL CIRCUIT
A DRIVER MUST BE NEEDED
TO APPLY V_{SD} OR/AND V_{SS} ,



For $V_{SS}=0$

$$V_{OUT} = A_{DM}(0 - V_N) + A_{DD} V_{SD}$$

$$V_N = V_{OUT}$$



THEN

$$V_{OUT} = -A_{DM} V_{OUT} + A_{DD} V_{SD}$$

$$V_{OUT} = \frac{A_{DD} V_{SD}}{1 + A_{DM}} \approx \frac{A_{DD} V_{SD}}{A_{DM}}$$

$$\frac{V_{OUT}}{V_{SD}} \approx \frac{1}{A_{DM}} \text{ PSPICE}$$

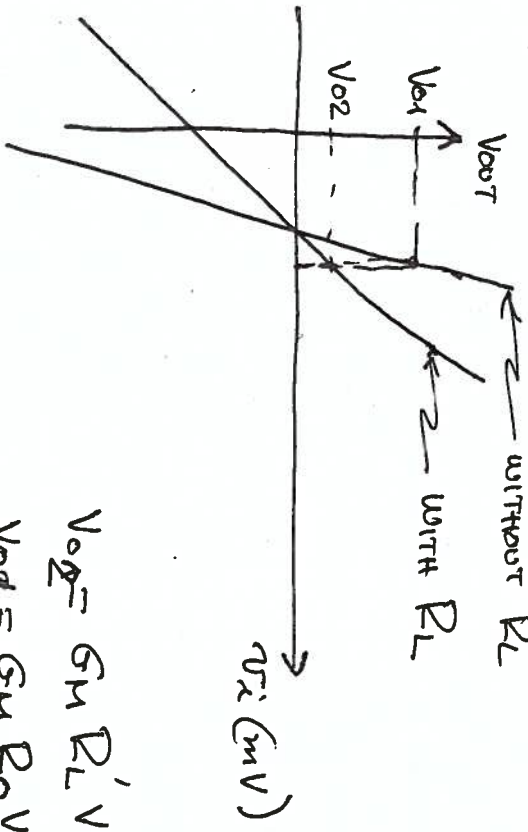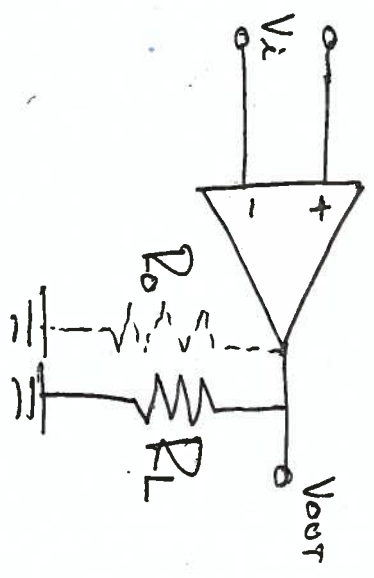- SIMULATING (MEASURING) THE OUTPUT RESISTANCE



$$R_{out} = \left(\frac{V_{o1}}{V_{o2}} - 1 \right) R_L$$

WAY

$$V_{o2} = G_m R_L' V_{in}$$

$$V_{o1} = G_m R_o V_{in}$$



$$\frac{V_{o2}}{V_{o1}} = \frac{1}{1 + \frac{R_o}{R_L}} ; R_L' = R_o // R_L$$

AN ALTERNATIVE WAY IS BY USING FEEDBACK

(B)

$$R_{out} = \frac{R_o}{1 + \beta A} \approx \frac{R_o}{\beta A}$$

- MEASURING SR AND 1% SETTLING TIME

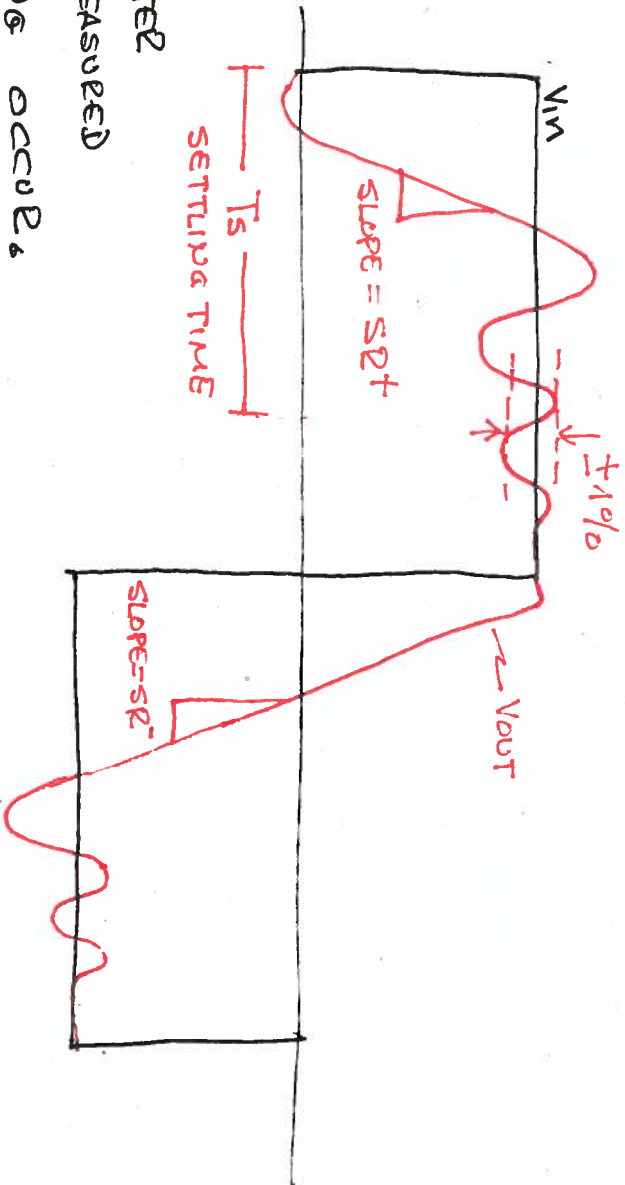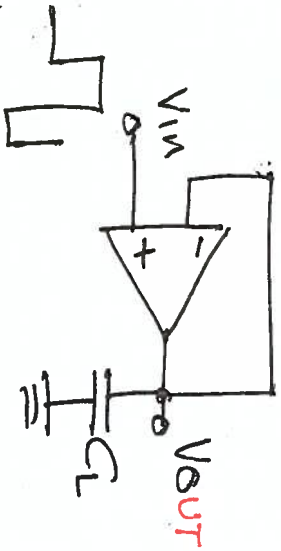

BETTER

NOTE.- T_s CAN BE MEASURED


SUCH THAT NO SLEWING OCCURS.

THAT IS THE OP AMP SHOULD


BE GB LIMITED FOR THIS (T_s)

MEASUREMENT.

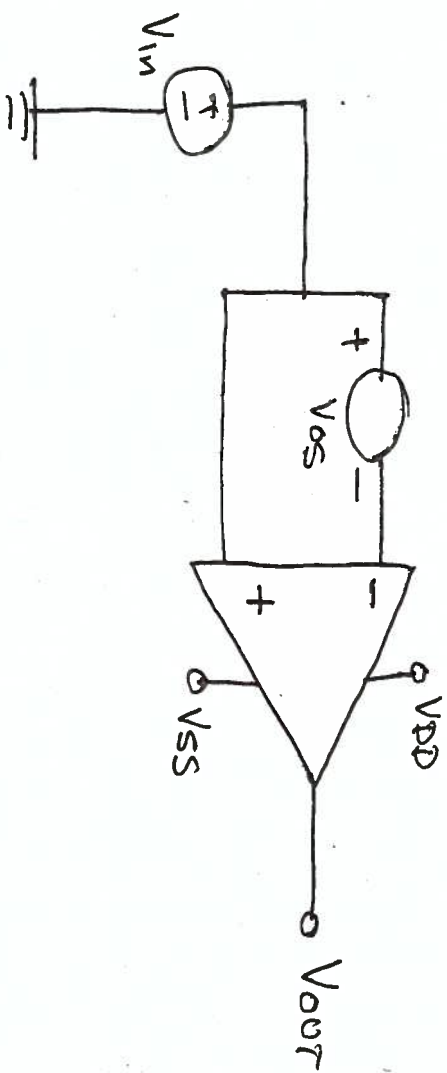~~MEASURING~~ SIMULATING COMMON-MODE GAIN ACM



MEASURING CMRR AND PSRR

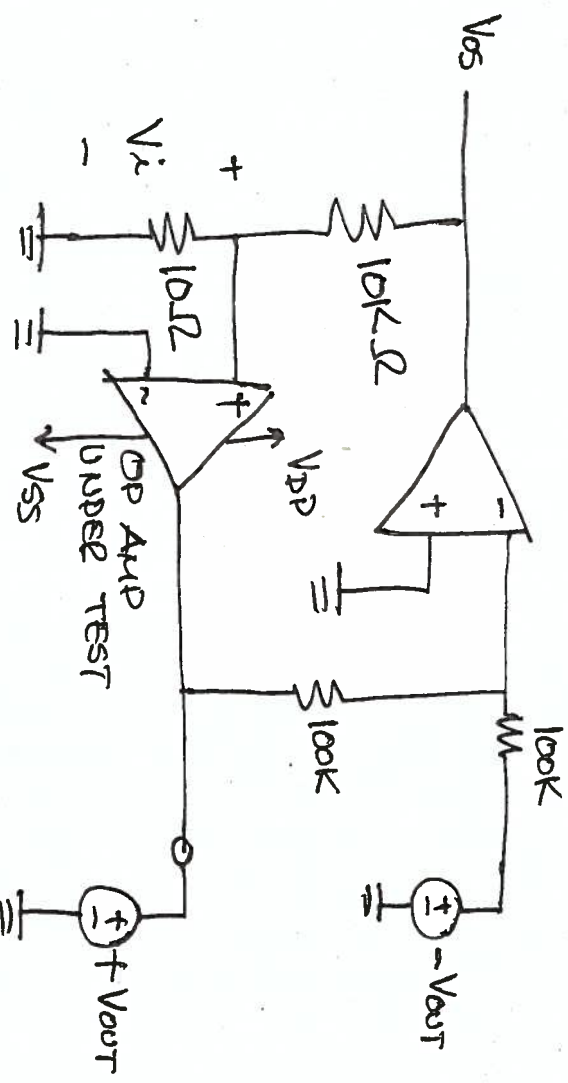

• CMRR
Two measurements:

First
 $V_{DD} \Rightarrow V_{DD} + 1V$
 $V_{SS} \Rightarrow V_{SS} + 1V$
 $-V_{OUT} = -1V$ } V_{OS1}

Second
 $V_{DD} \Rightarrow V_{DD} - 1V$
 $V_{SS} \Rightarrow V_{SS} - 1V$
 $-V_{OUT} = +1V$ } V_{OS2}

$$CMRR = \frac{2000}{|V_{OS1} - V_{OS2}|}$$