

CMOS Multipliers: Architectures and Transistor level Implementations

By Edgar Sánchez-Sinencio

Analog and Mixed-Signal Center, TAMU
607 Spring'12


Multipliers

What is a multiplier?

$$Z = Kxy$$

Where

 x and y are the input signals, Z is the output and K is a constant with suitable dimensions.



How do you obtain a multiplier?

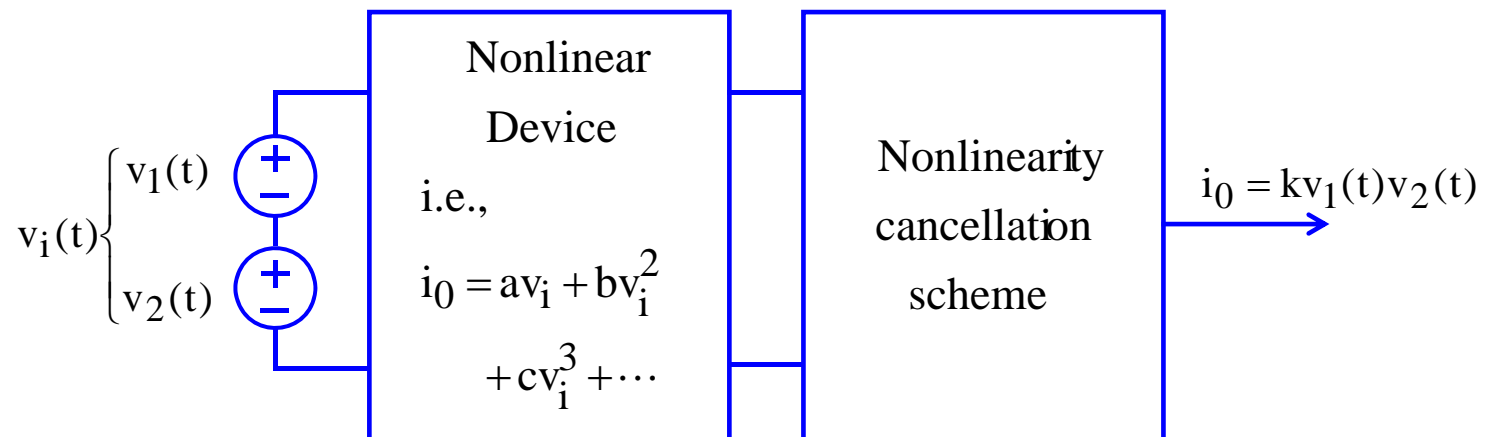


Fig. 1 Basic idea of multiplier

Transconductance-Mode Multiplier

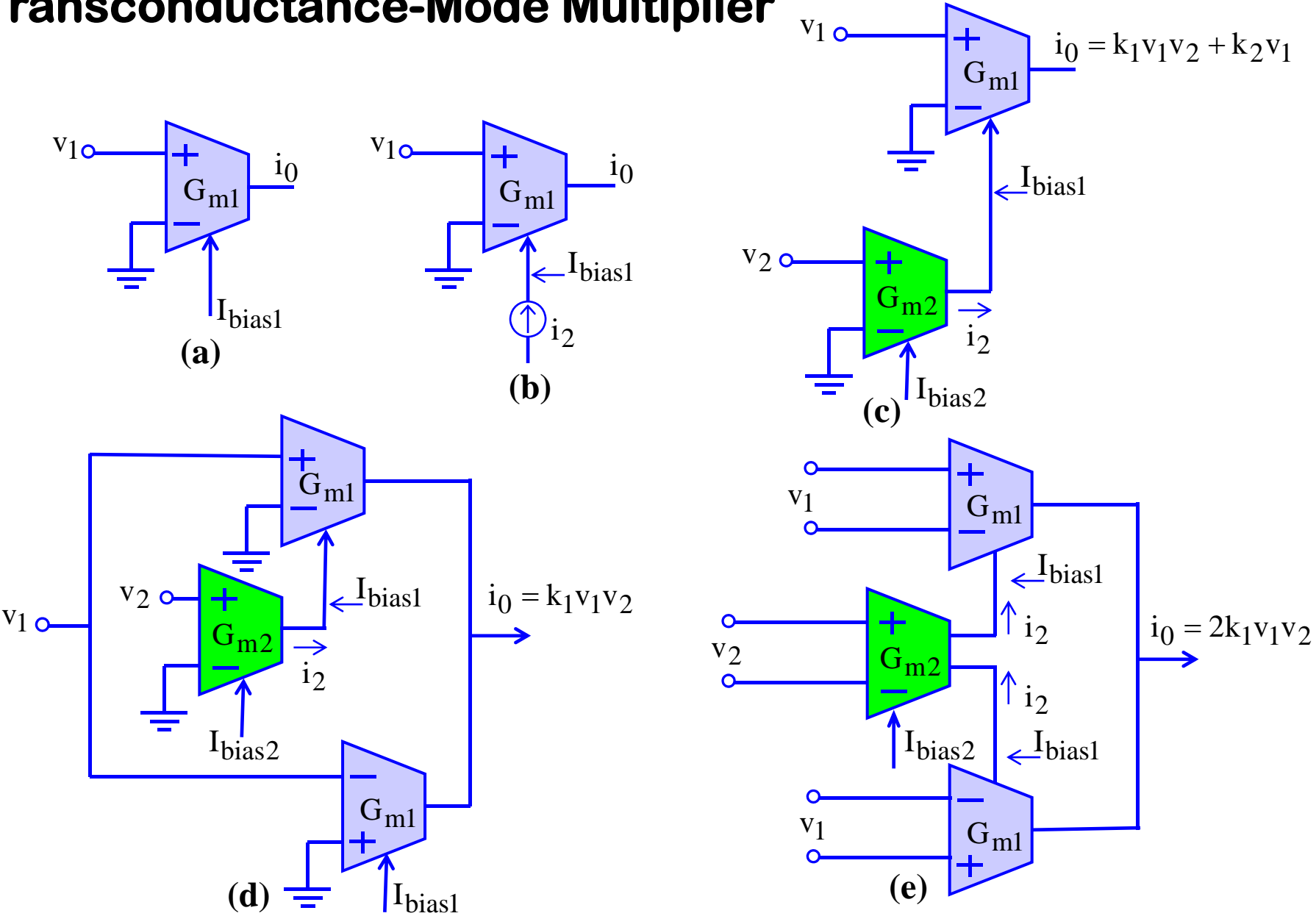


Fig. 2 Multiplication operation using programmable transconductor

How Does It Work?

$$i_0 = G_{m1}v_1 \quad (1)$$

where

$$G_{m1} = G_{m1}(I_{bias1}) \quad (2a)$$

For a bipolar transconductor, G_{m1} becomes

$$G_{m1} = \frac{I_{bias1}}{2V_t} \quad (2b)$$

$$i_0(t) = G_{m1}v_1 = \frac{I_{bias1} + G_{m2}v_2(t)}{2V_t} v_1(t) \quad (3a)$$

$$i_0(t) = \frac{G_{m2}v_1(t)v_2(t)}{2V_t} + \frac{I_{bias1}}{2V_t} v_1(t) = \frac{I_{bias2}v_1(t)v_2(t)}{2V_t 2V_t} + \frac{I_{bias1}v_1(t)}{2V_t} \quad (3b)$$


or

$$i_0(t) = k_1v_1(t)v_2(t) + k_2v_1(t) \quad (3c)$$


Thus, $i_0(t)$ represents the multiplication of two signals $v_1(t)$ and $v_2(t)$, and an unwanted component, $k_2v_1(t)$. This component can be eliminated as shown in Fig. 2(d). Better cancellation is achieved when the third transconductor (G_{m2}) becomes a fully differential transconductor, and v_1 and v_2 are fully differential inputs as illustrated in Fig. 2(e).

$$i_0(t) = 2k_1v_1(t)v_2(t) \quad (4)$$

Basic Multiplier Architectures

 

(a) using single-quadrant multipliers

 

(b) using square devices

Where capital (low case) letters represent DC (time domain) signals.


$$\begin{aligned} & [(X + x)(Y + y) + (X - x)(Y - y)] \\ & - [(X - x)(Y + y) + (X + x)(Y - y)] = 4xy \end{aligned}$$

or

$$\begin{aligned} & \left[\{(X + x) + (Y + y)\}^2 + \{(X - x) + (Y - y)\}^2 \right] \\ & - \left[\{(X - x) + (Y + y)\}^2 + \{(X + x) + (Y - y)\}^2 \right] = 8xy \end{aligned}$$

How the x and y Inputs can be Applied?

Consider a one transistor case first.

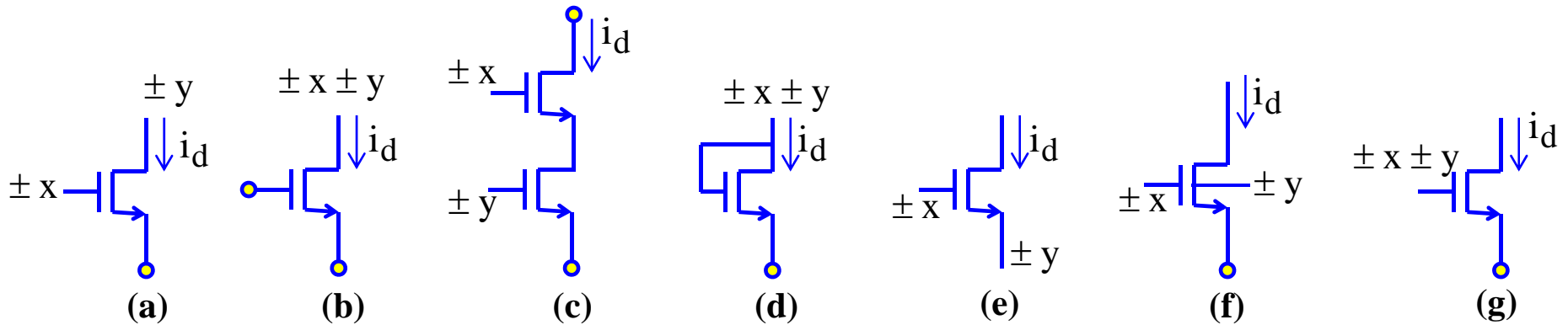

Voltage signal injection methods









The simple MOS transistor model is expressed as :

$$I_d = K \left[V_{gs} - V_T - \frac{V_{ds}}{2} \right] V_{ds} = K \left[V_{gs} V_{ds} - V_T V_{ds} - \frac{V_{ds}^2}{2} \right] \text{ for } V_{gs} > V_T, V_{ds} < V_{gs} - V_T$$

$$I_d = \frac{K}{2} [V_{gs} - V_T]^2 = \frac{K}{2} [V_{gs}^2 - 2V_{gs} V_T - V_T^2] \text{ for } V_{gs} > V_T, V_{ds} > V_{gs} - V_T$$





Results are summarized next.

Table 1. Summary of multiplier operating modes

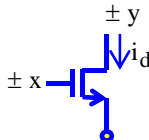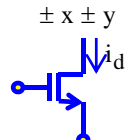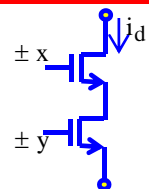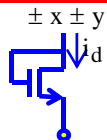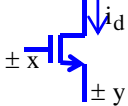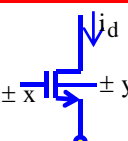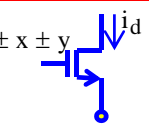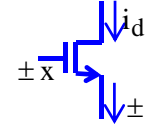Operating region	Input signal injection method	Active term	Cancellation method	Type	Comment
Linear		$V_{gs} V_{ds}$	single-quadrant	I	
		V_{ds}^2	square device	II	Not practical
		$V_{gs} V_{ds}$	single-quadrant	III	Not practical
Saturation		V_{gs}^2	square device	IV	Not practical
		V_{gs}^2	square device	V	
		V_{gb}^2	square device	VI	Not practical
		V_{gs}^2	square device	VII	
		V_{gs}^2	Gilbert cell (single-quadrant)	VIII	



Let us describe multipliers as functions of their mode of operations

- Linear Mode

    

Programmable transconductor in ohmic operation

Using V_{gs} V_{ds} (Type I)

  

Four-quadrants multipliers with two transistors operating in linear region

Multiplier Implementations Using $V_{gs} V_{ds}$ (Type I)


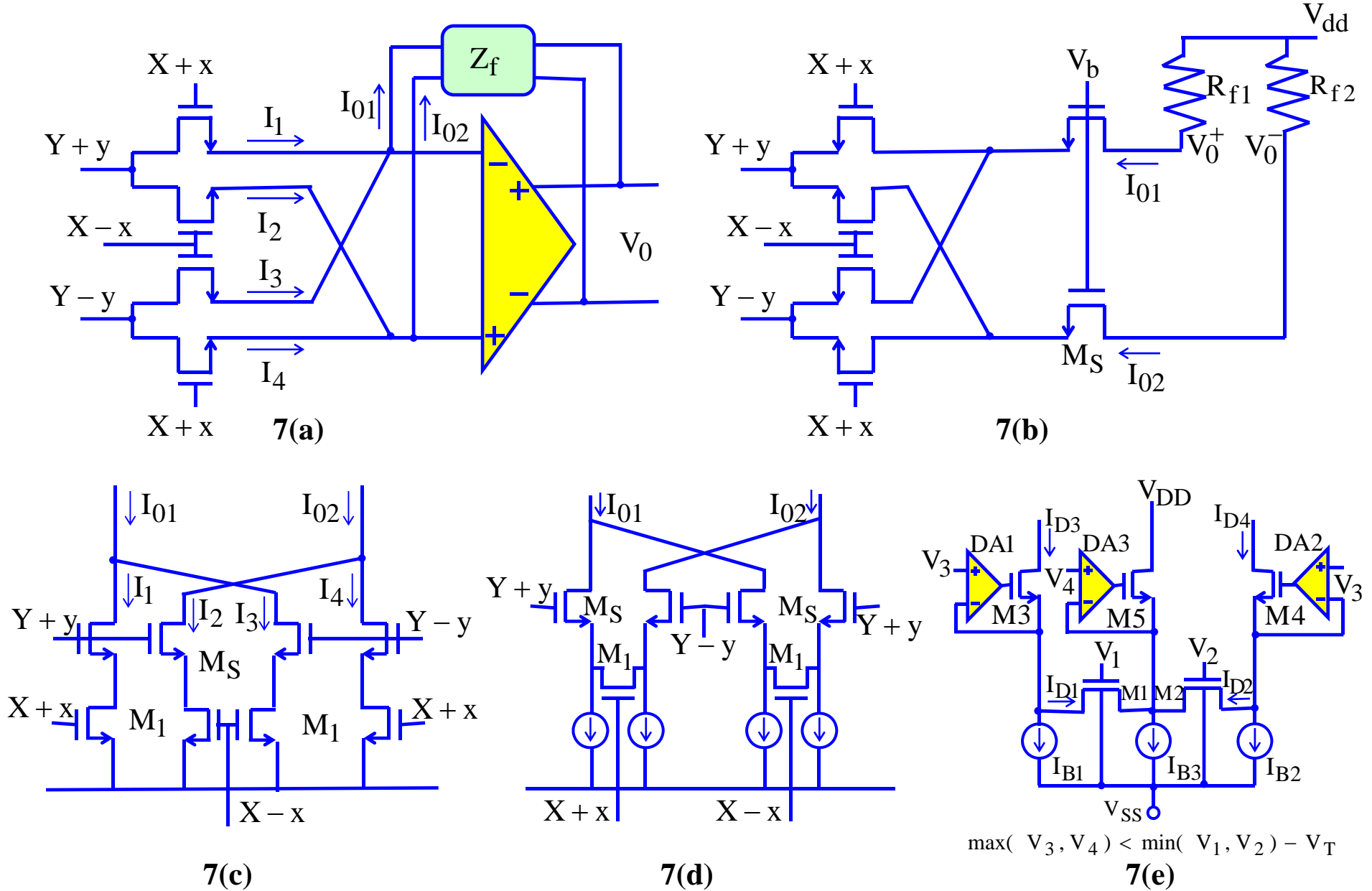


Fig. 7 Fully-differential four-quadrant multipliers using $V_{gs}V_{ds}$ term (Type I)

Example of a Complete Implementation of Multiplier $V_{gs} V_{ds}$ Type I. {From Fig. 7(e)}

$\pm 3V$ supply voltages

$2\mu\text{m}$ technology

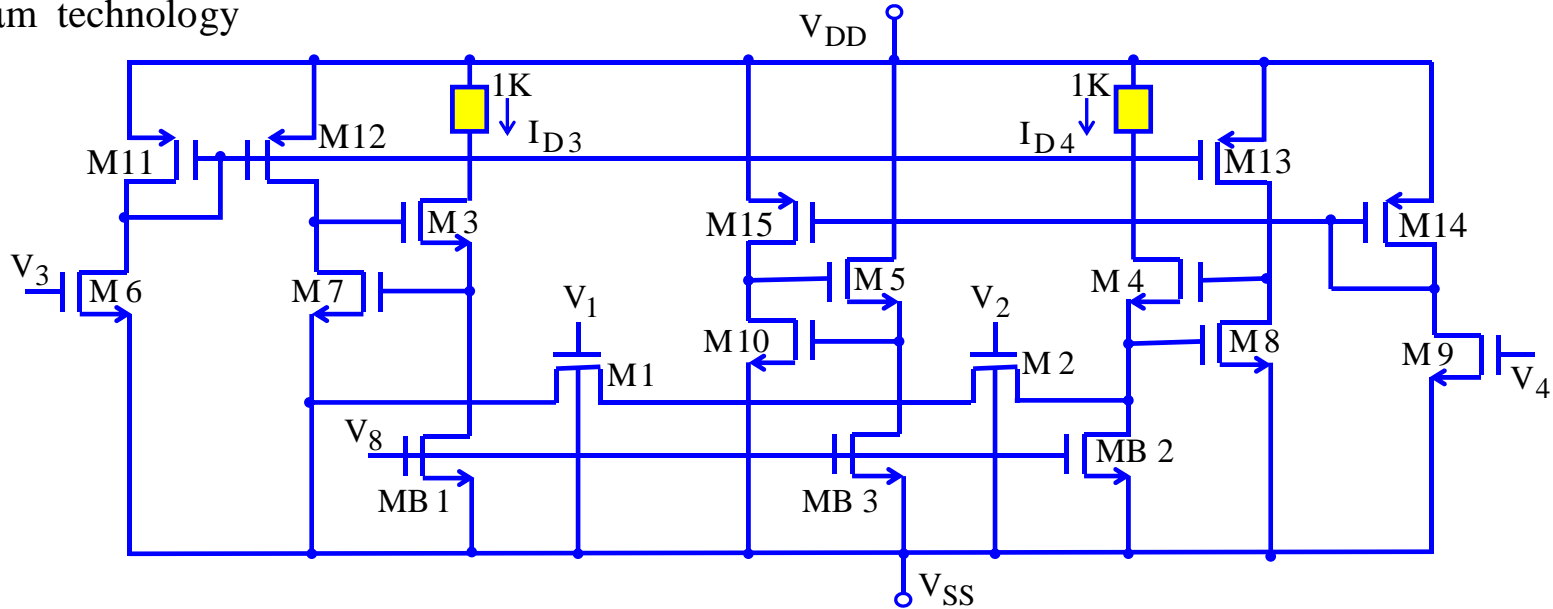

Transistors	M1 – M2	M3 – M5	M6 – M10	M11 – M15	MB 1 – MB 3
$W[\mu\text{m}]/L[\mu\text{m}]$	10/50	100/5	10/10	50/5	10/10

$$I_{D3} = I_{B1} + I_{D1} = I_{B1} + 2K_1 \left[(V_{GS1} - V_{T1})V_{DS1} - \frac{1}{2} V_{DS1}^2 \right] \quad (1)$$

and

$$I_{D4} = I_{B2} + I_{D2} = I_{B2} + 2K_2 \left[(V_{GS2} - V_{T2})V_{DS2} - \frac{1}{2} V_{DS2}^2 \right] \quad (2)$$


It is evident th at M1 and M2 have the same drain and source voltages. Thus $V_{DS1} = V_{DS2}$ and $V_{T1} = V_{T2}$

Now, let $K_1 = K_2 = K$ and $I_{B1} = I_{B2} = I_B$. The output current I_{out} can then be written as :

$$I_{out} = I_{D3} - I_{D4} = I_{D1} - I_{D2} = 2K(V_1 - V_2)(V_3 - V_4) \quad (3)$$


Low voltage multiplier working with transistors in linear region. (Coban & Allen)

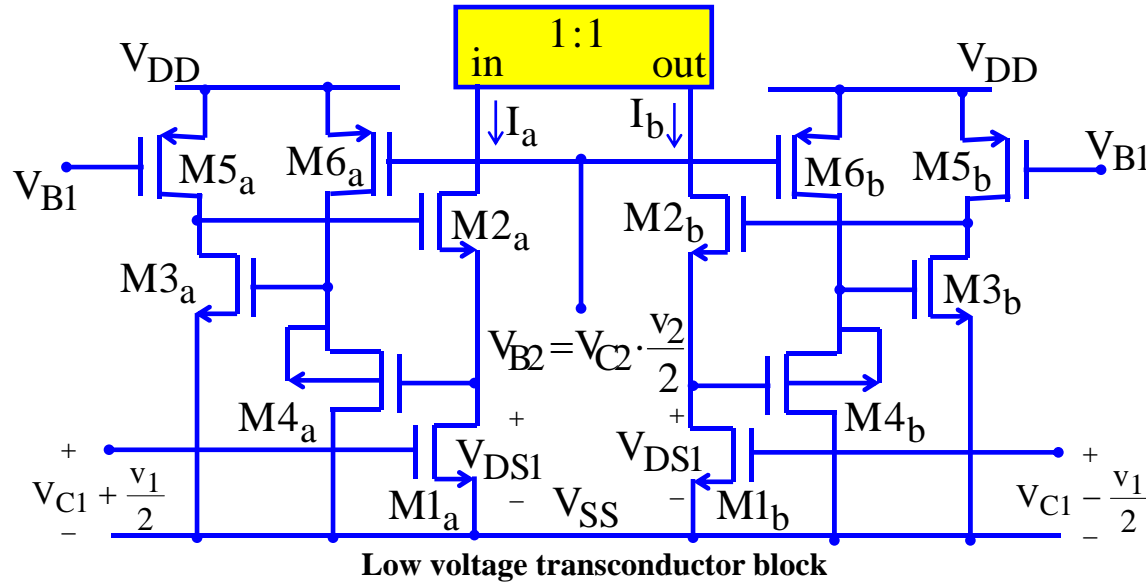- One single 1.5V supply
- $M1_a$ and $M1_b$ in linear range. $I_1 \cong K_1 v_1 V_{DS}$
 $I_0 = I_1 - I_1' = K v_1 v_2$ requires two of the following transconductors.
 with $K = K_1 \sqrt{K_6 / K_4}$




- Use composite transistor.
- Based on the regulated cascode circuit.

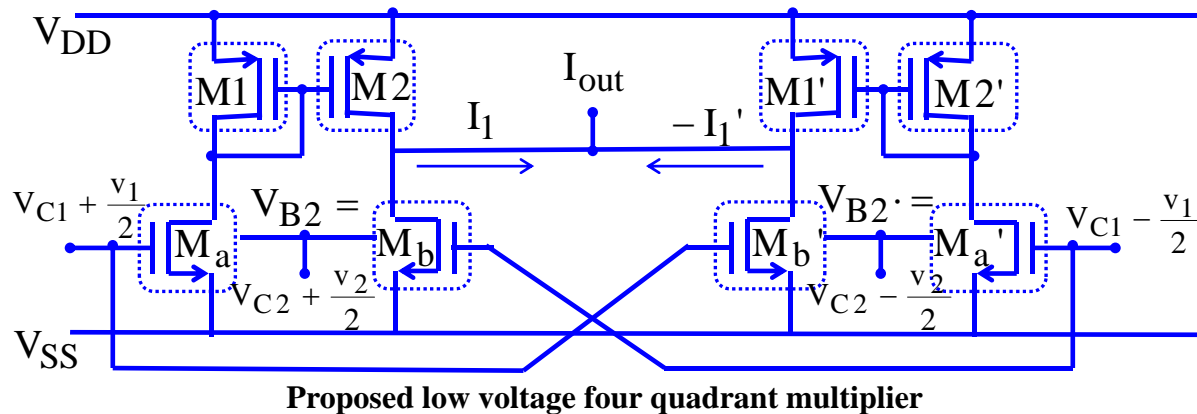- The complete circuit with composite transistors drawn as single transistors.



 Multiplier Using a Transistor in the Linear Range



M1 Operating in the linear (OHMIC) region


$$I_D = K_P \left(\frac{W}{L} \right) \left[V_{GS} - V_T - \frac{V_{DS}}{2} \right] V_{DS}$$

$$I_D = K_P \left(\frac{W}{L} \right) \left[V_{GS} V_{DS} - \left(V_T + \frac{V_{DS}}{2} \right) V_{DS} \right]$$

For $V_{DS} \ll V_{GS}$, I_D Becomes:

$$I_D \cong K_P \left(\frac{W}{L} \right) V_{GS} V_{DS} + \Delta I_D, \quad \Delta I_D \sim 0$$

 How to sense the drain current while at the same time provide the input voltage at the same node?



$$i_0 = k i_{in}$$


M3 acts as a voltage follower, i.e.

$$A_{V3} = \frac{1}{1 + g_{mb3} / g_{m3}}$$


M3 input voltage range is limited due to the feedback connection of M7, therefore it is needed to be boosted with a level shifter.

$$\frac{f_{nd}}{GBW} \cong \frac{V_{GS3} - V_{T3}}{V_{GS5} - V_{T5}} \cdot 2$$

A possible implementation follows:

 


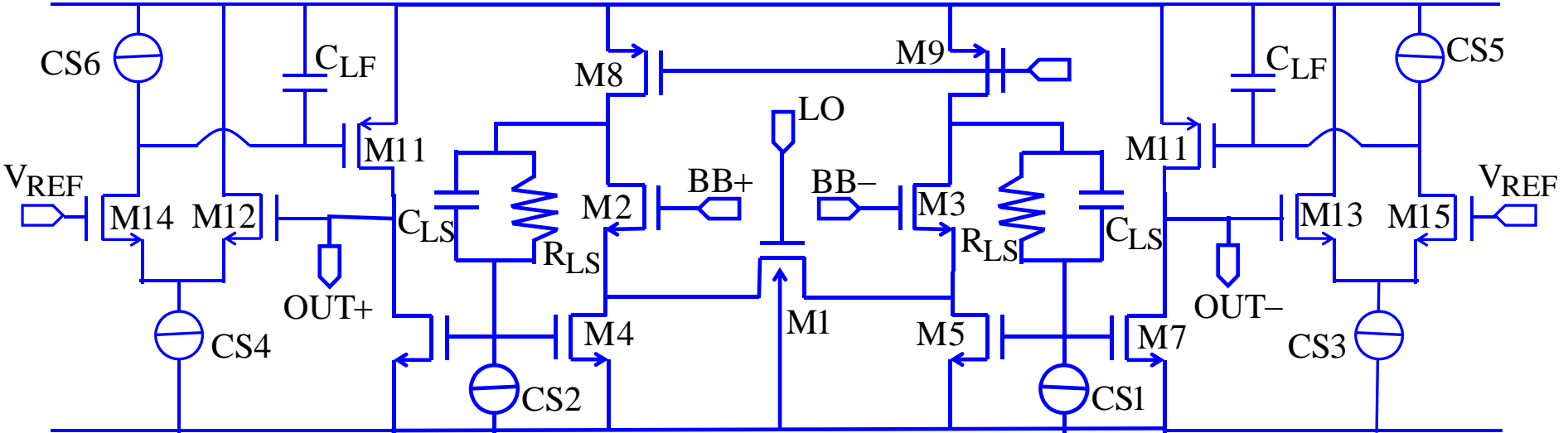Version 1 of a complete multiplier (mixer)



The differential linear up-conversion mixer; the single ended carrier signal is applied at the LO terminal and the differential baseband signal is applied at the BB terminals. The baseband modulation feedthrough in the output signal is suppressed through the output circuits (thin lines) which act as active coils

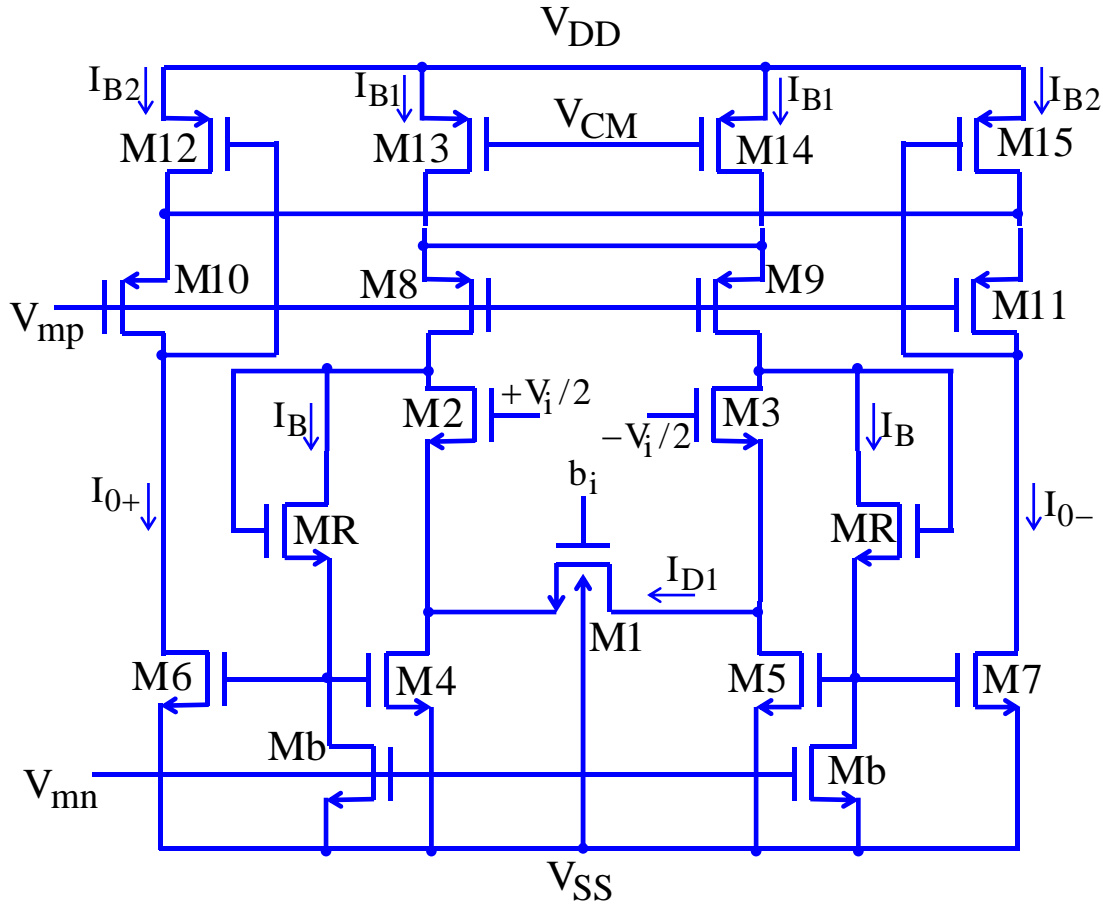Version 2: Multiplier Using Cascode Current Source.



Switching Modulator Based on Linear MOS

For $M2 = M3$

$$+V_1^+ - V_{S1} = V_{T0} + \sqrt{\frac{I_{B1}}{K_p(W/L)_2}}$$

$$V_1^- - V_{D1} = V_{T0} + \sqrt{\frac{I_{B1}}{K_p(W/L)_3}}$$

Thus for $V_1^+ = V_i/2$ and $V_1^- = -V_i/2$

$$V_{DS1} = -\frac{V_i}{2} - \frac{V_i}{2} = -V_i$$

Neglecting ΔI_D , it yields:

$$I_{D1} = K_p(W/L)_1$$

M4, M6 and M5, M7 act as CM, then

$$I_0^+ = K_p(W/L)_1 \frac{(W/L)_6}{(W/L)_4} \left[V_i \left(b_i - \frac{V_i}{2} \right) \right]$$

$$I_0^- = -K_p(W/L)_1 \frac{(W/L)_7}{(W/L)_5} \left[V_i \left(b_i - \frac{V_i}{2} \right) \right]$$

$$I_{0d} = \frac{I_0^+ - I_0^-}{2} = K_p \left(\frac{W}{L} \right)_1 \frac{(W/L)_{6,7}}{(W/L)_{4,5}} \left[2V_i b_i - V_i^2 \right]$$

$$I_{0d} \cong K_p \left(\frac{W}{L} \right)_1 \frac{(W/L)_{6,7}}{(W/L)_{4,5}} \left[V_i \cdot b_i \right] \quad \text{for } V_i \ll b_i$$

Linear Operation using V_{ds}^2 (Type II)


 


Fig. 8 Multiplier using V_{ds}^2 (Type II)

$$I_0 = I_{01} - I_{02} = Kxy$$

 

A possible summer implementation

Dual Gate in Linear Range (Type III)

$M_{d1} = M_{d2}$ in saturation region

M1 & M2 in Linear Region. Where $V_{pol} \cong \sqrt{\frac{I_{pol}}{K_d}}$ for $I_d \ll I_{pol}$

and $C = V_{com} - V_S - V_T - V_{pol}$ and $C \gg x, y$


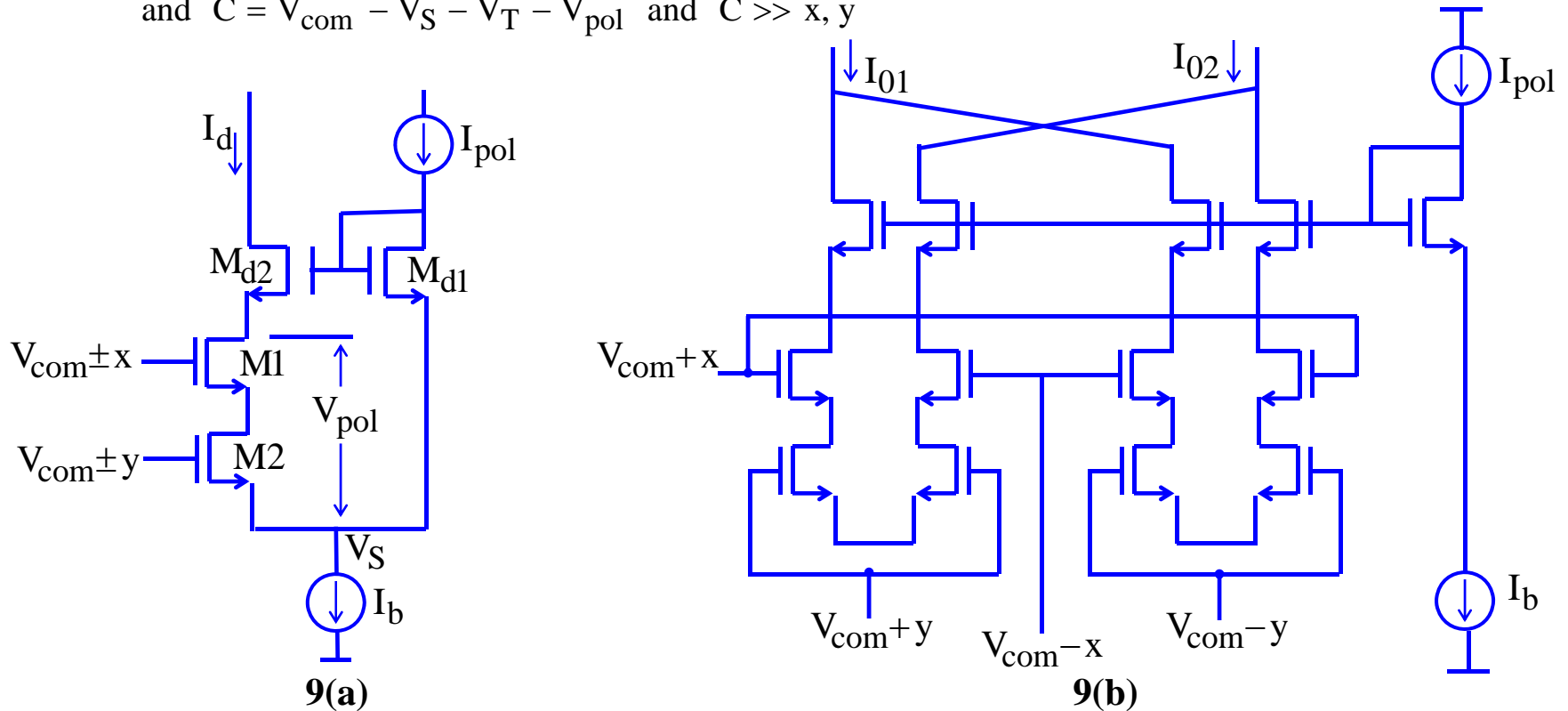


Fig. 9 Four quadrant multiplier using dual gate (Type III)

$$I_0 = I_{O1} - I_{O2} = 8KV_{pol}cxy \frac{x^2 + y^2 - 2c^2}{(4c^2 - (x + y)^2)(4c^2 - (x - y)^2)}$$

$$I_0 \cong \frac{KV_{pol}}{c} xy$$

 MOS Multipliers Operation in Saturation Region



Four cross coupled FETs multiplier

using V_{gs}^2 term. (Type V)

Based on the $4xy$ architecture

$$I_0 = I_{01} - I_{02} = 4Kxy$$



 


Fig.10 Multiplier using V_{gs}^2 with diode connection (Type IV)

 
Alternative Signal Injection Implementations using V_{GS}^2




12(a) Using OP Amp

 

12(b) Using a linear differential amp

 

12(c) Using source followers

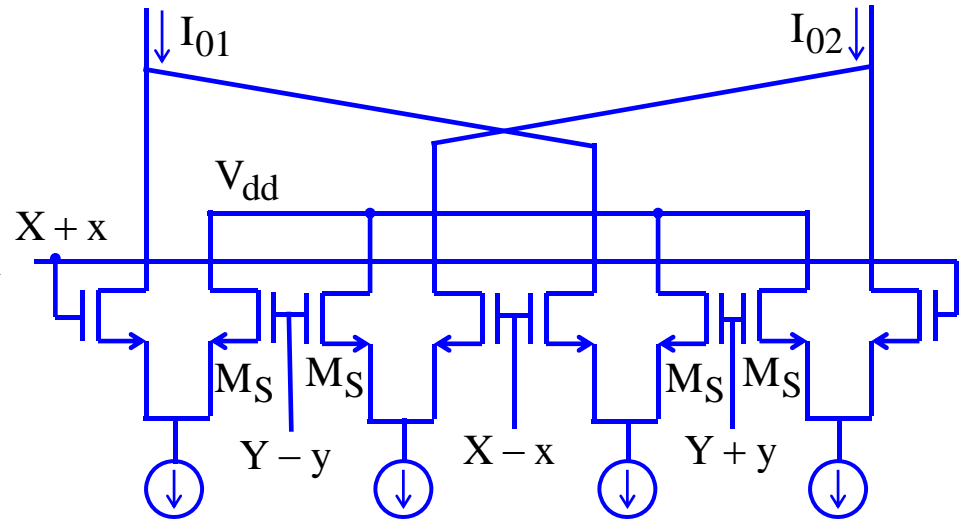

12(d) A separate follower for each cross-coupled transistor

Fig. 12 Source signal injection methods for multiplier using V_{gs}^2 term (Type V)

Bulk-Driven Transistor Using V_{gs}^2 (Type VI)

 



Fig. 13 Using substate signal injection (Type VI)

$$V_T = V_{T0} + \gamma \sqrt{2|\phi_F| - V_{bs}} - \sqrt{2|\phi_F|}$$


$$I_0 = I_{02} - I_{01} = \frac{4K\gamma}{2|\phi_F| - Y + s} \left[y \sqrt{2|\phi_F| - Y + s} + \left\{ \frac{y}{2(2|\phi_F| - Y + s)} \right\}^3 \right] x$$

$$I_0 \cong \frac{4K\gamma}{\sqrt{2|\phi_F| - Y + s}} xy \quad \text{for } 2|\phi_F| - Y + s \gg y$$

Voltage Adder (Type VII) using V_{gs}^2

 

14(a) with tail current

 

14(b) without the tail current

Fig. 14 Multipliers using voltage adder (Type VII)

This implementation is based on the $()^2$ cancellation scheme. Summers can be implemented with (i) resistors, (ii) capacitors, or (iii) active adders.

Floating Voltage Source (Type VII) Using V_{gs}^2

 



Fig. 15 Multiplier using floating voltage source (Type VII)

MOS Gilbert Cell (Type VIII)

Analysis:

One MOS differential pair yields $I_{0d} = I_{01} - I_{02} = 2\sqrt{KI_s}x \left(1 - \frac{Kx^2}{I_s}\right)^{\frac{1}{2}}$

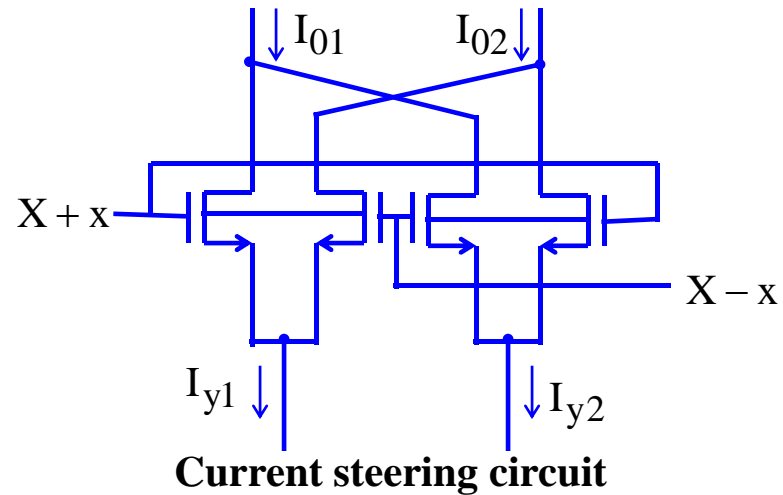In what follows x is a voltage signal and $y(I_y)$ is a current signal



For the two differential pairs, we obtain :

$$I_0 = I_{01} - I_{02} = 2\sqrt{K}x(\sqrt{I_{y1}} - \sqrt{I_{y2}})$$

Note that $\sqrt{I_{y1}} - \sqrt{I_{y2}}$ is generated by a third differential pair as shown next. Thus


$$\sqrt{I_{y1}} - \sqrt{I_{y2}} = y\sqrt{2K_3}$$

Thus


$$I_0 = I_{01} - I_{02} = 2xy\sqrt{2KK_3}$$

Here both x and y are voltage signals.

MOS Gilbert Multiplier Implementations

 

17(a) with tail current

 

17(b) without tail current

Fig. 17 MOS Gilbert multipliers (Type VIII)

- Improvement of this cell involve linearization of the differential pairs, folded architectures or active attenuators.
- This structure might not be suitable for low power supplies.


Comparisons

A specific comparison is application dependent. A limited qualitative and through simulation are discussed next.


Table 2. Summary of general qualitative comparison of 15 multiplier topologies.

NO.	Type	Circuit Diagram Figure	Worse than	Remark
1	I	7(a), 7(b)	2	Require additional circuitry.
2	I	7(c),7(d)		
3	II,III,IV	8, 9, 10	2	Require additional circuitry. Poor linearity.
4	V	12(a)	5	Require OP Amp
5	V	12(b), (c), (d)		
6	VI	13	5	Poor linearity
7	VII	14, 15	5	Require additional circuitry.
8	VIII	17	2	High power supply voltage. Poor linearity.

THD Comparisons


 


 Simulated Total Harmonic Distortion(THD) for W/L= 10 μ m/10 μ m for all transistors.



Effect of source follower's W/L ratio on THD

Linearity Comparison

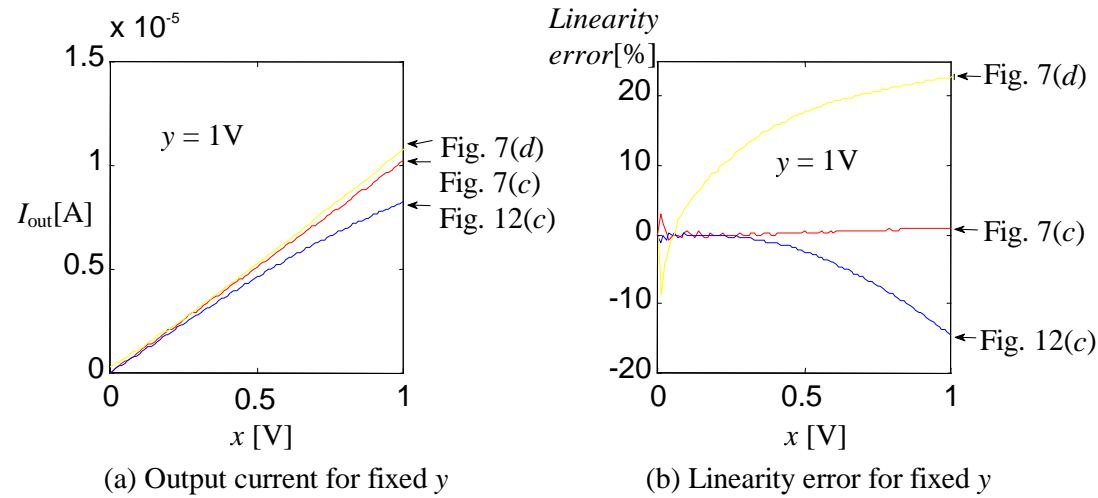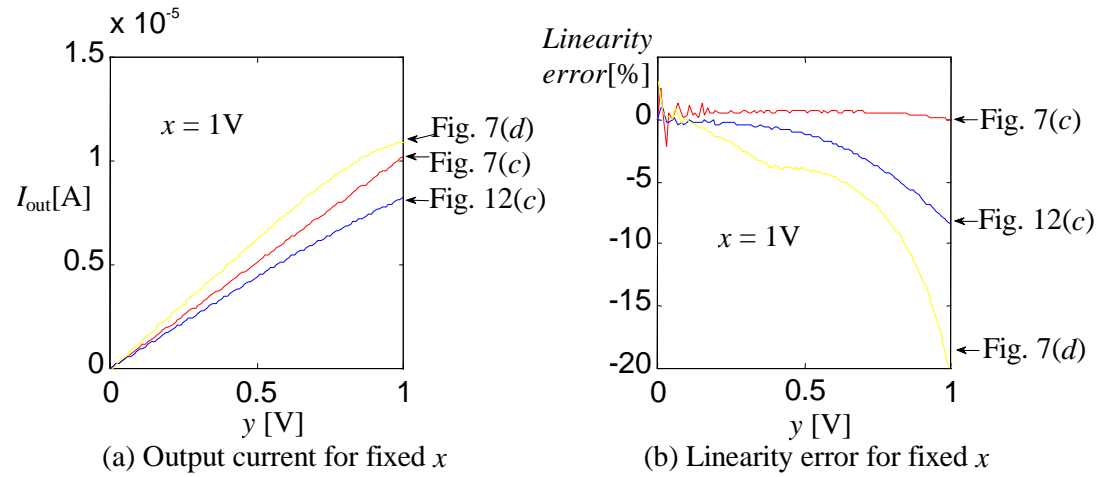

Measurement results for $W/L_{m1} = 5\mu\text{m}/17\mu\text{m}$ and $W/L_{\text{source follower}} = 50\mu\text{m}/10\mu\text{m}$.

$g_m = 10\mu\text{A}/\text{V}$, 360 μW consumption, $x, y = \pm 2\text{V}$
 2 μm CMOS technology.

Input Range and Minimum Power Supply

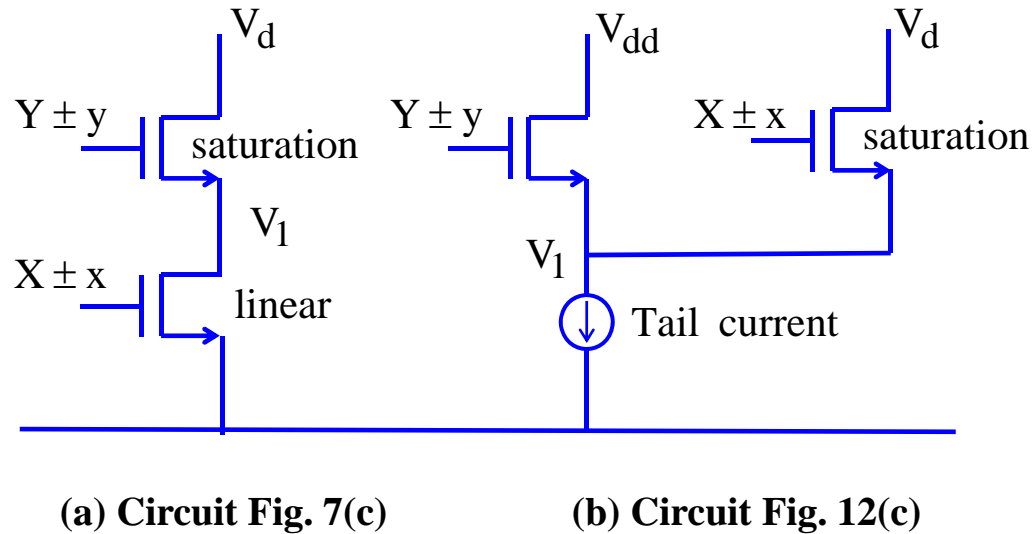


Fig. 24 Bias conditions

For Fig. 7(c):

$$V_T < X \pm x$$

$$V_1 = Y \pm y - V_T < X \pm x - V_T$$

$$V_T < Y \pm y$$

$$Y \pm y - V_T < V_d$$

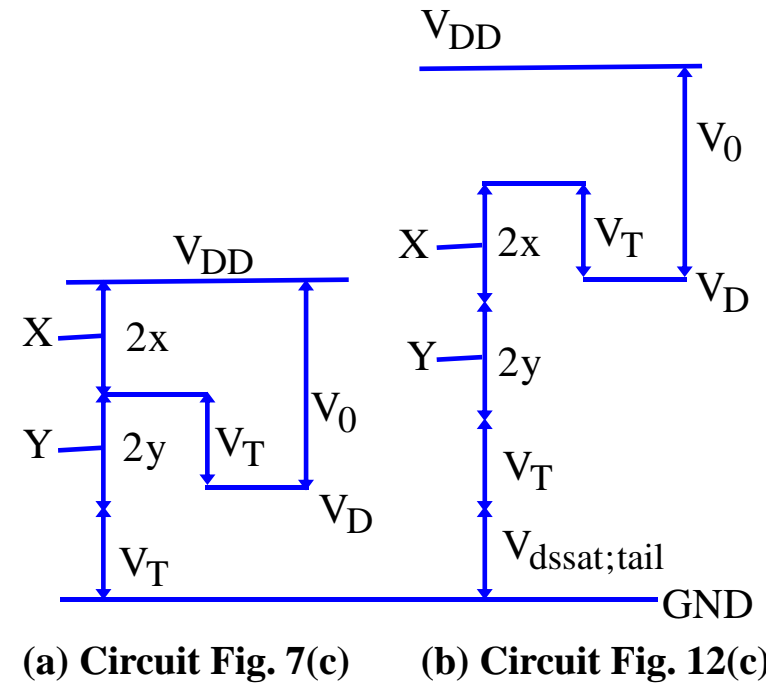


Fig. 25 Input range and power supply voltage

For Fig. 12(c)

$$V_{ds\ sat; tail} < V_1 = Y \pm y - V_T$$

$$V_1 + V_T = Y \pm y < X \pm x$$

$$X \pm x - V_T < V_D$$


Table 3. Summary of a comparative multiplier study for equal size transistors.

Circuit	Max G_m [$\mu\text{A/V}$]	Power Consumption[mW]	Mismatch Sensitivity	Linearity x	Linearity y
Fig. 7(c)	20	238	Good	Good	Bad
Fig. 7(d)	4.6	270	Bad	Good	Bad
Fig. 12(b)	5	200	Worst	Bad	Bad
Fig. 12(c)	40	295	Best	Bad	Best
Fig. 12(d)	25	480	Good	Worst	Worst


Table 4. Summary of comparison between circuit Fig. 7(c), Fig. 7(d), and Fig. 12(c)

Circuit	Linearity	Minimum Power Supply	Noise
Fig. 7(c)	Good	Good	Good
Fig. 7(d)	Bad	Bad	Bad
Fig. 12(c)	Good	Bad	Bad

Noise Consideration for Fig. 7(c).

 

(a)

 

(b)

Fig. 26 Noise dependency on $(W/L)_1$ for $(X+Y)/2 = 4$ volt and $X-Y = 2$ volt.

A Low Voltage Low Power CMOS Analog Multiplier

by Amir H. Miremadi*, Ahmad Ayatollah, Adib Abrishamifar (IUST)E-mail:
amirh_miremadi@yahoo.com.a-miremadi@wtiau.ac.ir

 


Fig. 1. Multiplier Core.

$$I_{OUT} = (I_{D1} + I_{D3}) - (I_{D2} + I_{D4}) \quad (5)$$

$$= 2aK_1(V_1 - V_2)(V_3 - V_4)$$

From Fig. 1, The multiplier core requires the input signals $V_4 + aV_1 + b$, $V_3 + aV_1 + b$, $V_3 + aV_2 + b$ and $V_4 + aV_2 + b$ which are applied to the gate terminals where a and b are constants.

 



Fig. 2. Flipped Voltage follower cell.

$$V_Z = V_M + \sqrt{\frac{K_5}{4K_6}} V_P - V_B \quad (12)$$

The input signals V_1 and V_4 are applied to P and M nodes, respectively. Therefore, the output voltage V_{D1} can be rewritten as

$$V_Z = V_4 + aV_1 + b \quad (13)$$
 
$$\text{Where } a = \sqrt{\frac{K_5}{4K_6}} \text{ \& } b = -V_B$$



The developed flipped voltage follower cell.

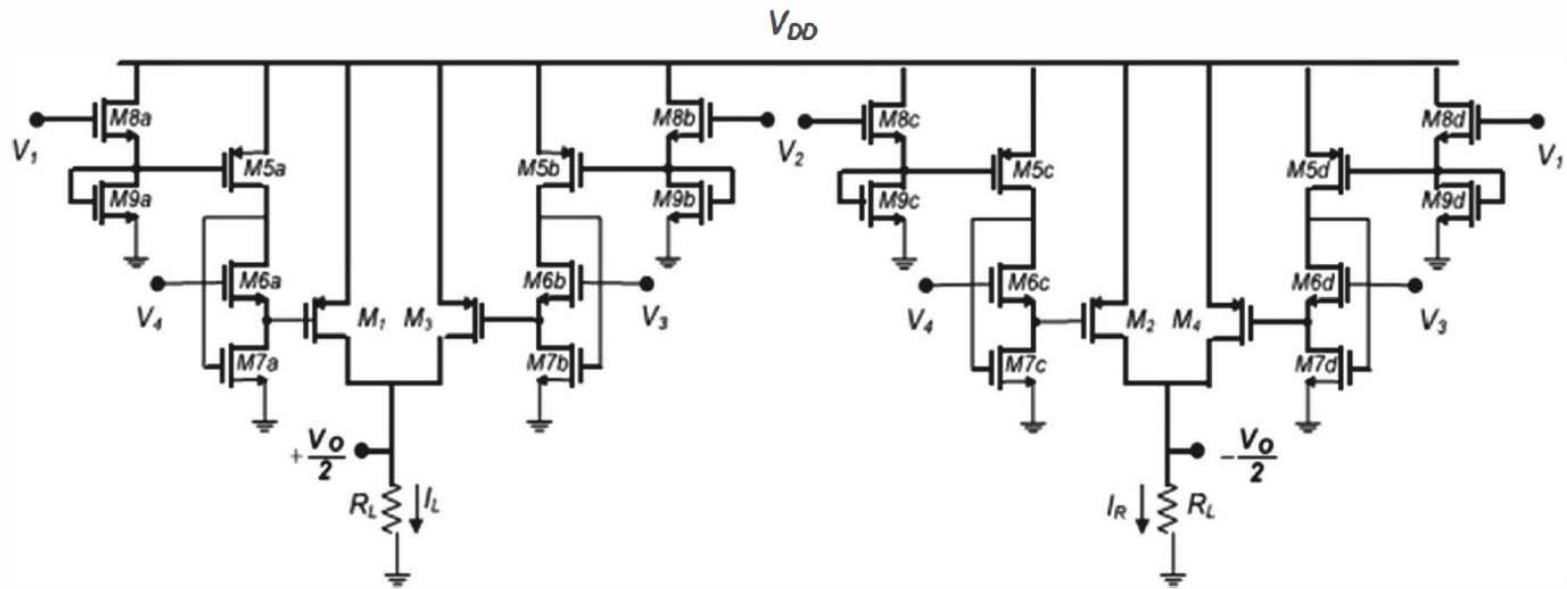




Fig. 4. The circuit diagram of the proposed analog multiplier.

A low voltage low power CMOS analog multiplier has been presented. The proposed multiplier works with a single supply of 0.9V and low power consumption ($58\mu\text{W}$). It has linearity error less than 1.8% for linear range 400mVp-p.


THD is smaller than 0.88% under the maximum-scale input 400mVp-p at both inputs.

MIXERS


Simple switch
used as a mixer

  

 
Implementation of switch
with an NMOS device




Active Mixer

 

 
Folding RF and image noise into the IF band




Downconversion of an AM Signal

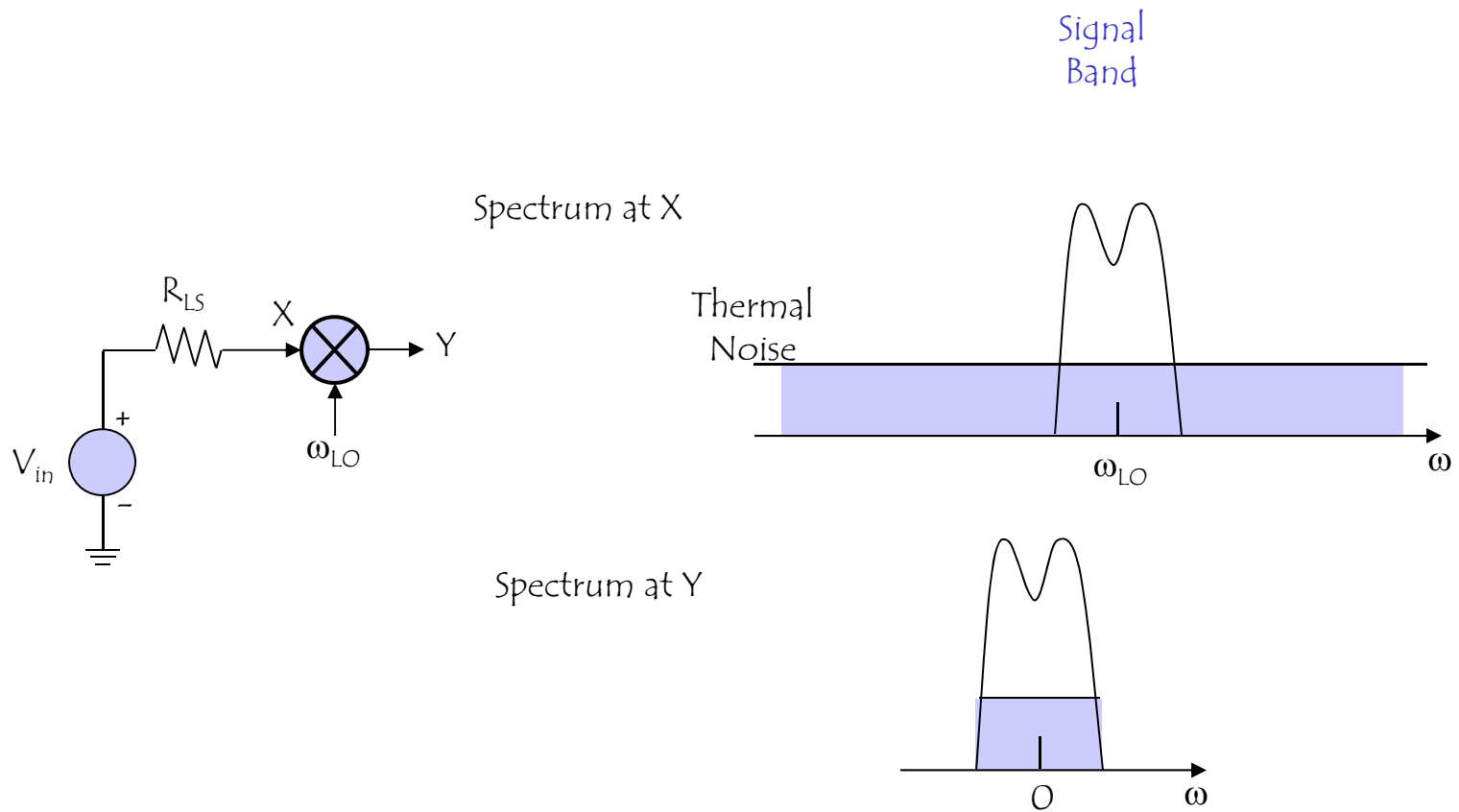


Single-balanced mixer

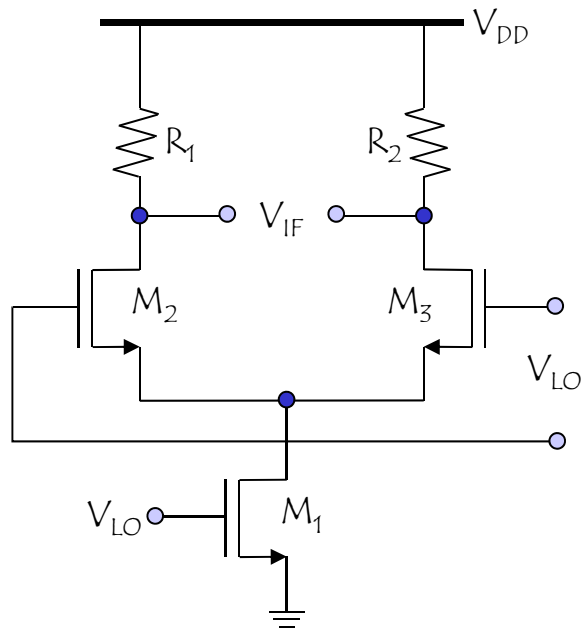


Double-balanced mixer

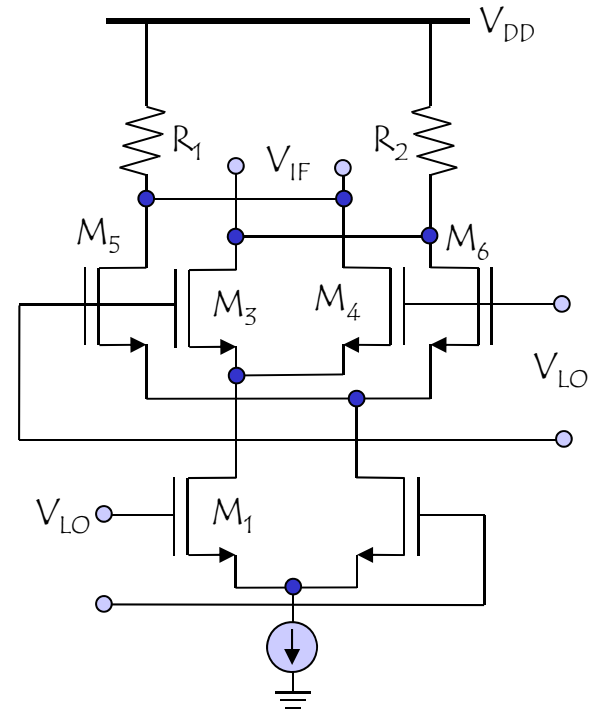


Sections of a mixer

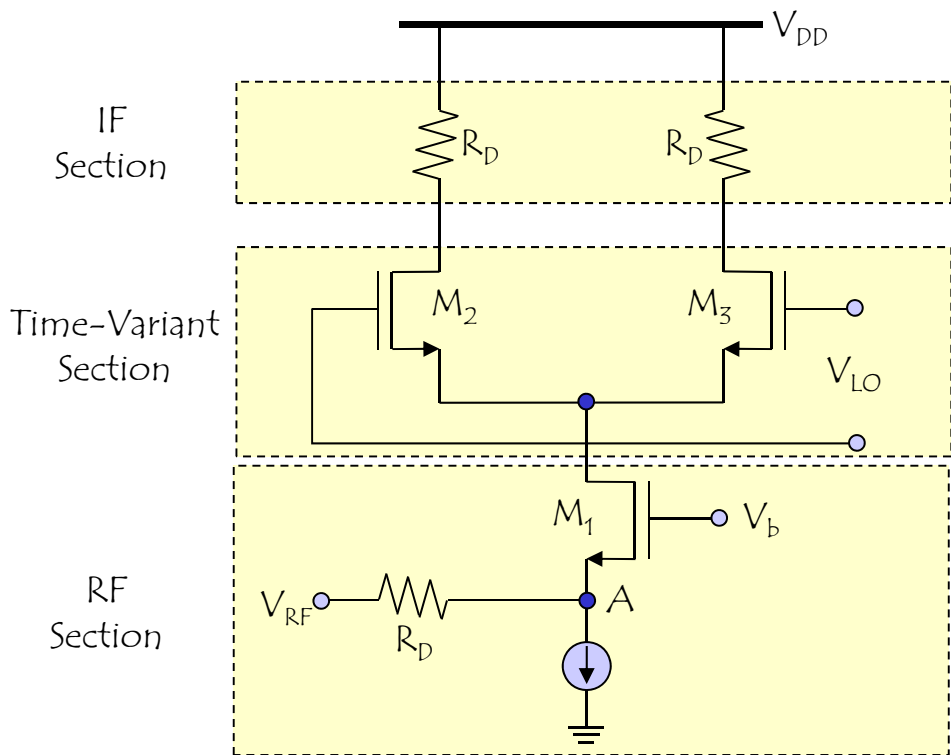


Modeling the noise in the RF section

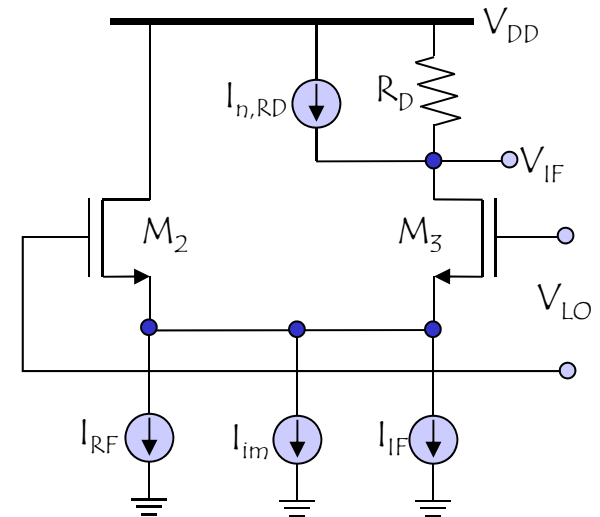

 
Modeling the noise in the time-variant section




Simple mixer with single-ended output

 

Simple mixer with differential outputs

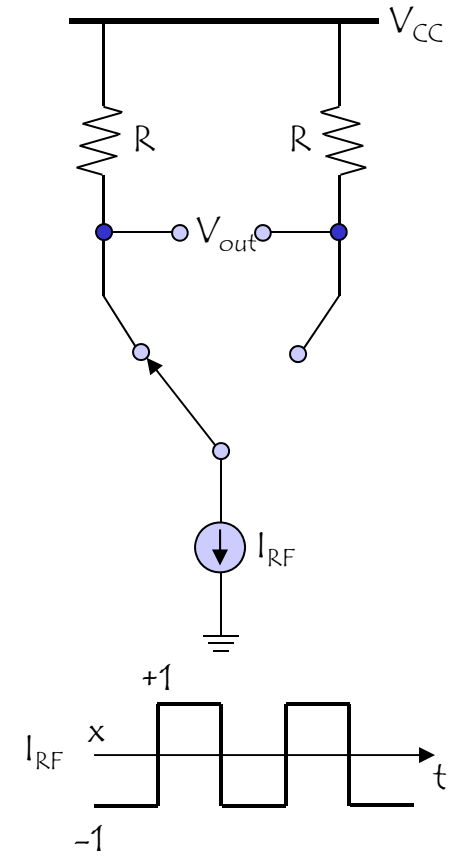

 Conversion of differential currents to single-ended outputs



- ◊ Most mixers need to be single-ended because the IF SAW filters are single ended devices.

References

- [1] G. Han and E. Sánchez-Sinencio, “CMOS Transconductance Multipliers: A Tutorial”, *IEEE Trans. on Circuits and Systems II*, vol. 45, No. 12, pp. 1550-1563, December 1998.
- [2] F.N. Trofimenkoff and R.E. Smallwood, “Four Quadrant JFET Multipliers”, *IEEE J. Solid-State Circuits*, pp. 316-319, June 1977.
- [3] Z. Czarnul and S. Takagi, “Design of Linear Tunable CMOS Differential Transconductor Cells”, *Electron. Lett.*, vol. 26, pp. 1809-1811, 1992.
- [4] Z. Czarnul, “Modification of Banu-Tsividis Continuous-Time Integrator Structure”, *IEEE Trans. on Circuits and Systems*, vol. CAS-33, No. 7, pp. 714-716, July 1986.
- [5] J-H Tsag et al, “CMOS Four-Quadrant Multiplier Using Triode Transistors Based on Regulated Cascode Structure”, *Electron Lett.*, vol. 31, pp. 962-963, June 1995.
- [6] B. Razavi, “RF Microelectronics”, Prentice Hall, 1998.

Recent References on Multipliers

- Zhuo Zou, Mendoza, D.S., Peng Wang, Qin Zhou, Jia Mao, Jonsson, F., Tenhunen, H., Li-Rong Zheng, "A Low-Power and Flexible Energy Detection IR-UWB Receiver for RFID and Wireless Sensor Networks", *Circuits and Systems I: Regular Papers, IEEE Transactions on*, On page(s): 1470 - 1482 Volume: 58, Issue: 7, July 2011
2. Weiwei Shan, Yuan Ma, Newcomb, R.W., Dongming Jin, "Analog Circuit Implementation of a Variable Universe Adaptive Fuzzy Logic Controller", *Circuits and Systems II: Express Briefs, IEEE Transactions on*, On page(s): 976 - 980 Volume: 55, Issue: 10, Oct. 2008
 3. Sigit Yuwono, Sok-Kyun Han, Sang-Gug Lee, "A 900-mV Area-Efficient **Source-Degenerated CMOS Four-Quadrant Multiplier** with 10.6-GHz Bandwidth", *Wireless Communications, Networking and Mobile Computing, 2009. WiCom '09. 5th International Conference on*, On page(s): 1 - 4
 4. Mokarram, M., Khoei, A., Hadidi, Kh., Gheysari, K., "Implementation of centroid defuzzifier block using CMOS circuits", *Intelligent Systems, 2008. IS '08. 4th International IEEE Conference*, On page(s): 2-26 - 2-29 Volume: 1, 6-8 Sept. 2008
 5. Wei Wu, Xiaoya Fan, Tingcun Wei, Charlesy, C.T., "A **low-voltage low-power self-mixer for 3.1#x2013;5GHz non-coherent UWB receiver**", *Electron Devices and Solid-State Circuits, 2009. EDSSC 2009. IEEE International Conference of*, On page(s): 24 - 27
 6. Mahmoud, S.A., "CMOS fully differential CMOS **Four-quadrant analog multiplier**", *Microelectronics, 2008. ICM 2008. International Conference on*, On page(s): 27 - 30
 7. Dei, M., Nizza, N., Bruschi, P., Piotto, M., "A **four quadrant CMOS analog multiplier** based on the non ideal MOSFET I-V characteristics", *Research in Microelectronics and Electronics, 2008. PRIME 2008. Ph.D.*, On page(s): 33 - 36
 8. Oliveira, V.J.S., Oki, N., "**Low voltage four-quadrant current multiplier**: An improved topology for n-well CMOS process", *Design & Technology of Integrated Systems in Nanoscale Era, 2007. DTIS. International Conference on*, On page(s): 52 - 55
 9. Diwakar, K., Senthilpari, C., Singh, A.K., Soong, L.W., "**Analog Multiplier with High Accuracy**", *Computational Intelligence, Communication Systems and Networks, 2009. CICSYN '09. First International Conference on*, On page(s): 62 - 66
 10. Lehne, M., Raman, S., "A 0.13- 1-GS/s CMOS Discrete-Time FFT Processor for Ultra-Wideband OFDM Wireless Receivers", *Microwave Theory and Techniques, IEEE Transactions on*, On page(s): 1639 - 1650 Volume: 59, Issue: 6, June 2011