

**ECEN 607 (ESS)
Spring 2008**


Name _____

EXAM #1


This is a closed book and notes exam. One information page is allowed for the exam.
This exam is worth 17% of your total grade.

Prob.	Maximum	Yours
1	4	
2	4	
3	5	
4	4	
Extra Credit	1	
Total	18	

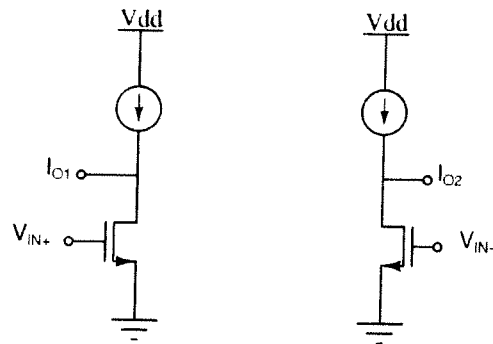Prob. 1. Write the differential and common-mode transconductance gain for the pseudo-differential circuits shown below (ignore the effect of g_{ds} and parasitic components). Discuss their differences i.e., effective transconductance, differential gains.




(a)

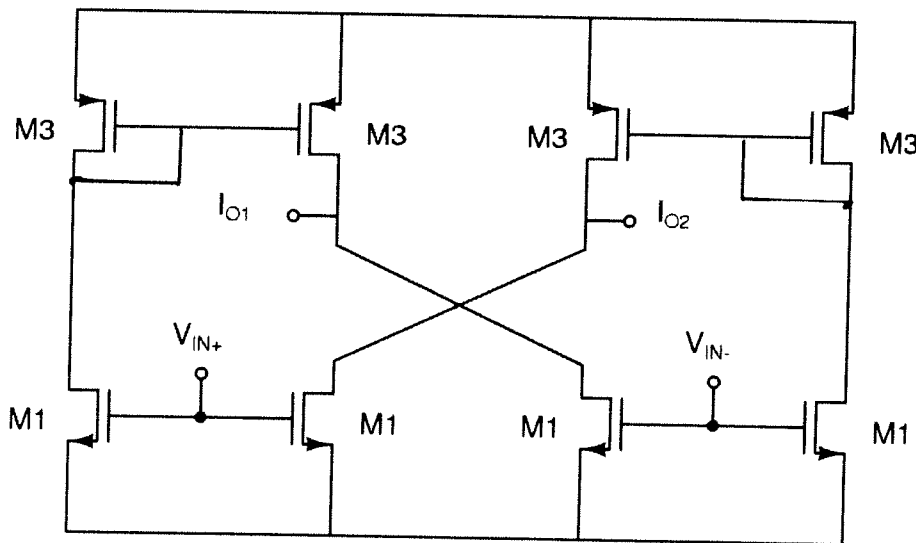

(b)

Prob.2

- 1) Assume Ideal Opamp. The current through M_1 and M_2 are equal. Obtain the expression for the bandgap reference output voltage V_{out} .
- 2) With a finite Opamp gain, in order to achieve the error voltage $(V_x - V_y)$ smaller than V_e , what should be the minimum Opamp Gain A_1 ? (You can use square law equations)

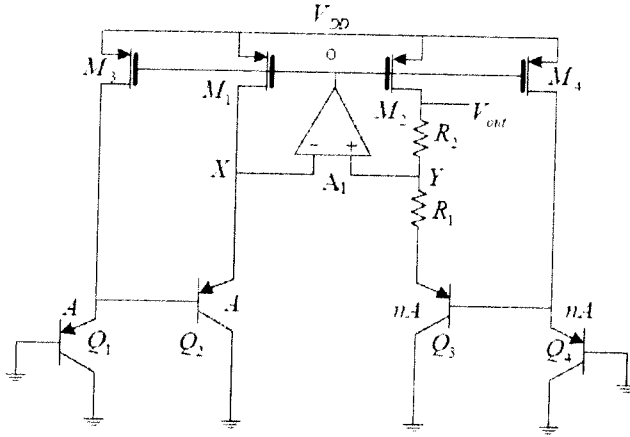

Prob 3. In the circuit shown below, relative sizes and bias currents are given as follows.


$$\text{Size}(M1) = 100 \cdot W/L$$

$$\text{Size}(M2) = W/(4L)$$


$$\text{Size}(M3) = W/(4L)$$

$$I_q = 8 \cdot I_s = 4 \cdot I_f$$

- Design a bias voltage generation circuit based on diode connected transistors that are scaled copies of M1, M2 and M3 to generate the bias voltage V_b . Assume small threshold voltage and ignore headroom constraints. Express the relative dimensions of the transistors in your design in terms of W/L or $W/(4L)$. Specify the value of current source used in your bias generator.
- It turns out that under quiescent condition, $V_{ds}(M3) = 2 \cdot V_{gs}(M3)$. Now, modify your bias generator to match the V_{gs} as well as the V_{ds} of bias generation copy of M3 and M3.

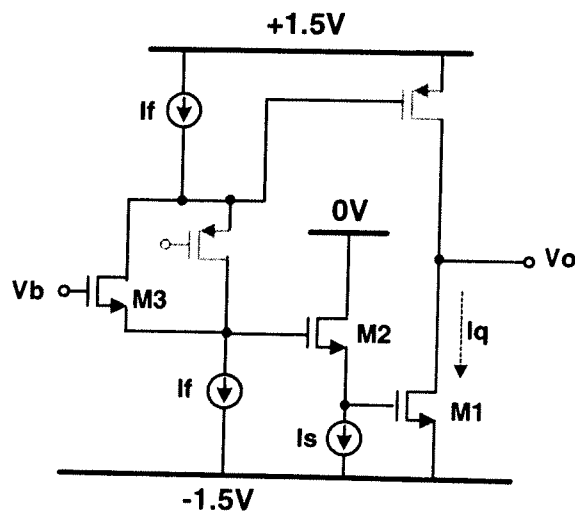

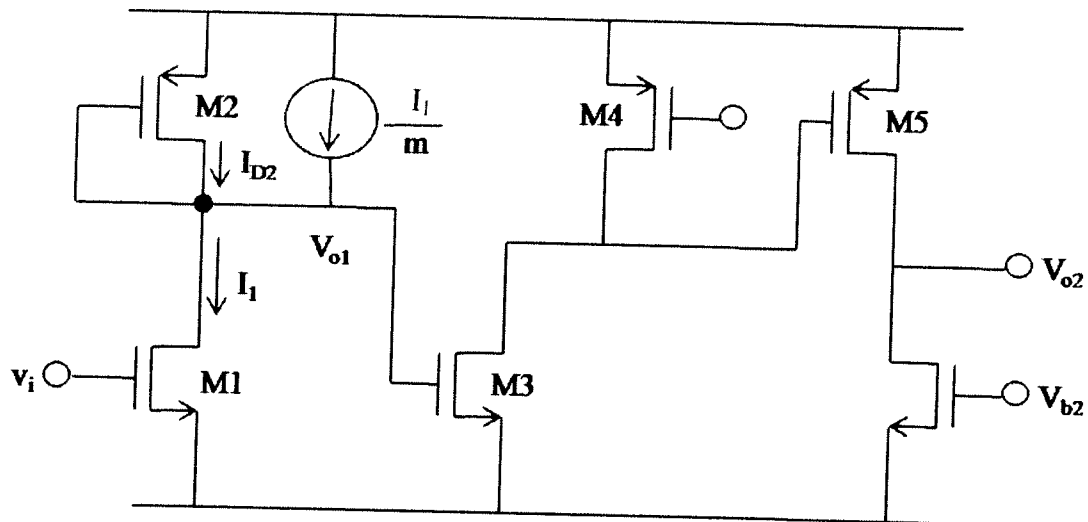Prob. 4. Obtain the low frequency small signal voltage gain expression (for V_{o1} and V_{o2}) of the following circuit. Assume ideal current sources and transistors operating in saturation.



EXTRA CREDIT. Obtain V_o as a function of V_D , R_1 , R_2 , kT , n and q .

