



# RAIL-to-RAIL OP AMPS




**Edgar Sánchez-Sinencio TAMU, AMSC**

*Thanks to Dr. Shouli Yan for his valuable input in helping in generating part of this material*

# Op Amp Configurations

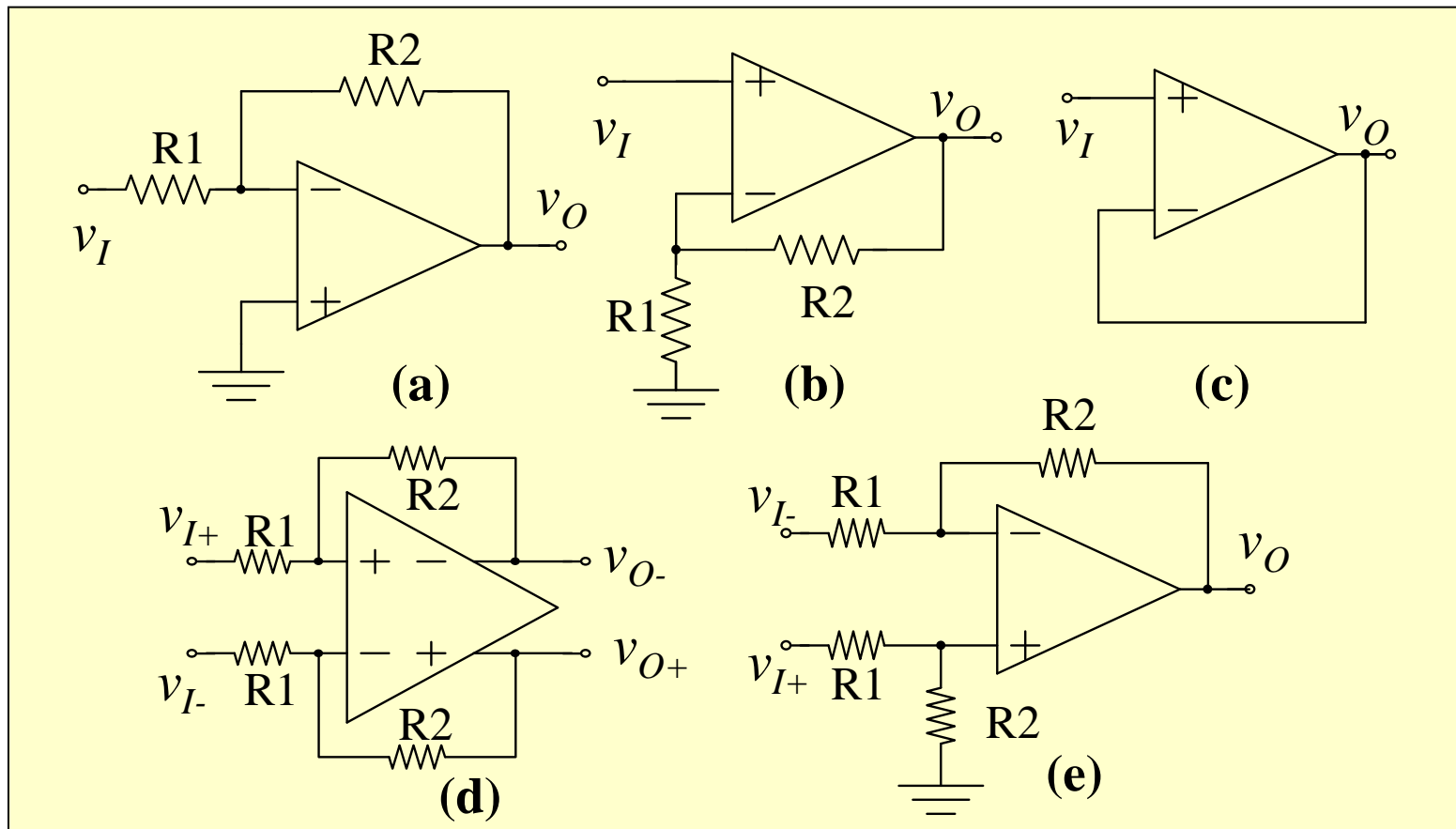(a) Inverting configuration, (b) Non-inverting configuration, (c) Voltage follower (or voltage buffer, a special case of (b)), (d) Fully-differential configuration, (e) Fully-differential to single-ended conversion



# Why Rail-to-Rail Differential Input Stage?


- The input and output swing requirements

Configuration	Figure	Input common mode voltage swing	Output voltage swing
Inverting	(a)	$\approx 0$	Rail-to-rail
Non-inverting	(b)	$R1/(R1+R2) * V_{SUP}$	
Voltage follower	(c)	Rail-to-rail	
Fully Differential	(d)	$R2/(R1+R2)*V_{I,CM}$	
FD to SE	(e)	$R2/(R1+R2)* V_{I+}$	


- From the above table, we see that for the inverting configuration, rail-to-rail input common mode range is not needed. But for all other configurations, there is a common mode voltage swing required. In particular for a voltage follower which usually works as an output buffer, **rail-to-rail** input common mode voltage range is required! To make an Op Amp work under any feedback condition, a differential input with **rail-to-rail** common mode range is very much needed.
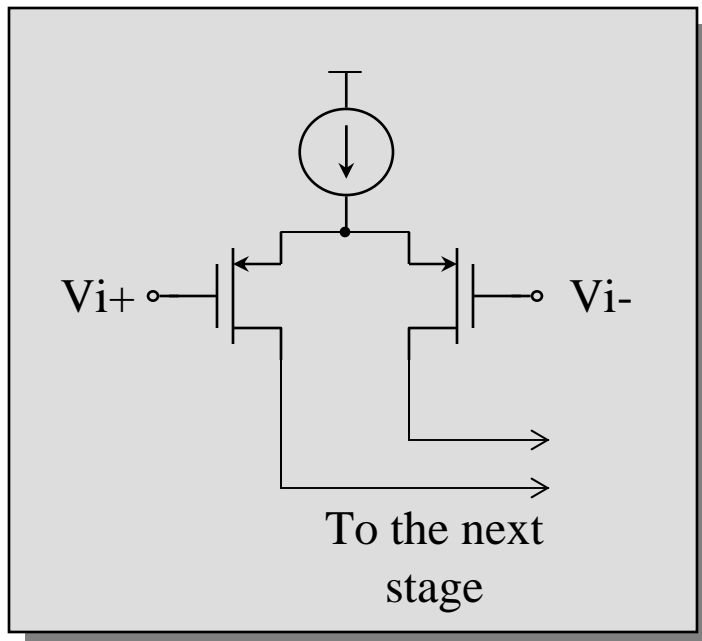
## How to Obtain a Rail-to-Rail Input Common Mode Range?

- The input stage of an op amp typically consists of a differential pair. There are two variations of differential pairs.




(a) P-type differential input stage

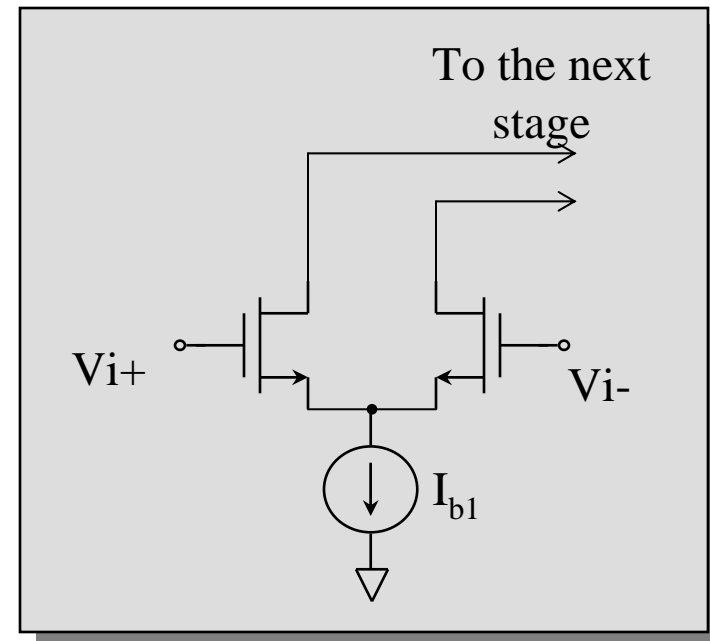

(b) N-type differential input stage
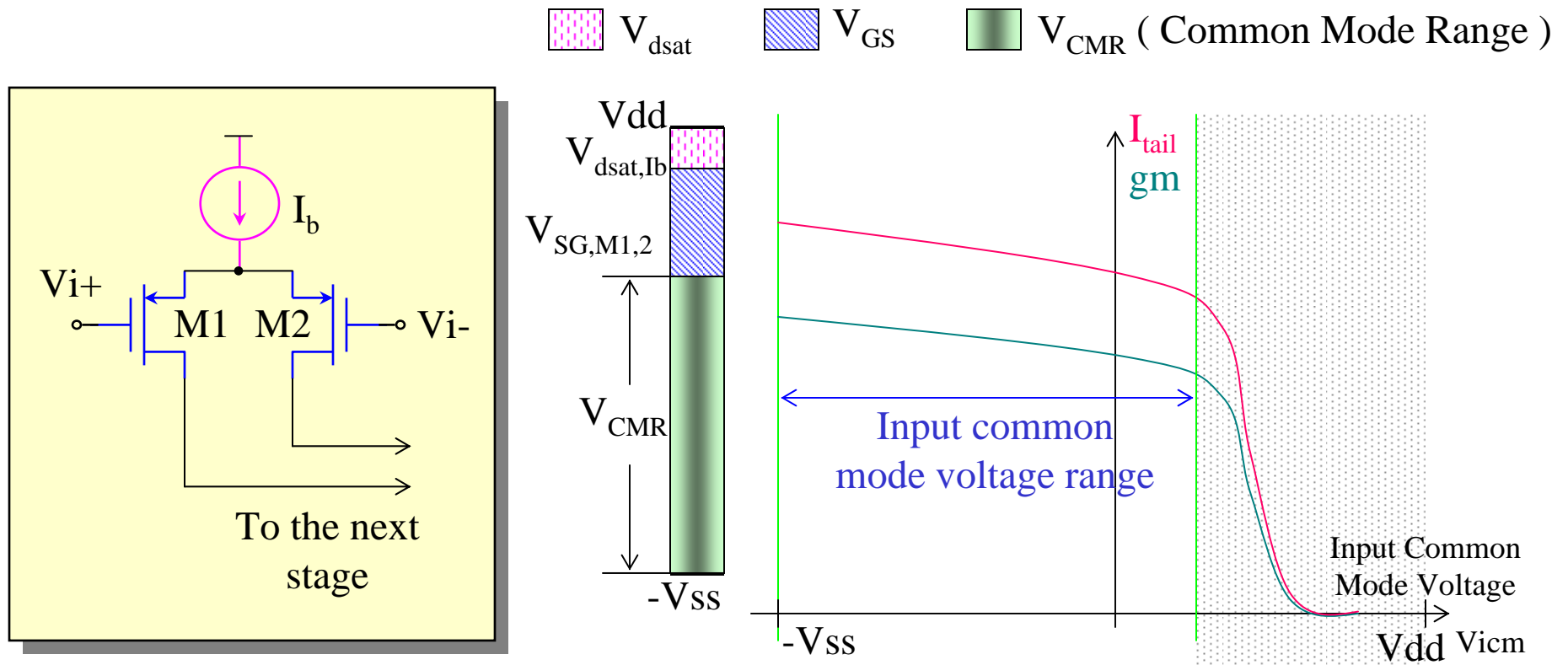
## How to Obtain a Rail-to-Rail Input Common Mode Range? ( cont'd )

- First, let us observe how a PMOS differential pair works with different input common mode voltage
  - P-type input differential pair





Where  $V_{SG} = V_{dsat} + V_T$

  
# How to Obtain a Rail-to-Rail Input Common Mode Range?

- N-type differential input stage


$V_{dsat}$ 
  $V_{GS}$ 
  $V_{CMR}$  ( Common Mode Range )


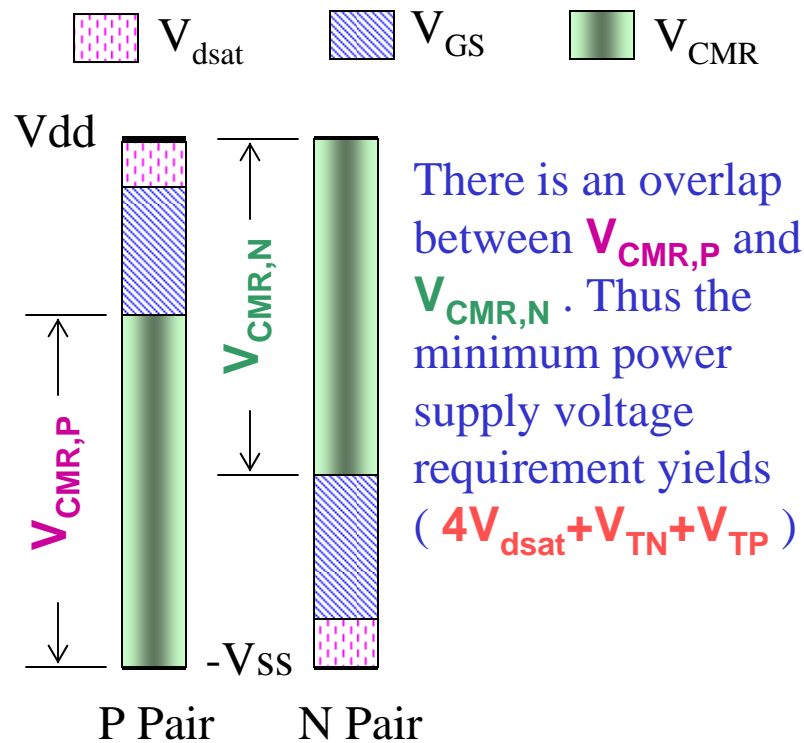
# By combining a PMOS and a NMOS Differential pairs a Rail-to-Rail Input Common Mode Range can be implemented


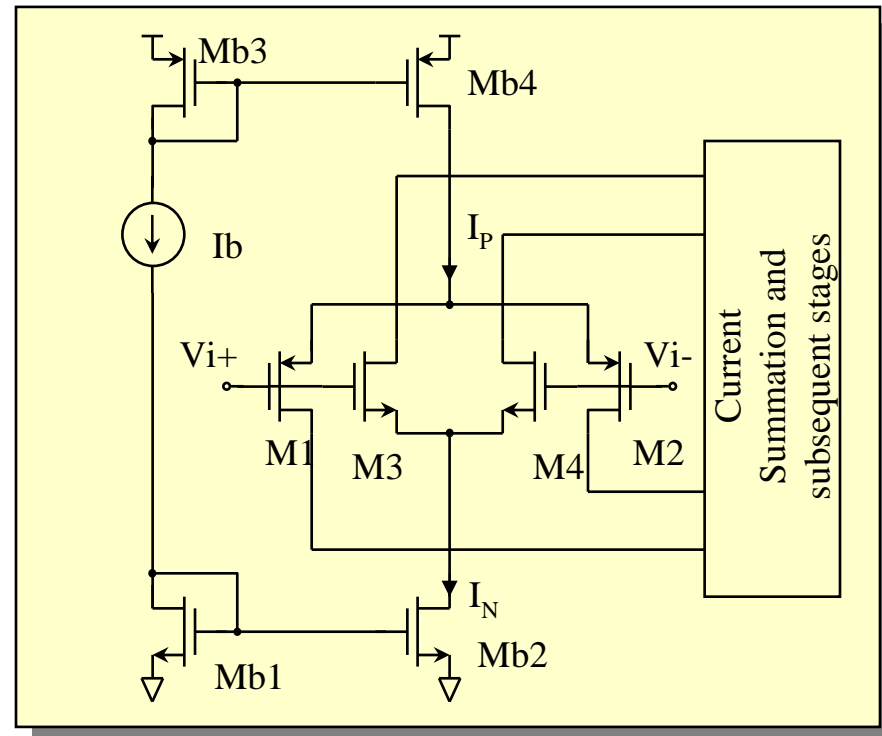
$$V_{SUP} \geq 4V_{dsat} + V_{TN} + V_{TP}$$




## Simple N-P complementary input stage

Almost all of the rail-to-rail input stages are doing in this way by some variations! But how well does it work?

## How to Obtain a Rail-to-Rail Input Common Mode Range? ( cont'd )

- Transconductance vs.  $V_{icm}$

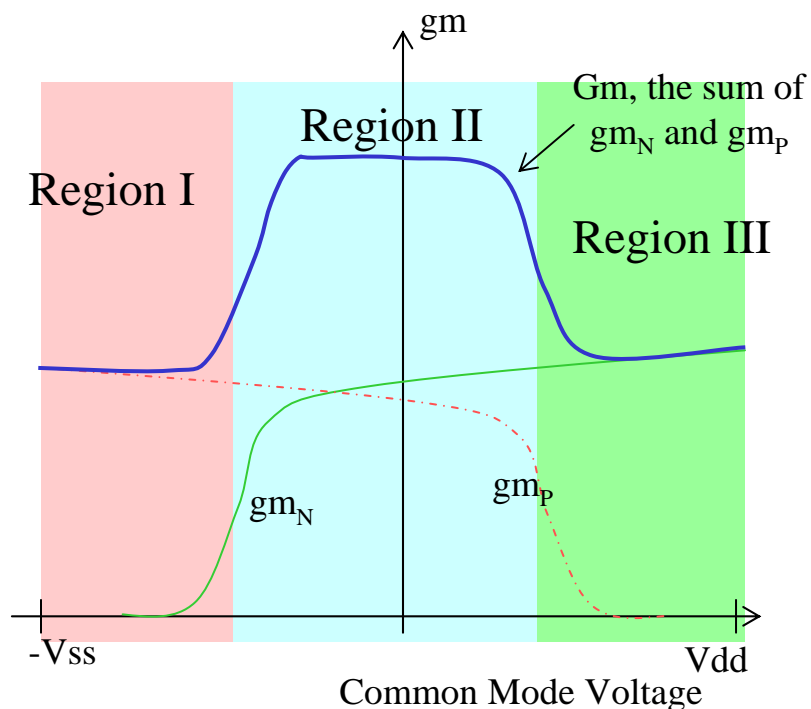

The total transconductance of the input stage varies from  $g_m$  to  $2g_m$ , the variation is **100%** !

- If  $K = \frac{1}{2} K P_N \left(\frac{W}{L}\right)_N = \frac{1}{2} K P_P \left(\frac{W}{L}\right)_P$   
and

$$I_N = I_P = I_{TAIL}$$

$$\text{then } g_{mN} = g_{mP} = g_m = \sqrt{2KI_{TAIL}} .$$

Region I. When  $V_{icm}$  is close to the negative rail, only P-channel pair operates. The N channel pair is off because its  $V_{GS}$  is less than  $V_T$ . The total transconductance of the differential pair is given by  $g_{mT} = g_{mP} = g_m$ .


Region II. When  $V_{icm}$  is in the middle range, both of the P and N pairs operate. The total transconductance is given by  $g_{mT} = g_{mN} + g_{mP} = 2g_m$ .

Region III. When  $V_{icm}$  is close to the positive rail, only N-channel pair operates. The total transconductance is given by  $g_{mT} = g_{mN} = g_m$ .


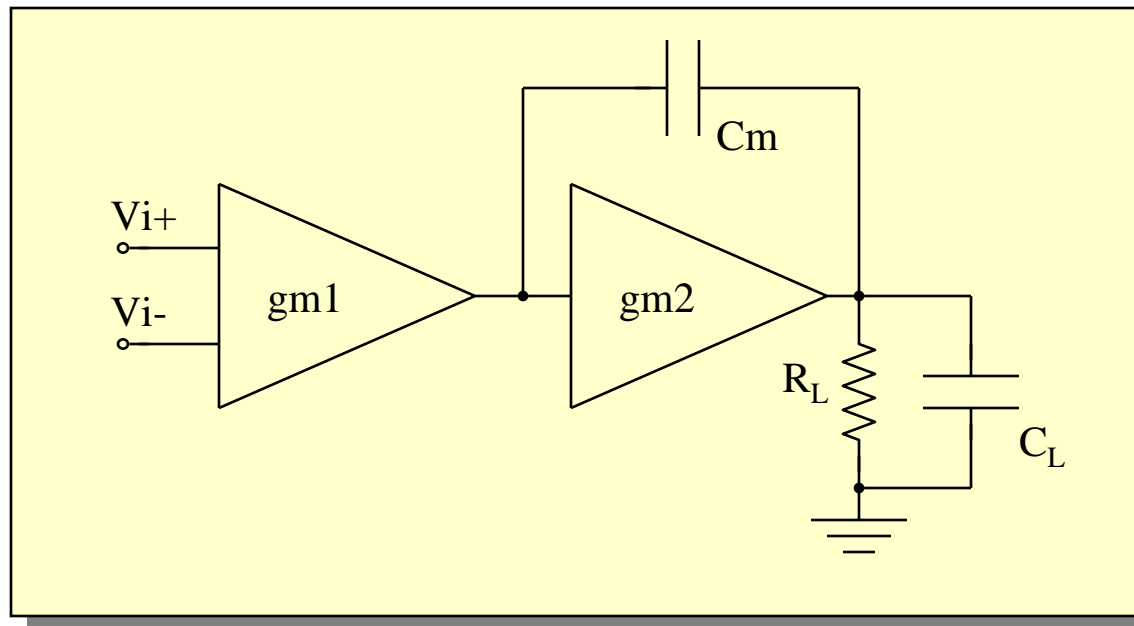
## Why is a Constant Gm needed ?

- The total transconductance,  $g_{mT}$ , of the input stage shown in the previous slide varies as much as twice for the common mode range!
- For an operational amplifier, constant transconductance of the input stage is very important for the functionality of the amplifier.
- As an example, we will analyze a simple two-stage CMOS operational amplifier. The conceptual model of the amplifier is shown below.



## Why is a Constant Gm needed ? ( cont'd )

- The transfer function of the amplifier is given by

$$A(s) \approx \frac{g_{m1}g_{m2}(1 - s\frac{C_m}{g_{m2}})}{s^2C_L C_m + sC_m g_{m2} + g_{o1}g_L} = A_0 \frac{1 - s\frac{z}{p_1}}{s^2 \frac{1}{p_1 p_2} + s\frac{1}{p_1} + 1}$$

where  $A_0 = \frac{g_{m1}g_{m2}}{g_{o1}g_L}$ , which is the DC gain of the amplifier.

$$p_1 = \frac{GBW}{A_0} = \frac{g_{m1}/C_m}{A_0}, \quad p_2 = \frac{g_{m2}}{C_L}, \quad \text{and} \quad z = \frac{g_{m2}}{C_m},$$

$p_1$  and  $p_2$  are the dominant pole and non-dominant pole of the amplifier respectively, and  $p_1 \ll p_2$ .

$z$  is the zero generated by the direct high frequency path through  $C_m$ .

## Why Should We Have a Constant Gm ( cont'd )

*GBW* is the Gain Bandwidth product, or the unity gain frequency of the amplifier, which is given by

$$GBW = \frac{g_{m1}}{C_m}.$$

We may notice that *GBW* changes with  $g_{m1}$ ! If  $g_{m1}$  changes 2 times, the *GBW* also does so!

- To ensure the stability of the amplifier, we should maintain a sufficient phase margin. Usually, we let  $p_2$  to be 2.5 times of *GBW*. Let's assume  $C_m = C_L/2$ , then  $z = 2p_2 = 5 \times GBW$ .
- If the total transconductance of the input stage,  $g_{m1}$ , varies 2 times as we have encountered in previous discussion, from  $gm$  to  $2gm$ , let us check how the stability is affected.

## Why is a Constant Gm needed ? ( cont'd )

- We can change  $gm$  by varying some parameters of the input stage. Let us assume that we design an amplifier with sufficient phase margin when  $g_{m1}$  is low ( which is now  $gm$  ). That is

$$p_2 = \frac{g_{m2}}{C_L} = 2.5GBW_{LOW} = 2.5 \frac{g_{m1,LOW}}{C_m} = 2.5 \frac{gm}{C_m},$$



- When  $g_{m1}=gm$ , we can get that the phase margin as  $57^\circ$ , which is sufficient to ensure the stability of the amplifier.
  - When the  $g_{m1}$  is at its maximum value,  $2gm$ , the  $GBW$  doubles, at this point, the phase margin changes to  $29^\circ$  ! It is not enough and the amplifier may be unstable and may oscillate !!
- We could design such that, when  $g_{m1}$  is  $2gm$ , we set the amplifier with sufficient phase margin, which means,

$$p_2 = \frac{g_{m2}}{C_L} = 2.5GBW_{HIGH} = 2.5 \frac{g_{m1,HIGH}}{C_m} = 5 \frac{gm}{C_m},$$
  
## ( cont'd )

We have to push  $g_{m2}$  to 2 times of its original value in previous case! It means **more power**, and might be near the limitation of the process, that is we can only design an amplifier with **50% of the GBW** that a specific process permits. Of course, we do not want either of these two situations.

- Transconductance variation of the input stage is not desirable, it prevents the optimal frequency compensation of the amplifier. There are other negative effects of the changing transconductance. For instance, gm variation may introduce extra harmonic distortion because of the changing voltage gain.
  - Let us consider a feedback voltage amplifier with input gm variation. As shown in the next slide.
  - Assume the open loop gain of the Op Amp is  $A_{OL}(s)$ , and the transfer function of feedback branch is  $H_{FB}(s)$ . The close loop gain of the amplifier is defined by



$$A_{CL}(s) = \frac{1}{H_{FB}(s) + \frac{1}{A_{OL}(s)}}$$

- For the practical case, close loop gain of the amplifier in the right figure is given by

$$A_{CL}(s) = \frac{1}{H_{FB} + \frac{1}{A_{OL}(s)}}, \text{ where } H_{FB} = \frac{R_2}{R_1 + R_2},$$

- $A_{CL}(s)$  changes if  $A_{OL}(s)$  varies with the input voltage, although to a less extent, which will introduce some nonlinear distortion at the output, especially at higher frequencies when  $A_{OL}(s)$  is low.

- In summary, we need a **constant** transconductance for the input stage!
- What are the structures capable to yield constant-gm N-P complementary input stage ?
- What are the tradeoffs and sensitivity to process variations ?

# Techniques for N-P Complementary Rail-to-Rail Input Stage

There is a host of constant gm rail-to-rail input stage structures in literature, we will do a review from their implementation basic ideas

1. For input stages with input transistors working in weak-inversion region, using current complementary circuit to keep the sum of  $I_N$  and  $I_P$  constant [1][2][6];
2. Using square root circuit to keep  $(\sqrt{I_p} + \sqrt{I_n})$  constant [3][13][16];
3. and 4. Using current switches to change the tail current of input differential pairs [3][4][5][6];
5. Using hex-pair structure to control the tail currents of backup pairs [7];



## Techniques for N-P Complementary Rail-to-Rail Input Stage ( cont'd )

6. Using maximum/minimum selection circuit to conduct the output current of the differential pair with larger current, as well as larger gm, to the next stage [8][9];
7. Using electronic zener diode to keep  $V_{GSn} + |V_{GSp}|$  constant [10];
8. Using DC level shift circuit to change the input DC level [11].

We will analyze them one by one in the following sections.

There are still other techniques [12][14][15][17][18], interested readers may check these references.

Note: Unless explicitly stated in this notes, we assume that the square law characteristic of MOS transistors in strong inversion and saturation region. Please notice that for short channel transistors in sub-micron processes, square law is not exactly followed.

# Rail-to-Rail Input Stage, Structure 2

## [3][13\*][16]

- Using square root circuit to keep  $(\sqrt{I_p} + \sqrt{I_n})$  constant
- Basic idea
  - For an input differential pair, using a 1st order approximation,

$$gm = \sqrt{2K_p(W/L)I_D} = \sqrt{K_p(W/L)I_{TAIL}}$$

Where the  $I_{TAIL}$  is the tail current of the differential pair. We can change gm by altering the tail current of the differential pair!

- The total transconductance of the input stage is given by

$$gm_T = gm_N + gm_P = \sqrt{KP_N(W/L)_N I_N} + \sqrt{KP_P(W/L)_P I_P}$$

If  $KP_N(W/L)_N = KP_P(W/L)_P = 2K$

We can get


$$gm_T = gm_N + gm_P = \sqrt{2K}(\sqrt{I_N} + \sqrt{I_P})$$

- To keep  $gm_T$  constant, we just need to keep  $(\sqrt{I_N} + \sqrt{I_P})$  constant!

\*:[13] is an improved version of this scheme, in [13]  $KP_N(W/L)_N = KP_P(W/L)_P$  is not required. The authors presented techniques to compensate KP variations.

# Rail-to-Rail Input Stage, Structure 2 ( cont'd )

- Block diagram

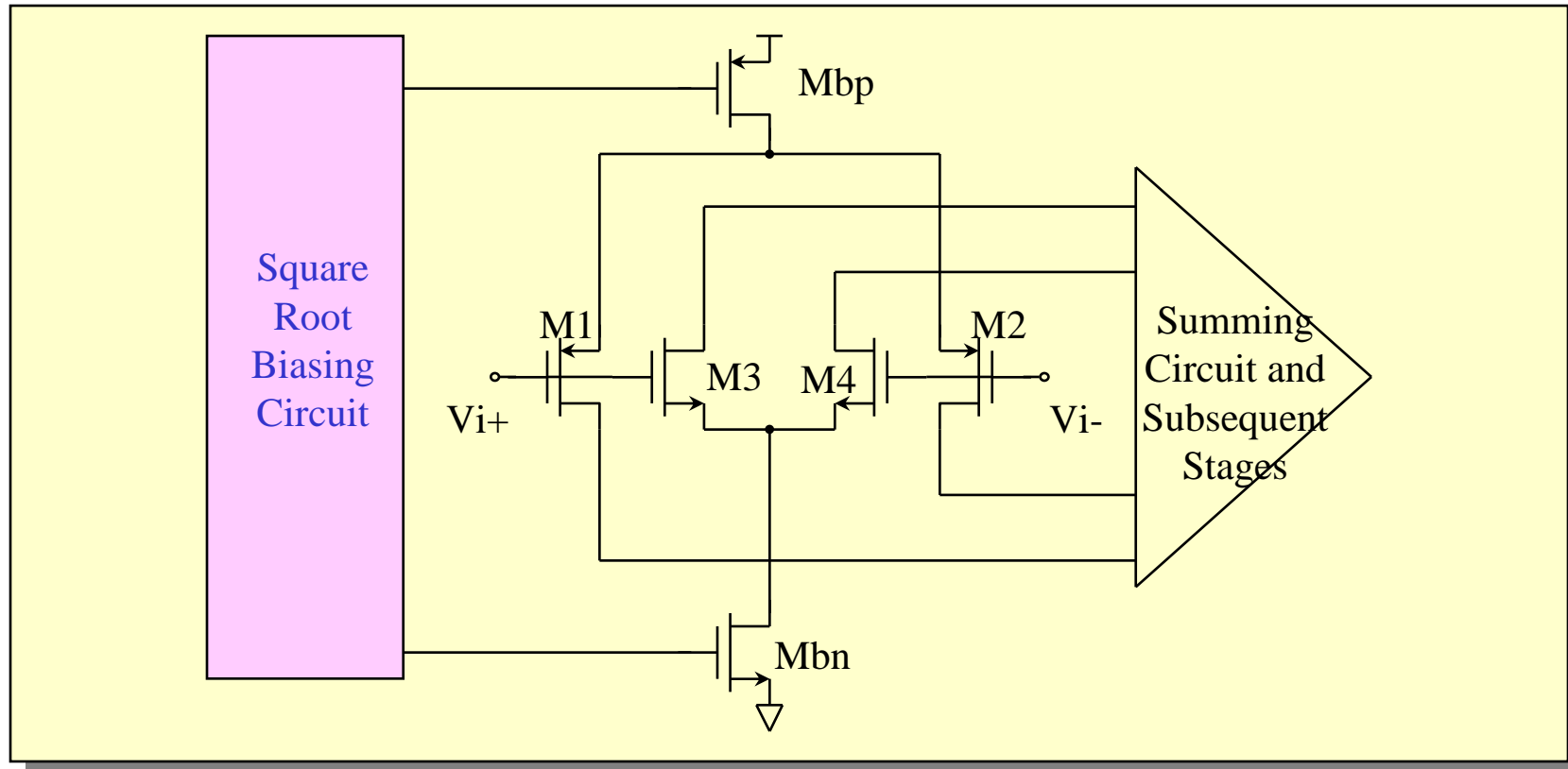

- We can utilize the square law characteristic of MOS transistors to implement the square root biasing circuit.

# Rail-to-Rail Input Stage, Structure 2 ( cont'd )

- Working Principle
  - The input transistors work in strong inversion region.
  - The square-root circuit M121-M125 keeps the sum of the square-roots of the tail currents of the input pairs and then the gm constant.
  - The current switch, M111, compares the common-mode input voltage with  $V_{b3}$  and decides which part of the current  $I_{b7}$  should be diverted to the square-root circuit.
  - In the common-mode input voltage range from  $V_{dd}$  to  $-V_{ss}+1.8V$  only the N channel pair operates. The current switch M111 is off and thus the tail current of the N channel input pair  $I_N$  equals  $I_{b7}=4I_{ref}=20\mu A$ .
  - The sum of the gate-source voltages of M123 and M125 is equal to reference voltage which is realized by M121 and M124. Since the current through M125 equals  $I_N$  and the current through M123 equals the tail current of the P channel input pair  $I_P$ .

## Rail-to-Rail Input Stage, Structure 2 ( cont'd )

- The summing circuit M21-M24 adds the output signals of the complementary input stage, and forms the output voltage at node #20.
- Discussion
  - The circuit is somewhat complex and the functionality relies on the square law of MOS transistors. For current sub-micron processes, the square law is not closely followed, which may introduce large error for the total transconductance.

# Rail-to-Rail Input Stage, Structure 3 [3][4][6]

- Using current switches to change the tail current of input differential pairs
- Basic idea
  - We know that, by first order approximation, for a MOS transistor working in strong inversion and saturation region, square law applies, that is

$$I_D = K(V_{GS} - V_T)^2, \quad \text{and} \quad gm = 2\sqrt{KI_D},$$

$$\text{where} \quad K = \frac{1}{2} KP \left(\frac{W}{L}\right)$$

- Suppose for the N and P input pairs,  $KP_N \left(\frac{W}{L}\right)_N = KP_P \left(\frac{W}{L}\right)_P = 2K$

and the tail currents of N and P pairs are equal, with the value of  $I_{\text{tail}}$ .

## Rail-to-Rail Input Stage, Structure 3 ( cont'd )

- When the input common mode voltage is in the mid-range, both of N and P pairs are conducting, so the total transconductance is

$$gm_T = gm_N + gm_P = 2\sqrt{2KI_{TAIL}}$$


- When the input common mode voltage is close to Vdd, the N pair operates. And when it is close to the -Vss, the P pair operates. In both cases, the total transconductance is only **half** of that when both of N and P pairs operate.

$$gm_T = gm_N = gm_P = \sqrt{2KI_{TAIL}}$$

We can increase the tail current to **4** times of its original value to have the same transconductance as that when both of N and P pairs operate.

# Rail-to-Rail Input Stage, Structure 3 ( cont'd )


- The circuit

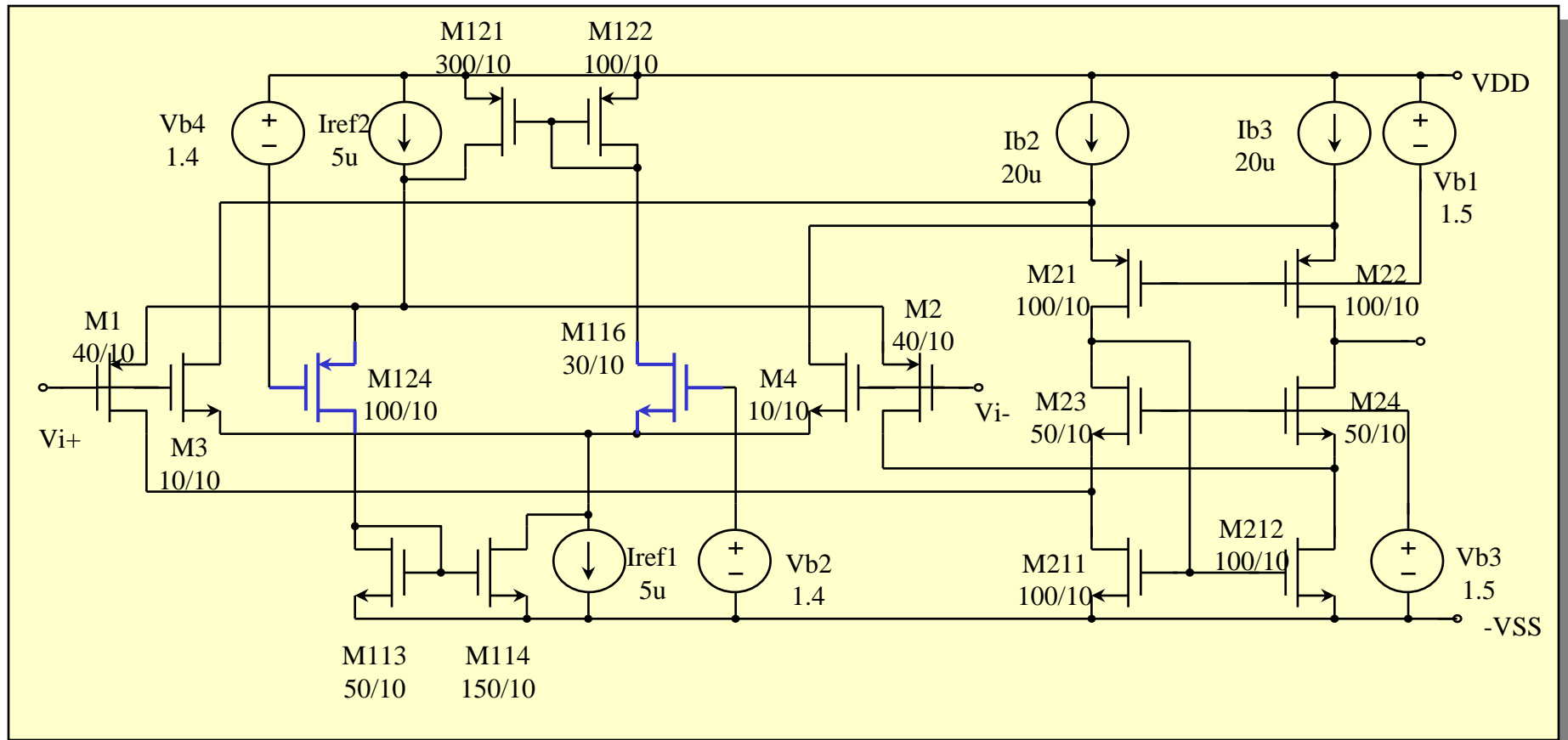



# Rail-to-Rail Input Stage, Structure 3 ( cont'd )


- Conceptual circuit

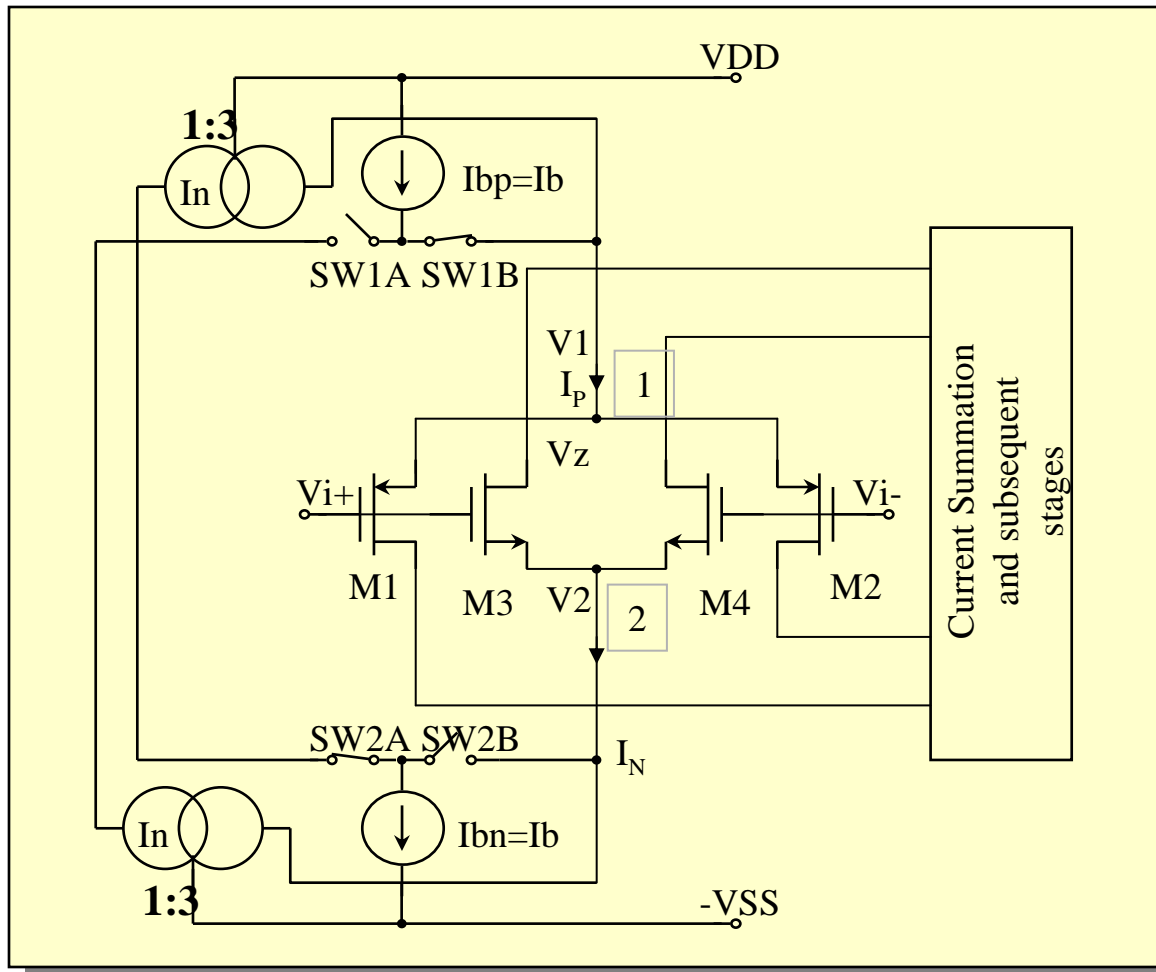

- When common mode input voltage,  $V_{icm}$ , is close to  $-V_{SS}$ , SW1B and SW2A are on, and SW1A and SW2B off.
- When  $V_{icm}$  is close to Vdd, SW1A and SW2B are on, and SW1B and SW2A off.
- In between, SW1B and SW2B are on, SW1A and SW2A off.
- In practice, SW1B and SW2B are never required, just short circuits. Say, if SW1A is on,  $I_{bp}$  will be diverted to the 1:3 current mirror; if SW1A is off,  $I_{bp}$  will provide tail current for M1 and M2.
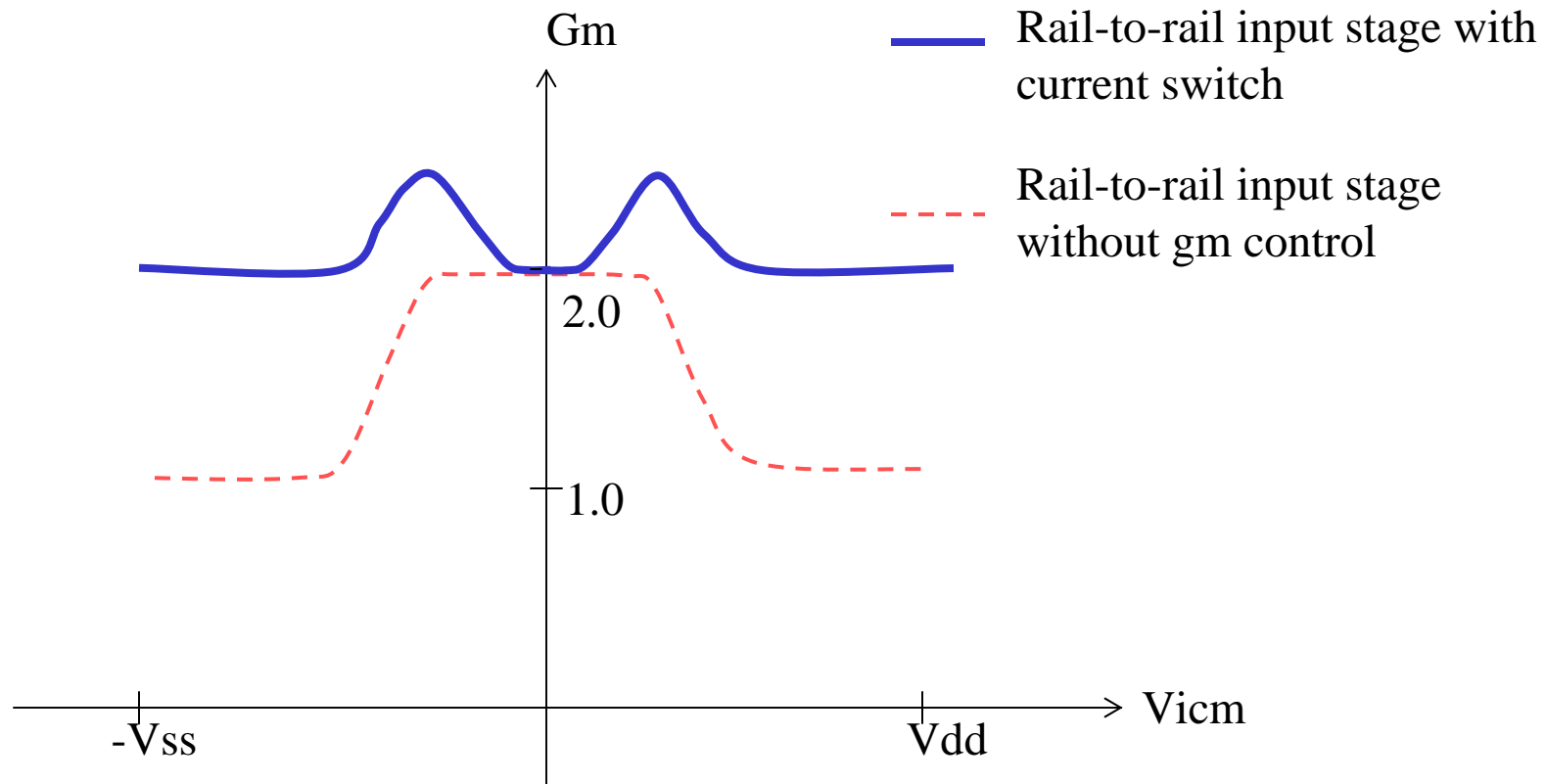
# Rail-to-Rail Input Stage, Structure 3 ( cont'd )


- Transconductance vs. input common mode voltage


 
# Rail-to-Rail Input Stage, Structure 6 [8][9]


- Using Maximum/Minimum selection circuit
- The basic idea
  - From previous analysis, we know that, when the common mode voltage drives the tail current transistor out of saturation region, the tail current of a differential pair decreases dramatically with the common mode voltage. As shown in the following figure.

- The differential pair, whichever it is N pair or P pair, with the larger current should be working properly. We just try to choose the pair with larger working current, and discard the output of another pair.




# Rail-to-Rail Input Stage, Structure 6 ( cont'd )

- The block diagram

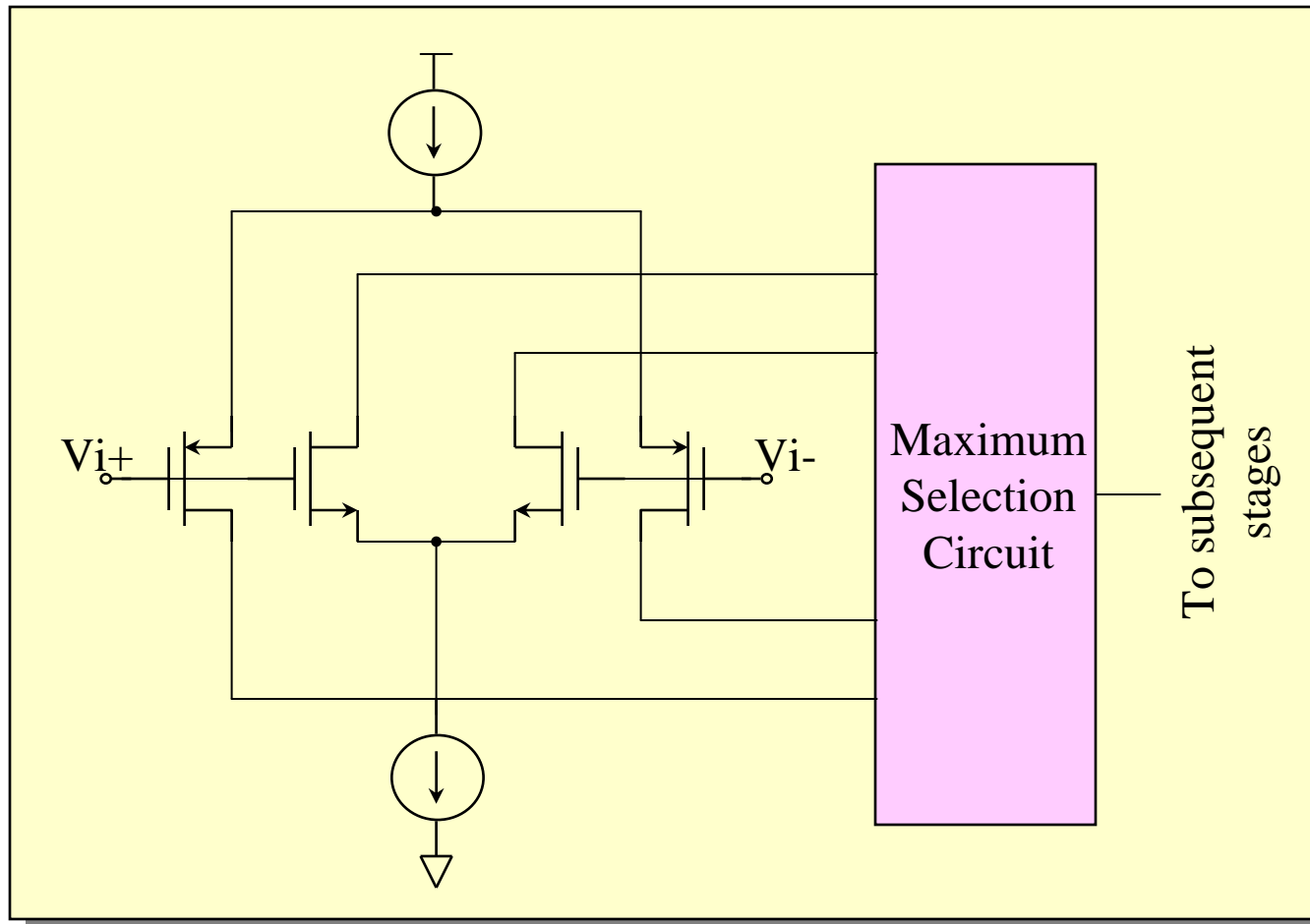

 
# Rail-to-Rail Input Stage, Structure 6a ( cont'd )

- Transconductance vs. input common mode voltage



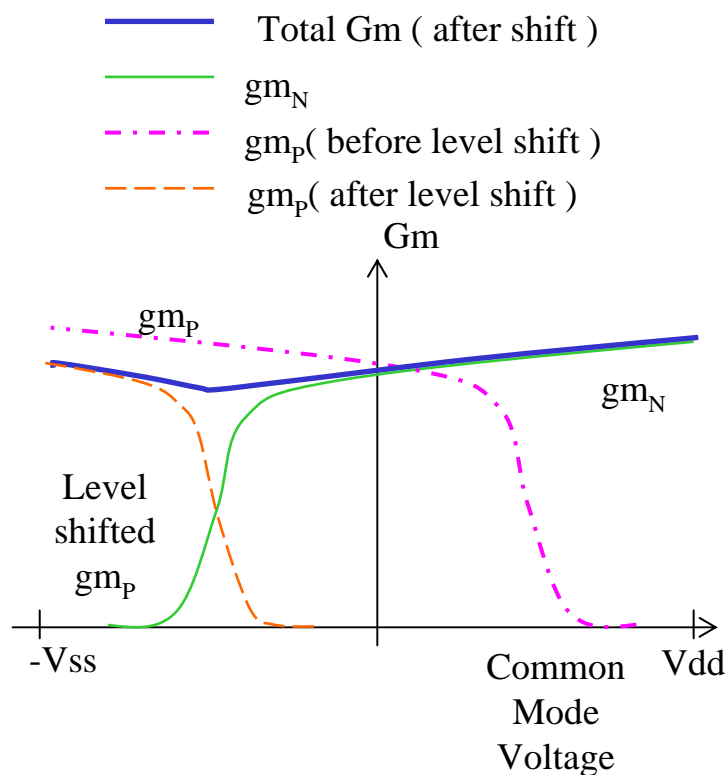
# Rail-to-Rail Input Stage, Structure 8 [11]

- Using DC shifting circuit to change the input DC level
- Basic idea




- We may notice that there is an overlap between  $g_{m_N}$  and  $g_{m_P}$ , so in the middle of the common mode voltage, the transconductance is doubled.
- How about shift one of the  $g_{m_N}$  and  $g_{m_P}$  curve? And let the transition regions of  $g_{m_N}$  and  $g_{m_P}$  come together, so that the total transconductance will be nearly constant among the common mode input range.
- Level shift can be implemented by common source voltage follower. We can change the shift level by altering the bias current  $I_b$ .

 

# Rail-to-Rail Input Stage, Structure 8 ( cont'd )


- The circuit [11]

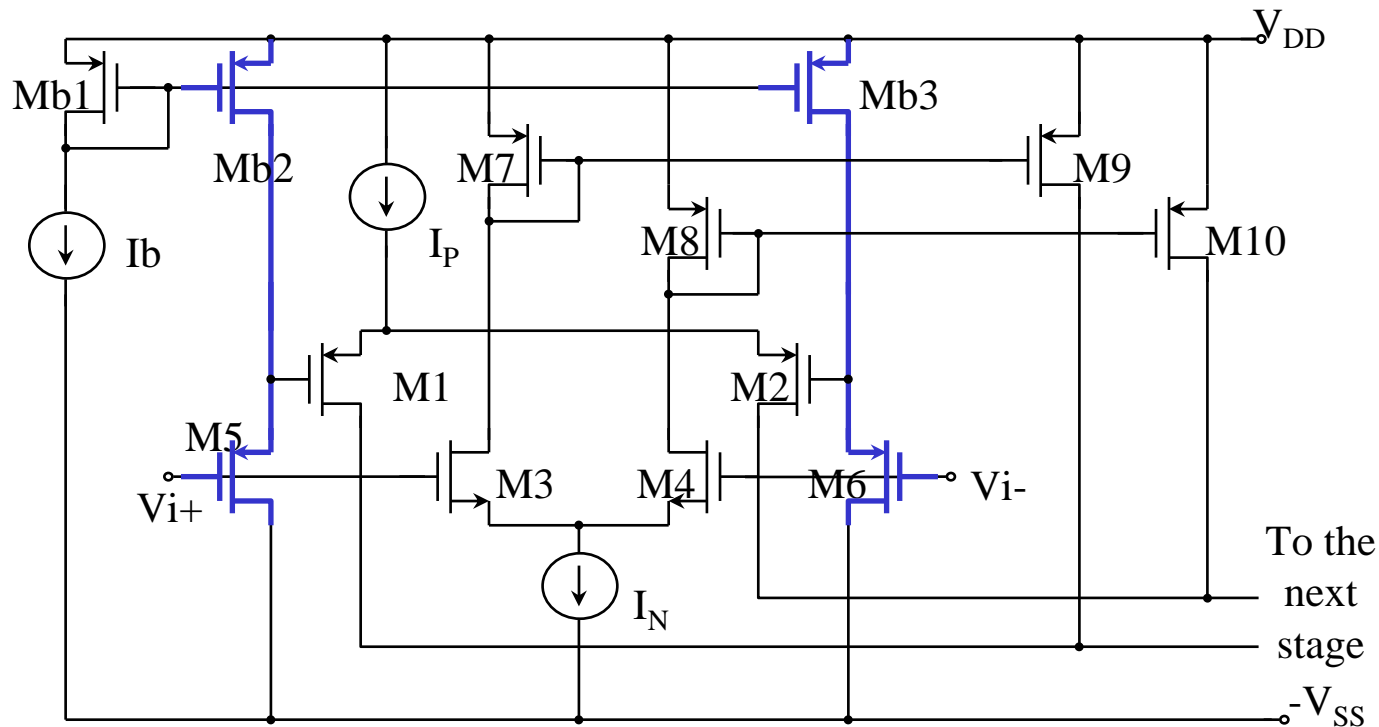

- Note: 1) M5 and M6 are level-shifting transistors  
 2) The voltage shifted by M5 and M6 can be altered by changing Ib

# Rail-to-Rail Input Stage, Structure 8 ( cont'd )

- Working principle
  - The input voltages are shifted by M5, M6 by  $|V_{GS,M5,M6}|$  towards the positive power supply rail, so the transition region for  $g_{mP}$  is shifted by the same value towards the negative power supply rail.
  - The transitions region of  $g_{mN}$  and  $g_{mP}$  overlap and we can get an constant gm over the common mode range.

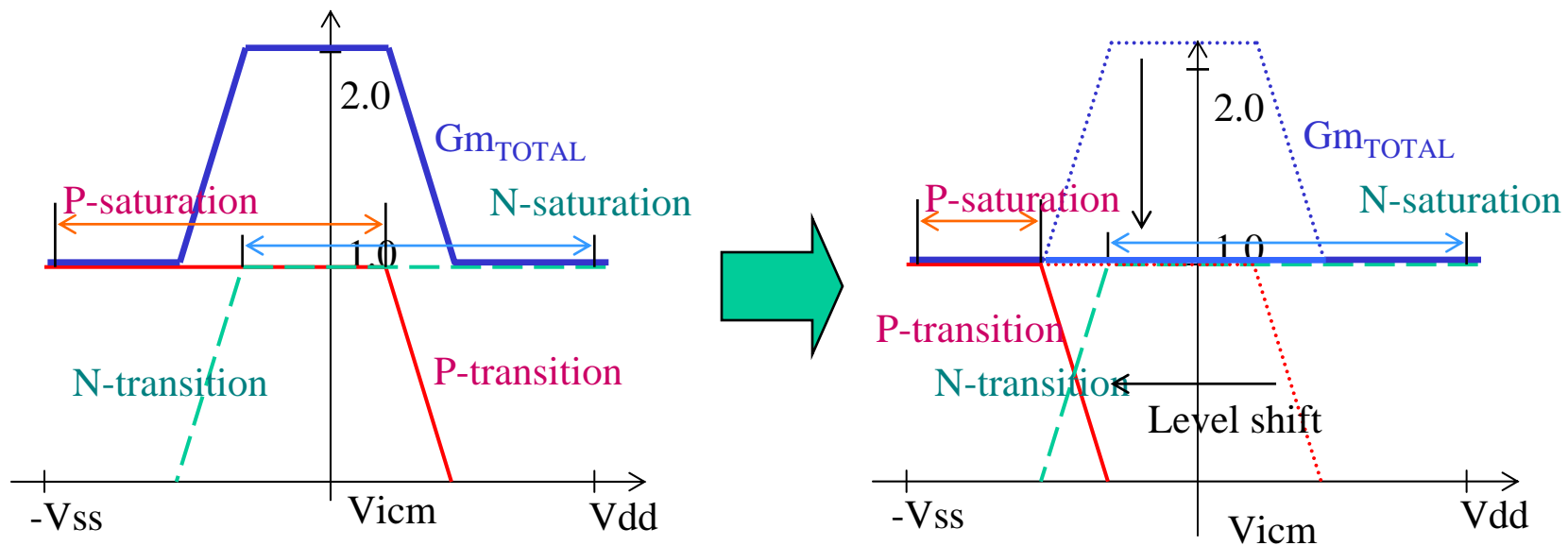



# Rail-to-Rail Input Stage, Structure 8 ( cont'd )


- Characteristics
  - We can obtain very small gm variation (  $\pm 5\%$  ) if the DC shift level is tuned well [11].
  - This circuit structure is sensitive to the power supply changes and  $V_T$  variations, but we can add some auto-bias circuit to overcome this problem.

# Summary and Comparison


Case	Principle	$\Delta g_m$	Slew Rate	CMRR	Advantage	Limitations
1	$I_N + I_P = const$ [1][2][6]	N/A for weak inversion 40% if in strong inversion	Constant	56dB@10Hz, 52dB@100KHz, measured in [2]	Small gm variation ( 6% ) in weak inversion operation	Only work well in weak inversion, can not used in high speed application
2	$\sqrt{I_N} + \sqrt{I_P} = const$ [3] [16]	-12% +6% ( simulated in this presentation )	$\sqrt{2}$ times variation	80 dB / 53 dB ( measured in [3] )		Depends on quadratic characteristics of MOSFETs, which is not exactly followed for short channel transistors in sub-micron processes
3	4 times $I_N$ or $I_P$ when only one pair operates [3][4][6]	+15% systematic gm variation	2 times variation	70dB / 43 dB ( measured in [4] )	Somewhat simple	1) Same with case 2, but we can change 4 to other numbers to have smaller gm variation for short channel transistors 2) Systematic gm deviation of 15% even for ideal MOSFETs with quadratic characteristics
4	Current switch, backup pairs [5]	+20% systematic gm variation	Constant	N/A	Constant slew rate	Systematic gm deviation of 20% even for ideal MOSFETs with quadratic characteristics
5	6-pair structure, back pairs [7]	+20% systematic gm variation ( analytical ), $\pm 10\%$ ( measured in [7] )	Constant	N/A	Constant slew rate	Same with Case 4
6	Max/min selection [8][9]	7% ( simulated [9] ) 5% ( strong inversion, measured [8] ) 20% ( weak inversion, measured [8] )	Constant	N/A		Somewhat complex
7	Electronic zener [10]	8% ( measured )		80 dB / 43 dB ( measured in [10] )		Same with Case 2
8	Level shift [11]	$\pm 4\%$ after tuning 13% before tuning ( measured )		$\geq 80$ dB ( DC ) ( measured in [11] )	Simple	Gm variation sensitive to $V_T$ variation and power supply voltage change

# A Rail-to-Rail Amplifier Input Stage with Less than $\pm 0.5\%$ Fluctuation in $g_m$


By courtesy of Timothy W. Fischer

 

# Previous Work

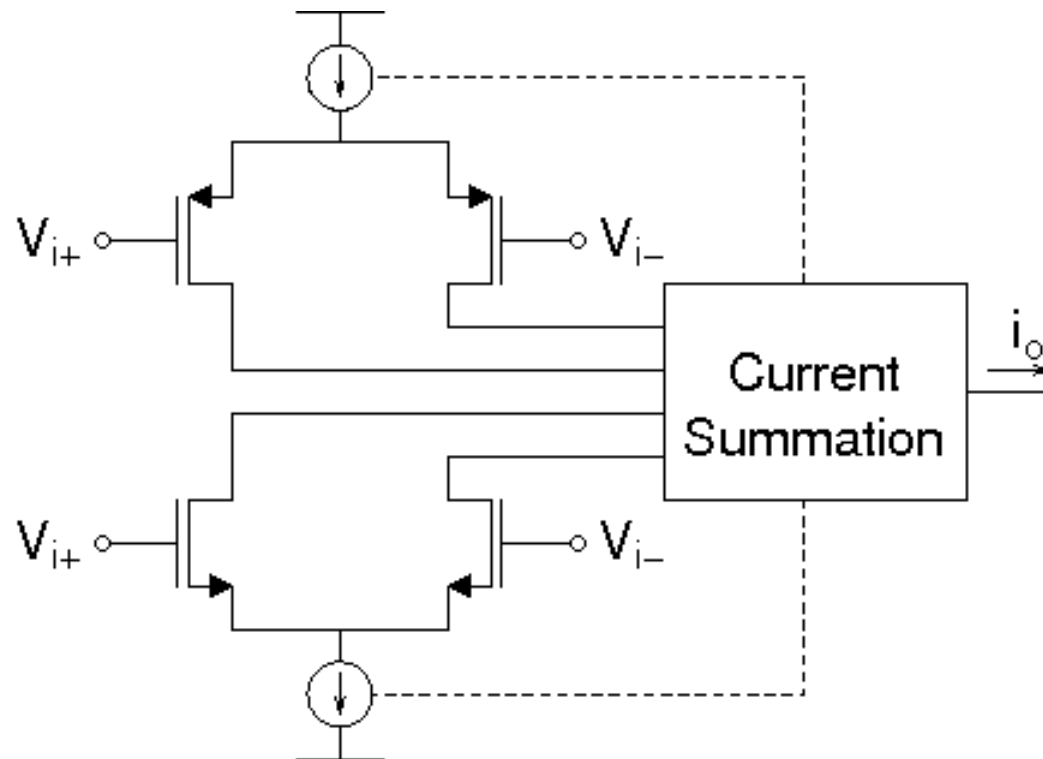


# Previous Work [2]

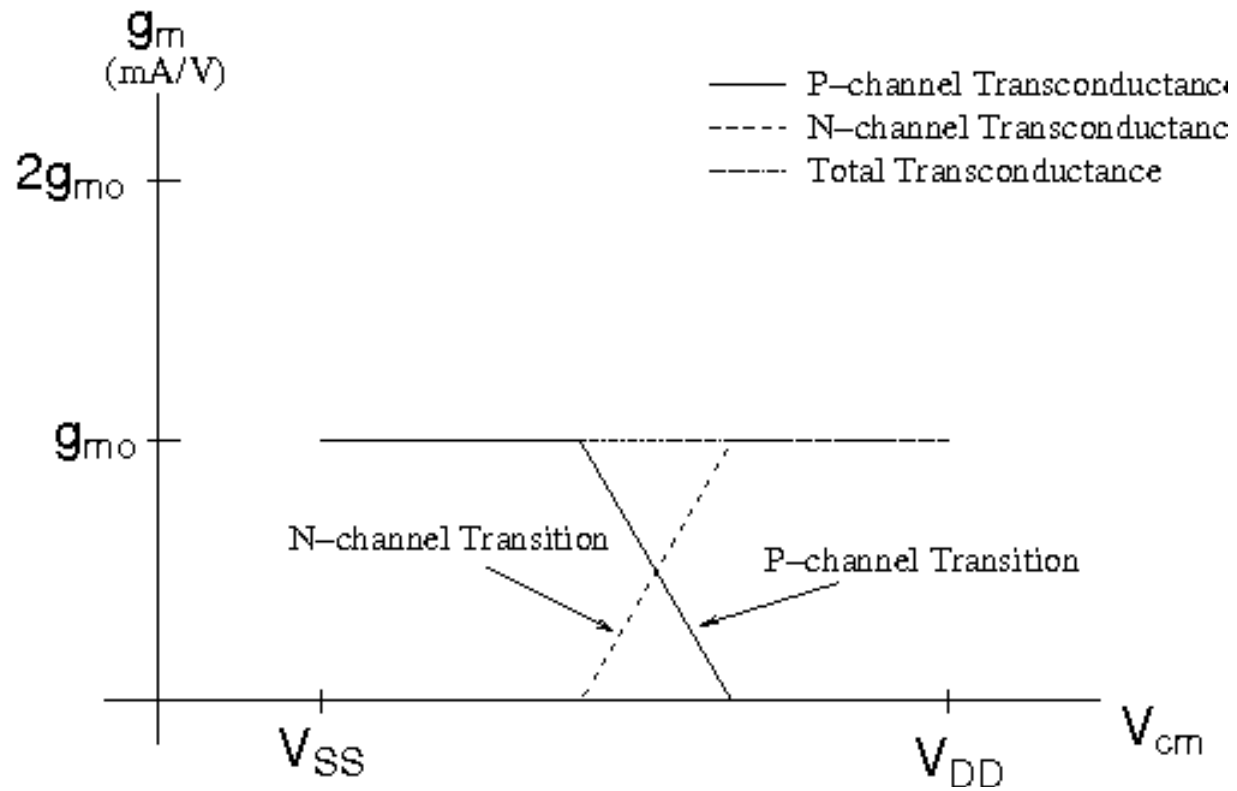

# Problems with Previous Work

- Mismatch between N-channel and P-channel transconductors
- Transition Region
  - CMRR degradation (40-60 dB)
  - Nonlinearity


# One Differential Pair Solution[4]

 

$$v_{in} = v_{cm} + v_{dm}$$

$$v'_{in} = \frac{C_1}{C_1 + C_2} v_{cm} + \frac{C_1}{C_1 + C_2} v_{dm}$$

# Proposed Solution

 


$$V_{in} = V_{cm} + V_{dm}$$

$$V_{in}' = \frac{V_{dm}}{2}$$



# Proposed Solution

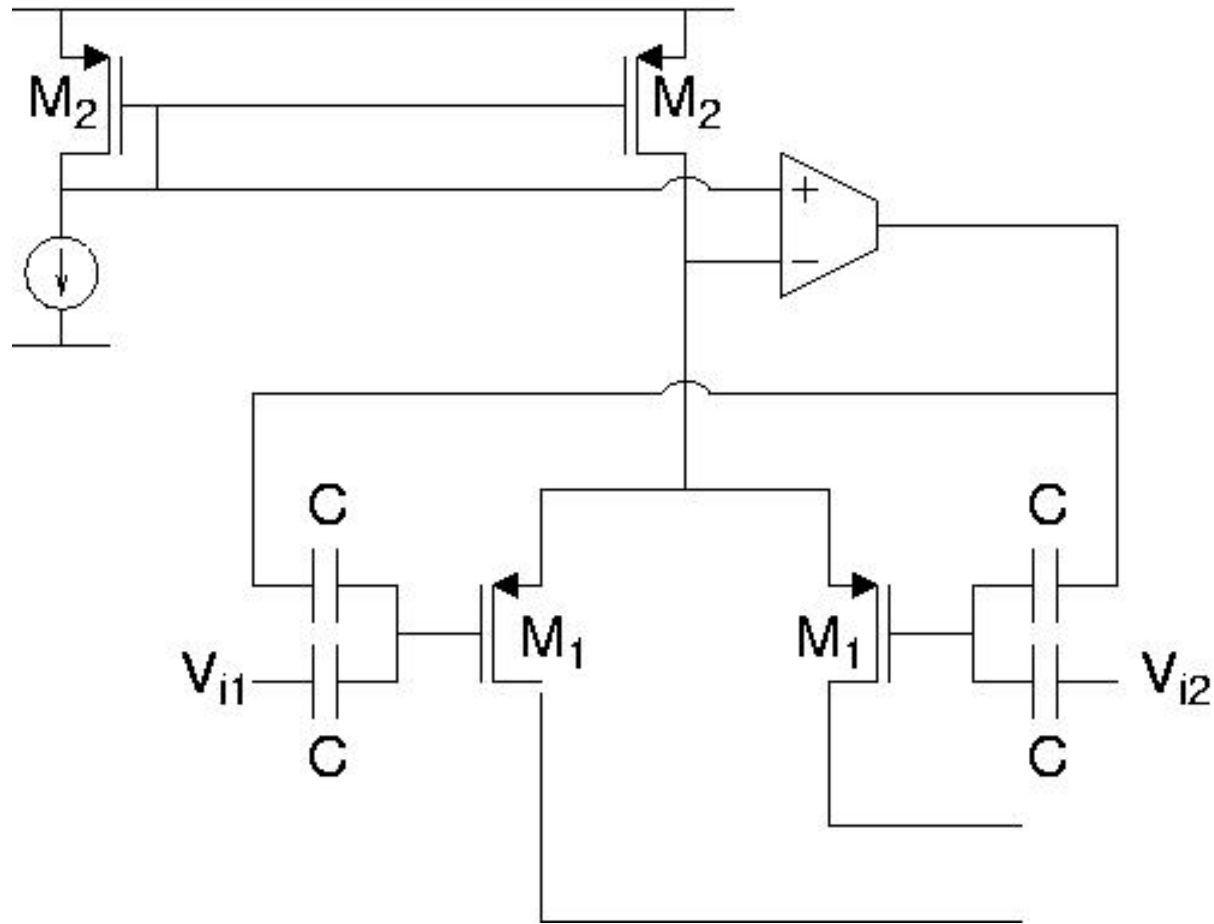

# Design Considerations

- Typically Floating Gate Caps are 5x-10x size of Parasitics


$$G_m = g_m \frac{C}{2C + C_{gs1} + C_{gd1} + C_{gb1}}$$

- What is effect of decreasing C?

# Design Considerations

- Decrease C, Increase  $W_1/L_1$  to compensate
- Increasing  $W_1/L_1$  increases size of parasitics, area
- Minimize total area
- $\text{Area}_{C,\text{drivers}} = 4C/C_{\text{poly}} + 2W_1L_1$
- Define  $C = RC_{\text{gs1}}$
- $\text{Area}_{C,\text{drivers}} = 8RW_1L_1C_{\text{ox}}/3C_{\text{poly}} + 2W_1L_1$
- Combine Area,  $G_m$  equations, find minimum R


# Minimized Area

 

# Complete Amplifier Design

- Proposed Input Transconductor
- Folded Cascode for High Gain
- Class-AB Output Stage for Rail-to-Rail Output Swing


# Die Micrograph

 
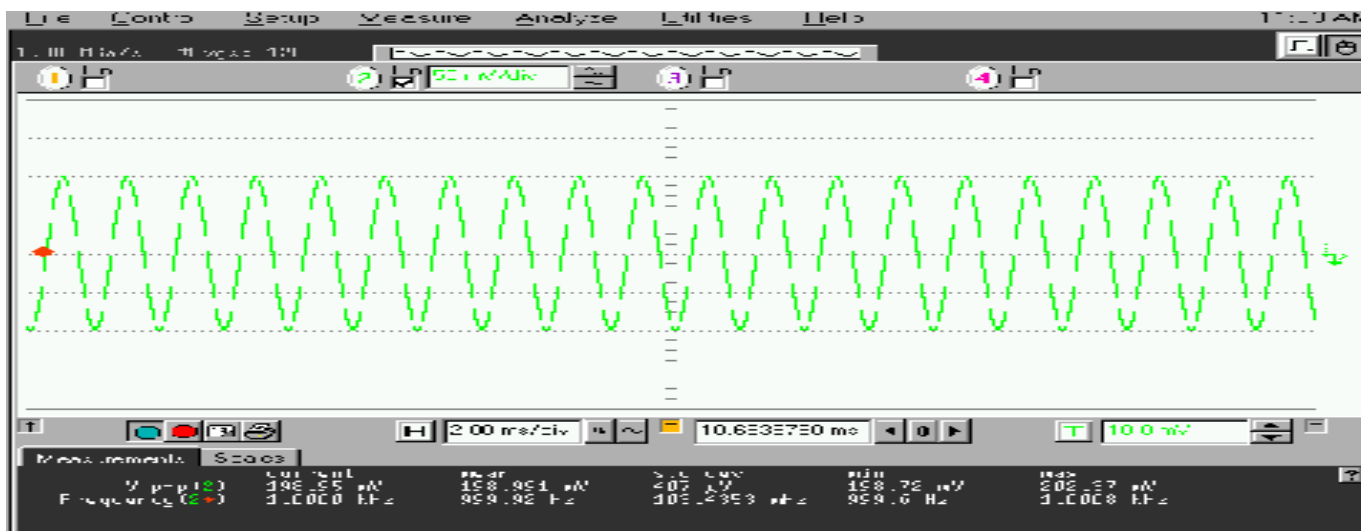
# Experimental Results – Input Stage




$V_{icm} = 4.4 V_{pp}$  50 Hz  
Triangle Wave




$V_{idm} = 0.1 \sin(2k\pi t)$

# Experimental Results – Input Stage

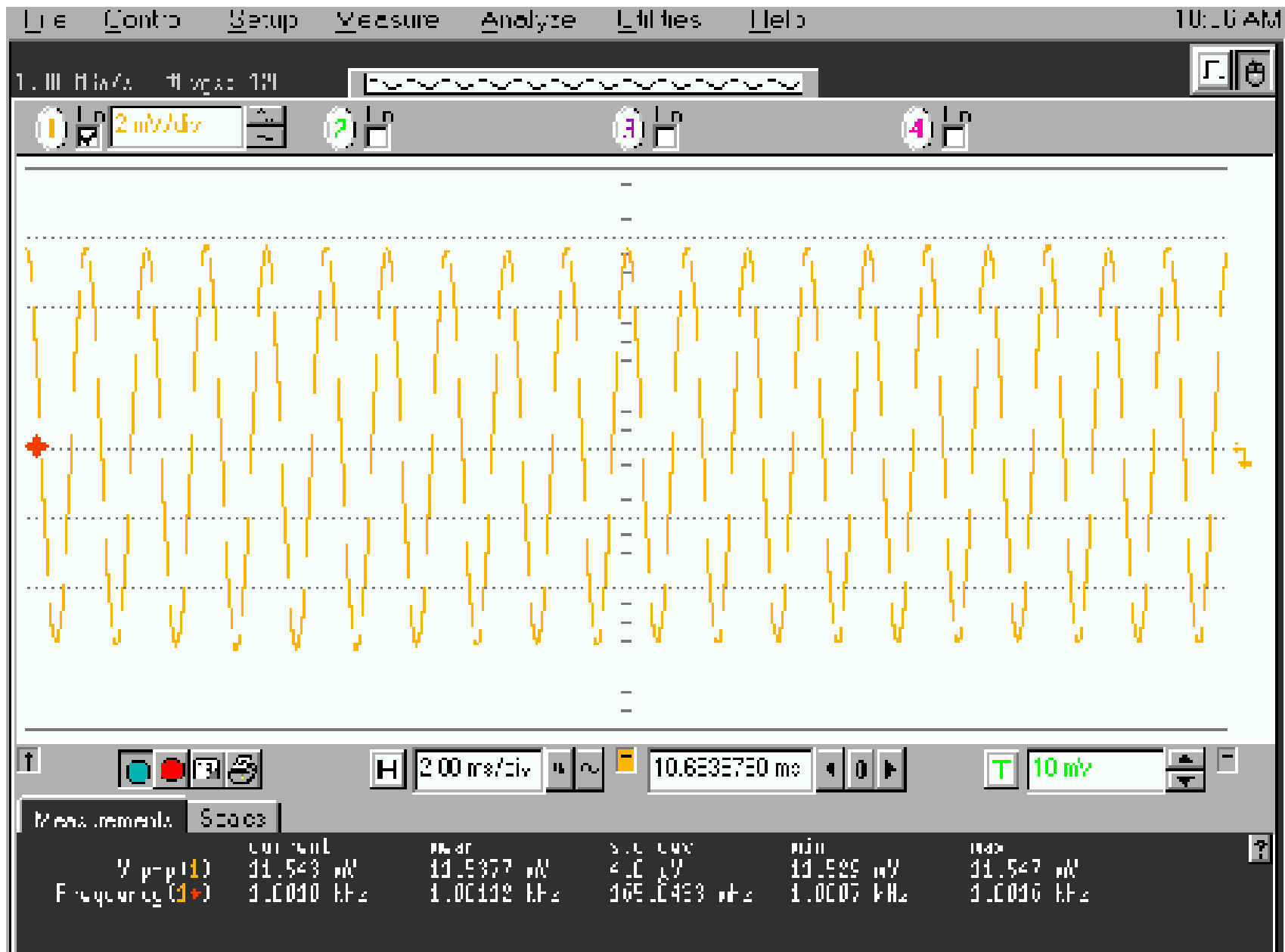




# Experimental Results – Input Stage

 

$G_m$  varies  $\pm 0.35\%$  from  $V_{SS}$  to  $V_{DD}$

$G_m$  varies  $\pm 1\%$  from  $-2\text{V}$  to  $2\text{V}$


# AC Gain – Complete Amplifier

 


$$A_{v0}=89\text{dB}$$

$$\text{GBW}=1.2\text{MHz}$$

# Unity Gain Step (Buffer)

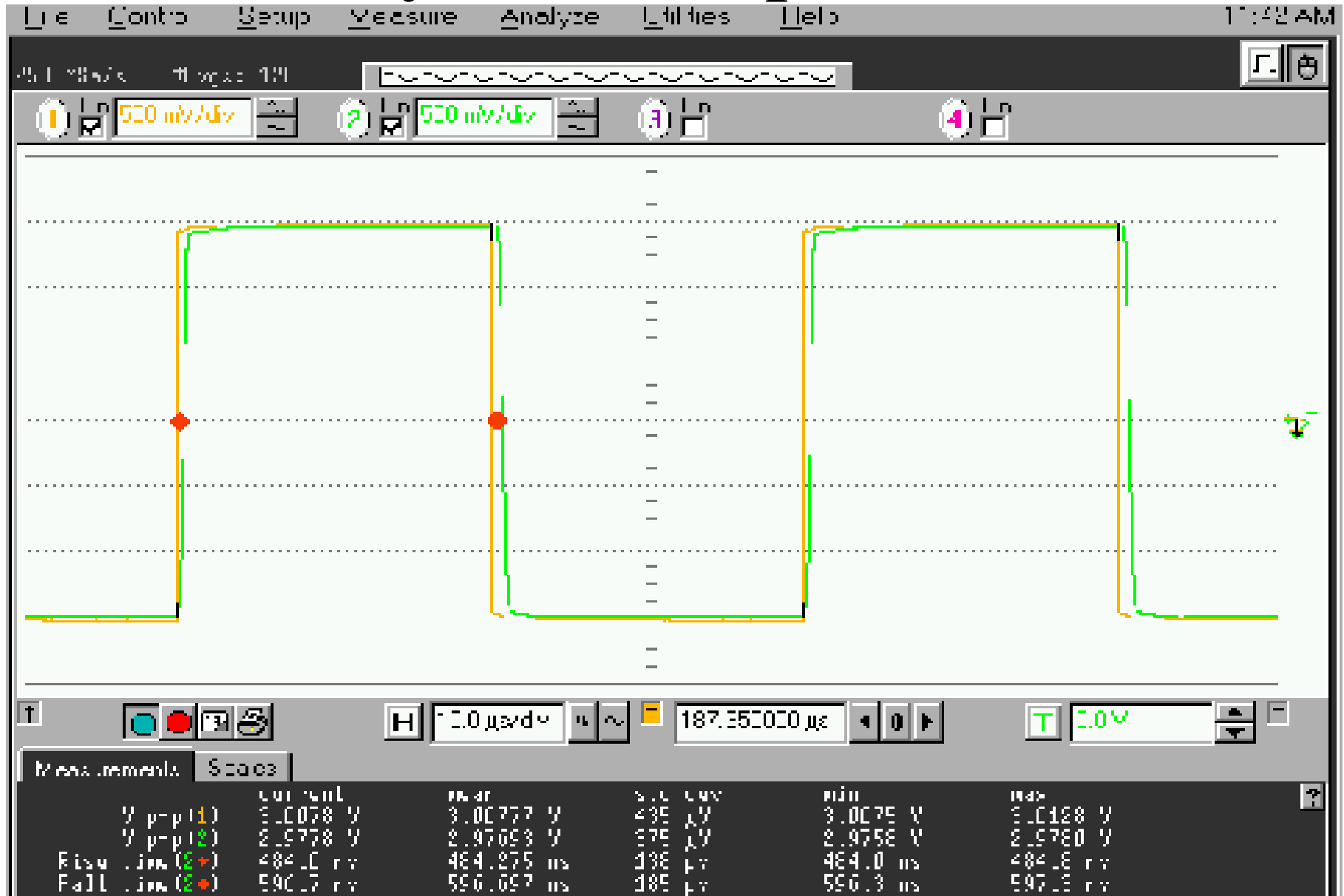

# Buffer Linearity

 

# Comparison to Other Work

Parameter	This Work	[1]	[2]	[3]	[4]	[5]
$\Delta G_m$	$\pm 0.35\%$	$\pm 1.5\%$	$\pm 4\%$	$\pm 3\%$	NA	$\pm 4.6\%$
$A_{v0}$ (dB)	89	70	110	84	60	59
GBW (MHz)	1.2	1	3.2	1.3	5	5.9
CMRR	80	NA	88	56	47	NA
SR (V/ $\mu$ s)	5	NA	5.8	1	7	6.4
Power (mW)	.51	NA	.31	.46	.19	NA
Area (mm <sup>2</sup> )	.36	NA	.12	1.2	.09	NA
Tech.	0.5 $\mu$ m	0.8 $\mu$ m	1.2 $\mu$ m	0.7 $\mu$ m	0.8 $\mu$ m	0.8 $\mu$ m


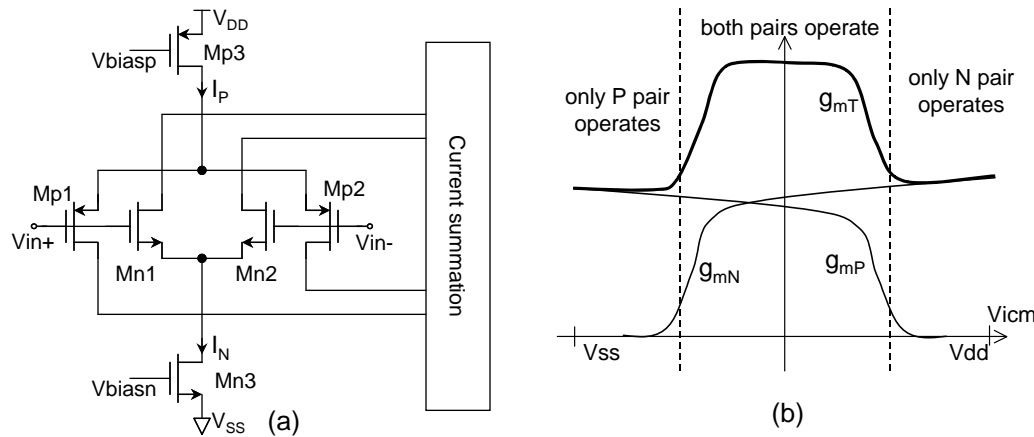
 


Fig. 1

IEEE TRANSACTIONS ON CIRCUITS AND SYSTEMS { I: FUNDAMENTAL THEORY AND APPLICATIONS 1

A Robust and Scalable Constant- $g_m$  Rail-to-Rail CMOS Input Stage with Dynamic Feedback for VLSI Cell Libraries

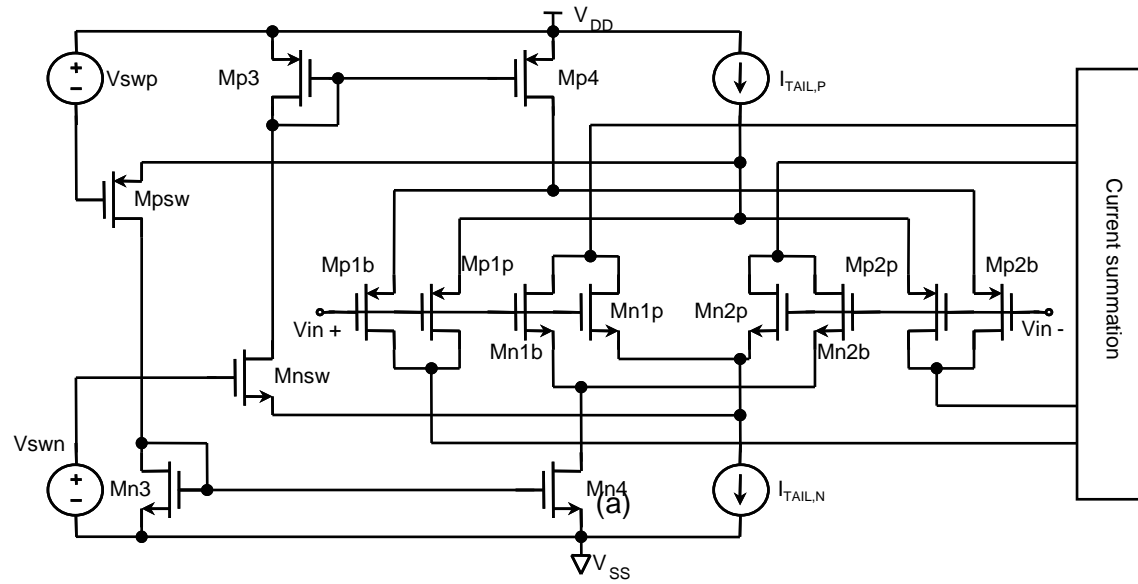Tongyu Song, *Student Member, IEEE*, Jingyu Hu, Xiaohong Li, Edgar Sanchez-Sinencio, *Fellow, IEEE*, and Shouli Yan, *Member, IEEE*



$$g_{mT} = \sqrt{\beta}(\sqrt{I_{TAIL}} + \sqrt{I_{TAIL} - I_x} + \sqrt{I_x}) \quad (4)$$


When  $I_x = I_{TAIL}/2$ ,  $g_{mT}$  reaches its maximum value, given by:

$$g_{mT,max} = \sqrt{\beta I_{TAIL}}(1 + \sqrt{2}) = g_{mT,nom} \frac{1 + \sqrt{2}}{2} \quad (5)$$

as illustrated in Fig. 2(b).

(b)


Fig. 2

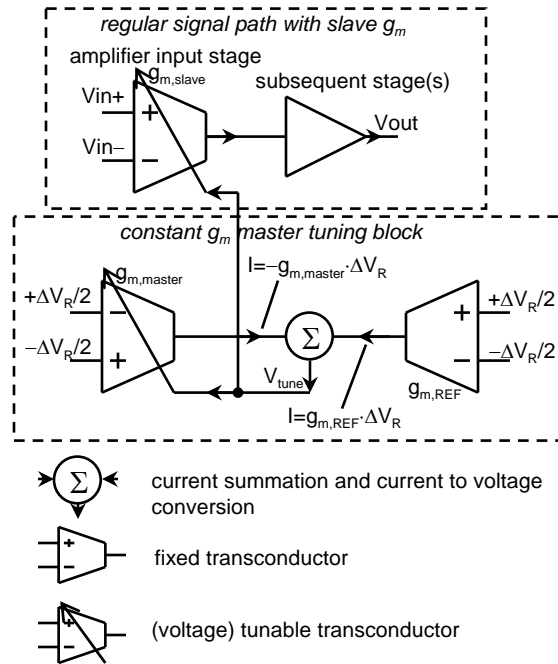

$$k = \frac{I_X}{I'_X} = \frac{g_{m,X}}{g'_{m,X}} \quad (6)$$

Fig. 3



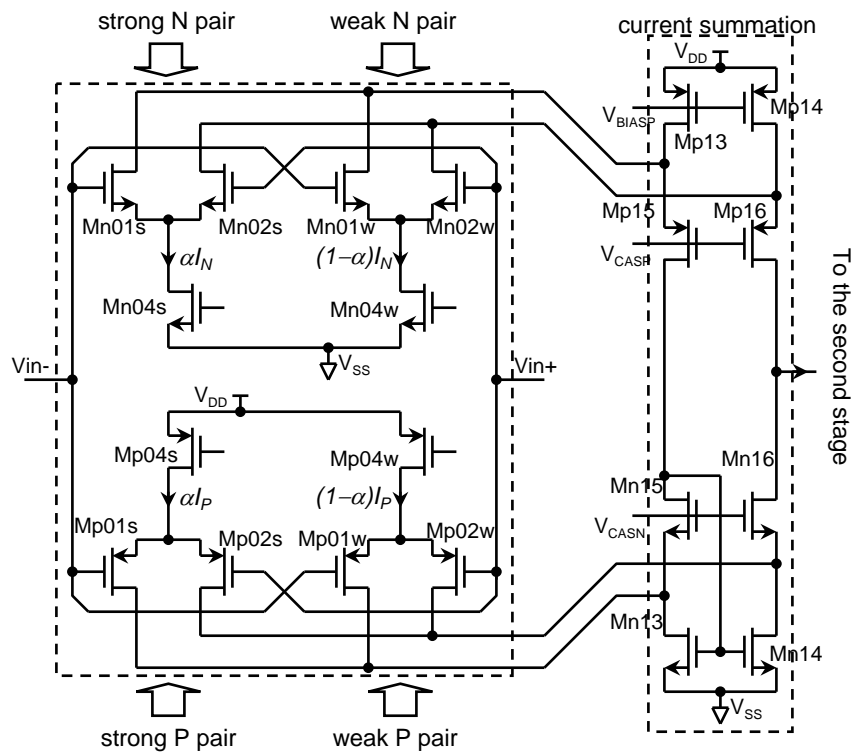

$$m = \frac{(W/L)_{N,strong}}{(W/L)_{N,weak}} = \frac{(W/L)_{P,strong}}{(W/L)_{P,weak}} \quad (7)$$

$$\begin{aligned} \beta_{strong} &= \mu_n C_{ox} (W/L)_{N,strong} \\ &= \mu_p C_{ox} (W/L)_{P,strong} \end{aligned} \quad (8)$$

and similarly

$$\begin{aligned} \beta_{weak} &= \mu_n C_{ox} (W/L)_{N,weak} \\ &= \mu_p C_{ox} (W/L)_{P,weak} \\ &= \frac{1}{m} \beta_{strong} \end{aligned} \quad (9)$$

Fig. 4 (old version)

The transconductance of the NMOS weak (narrow) pair is given by:

$$g_{mN,weak} = \sqrt{\frac{\beta_{strong}}{m}(1-\alpha)I_N} \quad (11)$$

The total transconductance of NMOS strong and weak composite pairs can be written as:

$$g_{mN} = (\sqrt{\alpha} + \sqrt{\frac{1-\alpha}{m}})\sqrt{\beta_{strong}I_N} = \sqrt{\beta_{eff}I_N} \quad (12)$$

where  $\beta_{eff}$  is defined as:

$$\beta_{eff} = (\sqrt{\alpha} + \sqrt{\frac{1-\alpha}{m}})^2\beta_{strong} \quad (13)$$

Similarly, the total transconductance of PMOS strong and weak composite pairs is given by:

$$g_{mP} = (\sqrt{\alpha} + \sqrt{\frac{1-\alpha}{m}})\sqrt{\beta_{strong}I_P} \quad (14)$$

where  $I_P$  is the total bias current of PMOS composite input pairs.

Therefore, the total transconductance of the NMOS and PMOS composite pairs is given by:

$$g_{mT} = g_{mN} + g_{mP} = \sqrt{\beta_{eff}}(\sqrt{I_N} + \sqrt{I_P}) \quad (15)$$

If the sum of  $I_P$  and  $I_N$  is kept constant, as  $I_P + I_N = I_{TAIL}$ ,  $(\sqrt{I_N} + \sqrt{I_P})$  varies from  $\sqrt{I_{TAIL}}$  to  $\sqrt{2I_{TAIL}}$ . This large  $g_m$  variation can be compensated for by changing the value of  $\beta_{eff}/\beta_{strong}$  from 0.5 to 1, as shown in Fig. 6. For example,

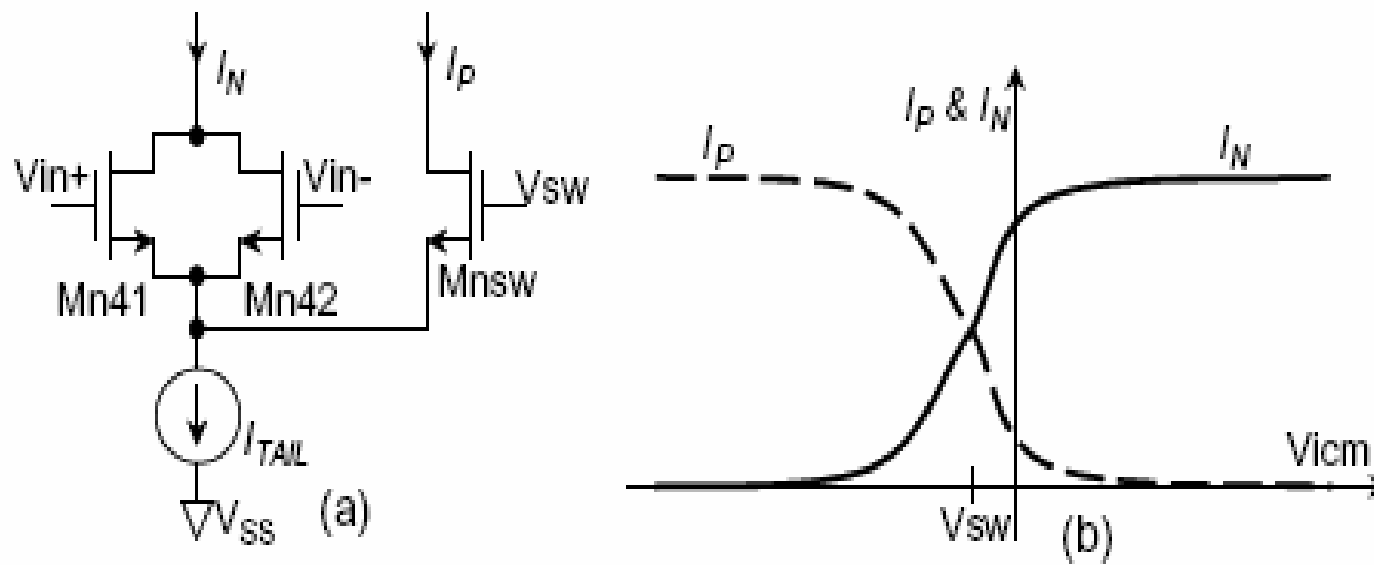


Fig. 5. Current switch circuit to keep  $I_N + I_P$  constant; (a) schematic; (b)  $I_N$  and  $I_P$  vs. input common-mode voltage.

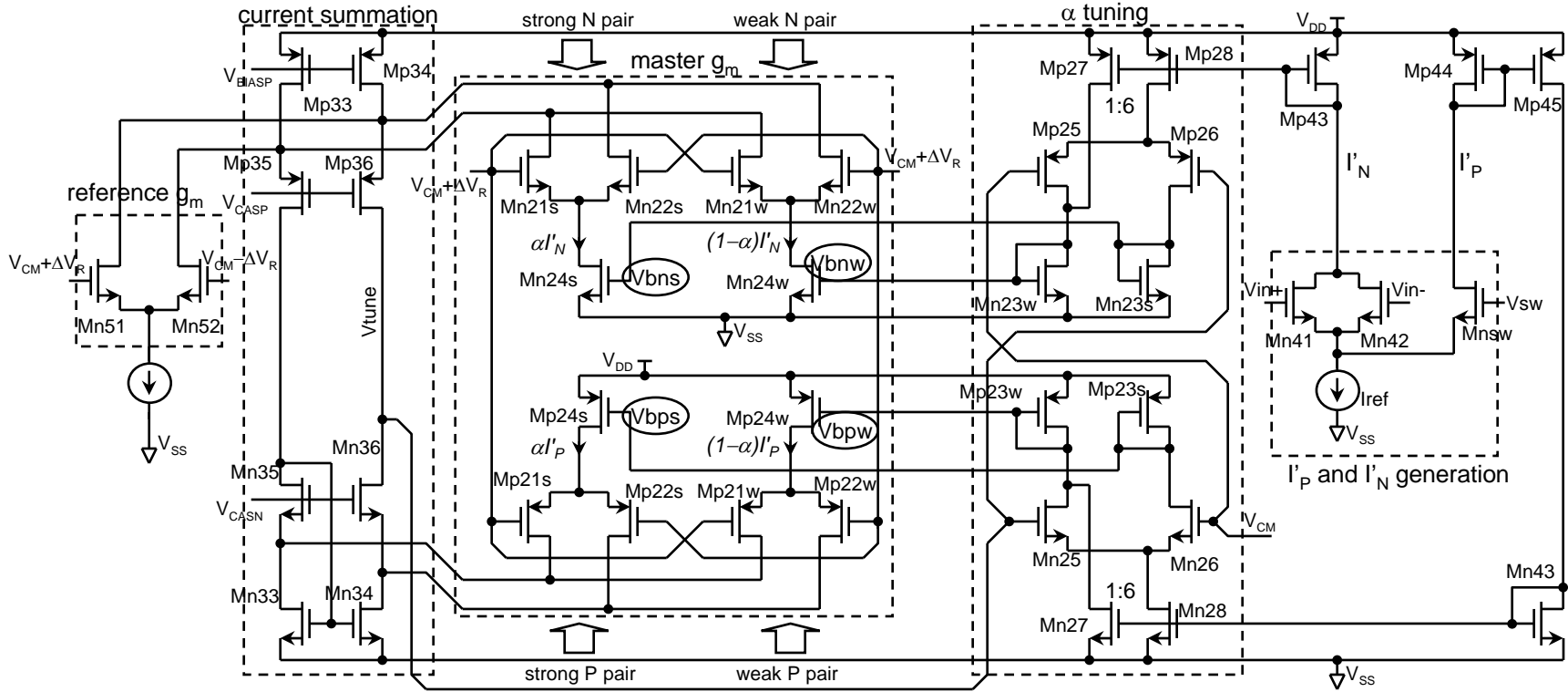
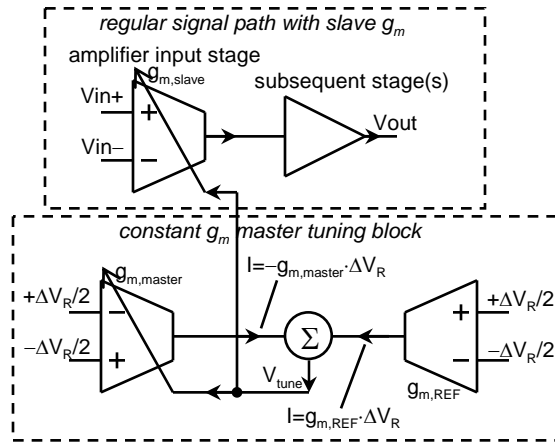


Fig. 7

 


Fig. 6.  $\beta_{eff}/\beta_{N,strong}$  vs.  $\alpha$  for different values of  $m$ .

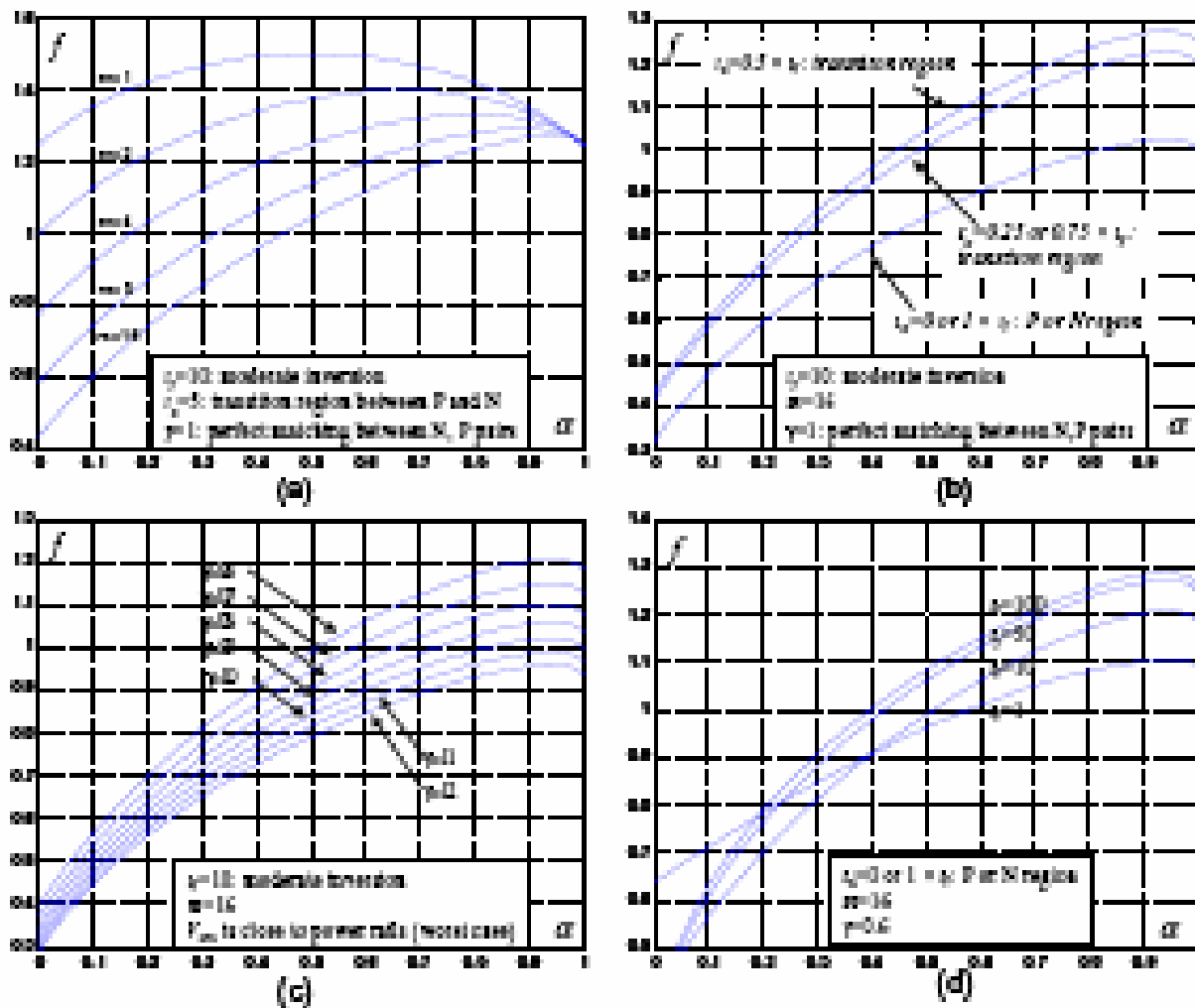


Fig. 8. Normalized total transconductance  $g_{mT}$  as a function of  $\alpha$ ; (a)  $f$  vs.  $\alpha$  with different values of  $m$ ; (b)  $f$  vs.  $\alpha$  with different input common mode voltages; (c)  $f$  vs.  $\alpha$  with process and temperature variations; (d)  $f$  vs.  $\alpha$  with different operation region of input transistors.

 


Fig. 10. Gain and phase of the dynamic feedback loop as a function of the input common mode voltage  $V_{CM}$ ; (a) gain magnitude (in dB) vs.  $V_{CM}$ ; (b) phase margin vs.  $V_{CM}$ .


 


Fig. 12. Measured total transconductance  $g_{mT}$  vs. input common mode voltage  $V_{cm}$ : (a) for a bias current  $I_{T,ALL} = 300\mu A$  and (b) for a bias current  $I_{T,ALL}$  varied from  $400\mu A$  to  $3\mu A$ .

 

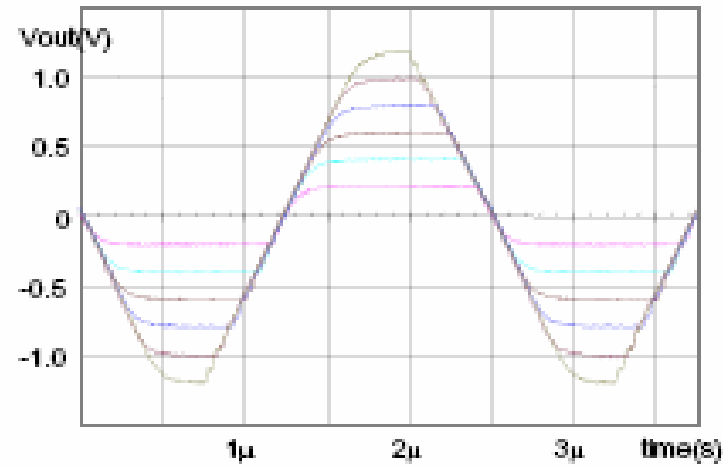


Fig. 13. Measured slew rate of the opamp in noninverting unity-gain configuration ( $C_L=150$  pF). The input is a 400 kHz square wave. Vertical axis: 0.5 V/div, horizontal axis: 0.5  $\mu$ s/div.

 


Fig. 14. Measured frequency response of the opamp in noninverting unity-gain configuration (load capacitance  $C_L=150$  pF).

TABLE I  
SUMMARY OF THE MEASURED PERFORMANCE

Transconductance $g_{mI}$	$1.895 \pm 0.025$ mA/V
Nominal bias current	$300 \mu\text{A}$
DC open loop voltage gain	$> 80$ dB
Unity gain frequency	1.1 MHz (CL = 180 pF)
Phase margin	$89^\circ$
Settling time of common-mode loop	$2 \mu\text{s}$
Supply voltage	3 V
Power consumption	3.3 mW
CMRR	$> 50$ dB
PSRR	$> 50$ dB
Slew rate+ / Slew rate -	$2.52/2.43$ V/ $\mu\text{s}$ (CL = 130 pF)
Input referred noise @ 100KHz / 1MHz	$48.4/21.0$ nV/ $\sqrt{\text{Hz}}$
Input referred offset	-6mV to 3mV; 1mV to 4mV variation from rail to rail
Active area	$0.09$ mm <sup>2</sup>
Technology	4-metal 2-poly 0.35 $\mu\text{m}$ CMOS

# References I

- [1] J. F. Duque-Carrillo, J. M. Carrillo, J. L. Ausin, and E. Sanchez-Sinencio, “Robust and universal constant- $g_m$  circuit technique,” *Electronics Letters*, vol. 38, no. 9, pp. 396-397, Apr. 2002.
- [2] M. Wang, T.L. Mayhugh, S.H.K. Embabi, and E. Sanchez-Sinencio, “Constant- $g_m$  Rail-to-Rail CMOS Op-Amp Input Stage with Overlapped Transition Regions,” *IEEE J. of Solid State Circuits*, vol. 34, no. 2, pp. 148-156, Feb. 1999.
- [3] G. Ferri and W. Sansen, “A Rail-to-Rail Constant- $g_m$  Low-Voltage CMOS Operational Transconductance Amplifier,” *IEEE J. of Solid State Circuits*, vol. 32, no. 10, pp. 1563-1567, Oct. 1997.
- [4] J. Ramirez-Angulo, R.G. Carvajal, J. Tombs, and A. Torralba, “Low-Voltage CMOS Op-Amp with Rail-toRail Input and Output Signal Swing for Continuous-Time Signal Processing Using Multiple-Input Floating-Gate Transistors,” *IEEE Trans. On Circuits and Systems – II*, vol. 48, no. 1, pp. 111-116, Jan 2001.
- [5] J.M. Carrillo, J.F. Duque-Carrillo, G. Torelli, and J.L. Ausin, “General Purpose rail-to-rail input circuit with constant behavior for VLSI cell libraries,” *IEEE International Symposium on Circuits and Systems*, vol. 3, pp. 607-610, May 2002.

## References II

- [1] J. H. Huijsing, and D. Linebarger, “Low voltage operational amplifier with rail-to-rail input and output stages,” *IEEE Journal of Solid-State Circuits*, vol. SC-20, no. 6, pp. 1144-1150, December 1985
- [2] W.-C. S. Wu, W. J. Helms, J. A. Kuhn, and B. E. Byrkett, “Digital-compatible high-performance operational amplifier with rail-to-rail input and output ranges,” *IEEE Journal of Solid-State Circuits*, vol. 29 , no. 1, pp. 63-66, January 1994
- [3] R. Hogervorst, R. J. Wiegerink, P. A. L. de Jong, J. Fonderie, R. F. Wassenaar, and J. H. Huijsing, “CMOS low-voltage operational amplifiers with constant-gm rail-to-rail input stage,” *IEEE Proc. ISCAS 1992*, pp. 2876-2879
- [4] R. Hogervost, J. P. Tero, R. G. H. Eschauzier and J. H. Huijsing, “A compact power-efficient 3-V CMOS rail-to-rail input/output operational amplifier for VLSI cell libraries,” *IEEE Journal of Solid-State Circuits*, vol. 29, no. 12, pp. 1505-1513, December 1994
- [5] R. Hogervorst, S. M. Safai, and J. H. Huijsing, “A programmable 3-V CMOS rail-to-rail opamp with gain boosting for driving heavy loads,” *IEEE Proc. ISCAS 1995*, pp. 1544-1547
- [6] J. H. Huijsing, R. Hogervorst, and K.-J. de Langen, “Low-power low-voltage VLSI operational amplifier cells,” *IEEE Trans. Circuits and Systems-I*, vol. 42. no. 11, pp. 841-852, November 1995

## References ( cont'd )

- [7] W. Redman-White, "A high bandwidth constant  $g_m$ , and slew-rate rail-to-rail CMOS input circuit and its application to analog cell for low voltage VLSI systems," *IEEE Journal of Solid-State Circuits*, vol. 32, no. 5, pp. 701-712, May 1997
- [8] C. Hwang, A. Motamed, and M. Ismail, "LV opamp with programmable rail-to-rail constant- $g_m$ ," *IEEE Proc. ISCAS 1997*, pp. 1988-1959
- [9] C. Hwang, A. Motamed, and M. Ismail, "Universal constant- $g_m$  input-stage architecture for low-voltage op amps," *IEEE Trans. Circuits and Systems-I*, vol. 42, no. 11, pp. 886-895, November 1995
- [10] R. Hogervost, J. P. Tero, and J. H. Huijsing, "Compact CMOS constant- $g_m$  rail-to-rail input stage with  $g_m$ -control by an electronic zener diode," *IEEE Journal of Solid-State Circuits*, vol. 31, no. 7, pp. 1035-1040, July 1996
- [11] M. Wang, T. L. Mayhugh, Jr., S. H. K. Embabi, and E. Sánchez-Sinencio, "Constant- $g_m$  rail-to-rail CMOS op-amp input stage with overlapped transition region," *IEEE Journal of Solid-State Circuits*, vol. 34, no. 2, pp. 148-156, February 1999
- [12] G. Ferri and W. Sansen, "A rail-to-rail constant- $g_m$  low-voltage CMOS operational transconductance amplifier," *IEEE Journal of Solid-State Circuits*, vol. 32, no. 10, pp. 1563-1567, October 1997

## References ( cont'd )

- [13] S. Sakurai and M. Ismail, "Robust design of rail-to-rail CMOS operational amplifiers for a low power supply voltage," *IEEE Journal of Solid-State Circuits*, vol. 31, no. 2, pp. 146-156, February 1996
- [14] J. H. Botma, R. F. Wassenaar, and R. J. Wiegerink, "Simple rail-to-rail low-voltage constant transconductance CMOS input stage in weak inversion," *Electronics Letters*, vol. 29, no. 12, pp. 1145-1147, June 1993
- [15] V. I. Prodanov and M. M. Green, "Simple rail-to-rail constant transconductance input stage operating in strong inversion," *IEEE 39<sup>th</sup> Midwest Symposium on Circuits and Systems*, vol 2, pp. 957-960, August 1996
- [16] J. H. Botma, R. F. Wassenaar, and R. J. Wiegerink, "A low voltage CMOS op amp with a rail-to-rail constant-gm input stage and a class AB rail-to-rail output stage," *IEEE Proc. ISCAS 1993*, vol. 2, pp. 1314-1317, May 1993
- [17] J. F. Duque-Carrillo, J. M. Valverde, and R. Perez-Aloe, "Constant-gm rail-to-rail common-mode range input stage with minimum CMRR degradation," *IEEE Journal of Solid-State Circuits*, vol. 28, no. 6, pp. 661-666, June 1993
- [18] A. L. Coban and P. E. Allen, "A low-voltage CMOS op amp with rail-to-rail constant-gm input stage and high-gain output stage," *IEEE Proc. ISCAS 1995*, vol. 2, pp. 1548-1551, April-May 1995

## References ( cont'd )

- [19] T. W. Fischer, A.I. Karsilayan, and E. Sánchez-Sinencio, “A Rail-to-Rail Amplifier Input Stage with  $\pm 0.35\%$  gm Fluctuation,” *IEEE Transactions On Circuits and Systems I*, vol. 52, No. 2, pp271-282, February 2005.
- [20] J. Hu, S. Yan, and E. Sánchez-Sinencio, “A Constant-GM Rail-to-Rail Op Amp Input Stage Using Dynamic Current Scaling Techniques,” *IEEE International Symposium on Circuits and Systems*, Kobe, Japan, May 23-26, 2005.
- [21] S. Yan, J. Hu, T. Song, and E. Sánchez-Sinencio, “Constant-gm Techniques for Rail-to-Rail CMOS Input Stages: A Comparative Study,” *IEEE International Symposium on Circuits and Systems 2005*, Kobe, Japan, May 23-26, 2005.
- [22] T. Song, J. Hu, X. Li, S. Yan and E. Sánchez-Sinencio, " [A Robust and Scalable Constant gm Rail-to-Rail CMOS Input Stage with Dynamic Feedback for VLSI Cell Libraries](#)", *IEEE Transactions on Circuits and Systems I*, pp804-816, Vol. 55, Issue 3, April 2008.