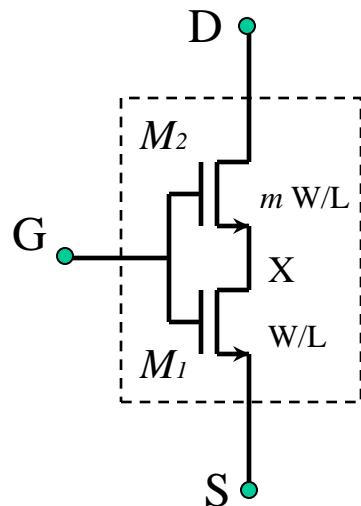


Low Voltage Circuit Design Techniques


ELEN 607 (ESS)

Analog and Mixed-Signal Center (AMSC)
Texas A&M University

What is a Self-Cascode Composite Transistor?



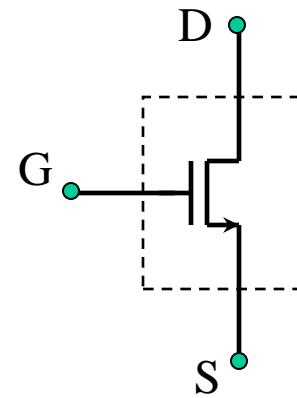(a) Self-Cascode Composite NMOS Transistor



(b) Equivalent Simple Transistor

In practical cases, for optimal operation the W/L ratio of M_2 should be larger than that of M_1 , *i.e.* $m > 1$.

The 2-transistor structure can be treated as a composite transistor, which has a much larger effective channel length (thus lower output conductance).

Working Conditions [5]

For the composite transistor to function properly, both M_2 and M_1 should conduct, thus, the following conditions should be satisfied:

$$V_G - V_X - V_T > 0 \quad (1)$$

$$V_G - V_S - V_T > 0 \quad (2)$$

We can rewrite (1) as:

$$V_X - V_S < V_G - V_S - V_T = V_{DSAT} \quad (3)$$

From (3) we know that transistor M_1 must be in linear region. Depending on the drain voltage, transistor M_2 can work in saturation region or linear region.

Equivalent Transistor Parameter (I)

For the composite transistor work in saturation region, we know M_2 should be in saturation and M_1 is in linear region. Thus, we can write equations for these two transistors as:

$$i_1 = \frac{\beta_2}{2} (V_{GS} - V_x - V_T)^2 \quad i_1 = \beta_1 \left(V_{GS} - V_T - \frac{1}{2} V_x \right) V_x$$

Solving i_1 we can obtain:

$$i_2 = \frac{1}{2} \frac{\beta_2 \beta_1}{\beta_2 + \beta_1} (V_{GS} - V_T)^2$$

From (3), we have $\beta_{eq} = \frac{\beta_2 \beta_1}{\beta_2 + \beta_1}$

If $\beta_2 = m \cdot \beta_1 \quad \beta_{eq} = \frac{m}{m+1} \beta_1 = \frac{1}{m+1} \beta_2$

$$\rightarrow \beta_{eq} \Big|_{m \rightarrow \infty} = \beta_1$$



Comments on V_{DSAT}


Because transistor M_1 always operates in linear region while the top transistor operates in saturation or linear region. Voltage between the source and drain terminal of M_1 is so small that there is no discernable V_{DSAT} difference in both the composite and simple transistors. Thus, self-cascode structure can be used in ***low voltage applications***.

$$V_{DSAT-eq} = V_{DSAT-M2} + V_{DS-M1} = V_{DSAT-M2} + I_{D2}R_{M1}$$

where $R_{M1} = \frac{1}{\mu C_{ox} (V_{GS} - V_T) \frac{W}{L}}$

The operating voltage of a regular cascode circuit is much higher than that of a single transistor. This characteristic makes regular cascode circuit not suitable for low voltage applications.

DC Simulation Results (I)

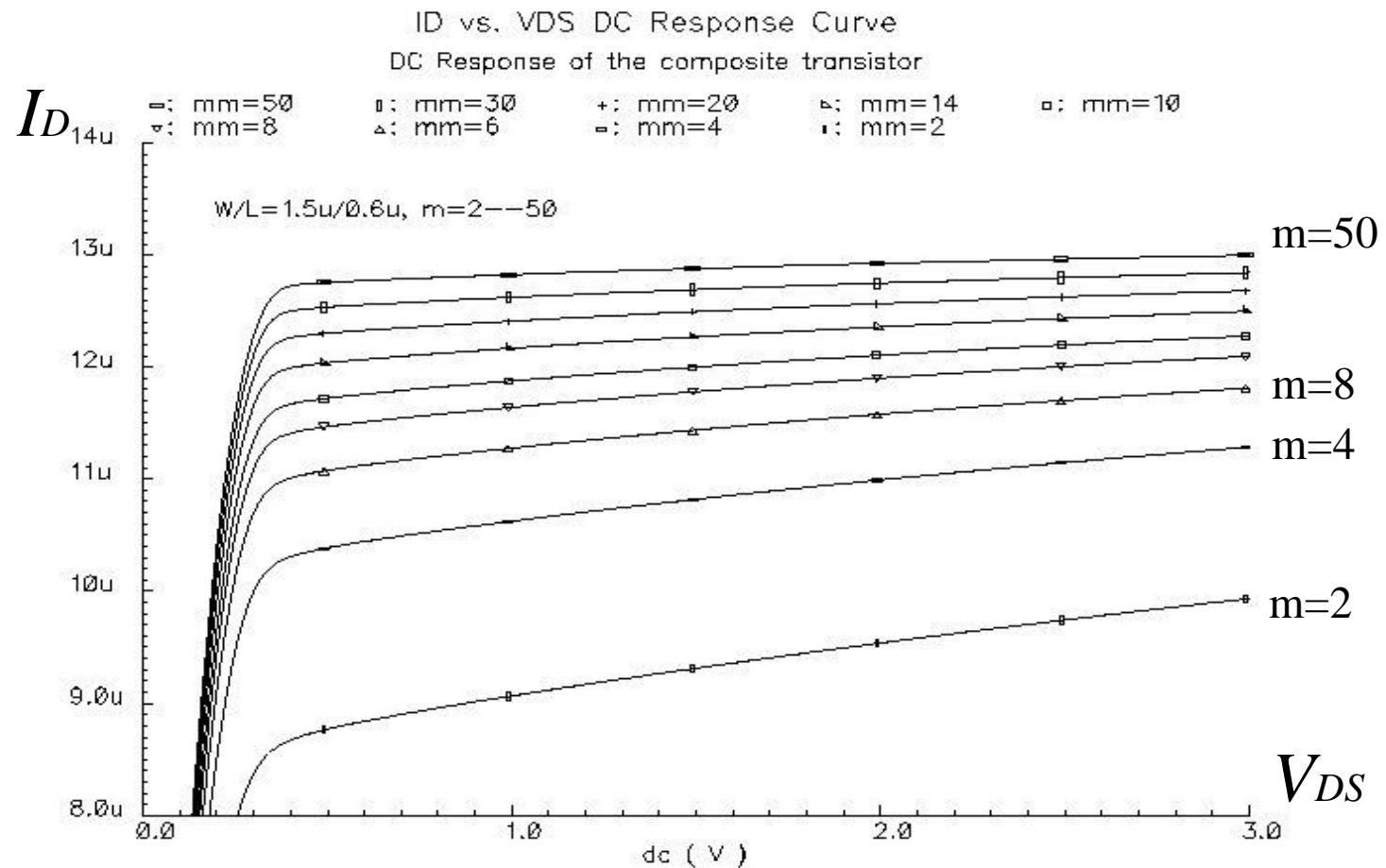

Effect of “ m ” on the output characteristics

DC Simulation Results (II)

From simulations (TMSC 0.35um process), we observe that:

m	W/L	Equivalent W/L
2	1.5/0.6	1.7/0.9
4	1.5/0.6	2.5/1.5
6	1.5/0.6	3.0/2.1
8	1.5/0.6	3.3/2.4
10	1.5/0.6	3.8/3.0
20	1.5/0.6	20/24

When m is larger, the effective length L is also larger

Equivalent (W/L)Transistor Parameter

Because β is proportional to W/L, we can have the equivalent W/L derived from previous results:


$$\left(\frac{W}{L}\right)_{eq} = \frac{\left(\frac{W}{L}\right)_2 \cdot \left(\frac{W}{L}\right)_1}{\left(\frac{W}{L}\right)_2 + \left(\frac{W}{L}\right)_1}$$

If lengths of M_2 and M_1 are equal, and M_2 is m times wider than M_1 , the equivalent W/L ratio is:

$$\left(\frac{W}{L}\right)_{eq} = \frac{m}{m+1} \left(\frac{W}{L}\right)_1 = \frac{1}{m+1} \left(\frac{W}{L}\right)_2$$

Equivalent Output Impedance


(Low frequency small signal)

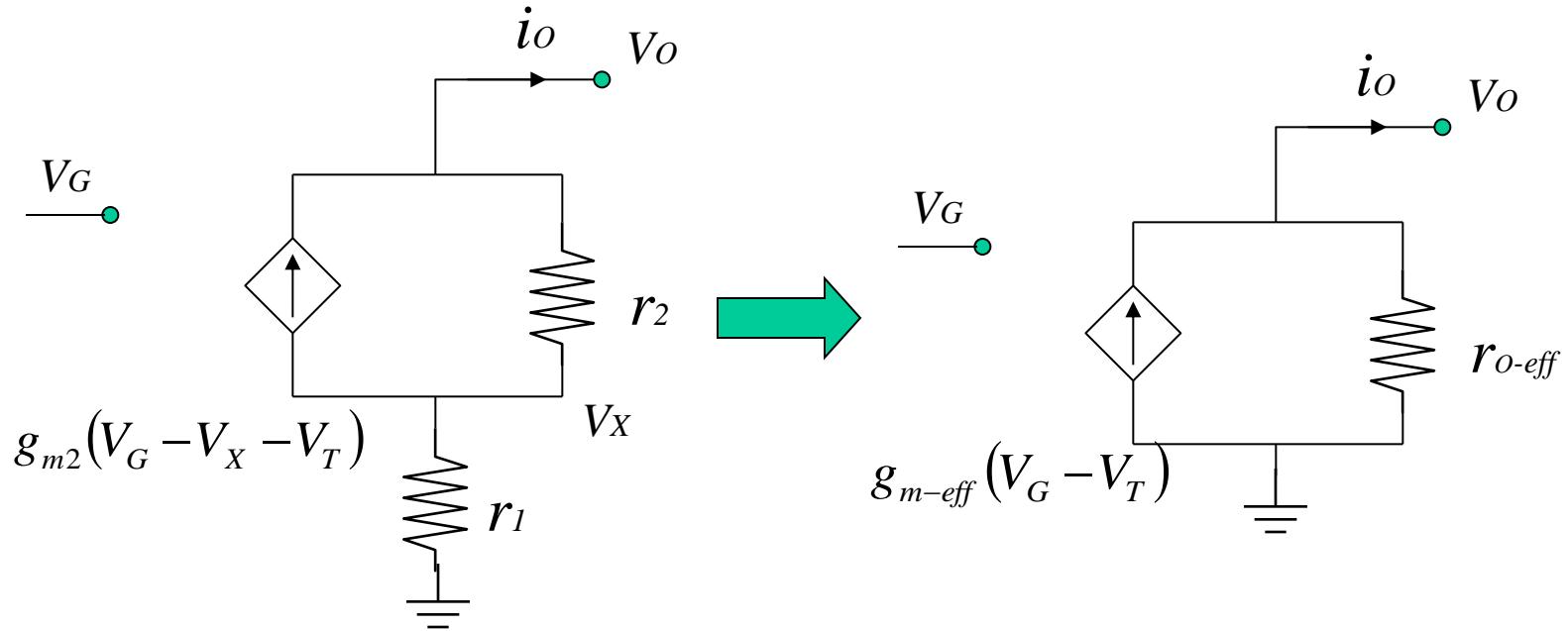

The equivalent output impedance of the composite transistor is:

$$r_o = g_{m2} r_2 r_1 - r_2 - r_1 \approx (g_{m2} r_1 - 1) r_2 = (m \cdot g_{m1} r_1 - 1) r_2 = (m - 1) \cdot r_2$$
$$(m \gg 1)$$


Effective Transconductance

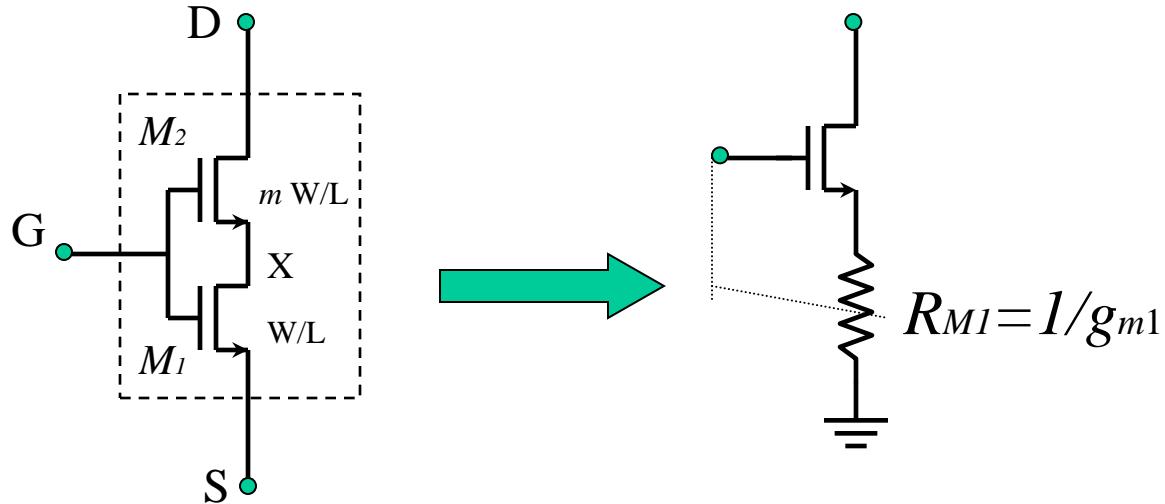

The lower transistor M_1 is equivalent to a resistor. But this resistor is input dependent.. The effective transconductance of the composite transistor is approximately equal to the transconductance of M_1 :

$$g_{m\text{-eff}} = g_{m2}/m = g_{m1}$$

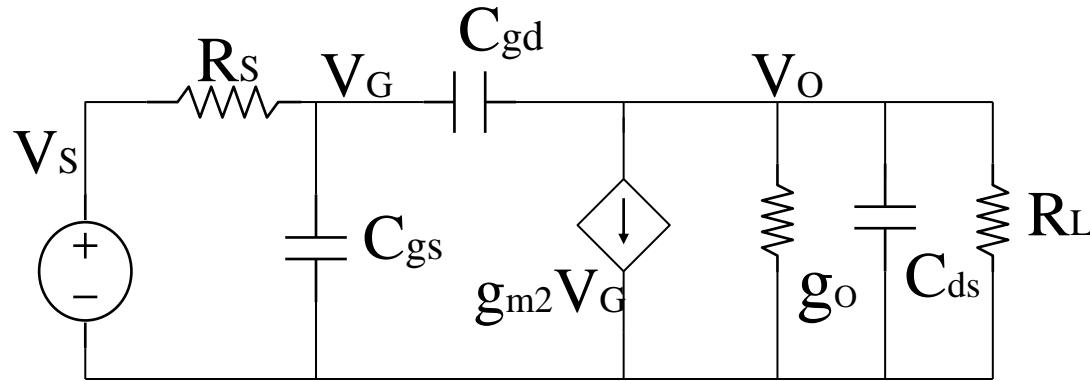Small-Signal Equivalent Circuit (Single Transistor)



Equations:

$$\frac{V_G - V_S}{R_S} + V_G \cdot sC_{gs} + (V_G - V_O) \cdot s \cdot C_{gd} = 0$$

$$\frac{V_O}{R_L} + V_O \cdot g_o + V_O \cdot s \cdot C_{ds} + g_{m2} \cdot V_G + (V_O - V_G) \cdot s \cdot C_{gd} = 0$$

Solve this equation set we can obtain the voltage gain as a function of the frequency:

$$A_2 = (C_{gs}C_{gd} + C_{gs}C_{ds} + C_{ds}C_{gd}) \cdot R_L$$

$$A_1 = (g_{m1}C_{gd} + g_0C_{gd} + g_0C_{gs} + g_{m2}C_{gd}) \cdot R_L$$

$$A_0 = -g_{m1}g_{m2} \cdot R_L$$

$$B_2 = (g_{m1}R_L R_S + R_L + R_S)(C_{gs}C_{ds} + C_{gs}C_{gd} + C_{ds}C_{gd})$$

$$B_1 = (C_{gs} + C_{ds}) + (C_{gd} + C_{ds}) \cdot g_{m1}R_L + (C_{gs} + C_{gd})(g_{m1}R_S + g_0R_L g_{m1}R_S + g_0R_S + g_0R_L) + C_{gd}g_{m2}(R_L + R_S + g_{m1}R_L R_S)$$


$$B_0 = g_{m2} + g_0 + g_{m1} + g_{m1}R_L g_0$$

This function has 2 poles and 2 zeros, but it is too complex!

$$A_V(s) = \frac{A_2 s^2 + A_1 s + A_0}{B_2 s^2 + B_1 s + B_0}$$



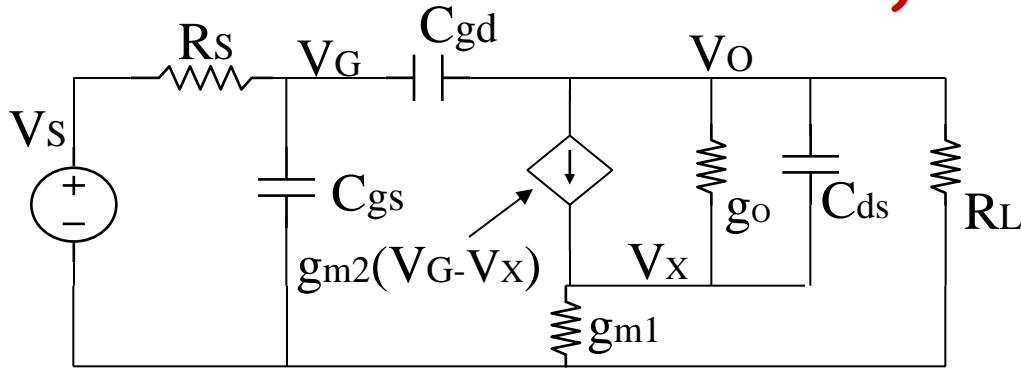Small-Signal Equivalent Circuit (Composite Transistor)



$$A_V(s) = \frac{A_2 s^2 + A_1 s + A_0}{B_2 s^2 + B_1 s + B_0}$$

Circuit Equations

$$(V_G - V_S)/R_S + V_G \cdot s C_{gs} + (V_G - V_O) \cdot s \cdot C_{gd} = 0$$

$$\frac{V_O}{R_L} + (V_O - V_X) \cdot (g_o + s \cdot C_{ds}) + g_{m2} \cdot (V_G - V_X) + (V_O - V_G) \cdot s \cdot C_{gd} = 0$$

$$V_X \cdot g_{m1} - g_{m2} \cdot (V_G - V_X) + (V_X - V_O) \cdot (g_o + s \cdot C_{ds}) = 0$$

Solving this equation set we can obtain the voltage gain as a function of the frequency:

$$A_2 = (C_{gs} C_{gd} + C_{gs} C_{ds} + C_{ds} C_{gd}) \cdot R_L$$

$$A_1 = (g_{m1} C_{gd} + g_0 C_{gd} + g_0 C_{gs} + g_{m2} C_{gd}) \cdot R_L$$

$$A_0 = -g_{m1} g_{m2} \cdot R_L$$

$$B_2 = (g_{m1} R_L R_S + R_L + R_S)(C_{gs} C_{ds} + C_{gs} C_{gd} + C_{ds} C_{gd})$$

$$B_0 = g_{m2} + g_0 + g_{m1} + g_{m1} R_L g_0$$

$$B_1 = (C_{gs} + C_{ds}) + (C_{gd} + C_{ds}) \cdot g_{m1} R_L + (C_{gs} + C_{gd}) (g_{m1} R_S + g_0 R_L g_{m1} R_S + g_0 R_S + g_0 R_L) + C_{gd} g_{m2} (R_L + R_S + g_{m1} R_L R_S)$$

Effect of the Capacitor C_{gd} (Simple)

Let's assume $C_{gs} = 0$ $C_{ds} = 0$ $R_L g_0 \ll 1$, thus

$$\begin{aligned} A_1 &= C_{gd} R_L & B_2 &= 0 \\ A_0 &= -g_{m2} R_L & B_1 &= C_{gd} R_L R_S g_0 + C_{gd} \cdot R_L + (g_{m2} R_L + 1) R_S C_{gd} \\ A_2 &= 0 & & \cong C_{gd} R_S g_{m2} R_L \\ & & B_0 &= R_L g_0 + 1 \cong 1 \end{aligned}$$

The simplified transfer function is:

$$A_V(s) = \frac{A_1 s + A_0}{B_1 s + B_0}$$

This means that if we consider the effect of only C_{gd} , the function is simplified to one pole and one zero

One zero:

$$\omega_Z = \frac{g_{m2}}{C_{gd}}$$

One pole:

$$\omega_P = \frac{1}{g_{m2} R_L R_S C_{gd}}$$

Effect of the Capacitor C_{gd} (Composite)

Let's assume $C_{gs} = 0$ $C_{ds} = 0$ $R_L g_0 \ll 1$, thus

$$A_2 = 0$$

$$A_1 = (g_{m1}C_{gd} + g_0C_{gd} + g_{m2}C_{gd}) \cdot R_L \cong (g_{m1} + g_{m2}) \cdot C_{gd} R_L$$

$$A_0 = -g_{m1}g_{m2} \cdot R_L$$

$$B_2 = 0$$

$$\begin{aligned} B_1 &= C_{gd} \cdot (g_{m1}R_L + g_{m1}R_S + g_0R_Lg_{m1}R_S + g_0R_S + g_0R_L + g_{m2}R_L + g_{m2}R_S + g_{m1}g_{m2}) \\ &\cong C_{gd}g_{m2}R_L \cdot (1 + g_{m1}R_S) \end{aligned}$$

$$B_0 = g_{m2} + g_0 + g_{m1} + g_{m1}R_Lg_0 \cong g_{m2}$$

The simplified transfer function is:

$$A_V(s) = \frac{A_1 s + A_0}{B_1 s + B_0}$$

One zero:

$$\omega_Z = \frac{g_{m1}g_{m2}}{(g_{m1} + g_{m2})C_{gd}} \cong \frac{g_{m1}}{C_{gd}}$$

One pole:

$$\omega_P = \frac{1}{(1 + g_{m1}R_S)R_L C_{gd}} \cong \frac{1}{g_{m1}R_S R_L C_{gd}}$$

Comments on the Poles and Zeros

Consider the effect of C_{gd} only, we can get the following conclusion:

The pole of the simple transistor is higher than that of the composite transistor.

$$\frac{\omega_{Z-Composite}}{\omega_{Z-Simple}} = \frac{g_{m1}}{g_{m2}} = \frac{1}{m}$$

The same conclusion can be applied to zeros:

$$\frac{\omega_{P-Composite}}{\omega_{P-Simple}} = \frac{g_{m1}}{g_{m2}} = \frac{1}{m}$$

Frequency Parameters

The transition time τ increases as the value of m .
According to reference[1], The relationship is:

$$\tau \cong \tau_u \left(1 + \sqrt{1 + m}\right)$$

Where τ_u is the transition time of an unit transistor used in the self-cascode structure.

For the saturated MOS transistor in strong inversion parameters ω_T (Cutoff frequency) and τ are related by:

$$\tau\omega_T = 2$$

Advantage of the Self-Cascode Structure

The main advantage of this structure is smaller transistor area. The sum of areas of M_D and M_S is smaller than the area of the equivalent simple transistor.

The table below shows the simulation results with MOSIS TSMC 0.35u CMOS process:

MS W/L	m	MD W/L	Equivalent FET W/L	Area Ratio*	Gain (RL=inf.)
3.0/0.6u	3	9.0u/0.6u	5.6u/1.2u	7.2/6.72	42dB
3.0u/0.6u	8	24.0u/0.6u	38.5u/12.0u	16.2/462.0	47dB
1.5u/0.6u	11	16.5u/0.6u	9.9u/12.0u	10.8/118.8	44dB

* COMPOSITE/SINGLE



For equal chip area:

$$A_{V-CASCODE} > A_{V-SELF-CASCODE} > A_{V-SIMPLE-TRANSISTOR}$$

To achieve the same voltage gain:


$$AREA_{CASCODE} < AREA_{SELF-CASCODE} < AREA_{SIMPLE-TRANSISTOR}$$

Applications (I)--Current Mirror

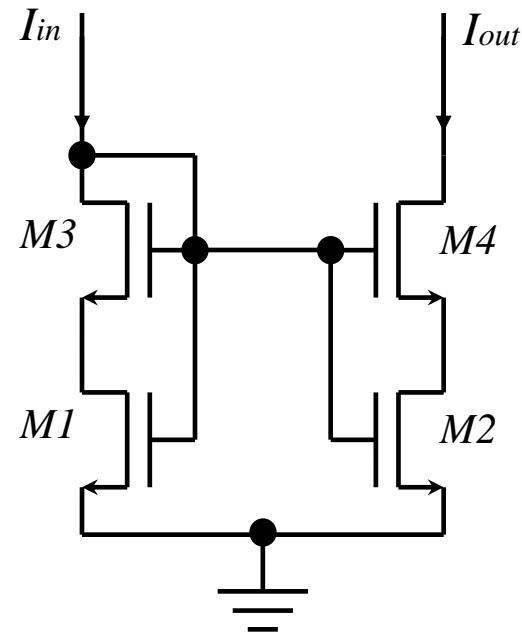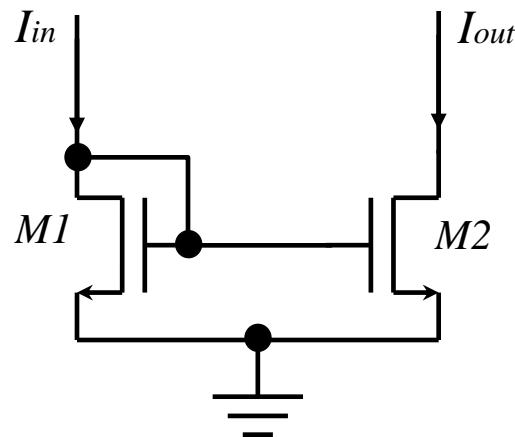


Simple transistors can be substituted with self-cascode structure to achieve better performance. (i.e. higher output impedance)

Schematic of the Circuit for Simulation

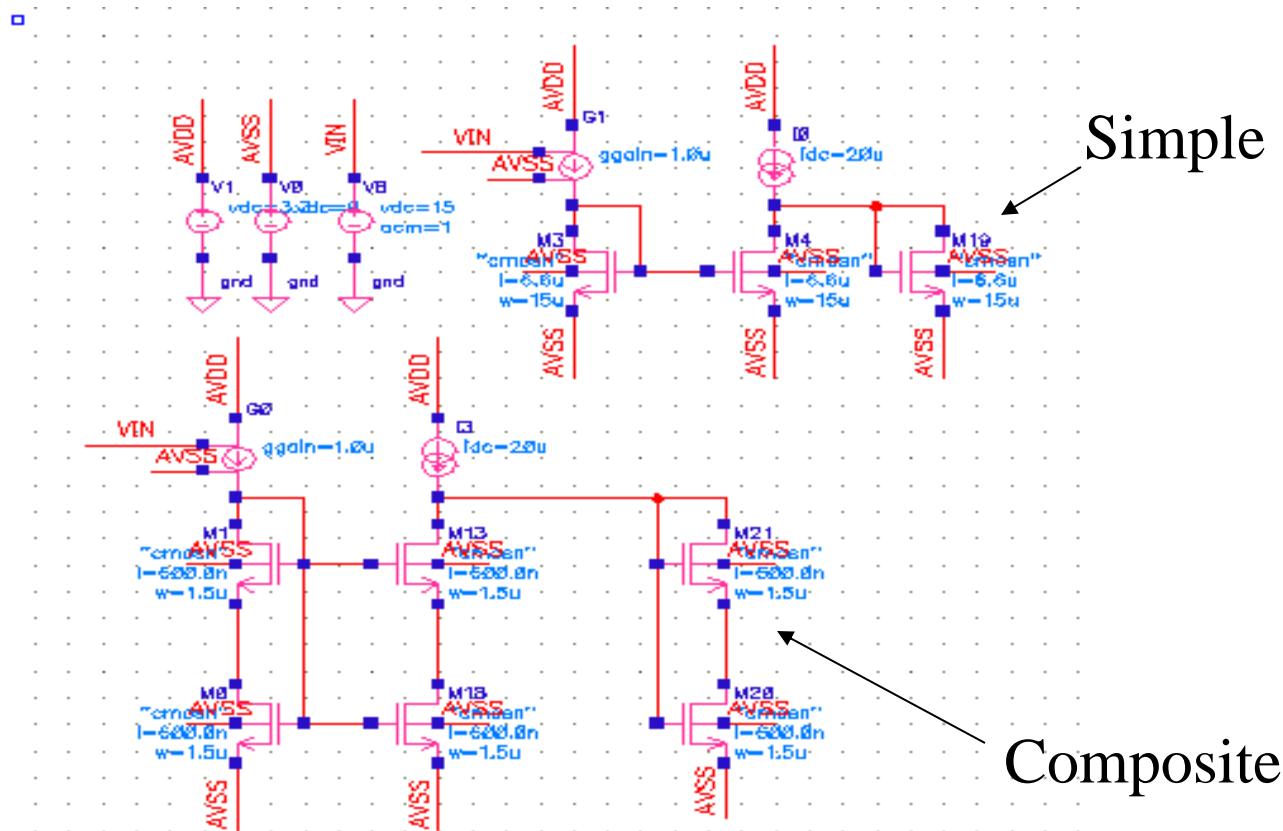


Model: TMSC 0.35um CMOS Process


Current Mirror Simulation Results (DC)

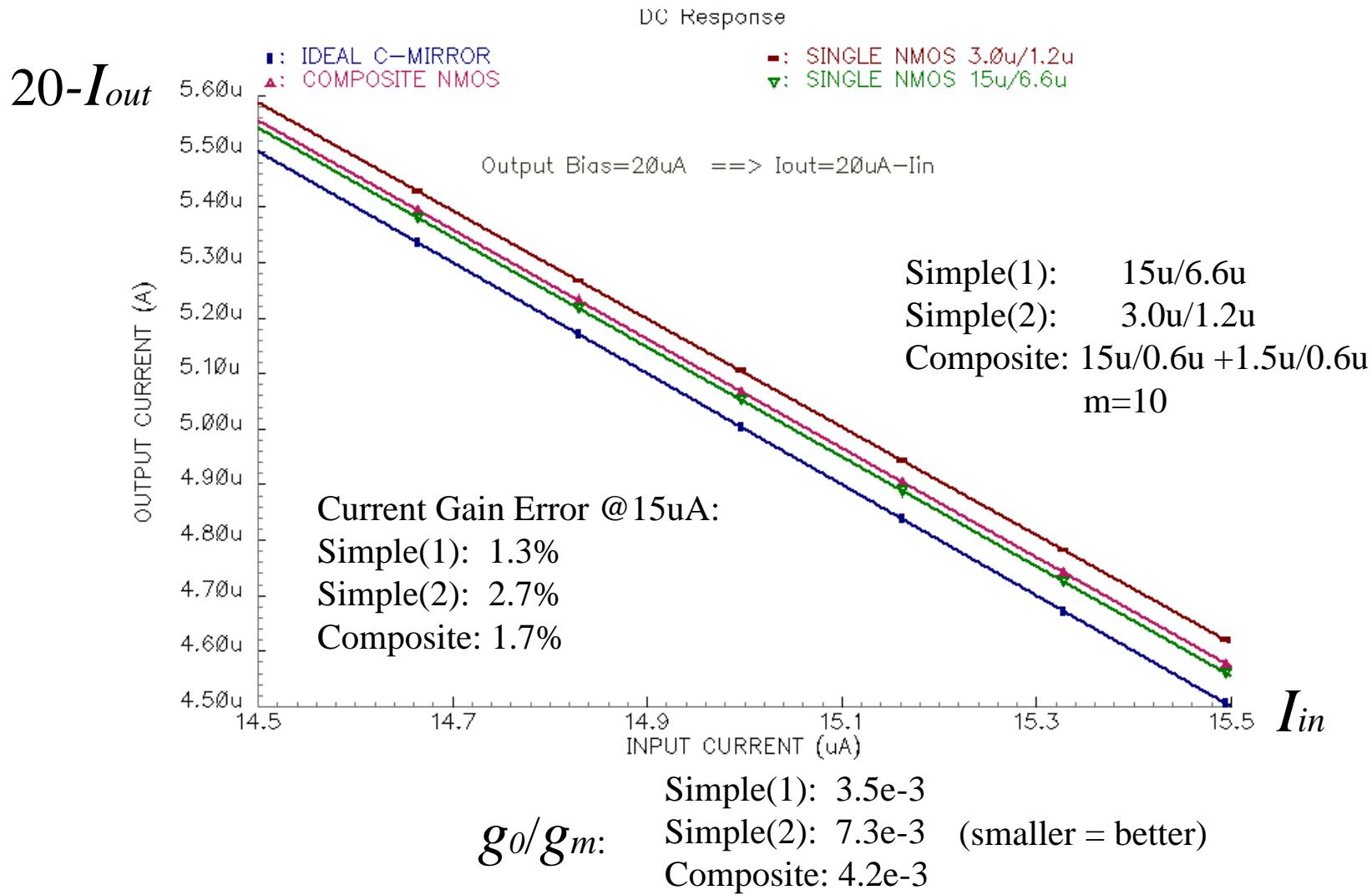

Current Mirror Simulation Results (AC)

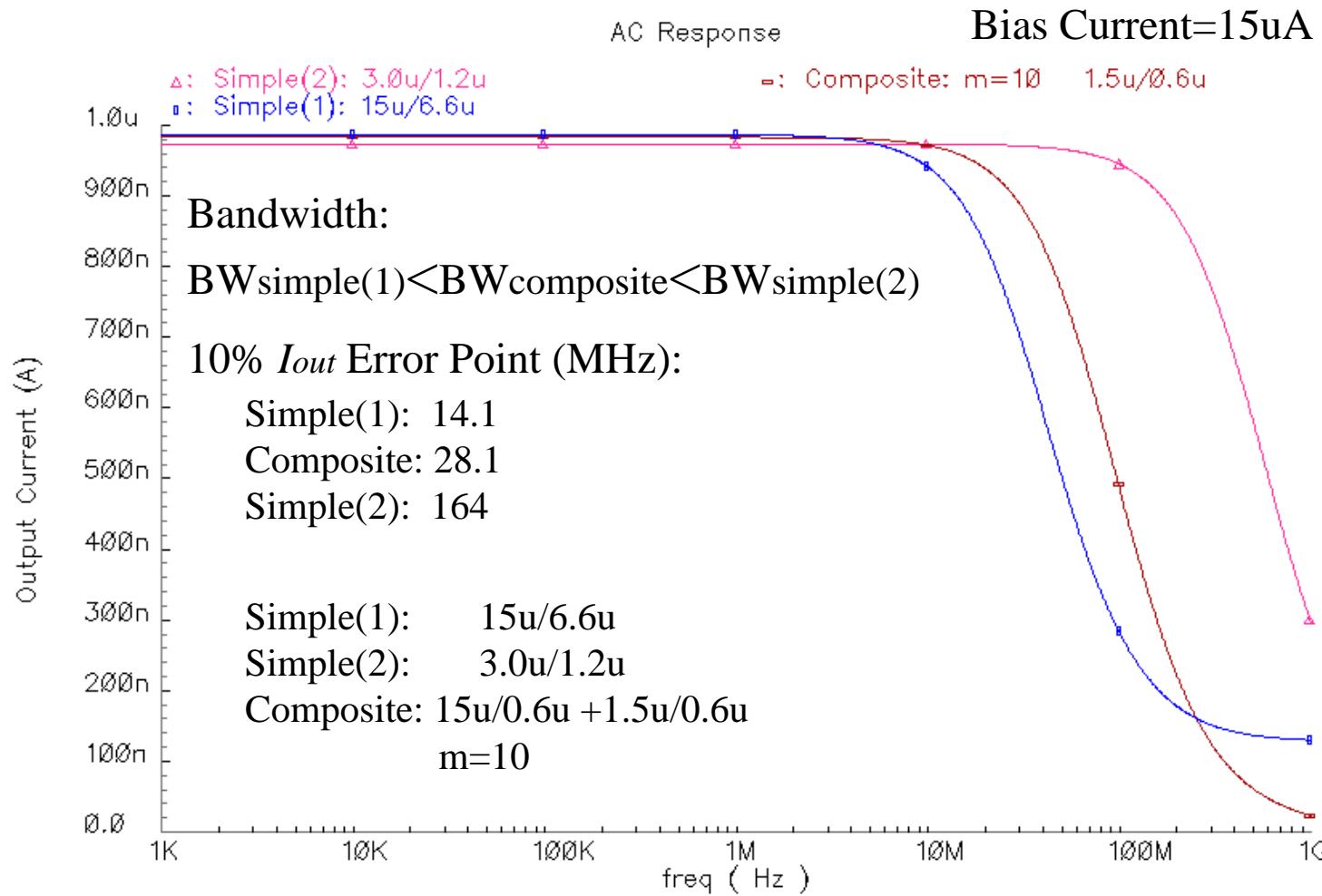

Application (I) – Current Mirrors

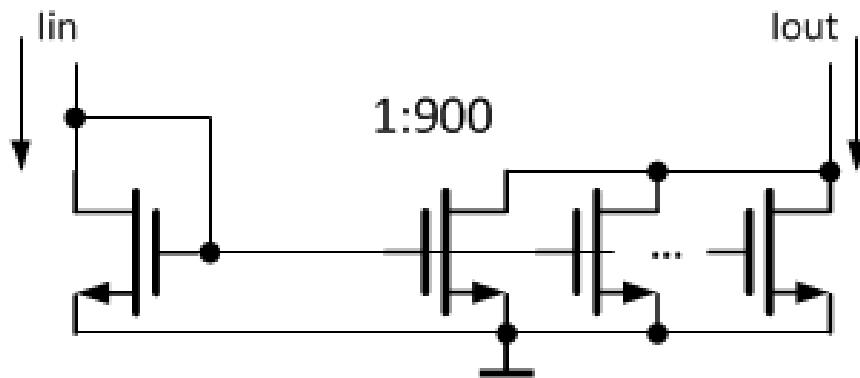

Traditional Current Mirror
Huge Area (901T)


Series-Parallel
Current Mirror

$$\text{Ex. } R = 30, S = 1$$


$$Q = 30, P = 1$$

Ratio: 1:900


Area: **60T**

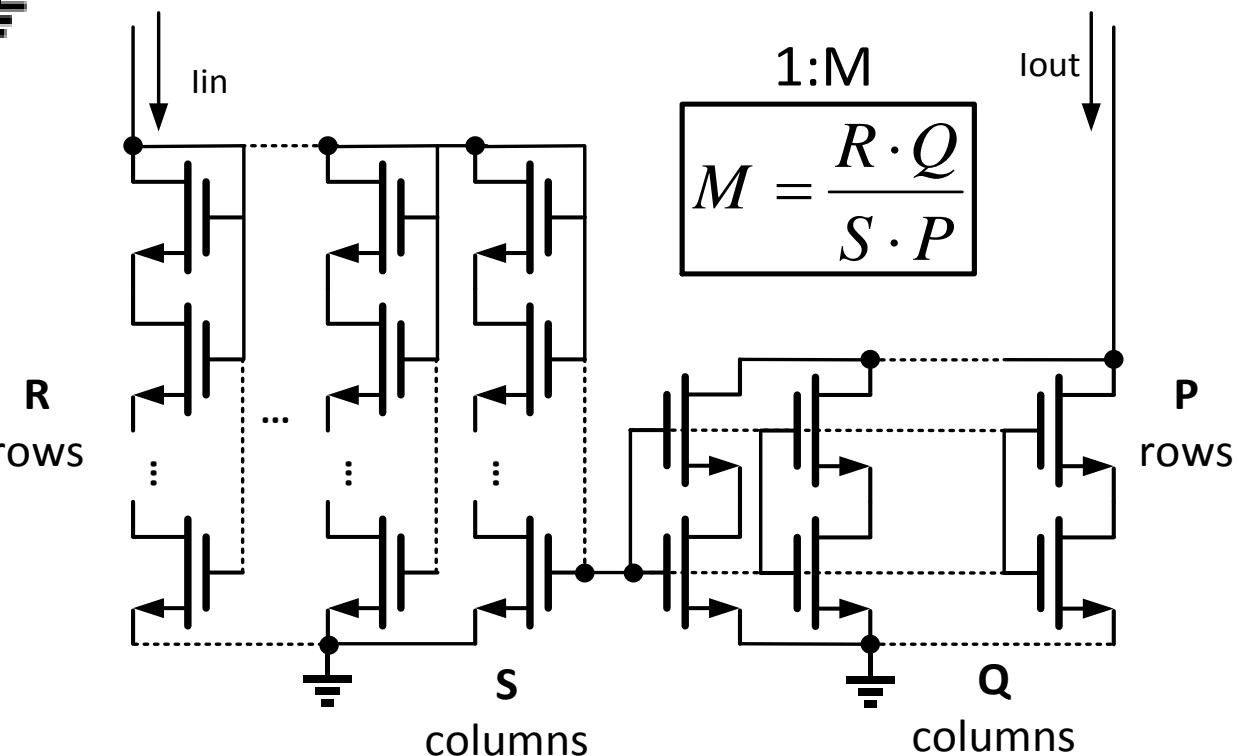

Traditional vs. Series-Parallel

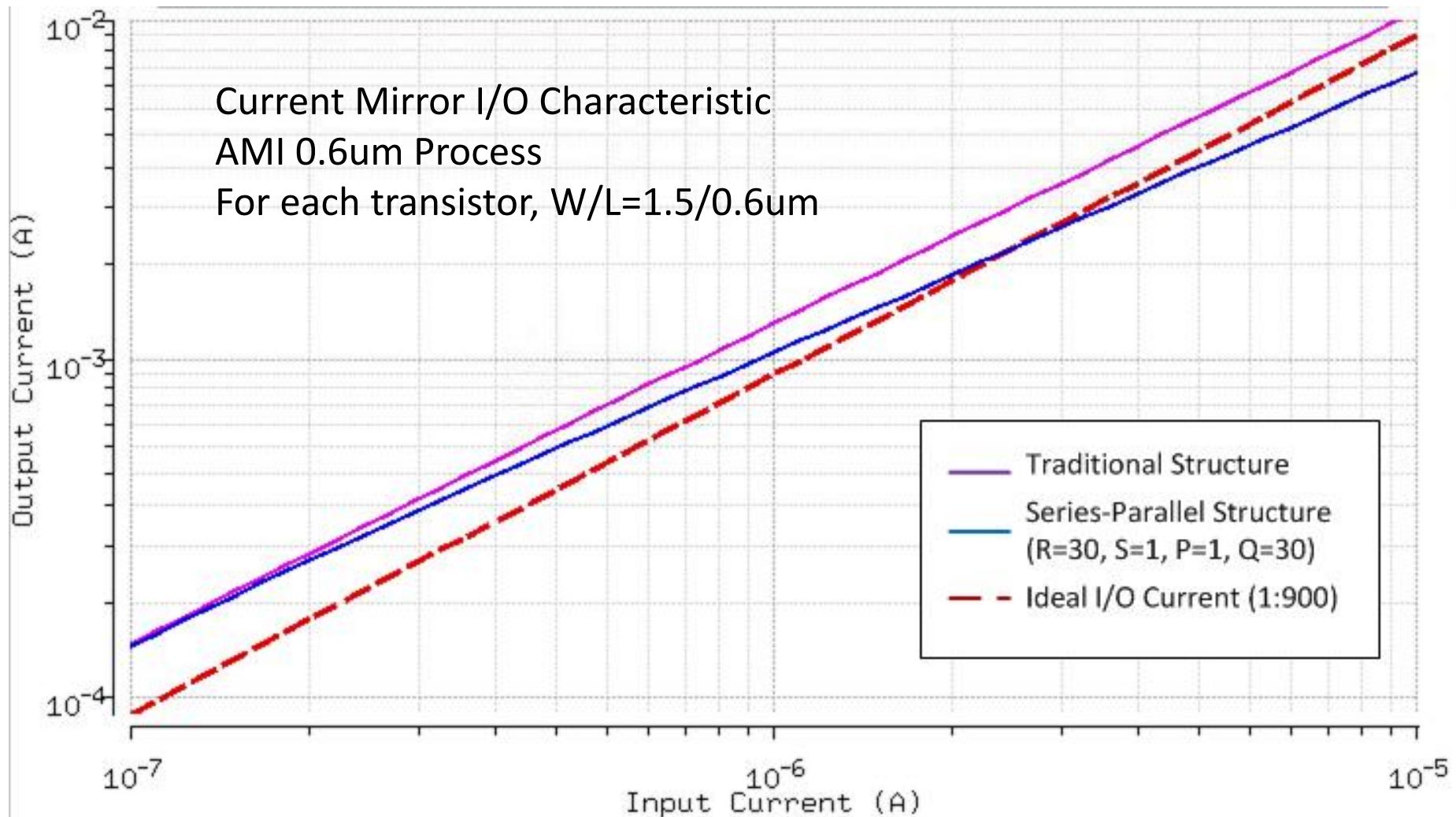

Series-Parallel Current Mirror

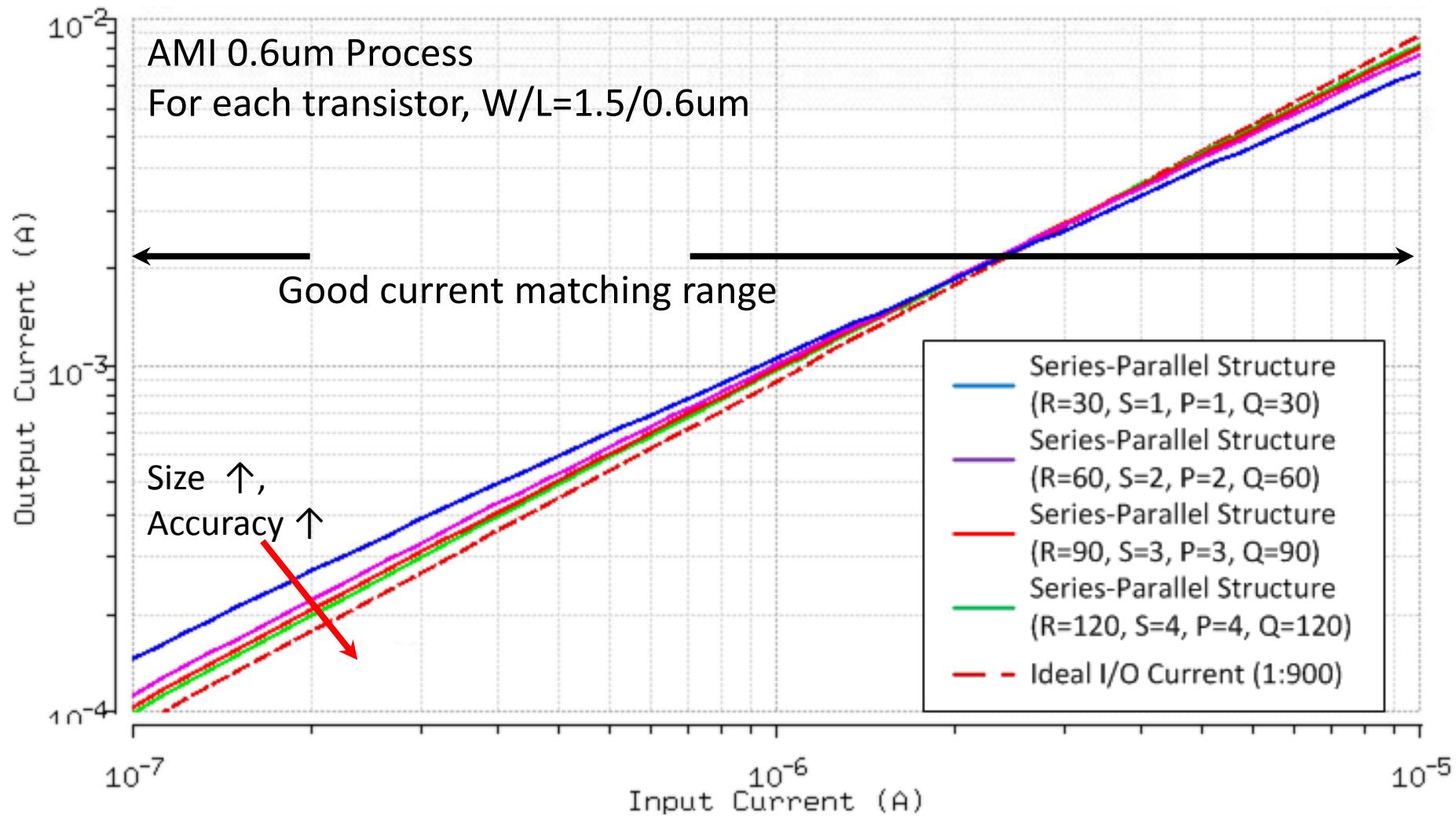

Compare Current Mirrors

Series-Parallel current mirror improves the output impedance

	R	S	P	Q	M	Area	Input Imp.	Output Imp.
Trad.	1	1	1	900	900	901T	71.5K	4.0K
Series-Parallel	30	1	1	30	900	60T	356.8K	12.4K
	60	2	2	60	900	240T	357.3K	20.7K
	90	3	3	90	900	540T	357.5K	28.8K
	120	4	4	120	900	960T	357.6K	36.8K

Output Impedance Comparison
Input Current = **1uA**, Ratio = 1:900

Compare Current Mirrors

	R	S	P	Q	M	Area	Input Imp.	Output Imp.
Trad.	1	1	1	900	900	901T	19.1K	800
Series-Parallel	30	1	1	30	900	60T	155.4K	4.3K
	60	2	2	60	900	240T	154.4K	4.8K
	90	3	3	90	900	540T	154.1K	5.5K
	120	4	4	120	900	960T	154.1K	6.2K

Output Impedance Comparison
Input Current = **10uA**, Ratio = 1:900


Voltage Swing

Stacked transistors limit the output swing of S-P current mirror

	R	S	P	Q	Output V _{dsat} (I _{in} =1uA)	Output V _{dsat} (I _{in} =10uA)
Trad.	1	1	1	900	89mV	245mV
Series-Parallel	30	1	1	30	441mV	1.4V
	60	2	2	60	303mV	1.0V
	90	3	3	90	244mV	830mV
	120	4	4	120	210mV	720mV


V_{dsat} (equivalent) of the output transistor reveals
the max swing of the output voltage

Applications (II)--Differential Pair

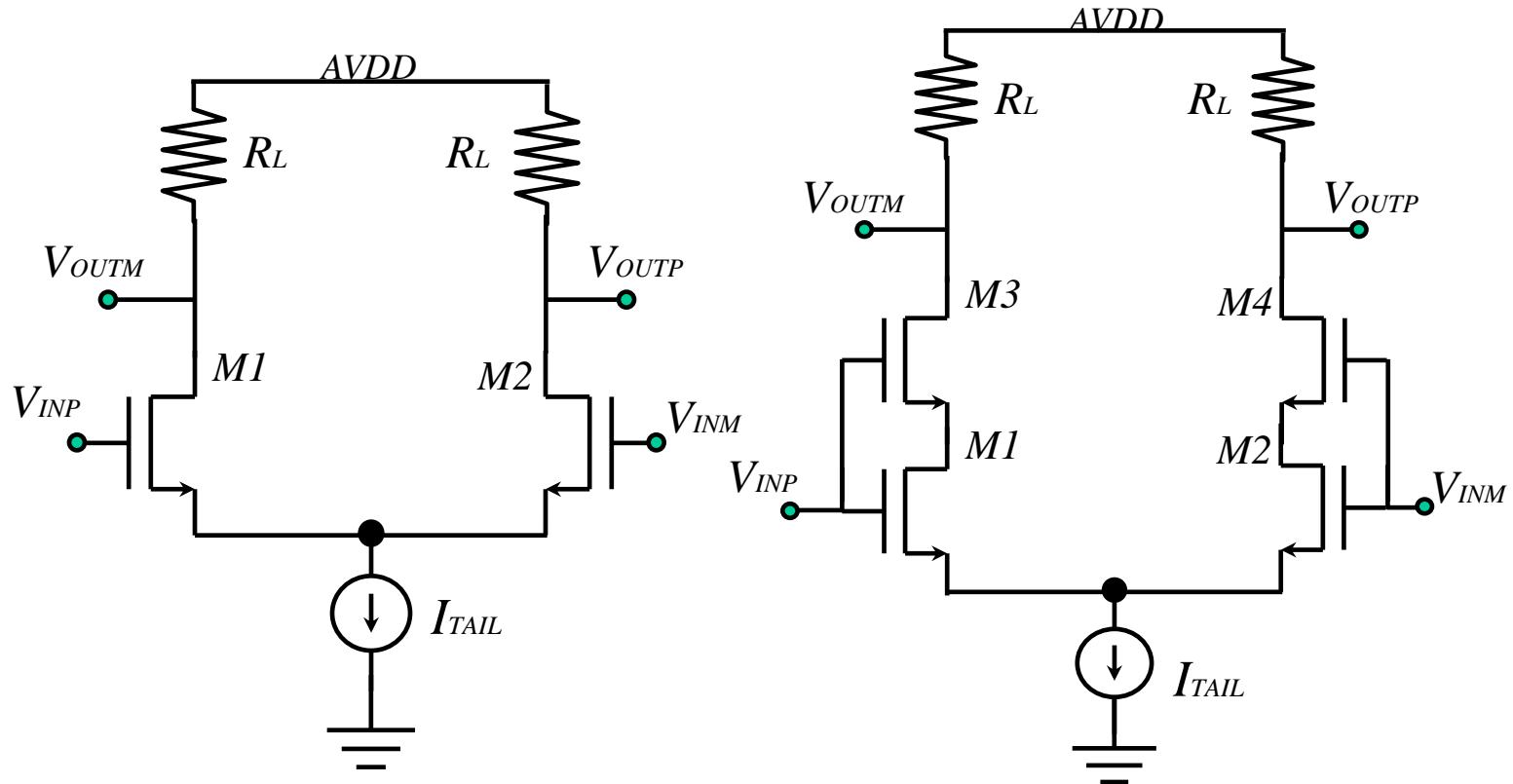


Composite transistors can replace single transistors in a differential pair. Through self-cascode structure, higher voltage gain can be achieved.

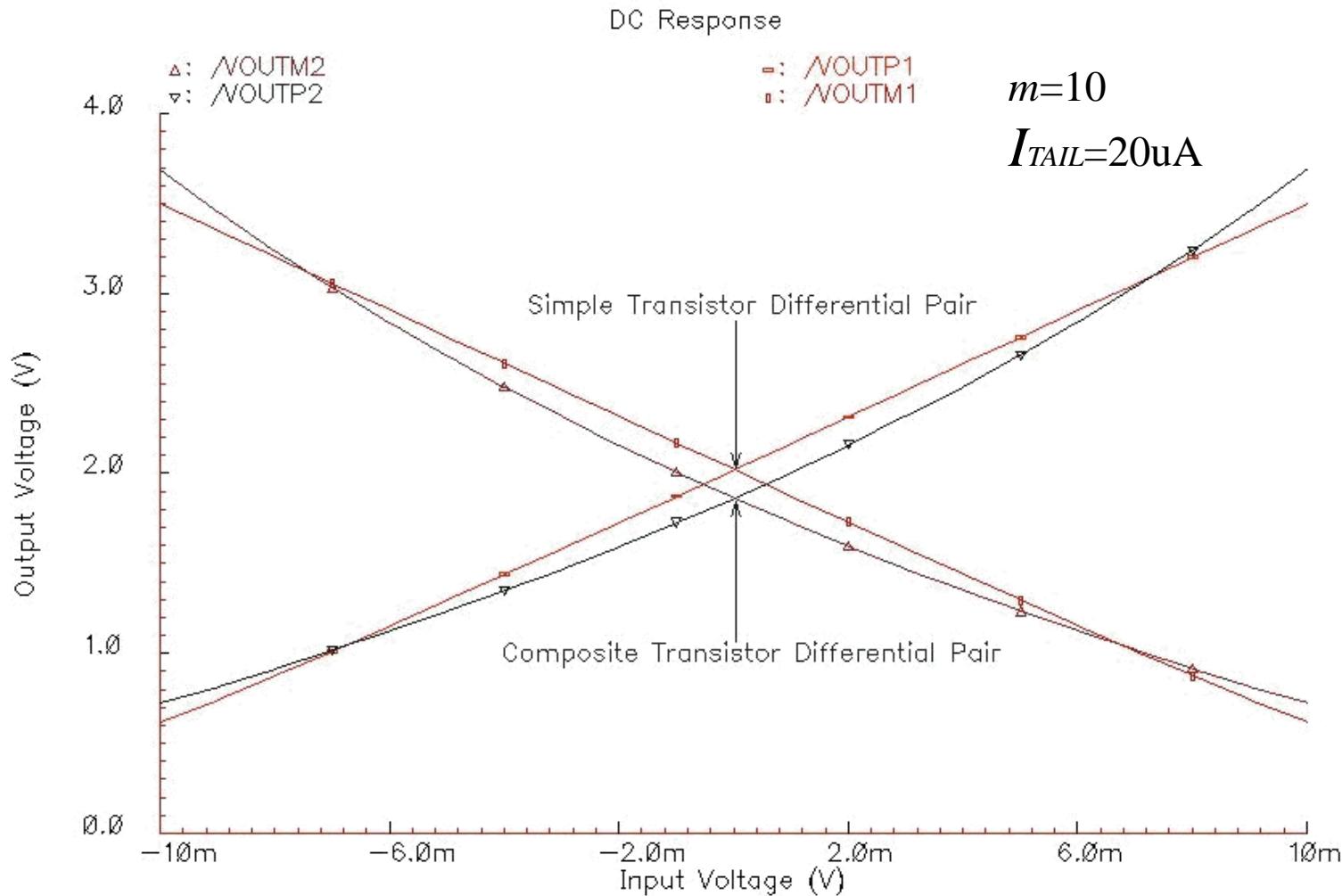Differential Pair Simulation Results (DC)



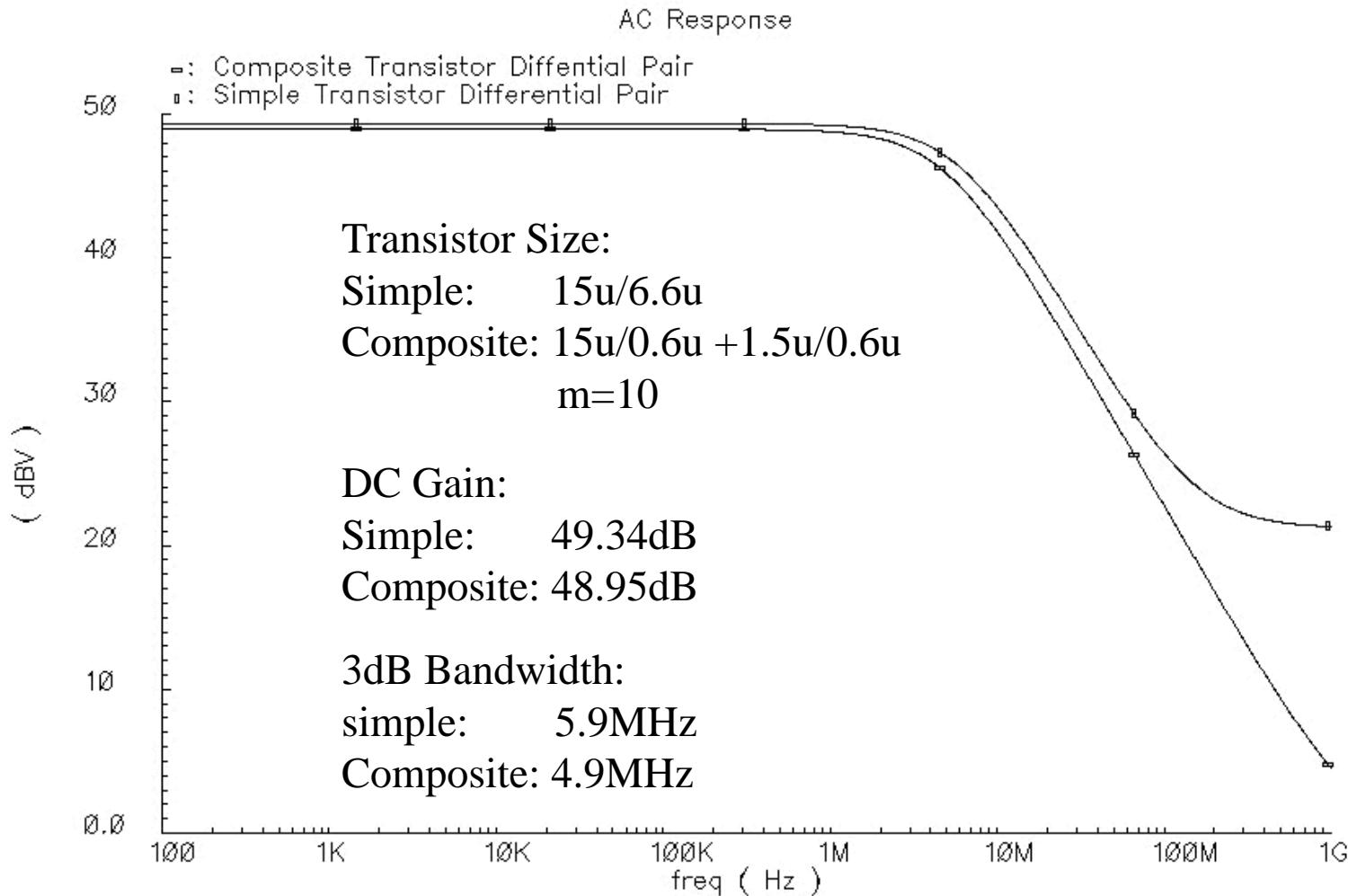
Differential Pair Simulation Results (AC)








References

1. C. Galup-Montoro, etc., “Series-Parallel Association of FET’s for High Gain and High Frequency Applications”, *IEEE JSSC*, Sept. 1994
2. D. Ceuster, etc., “Improvement of SOI MOS current-mirror performances using serial-parallel association of transistors”, *Electronics Letters*, Feb. 1996
3. P. Furth, H. Om’mani, “A 500-nW Floating-Gate Amplifier with Programmable Gain”, IEEE 1999
4. I. Fujimori, T. Sugimoto, “A 1.5V, 4.1mW Dual-Channel Audio Delta-Sigma D/A Converter”, *IEEE JSSC*, Dec. 1998
5. Personal note from Dr. Ugur Cilingiroglu
6. Yunchu Li, examples and SPICE tables

LOW VOLTAGE CURRENT-MIRRORS

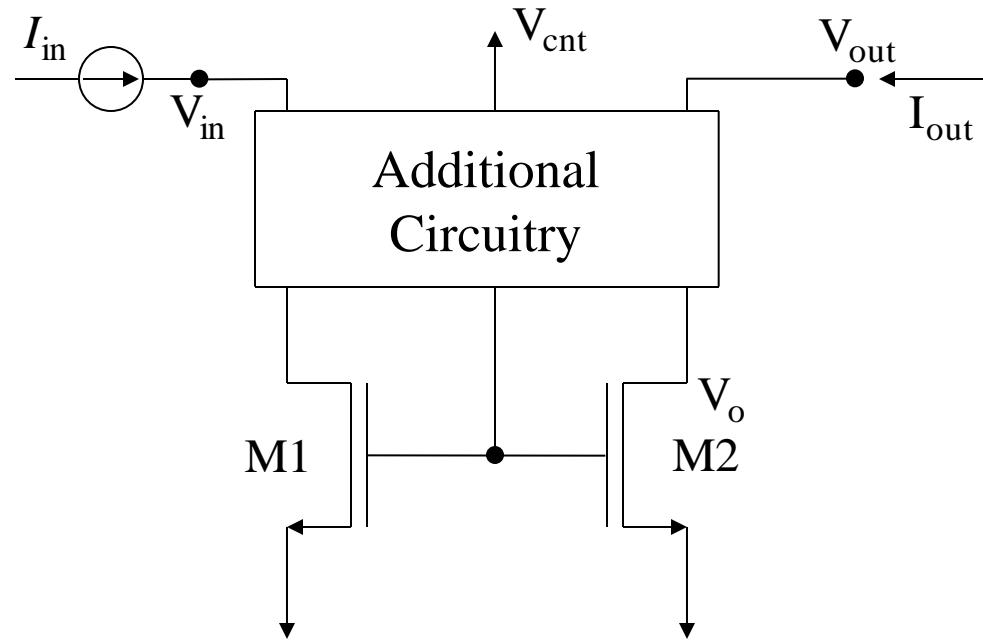


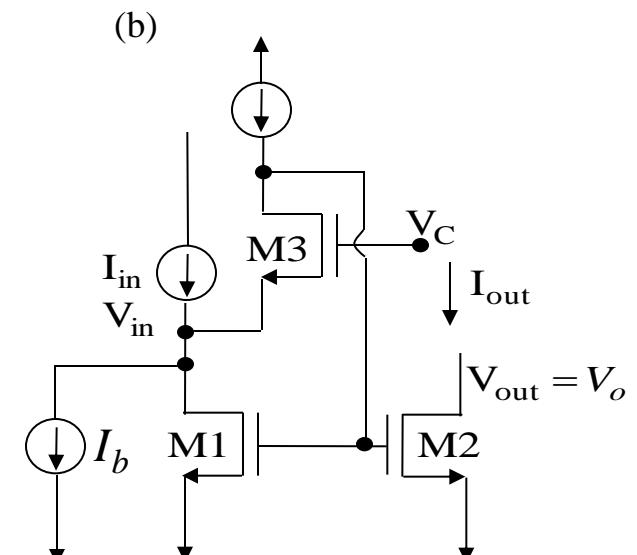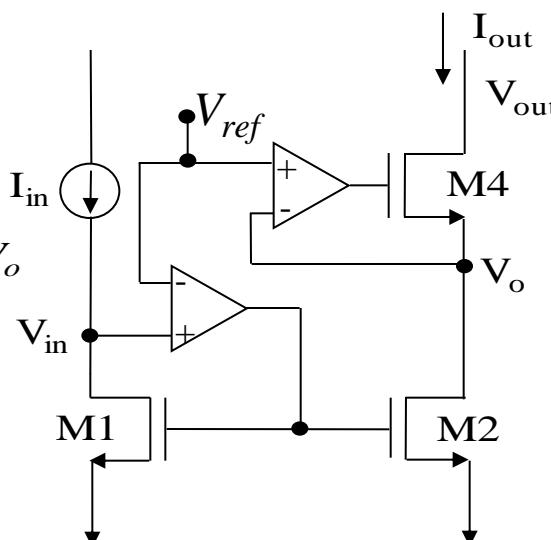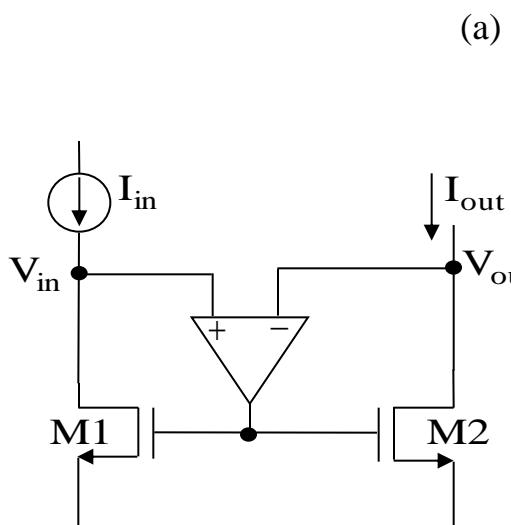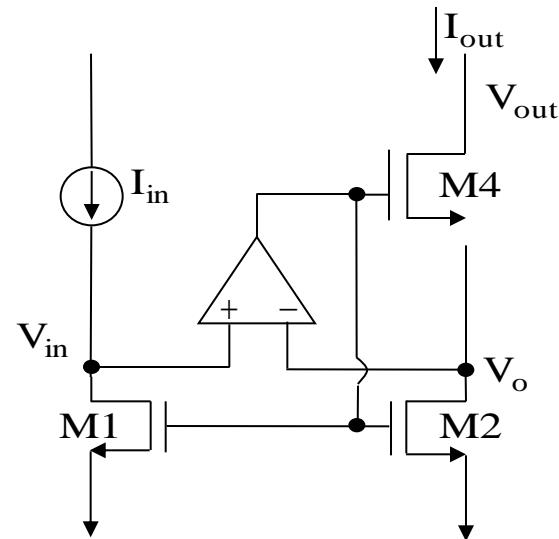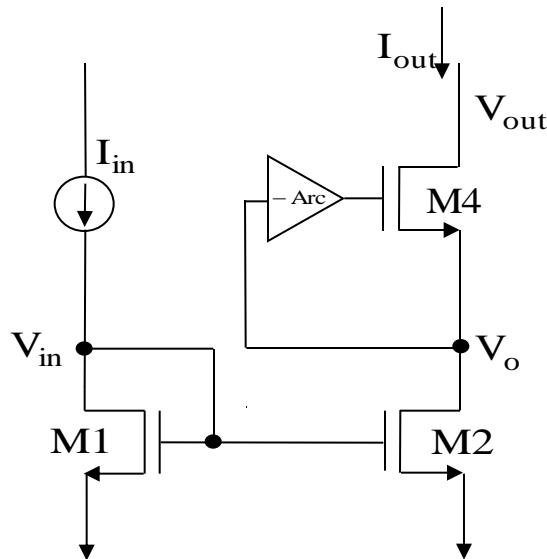General scheme for high-performance current mirror structure.



High-performance current mirrors:

Conventional active-input current mirror

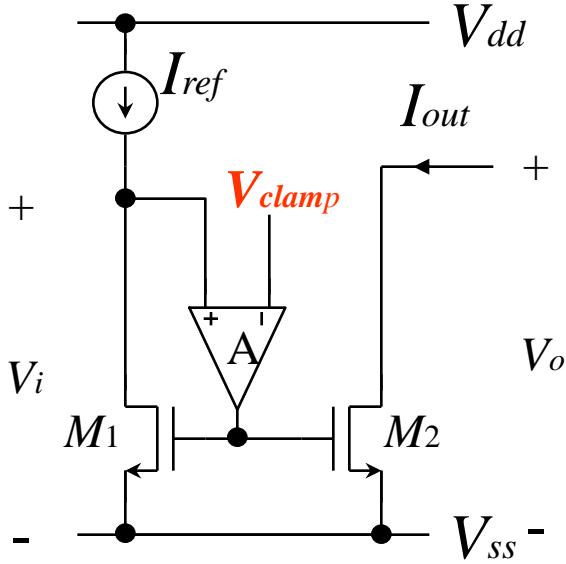

$$V_{i\min} = \max\left(\frac{V_{DSAT1} + V_T}{A} + V_{Clamp}, V_{DSAT1}\right)$$

$$V_{0\min} = V_{DSAT2}$$

$$R_{in} \approx \frac{1}{A \cdot g_{m1}}$$

$$R_{out} \approx \frac{1}{g_{o2}}$$


Advantage:

- Lower input impedance

Disadvantage:

- To achieve stability, g_{m1} can not be arbitrarily small.
Thus, can not work over a wide current range.
- Compensation of the amplifier depends on the value of I_{ref} .

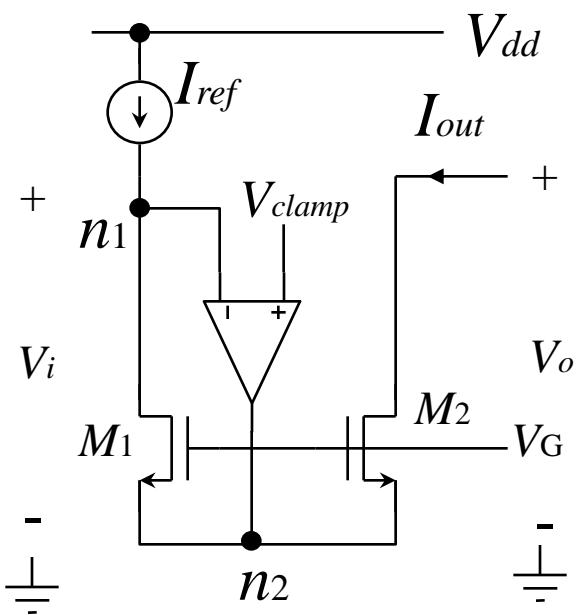Improved active input current mirrors (I)



Advantage:

This current mirror can operate over a very wide range of currents: from values equal to junction leakage currents up to the maximum current the OTA might be able to sink.

Disadvantage:

- Additional compensation capacitor between n_1 and n_2 may required to achieve stability
- The OTA must be able to sink twice the maximum expected value for I_{ref} , which imposes an important design constraint for the OTA.


$$V_{i\min} = \max\left(\frac{V_T + V_{DSAT} - V_G}{A} + V_{clamp}, \frac{V_{DSAT} + A \cdot V_{clamp}}{A+1}\right)$$

$$V_{0\min} = V_{DSAT2}$$

$$R_{in} \approx \frac{1}{A \cdot g_{m1} + (1+A) \cdot g_{o1}} \approx \frac{1}{A \cdot g_{m1}}$$

$$R_{out} \cong \frac{1}{g_{o2}}$$

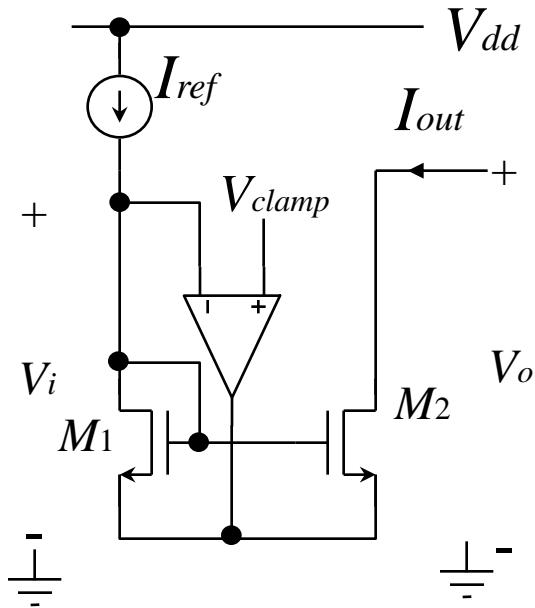Improved active input current mirrors (II)



Advantage:

- This current mirror can operate over a very wide range of currents: from values equal to junction leakage currents up to the maximum current the OTA might be able to sink.
- If the differential voltage amplifier is already compensated for unity gain feedback, the circuit is always stable.

Disadvantage:


- Higher power supply may be required for amplifier
- More chip area and power consumption

$$V_{i\min} = \frac{V_{DSAT1} + V_T + A \cdot V_{clamp}}{A+1}$$

$$R_{in} \approx \frac{1}{(1+A) \cdot (g_{m1} + g_{o1})} \approx \frac{1}{(1+A) \cdot g_{m1}}$$


$$R_{out} \approx \frac{1}{g_{o2}}$$

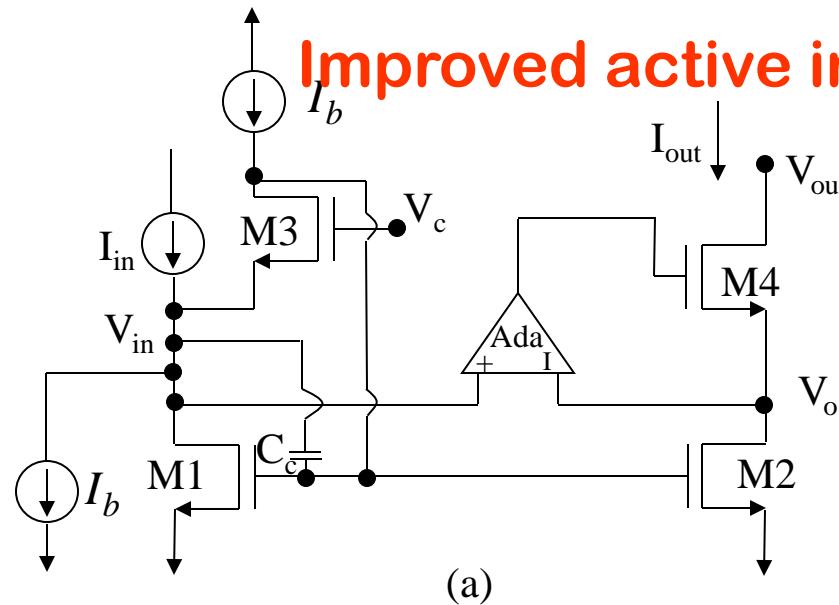Improved active input current mirrors (III)





$$V_{OUT} > 2V_{DSAT}^Q + V_{oV}^{MAX}$$

$$V_{CNOUT}^{MIN} \cong |V_{tp}| + 3V_{DSAT}^Q + V_{oV}^{MAX}$$

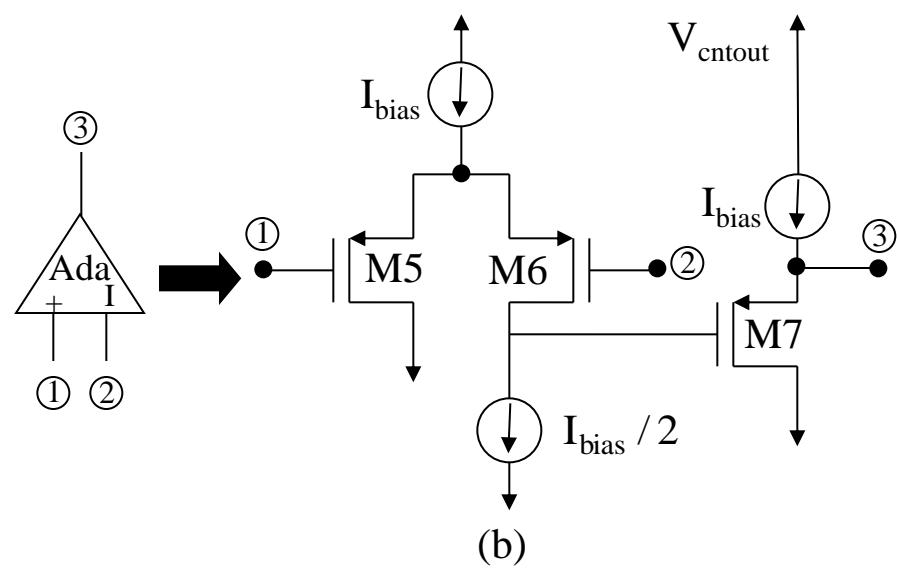


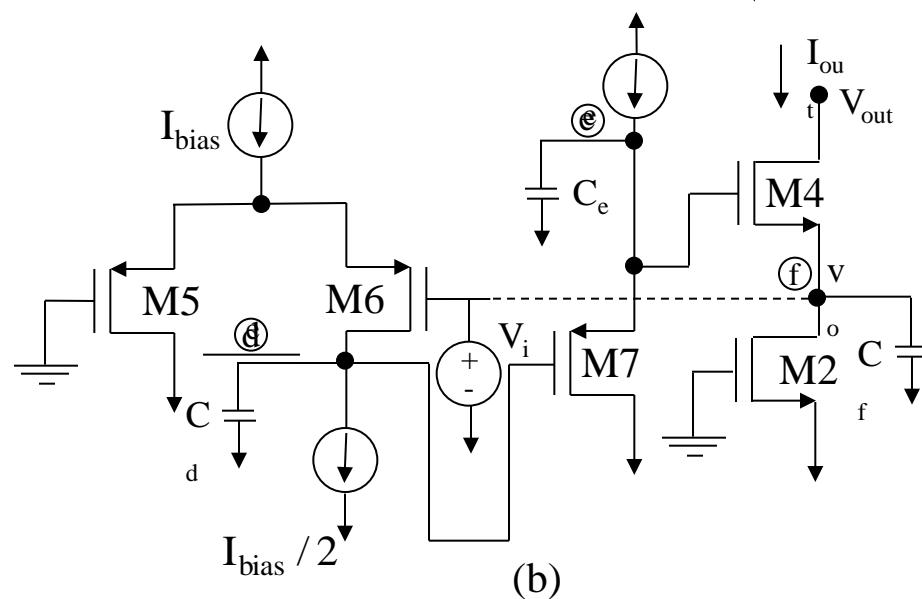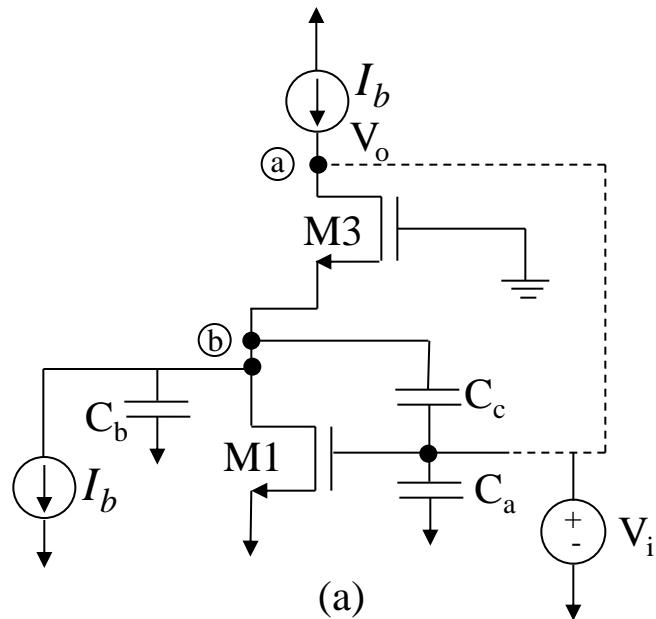- (a) Proposed low-voltage high-performance current mirror.
- (b) Implementation of the differential amplifier A_{da} .



Open-loop response analysis: (a) input side and (b) output side.

Active regulated cascode current mirror

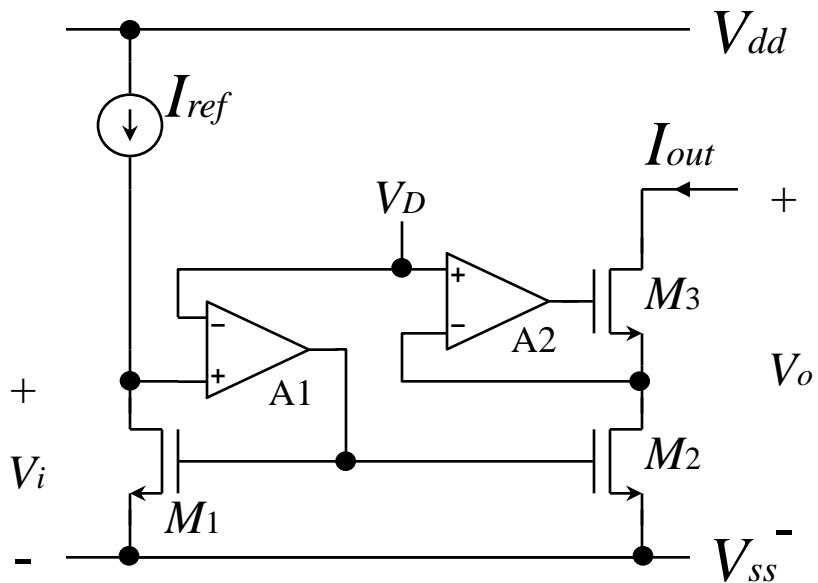

$$V_{i\min} = \max\left(\frac{V_T + V_{DSAT}}{A1} + V_D, V_{DSAT}\right)$$

$$V_{o\min} = 2V_{DSAT}$$

$$R_{in} \approx \frac{1}{A1 \cdot g_{m1}}$$

$$R_{out} = \frac{g_{m3}(1 + A2)}{g_{o3}g_{o2}}$$

Advantages:

- High output impedance
- Low input impedance


Disadvantages:

- Poles and zeros may cause instability
- more power and area

Techniques for Wideband Amplifiers


ELEN 607 (ESS)

Conventional

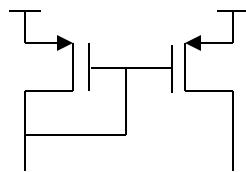

An example of its use:


ELEN 607 (ESS)

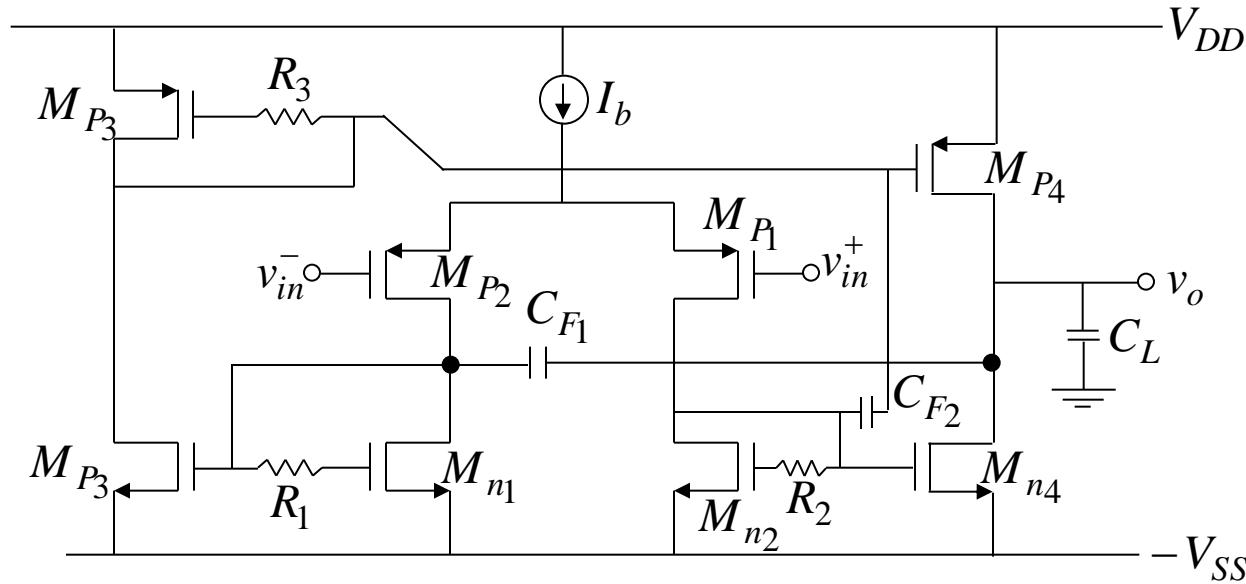

Wideband Amplifier with Feedforward Technique

- C_{F1} bypasses two current mirrors.
- C_{F2} is fed forward to the input of another FDCM and signal is amplified.

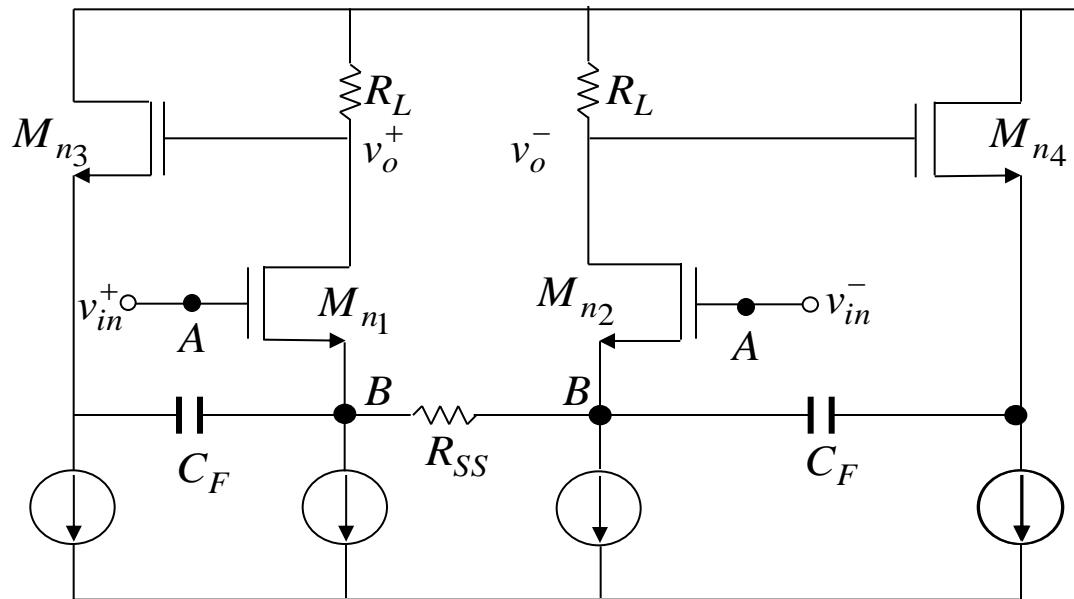
Next, we discuss different families of wideband reported in the literature.




- An alternative is to connect C_F instead to nodes B to nodes A

F. Centurelli et al, “A Bootstrap Technique for Wideband Amplifiers,” *IEEE Trans. on Circuits And Systems – I*, Vol. 49, No. 10, pp. 1474-1480, October 2002


FOLDED-CASCODE WIDEBAND AMPLIFIER

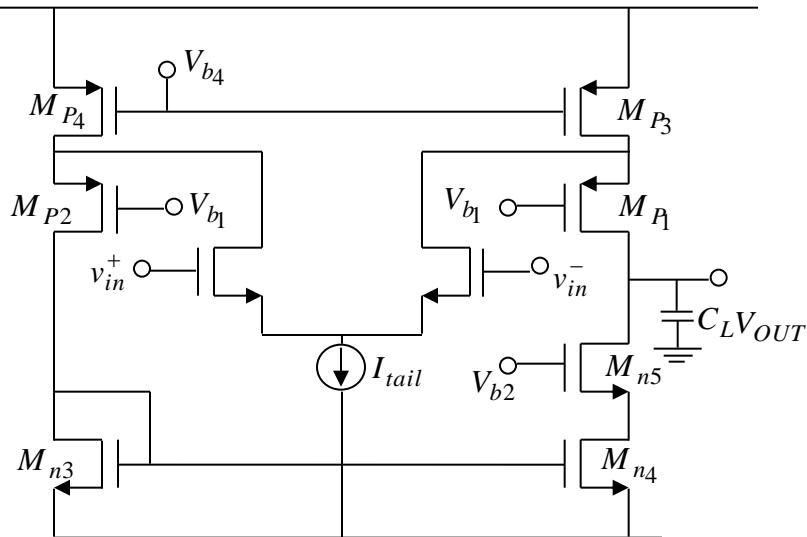

Conventional Folded-Cascode (FC)

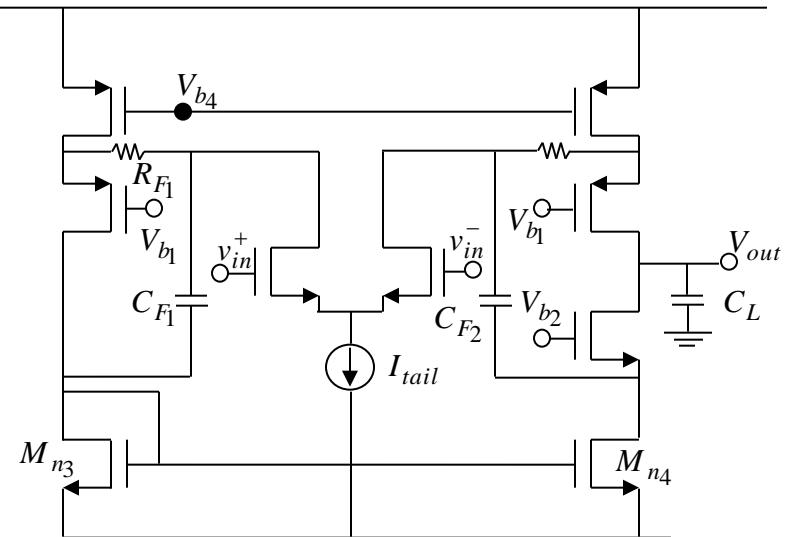

FC with Capacitive Feedforward

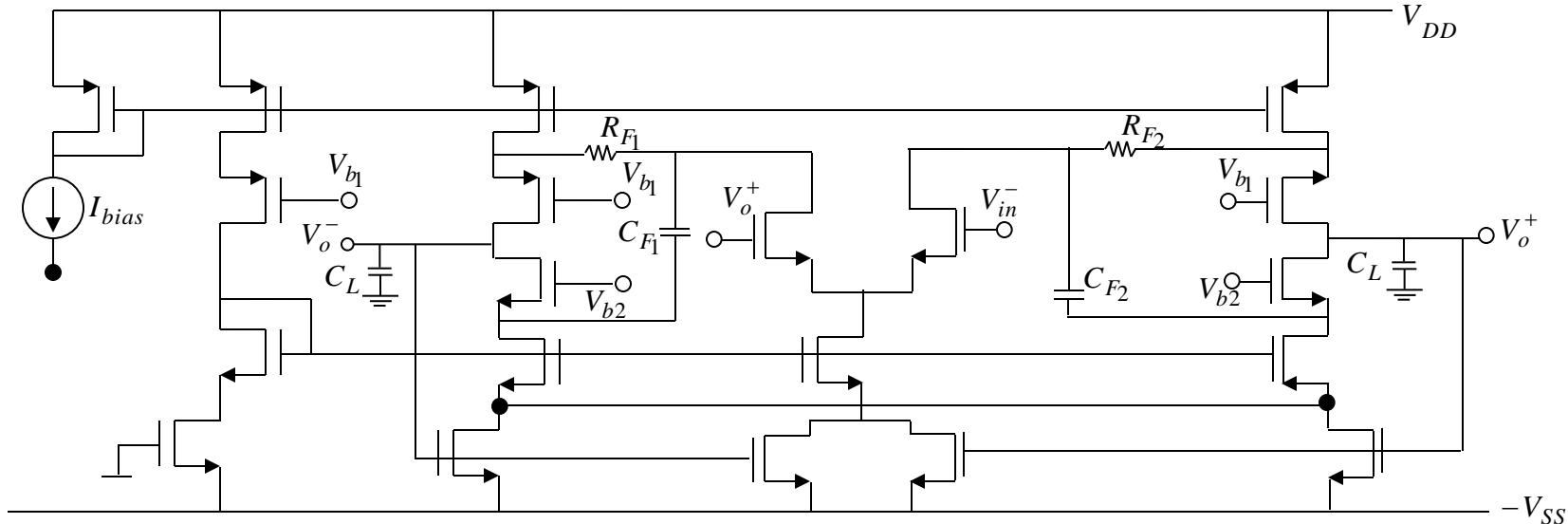


Differential Wideband Amplifier


References

- [1] E. Sánchez-Sinencio and A. Andreou, Editors, “*Low Power/Low Voltage Integrated Circuits and Systems*”, Piscataway, IEEE Press, 1999.
- [2] K. Laker, W. Sansen, “*Design of Analog Integrated Circuits and Systems*”, McGraw-Hill, New York, 1994
- [3] Edgar Sánchez-Sinencio, ELEN626 Notes, 1998
- [4] Teresa Serrano-Gotarredona, etc., “Very wide range tunable CMOS/Bipolar Current Mirrors with Voltage Clamped Input”, *IEEE Trans. On Circuits and Systems*, Oct. 1998.
- [5] D.A. Johns and K. Martin, “*Analog Integrated Circuit Design*”, New York, John Wiley 1997
- [6] R. Jacob Baker, H. Li, etc., “*CMOS Circuit Design, Layout, and Simulation*”, IEEE Press, 1997.

Different OTAs

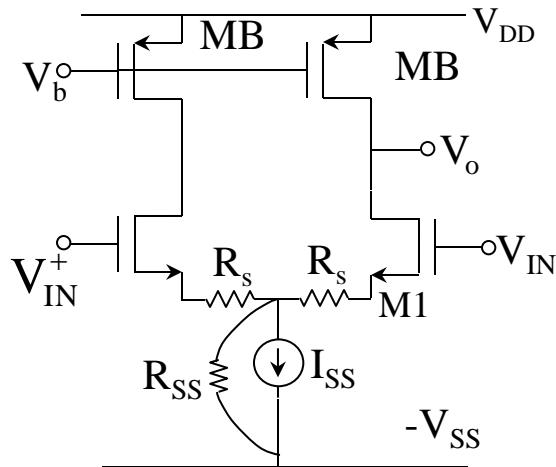

Source Degenerated OTA-1

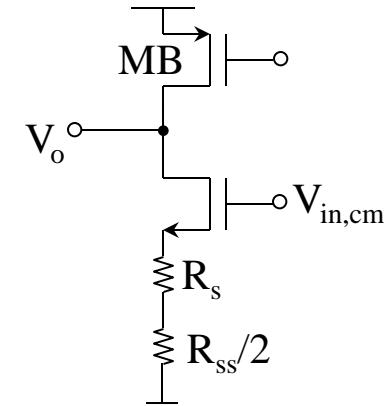

Common-Mode Equivalent Circuit

$$A_{cm} = \frac{g_{m,n}(r_{ds,p} // [(g_{m,n} + g_{mb,n})r_{ds,n}(R_s + 2R_{ss}) + r_{ds,n} + R_s + 2R_{ss}])}{1 + (g_{m,n} + g_{mb,n})(R_s + 2R_{ss})} \quad (1)$$

$$A_{df} = \frac{1}{2} \frac{g_{m,n}(r_{ds,p} // [(g_{m,n} + g_{mb,n})r_{ds,n}R_s + r_{ds,n} + R_s])}{1 + (g_{m,n} + g_{mb,n})R_s} \quad (2)$$

Differential-Mode
Equivalent Circuit.

Where

$$CMMR = \frac{A_{df}}{A_{cm}}$$


Assume

$$(g_{m,n} + g_{mb,n})r_{ds,n}(R_s + 2R_{ss}) \gg R_s, R_{ss}, r_{ds,n}, r_{ds,p}$$


$$(g_{m,n} + g_{mb,n})r_{ds,n}R_s \gg R_s, r_{ds,n}, r_{ds,p}$$

$$\frac{1}{g_{m,n} + g_{mb,n}} \ll R_s, R_s \ll R_{ss}$$
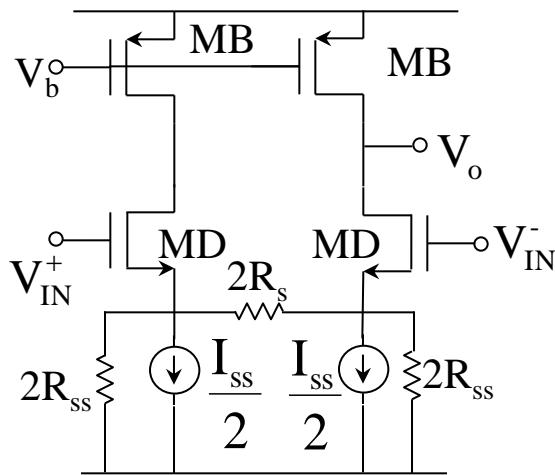
$$A_{cm} \approx \frac{r_{ds,p}}{2R_{ss}}, A_{df} \approx \frac{1}{2} \frac{r_{ds,p}}{2R_s}, CMRR \approx \frac{R_{ss}}{R_s}$$



Source Degenerated OTA-2

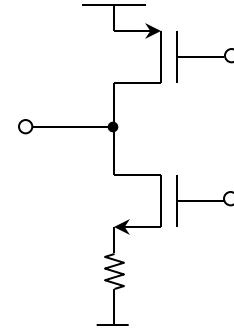

CM Equivalent Circuit

$$V_{DD} \quad V_b \quad A_{cm} = \frac{g_{m,n} \cdot (r_{ds,p} // [(g_{m,n} + g_{mb,n})r_{ds,n} 2R_{ss} + r_{ds,n} + 2R_{ss}])}{1 + (g_{m,n} + g_{mb,n})2R_{ss}} \quad (3)$$

$$V_{out} \quad V_{in} \quad 2R_{ss}||R_s \quad \text{Virtual Ground} \quad A_{df} = \frac{1}{2} \frac{g_{m,n} \cdot (r_{ds,p} // [(g_{m,n} + g_{mb,n})r_{ds,n}(R_s // 2R_{ss}) + r_{ds,n} + R_{ss} // 2R_{ss}])}{1 + (g_{m,n} + g_{mb,n})(R_s // R_{ss})} \quad (4)$$


Differential-Mode
Equivalent Circuit

Where

$$CMRR = \frac{A_{df}}{A_{cm}}, A_{cm} \approx \frac{r_{ds,p}}{2R_{ss}}, A_{df} \approx \frac{r_{ds,p}}{2R_s}$$

Then

$$CMRR \approx \frac{R_{ss}}{R_s}$$

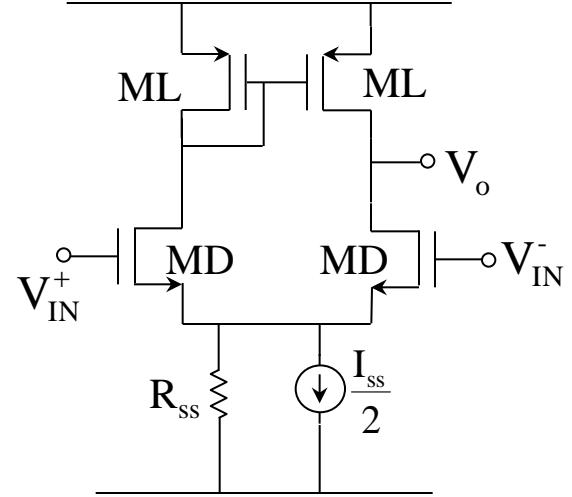

$$A_{cm} = \frac{g_{m,n} \cdot \left(\left(\frac{1}{g_{m,p}} // r_{ds,p} \right) // [(g_{m,n} + g_{mb,n})r_{ds,n} 2R_{ss} + r_{ds,n} + 2R_{ss}] \right)}{1 + (g_{m,n} + g_{mb,n})2R_{ss}} \quad (5)$$



$$A_{df} = g_{m,n} (r_{ds,p} // r_{ds,n}) \quad (6)$$

Where

$$CMRR = \frac{A_{df}}{A_{cm}}, \quad A_{cm} \approx \frac{1}{g_{m,p} \cdot 2R_{ss}} \quad , \quad A_{df} = g_{m,n}(r_{ds,p} // r_{ds,n})$$


Then
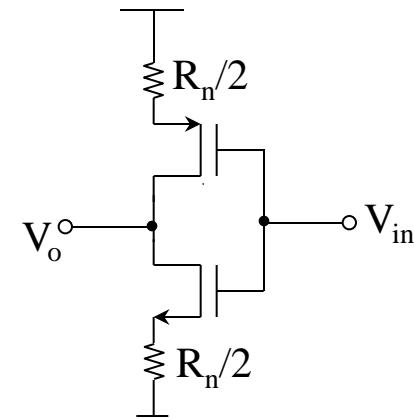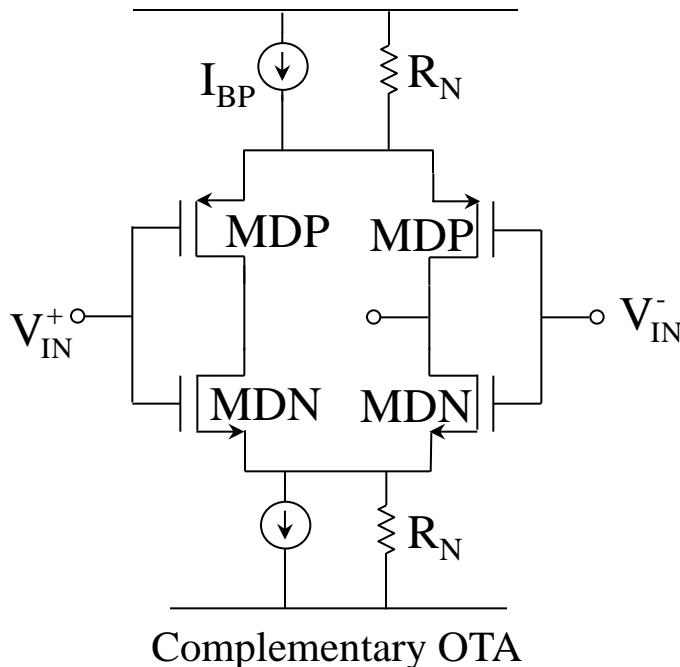
$$CMRR = g_{m,n}(r_{ds,p} // r_{ds,n})g_{m,p} \cdot 2R_{ss}$$



$$A_{cm} = \frac{[(g_{m,p} + g_{mb,p})r_{ds,p}2R_N + r_{ds,p} + 2R_N]//[(g_{m,n} + g_{mb,n})r_{ds,n}2R_N + r_{ds,n} + 2R_N]}{\left(\frac{1 + (g_{m,n} + g_{mb,n})2R_N}{g_{m,n}}\right)//\left(\frac{1 + (g_{m,p} + g_{mb,p})2R_N}{g_{m,p}}\right)}$$

Virtual Ground

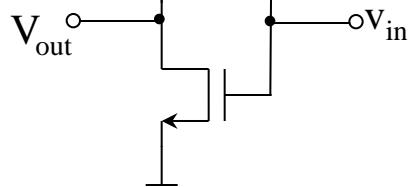

$$A_{df} = \frac{1}{2} (g_{m,n} + g_{m,p}) (r_{ds,p} // r_{ds,n})$$

Where


$$CMRR = \frac{A_{df}}{A_{cm}} , \quad A_{cm} \approx 2 \{ [(g_{m,p} + g_{mb,p})r_{ds,p}] / [(g_{m,n} + g_{mb,n})r_{ds,n}] \} ,$$

$$A_{df} = \frac{1}{2} (g_{m,n} + g_{m,p}) (r_{ds,p} // r_{ds,n})$$

Then

$$CMRR = \frac{(g_{m,n} + g_{m,p})(r_{ds,p} // r_{ds,n})}{4 \{ [(g_{m,p} + g_{mb,p})r_{ds,p}] / [(g_{m,n} + g_{mb,n})r_{ds,n}] \}}$$

$$T_1 = \frac{V_o^+ - V_o^-}{v_{cmc}} \Big|_{v_i^+ = v_i^- = 0} = 0$$

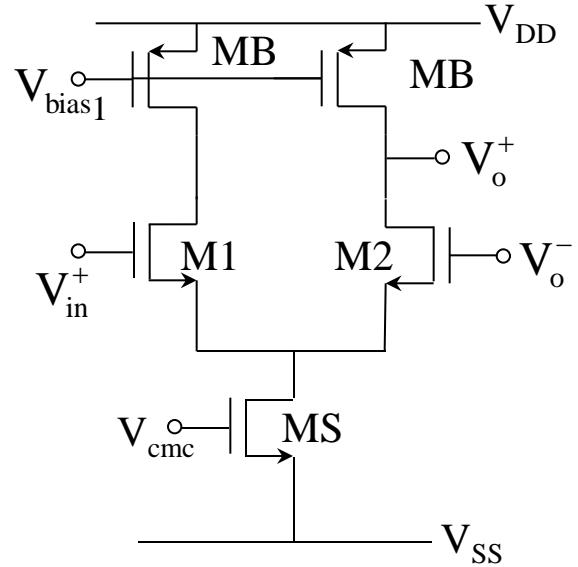

Simple Differential OTA

$$T_2 = \frac{V_o^+ + V_o^-}{2v_{cmc}} \Big|_{v_i^+ = v_i^- = 0} = \frac{g_{m,MS}}{2} \left\{ r_{ds,MB} // [(g_{m,M1} + g_{mb,M1})r_{ds,M1} 2r_{ds,MS} + r_{ds,M1} + 2r_{ds,MS}] \right\}$$

$$A_{dm} = T_3 = \frac{V_o^+ - V_o^-}{v_i^+ - v_i^-} \Big|_{v_{cmc} = V_{bias}} = g_{m,M1,2} (r_{ds,MB} // r_{ds,M1})$$

$$A_{cm} = T_4 = \frac{V_o^+ + V_o^-}{v_i^+ + v_i^-} \Big|_{v_{cmc} = V_{bias}} = \frac{r_{ds,MB} // [2(g_{m,M1} + g_{mb,M1})r_{ds,M1}r_{ds,MS} + r_{ds,M1} + 2r_{ds,MS}]}{1 + 2(g_{m,M1} + g_{mb,M1})r_{ds,MS}} \approx \frac{r_{ds,MB}}{2r_{ds,MS}} g_{m,M1}$$

Folding Cascode Amplifier Architecture

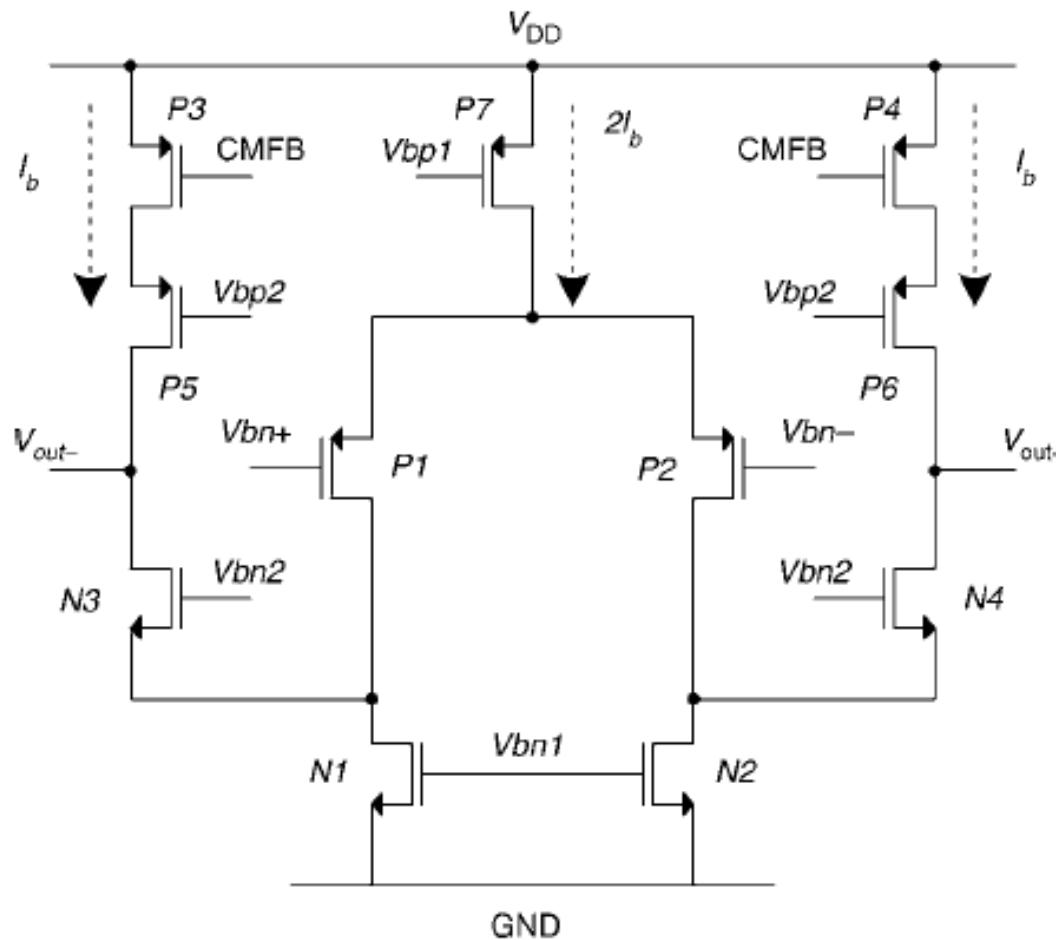


Fig. 1 Conventional folded cascode

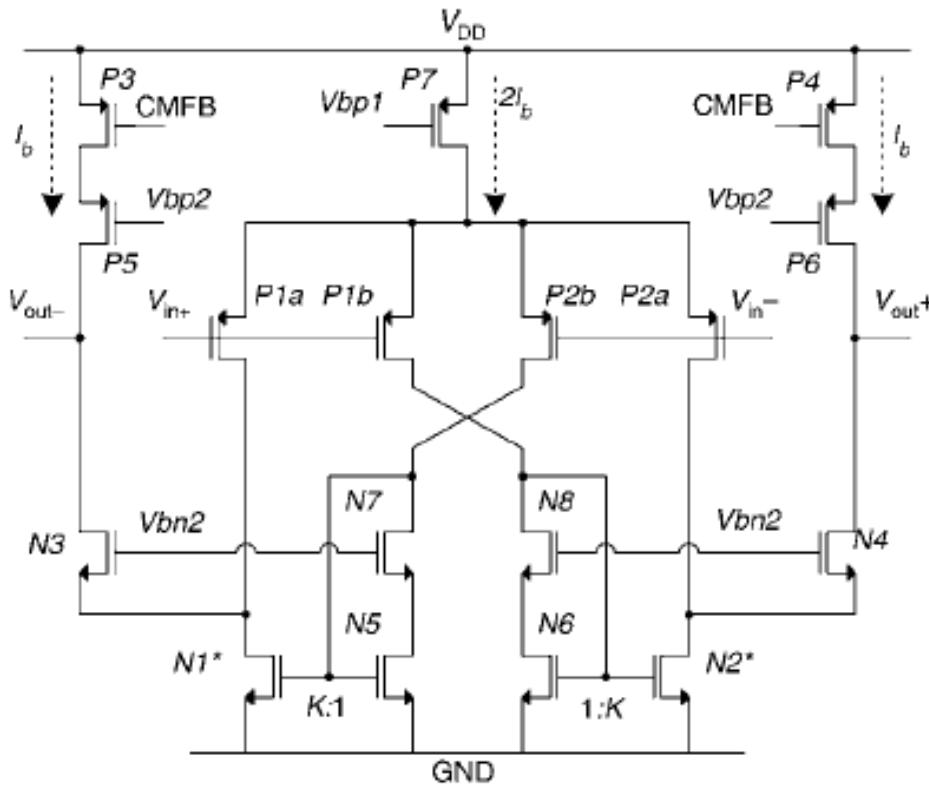


Fig. 2 Recycling folded cascode

Recycling folded cascode (RFC): The conventional FC is shown in Fig. 1. Note that transistors $N1$ and $N2$ conduct the most current and thus have the largest transconductance, yet act as current sinks only. Previous work to enhance the performance of the FC exploited multipath schemes [3]. However, $N1$ and $N2$ were left unexplored.

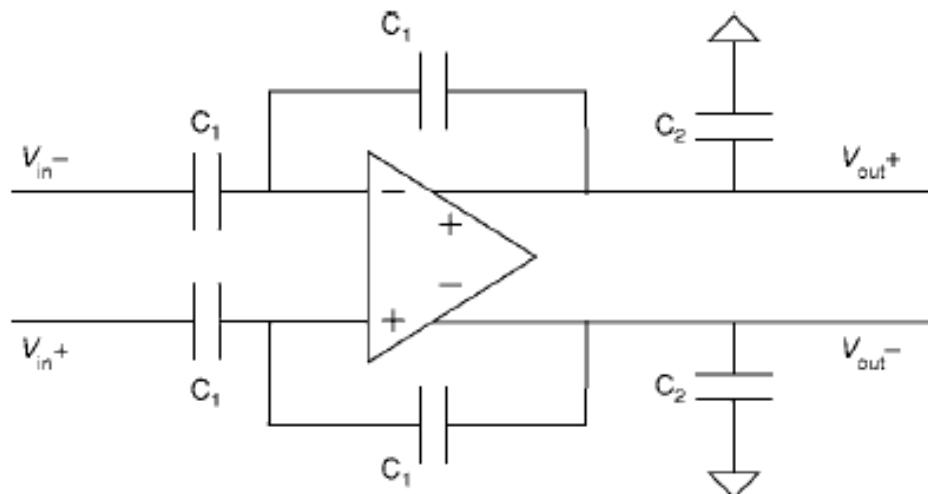


Fig. 3 Unity gain capacitive buffer

Table 1: Performance summary of conventional folded cascode and recycling folded cascode

Parameter	Folded cascode	Recycling folded cascode
C_L (pF)	1	1
GBW (MHz)	467.7	489.8
Power (μ A)	1185	551
Gain (dB)	41.1	50.9
Phase margin (deg)	85.1	77.2
0.1% setting time (ns)	5.7	5.1
Static error (%)	2.04	0.61

Cascode with positive feedback and bulk-driven input stage

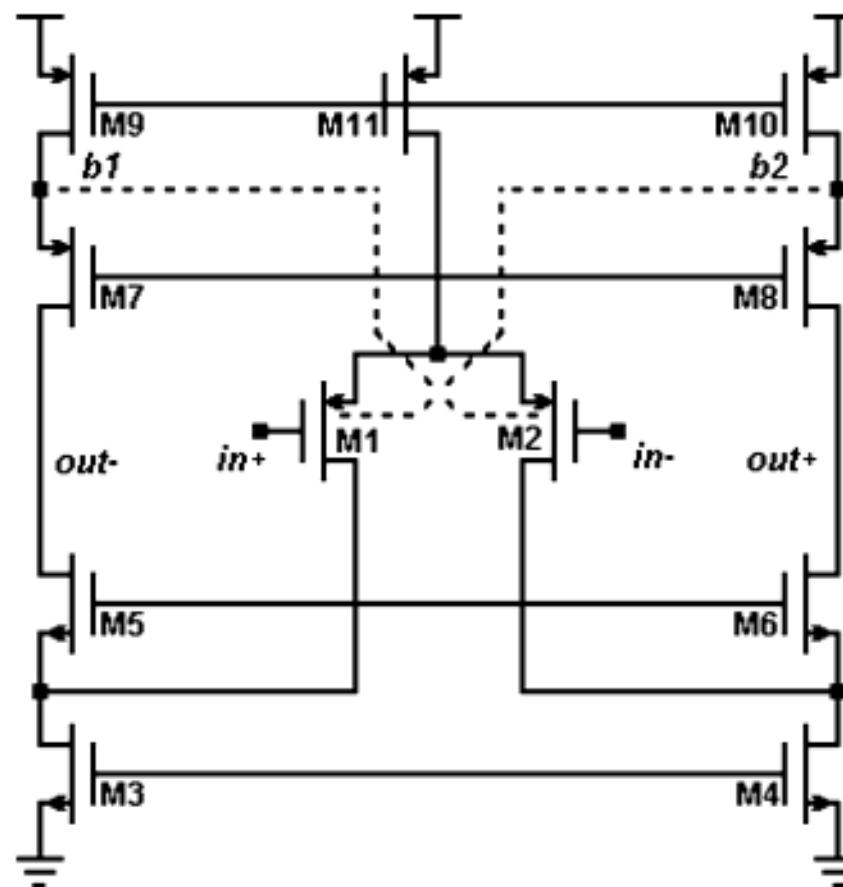


Fig. 1 Scheme of the initial idea to use of bulk and positive feedback.

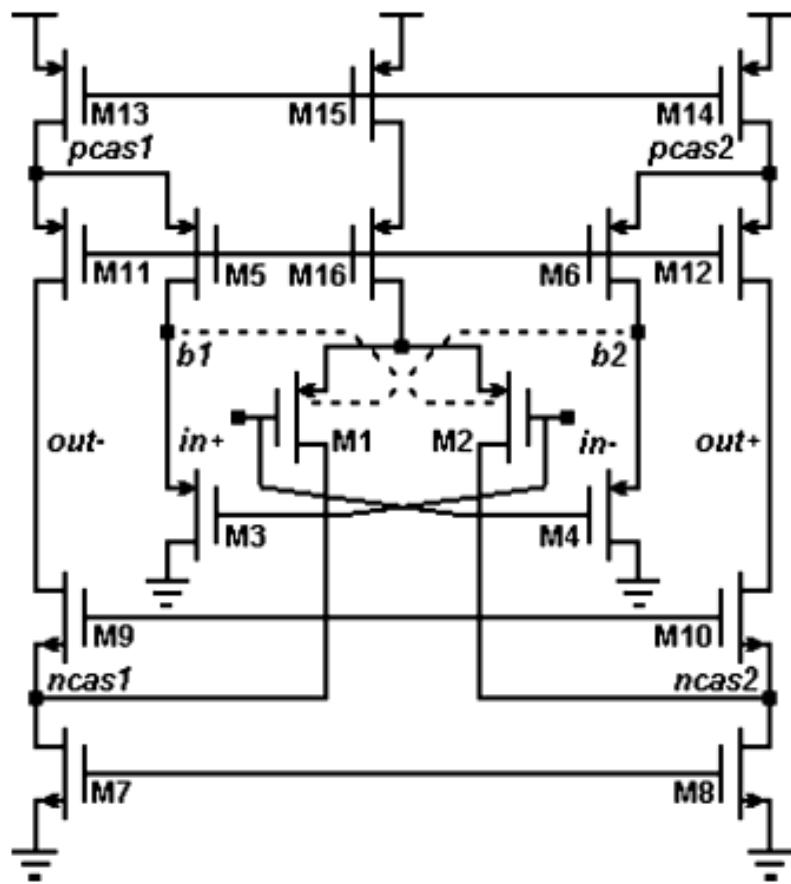


Fig. 2 Scheme of the proposed op-amp.

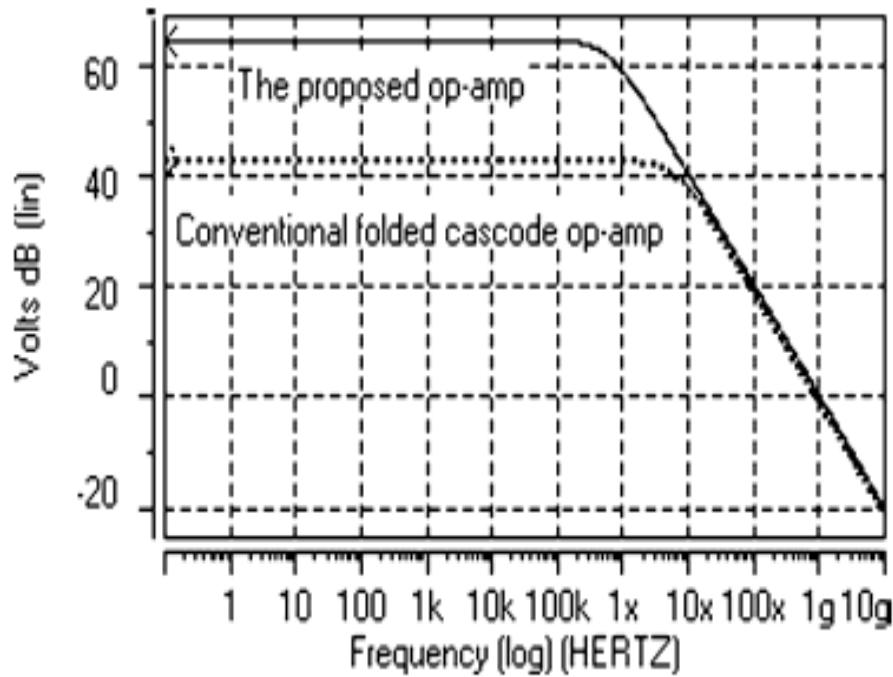


Fig. 3 Gain of the proposed and conventional folded cascode op-amp.

1V CDB Folded Cascode OTA

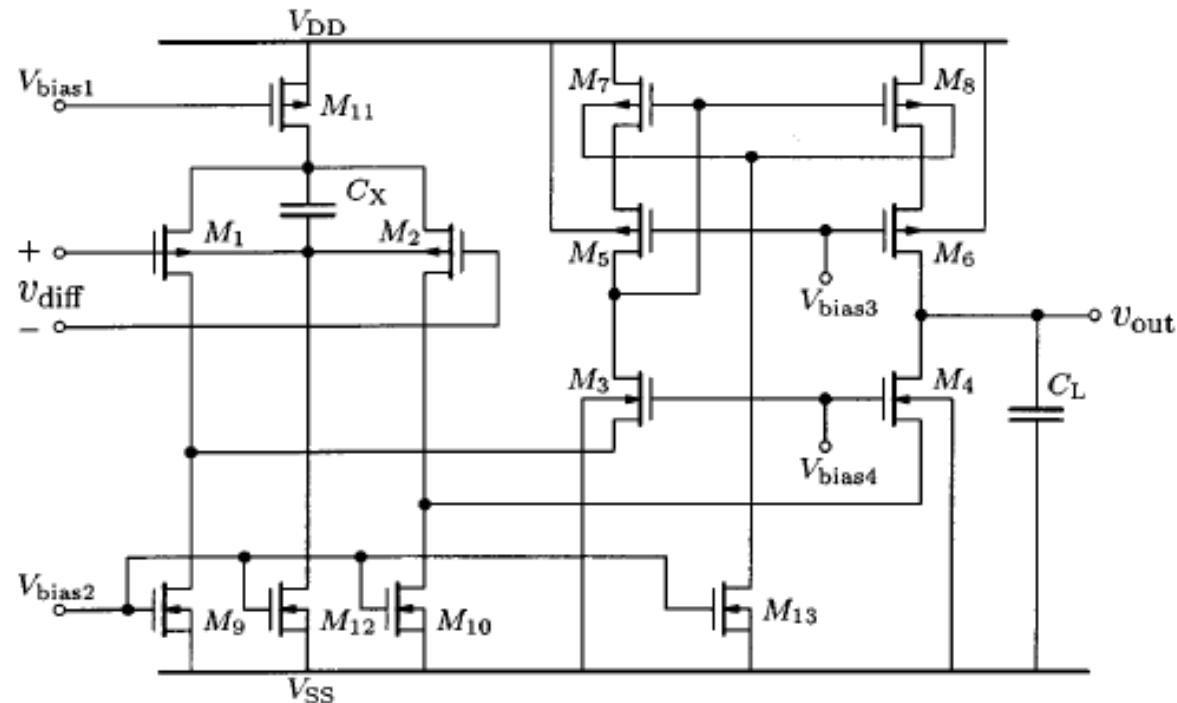


Fig. 6. 1-V CDB folded cascode OTA.

References

S Mallya, and JH Nevin [Design procedures for a fully differential folded-cascode CMOS operational amplifier –IEEE J. of Solid-State Circuits](#) , vol. 24, No. 6, pp, 1737-1740, December 1989 -

- [Folded cascode amplifier with rail-to-rail common-mode range - all 2 versions »](#)

WC Hsu, WR Krenik, JR Hellums - US Patent 4,797,631, 1989 - Google Patents

Page 1. [54] **FOLDED CASCODE AMPLIFIER WITH RAIL-TO-RAIL COMMON-MODE RANGE** [75]

Inventors: Wei-ChanHsu,Piano;WilliamR. Krenik, Dallas; James R. Heliums, ...

Design of a New Folded Cascode Op-Amp Using Positive Feedback and Bulk Amplification

Mohsen ASLONI^{†a)}, Student Member, Khayrollah HADIDI^{†b)}, and Abdollah KHOEI^{†c)}, Members

- R. Assaad and J. Silva-Martinez, "[Enhancing General Performance of the Folded-Cascode Amplifier by Recycling Current](#)", *IEEE Electronics Letters*. Vol. 43, Issue 23, November 2007.

T. Lehmann, M. Cassia, 1-V power supply CMOS cascode amplifier
IEEE J. of Solid-State Circuits, vol 36, pp. 1082-1086, July