

ECEN 607 Exam 1 Problem 4 Solution

Alexander Edward

March 20, 2014

Reverse Nested Miller Compensation (RNMC) with Voltage Buffers

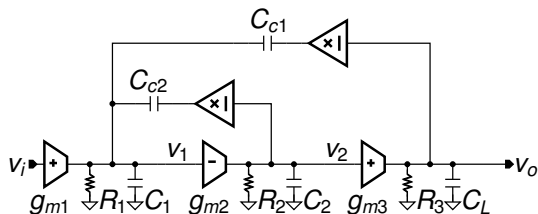


Figure : 3-Stage RNMC with Voltage Buffers Topology

- Write Nodal equations as usual:

$$\frac{v_1}{R_1} + v_1 s C_1 + (v_1 - v_2) s C_{c2} + (v_1 - v_o) s C_{c1} = g_{m1} v_i \quad (1)$$

$$\frac{v_2}{R_2} + v_2 s C_2 = -g_{m2} v_1 \quad (2)$$

$$\frac{v_3}{R_3} + v_3 s C_L = g_{m3} v_2 \quad (3)$$

RNMC with Voltage Buffers: Signal Flow Graph (SFG)

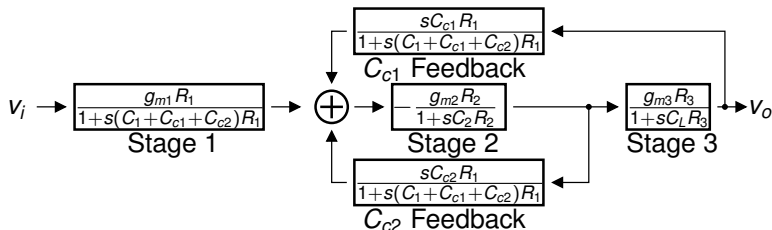


Figure : SFG of 3-Stage RNMC with Voltage Buffers

- ▶ Transform equations to SFG:

$$v_1 = \frac{g_{m1}R_1(v_i) + sC_{c2}R_1(v_2) + sC_{c1}R_1(v_o)}{1 + s(C_1 + C_{c1} + C_{c2})R_1} \quad (4)$$

$$v_2 = -\frac{g_{m2}R_2(v_1)}{1 + sC_2R_2} \quad (5)$$

$$v_3 = \frac{g_{m3}R_3(v_2)}{1 + sC_LR_3} \quad (6)$$

Solve SFG with Mason's Rule

- Use Mason's Rule,

$$\frac{v_o}{v_i} = \frac{\overbrace{\frac{g_{m1}R_1}{1 + s(C_1 + C_{c1} + C_{c2})R_1} + \frac{g_{m2}R_2}{1 + sC_2R_2} + \frac{g_{m3}R_3}{1 + C_LR_3}}^{\text{Feedforward Path } v_i \text{ to } v_o}}{1 + \underbrace{\frac{g_{m2}R_2}{1 + sC_2R_2}}_{C_{c2} \text{ Feedback}} + \underbrace{\frac{g_{m2}R_2}{1 + sC_2R_2} + \frac{g_{m3}R_3}{1 + sC_LR_3} + \frac{sC_{c1}R_1}{1 + s(C_1 + C_{c1} + C_{c2})R_1}}_{C_{c1} \text{ Feedback}}} \quad (7)$$

- Equalize Denominator,

$$\begin{aligned} D(s) &= (1 + s(C_1 + C_{c1} + C_{c2})R_1)(1 + sC_2R_2)(1 + sC_LR_3) \\ &\quad + (1 + sC_LR_3)g_{m2}R_2sC_{c2}R_1 \\ &\quad + g_{m2}R_2g_{m3}R_3sC_{c1}R_1 \end{aligned} \quad (8)$$

- Expand denominator, separate coefficients, do approximation, . . . , and done!

Comments

- ▶ “Works” because voltage buffers greatly simplify SFG (unidirectional).
- ▶ Without voltage buffers, C_{c1} and C_{c2} becomes bidirectional and you need to add extra feedforward paths in SFG.
- ▶ Mason’s rule still holds but becomes more complicated.
- ▶ Good exercise to analyze Miller or Ahuja compensation or transistor-level circuits with this method.