622 (ESS)

ACTIVE - RC FILTERS

The basic building block is illustrated below





Let us assume that $A \rightarrow \infty$, then

 $H(s) = -\frac{Z_2}{Z_1}$

Next we consider particular cases





$$H(s) = -\frac{1}{sR_1C_2}$$
 Integrator

 $H(s) = -s R_2 C$ Differentiator



EXAMPLE: Let
$$Z_1 = \frac{R_1}{1 + sR_1C_1}$$
, $Z_F = \frac{R_F}{1 + sR_FC_F}$
Assuming ideal op amp A $\longrightarrow \infty$. Then using (1)

$$H_{1} = \frac{V_{01}}{V_{1}} = -\frac{R_{F}/R_{1}(1 + sR_{1}C_{1})}{(1 + sR_{F}C_{F})} = -\frac{K_{n}(1 + s/\omega_{z})}{(1 + s/\omega_{p})}$$
(4)



(3)

Particular cases are easily derived from (3) and (4)

- Integrator:
$$C_1 \rightarrow 0$$
, $R_F \rightarrow \infty$
 $H_1 \cong -\frac{R_F}{R_1} \frac{1}{sR_F C_F} = -\frac{1}{sC_F R_1}$
- Differentiator; $R_1 \rightarrow \infty$, $C_F \rightarrow 0$
 $H_1 \cong -\frac{R_F}{R_1} sR_1 C_1 = -sR_F C_1$
- Low-Pass: $C_1 = 0$
 $H_1 = \frac{-\frac{R_F}{R_1}}{1+sR_F C_F}$
- High-Pass: $R_1 \rightarrow \infty$
 $H_1 \cong -\frac{R_F}{R_1} \frac{sR_1 C_1}{1+sR_F C_F}$



Exercise 1. Obtain the transfer function of the following circuit.



Second-Order Filters Based on a Two-Integrator Loop.

• We can design a second-order filter by cascading two inverters. i.e.



$$\frac{V_{o}}{v_{i}} = \frac{-\frac{R_{F1}}{R_{1}} \left(-\frac{R_{F2}}{R_{2}}\right)}{(1+sC_{F1}R_{F1})(1+sC_{F2}R_{F2})} = \frac{\frac{R_{F1}}{R_{1}}\frac{R_{F2}}{R_{2}}}{s^{2}C_{F1}R_{F1}C_{F2}R_{F2} + s(C_{F1}R_{F1} + C_{F2}R_{F2}) + 1}$$
(6)

What are the locations of the poles?

$$s_{p_{1,2}} = \frac{-(C_{F1}R_{F1} + C_{F2}R_{F2}) \pm \sqrt{(C_{F1}R_{F1} + C_{F2}R_{F2})^2 - 4C_{F1}R_{F1}C_{F2}R_{F2}}}{2C_{F1}R_{F1}C_{F2}R_{F2}}$$

To have complex poles it requires that

$$(C_{F1}R_{F1})^2 + (C_{F2}R_{F2})^2 - 2C_{F1}R_{F1}C_{F2}R_{F2} < 0?$$

Which it is impossible to satisfy. Therefore, cascading two first-order filter yield a second-order filter with only real poles.

The general form of the second order two-integrator loop has the following topology.



Note the similarity of Eq. (7a) with (2). Also observe that A "-1" needs to be inserted before or after the second inverter to yield a negative feedback loop.

Let us consider the following filter where

$$Z_3 = R_3, Z_1 = R_1, Z_2 = R_2, Z_{F1} = \frac{1}{sC_{F1}}, Z_{F2} = \frac{R_{F2}}{1 + sC_{F2}R_{F2}}$$

Thus Eq. (7a) yields:

$$H = \frac{-\frac{1}{sC_{F1}R_3} \frac{R_{F2}/R_2}{(1 + sC_{F2}R_{F2})}}{1 + \frac{1}{sC_{F1}R_1} \frac{R_{F2}/R_2}{(1 + sC_{F2}R_{F2})}}$$

$$H = \frac{-\frac{1}{C_{F1}R_{3}C_{F2}R_{2}}}{s^{2} + \frac{s}{C_{F2}R_{F2}} + \frac{1}{C_{F1}R_{1}C_{F2}R_{2}}} = \frac{-\omega_{o1}^{2}}{s^{2} + \frac{\omega_{o}}{Q}s + \omega_{o}^{2}}$$

By injecting in different current summing nodes a general biquad filter can be obtained.



$$V_{o} = \frac{V_{3} \frac{1}{C_{F1}R_{3}C_{F2}R_{2}} + V_{2}sC_{F1}R_{1}K_{2} - V_{3}sC_{1}R_{1}K_{3}}{s^{2} + \frac{s}{C_{F2}R_{F2}} + \frac{1}{C_{F1}R_{1}C_{F2}R_{2}}}$$

Exercise 2. Obtain the expressions of V_{o1} and V_{o2} .

More general biquad expressions and topologies can be obtained by adding a summer.



Exercise 3. Draw an active-RC topology of the block diagram show above.

Exercise 4 a) For only $V_1 \neq 0$ obtain V_0 and V_{01} when instead of the resistor R_{F2}/K_3 a capacitor $K_4 C_{F2}$ is used. b) For only $V_3 \neq 0$ obtain V_{01} when the resistor R_3 is replaced by a capacitor $K_{HP}C_{F1}$.

By using also the positive input of the op amp other useful filters can be obtained.



Example. Phase shifter $Z_2 = R_2 = R_1$, $Z_1 = R_1$, $Z_R = R_1$, $Z_C = \frac{1}{sC}$ and $A \rightarrow \infty$ with $V_1 = V_2$

$$\frac{V_{o}}{V_{1}} = -1 + \frac{sRC}{1 + sRC} \cdot 2 = \frac{-1 - sRC + 2sRC}{1 + sRC} = -\frac{1 - sRC}{1 + sRC}$$

Sallen and Key Bandpass Filter



K is a non-inverting amplifier

Using Nodal Analysis

$$V_{1}\left(s(C_{1}+C_{2})+\frac{1}{R_{1}}+\frac{1}{R_{3}}\right)-sC_{2}V_{2}-\frac{V_{o}}{R_{3}}=\frac{V_{i}}{R_{1}}$$
(1)

$$-V_{1}(sC_{2}) + V_{2}\left(sC_{2}+\frac{1}{R_{2}}\right)=0$$
(2)

$$V_{o}=KV_{2}$$
(3)

$$H(s)=\frac{V_{o}(s)}{V_{i}(s)}=\frac{K\frac{s}{R_{1}C_{1}}}{s^{2}+\left[\frac{1}{R_{2}C_{2}}+\left(1-K+\frac{R_{3}}{R_{1}}+\frac{R_{3}}{R_{2}}\right)\frac{s}{R_{3}C_{1}}+\frac{R_{1}+R_{3}}{R_{1}R_{3}R_{2}C_{1}C_{2}}\right]}$$

A particular case is for $R_1 = R_2 = R_3 = R$, $C_1 = C_2 = C$

Then

$$\omega_{o}^{2} = \frac{2}{(RC)^{2}} ; \quad Q = \frac{\sqrt{2}}{4 - K}$$

or for a given ω_{o} and Q
 $RC = \frac{\sqrt{2}}{\omega_{o}}$ and $K = 4 - \frac{\sqrt{2}}{Q}$

Exercise 5. Prove the transfer function is a BP filter of the following circuit



In the past before IC fabrication, active filters implementation preferred one op amp structure. One very popular type is the Sallen and Key unity gain implementations.



 $H_{LP}(s) = \frac{\omega_o^2}{s^2 + \frac{\omega_o}{Q}s + \omega_o^2}$ $R_1 = R_2 = R$ $C_1 = C$ $C_2 = 4Q^2C$ $RC = 1/2 \omega_o Q$

One also popular topology is the Rauch Filter



$$H(s) = \frac{\frac{1}{R_2 C_2 R_3 C_1}}{s^2 + \frac{s}{C_1} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right) + \frac{1}{R_1 C_1 R_2 C_2}}$$

LP Rauch Filer

Another technique for analysis and design based on state-variable uses building blocks.



REPRESENTATION







Let us apply to a two-integrator loop plus Mason's Rule.



For Second-topology

$$V_{o1} = \frac{-K_{1}V_{in}}{1 + \frac{K_{Q}}{s} + \frac{K_{o1}K_{o2}}{s^{2}}} = \frac{-K_{1}s^{2}V_{in}}{s^{2} + K_{Q}s + K_{o1}K_{o2}}$$
HP
$$V_{o2} = \frac{\frac{-K_{1}}{s}V_{in}}{1 + \frac{K_{Q}}{s} + \frac{K_{o1}K_{o2}}{s^{2}}} = \frac{-K_{1}sV_{in}}{s^{2} + K_{Q}s + K_{o1}K_{o2}}$$
BP

15

Next we show that we can go from an Active-RC representation into a block diagram or vice versa.





ELEN 622 (ESS) Non-Ideal Active-RC Integrators

Op Amp Non-Idealities





where

$$\beta = \frac{Z_1}{Z_1 + Z_2}$$

Integrator

Case 1

$$Z_1 = R_1; Z_2 = \frac{1}{sC_2}; \frac{GB}{s} = A(s)$$

$$H(s) \cong \frac{-1}{\frac{sRC}{GB}} \left(s + \frac{1}{RC} + GB\right) \cong -\frac{1}{sRC(1 + s/GB)}; GBRC >> 1$$

$$H(j\omega) = \frac{-1}{\frac{-\omega^2 RC}{GB} + j\omega RC}; \quad \phi = \langle H(j\omega) = -\frac{\pi}{2} - tan^{-1}(\omega/GB)$$

 $\phi = -90^{\circ} + \Delta \phi$



$$\Delta \phi \cong -tan^{-1} \frac{\omega}{GB} \cong -tan^{-1} \frac{1}{|A(j\omega)|} \quad ; \quad \text{i.e.} \frac{\omega_{\text{o}}}{GB} = \frac{1}{10}$$
$$\Delta \phi \cong -5.7^{\circ}$$

$$\left|H\left(j\omega_{o}\right)\right| = \frac{1}{\left|\frac{-\omega_{o}}{GB} + \frac{j\omega_{o}}{\omega_{o}}\right|} = \frac{1}{\sqrt{1 + \frac{\omega_{o}^{2}}{GB^{2}}}} = 1 + \Delta_{M}$$



i.e.
$$\frac{\omega_o}{GB} = 0.1$$

 $\Delta_M \sim 5\%$ error

It follows that the ideal -6 dB/octave roll-off expected from an ideal integrator changes to -12 dB/octave at the frequency of the parasitic pole given by

$$s_p = -\left(\omega_t + \frac{1}{CR}\right)$$



$$Q_L = -\left(\frac{\omega_t}{\omega}\right) = -\left(\frac{GB}{\omega}\right)$$

In general

$$T(j\omega) = \frac{1}{R(\omega) + jX(\omega)}$$

then we define the integrator Q-factor by

$$Q_{I} = \frac{X(\omega)}{R(\omega)}$$
$$Q_{I} = -\left(\frac{\omega_{t}}{\omega}\right) = -|A(j\omega)|$$

Making an analogy of Q_L of an inductor

$$Q_L = \frac{\omega_o L}{R_L} \qquad \qquad \underbrace{\begin{array}{c} L \\ -\infty \\ Lossy Part \end{array}}_{\text{Lossy Part}}$$

For an integrator one can obtain

$$Q_{I} = \frac{\omega RC}{\frac{-\omega^{2} RC}{GB}} = -\frac{1}{\frac{\omega}{GB}} = \frac{-1}{\omega} GB = -|A(j\omega)|$$



Miller Integrator

How can we compensate this degradation of performance?









This integrator yields a positive

$$Q_I = + |A(j\omega)|$$

622 (ESS)

ACTIVE - RC INTEGRATOR: Pole Shift and Predistortion



Let $A(s) = \frac{A_0 \omega_{3dB}}{s + \omega_{3dB}}$; where A_0 is the DC gain and ω_{3dB} the dominant pole in open loop.

Then (1b) becomes

$$\frac{V_{o}}{V_{i}} = \frac{-\frac{A_{o}\omega_{3dB}}{RC}}{s^{2} + s\left(A_{o}\omega_{3dB} + \omega_{3dB} + \frac{1}{RC}\right) + \frac{\omega_{3dB}}{RC}} \approx \frac{-\frac{A_{o}\omega_{3dB}}{RC}}{s^{2} + sA_{o}\omega_{3dB} + \frac{\omega_{3dB}}{RC}}$$
(2)

Let GB= $A_0 \omega_{3dB}$

G. Daryanani, "Principles of Active Network Synthesis and Design," John Wiley and Sons, 1976.

The roots of the denominator are

$$P_{1,2} = -\frac{GB}{2} \pm \frac{GB}{2} \left[1 - \frac{4\omega_{3dB}}{(GB)^2 RC} \right]^{1/2}$$
(3a)

Using the approximation $(1-X)^{1/2} \cong 1 - X/2$ for X<<1, then

$$P_{1,2} = -\frac{GB}{2} \pm \frac{GB}{2} \left[1 - \frac{2\omega_{3dB}}{(GB)^2 RC} \right]$$

Thus the roots yield

$$P_1 = -\frac{1}{A_o RC}$$

$$P_2 = -GB + \frac{1}{A_0 RC} \cong -GB$$

(3b)

The Bode Plot Looks Like



PREDISTORTION; FREQUENCY COMPENSATION

In order to relax the bandwidth op amp requirement one can use a R_C or C_C on the Miller Integrator. That is



Use
$$R_C C = \frac{1}{GB}$$
 or $C_C R \cong \frac{1}{GB}$

B. Wu and Y. Chiu, "A 40nm CMOS Derivative-Free IF Active-RC BPF with Programmable Bandwidth and Center Frequency Achieving Over 30dBm IIP3", IEEE JSSC, Vol. 50, No. 8, pp 1772-1784, August 2015.

Using VCVS vs. VCIS in Active-RC Filters

The motivation is to use OTA (VCIS) instead of more power hungry Op Amp (VCVS)



For $R_0 = Z_0 = 0$ $\frac{V_o}{V_i} = \frac{-\frac{Z_F}{Z_1}}{1 + \frac{1}{A} \left(1 + \frac{Z_F}{Z}\right)}$ If $A \rightarrow \infty$, then $\frac{V_o}{V_i} = -\frac{Z_F}{Z_1}$ $\frac{V_{o}}{V_{i}} = -\frac{Z_{2}}{Z_{1}} \frac{1 - \frac{1}{g_{m}Z_{2}}}{\frac{1}{Z_{1}} + \frac{Z_{1} + Z_{2}}{Z_{1}Z_{L}}}$ $g_{m} >> \frac{1}{Z_{2}} \\ g_{m} >> \frac{1}{Z_{1}} + \frac{Z_{1} + Z_{2}}{Z_{1}Z_{T}} \begin{cases} \frac{V_{o}}{V_{i}} = -\frac{Z_{2}}{Z_{1}} \end{cases}$ It can be shown that for equal $A(s) = \frac{GB}{s}$, the Tow-Thomas filter has the following deviations



$$Q_{a} = Q_{o} \frac{1}{1 - 4Q_{o}\omega_{o}/GB}$$
or
$$\frac{4Q_{o}\omega_{o}}{GB} < 1; \quad 4Q_{o}\omega_{o} < GB$$
and
$$\frac{\Delta\omega_{o}}{\omega_{o}} \approx -\frac{2 + k}{2} \frac{\omega_{o}}{GB}$$

Improved version by replacing noninverting integrator:



How to generate Fully-Differential Filters based on Single-Ended Version?



Fully-Differential Version

Particular Case. Assume no V_i^- is Available.





KHN State Variable Two-Integrator Filter

Use Mason's Rule:

$$\frac{V_{LP}}{V_i} = \frac{-K_{32}K_{01}K_{02}/s^2}{1 + \frac{K_{01}K_{02}}{s} + \frac{K_{01}K_{02}K_{03}}{s^2}} = \frac{-K_{32}K_{01}K_{02}}{s^2 + K_{01}K_{02}s + K_{01}K_{02}K_{03}}$$

Next we consider the fully-differential version of the KHN filter.



KHN Fully-Differential Version

How can we take advantage of improved combination of $\pm Q_I$ in fully differential versions?



622 (ESS)

Effects of Non-Ideal Op Amps on the Tow-Thomas Biquad



When A_i (i = 1,2,3) are finite, the denominator becomes of the transfer function yields:

$$D(s) = s^{2} + s\frac{\omega_{o}}{Q}\frac{1 + \frac{2Q+1}{A_{1}} + \frac{1+Q}{A_{2}} + \frac{3Q+1}{A_{1}A_{2}}}{1 + \frac{1}{A_{1}} + \frac{1}{A_{2}} + \frac{1}{A_{1}A_{2}}} + \omega_{o}^{2}\frac{\frac{1}{1 + \frac{2}{A_{3}}} + \frac{2}{A_{1}A_{2}} + \frac{1}{QA_{2}} + \frac{1}{QA_{1}A_{2}}}{1 + \frac{1}{A_{1}} + \frac{1}{A_{2}} + \frac{1}{A_{1}A_{2}}}$$

Let
$$A_i = \frac{GB_i}{s}$$
, $i = 1, 2, 3$
Furthermore assume the range of interest $\omega >> \frac{GB_i}{A_{oi}}$ and $\frac{\omega_o}{GB_i} << 1, Q >> 1$. Then D(s) becomes:

$$D(s) = \frac{1}{\omega_o} \left(\frac{\omega_o}{GB_1} + \frac{\omega_o}{GB_2} + 2\frac{\omega_o}{GB_3} \right) s^3 + \left(1 + 2\frac{\omega_o}{GB_1} + \frac{\omega_o}{GB_2} \right) s^2 + \frac{\omega_o}{Q} \left(1 + \frac{\omega_o}{GB_2} \right) s + \omega_o^2$$

$$D(s) = \left(s^{2} + \frac{\omega_{oa}}{Q_{a}}s + \omega_{oa}^{2}\right)\left(\frac{s}{\omega_{o}}\right)\left(\frac{\omega_{o}}{GB_{1}} + \frac{\omega_{o}}{GB_{2}} + 2\frac{\omega_{o}}{GB_{3}}\right)$$

Thus

$$\begin{split} \omega_{oa} & \underline{\Delta} \; \omega_{o} (1 + \Delta_{\omega}) \\ \text{or } \Delta_{\omega} &= \frac{\omega_{oa} - \omega_{o}}{\omega_{o}} \\ \text{for } \Delta_{\omega} &< 1 \text{ and } Q_{a} >> 1, \text{ then} \\ \Delta_{\omega} &= -\frac{\omega_{o}}{GB_{1}} - \frac{1}{2} \frac{\omega_{o}}{GB_{2}} \bigg|_{GB_{1} = GB_{2} = GB} = -\frac{3}{2} \bigg(\frac{\omega_{o}}{GB} \bigg) \end{split}$$
$$\frac{Q_a}{Q} \approx \frac{1}{1 - Q\left(\frac{\omega_o}{GB_1} + \frac{\omega_o}{GB_2} + 2\frac{\omega_o}{GB_3}\right)}$$

For equal $GB_1 = GB_2 = GB_3$

$$\begin{aligned} Q_{a} &= \frac{Q}{1 - 4Q(\omega_{o}/GB)} \\ Q_{a} &\cong Q \bigg(1 + 4Q \bigg(\frac{\omega_{o}}{GB} \bigg) \bigg) \quad , \quad \text{for } 4Q \bigg(\frac{\omega_{o}}{GB} \bigg) <<1 \end{aligned}$$

Note that for a stable filter $4Q \ \omega_o/GB < 1$ or $Q < \frac{GB}{4\omega_o}$

ECEN 622 (ESS) TAMU

KEY FILTER PARAMETERS IN ACTIVE-RC FILTERS

- Dynamic Range
- Signal-To-Noise Ratio
- Total Output Noise
- Noise Power Spectral Density
- Total Area

Resistor and Capacitors can be expressed as:

 $R_\ell = r_\ell \ R \quad , \quad C_\ell = c_\ell \ C$

where r_{ℓ} and c_{ℓ} are the normalized filter values.

The resistor power dissipation for a sinusoidal input yields

$$P_{R}(f) = \sum_{\ell} \frac{|V_{i}H_{i\ell}|^{2}}{2R_{\ell}} = \frac{|V_{i}|^{2}}{2R} \sum_{\ell} \frac{|H_{i\ell}(f)|^{2}}{r_{\ell}}$$
(1)

Where $H_{i\ell}(f)$ is the transfer function from the input to the terminals of resistor R_{ℓ}

Reference. L. oth et all, "General Results for Resistive Noise in Active RC and MOSFET-C Filters", *IEEE Trans on Circuits and Systems II*, Vol. 42, No. 12, pp. 785-793, December 1995.

Focusing on the noise resistor, the power spectral density is given by

$$S_{R}(f) = \sum_{\ell} 4kTR_{\ell} |H_{\ell o}(f)|^{2} = 4kTR\sum_{\ell} r_{\ell} |H_{\ell o}(f)|^{2}$$
(2)

The definition of $H_{\ell o}(f)$ is pictorially shown below:



Thus, the total output noise (mean squared value) due to the resistors become

$$N_R = \int_0^\infty S_R(f) df$$

In practice the upper limit of the integration is limited to a useful practical value.

The signal-to-ratio for a given V_i and frequency f is given by

$$SNR = \frac{|V_i H(f)|^2}{2N_R}$$
(3)

and

 $\max_{f} P_{R}(f) \leq P_{R,max}$

where $P_{R,max}$ is the maximum specified power dissipation in the resistors. Then

$$DR = \frac{\left|V_{i}\right|_{\max}^{2} \max_{f} \left|H(f)\right|^{2}}{2N_{R}}$$
(4)

Let us consider a second - order BP filer example

$$H_{BP}(s) = \frac{\frac{\omega_c}{Q}s}{s^2 + \frac{\omega_c}{Q}s + \omega_c^2}$$

Using the following notation the above $H_{BP}(s)$ yields

$$H_{BP}(f) = \frac{Q^{-1}f_{c}(jf)}{(jf)^{2} + Q^{-1}f_{c}(jf) + f_{c}^{2}}$$

$$P_{R}(f_{c}) = \frac{\left|V_{i}\right|^{2}}{R} a \left(a + Q^{-1}\right)$$

For the biquad shown below



and

$$N_{R} = \frac{2kT}{C} \frac{\left(1 + Q/a\right)}{a}$$

 $a \uparrow \Rightarrow N_R \downarrow \Rightarrow a V_{OBP}$ limited by linearity and by resistor power dissipation which is proportional to $(a)^2$.

Fully Differential Fully Balanced Circuits

What is the problem with single-input / single-output?



$$\begin{split} \mathbf{V}_{n} &= \frac{\mathbf{V}_{o}\mathbf{Z}_{1}}{\mathbf{Z}_{1} + \mathbf{Z}_{F}} \\ \mathbf{V}_{1} &= \mathbf{V}_{n} = \frac{\mathbf{V}_{o}}{\mathbf{A}} \begin{vmatrix} = \mathbf{0} \\ \mathbf{A} \rightarrow \mathbf{\infty} \end{vmatrix} \end{split}$$

For
$$V_i = V_{id} + V_{icm}$$

 $V_o = \left(1 + \frac{Z_F}{Z_1}\right)(V_{id} + V_{icm})$

No elimination of common-mode signal.

How to solve this problem?



For
$$V_i = V_{id} + V_{icm} = (V_1 - V_2) + \frac{(V_1 + V_2)}{2}$$

 $V_o = \frac{Z_F}{Z_1}(V_1 - V_2)$
No common-mode output.

How to obtain a fully differential circuit? We will discuss two potential approaches

Approach 1

Approach 2



Remark: sensitive to CM signals

common-mode signals

First-Order FB Low Pass with Op Amp
*
.subckt opamp non inv out
rin non inv 100K
egain 1 0 (non, inv) 200K
ropen 1 2 2K
copen 2 0 15.9155u
eout 3 0 (2,0) 1
rout 3 out 50
.ends
*vin 3 31 ac 1.0
vin 31 0 ac 1.0
x1 4 1 2 opamp
x2 4 11 22 opamp
R1 3 1 1K
R11 3 4 1K
R1B 31 4 1K
R1BB 31 11 1K
RF1 2 1 1K
RF1B 22 11 1K
RF11 4 0 1K
RF11B 4 0 1K
C1 2 1 0.159155u
C1B 22 11 0.159155u
C1A 4 0 0.159155u
C11B 4 0 0.159155u
rdummy 3 31 1
.ac dec 10 10Hz 10KHz
.probe
.end



Fully Balanced T-T Active-RC Implementation



622 Active FiltersBy Edgar Sánchez-SinencioTexas A&M University

Introduction to Matlab and Simulink For Filter Design

Example 1: Ideal Integrator



 $R = 1K\Omega$ C = 0.159mF

Bode Plot: Ideal Integrator (Matlab)



Bode Plot: Ideal Integrator (Simulink)

1) Create Model using Gain, Integrator, and In/Out blocks



2) Go to: Tools => Control Design=> Linear Analysis

3) Then press: Linearize model



Tow-Thomas Biquad (Simulink)



Output Waveform (Scope)



Integrator Non-ideal amplifier

```
clear
clc
s=tf('s');
R=1;
                   %Resistor Value
C=0.159e-3;
                   %Capacitor Value
hs1=-1/(R*C*s);
                   %hs= Vo(s)/Vi(s)
figure(1)
bodemag(hs1)
hold on
f=1e3;
for i=1:5;
GBW=2*pi*f;
A=GBW/s;
Beta=R/(R+1/(s*C));
hs2=-1/(R*C*s)*1/(1+1/(A*Beta));
hold on
bodemag(hs2,{2*pi*1,2*pi*1e5})
f=10*f:
end
grid minor
                       %Add grid to plot
                        %change X-axis units
h= gcr;
h.AxesGrid.Xunits = 'Hz'; %Set units to Hz
legend('ideal', 'GBW=1kHz', 'GBW=10kHz', 'GBW=100kHz', 'GBW=1MHz', 'GBW=10MHz', 1)
```



Filter Approximation: Low-Pass Butterworth

 E.g.: Use Matlab to find the numerator b and denominator a coefficients for a third-order Butterworth low-pass filter prototype with normalized cutoff frequency.

[z,p,k]=buttap(3); % To get gain and poles [b,a]=zp2tf(z,p,k); %To get b and a coefficients H=tf([b],[a]); %to generate transfer function figure(1) bode(H); %Bode plot grid minor; figure(2) pzmap(H); %plot poles and zeros grid minor;

The squared magnitude of a low-pass butterworth filter is given by:

$$|H(\omega)|^2 = \frac{1}{1 + (\omega/\omega_0)^{2n}}$$

Results:

```
b = 0 0 0 1
a = 1 2 2 1
```

Thus,

$$H(s) = \frac{1}{s^3 + 2s^2 + 2s + 1}$$

Pole-zero plot



Bode Plot



• Use the Matlab cheb1ap function to design a second order Type I Chebyshev low-pass filter with 3dB ripple in the pass band

```
w=0:0.05:400; % Define range to plot
[z,p,k]=cheb1ap(2,3);
[b,a]=zp2tf(z,p,k); % Convert zeros and poles of G(s) to polynomial form
bode(b,a)
grid minor;
```



% Another way to write the code!

w=0:0.01:10;

[z,p,k]=cheb1ap(2,3);

[b,a]=zp2tf(z,p,k);

Gs=freqs(b,a,w);

xlabel('Frequency in rad/s');

ylabel('Magnitude of G(s)');

semilogx(w,abs(Gs));

title('Type 1 Chebyshev Low-Pass Filter'); Grid;



Inverse Chebyshev

• Using the Matlab cheb2ap function, design a third order Type II Chebyshev analog filter with 3dB ripple in the stop band.

```
w=0:0.01:1000;
[z,p,k]=cheb2ap(3,3);
[b,a]=zp2tf(z,p,k); Gs=freqs(b,a,w);
semilogx(w,abs(Gs));
xlabel('Frequency in rad/sec');
ylabel('Magnitude of G(s)');
title('Type 2 Chebyshev Low-Pass Filter, k=3, 3 dB ripple in stop
band');
grid
```

Inverse Chebyshev



Elliptic Low-Pass Filter

• Use Matlab to design a four pole elliptic analog low-pass filter with 0.5dB maximum ripple in the pass-band and 20dB minimum attenuation in the stop-band with cutoff frequency at 200 rad/s.

```
w=0: 0.05: 500;
[z,p,k]=ellip(4, 0.5, 20, 200, 's');
[b,a]=zp2tf(z,p,k);
Gs=freqs(b,a,w);
plot(w,abs(Gs))
title('4-pole Elliptic Low Pass Filter');
grid
```

Elliptic Low-Pass Filter



Transformation Methods

- Transformation methods have been developed where a low pass filter can be converted to another type of filter by simply transforming the complex variable s.
- Matlab lp2lp, lp2hp, lp2bp, and lp2bs functions can be used to transform a low pass filter with normalized cutoff frequency, to another low-pass filter with any other specified frequency, or to a high pass filter, or to a band-pass filter, or to a band elimination filter, respectively.

LPF with normalized cutoff frequency, to another LPF with any other specified frequency

• Use the MATLAB **buttap** and **lp2lp** functions to find the transfer function of a third-order Butterworth low-pass filter with cutoff frequency fc=2kHz.

```
% Design 3 pole Butterworth low-pass filter (wcn=1 rad/s)
[z,p,k]=buttap(3);
[b,a]=zp2tf(z,p,k);
                           % Compute num, den coefficients of this filter
(wcn=lrad/s)
f=1000:1500/50:10000; % Define frequency range to plot
                            % Convert to rads/sec
w=2*pi*f;
fc=2000;
                           % Define actual cutoff frequency at 2 KHz
wc=2*pi*fc;
                           % Convert desired cutoff frequency to rads/sec
                          % Compute num, den of filter with fc = 2 \text{ kHz}
[bn,an]=lp2lp(b,a,wc);
Gsn=freqs(bn,an,w);
                          % Compute transfer function of filter with fc = 2 \text{ kHz}
semilogx(w,abs(Gsn));
grid;
xlabel('Radian Frequency w (rad/sec)')
ylabel('Magnitude of Transfer Function')
title('3-pole Butterworth low-pass filter with fc=2 \text{ kHz} or wc = 12.57 \text{ kr/s'})
```

LPF with normalized cutoff frequency, to another LPF with any other specified frequency



High-Pass Filter

• Use the MATLAB commands **cheb1ap** and **lp2hp** to find the transfer function of a 3-pole Chebyshev high-pass analog filter with cutoff frequency fc = 5KHz.

% Design 3 pole Type 1 Chebyshev low-pass filter, wcn=1 rad/s

[z,p,k]=cheb1ap(3,3);

[b,a]=zp2tf(z,p,k); f=1000:100:100000;

fc=5000;

wc=2*pi*fc;

[bn,an]=lp2hp(b,a,wc);

% Compute num, den coef. with wcn=1 rad/s

% Define frequency range to plot

% Define actual cutoff frequency at 5 KHz

% Convert desired cutoff frequency to rads/sec

% Compute num, den of high-pass filter with fc =5KHz

Gsn=freqs(bn,an,2*pi*f); % Compute and plot transfer function of filter with fc = 5 KHz semilogx(f,abs(Gsn));

grid;

xlabel('Frequency (Hz)');

ylabel('Magnitude of Transfer Function')

title('3-pole Type 1 Chebyshev high-pass filter with fc=5 KHz ')

High-Pass Filter



Band-Pass Filter

• Use the MATLAB functions **buttap** and **lp2bp** to find the transfer function of a 3-pole Butterworth analog band-pass filter with the pass band frequency centered at fo = 4kHz, and bandwidth BW =2KHz.

% Design 3 pole Butterworth low-pass filter with wcn=1 rad/s [z,p,k]=buttap(3);[b,a]=zp2tf(z,p,k);% Compute numerator and denominator coefficients for wcn=1 rad/s % Define frequency range to plot f=100:100:100000; f0=4000; % Define centered frequency at 4 KHz W0=2*pi*f0; % Convert desired centered frequency to rads/s fbw=2000; % Define bandwidth Bw=2*pi*fbw; % Convert desired bandwidth to rads/s [bn,an]=lp2bp(b,a,W0,Bw); % Compute num, den of band-pass filter % Compute and plot the magnitude of the transfer function of the band-pass filter Gsn=freqs(bn,an,2*pi*f); semilogx(f,abs(Gsn));

grid;

xlabel('Frequency f (Hz)');

ylabel('Magnitude of Transfer Function');

title('3-pole Butterworth band-pass filter with f0 = 4 KHz, BW = 2KHz')

Band-Pass Filter



Band-Elimination (band-stop) Filter

• Use the MATLAB functions **buttap** and **lp2bs** to find the transfer function of a 3-pole Butterworth band-elimination (band-stop) filter with the stop band frequency centered at fo = 5 kHz, and bandwidth BW = 2kHz.

[z,p,k]=buttap(3);	% Design 3-pole Butterworth low-pass filter, wcn = 1 r/s
[b,a]=zp2tf(z,p,k);	% Compute num, den coefficients of this filter, wcn=1 r/s
f=100:100:100000;	% Define frequency range to plot
f0=5000;	% Define centered frequency at 5 kHz
W0=2*pi*f0;	% Convert centered frequency to r/s
fbw=2000;	% Define bandwidth
Bw=2*pi*fbw;	% Convert bandwidth to r/s

% Compute numerator and denominator coefficients of desired band stop filter [bn,an]=lp2bs(b,a,W0,Bw);

% Compute and plot magnitude of the transfer function of the band stop filter Gsn=freqs(bn,an,2*pi*f); semilogx(f,abs(Gsn));

grid;

xlabel('Frequency in Hz'); ylabel('Magnitude of Transfer Function'); title('3-pole Butterworth band-elimination filter with f0=5 KHz, BW = 2 KHz')

Band-Elimination (band-stop) Filter


How to find the minimum order to meet the filter specifications ?

The following functions in Matlab can help you to find the minimum order required to meet the filter specifications:

- Buttord for butterworth
- Cheb1ord for chebyshev
- Ellipord for elliptic
- Cheb2ord for inverse chebyshev

Calculating the order and cutoff frequency of a inverse chebyshev filter

• Design a 4MHz Inverse Chebyshev approximation with Ap gain at passband corner. The stop band is 5.75MHz with -50dB gain at stop band.

```
clear all:
Fp = 4e6; Wp = 2*pi*Fp;
Fs=1.4375*Fp; Ws=2*pi*Fs;
Fplot = 20*Fs;
f = 1e6:Fplot/2e3:Fplot;
w = 2*pi*f;
Ap = 1;
As = 50;
% Cheb2ord helps you find the order and wn (n and Wn) that
% you can pass to cheby2 command.
[n, Wn] = cheb2ord(Wp, Ws, Ap, As, 's');
[z, p, k] = cheby2(n, As, Wn, 'low', 's');
[num, den] = cheby2(n, As, Wn, 'low', 's');
```

```
bode(num, den)
```

Bode Plot



References

[1] S. T. Karris, "Signals and Systems with Matlab Computing and Simulink Modeling," Fifth Edition. Orchard Publications

[2] Matlab Help Files