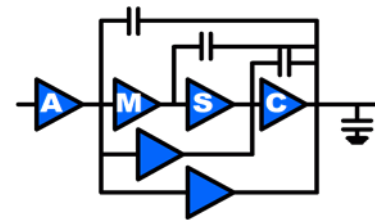


## ACTIVE RC FILTERS



### 1. Basic Building Blocks

- First-Order Filters
- Second-Order Filters, using multiple VCVS
- Second-Order Filter, using one VCVS ( Op Amp)
- State-Variable Biquad


### 2. Non-Ideal Active – RC Filters

- Using VCVS ( Op Amp) vs. VCCS ( transconductance Amp)
- Second-Order Non-idealities
- Fully Differential Versions
- Fully Balanced, Fully Symmetric Balance Circuits

### 3. Introduction to Matlab and Simulink for filter Design and filter approximation techniques
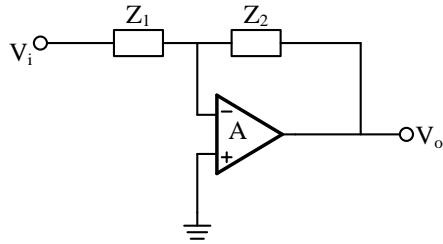
# ACTIVE - RC FILTERS

The basic building block is illustrated below




$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{-Z_2}{1 + \frac{1}{A} \left( 1 + \frac{Z_2}{Z_1} \right)}$$


Let us assume that  $A \rightarrow \infty$ , then

$$H(s) = -\frac{Z_2}{Z_1}$$

Next we consider particular cases

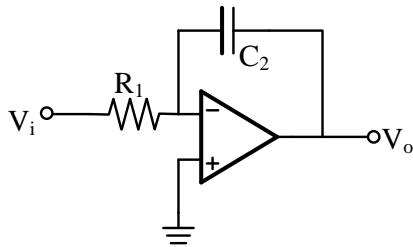
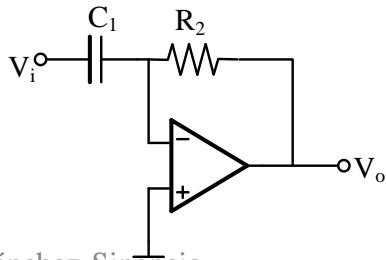
$$H(s) = -\frac{1}{sR_1C_2} \quad \text{Integrator}$$



$$H(s) = -sR_2C_1 \quad \text{Differentiator}$$


$Z_1$   
 or  
 $Z_F = Z_2$   
 Can be:

$$\left\{ \begin{array}{ll}
 \begin{array}{c} \text{---} \text{R} \text{---} \\ | \\ \text{---} \text{C} \text{---} \\ | \\ \text{---} \end{array} & \frac{R}{sC} \\
 \begin{array}{c} \text{---} \text{R} \text{---} \text{C} \text{---} \\ | \\ \text{---} \end{array} & \frac{1 + sRC}{sC} \\
 \begin{array}{c} \text{---} \text{C} \text{---} \\ | \\ \text{---} \text{R} \text{---} \\ | \\ \text{---} \end{array} & \frac{R}{1 + sRC}
 \end{array} \right. \quad (3)$$

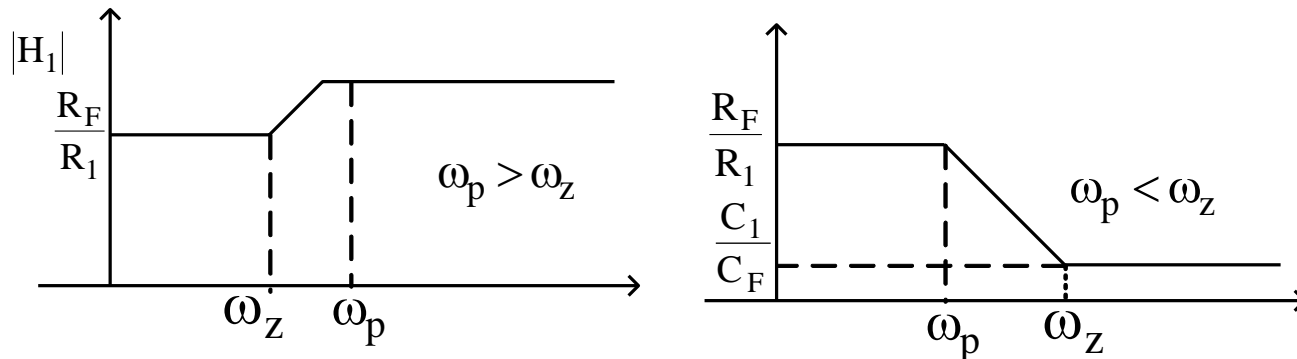EXAMPLE: Let  $Z_1 = \frac{R_1}{1 + sR_1C_1}$ ,  $Z_F = \frac{R_F}{1 + sR_FC_F}$

Assuming ideal op amp A  $\rightarrow \infty$ . Then using (1)

$$H_1 = \frac{V_{O1}}{V_1} = -\frac{R_F/R_1(1 + sR_1C_1)}{(1 + sR_FC_F)} = -\frac{K_n(1 + s/\omega_z)}{(1 + s/\omega_p)} \quad (4)$$



Particular cases are easily derived from (3) and (4)

— Integrator:  $C_1 \rightarrow 0$  ,  $R_F \rightarrow \infty$

$$H_1 \cong -\frac{R_F}{R_1} \frac{1}{sR_FC_F} = -\frac{1}{sC_FR_1}$$

— Differentiator ;  $R_1 \rightarrow \infty$  ,  $C_F \rightarrow 0$

$$H_1 \cong -\frac{R_F}{R_1} sR_1C_1 = -sR_FC_1$$


— Low-Pass:  $C_1 = 0$

$$H_1 = \frac{-\frac{R_F}{R_1}}{1 + sR_FC_F}$$

— High-Pass:  $R_1 \rightarrow \infty$

$$H_1 \cong -\frac{R_F}{R_1} \frac{sR_1C_1}{1 + sR_FC_F}$$


— One pole and one zero

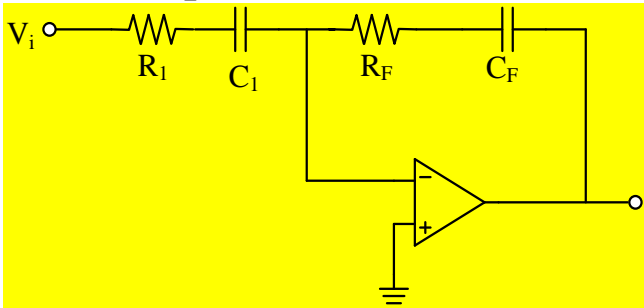

$$\frac{V_o}{V_i} = -\frac{1 + sR_F C_F}{sC_F} \frac{sC_1}{1 + sR_1 C_1} = -\frac{C_1}{C_F} \frac{1 + sR_F C_F}{1 + sR_1 C_1} \quad (5)$$


What are the key differences between Eqs. (4) and (5)?

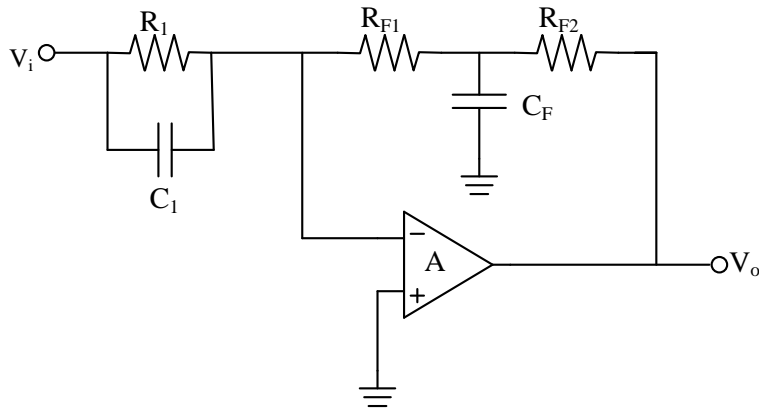Exercise 1. Obtain the transfer function of the following circuit.


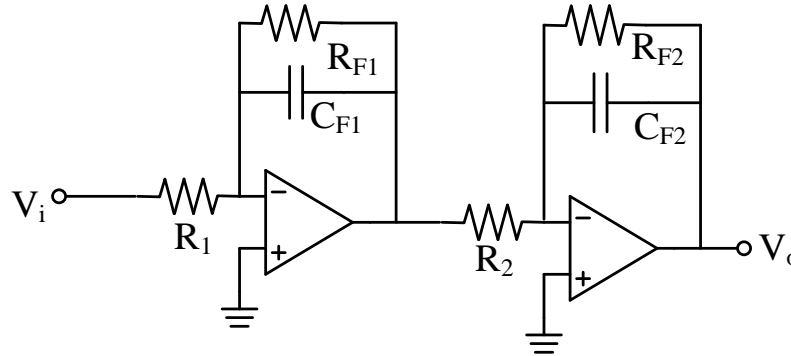
## Second-Order Filters Based on a Two-Integrator Loop.

- We can design a second-order filter by cascading two inverters. i.e.



$$\frac{V_o}{V_i} = \frac{-\frac{R_{F1}}{R_1} \left( -\frac{R_{F2}}{R_2} \right)}{(1 + sC_{F1}R_{F1})(1 + sC_{F2}R_{F2})} = \frac{\frac{R_{F1}}{R_1} \frac{R_{F2}}{R_2}}{s^2 C_{F1}R_{F1}C_{F2}R_{F2} + s(C_{F1}R_{F1} + C_{F2}R_{F2}) + 1} \quad (6)$$

What are the locations of the poles?


$$s_{p1,2} = \frac{-(C_{F1}R_{F1} + C_{F2}R_{F2}) \pm \sqrt{(C_{F1}R_{F1} + C_{F2}R_{F2})^2 - 4C_{F1}R_{F1}C_{F2}R_{F2}}}{2C_{F1}R_{F1}C_{F2}R_{F2}}$$

To have complex poles it requires that

$$(C_{F1}R_{F1})^2 + (C_{F2}R_{F2})^2 - 2C_{F1}R_{F1}C_{F2}R_{F2} < 0?$$

Which it is impossible to satisfy. Therefore, cascading two first-order filter yield a second-order filter with only real poles.

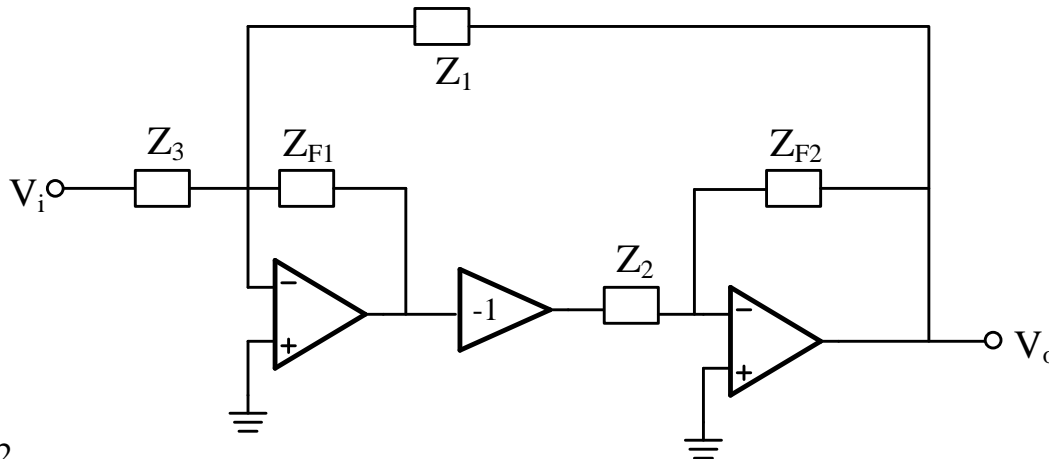The general form of the second order two-integrator loop has the following topology.



$$H = \frac{-\frac{Z_{F1}}{Z_3} \frac{Z_{F2}}{Z_2}}{1 + \frac{Z_{F1}}{Z_1} \frac{Z_{F2}}{Z_2}}$$

(7a)

Note the similarity of Eq. (7a) with (2). Also observe that A “-1” needs to be inserted before or after the second inverter to yield a negative feedback loop.

Let us consider the following filter where

$$Z_3 = R_3, Z_1 = R_1, Z_2 = R_2, Z_{F1} = \frac{1}{sC_{F1}}, Z_{F2} = \frac{R_{F2}}{1 + sC_{F2}R_{F2}}$$


Thus Eq. (7a) yields:

$$H = \frac{-\frac{1}{sC_{F1}R_3} \frac{R_{F2}/R_2}{(1 + sC_{F2}R_{F2})}}{1 + \frac{1}{sC_{F1}R_1} \frac{R_{F2}/R_2}{(1 + sC_{F2}R_{F2})}}$$

$$H = \frac{-\frac{1}{C_{F1}R_3C_{F2}R_2}}{s^2 + \frac{s}{C_{F2}R_{F2}} + \frac{1}{C_{F1}R_1C_{F2}R_2}} = \frac{-\omega_{o1}^2}{s^2 + \frac{\omega_o}{Q}s + \omega_o^2}$$



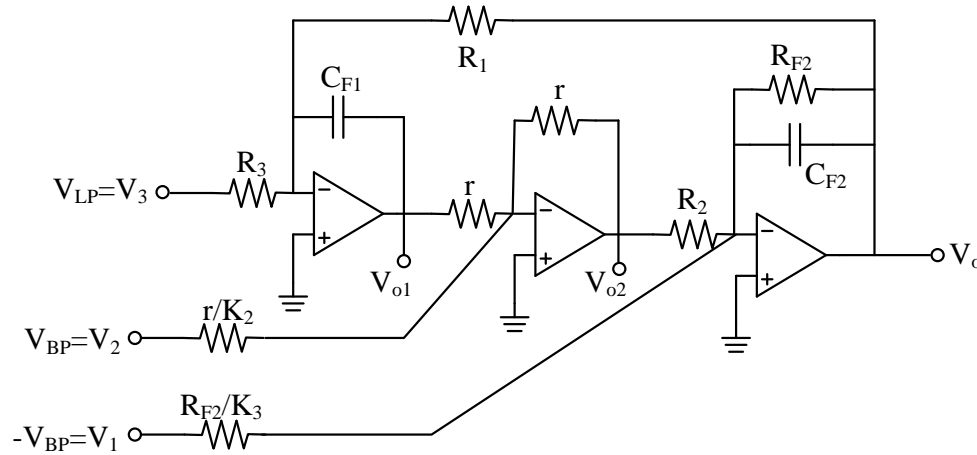By injecting in different current summing nodes a general biquad filter can be obtained.




$$V_o = \frac{V_3 \frac{1}{sC_{F1}R_3} \frac{R_{F2}/R_2}{(1 + sC_{F2}R_{F2})} + \frac{-K_2 \frac{R_{F2}}{R_2}}{(1 + sC_{F2}R_{F2})} - \frac{K_3 \frac{R_{F2}}{R_{F2}} V_1}{(1 + sC_{F2}R_{F2})}}{1 + \frac{1}{sC_{F1}R_1} \frac{R_{F2}/R_2}{(1 + sC_{F2}R_{F2})}}$$

$$V_o = \frac{V_3 \frac{1}{C_{F1}R_3C_{F2}R_2} + V_2sC_{F1}R_1K_2 - V_3sC_1R_1K_3}{s^2 + \frac{s}{C_{F2}R_{F2}} + \frac{1}{C_{F1}R_1C_{F2}R_2}}$$

Exercise 2. Obtain the expressions of  $V_{o1}$  and  $V_{o2}$ .


More general biquad expressions and topologies can be obtained by adding a summer.

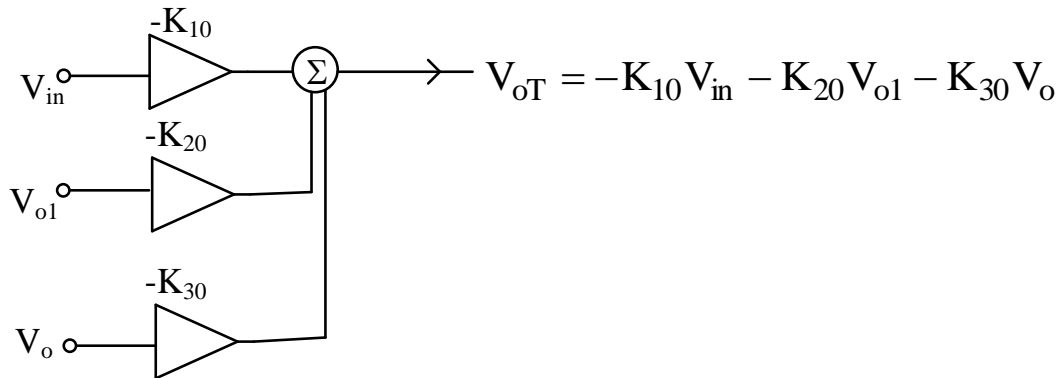

Exercise 3. Draw an active-RC topology of the block diagram show above.

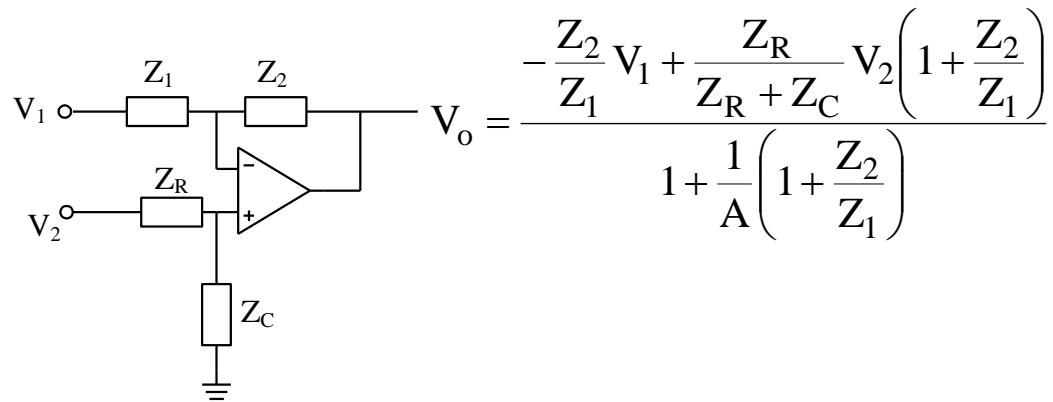Exercise 4 a) For only  $V_1 \neq 0$  obtain  $V_o$  and  $V_{o1}$  when instead of the resistor  $R_{F2}/K_3$  a capacitor  $K_4 C_{F2}$  is used. b) For only  $V_3 \neq 0$  obtain  $V_{o1}$  when the resistor  $R_3$  is replaced by a capacitor  $K_{HP} C_{F1}$ .


By using also the positive input of the op amp other useful filters can be obtained.



Example. Phase shifter  $Z_2=R_2=R_1$ ,  $Z_1=R_1$ ,  $Z_R=R$   $Z_C = \frac{1}{sC}$  and  $A \rightarrow \infty$  with  $V_1 = V_2$

$$\frac{V_o}{V_1} = -1 + \frac{sRC}{1+sRC} \cdot 2 = \frac{-1-sRC+2sRC}{1+sRC} = -\frac{1-sRC}{1+sRC}$$

## Sallen and Key Bandpass Filter

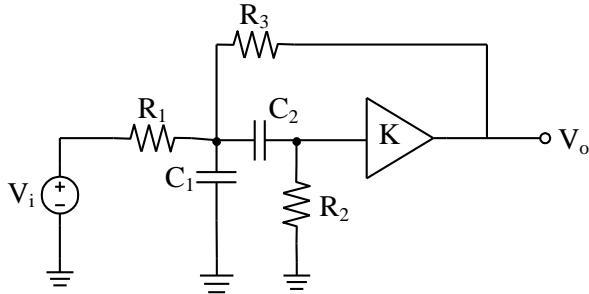

$K$  is a non-inverting amplifier

Using Nodal Analysis

$$V_1 \left( s(C_1 + C_2) + \frac{1}{R_1} + \frac{1}{R_3} \right) - sC_2 V_2 - \frac{V_o}{R_3} = \frac{V_i}{R_1} \quad (1)$$

$$-V_1(sC_2) + V_2 \left( sC_2 + \frac{1}{R_2} \right) = 0 \quad (2)$$

$$V_o = KV_2 \quad (3)$$

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{K \frac{s}{R_1 C_1}}{s^2 + \left[ \frac{1}{R_2 C_2} + \left( 1 - K + \frac{R_3}{R_1} + \frac{R_3}{R_2} \right) \frac{s}{R_3 C_1} + \frac{R_1 + R_3}{R_1 R_3 R_2 C_1 C_2} \right]}$$

A particular case is for  $R_1=R_2=R_3=R$ ,  $C_1=C_2=C$


Then

$$\omega_0^2 = \frac{2}{(RC)^2} \quad ; \quad Q = \frac{\sqrt{2}}{4-K}$$

or for a given  $\omega_0$  and  $Q$


$$RC = \frac{\sqrt{2}}{\omega_0} \quad \text{and} \quad K = 4 - \frac{\sqrt{2}}{Q}$$

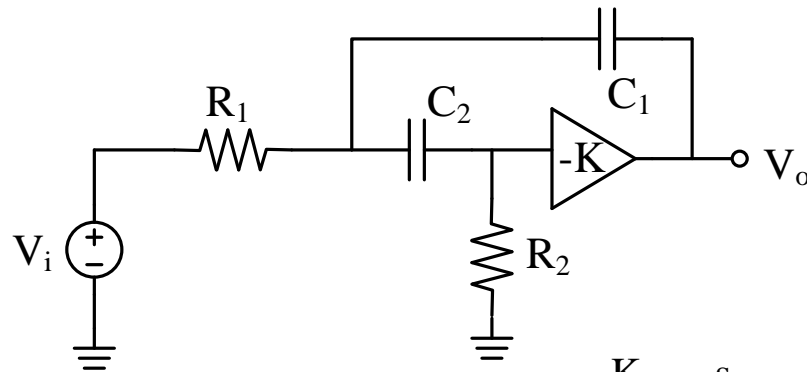Exercise 5. Prove the transfer function is a BP filter of the following circuit



$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{-K \frac{s}{R_1 C_1}}{s^2 + \frac{1}{K+1} \left[ \frac{R_1 + R_2}{R_1 R_2 C_1} + \frac{1}{R_2 C_2} \right] s + \frac{1}{(K+1) R_1 R_2 C_1 C_2}}$$

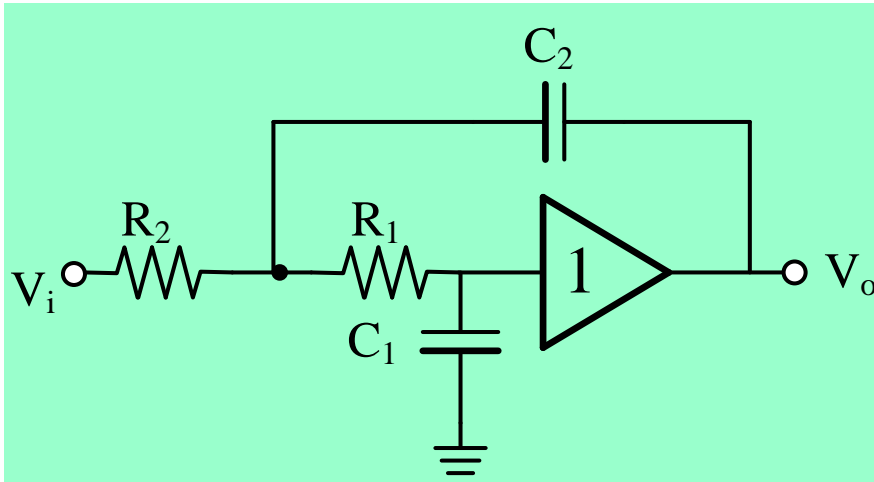In the past before IC fabrication, active filters implementation preferred one op amp structure. One very popular type is the Sallen and Key unity gain implementations.



*LP Sallen - Key*

$$H_{LP}(s) = \frac{\omega_o^2}{s^2 + \frac{\omega_o}{Q}s + \omega_o^2}$$


$$R_1 = R_2 = R$$

$$C_1 = C$$

$$C_2 = 4Q^2C$$

$$RC = 1/2 \omega_o Q$$

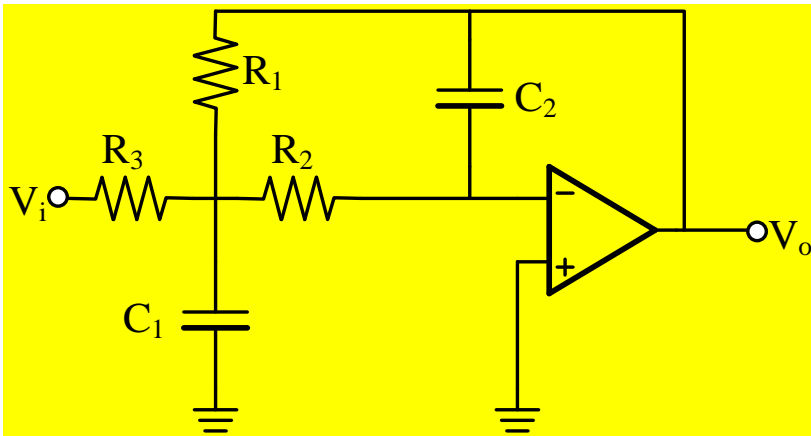
One also popular topology is the Rauch Filter






$$H(s) = \frac{1}{R_2 C_2 R_3 C_1} \frac{1}{s^2 + \frac{s}{C_1} \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) + \frac{1}{R_1 C_1 R_2 C_2}}$$

Another technique for analysis and design based on state-variable uses building blocks.



CIRCUIT

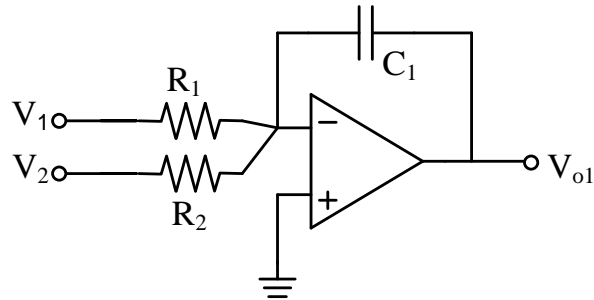

REPRESENTATION

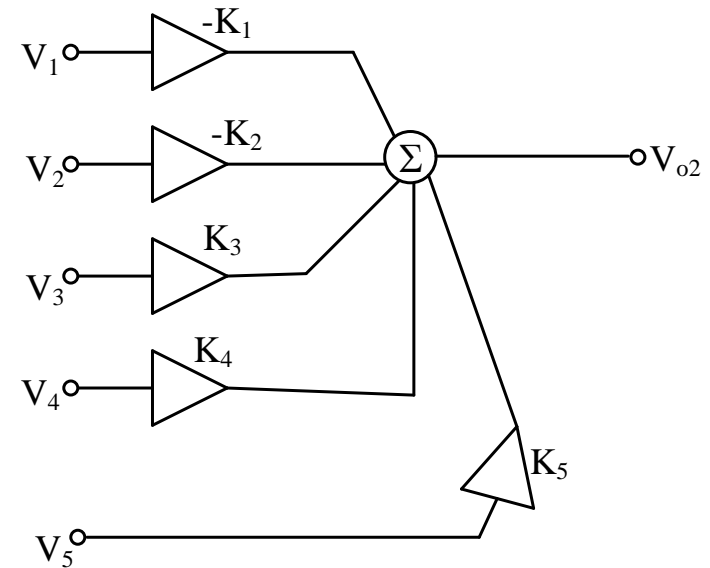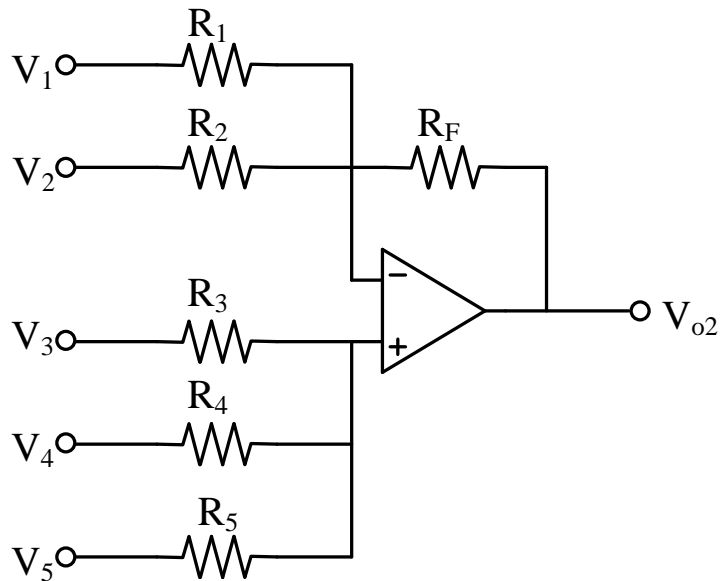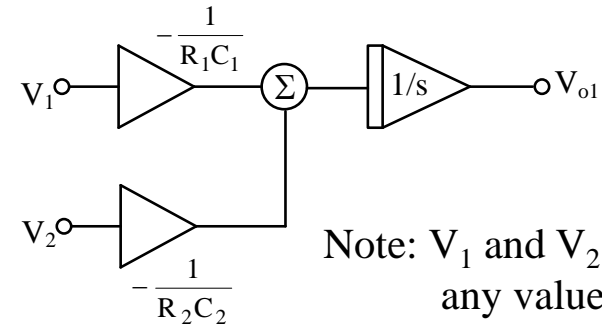

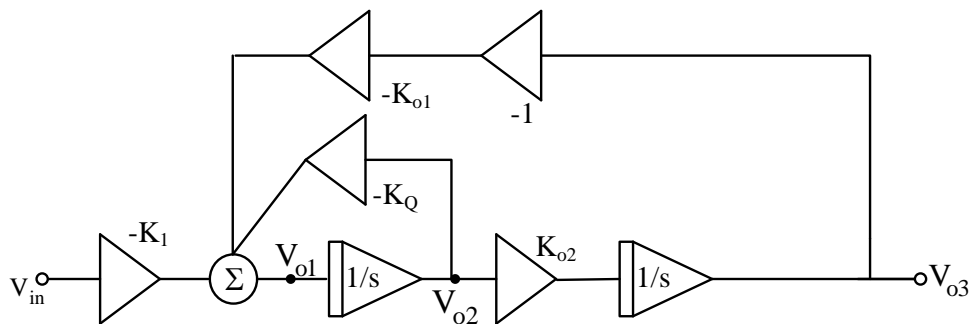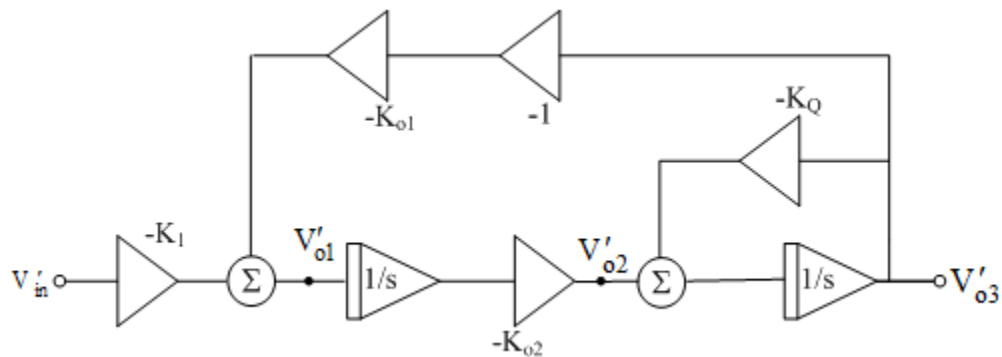Let us apply to a two-integrator loop plus Mason's Rule.




For Second-topology

$$V_{o1} = \frac{-K_1 V_{in}}{1 + \frac{K_Q}{s} + \frac{K_{o1} K_{o2}}{s^2}} = \frac{-K_1 s^2 V_{in}}{s^2 + K_Q s + K_{o1} K_{o2}} \quad \text{HP}$$


$$V_{o2} = \frac{\frac{-K_1}{s} V_{in}}{1 + \frac{K_Q}{s} + \frac{K_{o1} K_{o2}}{s^2}} = \frac{-K_1 s V_{in}}{s^2 + K_Q s + K_{o1} K_{o2}} \quad \text{BP}$$



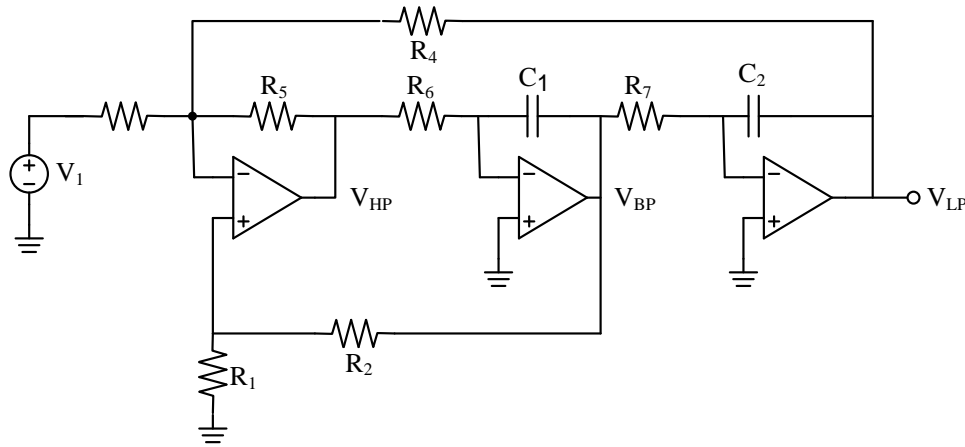
Next we show that we can go from an Active-RC representation into a block diagram or vice versa.



KHN Biquad Filter

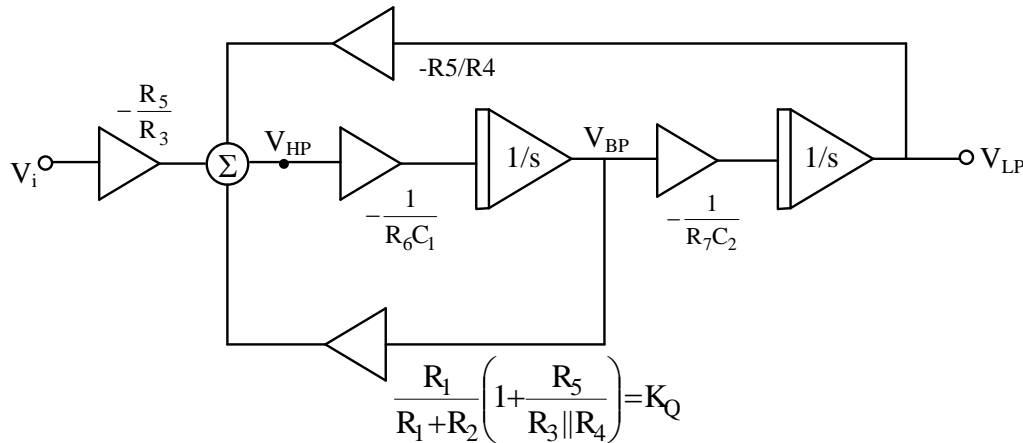
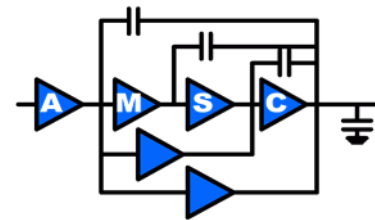
$$\frac{V_{HP}}{V_i} = \frac{-\frac{R_5}{R_3}}{1 + \frac{K_Q}{R_6 C_1} \frac{1}{s} + \frac{R_5/R_4}{R_6 C_1 R_7 C_2 s^2}} = \frac{-\frac{R_5}{R_3} s^2}{s^2 + \frac{K_Q}{R_6 C_1} s + \frac{R_5/R_4}{R_6 C_1 R_7 C_2}}$$



# ACTIVE RC FILTERS

## 1. Basic Building Blocks


- First-Order Filters
- Second-Order Filters, using multiple VCVS
- Second-Order Filter, using one VCVS ( Op Amp)
- State-Variable Biquad

## 2. Non-Ideal Active – RC Filters


- Using VCVS ( Op Amp) vs. VCCS ( transconductance Amp)
- Second-Order Non-idealities
- Fully Differential Versions
- Fully Balanced, Fully Symmetric Balance Circuits

## 3. Introduction to Matlab and Simulink for filter Design and filter approximation techniques
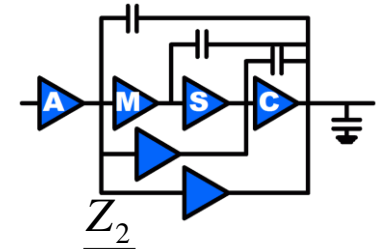
# ELEN 622 (ESS) Non-Ideal Active-RC Integrators



## Op Amp Non-Idealities

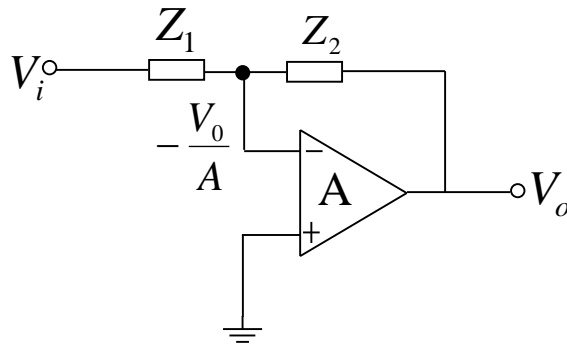

$$H(s) = \frac{-\frac{Z_2}{Z_1}}{1 + \frac{1}{A} \left( 1 + \frac{Z_2}{Z_1} \right)} = -A\beta \frac{Z_2}{Z_1 + Z_2}$$

where

$$\beta = \frac{Z_1}{Z_1 + Z_2}$$

## Integrator

Case 1  $Z_1 = R_1 ; Z_2 = \frac{1}{sC_2} ; \frac{GB}{s} = A(s)$

$$H(s) \cong \frac{-1}{\frac{sRC}{GB} \left( s + \frac{1}{RC} + GB \right)} \cong -\frac{1}{sRC(1 + s/GB)} ; GBRC \gg 1$$

$$H(j\omega) = \frac{-1}{-\omega^2 RC + j\omega RC} ; \quad \phi = \angle H(j\omega) = -\frac{\pi}{2} - \tan^{-1}(\omega/GB)$$

$$\phi = -90^\circ + \Delta\phi$$

$$\Delta\phi \cong -\tan^{-1} \frac{\omega}{GB} \cong -\tan^{-1} \frac{1}{|A(j\omega)|} \quad ; \quad \text{i.e.} \frac{\omega_o}{GB} = \frac{1}{10}$$

$$\Delta\phi \cong -5.7^\circ$$

$$|H(j\omega_o)| = \frac{1}{\left| \frac{-\omega_o}{GB} + \frac{j\omega_o}{\omega_o} \right|} = \frac{1}{\sqrt{1 + \frac{\omega_o^2}{GB^2}}} = 1 + \Delta_M$$

$$\Delta_M = \frac{1 - \sqrt{1 + \frac{\omega_o^2}{GB^2}}}{\sqrt{1 + \frac{\omega_o^2}{GB^2}}} \quad \text{i.e.} \quad \frac{\omega_o}{GB} = 0.1$$


$$\Delta_M \sim 5\% \text{ error}$$

It follows that the ideal -6 dB/octave roll-off expected from an ideal integrator changes to -12 dB/octave at the frequency of the parasitic pole given by

$$s_p = -\left(\omega_t + \frac{1}{CR}\right)$$

which may be approximated by,
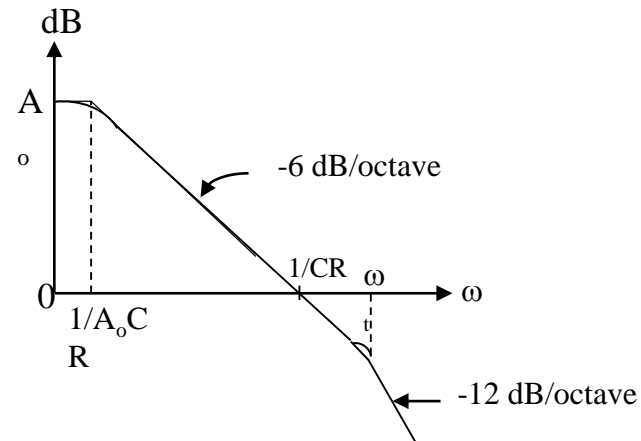
$$s = -\omega_t \quad \text{for} \quad \omega_t \gg \frac{1}{CR}$$



$$Q_L = -\left(\frac{\omega_t}{\omega}\right) = -\left(\frac{GB}{\omega}\right)$$

In general


$$T(j\omega) = \frac{1}{R(\omega) + jX(\omega)}$$

then we define the integrator Q-factor by

$$Q_I = \frac{X(\omega)}{R(\omega)}$$
$$Q_I = -\left(\frac{\omega_t}{\omega}\right) = -|A(j\omega)|$$


Making an analogy of  $Q_L$  of an inductor

$$Q_L = \frac{\omega_o L}{R_L}$$

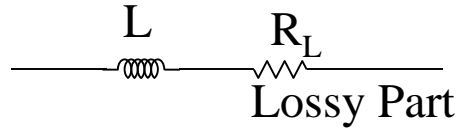

For an integrator one can obtain

$$Q_I = \frac{\omega RC}{-\omega^2 RC} = -\frac{1}{\omega} = \frac{-1}{\omega} GB = -|A(j\omega)|$$

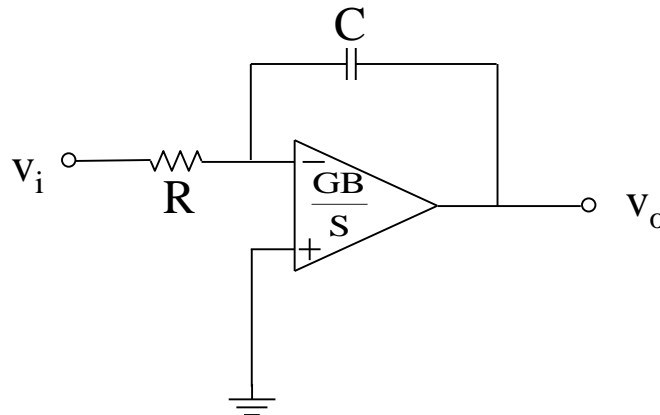


Miller Integrator



How can we compensate this degradation of performance?

a)

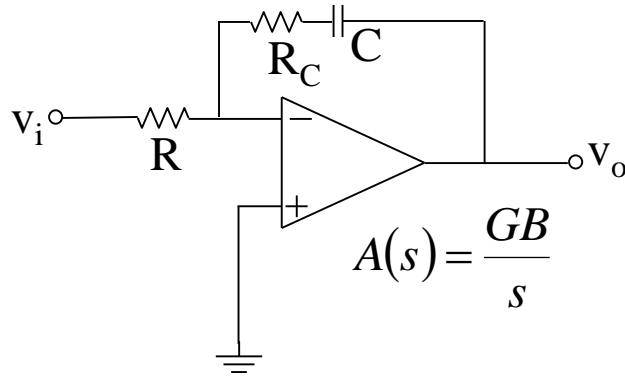


If we make

$$R_C = \frac{1}{GB \cdot C}$$

Ideally we obtain

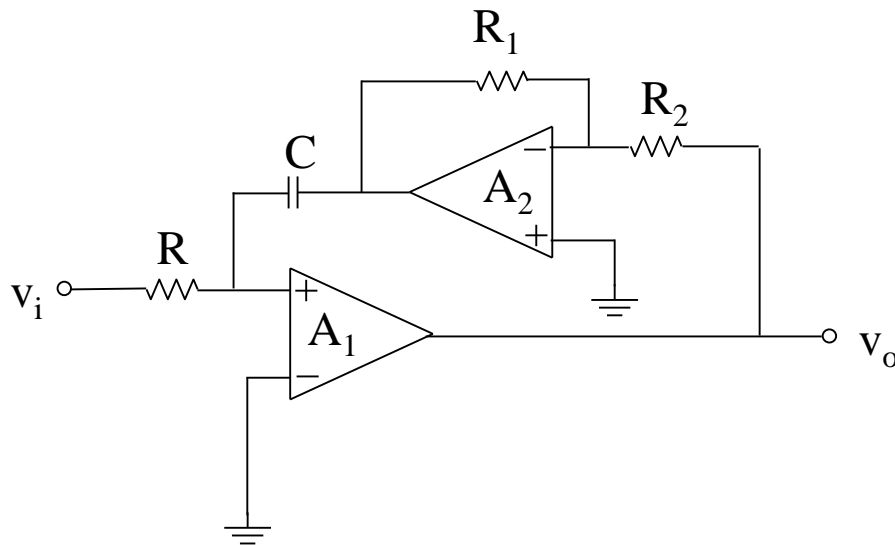
$$\frac{V_o(s)}{V_i(s)} = -\frac{1}{RC}$$



This integrator yields a positive

$$Q_I = +|A(j\omega)|$$
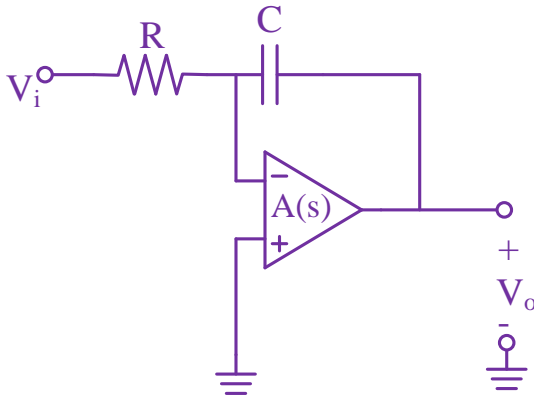
## ACTIVE – RC INTEGRATOR: Pole Shift and Predistortion



$$\frac{V_o}{V_i} = \frac{-\frac{1}{sRC}}{1 + \frac{1}{A(s)}\left(1 + \frac{1}{sRC}\right)} \Bigg|_{A(s) \rightarrow \infty} = -\frac{1}{sRC} \quad (1a)$$

$$\frac{V_o}{V_i} = \frac{-1}{sRC + \frac{1}{A(s)}(sRC + 1)} \quad (1b)$$

Let  $A(s) = \frac{A_o \omega_{3dB}}{s + \omega_{3dB}}$  ; where  $A_o$  is the DC gain and  $\omega_{3dB}$  the dominant pole in open loop.

Then (1b) becomes

$$\frac{V_o}{V_i} = \frac{-\frac{A_o \omega_{3dB}}{RC}}{s^2 + s\left(A_o \omega_{3dB} + \omega_{3dB} + \frac{1}{RC}\right) + \frac{\omega_{3dB}}{RC}} \cong \frac{-\frac{A_o \omega_{3dB}}{RC}}{s^2 + sA_o \omega_{3dB} + \frac{\omega_{3dB}}{RC}} \quad (2)$$

Let  $GB = A_o \omega_{3dB}$

G. Daryanani, "Principles of Active Network Synthesis and Design," John Wiley and Sons, 1976.

The roots of the denominator are

$$P_{1,2} = -\frac{GB}{2} \pm \frac{GB}{2} \left[ 1 - \frac{4\omega_{3dB}}{(GB)^2 RC} \right]^{1/2} \quad (3a)$$

Using the approximation  $(1-X)^{1/2} \cong 1 - X/2$  for  $X \ll 1$ , then


$$P_{1,2} = -\frac{GB}{2} \pm \frac{GB}{2} \left[ 1 - \frac{2\omega_{3dB}}{(GB)^2 RC} \right] \quad (3b)$$

Thus the roots yield

$$P_1 = -\frac{1}{A_o RC}$$


$$P_2 = -GB + \frac{1}{A_o RC} \cong -GB$$

## The Bode Plot Looks Like

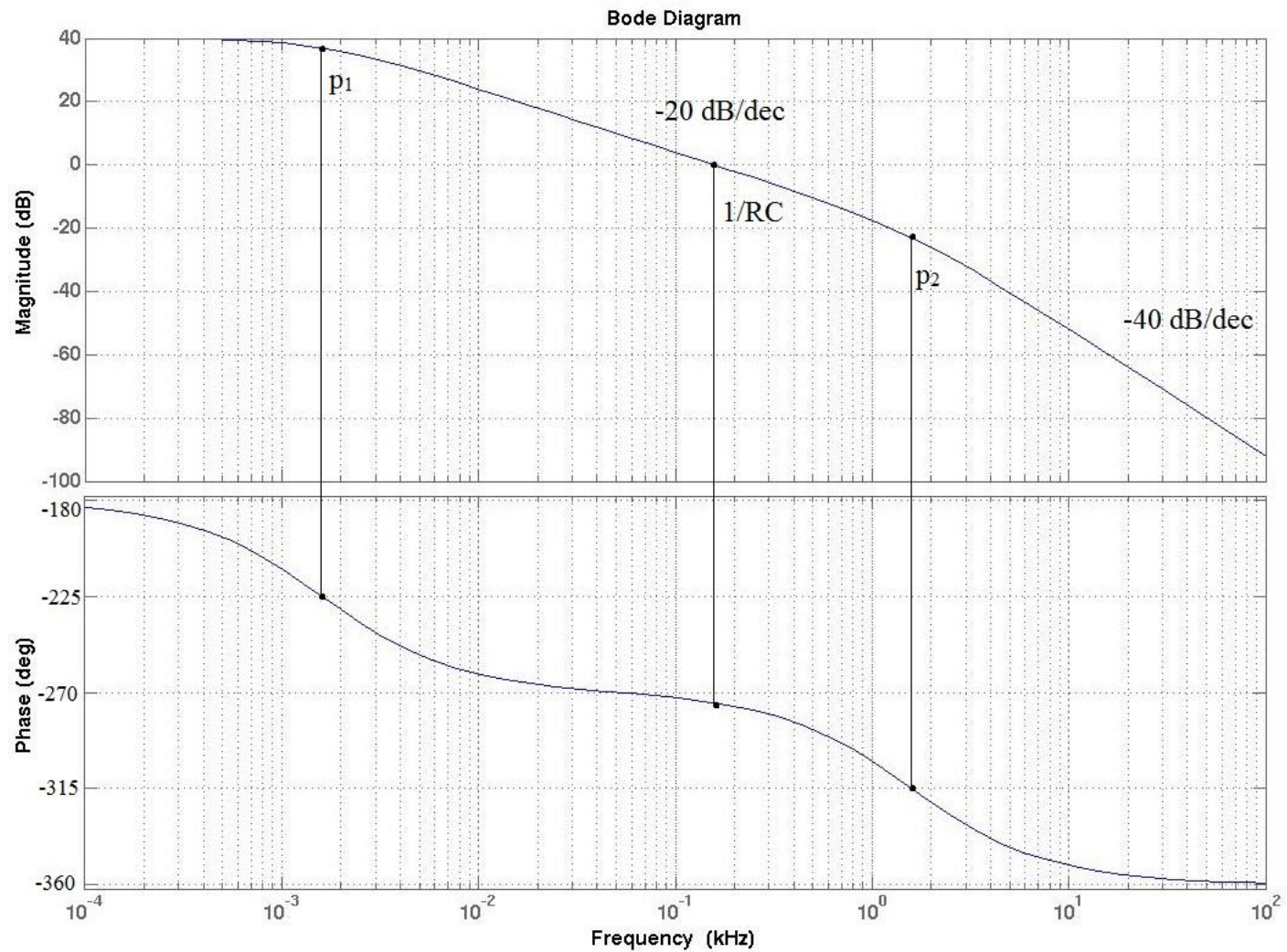
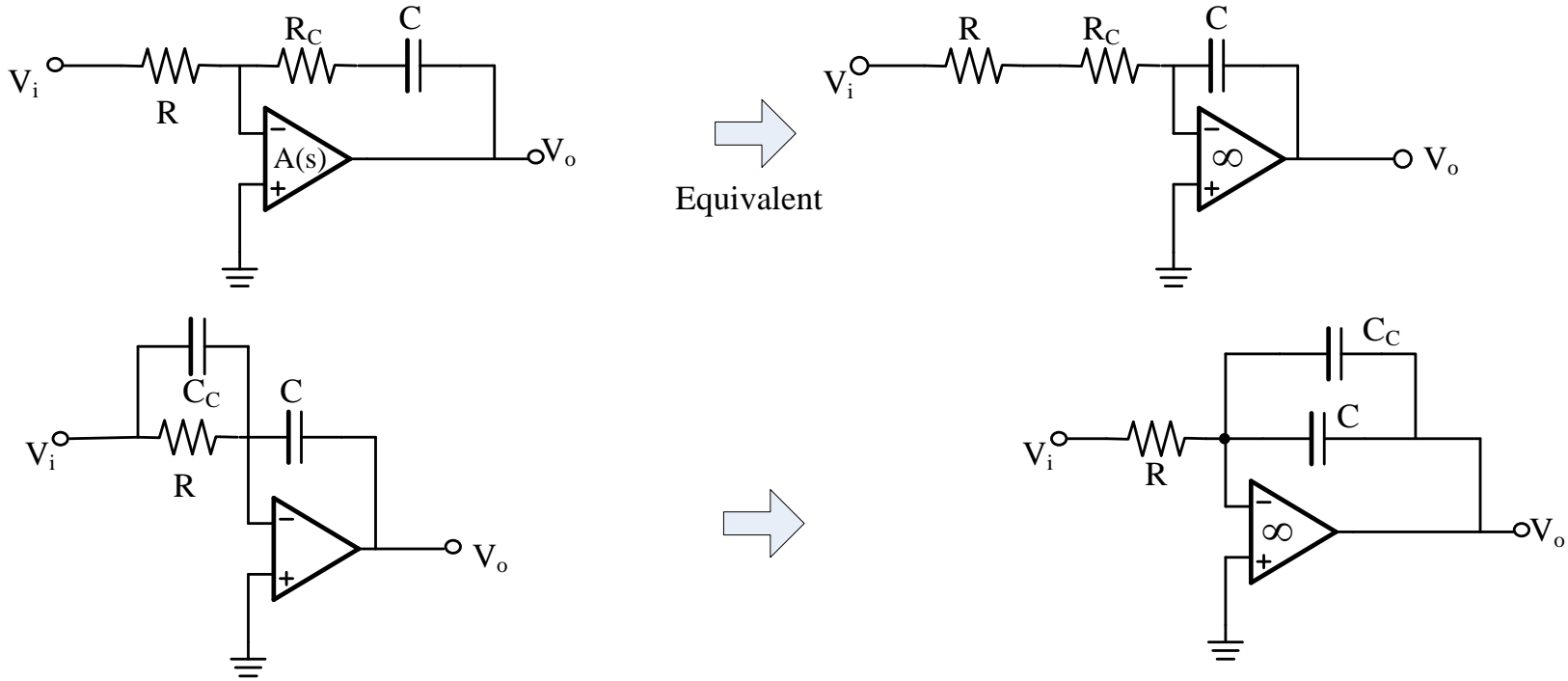
## PREDISTORTION; FREQUENCY COMPENSATION


In order to relax the bandwidth op amp requirement one can use a  $R_C$  or  $C_C$  on the Miller Integrator. That is



$$\text{Use } R_C C = \frac{1}{GB} \text{ or } C_C R \cong \frac{1}{GB}$$
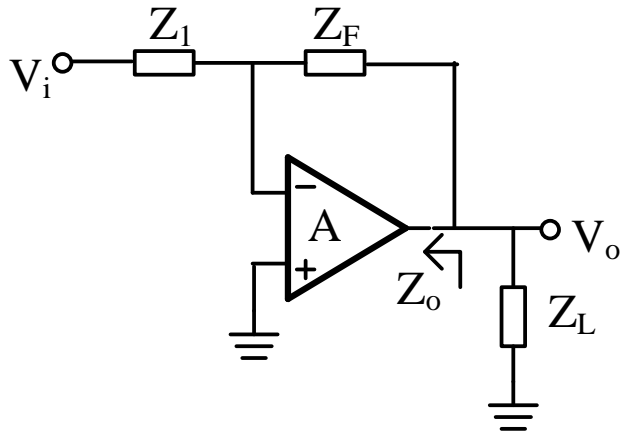
# Using VCVS vs. VCIS in Active-RC Filters

- The motivation is to use OTA (VCIS) instead of more power hungry Op Amp (VCVS)




For  $R_o = Z_o = 0$

$$\frac{V_o}{V_i} = \frac{-\frac{Z_F}{Z_1}}{1 + \frac{1}{A} \left( 1 + \frac{Z_F}{Z_1} \right)}$$

If  $A \rightarrow \infty$ , then


$$\frac{V_o}{V_i} = -\frac{Z_F}{Z_1}$$

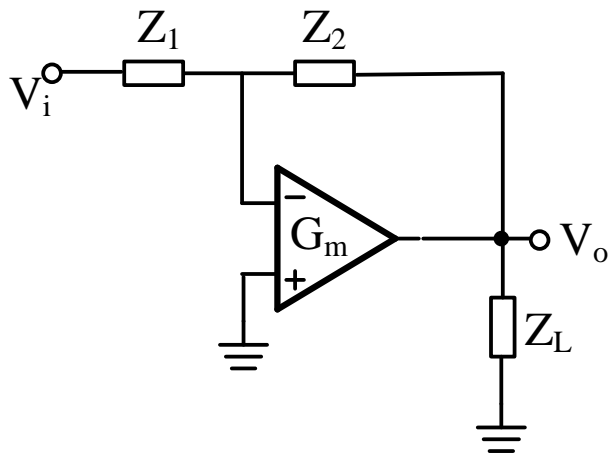

$$\frac{V_o}{V_i} = -\frac{Z_2}{Z_1} \frac{1 - \frac{1}{g_m Z_2}}{\frac{1}{Z_1} + \frac{Z_1 + Z_2}{Z_1 Z_L}} \frac{1}{1 + \frac{g_m}{Z_1 Z_L}}$$

$$\left. \begin{array}{l} g_m \gg \frac{1}{Z_2} \\ g_m \gg \frac{1}{Z_1} + \frac{Z_1 + Z_2}{Z_1 Z_L} \end{array} \right\} \frac{V_o}{V_i} = -\frac{Z_2}{Z_1}$$

# Using VCVS

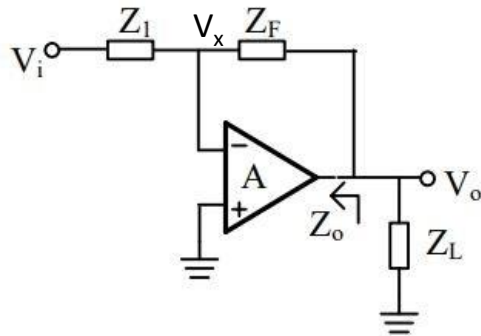


$$\frac{V_i - V_x}{Z_1} + \frac{V_o - V_x}{Z_F} = 0$$

$$V_o = -AV_x$$

$$V_x = V_i \frac{Z_F}{Z_1 + Z_F} + V_o \underbrace{\frac{Z_1}{Z_1 + Z_F}}_{\beta}$$

Signal flow graph:

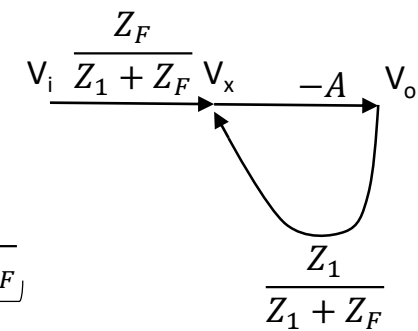


Using Mason's rule:

$$\frac{V_o}{V_i} = \frac{-A \frac{Z_F}{Z_1 + Z_F}}{1 + A \frac{Z_1}{Z_1 + Z_F}} = \frac{-Z_F/Z_1}{1 + \frac{1}{A} \left(1 + \frac{Z_F}{Z_1}\right)}$$

Thus as  $A \rightarrow \infty$  the gain becomes  $-Z_F/Z_1$

# Using VCCS

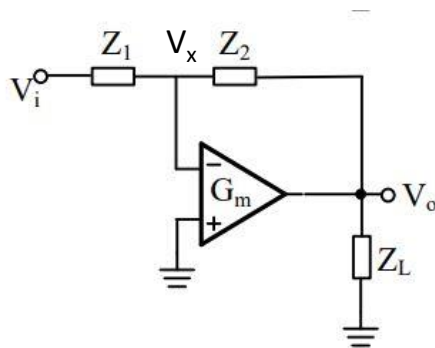


$$\frac{V_i - V_x}{Z_1} + \frac{V_o - V_x}{Z_2} = 0$$

$$\frac{V_o - V_x}{Z_2} + \frac{V_o}{Z_L} = -G_m V_x$$

$$V_x = V_i \frac{Z_2}{Z_1 + Z_2} + V_o \underbrace{\frac{Z_1}{Z_1 + Z_2}}_{\beta}$$

$$V_o = \frac{1 - G_m Z_2}{1 + Z_2/Z_L} V_x$$

Signal flow graph:

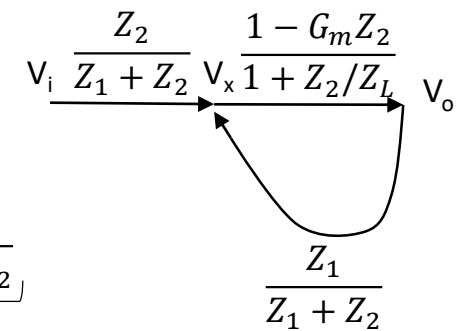


Using Mason's rule:

$$\frac{V_o}{V_i} = \frac{\frac{Z_2}{Z_1 + Z_2} \frac{1 - G_m Z_2}{1 + Z_2/Z_L}}{1 - \frac{1 - G_m Z_2}{1 + Z_2/Z_L} \frac{Z_1}{Z_1 + Z_2}} = \frac{-Z_2/Z_1}{1 + \frac{1}{G_m Z_2 - 1} \left(1 + \frac{Z_2}{Z_1}\right) \left(1 + \frac{Z_2}{Z_L}\right)}$$


What conditions do we need to impose on  $G_m$  for proper operation?



# Using VCCS: Acceptable $G_m$ Range

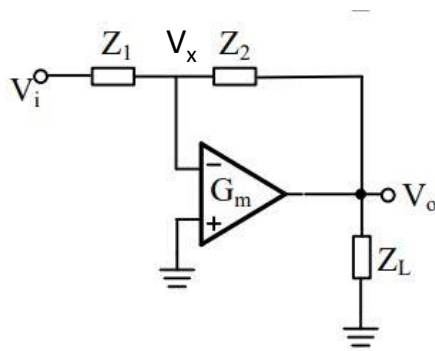

Signal flow graph:

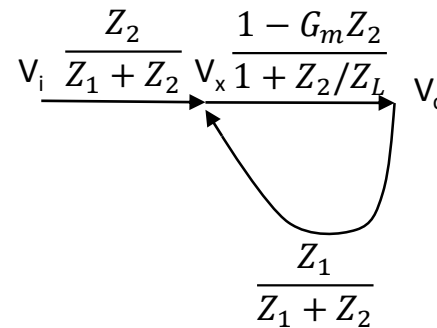

$$\frac{V_o}{V_i} = \frac{-Z_2/Z_1}{1 + \frac{1}{G_m Z_2 - 1} \left(1 + \frac{Z_2}{Z_1}\right) \left(1 + \frac{Z_2}{Z_L}\right)}$$


Note from the signal flow graph that having a negative feedback loop requires  $G_m Z_2 > 1$

For the gain to approach the ideal gain of  $-Z_2/Z_1$ , we need

$$G_m Z_2 - 1 \gg \left(1 + \frac{Z_2}{Z_1}\right) \left(1 + \frac{Z_2}{Z_L}\right) \Rightarrow G_m Z_2 \gg 1 + \left(1 + \frac{Z_2}{Z_1}\right) \left(1 + \frac{Z_2}{Z_L}\right)$$

Thus, guaranteeing this second condition automatically guarantees the negative feedback condition

# Using VCCS: Practical Considerations

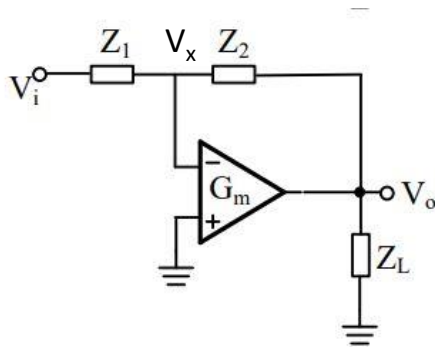

$$G_m Z_2 \gg 1 + \left(1 + \frac{Z_2}{Z_1}\right) \left(1 + \frac{Z_2}{Z_L}\right)$$

In practice,  $Z_L = R_o \parallel Z_{Load}$  where  $R_o$  is the OTA's output resistance and  $Z_{Load}$  is the external load impedance

One should note that  $G_m$  and  $R_o$  are not independent since increasing current to increase  $G_m$  will reduce  $R_o$ . To a first order, one can consider  $A = G_m R_o$  to be constant.

Finally, in cascaded filter designs, the load of one stage is the input resistor of the next one. We can thus assume  $Z_{Load} = Z_1$  as a realistic condition ( $Z_{Load} = \infty$  places a looser constraint on  $G_m$ )



Substituting for  $Z_L$  as described above yields the following constraint on  $G_m$ :

$$G_m \gg \frac{1}{Z_1} \frac{2(1 + Z_1/Z_2) + Z_2/Z_1}{1 - \frac{1}{A}(1 + Z_2/Z_1)}$$



# Numerical Example

- Ideal VCVS and VCCS components from Cadence were used to simulate the above circuits.
- Two configurations were tested:
  1. Unity gain inverting amplifier ( $Z_2 = Z_1 = R$ )
  2. Lossy integrator with corner frequency 1 MHz ( $Z_2 = R||C$ )
- To have a fair comparison, the value of  $A$  was fixed to 30 for both the VCVS and VCCS implementations (thus the VCCS had  $R_o = 30/G_m$ ). This is a typical value for the voltage gain of a single stage amplifier.
- In all tests,  $R = 100k\Omega$ , the output resistance of the VCVS is set to  $1k\Omega$  and a load capacitance is added to the output of the amplifier to give an output pole at 10 MHz.
- With these numbers, the constraint on  $G_m$  is  $G_m \gg 54 \mu S$
- The value of  $G_m$  was swept from  $30 \mu S$  to  $600 \mu S$  and the simulation results are shown in the following slides.
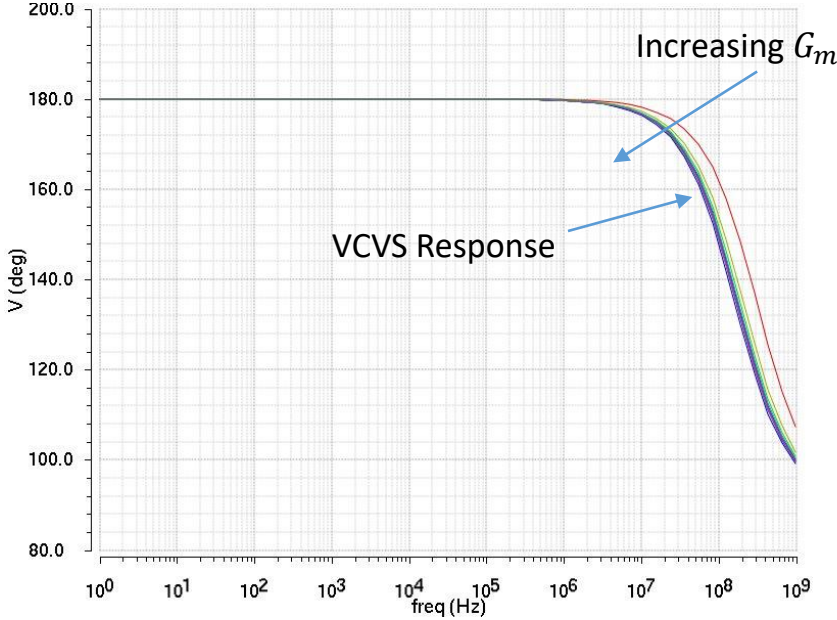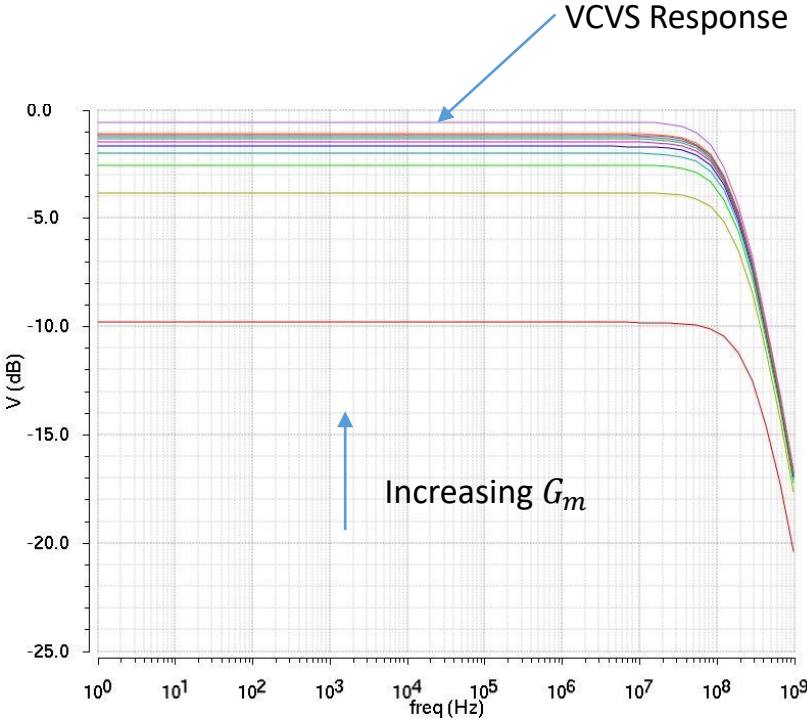
# Simulation Results: Inverting Amplifier



# Simulation Results: Lossy Integrator

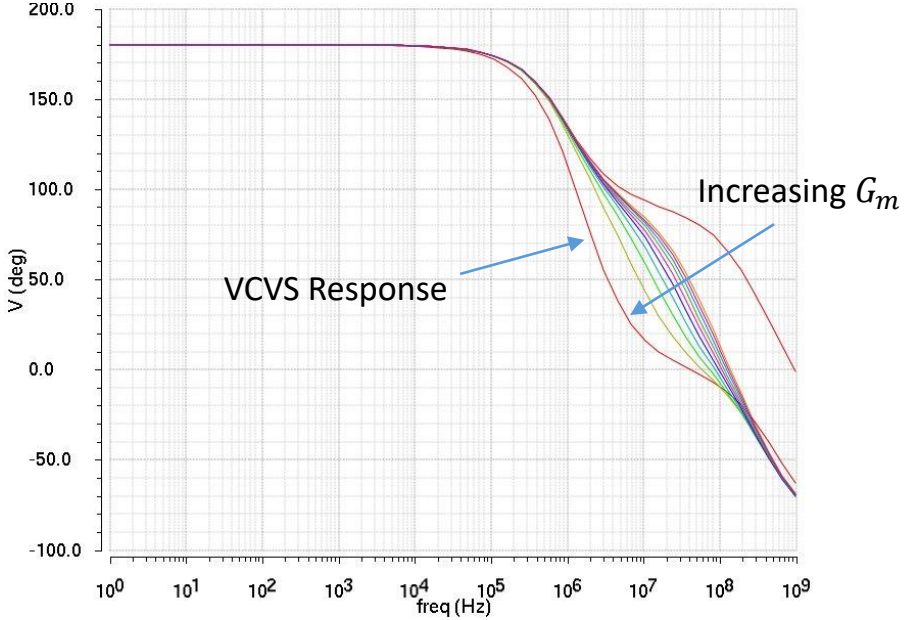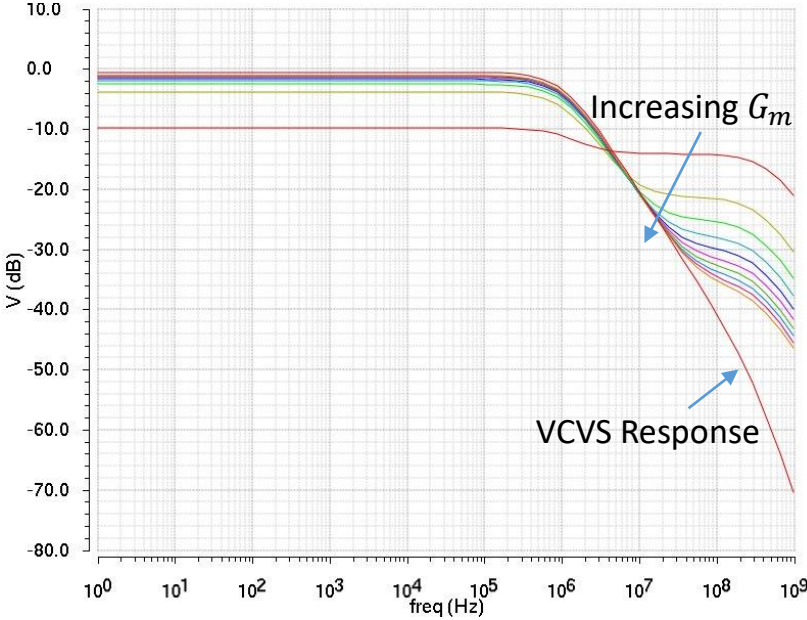

# Conclusions

- It is possible to use VCCS (OTA) instead of VCVS (Opamp) in active-RC filters in order to avoid using costly buffer stages.
- Proper performance requirements place a lower limit on the transconductance of the OTA used.
- Using a transconductance of 10-15x the minimum requirement yields a comparable performance to a design employing an Opamp implementation.

It can be shown that for equal  $A(s) = \frac{GB}{s}$ , the Tow-Thomas filter has the following deviations


$$Q_a = Q_o \frac{1}{1 - 4Q_o\omega_o/GB}$$

or


$$\frac{4Q_o\omega_o}{GB} < 1; \quad 4Q_o\omega_o < GB$$

and
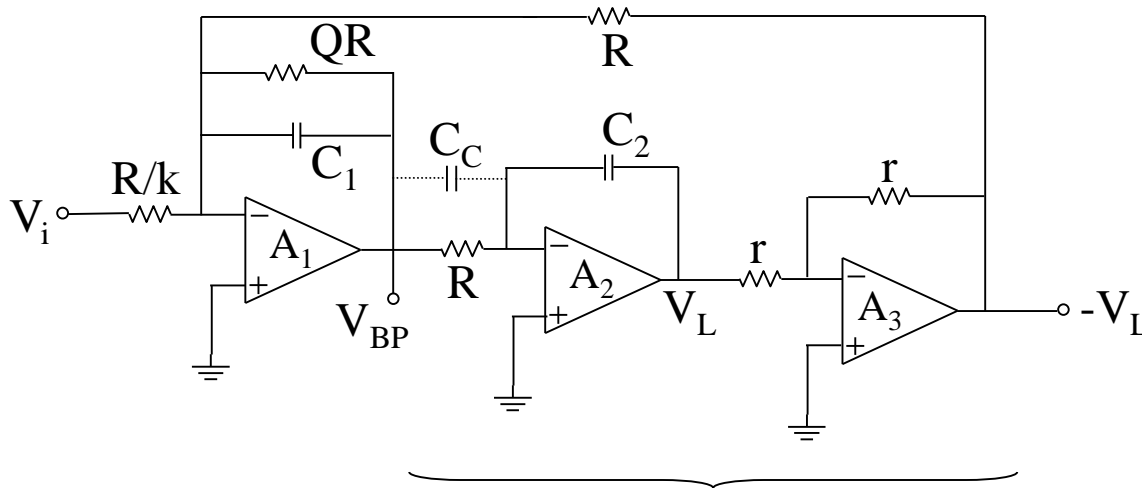
$$\frac{\Delta\omega_o}{\omega_o} \cong -\frac{2+k}{2} \frac{\omega_o}{GB}$$



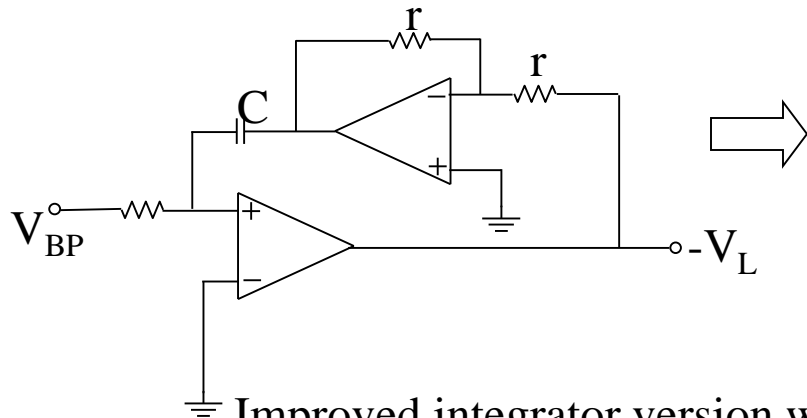
Improved version by replacing noninverting integrator:



$$Q_a = Q_o \frac{1 - \frac{1}{2}(2+k)\omega_o/GB}{1 + \frac{\omega_o}{GB} + \frac{kQ_o\omega_o^2}{GB^2}}$$





Improved integrator version with positive  $Q_I$
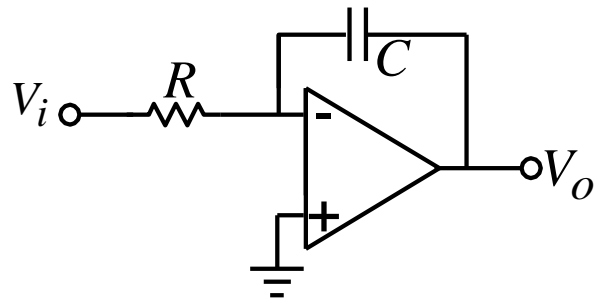
# How to generate Fully-Differential Filters based on Single-Ended Version?



$$\frac{V_o}{V_i} = -\frac{1}{CRs}$$



Single Ended

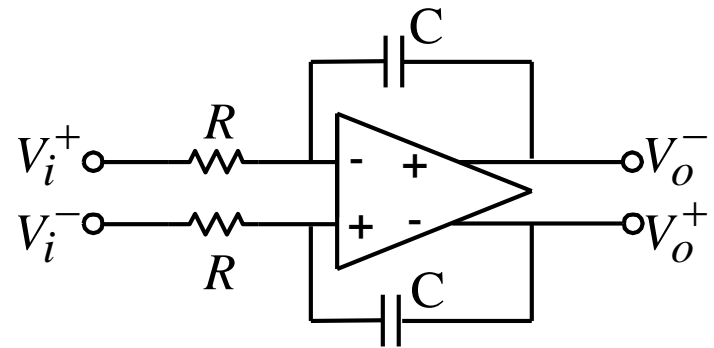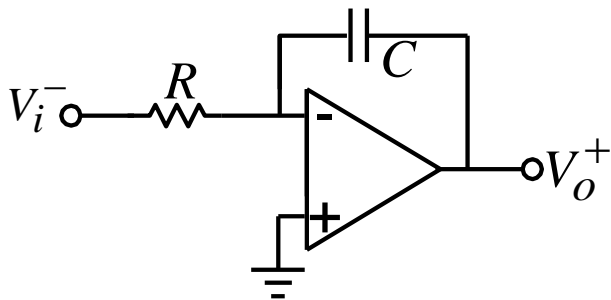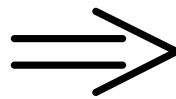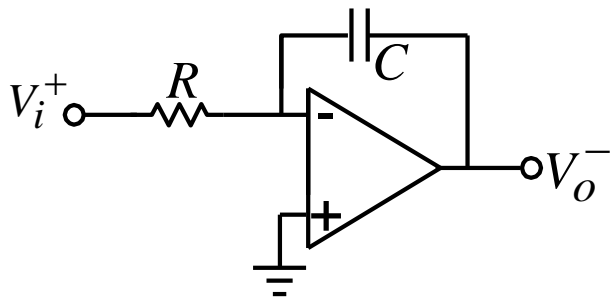


Fully-Differential Version


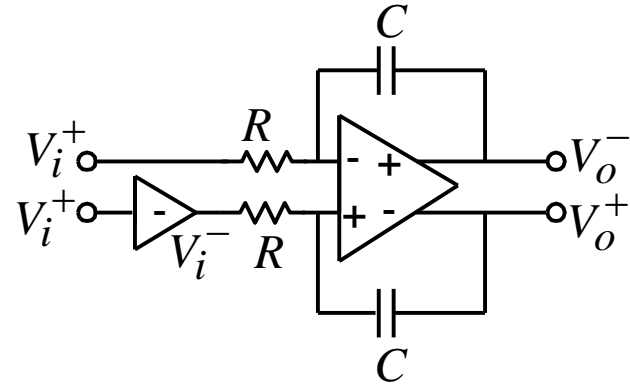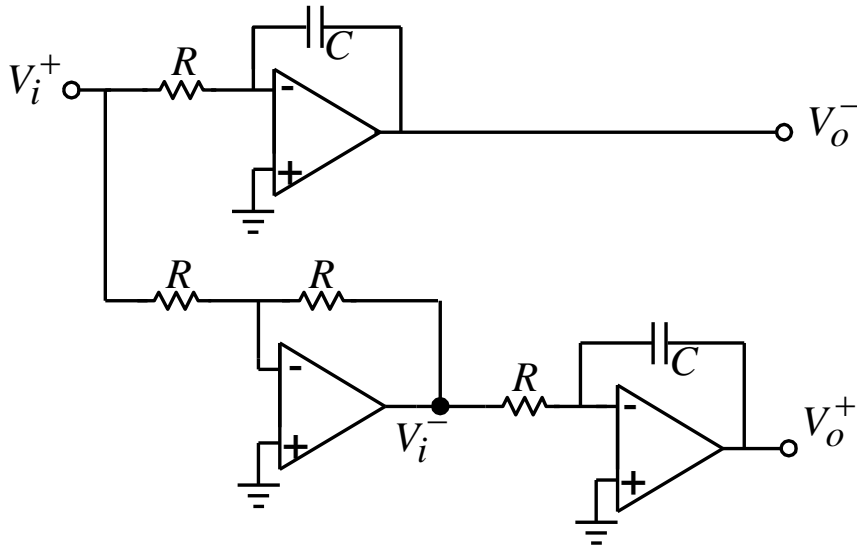
# Particular Case. Assume no $V_i^-$ is Available.




## State -Variable Filter

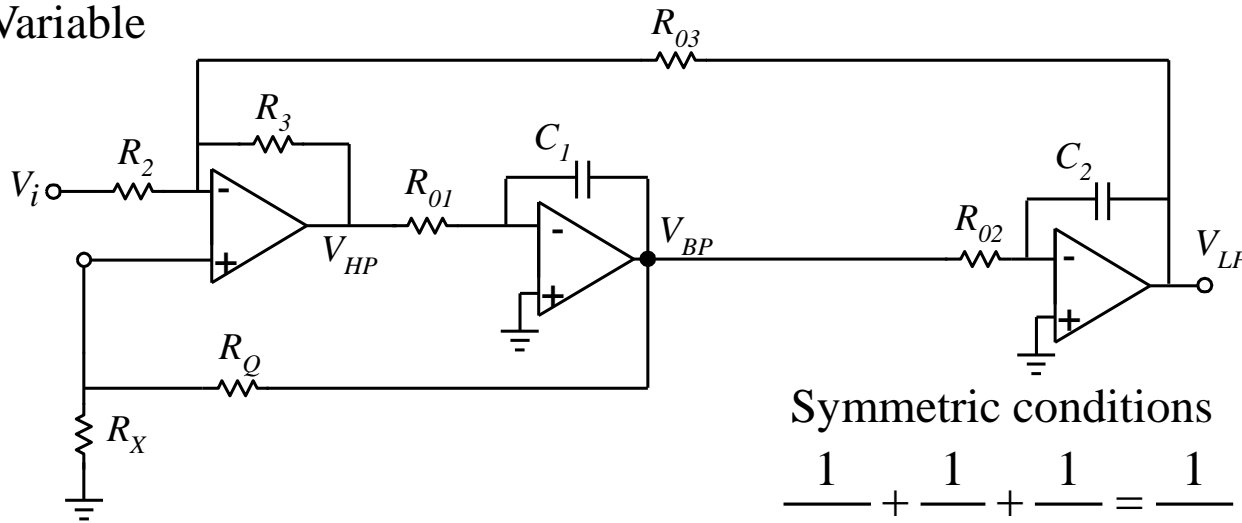

Symmetric conditions

$$\frac{1}{R_{03}} + \frac{1}{R_3} + \frac{1}{R_2} = \frac{1}{R_Q} + \frac{1}{R_X}$$

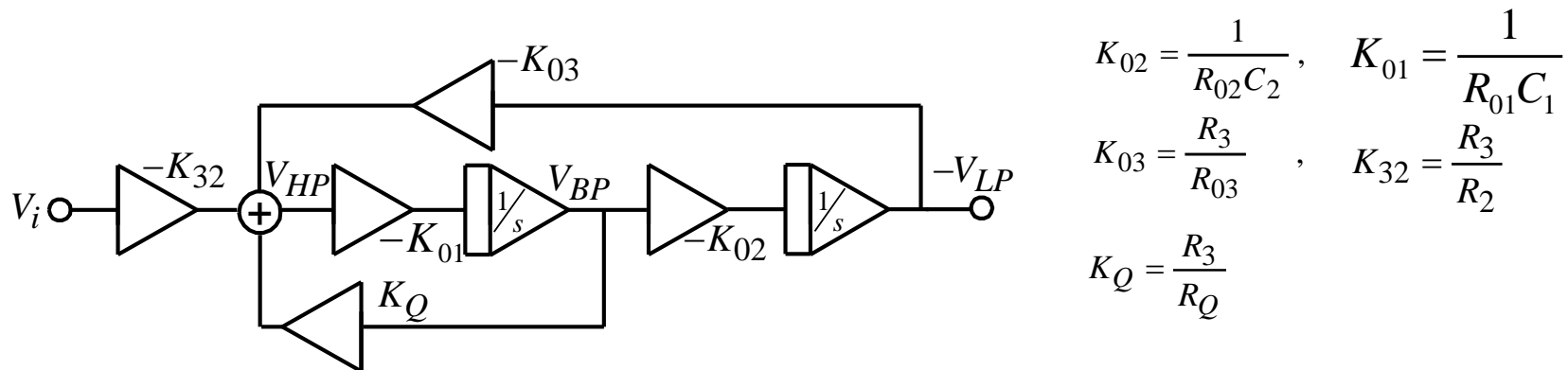Read fully balanced - fully symmetric circuits from 607.




## KHN State Variable Two-Integrator Filter

Use Mason's Rule:


$$\frac{V_{LP}}{V_i} = \frac{-K_{32} K_{01} K_{02} / s^2}{1 + \frac{K_{01} K_Q}{s} + \frac{K_{01} K_{02} K_{03}}{s^2}} = \frac{-K_{32} K_{01} K_{02}}{s^2 + K_{01} K_Q s + K_{01} K_{02} K_{03}}$$

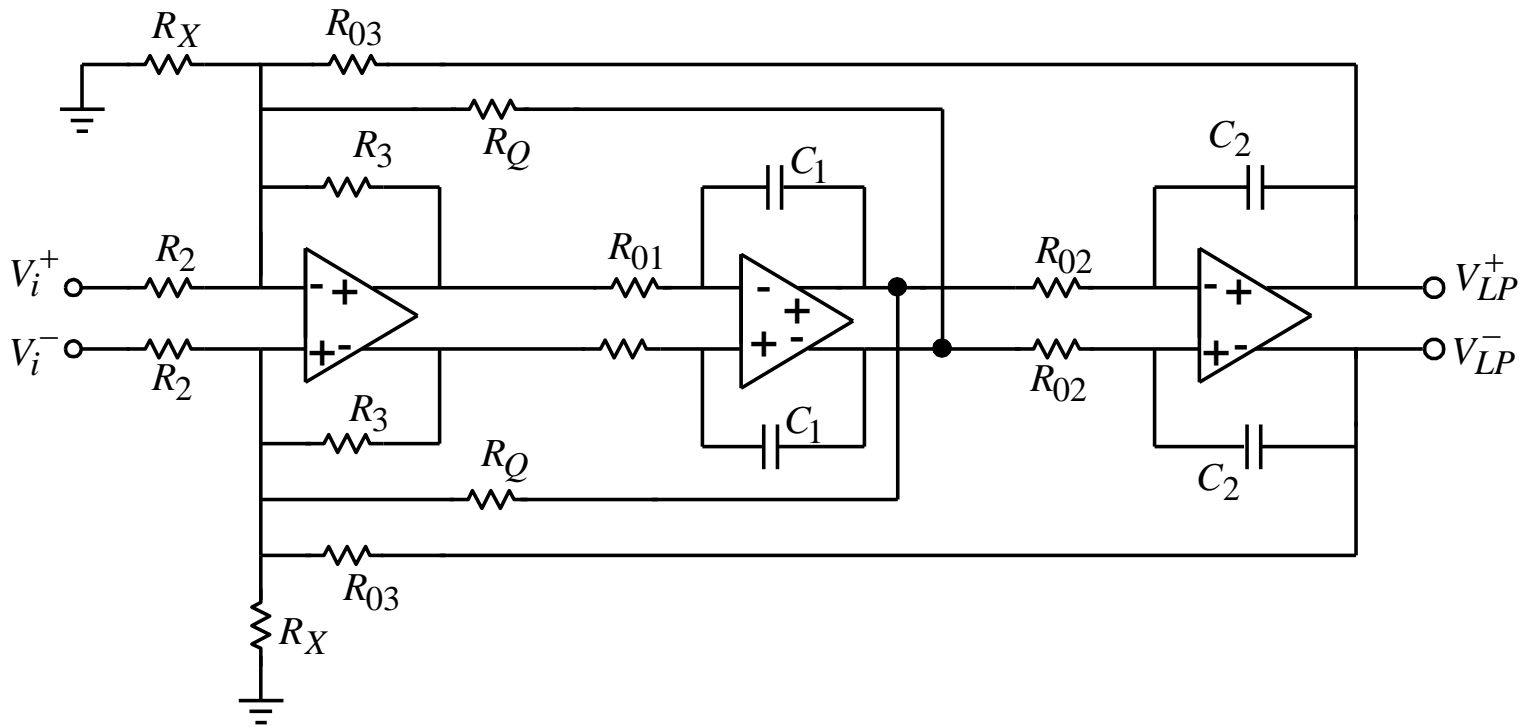Next we consider the fully-differential version of the KHN filter.



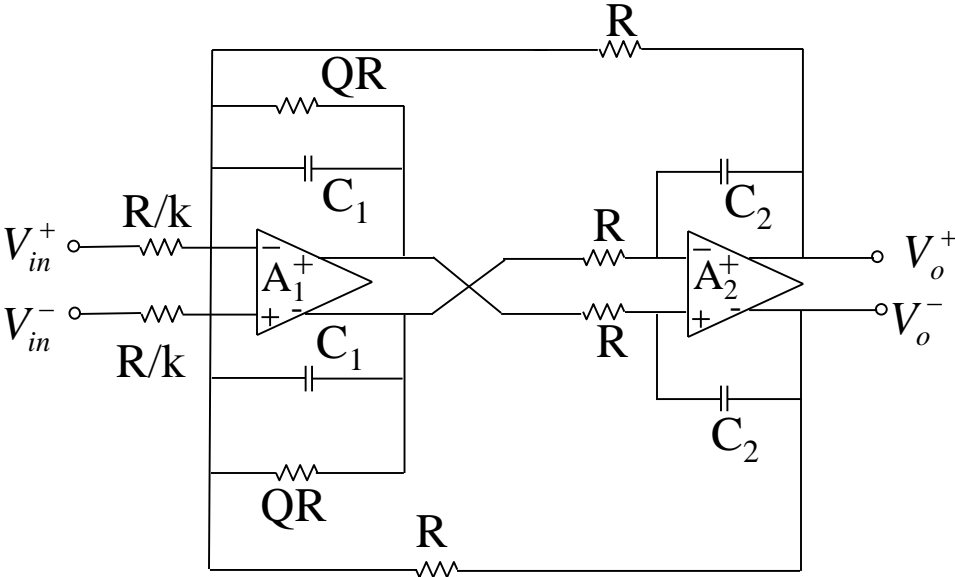
## KHN Fully-Differential Version

How can we take advantage of improved combination of  $\pm Q_I$  in fully differential versions?




SAME!

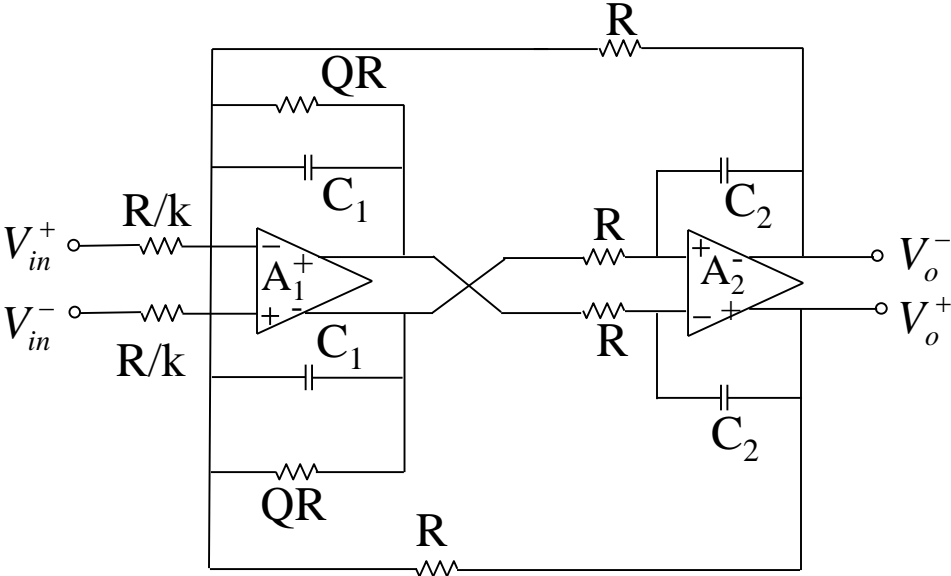

622 (ESS)
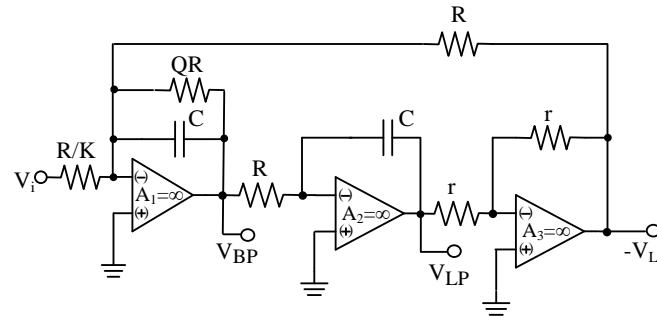
## Effects of Non-Ideal Op Amps on the Tow-Thomas Biquad



When  $A_i$  ( $i = 1, 2, 3$ ) are finite, the denominator becomes of the transfer function yields:

$$D(s) = s^2 + s \frac{\omega_0}{Q} \frac{1 + \frac{2Q+1}{A_1} + \frac{1+Q}{A_2} + \frac{3Q+1}{A_1 A_2}}{1 + \frac{1}{A_1} + \frac{1}{A_2} + \frac{1}{A_1 A_2}} + \omega_0^2 \frac{1 + \frac{2}{A_3} + \frac{2}{A_1 A_2} + \frac{1}{Q A_2} + \frac{1}{Q A_1 A_2}}{1 + \frac{1}{A_1} + \frac{1}{A_2} + \frac{1}{A_1 A_2}}$$

$$\text{Let } A_i = \frac{GB_i}{s}, i = 1, 2, 3$$

Furthermore assume the range of interest  $\omega \gg \frac{GB_i}{A_{oi}}$  and  $\frac{\omega_o}{GB_i} \ll 1, Q \gg 1$ . Then  $D(s)$  becomes:

$$D(s) = \frac{1}{\omega_o} \left( \frac{\omega_o}{GB_1} + \frac{\omega_o}{GB_2} + 2 \frac{\omega_o}{GB_3} \right) s^3 + \left( 1 + 2 \frac{\omega_o}{GB_1} + \frac{\omega_o}{GB_2} \right) s^2 + \frac{\omega_o}{Q} \left( 1 + \frac{\omega_o}{GB_2} \right) s + \omega_o^2$$

$$D(s) = \left( s^2 + \frac{\omega_{oa}}{Q_a} s + \omega_{oa}^2 \right) \left( \frac{s}{\omega_o} \right) \left( \frac{\omega_o}{GB_1} + \frac{\omega_o}{GB_2} + 2 \frac{\omega_o}{GB_3} \right)$$

Thus

$$\omega_{oa} \triangleq \omega_o (1 + \Delta_\omega)$$

$$\text{or } \Delta_\omega = \frac{\omega_{oa} - \omega_o}{\omega_o}$$

for  $\Delta_\omega \ll 1$  and  $Q_a \gg 1$ , then

$$\Delta_\omega = - \frac{\omega_o}{GB_1} - \frac{1}{2} \frac{\omega_o}{GB_2} \Bigg|_{GB_1=GB_2=GB} = - \frac{3}{2} \left( \frac{\omega_o}{GB} \right)$$

$$\frac{Q_a}{Q} \cong \frac{1}{1 - Q \left( \frac{\omega_o}{GB_1} + \frac{\omega_o}{GB_2} + 2 \frac{\omega_o}{GB_3} \right)}$$

For equal  $GB_1 = GB_2 = GB_3$

$$Q_a = \frac{Q}{1 - 4Q(\omega_o/GB)}$$

$$Q_a \cong Q \left( 1 + 4Q \left( \frac{\omega_o}{GB} \right) \right) , \quad \text{for } 4Q \left( \frac{\omega_o}{GB} \right) \ll 1$$

Note that for a stable filter

$$4Q \omega_o/GB < 1$$

or

$$Q < \frac{GB}{4\omega_o}$$

## KEY FILTER PARAMETERS IN ACTIVE-RC FILTERS

- Dynamic Range
- Signal-To-Noise Ratio
- Total Output Noise
- Noise Power Spectral Density
- Total Area

Resistor and Capacitors can be expressed as:

$$R_\ell = r_\ell R \quad , \quad C_\ell = c_\ell C$$

where  $r_\ell$  and  $c_\ell$  are the normalized filter values.

The resistor power dissipation for a sinusoidal input yields

$$P_R(f) = \sum_{\ell} \frac{|V_i H_{i\ell}|^2}{2R_\ell} = \frac{|V_i|^2}{2R} \sum_{\ell} \frac{|H_{i\ell}(f)|^2}{r_\ell} \quad (1)$$

Where  $H_{i\ell}(f)$  is the transfer function from the input to the terminals of resistor  $R_\ell$


Reference. L. Oth et al, "General Results for Resistive Noise in Active RC and MOSFET-C Filters", *IEEE Trans on Circuits and Systems II*, Vol. 42, No. 12, pp. 785-793, December 1995.



Focusing on the noise resistor, the power spectral density is given by

$$S_R(f) = \sum_{\ell} 4kTR_{\ell} |H_{\ell o}(f)|^2 = 4kTR \sum_{\ell} r_{\ell} |H_{\ell o}(f)|^2 \quad (2)$$

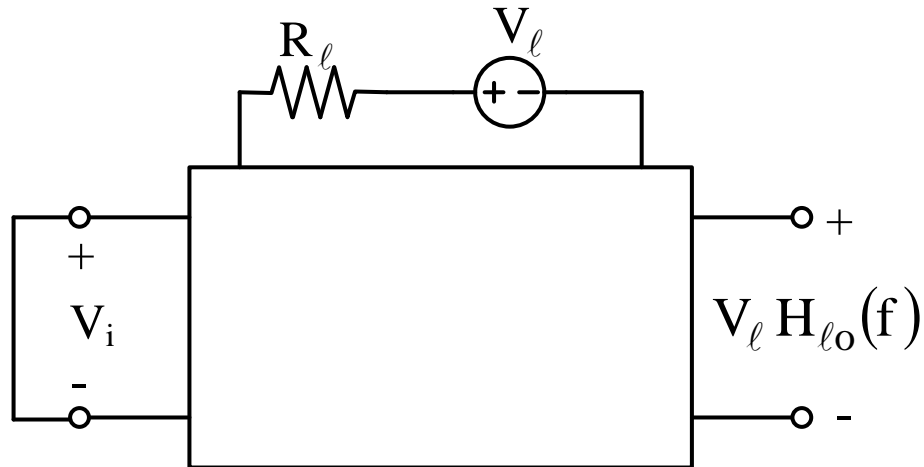The definition of  $H_{\ell o}(f)$  is pictorially shown below:



Thus, the total output noise (mean squared value) due to the resistors become

$$N_R = \int_0^{\infty} S_R(f) df$$

In practice the upper limit of the integration is limited to a useful practical value.

The signal-to-noise ratio for a given  $V_i$  and frequency  $f$  is given by

$$\text{SNR} = \frac{|V_i H(f)|^2}{2N_R} \quad (3)$$

and

$$\max_f P_R(f) \leq P_{R,\max}$$

where  $P_{R,\max}$  is the maximum specified power dissipation in the resistors. Then

$$\text{DR} = \frac{|V_i|_{\max}^2 \max_f |H(f)|^2}{2N_R} \quad (4)$$

Let us consider a second - order BP filter example


$$H_{\text{BP}}(s) = \frac{\frac{\omega_c}{Q} s}{s^2 + \frac{\omega_c}{Q} s + \omega_c^2}$$

Using the following notation the above  $H_{\text{BP}}(s)$  yields

$$H_{\text{BP}}(f) = \frac{Q^{-1} f_c (jf)}{(jf)^2 + Q^{-1} f_c (jf) + f_c^2}$$

$$P_R(f_c) = \frac{|V_i|^2}{R} a (a + Q^{-1})$$

For the biquad shown below

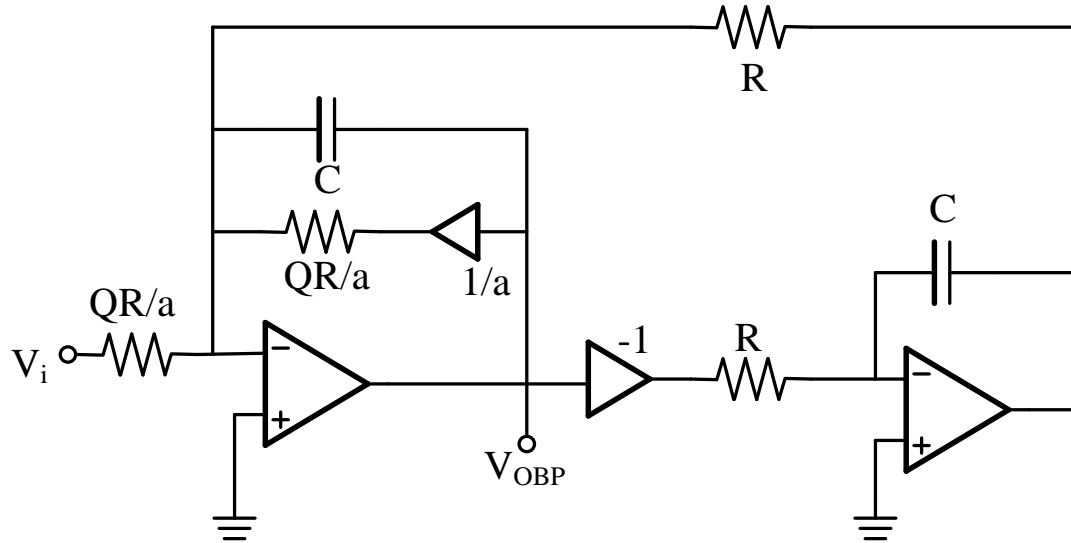


and

$$N_R = \frac{2kT}{C} \frac{(1 + Q/a)}{a}$$

$a \uparrow \Rightarrow N_R \downarrow \Rightarrow a V_{OBP}$  limited by linearity and by resistor power dissipation which is proportional to  $(a)^2$ .
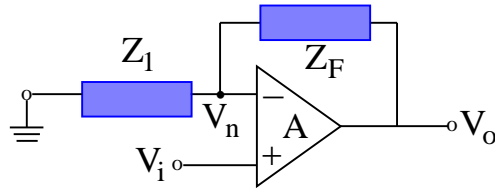
# Fully Differential Fully Balanced Circuits

What is the problem with single-input / single-output?



$$V_n = \frac{V_o Z_1}{Z_1 + Z_F}$$

$$V_1 - V_n = \frac{V_o}{A} \Big|_{A \rightarrow \infty} = 0$$


For  $V_i = V_{id} + V_{icm}$

$$V_o = \left(1 + \frac{Z_F}{Z_1}\right) (V_{id} + V_{icm})$$



No elimination of common-mode signal.

How to solve this problem?

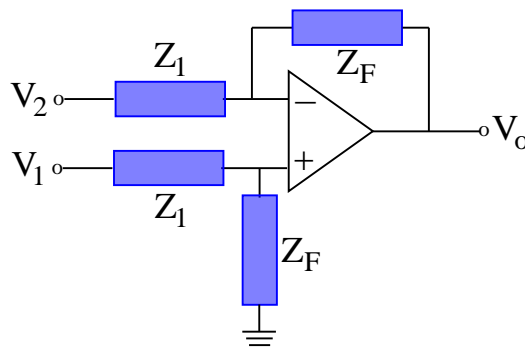

$$\text{For } V_i = V_{id} + V_{icm} = (V_1 - V_2) + \frac{(V_1 + V_2)}{2}$$


$$V_o = \frac{Z_F}{Z_1} (V_1 - V_2)$$



No common-mode output.

How to obtain a fully differential circuit?  
 We will discuss two potential approaches

Approach 1

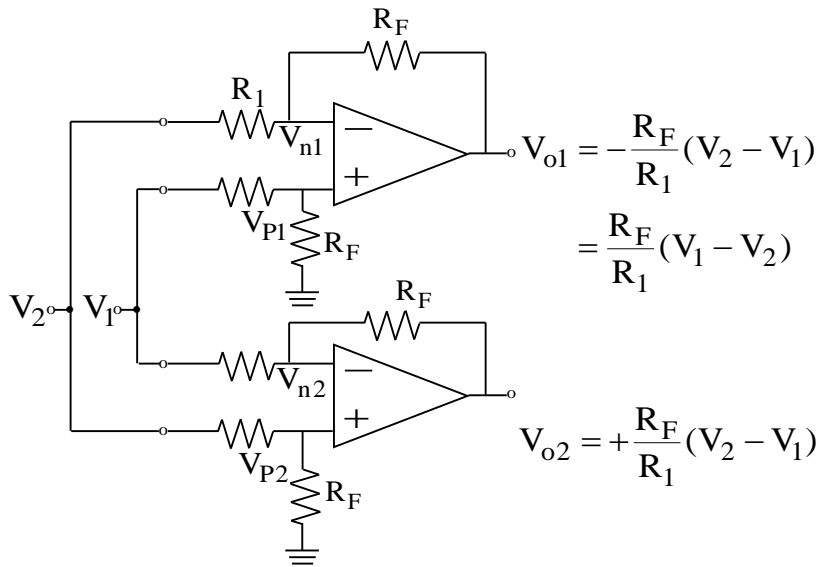


$$V_{o1} - V_{o2} = \frac{R_F}{R_1} (V_1 - V_2 - V_2 + V_1) =$$

$$V_{oD} = \frac{2R_F}{R_1} (V_1 - V_2)$$

conditions  $V_{n2} = V_{p2}$  ;  $V_{n1} = V_{p1}$

Remark: sensitive to CM signals

Approach 2

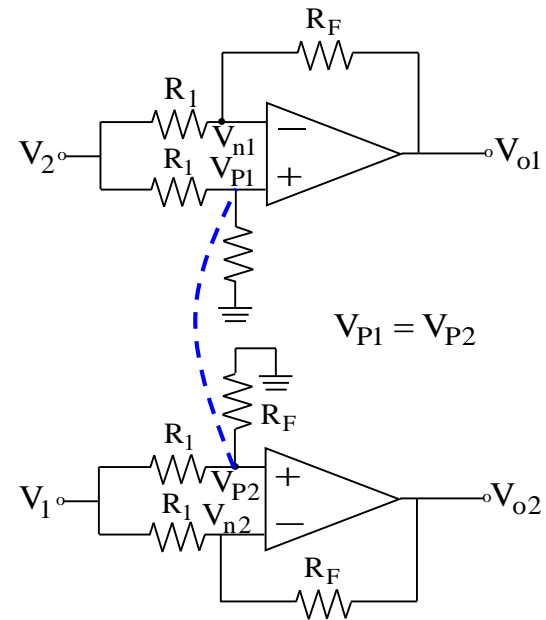

Remark:


More robust to reject  
 common-mode signals

### First-Order FB Low Pass with Op Amp


```

*
.subckt opamp non inv out
rin non inv 100K
egain 1 0 (non, inv) 200K
ropen 1 2 2K
copen 2 0 15.9155u
eout 3 0 (2, 0) 1
rout 3 out 50
.ends
*vin 3 31 ac 1.0
vin 31 0 ac 1.0
x1 4 1 2 opamp
x2 4 11 22 opamp
R1 3 1 1K
R11 3 4 1K
R1B 31 4 1K
R1BB 31 11 1K
RF1 2 1 1K
RF1B 22 11 1K
RF11 4 0 1K
RF11B 4 0 1K
C1 2 1 0.159155u
C1B 22 11 0.159155u
C1A 4 0 0.159155u
C11B 4 0 0.159155u
rdummy 3 31 1
.ac dec 10 10Hz 10KHz
.probe
.end

```

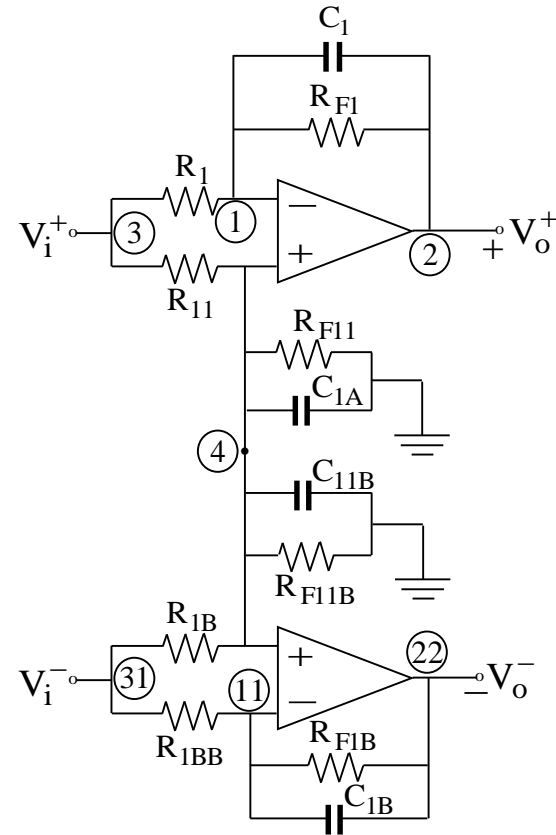
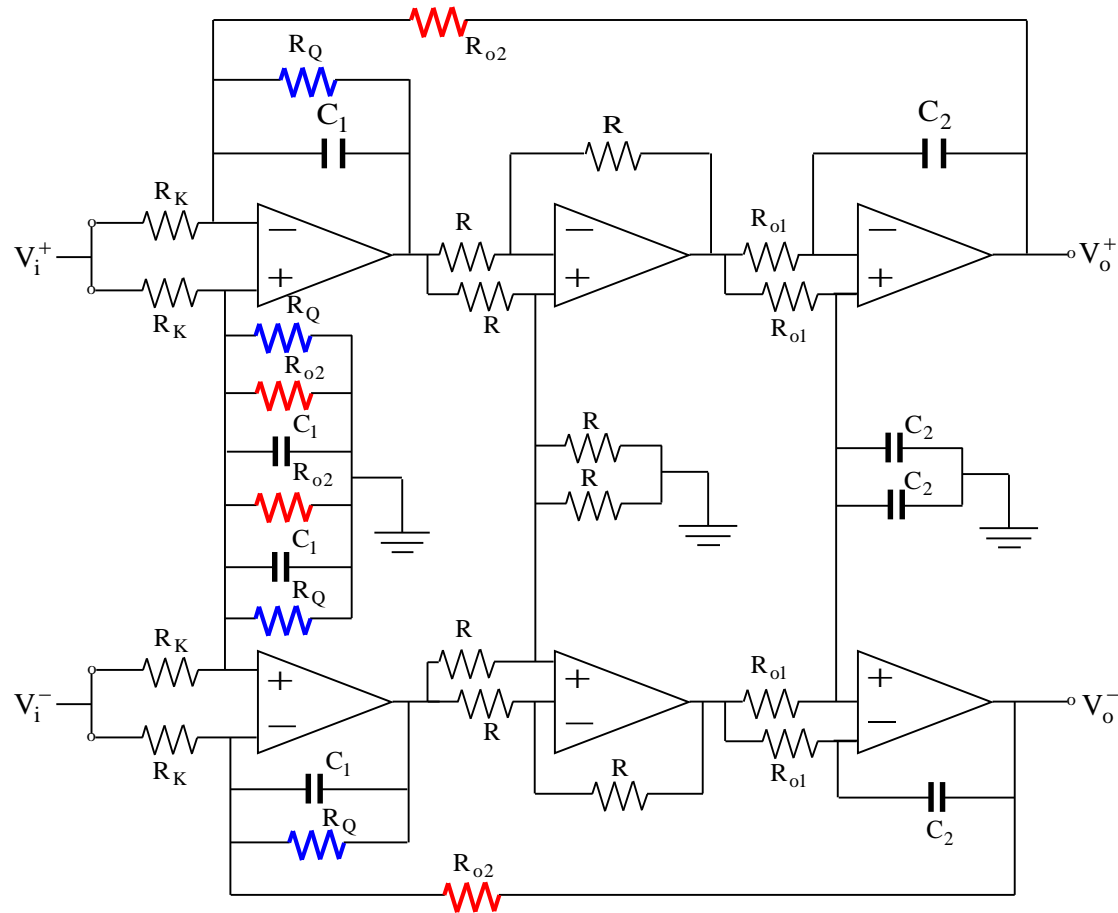
# Fully Balanced T-T Active-RC Implementation



622 Active Filters


By Edgar Sánchez-Sinencio

Texas A&M University

# **Introduction to Matlab and Simulink For Filter Design**




# Example 1: Ideal Integrator

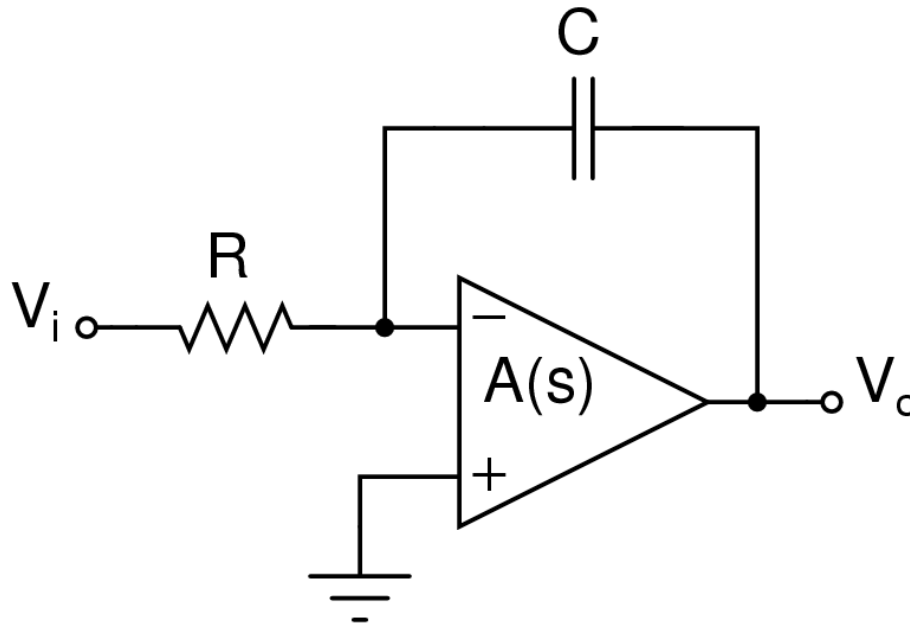

$$R = 1\text{K}\Omega \quad C = 0.159\text{mF}$$

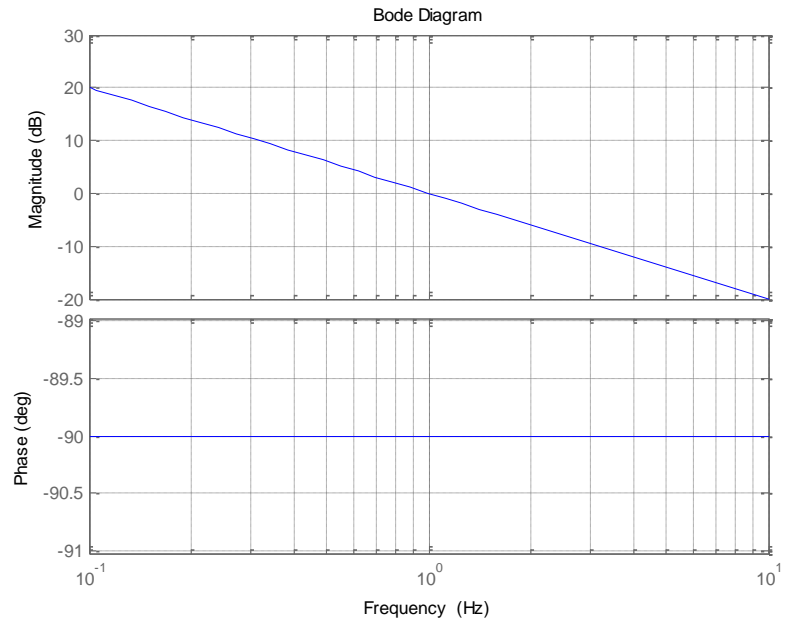
# Bode Plot: Ideal Integrator (Matlab)

```
s=tf('s');  
R=1e3;           %Resistor Value  
C=0.159e-3;     %Capacitor Value  
hs=1/(R*C*s);   %hs= Vo(s)/Vi(s)  
figure(1)  
bode(hs)        %Create Bode Plot  
grid minor     %Add grid to plot  
H= gcr;        %change X-axis  
units  
h.AxesGrid.Xunits = 'Hz'; %Set units to  
Hz  
pole(hs);      %calculates hs poles  
zero(hs);      %calculates hs zeros
```





# Bode Plot: Ideal Integrator (Simulink)

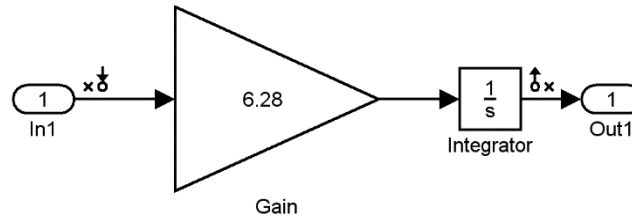1) Create Model using Gain, Integrator, and In/Out blocks




2) Go to: Tools => Control Design=> Linear Analysis


3) Then press: Linearize model

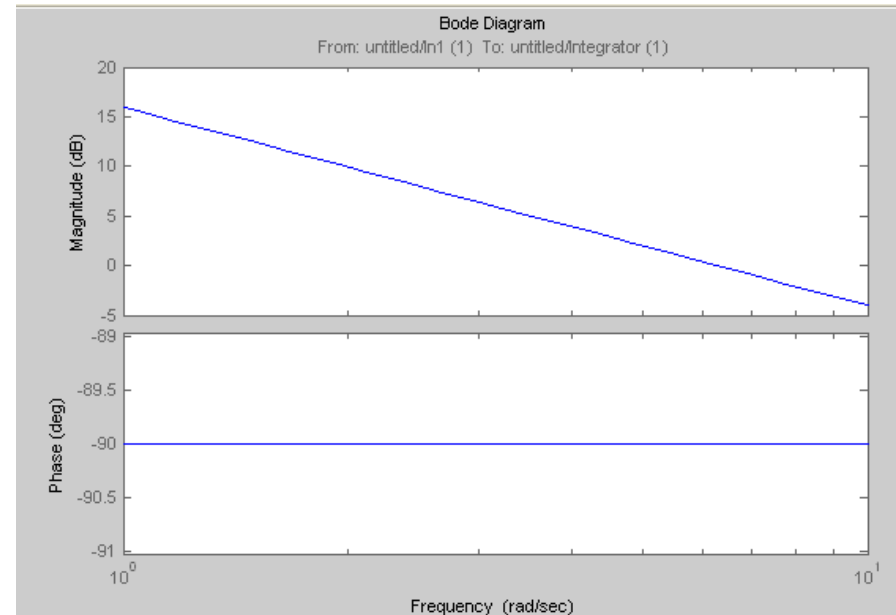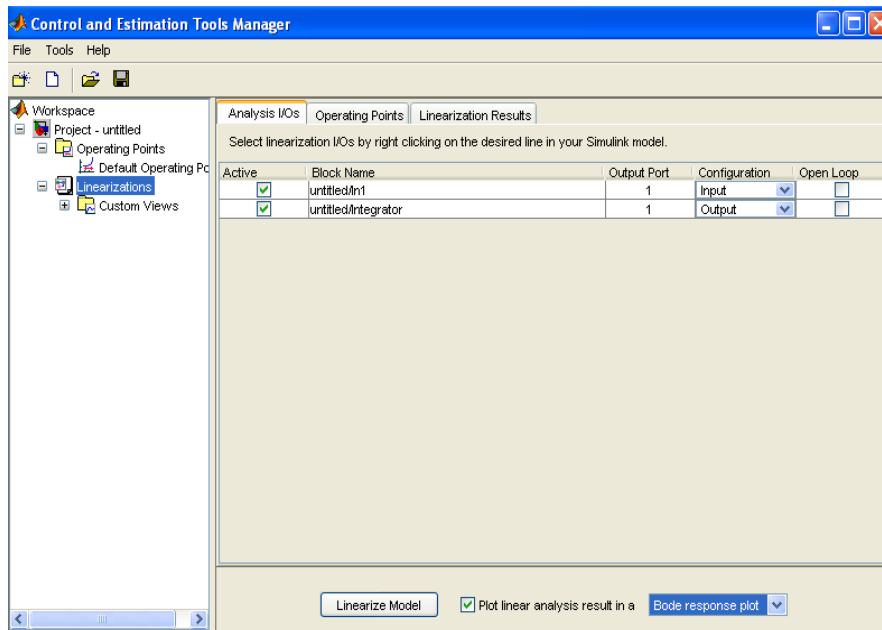

# Tow-Thomas Biquad (Simulink)

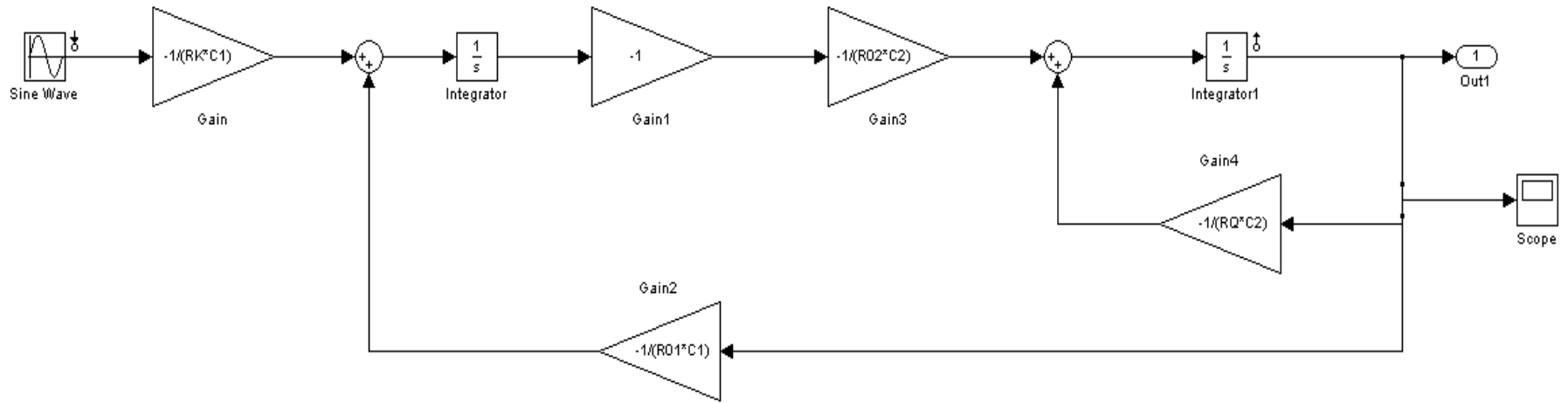

# Output Waveform (Scope)

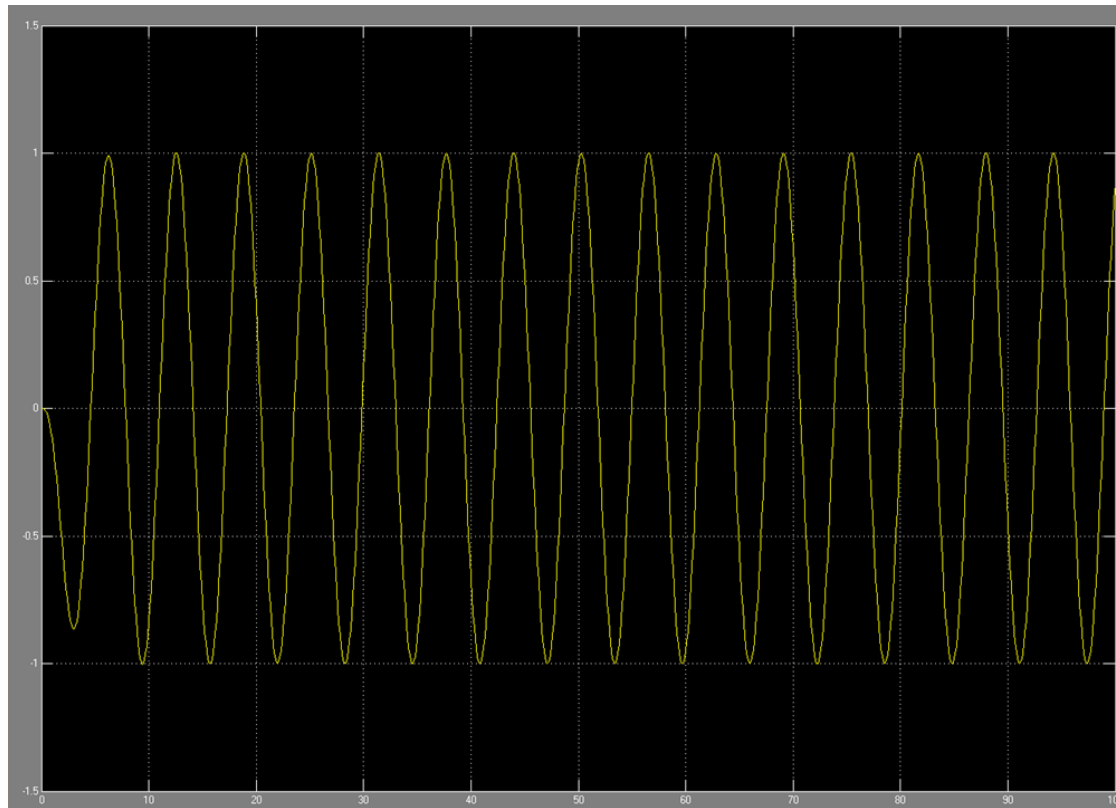


# Integrator Non-ideal amplifier

```

clear
clc
s=tf('s');
R=1;           %Resistor Value
C=0.159e-3;   %Capacitor Value
hs1=-1/(R*C*s); %hs= Vo(s)/Vi(s)
figure(1)
bodemag(hs1)
hold on
f=1e3;
for i=1:5;
GBW=2*pi*f;
A=GBW/s;
Beta=R/(R+1/(s*C));
hs2=-1/(R*C*s)*1/(1+1/(A*Beta));
hold on
bodemag(hs2,{2*pi*1,2*pi*1e5})
f=10*f;
end
grid minor           %Add grid to plot
h= gcr;              %change X-axis units
h.AxesGrid.Xunits = 'Hz'; %Set units to Hz
legend('ideal', 'GBW=1kHz', 'GBW=10kHz', 'GBW=100kHz', 'GBW=1MHz', 'GBW=10MHz', 1)

```

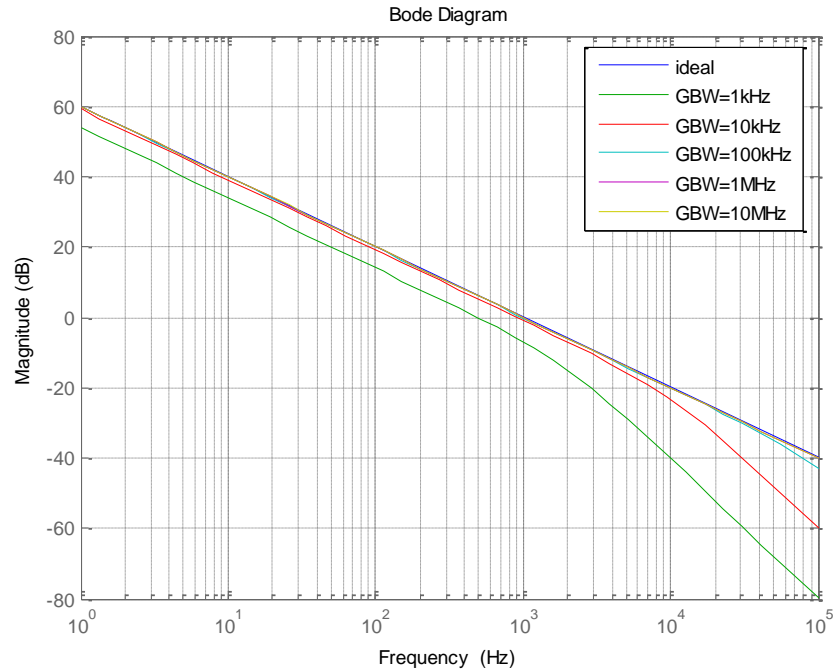

# Filter Approximation: Low-Pass Butterworth

- E.g.: Use Matlab to find the numerator b and denominator a coefficients for a third-order Butterworth low-pass filter prototype with normalized cutoff frequency.

```
[z,p,k]=buttap(3); % To get gain and poles
[b,a]=zp2tf(z,p,k); %To get b and a coefficients
H=tf([b],[a]); %to generate transfer function
figure(1)
bode(H); %Bode plot
grid minor;
figure(2)
pzmap(H); %plot poles and zeros
grid minor;
```

The squared magnitude of a low-pass butterworth filter is given by:

$$|H(\omega)|^2 = \frac{1}{1 + (\omega/\omega_0)^{2n}}$$

Results:


$$b = 0 \ 0 \ 0 \ 1$$

$$a = 1 \ 2 \ 2 \ 1$$

Thus,


$$H(s) = \frac{1}{s^3 + 2s^2 + 2s + 1}$$

# Pole-zero plot

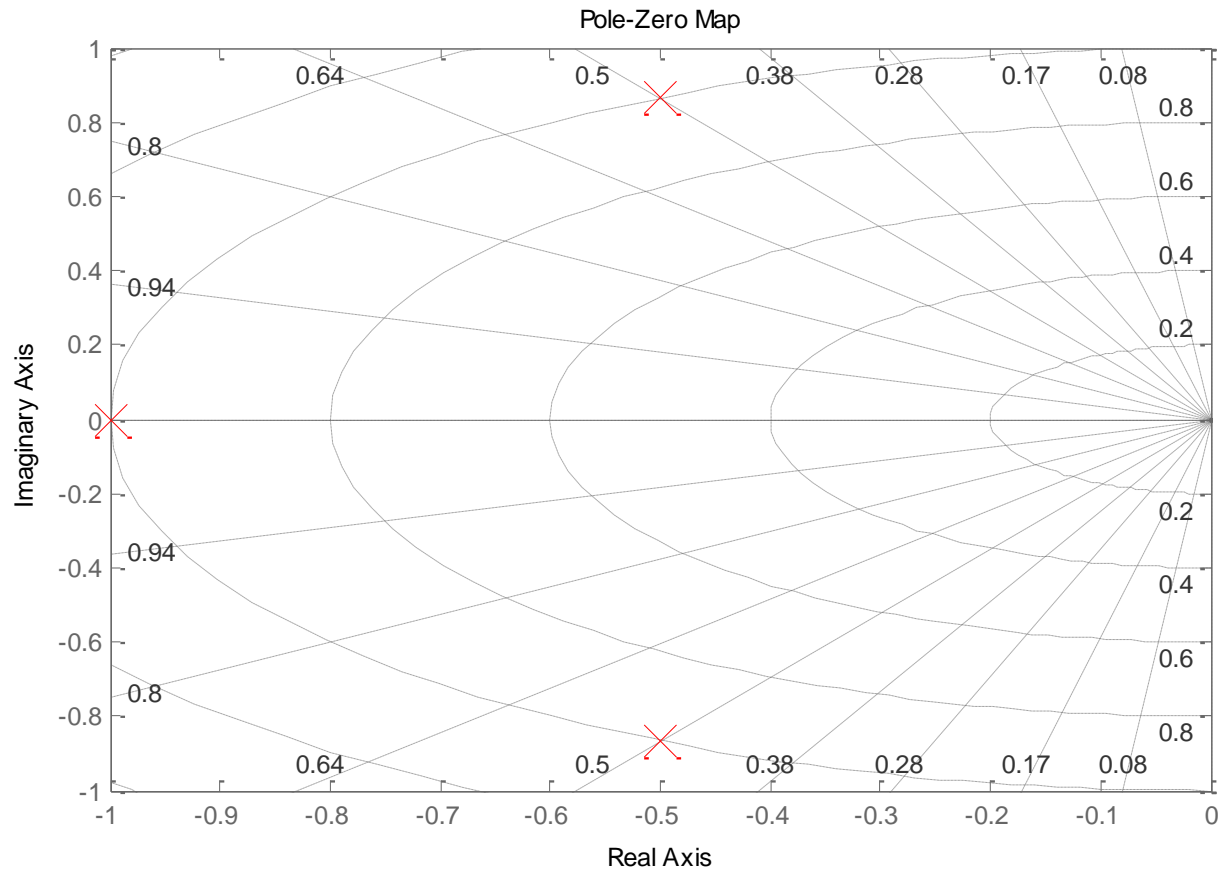



# Bode Plot

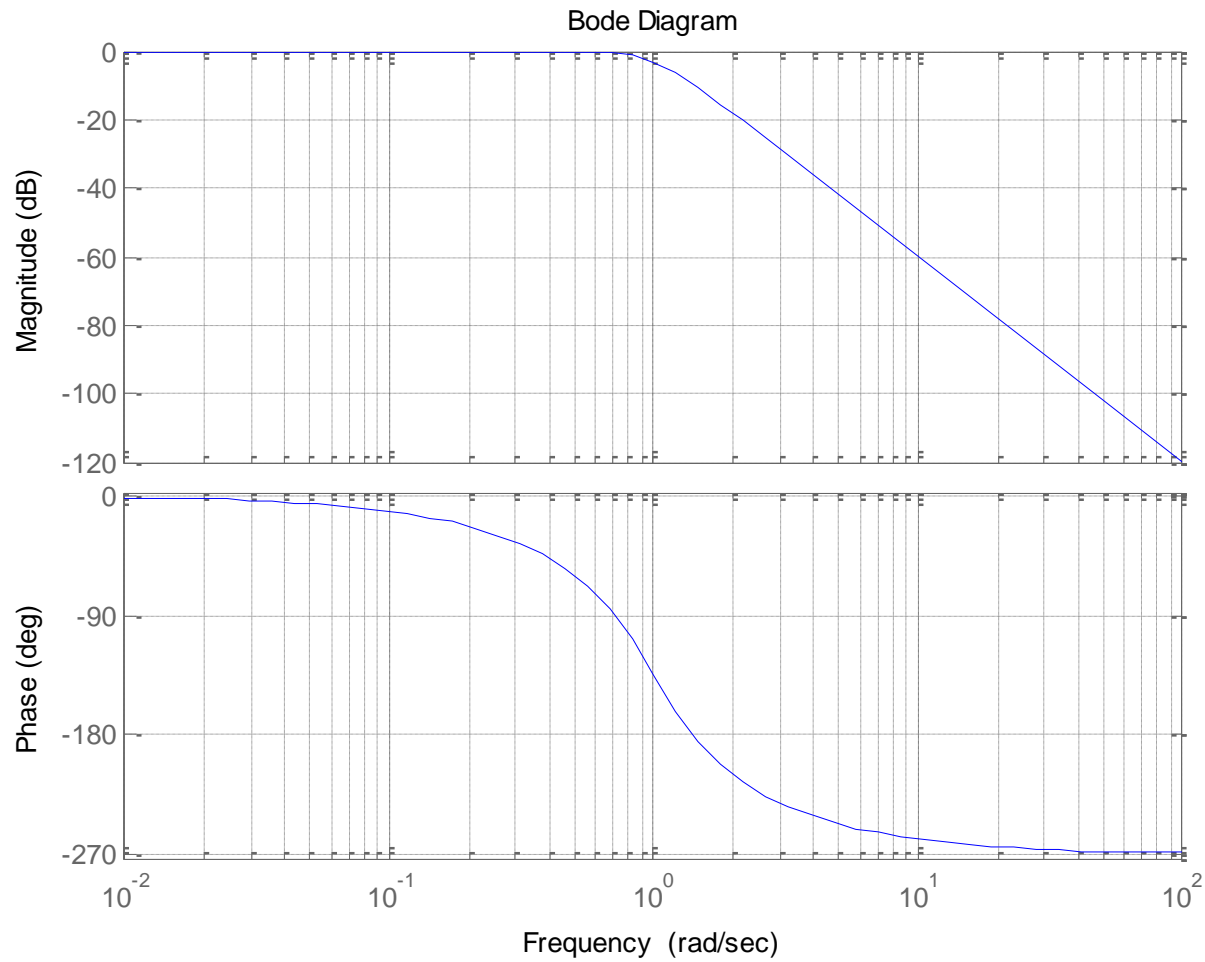

# Low-pass Chebyshev Filter

- Use the Matlab `cheb1ap` function to design a second order Type I Chebyshev low-pass filter with 3dB ripple in the pass band

```
w=0:0.05:400; % Define range to plot
```


```
[z,p,k]=cheb1ap(2,3);
```

```
[b,a]=zp2tf(z,p,k); % Convert zeros and poles of G(s) to polynomial form
```

```
bode(b,a)
```

```
grid minor;
```

# Low-pass Chebyshev Filter

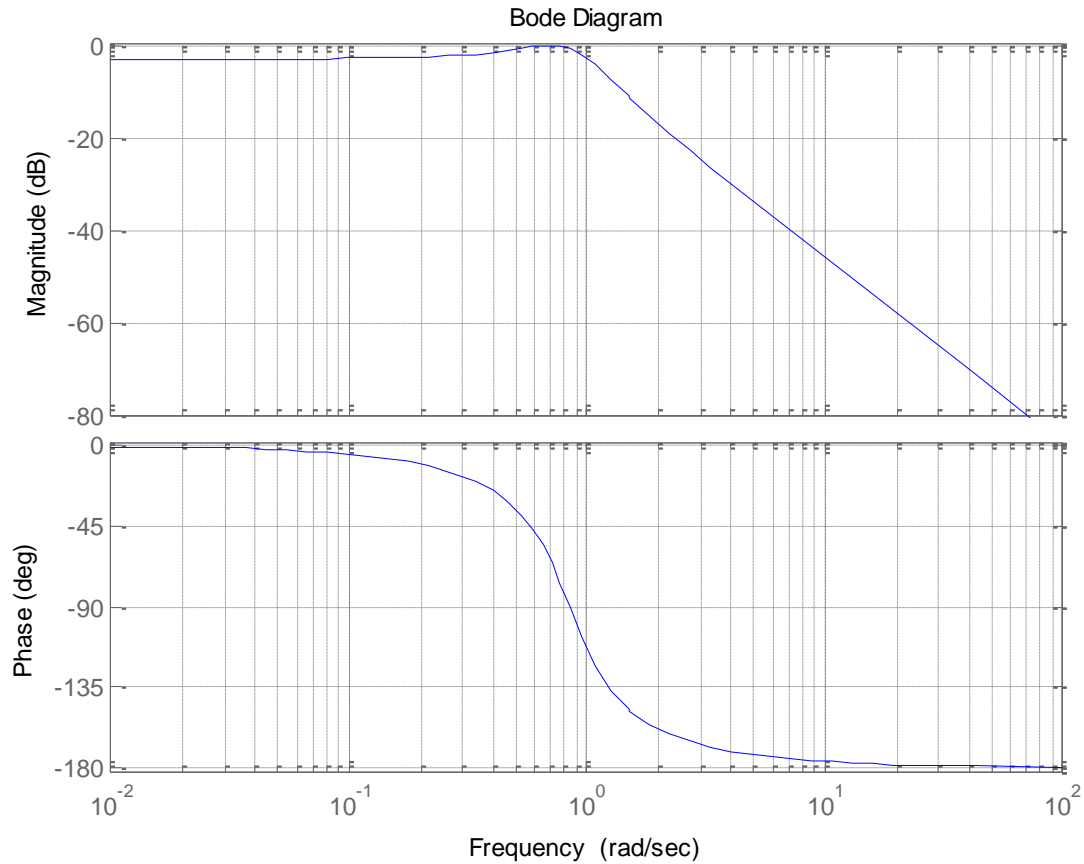

# Low-pass Chebyshev Filter

**% Another way to write the code!**

```
w=0:0.01:10;
```

```
[z,p,k]=cheb1ap(2,3);
```

```
[b,a]=zp2tf(z,p,k);
```

```
Gs=freqs(b,a,w);
```

```
xlabel('Frequency in rad/s');
```


```
ylabel('Magnitude of G(s)');
```

```
semilogx(w,abs(Gs));
```

```
title('Type 1 Chebyshev Low-Pass Filter');
```

```
Grid;
```

# Low-pass Chebyshev Filter

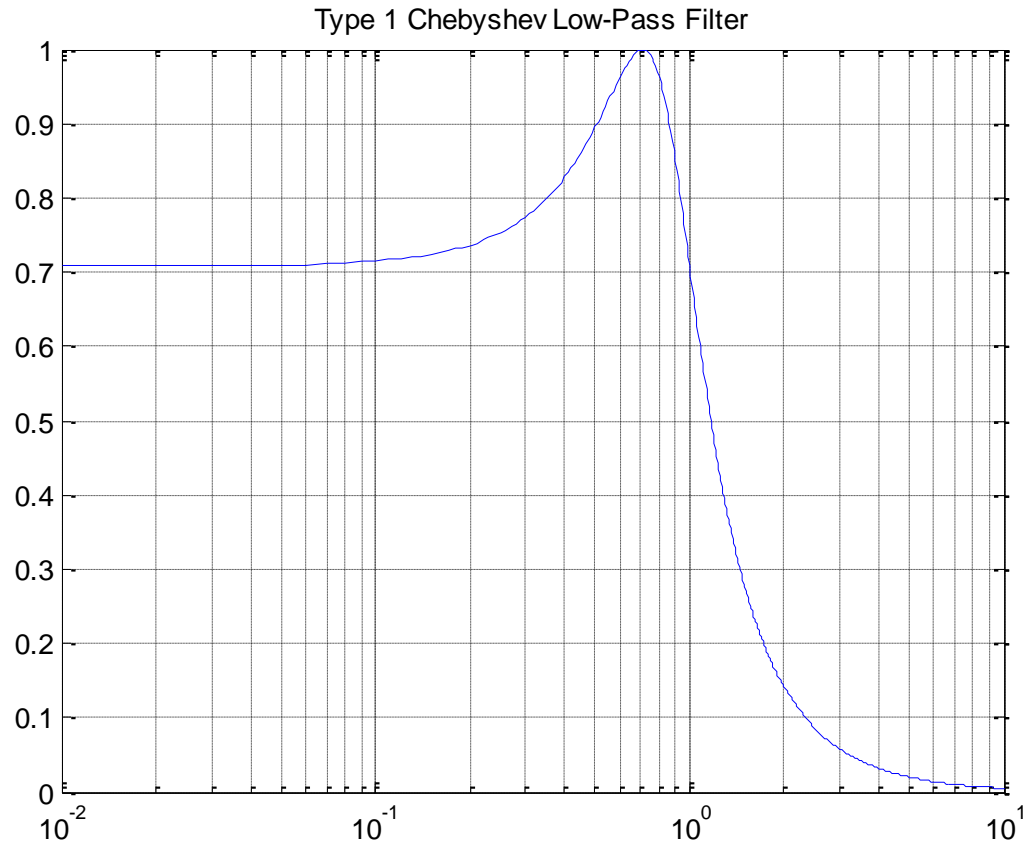


# Inverse Chebyshev

- Using the Matlab `cheb2ap` function, design a third order Type II Chebyshev analog filter with 3dB ripple in the stop band.

```
w=0:0.01:1000;  
[z,p,k]=cheb2ap(3,3);  
[b,a]=zp2tf(z,p,k); Gs=freqs(b,a,w);  
semilogx(w,abs(Gs));  
xlabel('Frequency in rad/sec');  
ylabel('Magnitude of G(s)');  
title('Type 2 Chebyshev Low-Pass Filter, k=3, 3 dB ripple in stop  
band');  
grid
```

# Inverse Chebyshev

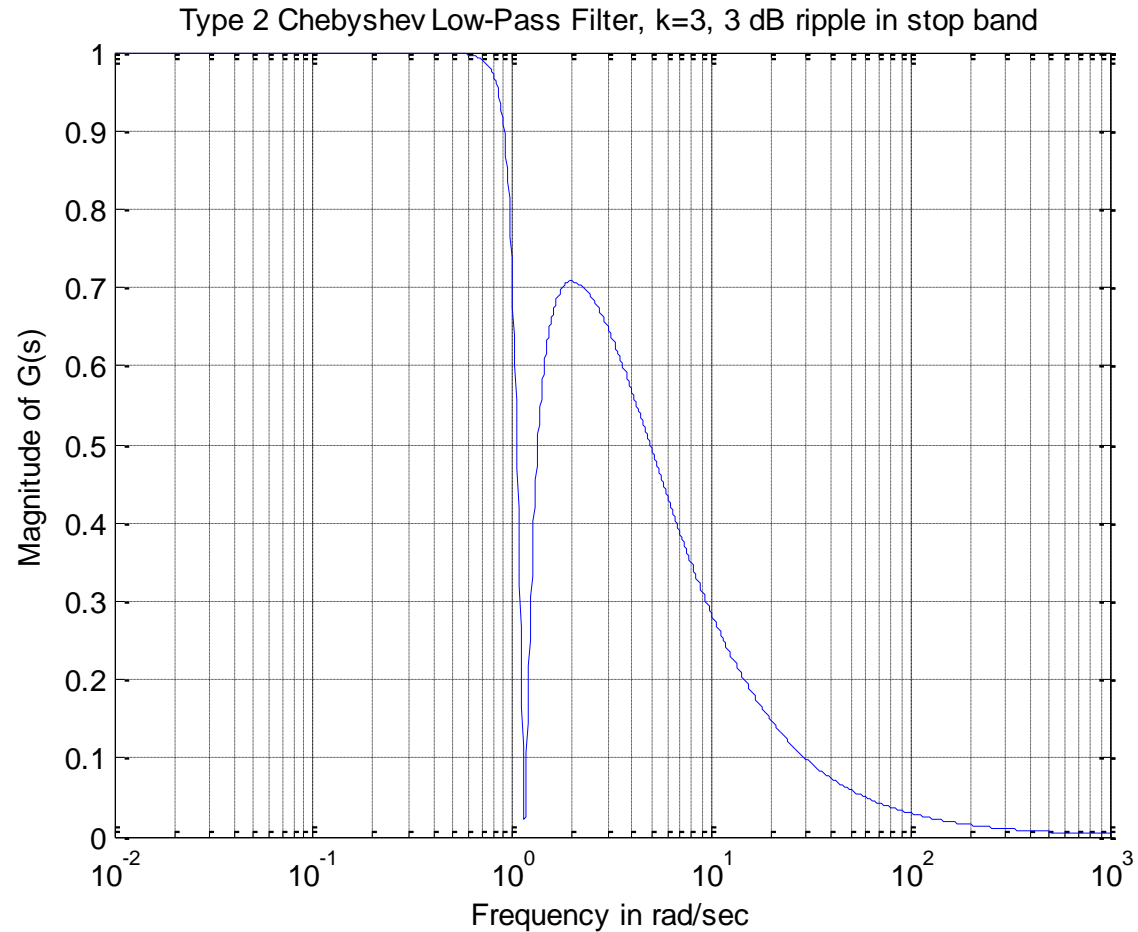


# Elliptic Low-Pass Filter

- Use Matlab to design a four pole elliptic analog low-pass filter with 0.5dB maximum ripple in the pass-band and 20dB minimum attenuation in the stop-band with cutoff frequency at 200 rad/s.

```
w=0: 0.05: 500;  
[z,p,k]=ellip(4, 0.5, 20, 200, 's');  
[b,a]=zp2tf(z,p,k);  
Gs=freqs(b,a,w);  
plot(w,abs(Gs))  
title('4-pole Elliptic Low Pass Filter');  
grid
```



# Elliptic Low-Pass Filter

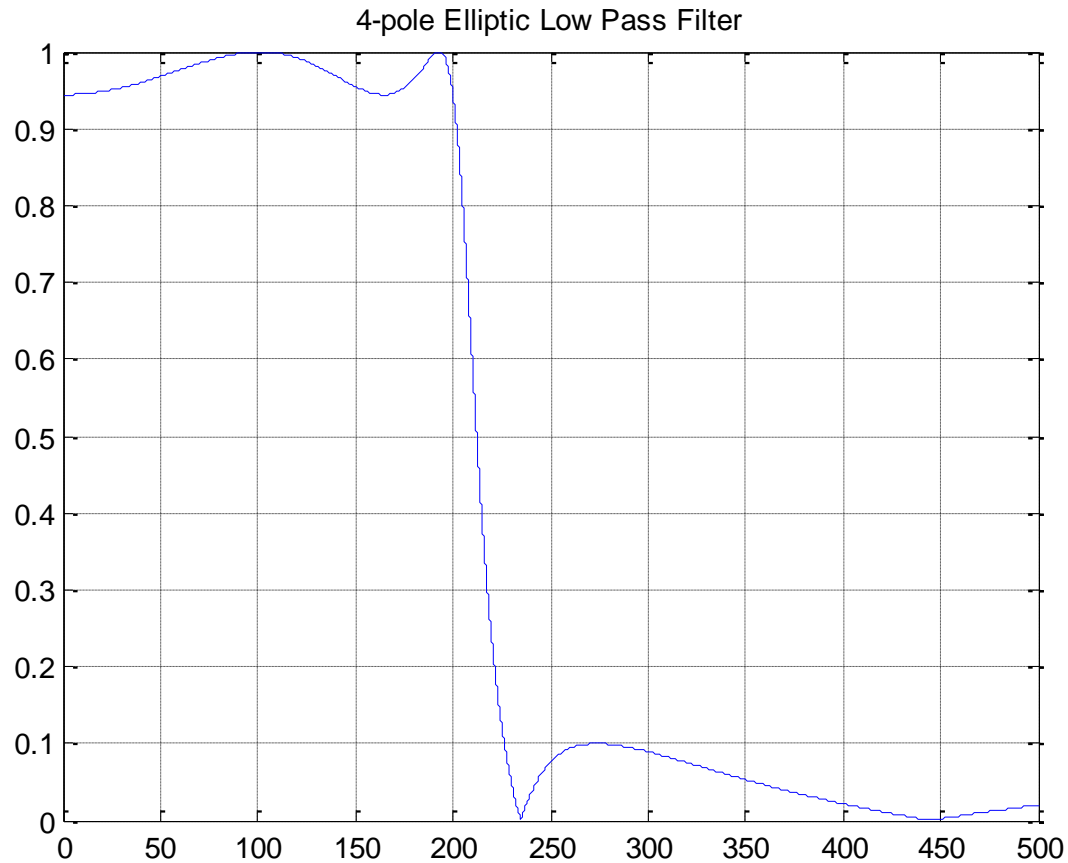

# Transformation Methods


- Transformation methods have been developed where a low pass filter can be converted to another type of filter by simply transforming the complex variable  $s$ .
- Matlab `lp2lp`, `lp2hp`, `lp2bp`, and `lp2bs` functions can be used to transform a low pass filter with normalized cutoff frequency, to another low-pass filter with any other specified frequency, or to a high pass filter, or to a band-pass filter, or to a band elimination filter, respectively.

## LPF with normalized cutoff frequency, to another LPF with any other specified frequency

- Use the MATLAB **buttap** and **lp2lp** functions to find the transfer function of a third-order Butterworth low-pass filter with cutoff frequency  $f_c=2\text{kHz}$ .

```
% Design 3 pole Butterworth low-pass filter (wcn=1 rad/s)
[z,p,k]=buttap(3);
[b,a]=zp2tf(z,p,k);      % Compute num, den coefficients of this filter
(wcn=1rad/s)
f=1000:1500/50:10000;    % Define frequency range to plot
w=2*pi*f;                % Convert to rads/sec
fc=2000;                  % Define actual cutoff frequency at 2 KHz
wc=2*pi*fc;              % Convert desired cutoff frequency to rads/sec
[bn,an]=lp2lp(b,a,wc);   % Compute num, den of filter with fc = 2 kHz
Gsn=freqs(bn,an,w);      % Compute transfer function of filter with fc = 2 kHz
semilogx(w,abs(Gsn));
grid;
xlabel('Radian Frequency w (rad/sec)')
ylabel('Magnitude of Transfer Function')
title('3-pole Butterworth low-pass filter with fc=2 kHz or wc = 12.57 kr/s')
```
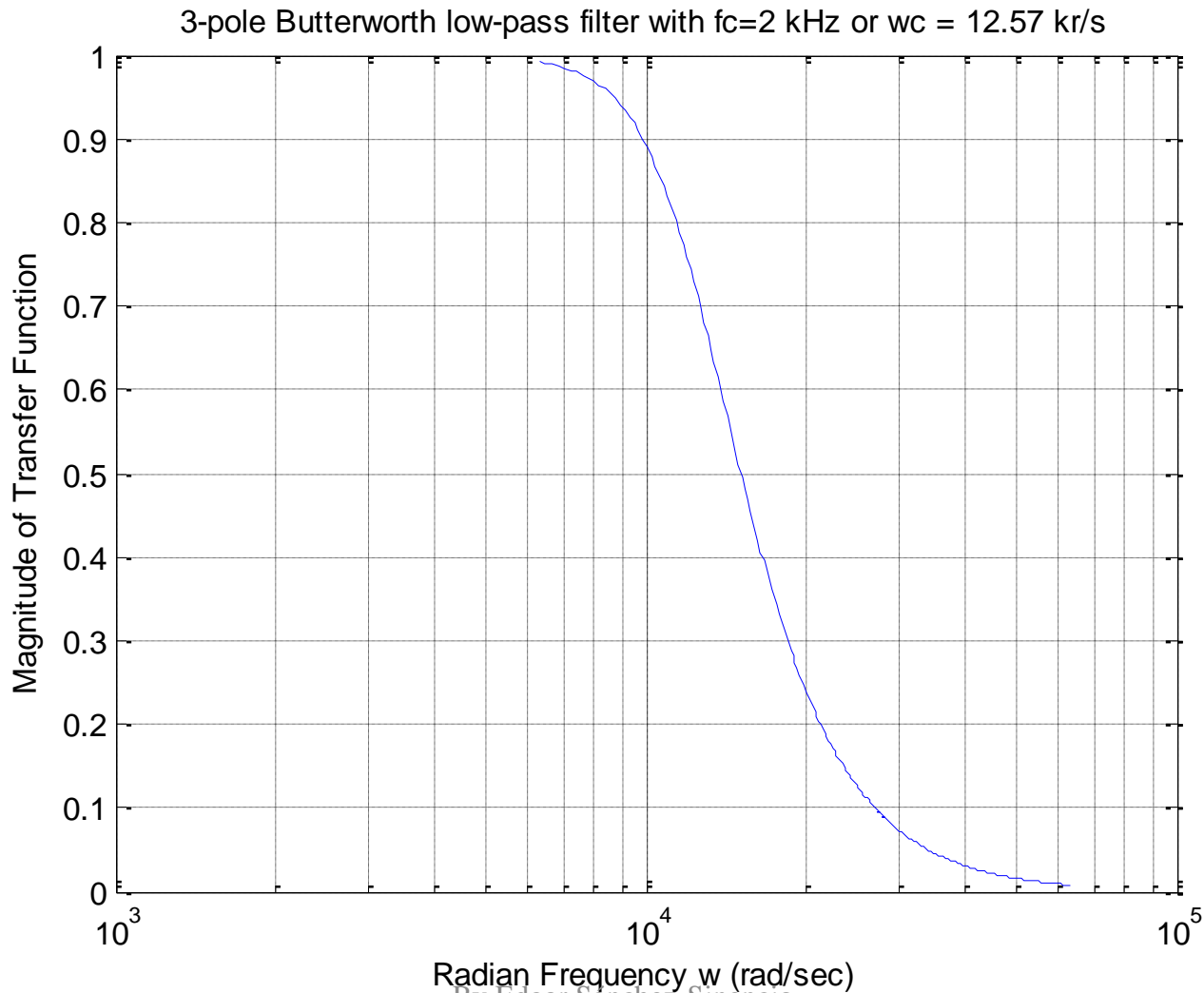
# LPF with normalized cutoff frequency, to another LPF with any other specified frequency




# High-Pass Filter

- Use the MATLAB commands **cheb1ap** and **lp2hp** to find the transfer function of a 3-pole Chebyshev high-pass analog filter with cutoff frequency  $f_c = 5\text{KHz}$ .

```
% Design 3 pole Type 1 Chebyshev low-pass filter, wcn=1 rad/s
[z,p,k]=cheb1ap(3,3);
[b,a]=zp2tf(z,p,k);           % Compute num, den coef. with wcn=1 rad/s
f=1000:100:100000;           % Define frequency range to plot
fc=5000;                       % Define actual cutoff frequency at 5 KHz
wc=2*pi*fc;                   % Convert desired cutoff frequency to rads/sec
[bn,an]=lp2hp(b,a,wc);        % Compute num, den of high-pass filter with fc =5KHz
Gsn=freqs(bn,an,2*pi*f);      % Compute and plot transfer function of filter with fc = 5 KHz
semilogx(f,abs(Gsn));
grid;
xlabel('Frequency (Hz)');
ylabel('Magnitude of Transfer Function')
title('3-pole Type 1 Chebyshev high-pass filter with fc=5 KHz ')
```

# High-Pass Filter

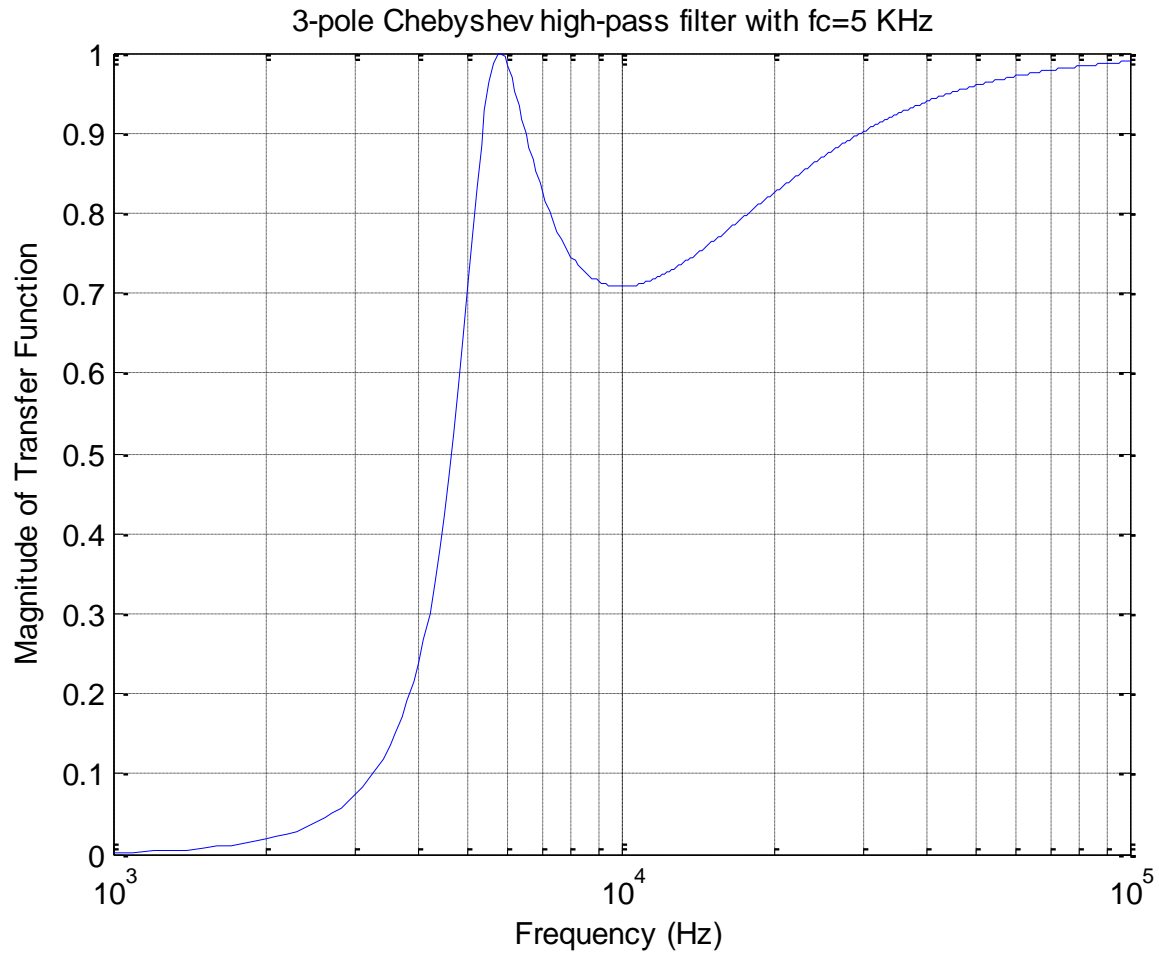


# Band-Pass Filter

- Use the MATLAB functions **buttap** and **lp2bp** to find the transfer function of a 3-pole Butterworth analog band-pass filter with the pass band frequency centered at  $f_0 = 4\text{kHz}$ , and bandwidth  $BW = 2\text{KHz}$ .

```
[z,p,k]=buttap(3);    % Design 3 pole Butterworth low-pass filter with wcn=1 rad/s
[b,a]=zp2tf(z,p,k);  % Compute numerator and denominator coefficients for wcn=1 rad/s
f=100:100:100000;    % Define frequency range to plot
f0=4000;             % Define centered frequency at 4 KHz
W0=2*pi*f0;         % Convert desired centered frequency to rads/s
fbw=2000;           % Define bandwidth
Bw=2*pi*fbw;        % Convert desired bandwidth to rads/s
[bn,an]=lp2bp(b,a,W0,Bw); % Compute num, den of band-pass filter
% Compute and plot the magnitude of the transfer function of the band-pass filter
Gsn=freqs(bn,an,2*pi*f);
semilogx(f,abs(Gsn));
grid;
xlabel('Frequency f (Hz)');
ylabel('Magnitude of Transfer Function');
title('3-pole Butterworth band-pass filter with f0 = 4 KHz, BW = 2KHz')
```

# Band-Pass Filter

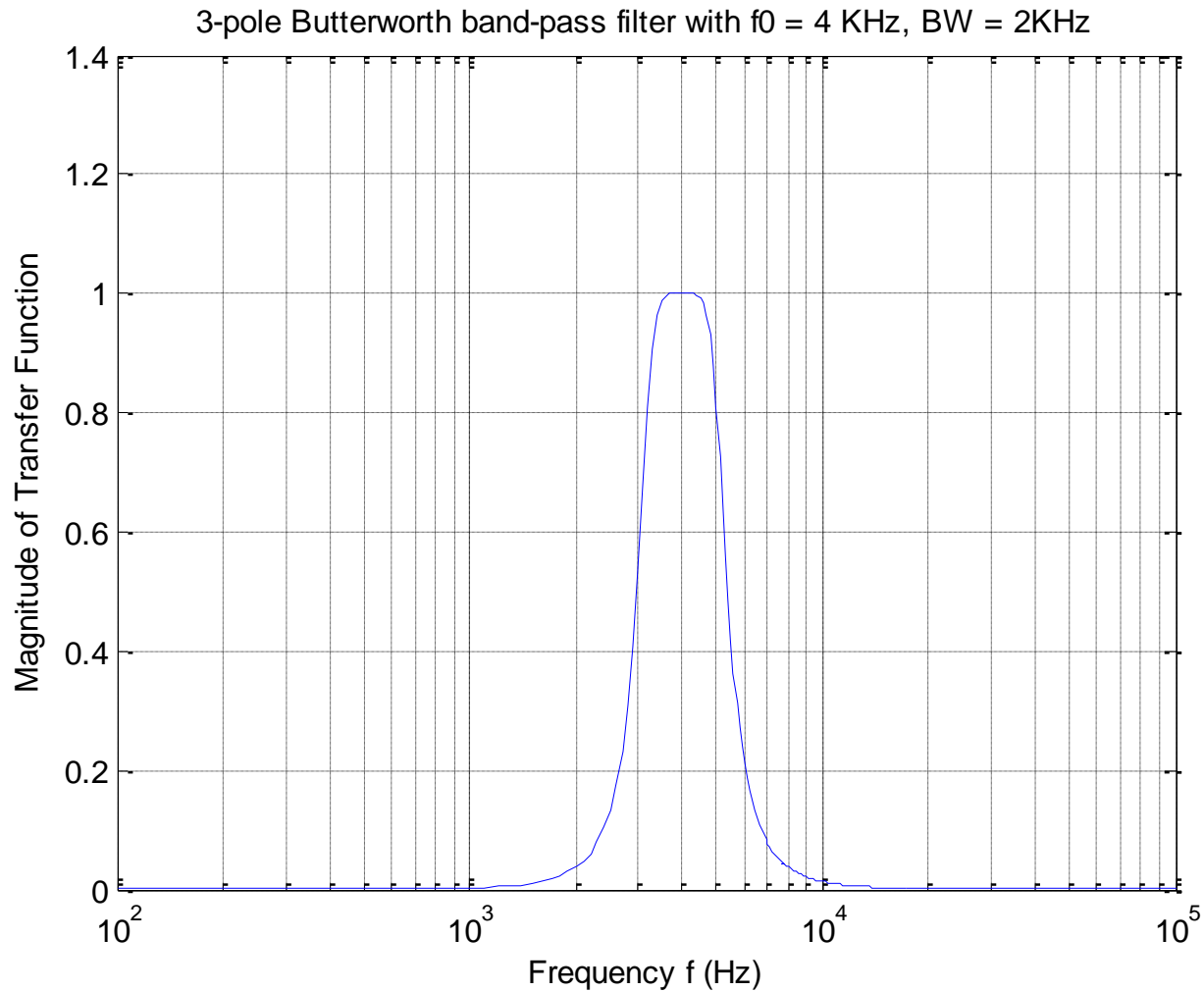




# Band-Elimination (band-stop) Filter

- Use the MATLAB functions **buttap** and **lp2bs** to find the transfer function of a 3-pole Butterworth band-elimination (band-stop) filter with the stop band frequency centered at  $f_0 = 5$  kHz , and bandwidth  $BW = 2$  kHz.

```
[z,p,k]=buttap(3);           % Design 3-pole Butterworth low-pass filter, wcn = 1 r/s
[b,a]=zp2tf(z,p,k);         % Compute num, den coefficients of this filter, wcn=1 r/s
f=100:100:100000;          % Define frequency range to plot
f0=5000;                    % Define centered frequency at 5 kHz
W0=2*pi*f0;                 % Convert centered frequency to r/s
fbw=2000;                   % Define bandwidth
Bw=2*pi*fbw;                % Convert bandwidth to r/s
% Compute numerator and denominator coefficients of desired band stop filter
[bn,an]=lp2bs(b,a,W0,Bw);
% Compute and plot magnitude of the transfer function of the band stop filter
Gsn=freqs(bn,an,2*pi*f);
semilogx(f,abs(Gsn));
grid;
xlabel('Frequency in Hz'); ylabel('Magnitude of Transfer Function');
title('3-pole Butterworth band-elimination filter with f0=5 KHz, BW = 2 KHz')
```

# Band-Elimination (band-stop) Filter

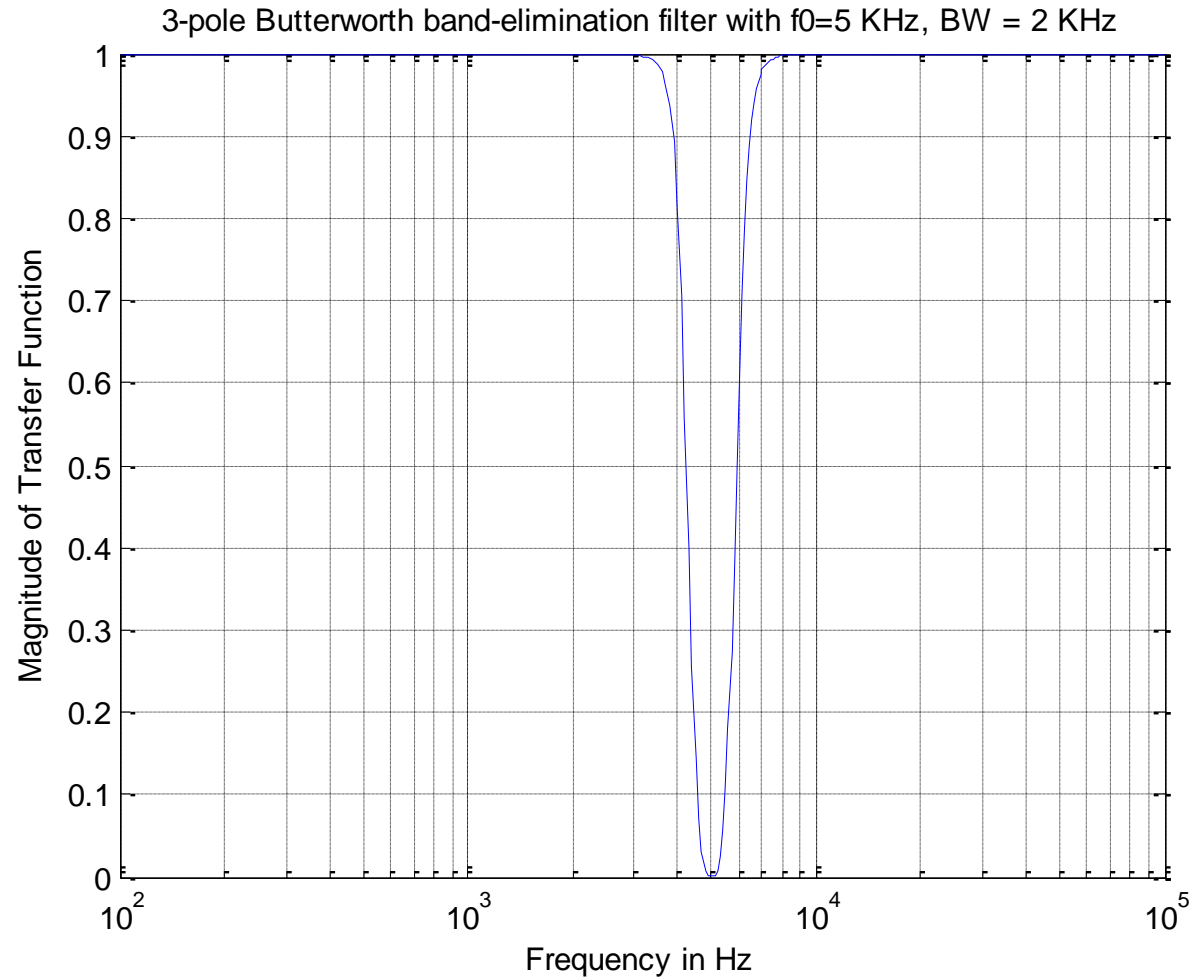

# How to find the minimum order to meet the filter specifications ?

The following functions in Matlab can help you to find the minimum order required to meet the filter specifications:


- `Buttord` for butterworth
- `Cheb1ord` for chebyshev
- `Ellipord` for elliptic
- `Cheb2ord` for inverse chebyshev

# Calculating the order and cutoff frequency of a inverse chebyshev filter

- Design a 4MHz Inverse Chebyshev approximation with  $A_p$  gain at passband corner. The stop band is 5.75MHz with -50dB gain at stop band.

```
clear all;
Fp = 4e6; Wp=2*pi*Fp;
Fs=1.4375*Fp; Ws=2*pi*Fs;
Fplot = 20*Fs;
f = 1e6:Fplot/2e3:Fplot ;
w = 2*pi*f;
Ap = 1;
As = 50;
% Cheb2ord helps you find the order and wn (n and Wn) that
%you can pass to cheby2 command.
[n, Wn] = cheb2ord(Wp, Ws, Ap, As, 's');
[z, p, k] = cheby2(n, As, Wn, 'low', 's');
[num, den] = cheby2(n, As, Wn, 'low', 's');
bode(num, den)
```

# Bode Plot

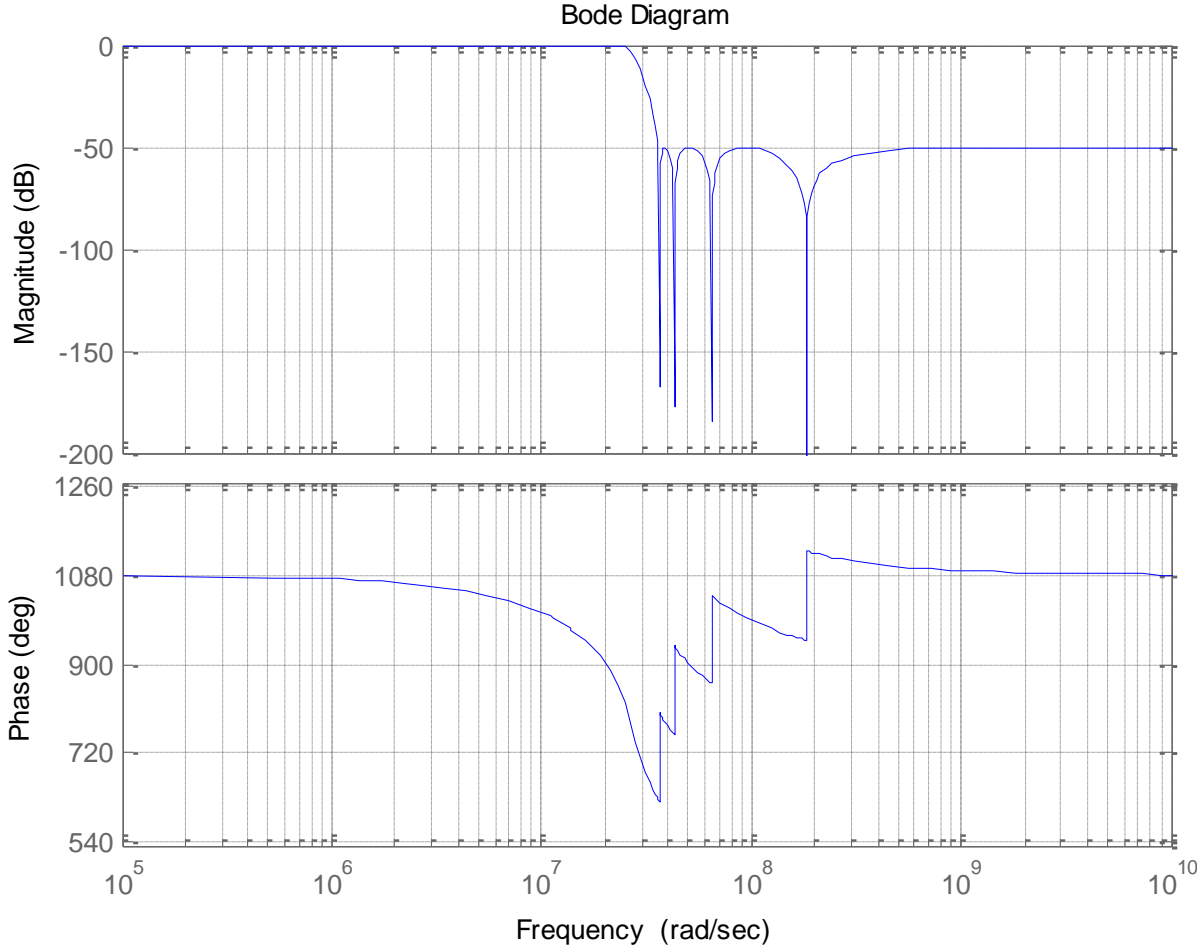

# References

- [1] S. T. Karris, “Signals and Systems with Matlab Computing and Simulink Modeling,” Fifth Edition. Orchard Publications
- [2] Matlab Help Files