

HOMWORK ASSIGNMENT #2

Problem 1. Given the first-order filter

$$H(s) = \frac{K_o \left(1 + \frac{s}{\omega_z}\right)}{1 + \frac{s}{\omega_p}}$$

Obtain the corresponding $H(z)$ using bilinear mapping. Then verify the result for

$$\omega_z = 2\pi \times 50 \text{ K r/s}, \quad \omega_p = 2\pi \times 10 \text{ K r/s}, \quad K_o = 1, \quad f_c = 100 \text{ KHz}$$

- i) Plot $H(s)$ and $H(z)$ in the same figure.
- ii) Obtain the block diagram of $H(z)$.
- iii) Assuming the feedback capacitor $C_F = 10 \text{ pF}$, propose a SC implementation and simulate the SC implementation for a) ideal op amp and b) with a minimum finite GB value that satisfy

$$aGB \frac{T}{2} > 5$$

Plot the results of a) and b). Make comments of your results.


Problem 2. The following transfer function describes a bandpass

$$H^{oo}(Z) = -\frac{K_Q}{1+K_Q} \frac{1-Z^{-1}}{1-2r \cos \Theta Z^{-1} + r^2 Z^{-2}}$$

where

$$r^2 = \frac{1}{1+K_Q}$$
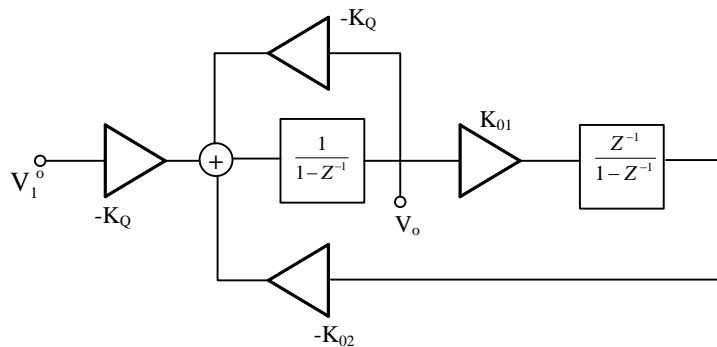
$$-2r \cos \Theta = \frac{2+K_Q - K_{o1} K_{o2}}{1+K_Q}$$



Using MATLAB (SIMULINK) or CADENCE macromodel simulate the filter shown above for $r = 0.9710303$ and $\Theta = 35.957^\circ$

- Assume $GBT \rightarrow \infty$; $T = 1/f_c$
- Assume $GBT = \{15,600\}$

Compare results and make comments. Notice that we are using a normalized $GB_n = GB/f_c = GBT$. Hint make $K_{O1} = K_{O2}$