

- **FULLY CURRENT-MODE**

Input Signal: Current

Output Signal: Current

Basic Building Blocks are:

Inverting Integrators


Inverting (Current Amplifiers)

Primitive Circuit Implementations:



Single Transistor Inverting Amplifier

Simple Current Mirror



Capacitor

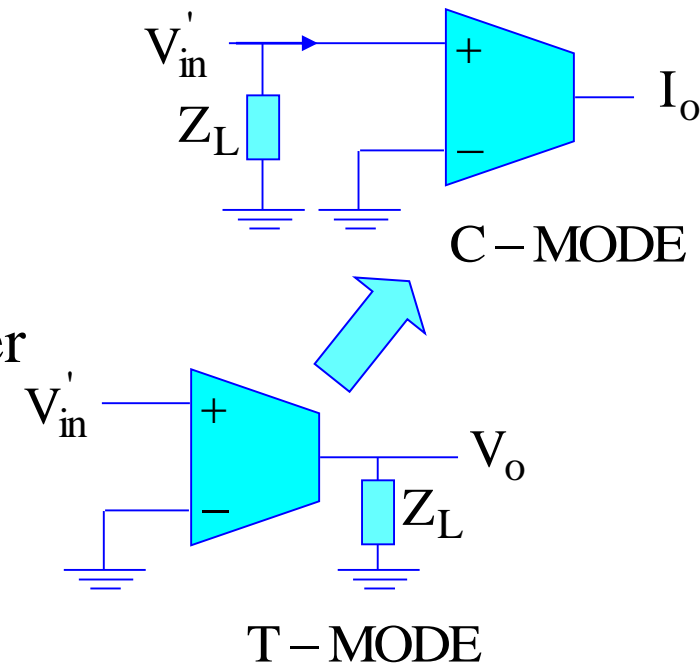


Current-Mode Implementation using OTA's

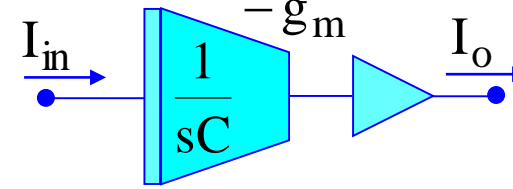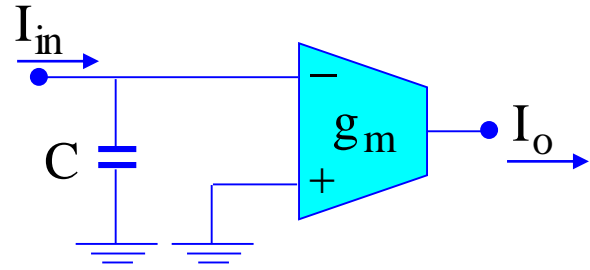

Integrator

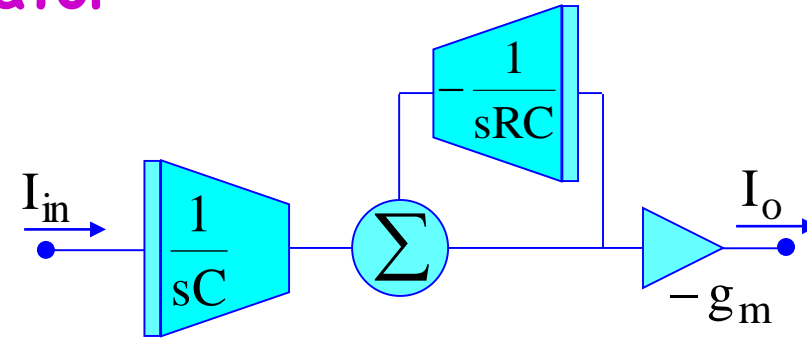
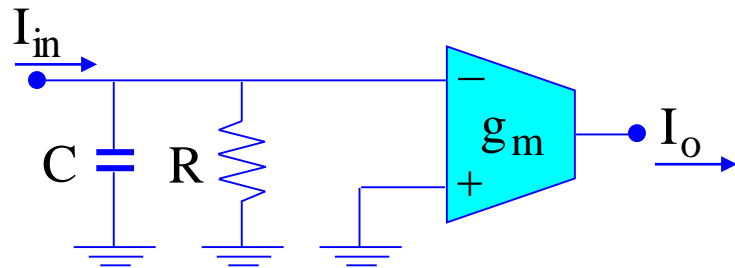


Self Loop Integrator




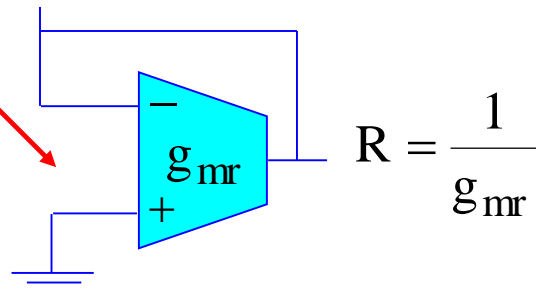


In order to fully obtain the benefits of current-mode techniques simpler circuits with reduced parasitics are desirable.


Primitive CM Circuits

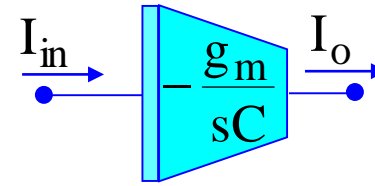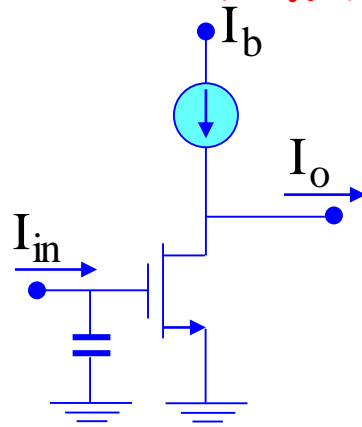

Inverting Integrator

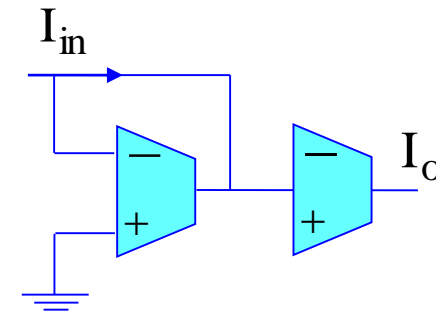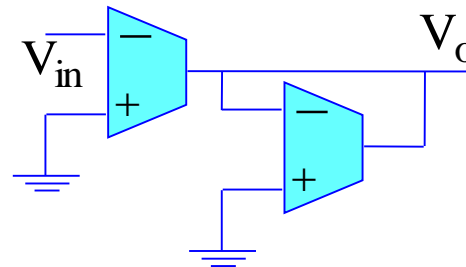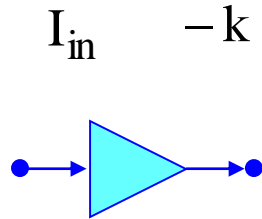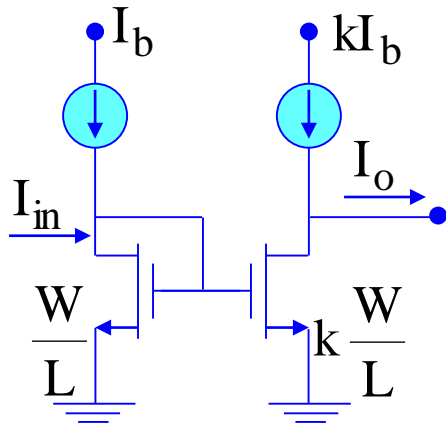

Amplifier (Multiplier by a constant)

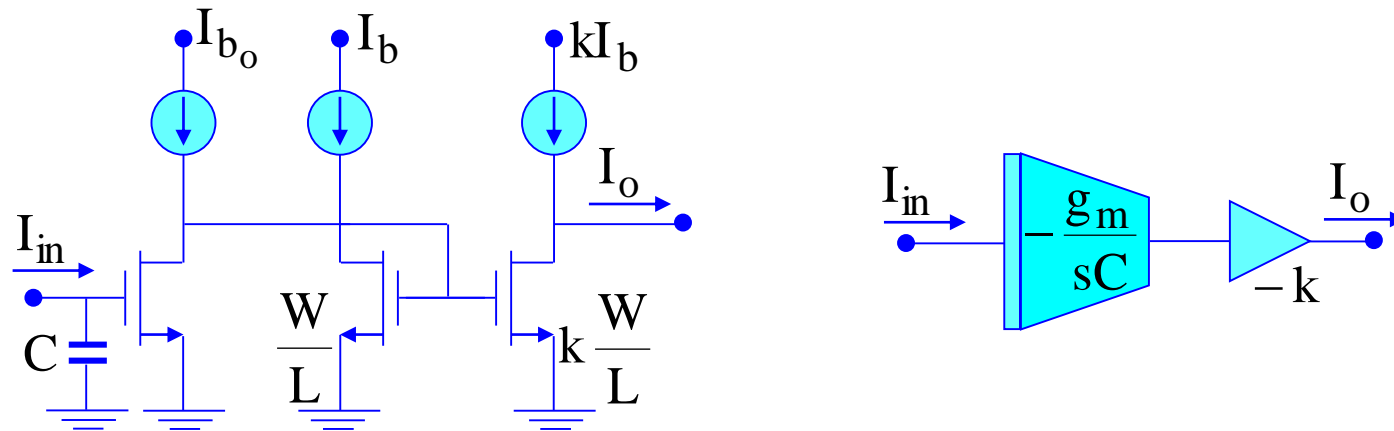

Non-Inverting Integrator

3.3V Power supply

High frequency


Low area

Suitable for digital process

Good PSR

Poor linearity, efficiency (1% THD $\Rightarrow \eta < 4\%$)

Poor voltage gain

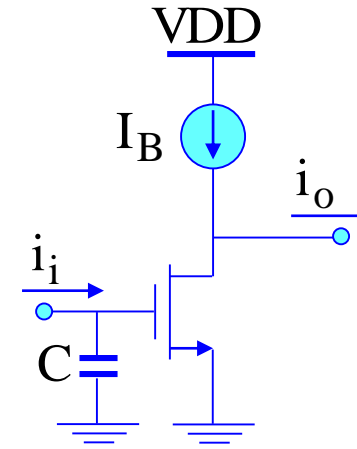

Low power supply (3.3V)

High frequency

Low area



Suitable for digital process


Very good PSR

Good Linearity (differential)

Excellent efficiency ($\approx 100\%$)

Poor common mode rejection

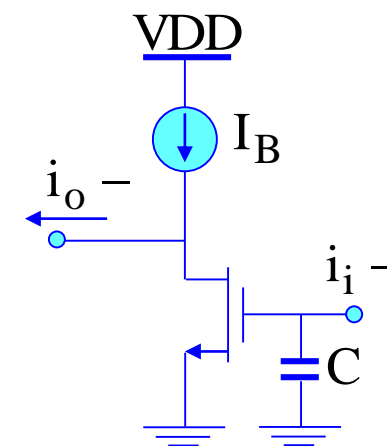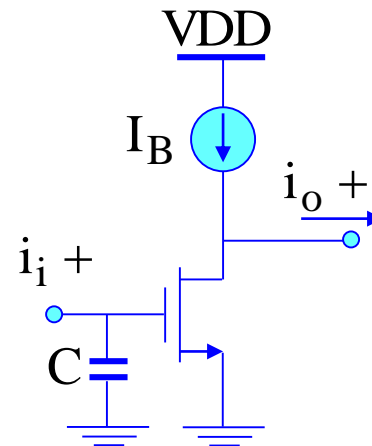

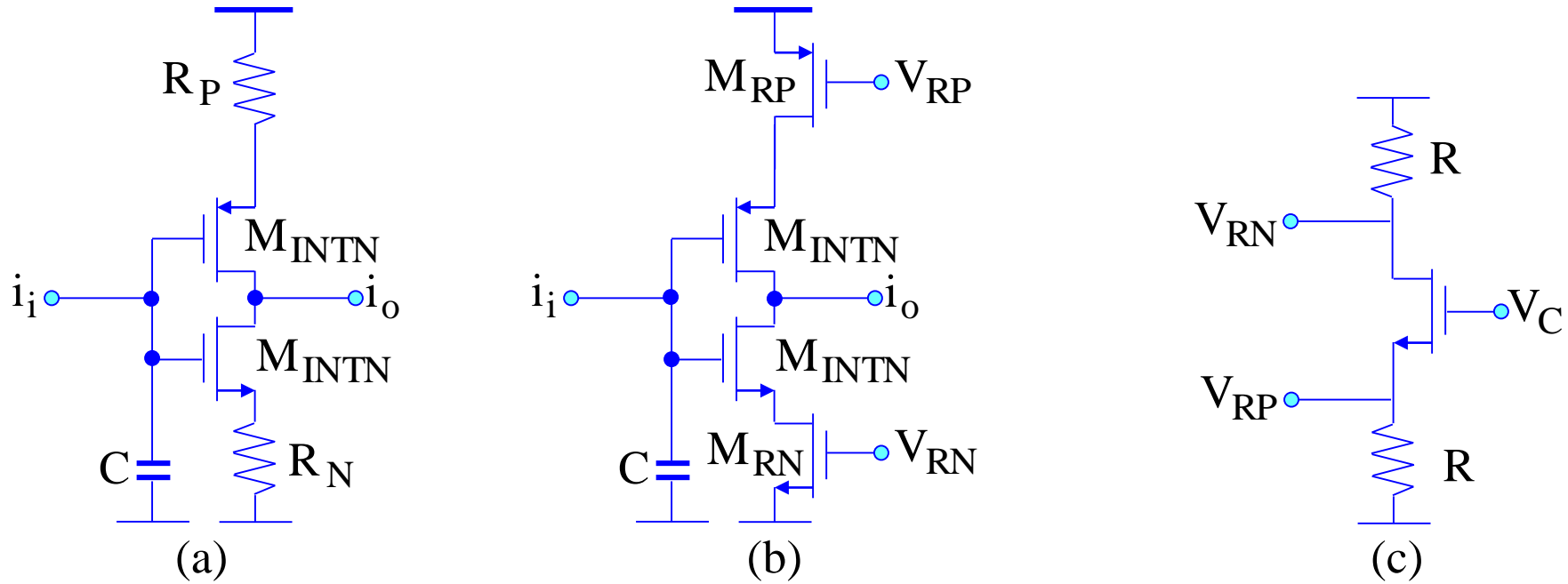

(a) Tunable CMOS class AB integrator (b) Transistor Implementation with M_{rn} and M_{rp} operating in triode region (c) Bias implementation (diffusion or poly resistors).

Linearity sufficient

Very high efficiency ($> 100\%$) \Rightarrow AB, low power

Very high frequency


Small area

Low Power Supply

Linearity dep. on process variations


PSR poor

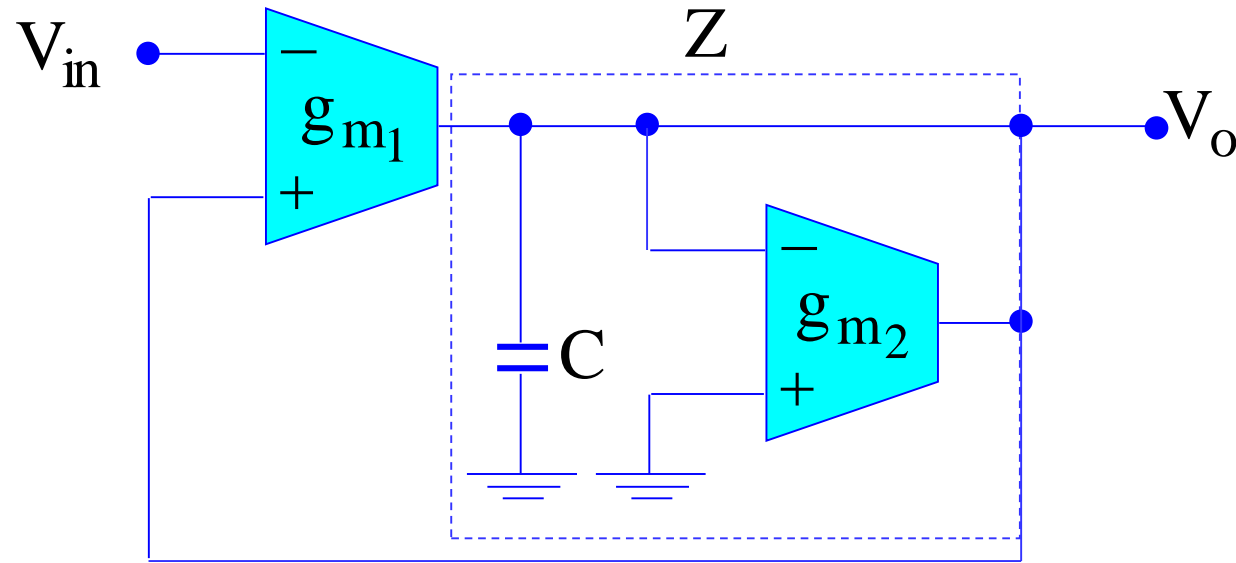How to convert a Lossy Transconductance Integrator With Positive Feedback into a Current-Mode Lossy Integrator




$$\frac{V_o}{V_{in}} = \frac{-g_{m1}Z}{1 - g_{m1}Z} = -\frac{g_{m1}}{sC_2 + (g_{m2} - g_{m1})}$$

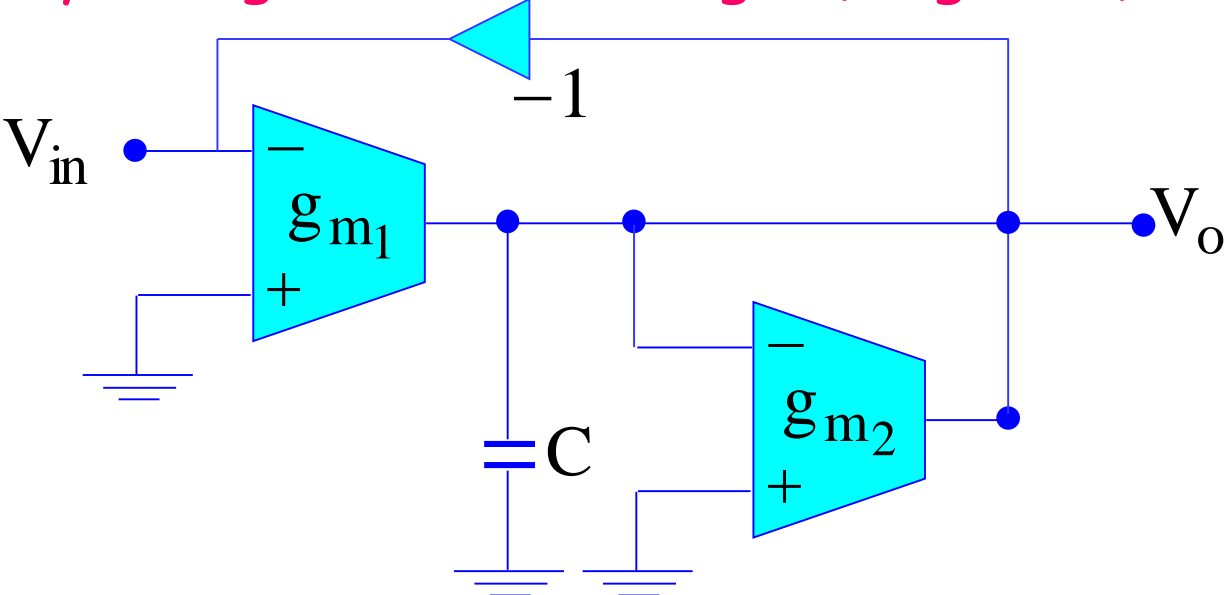
OTA-C Lossy Integrator With Single (Negative) Input OTA's




Current-Mode Version

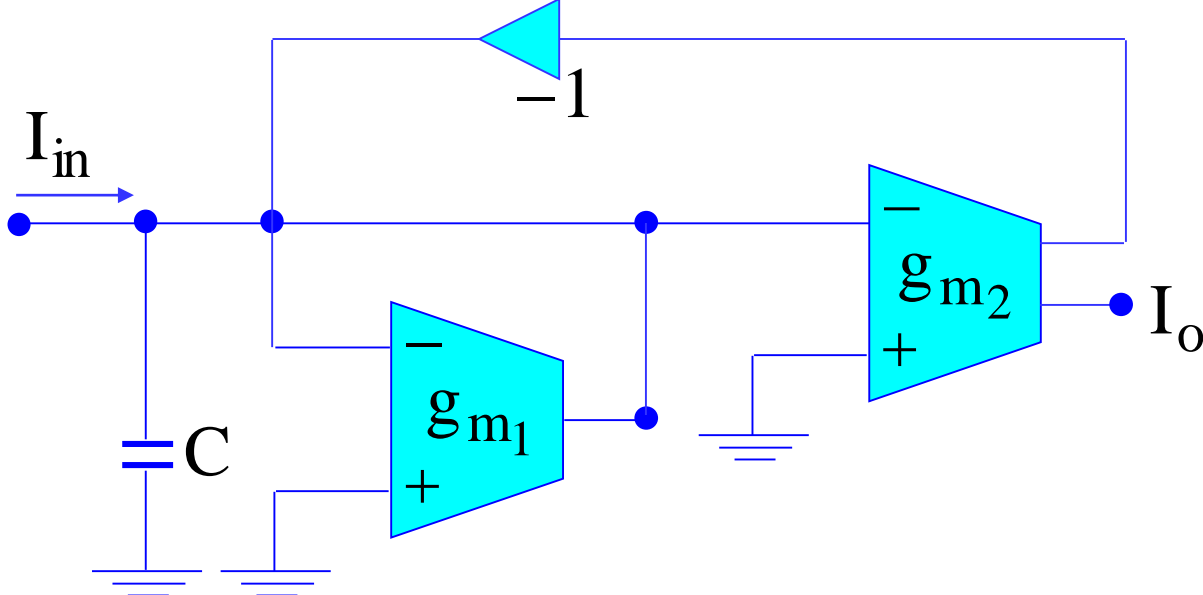


Current-Mode Version

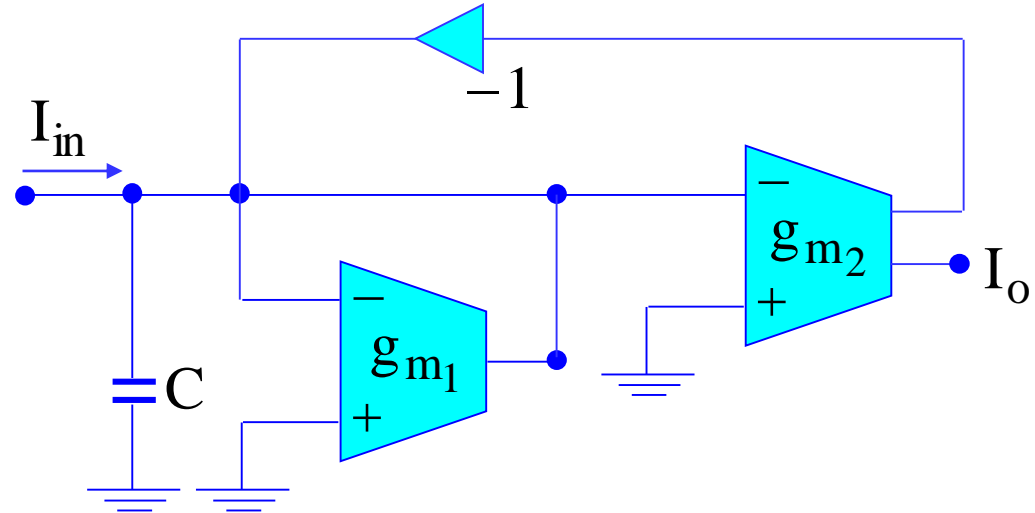


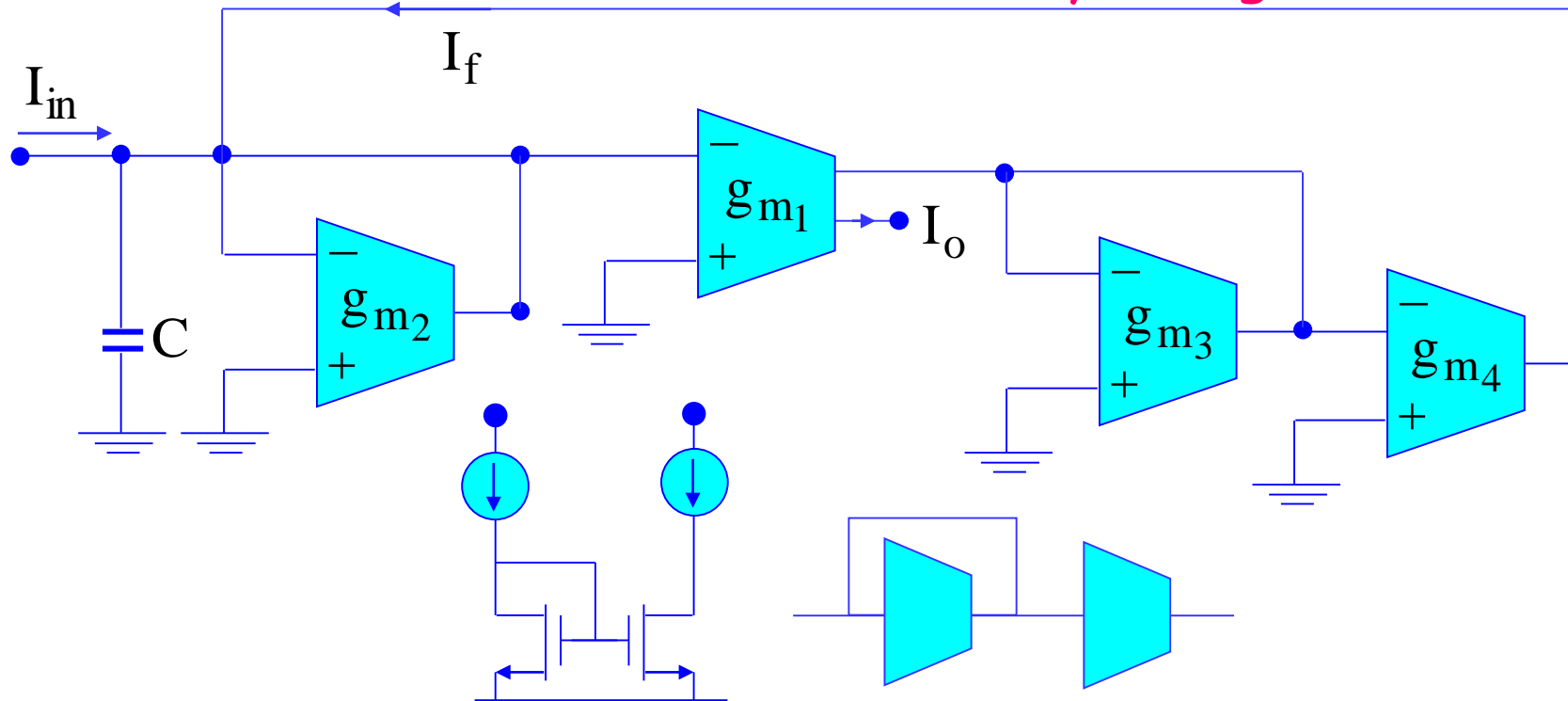Generalized Current-Mode Lossy Integrator



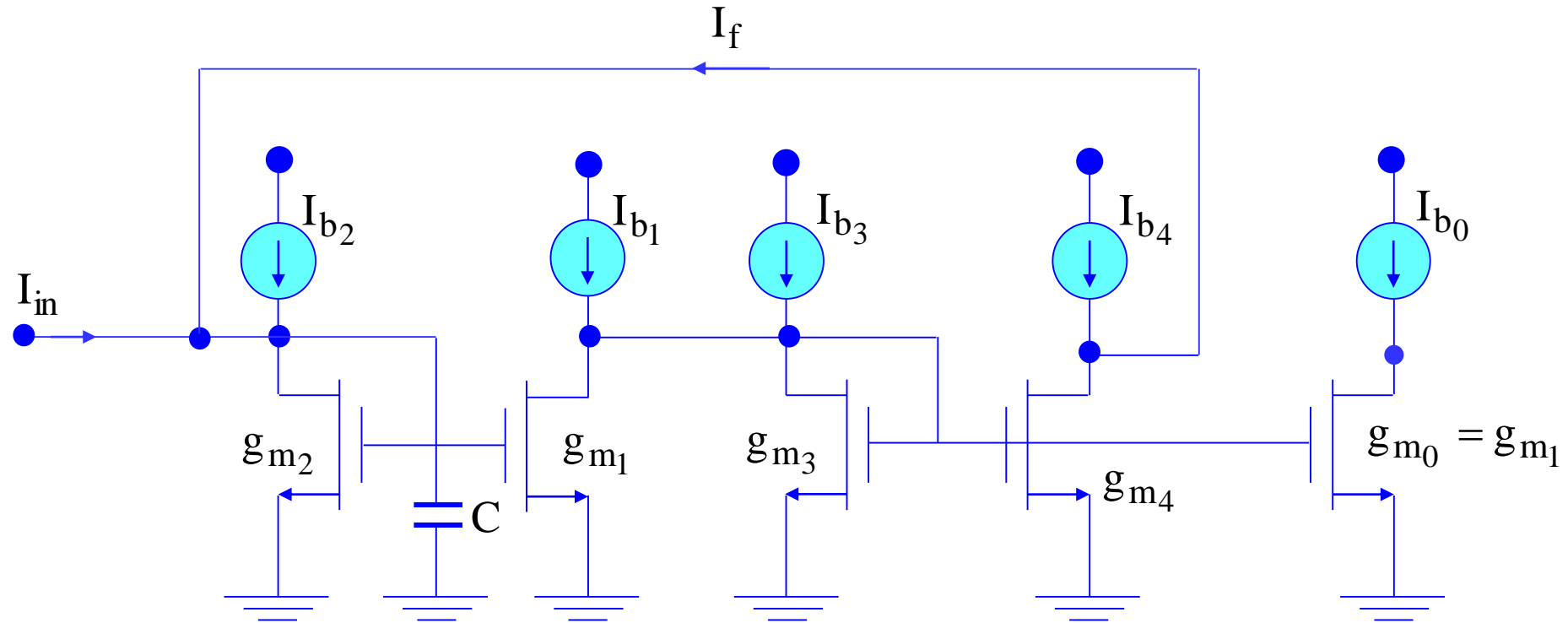


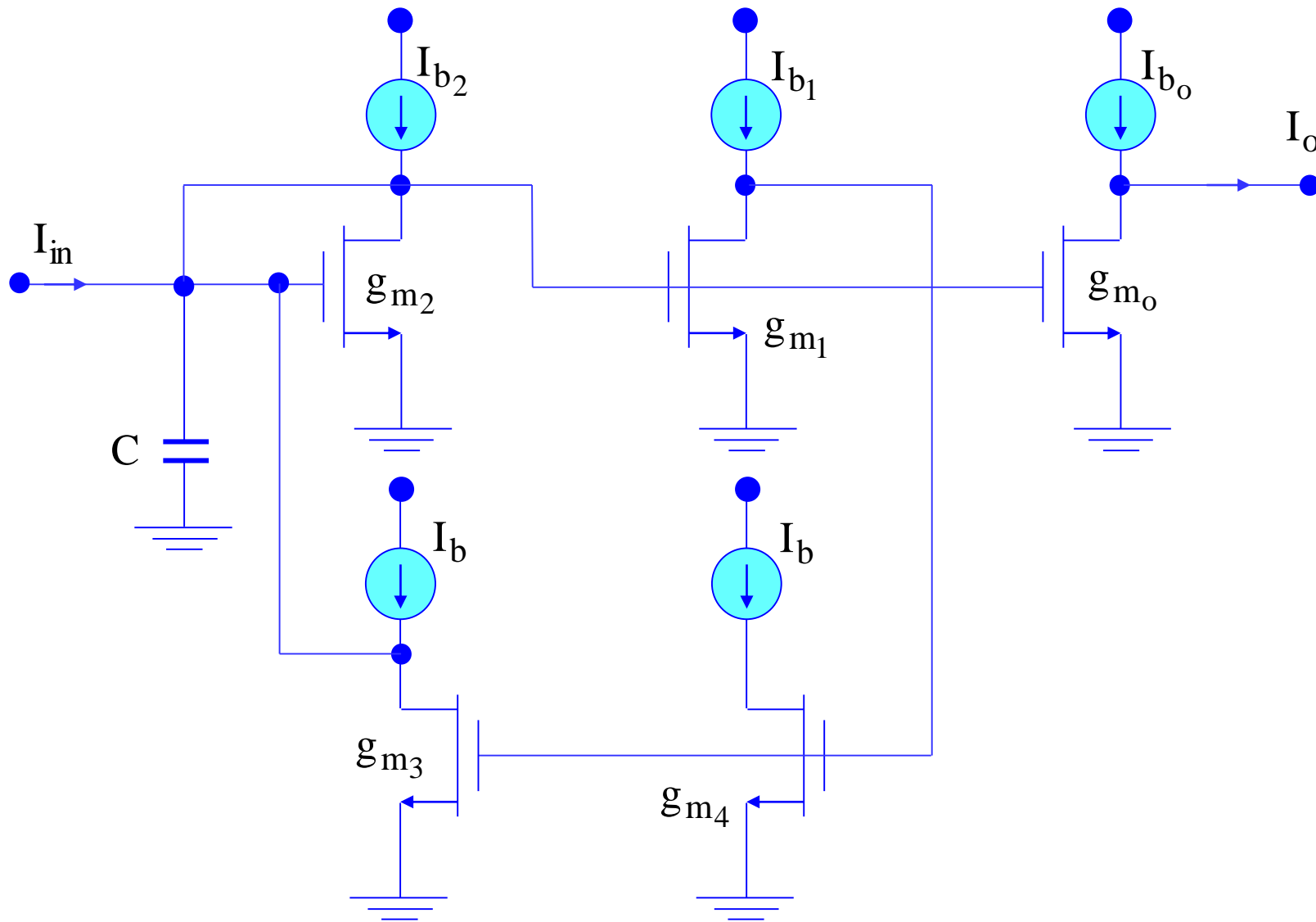Transistor Level Implementation
 CM Lossy (Lossless) Integrator



Redrawing the CM Integrator



Fully Pseudo Differential Integrator

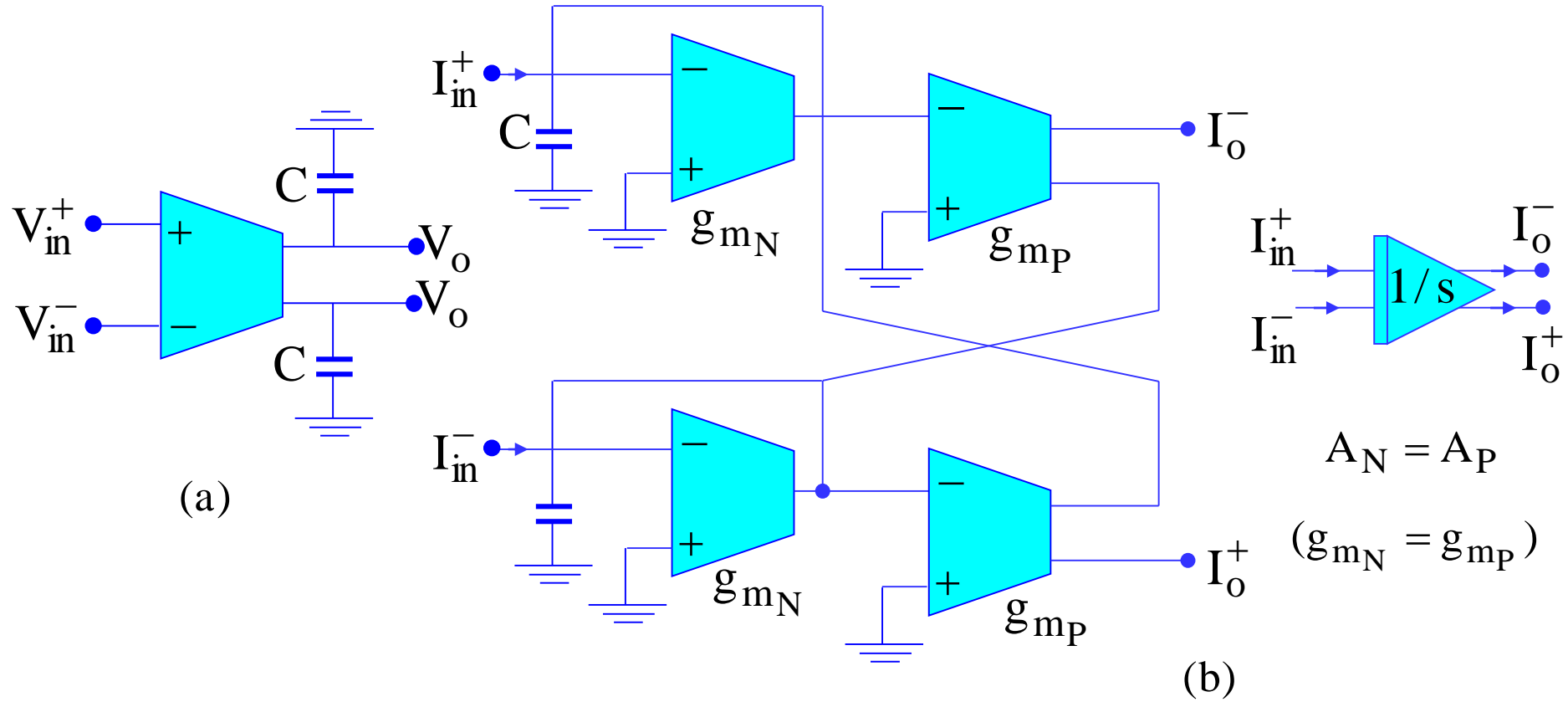

$$A_{dm} = \frac{I_o^+ I_o^-}{I_{in}^+ - I_{in}^-} = \frac{-\omega_u}{s + (A_N + A_P)\omega_u}$$

$$A_{cm} = \frac{I_o^+ + I_o^-}{I_{in}^+ + I_{in}^-} = \frac{-\omega_u}{s + (A_N + A_P)\omega_u}$$

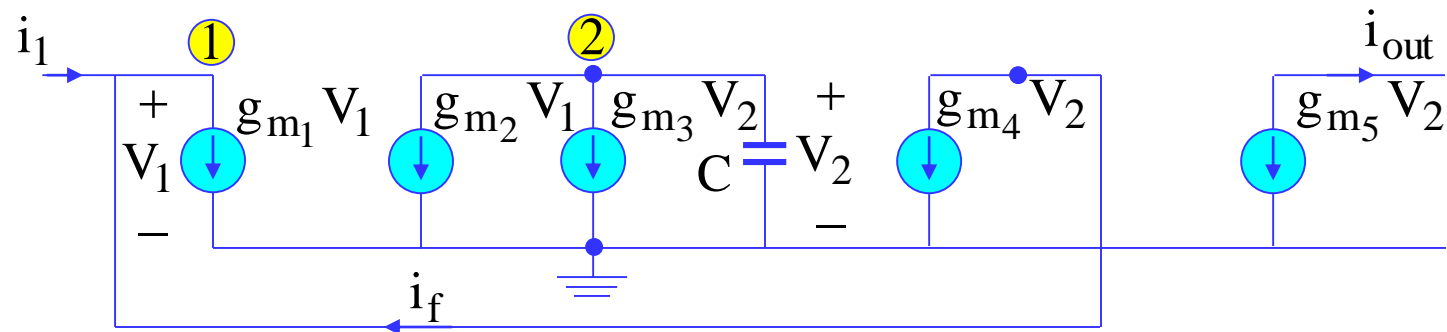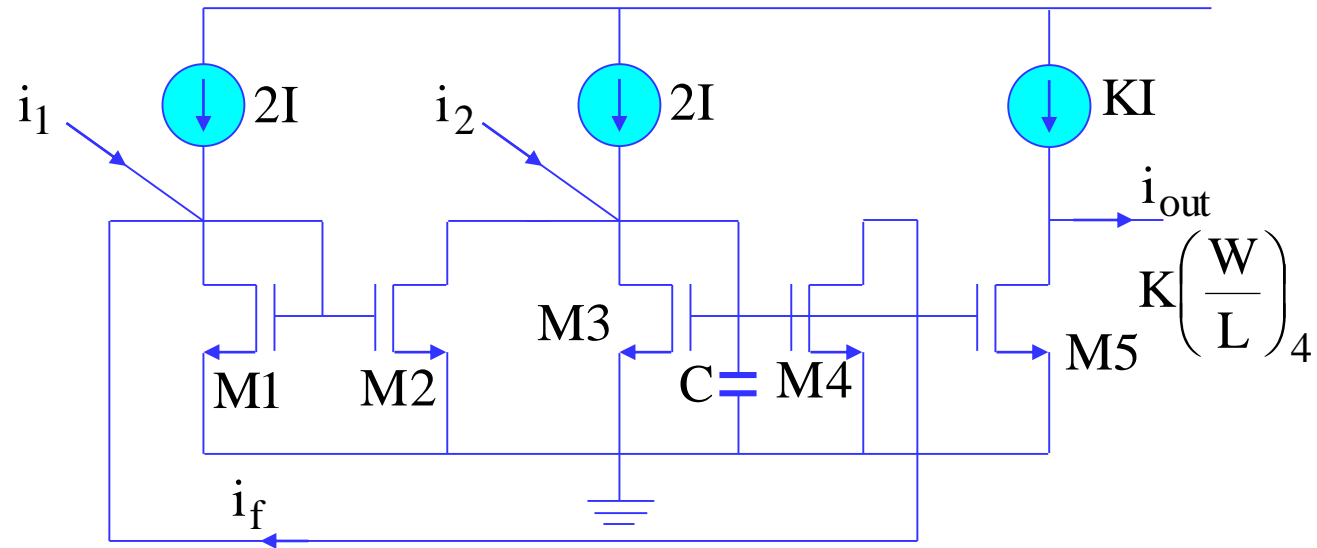Continuous - Time Current-Mode Integrator Based On Current-Mirrors.



$$i_f = \frac{i_1 \frac{g_{m2}}{g_{m1}} - i_2}{g_{m1} (g_{m3} + sC) - g_{m2} g_{m4}} \bullet g_{m1} g_{m4}$$

$$i_f = g_{m1} g_{m4} \frac{i_1 \frac{g_{m2}}{g_{m1}} - i_2}{g_{m1} g_{m3} - g_{m2} g_{m4} + g_{m1} sC}$$

a) Lossless Integrator

$$g_{m1} = g_{m2} \quad \text{and} \quad g_{m3} = g_{m4}$$

$$i_f = \frac{g_{m4}}{sC} (i_1 - i_2)$$

$$i_{\text{out}} = K \frac{g_{m4}}{sC} (i_1 - i_2)$$

b) Lossy Integrator

$$g_{m_1} g_{m_3} > g_{m_2} g_{m_4} \quad , \quad g_{m_1} = k g_{m_2} \quad , \quad g_{m_3} = k g_{m_4}$$

$$i_f = \frac{k}{k^2 - 1} \frac{k i_1 - i_2}{1 + \frac{sC}{g_{m_4}} \frac{k^2 - 1}{k}} \quad , \quad k > 1$$

i.e. $k = 2$

$$i_f = \frac{2}{3} \frac{2i_1 - i_2}{1 + \frac{sC}{g_{m_4}} \frac{3}{2}}$$

If the parasitic capacitances and the output conductances are considered, then

$$i_f = \frac{-k_1(s - z_1)i_1}{(s + p_1)(s + p_2)} - \frac{k_2(s + z_2)}{(s + p_1)(s + p_2)}$$

Where

$$k_1 = g_o / C_1 \quad , \quad k_2 = g_m / C_2$$

$$p_1 = 4g_o / C_2 \quad , \quad p_2 = g_m / C_1$$

$$z_1 = \frac{g_m}{C_2} \frac{g_m}{g_o} \quad , \quad z_2 = \frac{g_m + g_o}{C_1}$$


All transistors are equal, and C_1 and C_2 are the lumped nodal capacitances associated with nodes 1 and 2. Note that p_1 moves from the origin to

$$p_1 \rightarrow \frac{\omega_o}{\alpha} = \frac{\frac{g_{m3}}{C_2}}{\frac{g_m}{4g_o}} = \frac{g_{m3}}{g_m} \frac{4g_o}{C_2}$$

And

$$Q = -\frac{g_{m1}}{g_{m3}} \frac{C_2}{C_1}$$

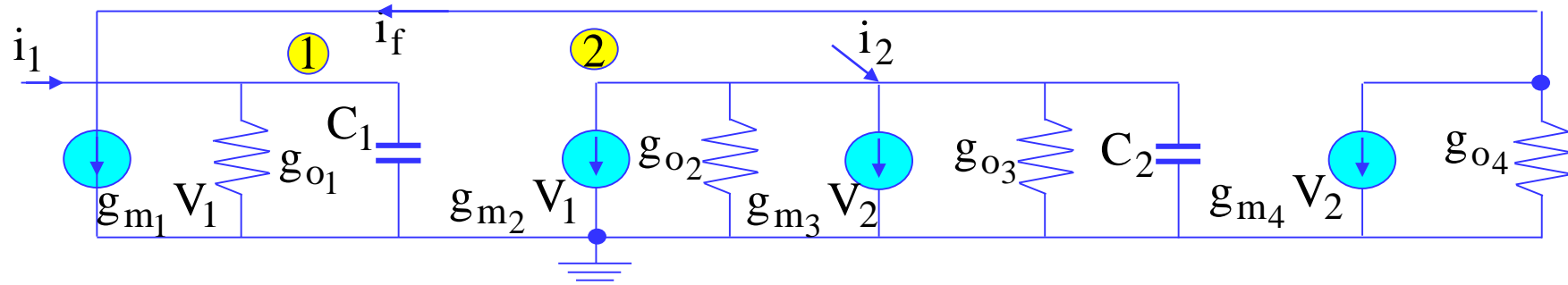Let's consider the input and output impedance,



$$Z_{\text{in}} = \left. \frac{V_1}{i_1} \right|_{i_2 = 0} = \frac{g_{m_3} + g_{o_2} + g_{o_3} + sC_2}{-g_{m_4}g_{m_2} + (g_{m_1} + g_{o_1} + g_{o_4} + sC_1)(g_{m_3} + g_{o_2} + g_{o_3} + sC_2)}$$

$$Z_{\text{in}} = \left. \frac{V_1}{i_1} \right|_{i_2 = 0} \approx \frac{g_{m_3} (1 + sC_2 / g_{m_3})}{-g_{m_4}g_{m_2} + g_{m_1}g_{m_3} + s(C_2g_{m_1} + C_1g_{m_3}) + s^2C_1C_2}$$

a) Lossless Integrator

$$z_{\text{in}}(0) \cong \frac{g_{m3}}{-g_{m4}g_{m2} + g_{m1}g_{m3}} \left| \begin{array}{l} g_{m1} = g_{m2} \\ g_{m3} = g_{m4} \end{array} \right. \rightarrow \infty$$

b) Lossy Integrator

$$z_{\text{in}}(0) \cong \frac{k^2}{k^2 - 1} \frac{1}{g_{m1}}, \quad k > 0$$

$$z_{\text{o}}(0) \cong \frac{1}{g_{o5}}$$