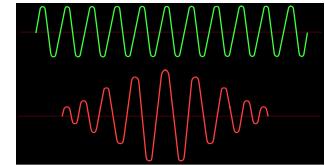


Oscillators: Fundamentals and Implementations


- Oscillator is a system that is able to produce independently bounded and permanent oscillations of at least one of the variables that describe it.
- Types of Oscillators:
 - **Periodic.** This oscillator has an spectrum consisting of a fundamental frequency plus and infinite number of harmonics.
 - **Pseudo-periodic.** The spectrum consists of more than one frequencies not related to each other.
 - **Chaotic.** The spectrum of the response is flat. That is, it contains frequency components of all frequencies.

For sinusoidal oscillators a figure of merit is the distortion which is characterized by the Total Harmonic Distortion (THD)

SINUSOIDAL OSCILLATORS



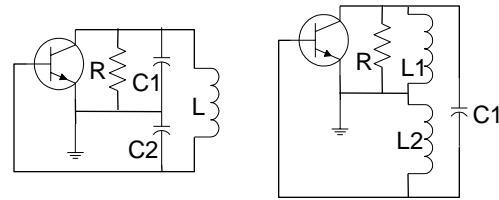There are a number of circuit implementations of sinusoidal oscillators. In traditional communication circuits oscillators use one transistor, R's, C's and sometimes inductors. These filters were often used in RF circuits. Current RF oscillators used either ring oscillators or LC tuned oscillators. The last one consists of differential pairs and inductor(s) and capacitor(s)



In these notes we will first focus more on oscillators based on *state-variable structures* (SVS). We will discuss several implementations and the design procedures.

SINUSOIDAL OSCILLATORS



A **sinusoidal** oscillator is composed of:

1. A linear circuit that sets the oscillation frequency.
2. An active element that gains power at the frequency of oscillation.
3. A nonlinear mechanism to stabilize the amplitude.

Nonlinear
Mechanism

Static, when its input-output characteristic is fixed in time, as in a hard limiting device or an amplifier nonlinear gain.
Dynamic, when its characteristic changes in time as in an AGC.

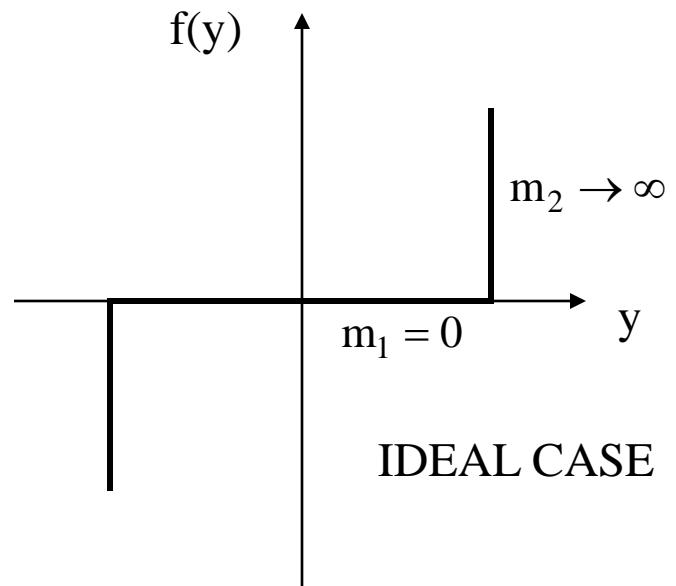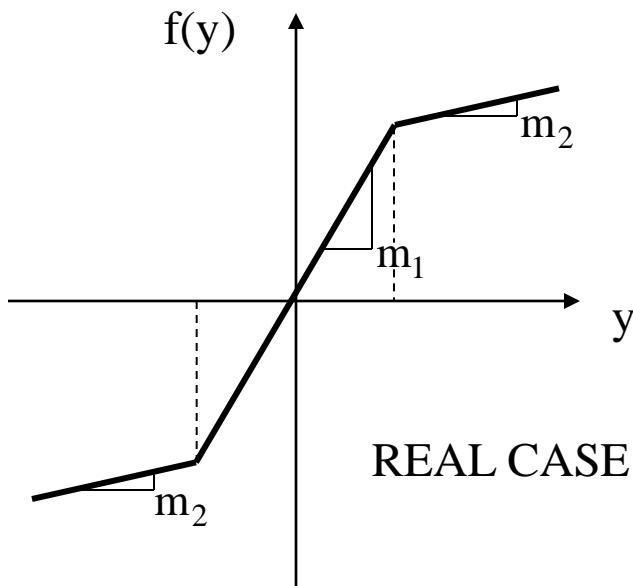Examples of Nonlinear (static) Characteristics




There are a number of topologies yielding sinusoidal oscillators. In our discussion we will first present two popular types in frequency ranges below hundreds of MHz:

i) **Quadrature Oscillator**

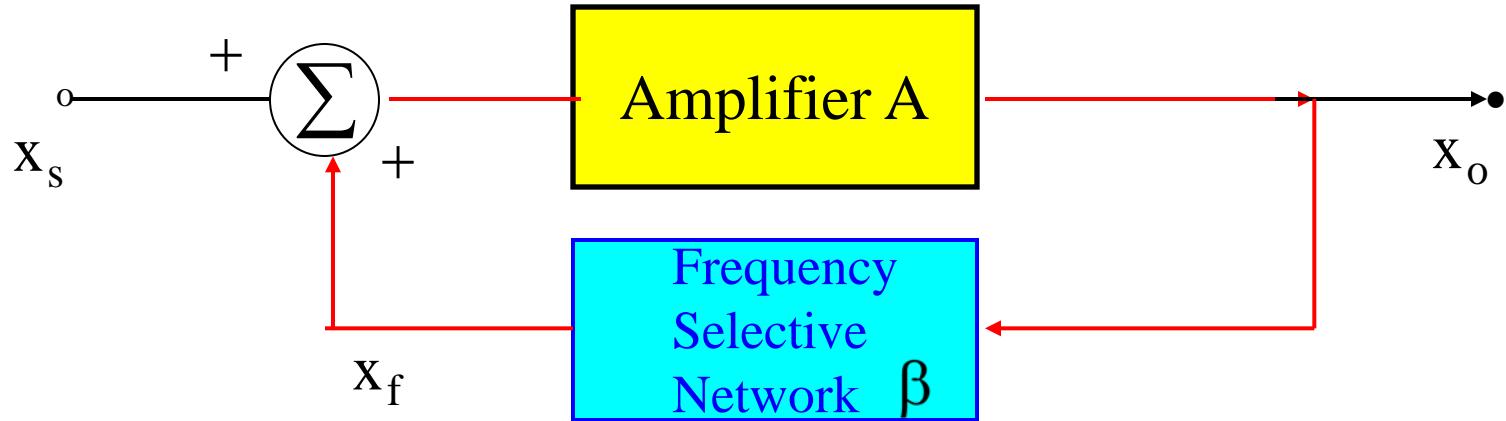ii) **Bandpass - based**

OSCILLATORS

Fundamentals. Linear Aspects: Oscillation conditions.



$$A_f = \frac{x_o}{x_s} = \frac{A}{1 - \beta A} = \frac{A(s)}{1 - \beta(s) A(s)}$$


$$D(s) = 1 - \beta(s) A(s) = 1 - L(s)$$

$$L(j\omega_o) \triangleq A(j\omega_o) \beta(j\omega_o) = 1 \quad \text{Barkhausen Criteria}$$


Note that for the circuit to oscillate at one frequency the oscillation criterion should be satisfied at one frequency only; otherwise the resulting waveform will not be a simple sinusoid.

Need of Nonlinear Amplitude Control


Location of poles

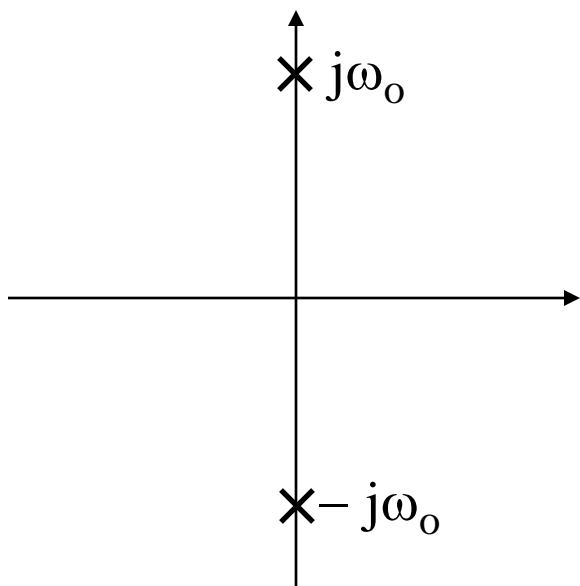

Not practical
why?

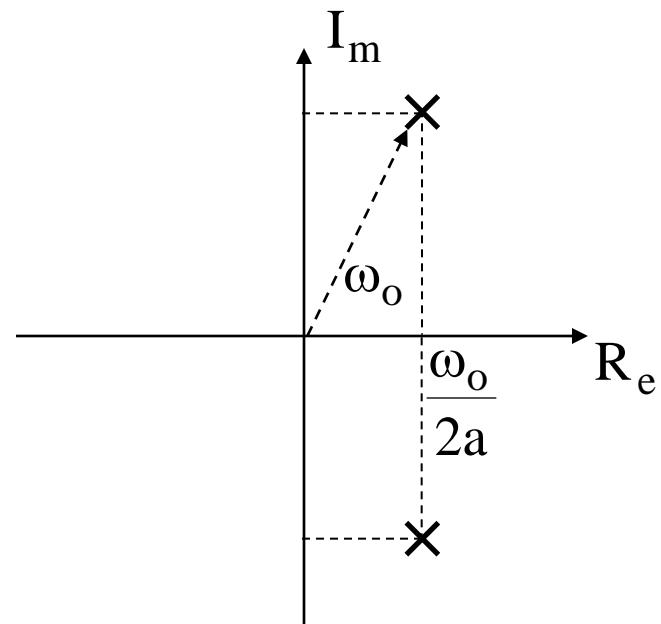


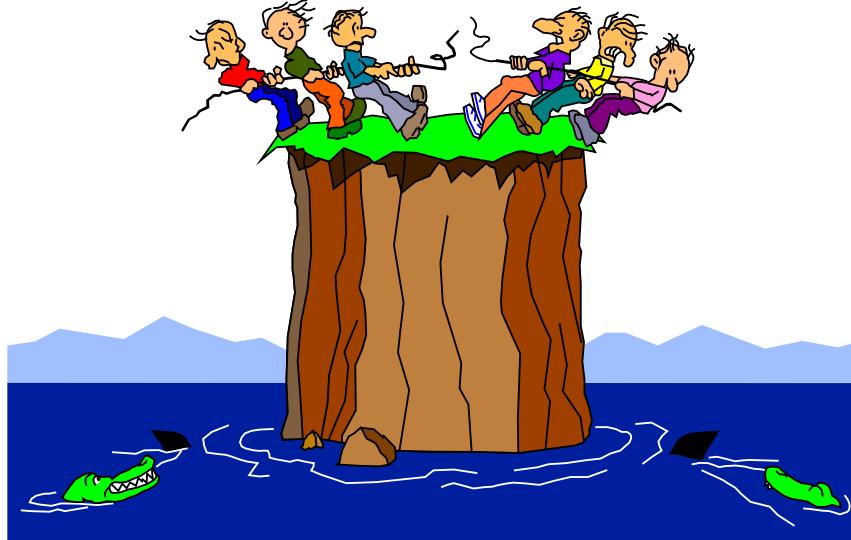Practical.
How do you push
the poles into the
 $j\omega$ axis?




In the ideal case this is easy to design, but in the real case there are a lot of system parameters that can change the poles due to their physical characteristics.

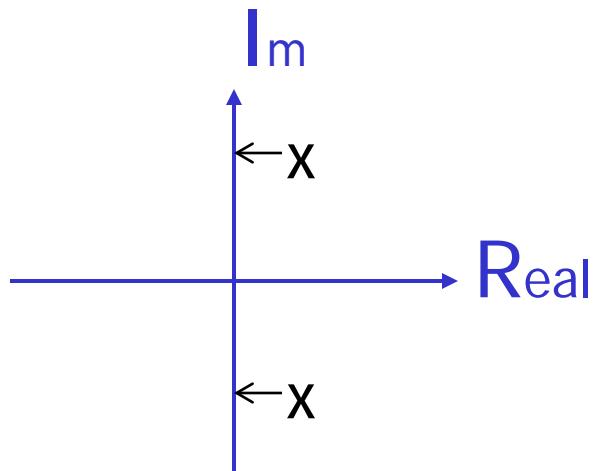Therefore, the poles should not lie on the imaginary axis. One should design the poles so that they lie in the right half of the s-plane. This creates positive feedback and guarantees that the circuit will oscillate. How far should we place the poles ?



BP Based Oscillator

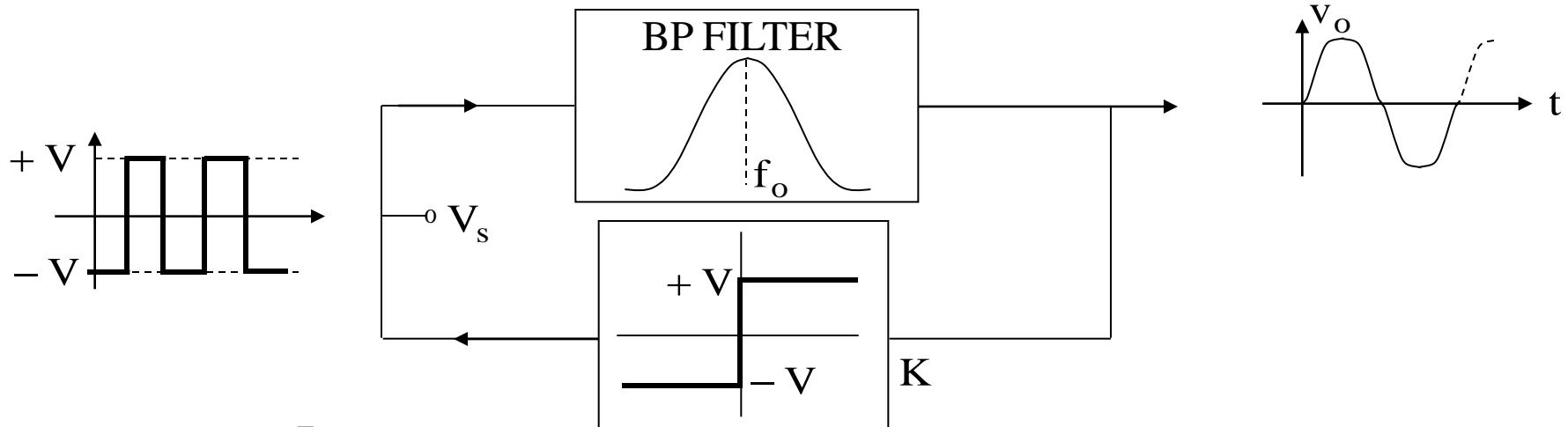

Let

$$H_{BP}(s) = \frac{K_1 s}{s^2 + \frac{\omega_o}{Q} s + \omega_o^2}$$

$$D(s) = 1 - K H_{BP}(s)$$



$$\left(s^2 + \frac{\omega_o}{Q} s + \omega_o^2 \right) D(s) = s^2 + \frac{\omega_o}{Q} s + \omega_o^2 - K K_1 s$$

Characteristic Equation


$$s^2 - s \left(K K_1 - \frac{\omega_o}{Q} \right) + \omega_o^2$$

$$K K_1 > \frac{\omega_o}{Q} \quad \text{i.e. positive feedback}$$

A bandpass based Sinusoidal Oscillator

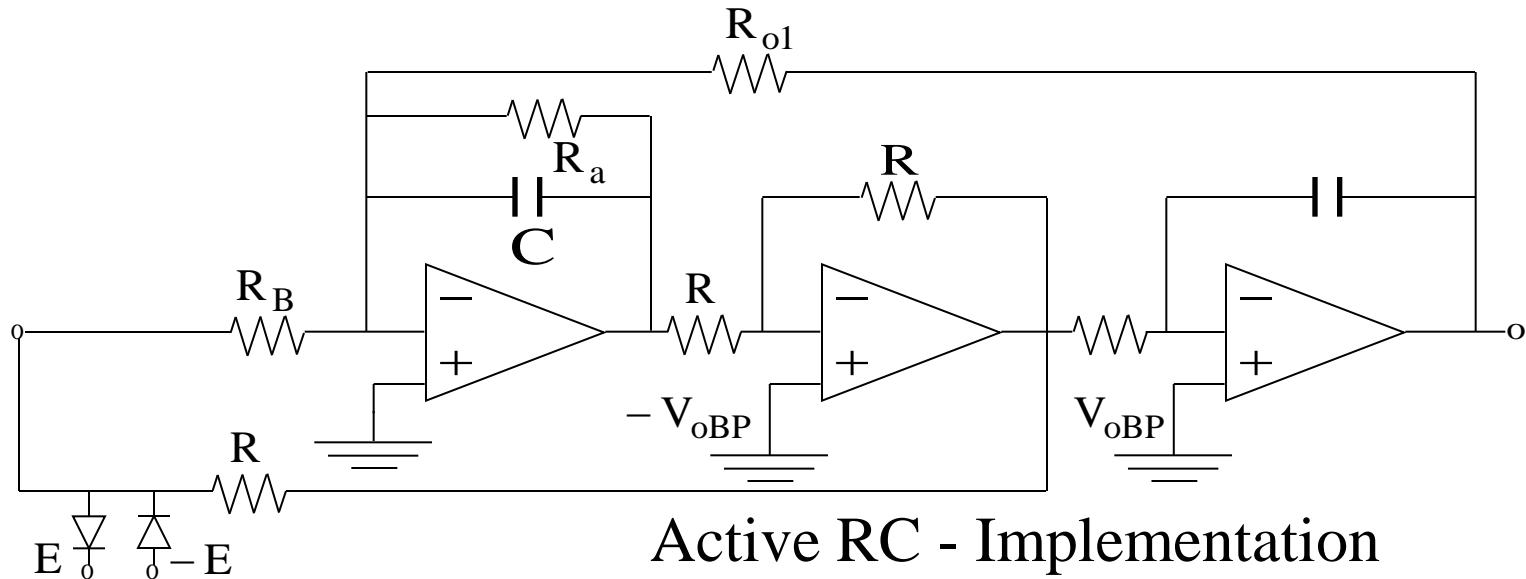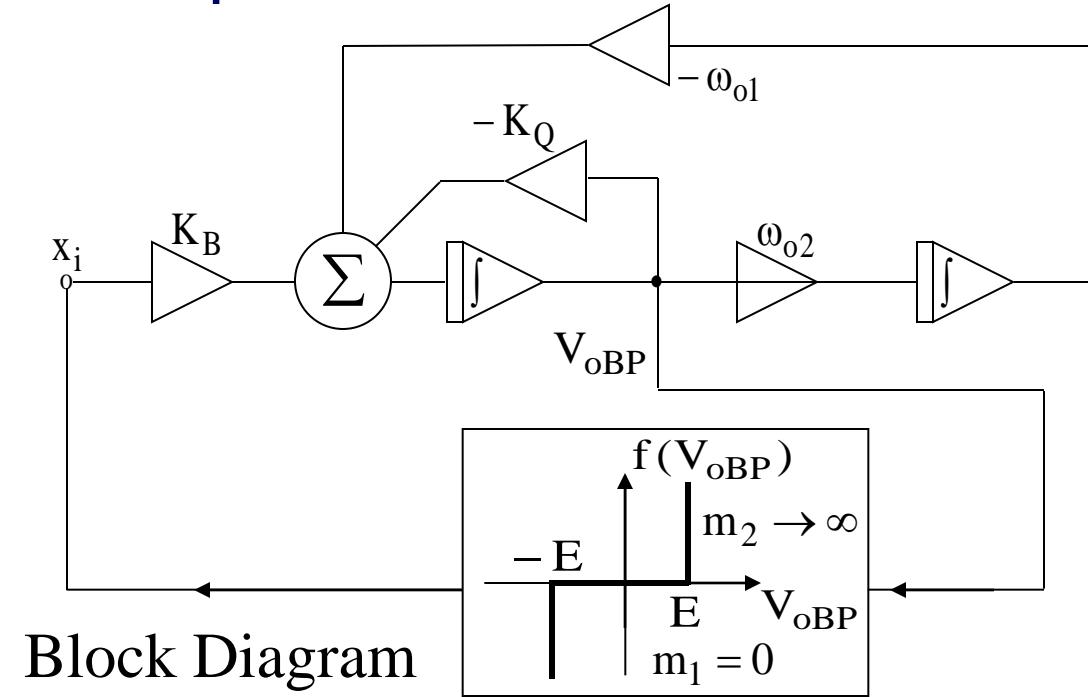

BP Oscillator

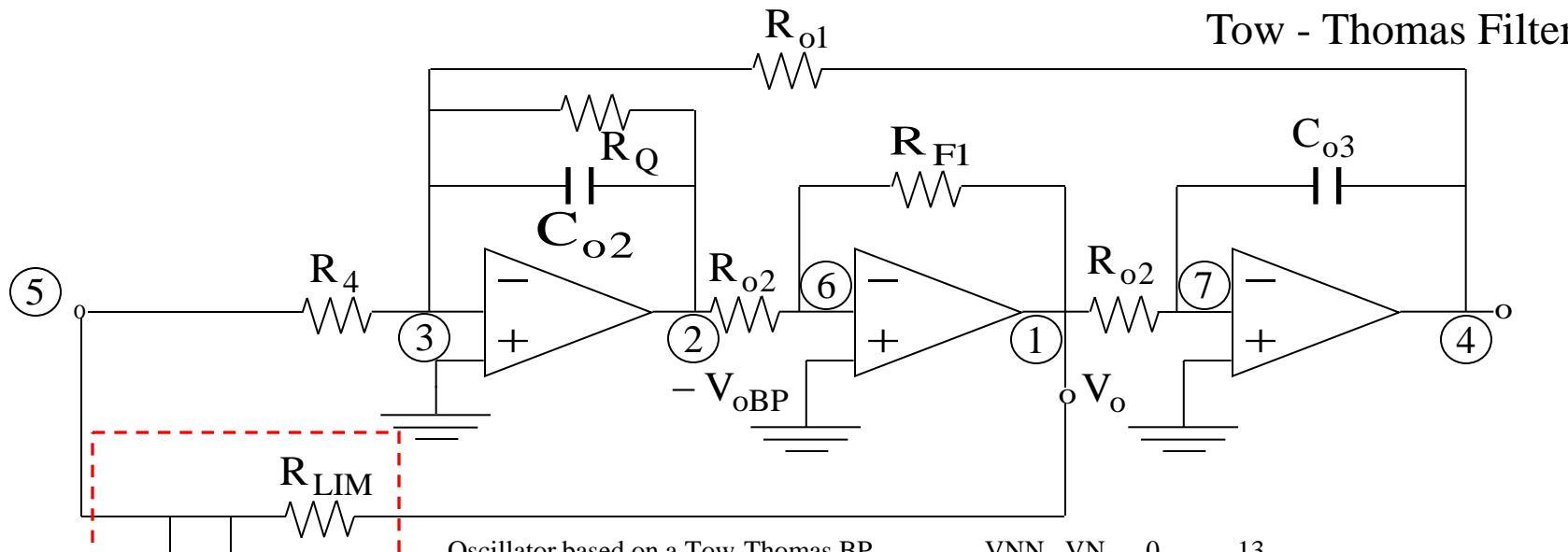

Oscillator based on a Tow-Thomas BP

R4 5 3 16K

R01 4 3 1K

RQ 2 3 16K

RF1 6 1 1K

R02 1 7 1K

C02 3 2 0.1591549U

R03 2 6 1K

C03 7 4 0.1501549U

.SUBCKT OPAMP vi- vi+ v0+ v0-

*

*

RIN vi- vi+ 10E6

EIN 1 0 vi+ vi- 2E05

R3DB 1 2 1K

C3DB 2 0 0.159E-04

EOUT 3 VO- 2 0 1

DP 2 VP DIODE

DN VN 2 DIODE

VPP VP 0 13

VNN VN 0 -13

ROUT 3 v0+ 75.

.MODEL DIODE D(IS=10E-08 N=0.01)

.ENDS OPAMP

* DESCRIPTION OF OPAMPS AND THEIR NODES

XOP1 3 0 2 0 OPAMP

XOP2 6 0 1 0 OPAMP

XOP3 7 0 4 0 OPAMP

*LIMITER CIRCUIT DESCRIPTION

RLIM 1 5 200

DP 5 VP DL

DN VN 5 DL

.MODEL DL D (IS=10E-09 N=0.0001)

VNL VN 0 -2

VPL VP 0 2

.TRAN 5U 20m UIC

.FOURIER 57 V(1) V(2) V(4)


.IC V(1)=2 V(2)=-2 V(4)=-2 V(5)=2

.OPTIONS POST


.END

OSCILLATOR BASED ON A TOW-THOMAS BP

95/04/22 15:41:53

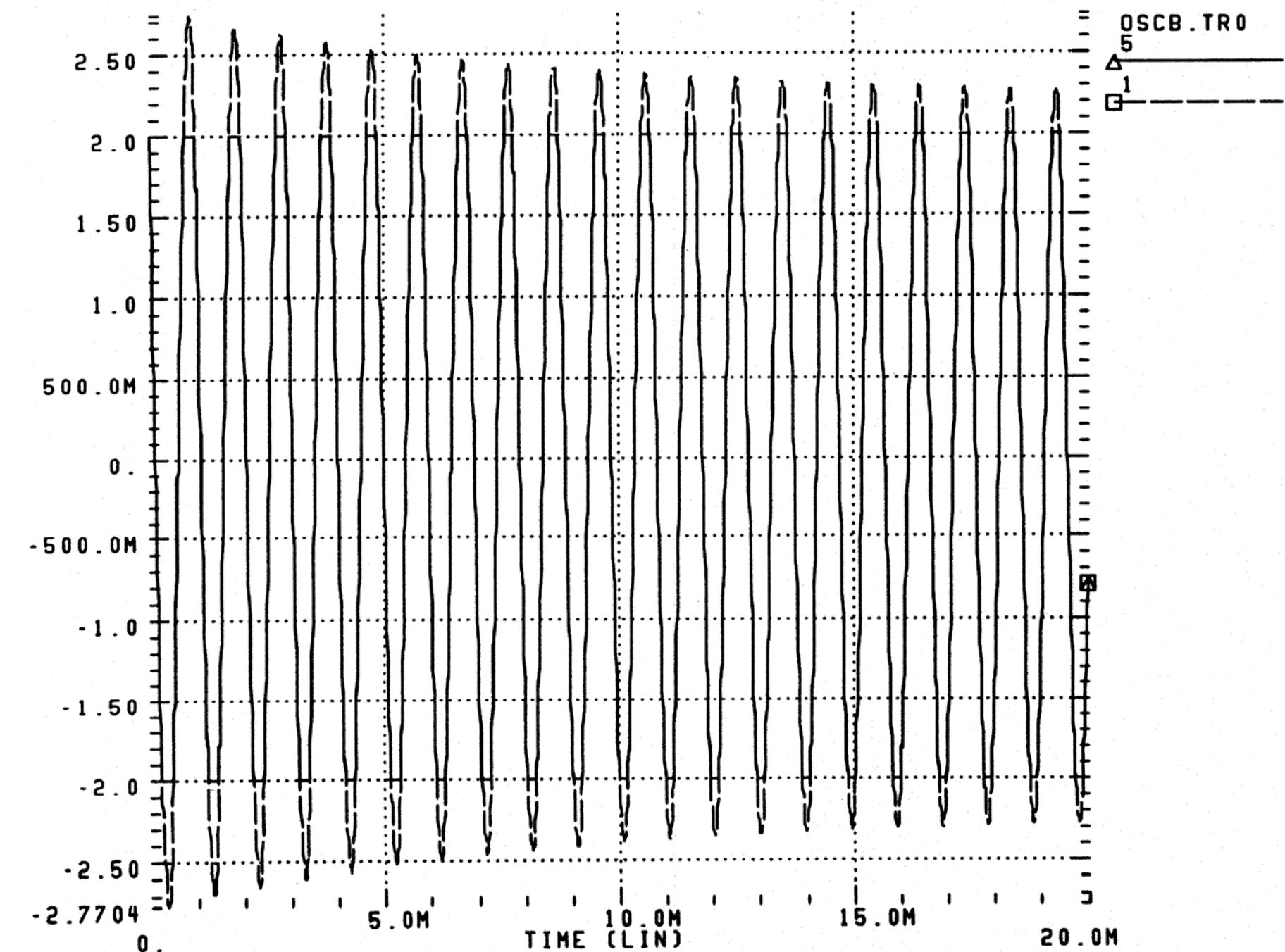

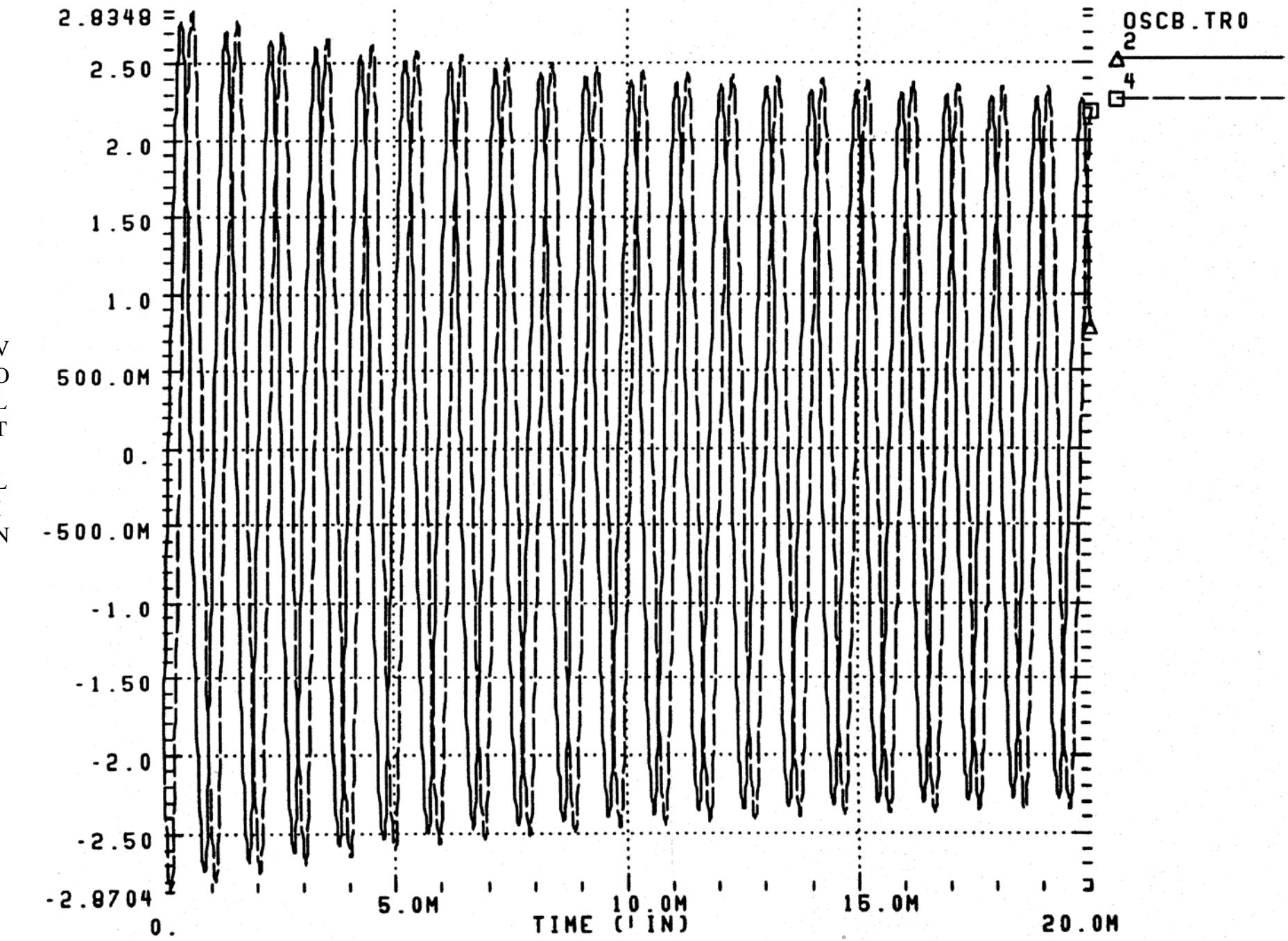
OSCILLATOR BASED ON A TOW-THOMAS BP
95/04/22 15:41:53




Oscillator based on a Tow-Thomas BP

R4 5 3 16K
R01 4 3 1K
RQ 2 3 16K
R 6 1 1K
R 1 7 1K
C02 3 2 0.1591549U
R03 2 6 1K
C03 7 4 0.1501549U
.SUBCKT OPAMP vi- vi+ v0+ v0-
*
*
RIN vi- vi+ 10E6
EIN 1 0 vi+ vi- 2E05
R3DB 1 2 1K
C3DB 2 0 0.159E-04
EOUT 3 V0- 2 0 1
DP 2 VP DIODE
DN VN 2 DIODE

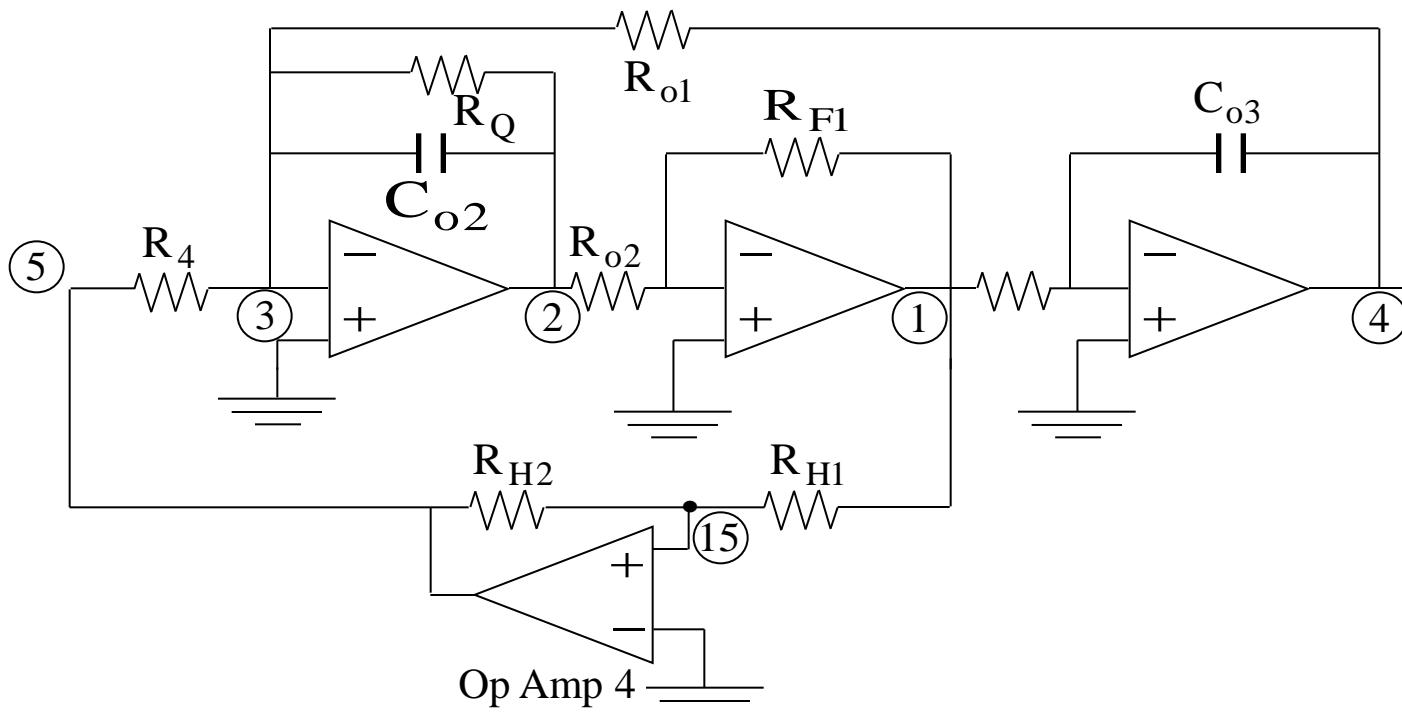
VPP VP 0 13
VNN VN 0 -13
ROUT 3 v0+ 75.
.MODEL DIODE D(IS=10E-08 N=0.01)
.ENDS OPAMP
* DESCRIPTION OF OPAMPS AND THEIR NODES
XOP1 3 0 2 0 OPAMP
XOP2 6 0 1 0 OPAMP
XOP3 7 0 4 0 OPAMP
*LIMITER Hysteresis CIRCUIT DESCRIPTION
RH1 1 15 2K
RH2 15 5 13K
XOP4 0 15 5 0 OPAMP
* DESIRED ANALYSIS RESPONSE
.TRAN 5U 20m UIC
.FOURIER 57 V(1) V(2) V(4)
.IC V(1)=2 V(2)=-2 V(4)=-2 V(5)=2
.OPTIONS POST
.END



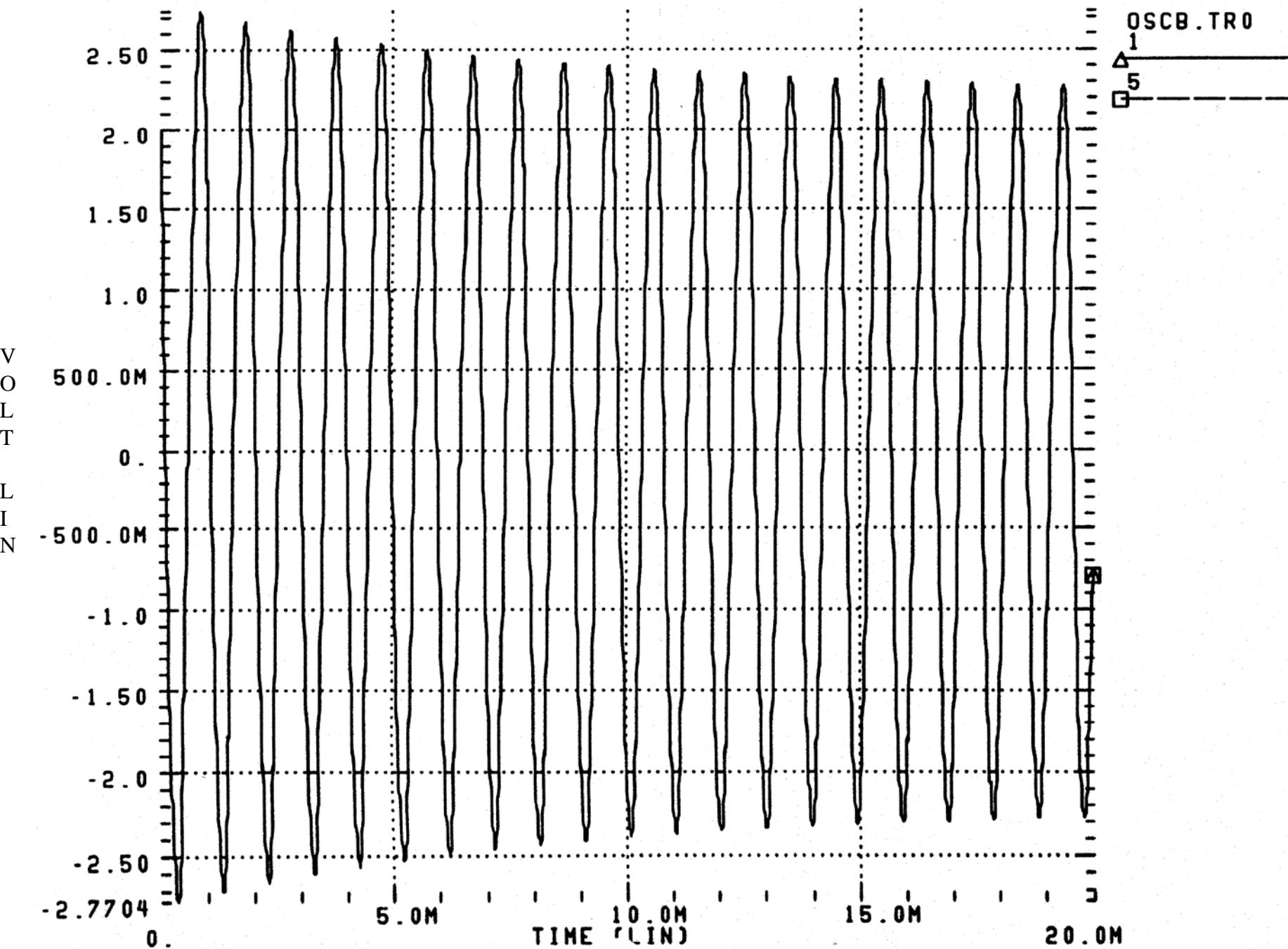OSCILLATOR BASED ON A TOW-THOMAS BP
95/04/22 15:41:53



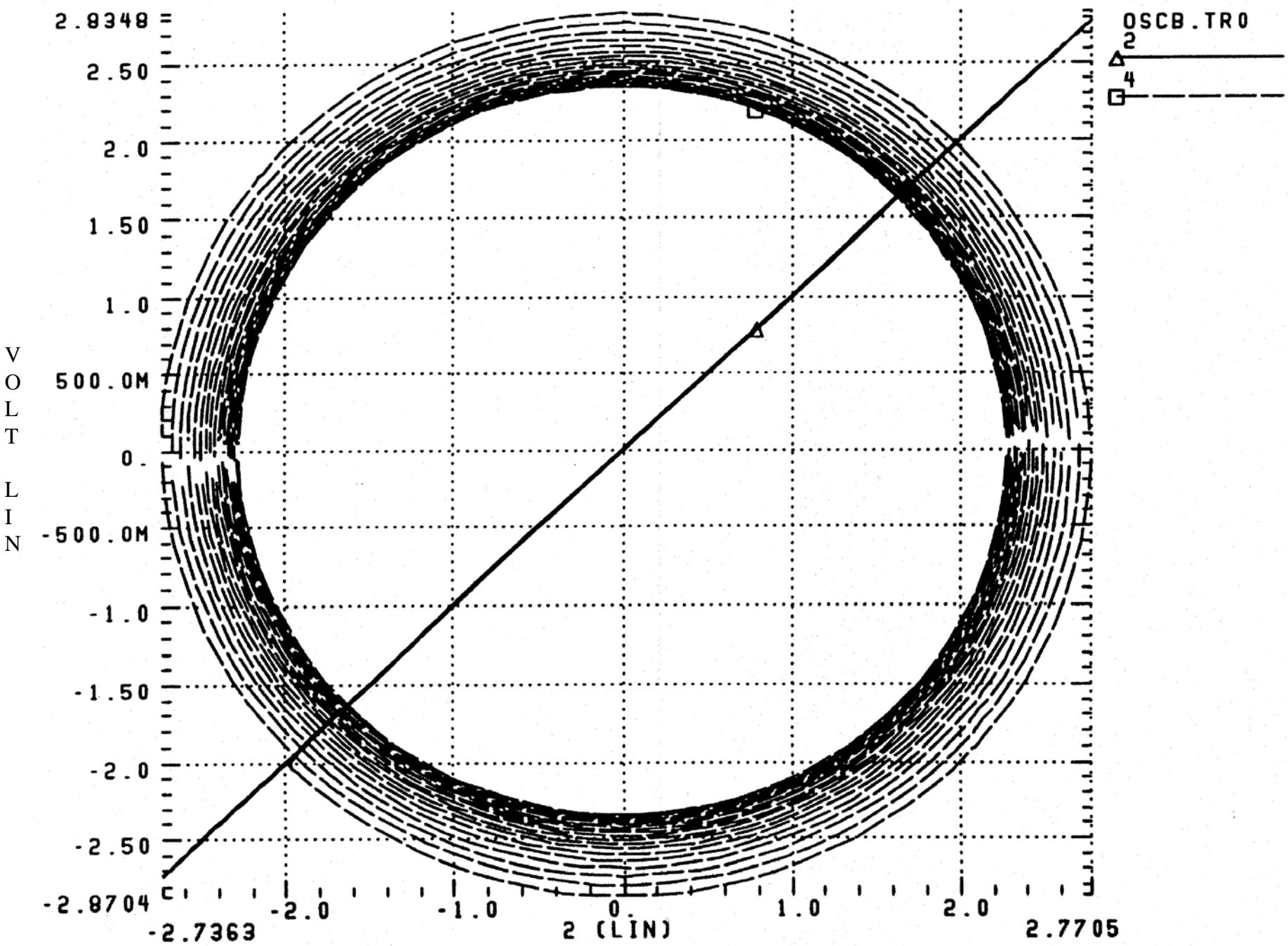OSCILLATOR BASED ON A TOW-THOMAS BP
95/04/22 15:41:53




Oscillator based on a Tow-Thomas BP

R4 5 3 35K
R01 4 3 1.4K
RQ 1 3 9.6K
R 6 1 1K
R 1 7 1K
C02 3 2 0.1591549U
R03 2 6 1K
C03 7 4 0.1501549U
.SUBCKT OPAMP vi- vi+ v0+ v0-
*
*
RIN vi- vi+ 10E6
EIN 1 0 vi+ vi- 2E05
R3DB 1 2 1K
C3DB 2 0 0.159E-04
EOUT 3 V0- 2 0 1
DP 2 VP DIODE
DN VN 2 DIODE


VPP VP 0 13
VNN VN 0 -13
ROUT 3 v0+ 75.
.MODEL DIODE D(IS=10E-08 N=0.01)
.ENDS OPAMP
* DESCRIPTION OF OPAMPS AND THEIR NODES
XOP1 3 0 2 0 OPAMP
XOP2 6 0 1 0 OPAMP
XOP3 7 0 4 0 OPAMP
*LIMITER Hysteresis CIRCUIT DESCRIPTION
RH1 1 15 2K
RH2 15 5 13K
XOP4 0 15 5 0 OPAMP
* DESIRED ANALYSIS RESPONSE
.TRAN 5U 20m UIC
.FOURIER 57 V(1) V(2) V(4)
.IC V(1)=2 V(2)=-2 V(4)=-2 V(5)=2
.OPTIONS POST
.END

Double Positive Feedback

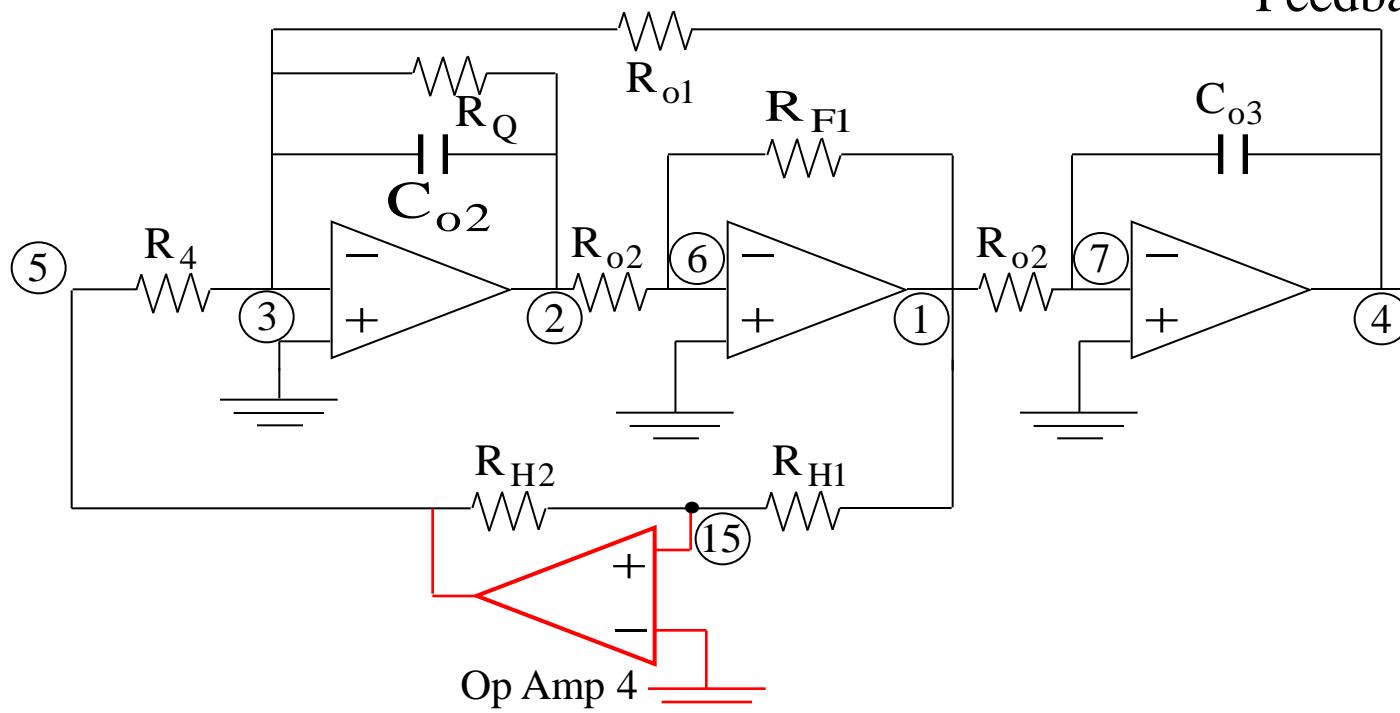



OSCILLATOR BASED ON A TOW-THOMAS BP

95/04/22 15:41:53

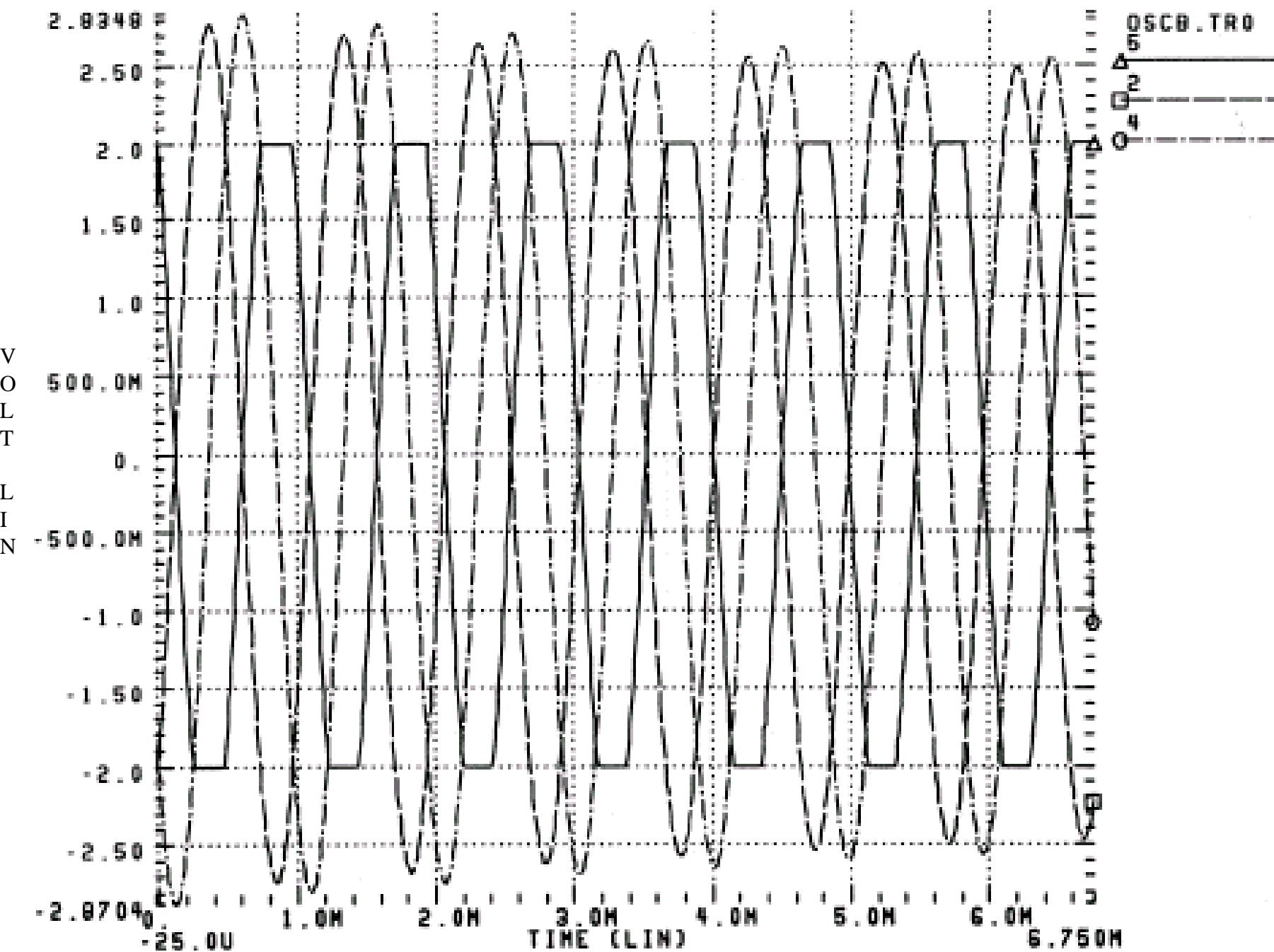


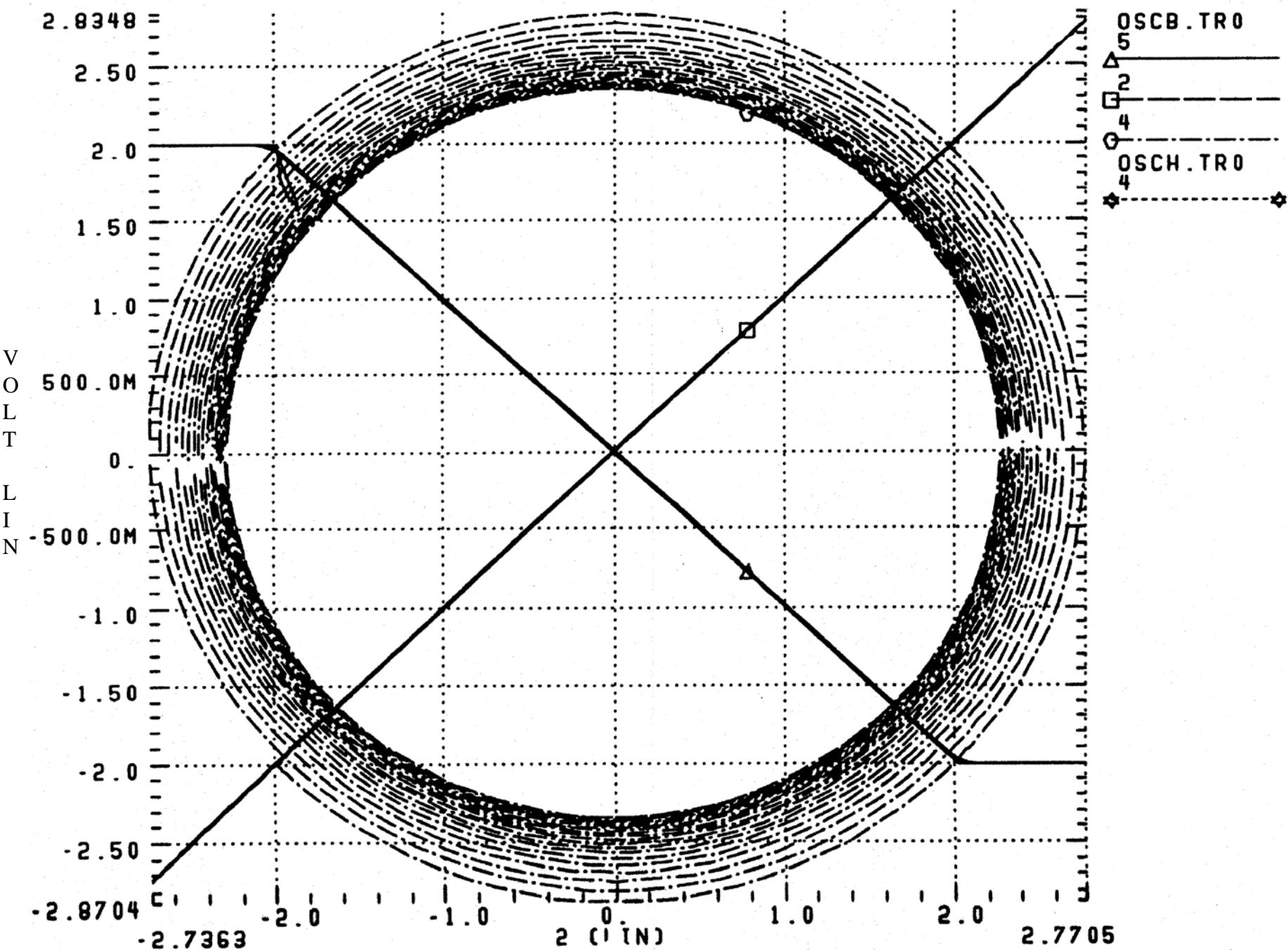
OSCILLATOR BASED ON A TOW-THOMAS BP
95/04/22 15:41:53



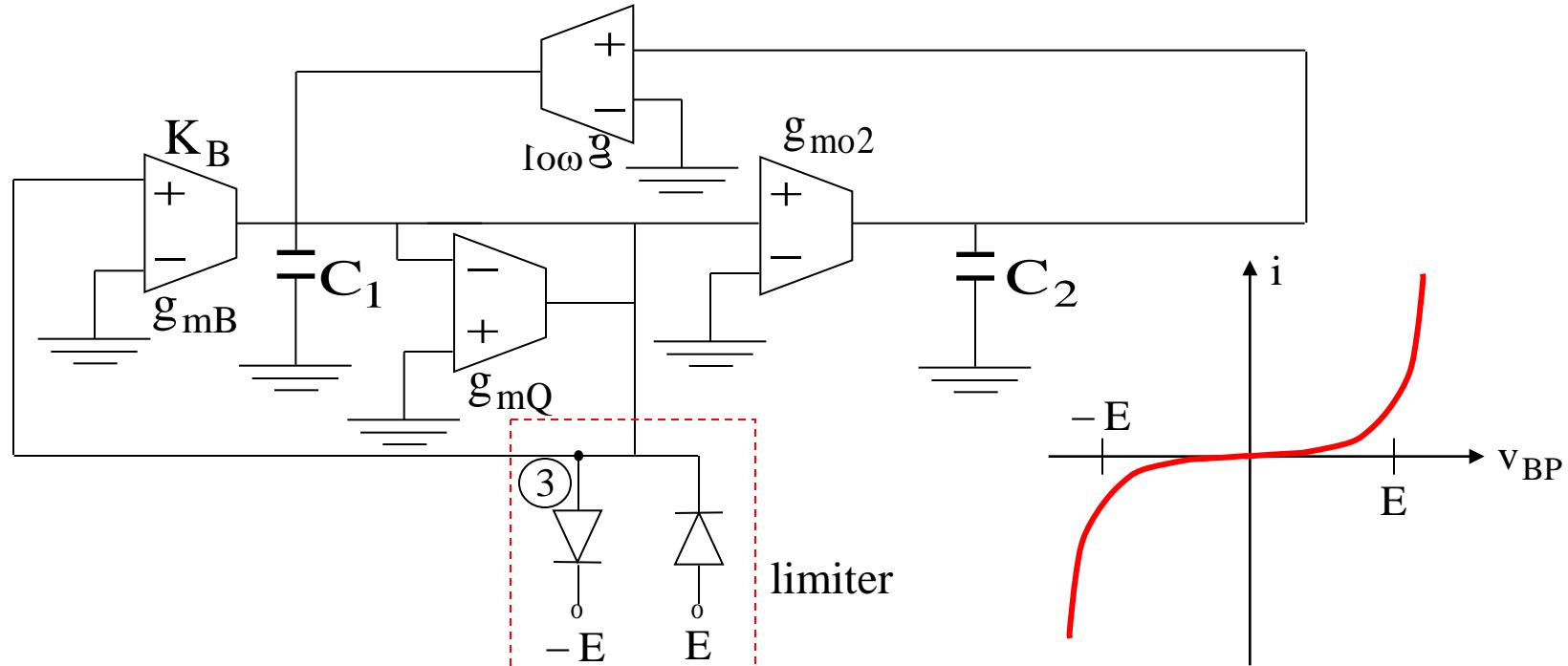

OTA - C Bandpass Based Oscillator

Another possible limiter can be:

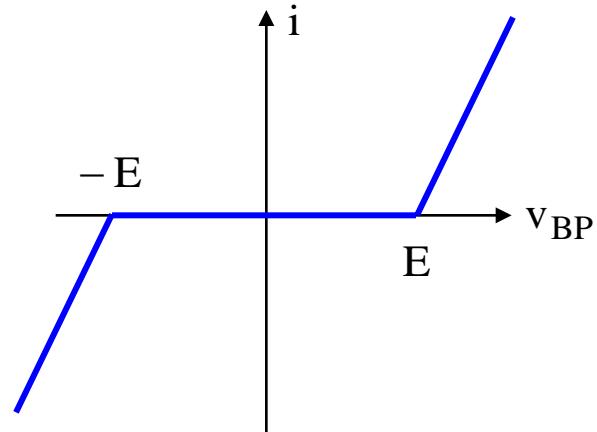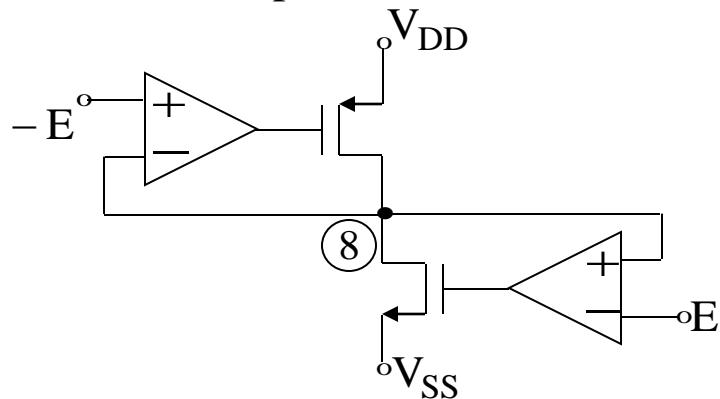


Simulations

Active-Filter Tuned Oscillator

Hints

- First design a band pass filter
 - High Q
 - Gain
- Next decide on type of limiter
 - Finally be sure the path from the band pass output through the limiter to the input is positive feedback.


Quadrature Oscillator

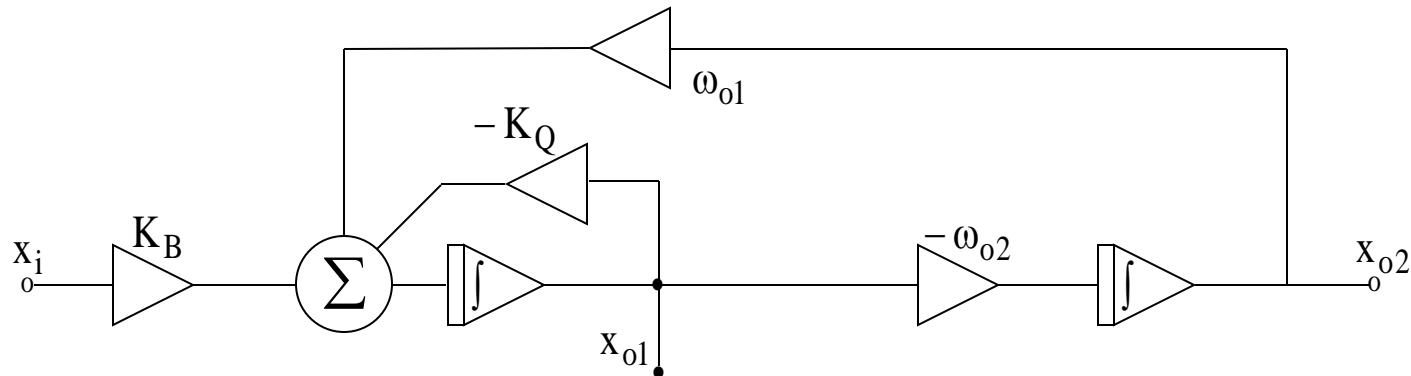

Two Integrator Loop Filter

$$H_1(s) = \frac{x_{o1}(s)}{x_i(s)} = \frac{\frac{K_B}{s}}{1 + \frac{K_Q}{s} + \frac{\omega_{o1} \cdot \omega_{o2}}{s^2}} = \frac{K_B s}{s^2 + K_Q s + \omega_{o1} \omega_{o2}}$$

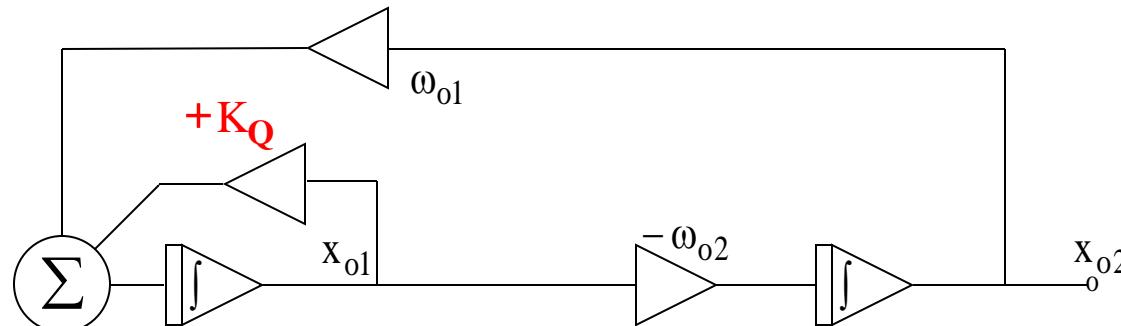$H_1(s)$ is a second-order bandpass. The topology of this integrator loop can be modified to yield a *quadrature oscillator*.



Quadrature Oscillator Architecture

Observe that the characteristic equation yields:

$$1 - \frac{K_Q}{s} + \frac{\omega_{o1}\omega_{o2}}{s^2} = 0$$

or


$$s^2 - K_Q s + \omega_{o1}\omega_{o2} = 0$$

The roots are placed at


$$s_{1,2} = \frac{K_Q \pm \sqrt{K_Q^2 - 4\omega_{o1}\omega_{o2}}}{2} \quad \left| \begin{array}{l} = \frac{K_Q}{2} \pm \frac{j}{2} \sqrt{4\omega_{o1}\omega_{o2} - K_Q^2} \\ K_Q^2 < 4\omega_{o1}\omega_{o2} \end{array} \right.$$

To provide sustained oscillations we need to locate the poles on the $j\omega$ axis, this requires:

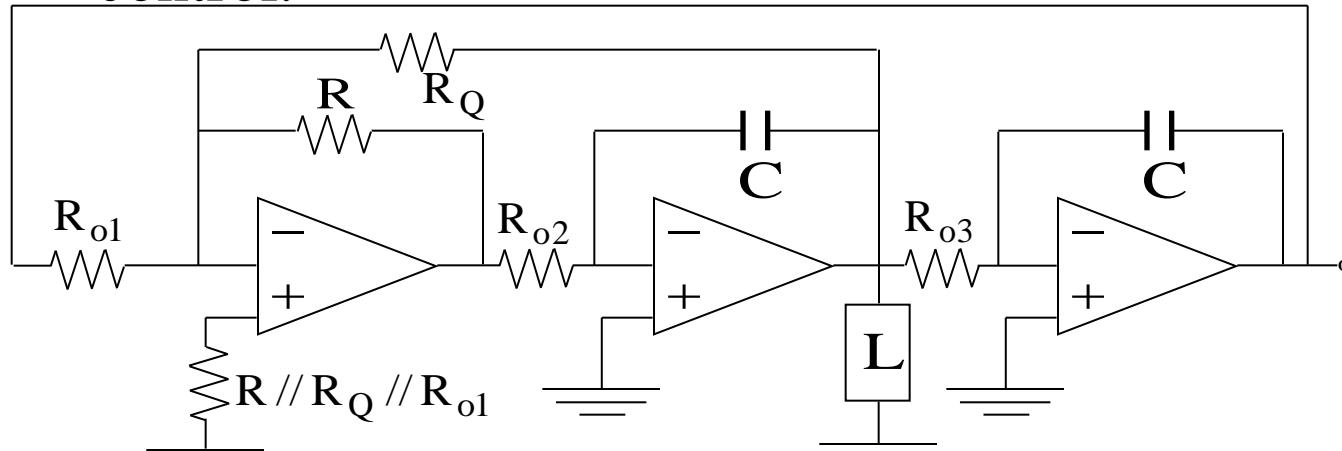- i) $K_Q = E$ small positive value
- ii) To limit the output by means of a nonlinear gain control.



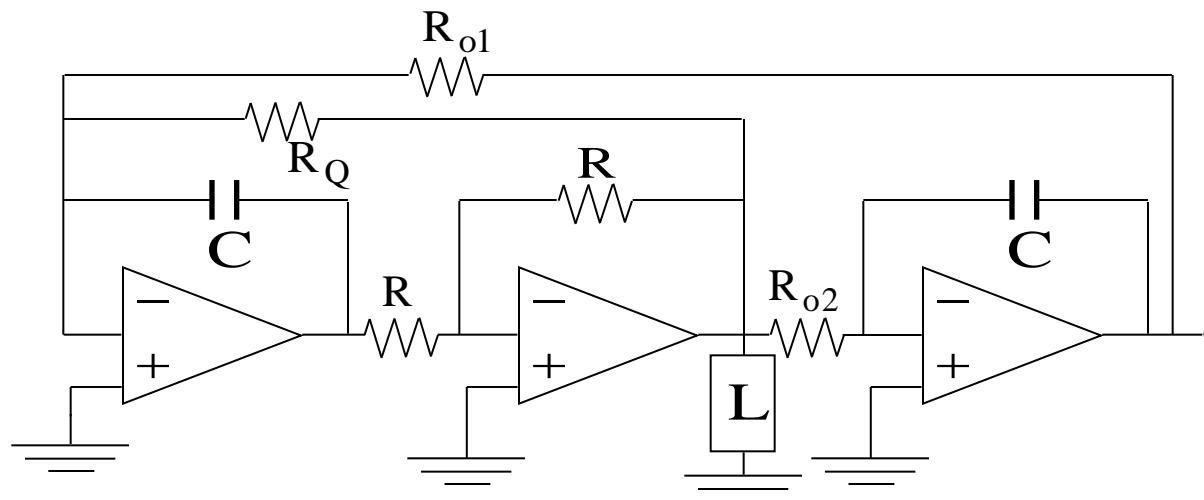One possible Quadrature Oscillator Structure



Oscillator at component level simulation

```

RO1 4 3 220K
RQ 1 3 510K
RF1 3 2 310K
RO2 2 6 100K
CO2 6 1 0.01U
RO3 1 7 100K
CO3 7 4 0.001U
.SUBCKT OPAMP vi- vi+ v0+ v0-
*
*
RIN vi- vi+ 10E6
BIN 1 0 vi+ vi- 2E05
R3DB 1 2 1K
C3DB 2 0 0.159E-04
BOUT 3 V0- 2 0 1
DP 2 VP DIODE

```

```
DN VN 2 DIODE
```

```
VPP VP 0 13
```

```
VNN VN 0 -13
```

```
ROOT 3 v0+ 75.
```

```
.MODEL DIODE D (IS=10E-05 N=0.001)
```

```
.ENDS OPAMP
```

* DESCRIPTION OF OPAMPS AND THEIR NOOES

```
XOP1 3 0 2 0 OPAMP
```

```
XOP2 6 0 1 0 OPAMP
```

```
XOP3 7 0 4 0 OPAMP
```

```
.TRAN 10U 40m UIC
```


```
.FOURIER 57 V(1) V(2) V(4)
```

```
.IC V(1)=.2 V(2)=-.2 V(4)=-.2
```

.OPTIONS POST

.OP .08


.END

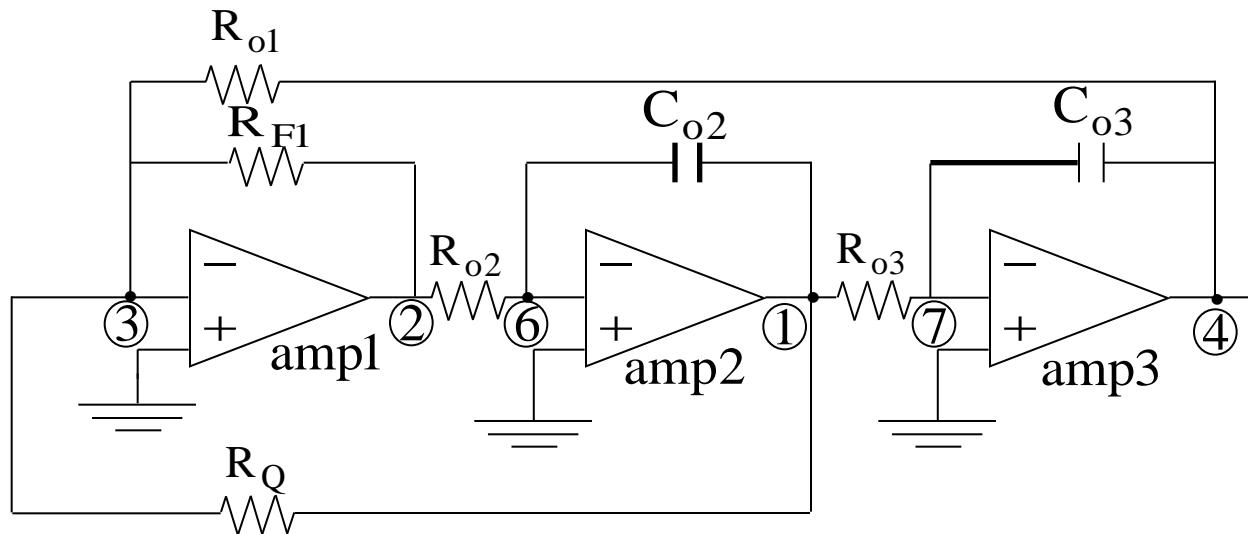


**QUADRATURE OSCILLATOR
(NO EXTERNAL LIMITER)**

OSCILLATOR AT COMPONENT LEVEL SIMULATION

95/04/22 11:53:54

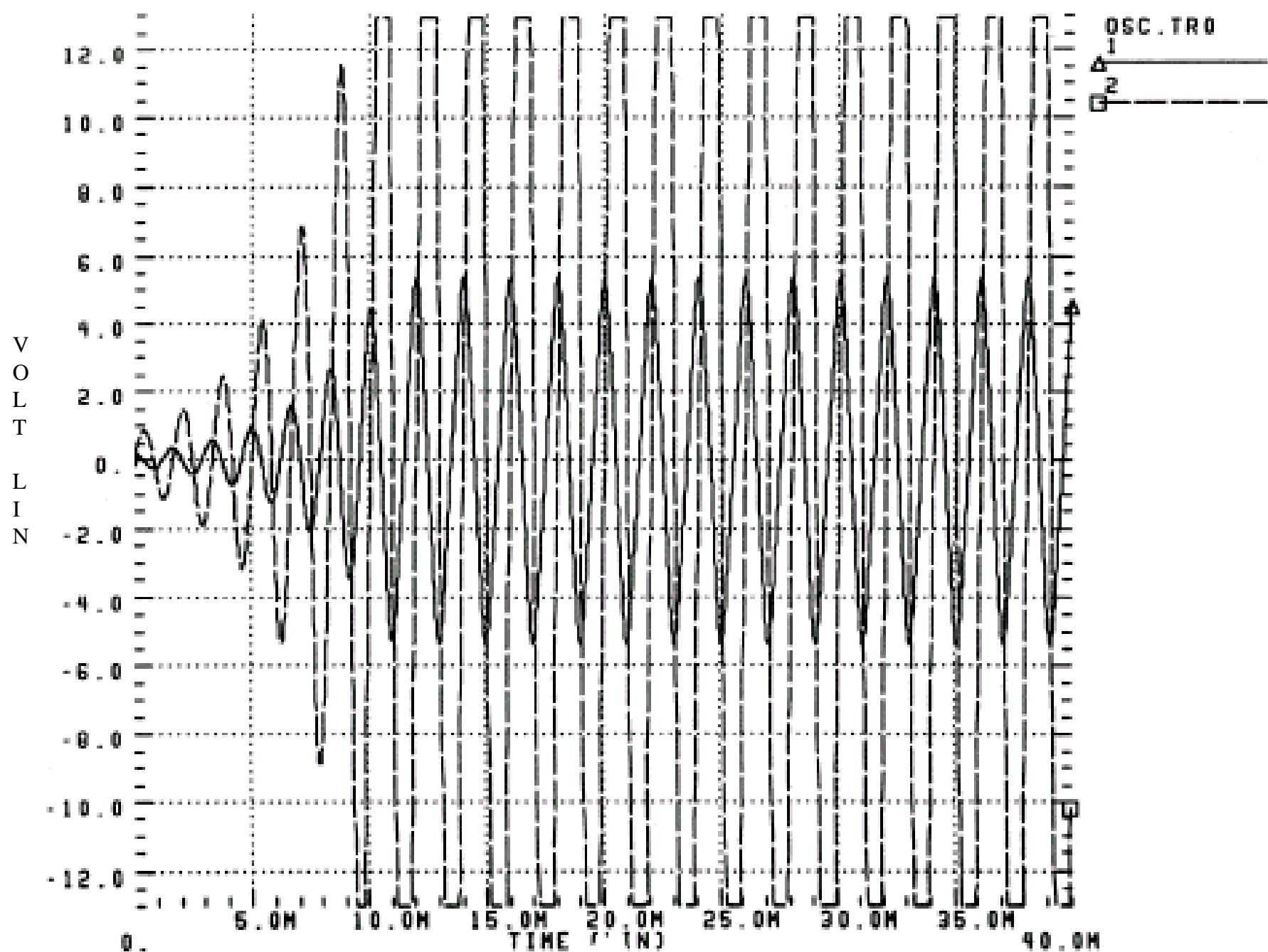

OTA-C QUADRATURE OSCILLATOR

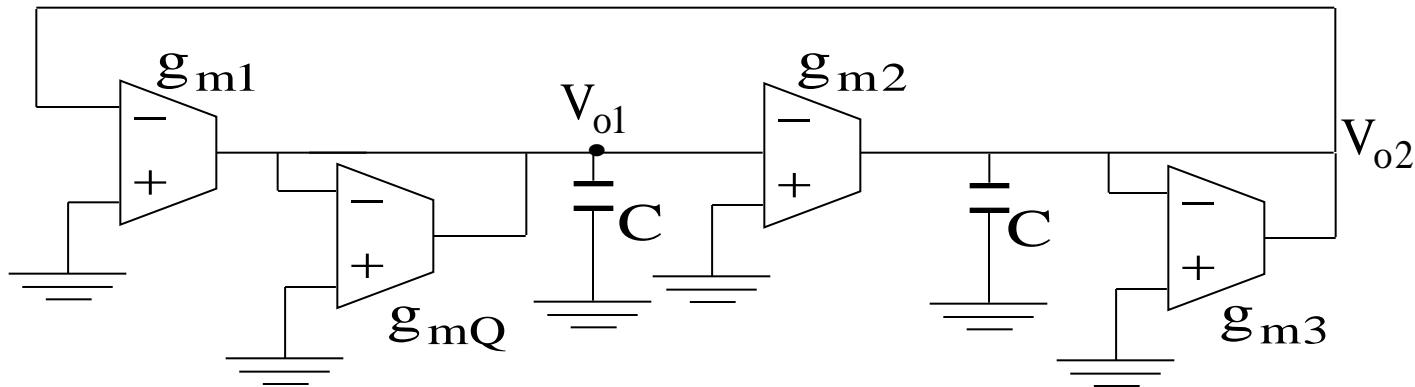

Structure 1. Note the positive feedback in the main loop

$$V_{o1} = \frac{g_{m1} V_{o2}}{g_{mQ} + sC} \quad (1)$$

$$V_{o2} = \frac{g_{m2} V_{o1}}{g_{m3} + sC} \quad (2)$$

C.E

$$1 - \frac{g_{m1}}{g_{mQ} + sC} \frac{g_{m2}}{g_{m3} + sC} = 0$$

or


$$s^2 - K_Q s + \omega_{o1}\omega_{o2} = 0$$

Where

$$K_Q = \frac{g_{mQ} - g_{m3}}{C}$$

$$\omega_o^2 = \frac{g_{m1}g_{m2} - g_{mQ}g_{m3}}{C^2}$$

An alternative structure is considered next

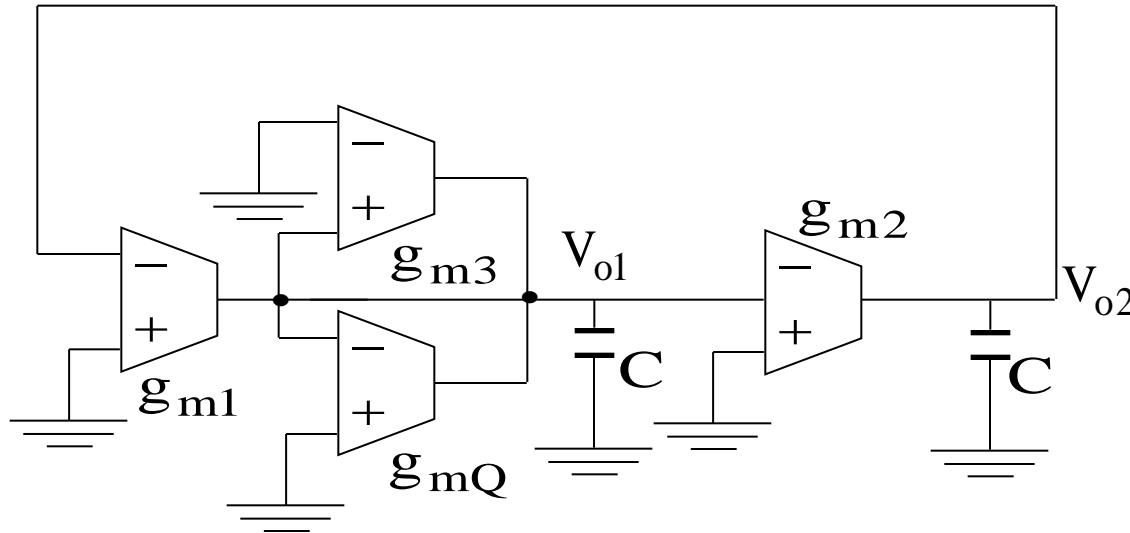


Structure 2. Observe the positive and negative resistance associated with integrator 1.

Where $\omega_o^2 = \frac{g_{m1}g_{m2}}{C^2}$

$$K_Q = \frac{g_{mQ} - g_{m3}}{C}$$

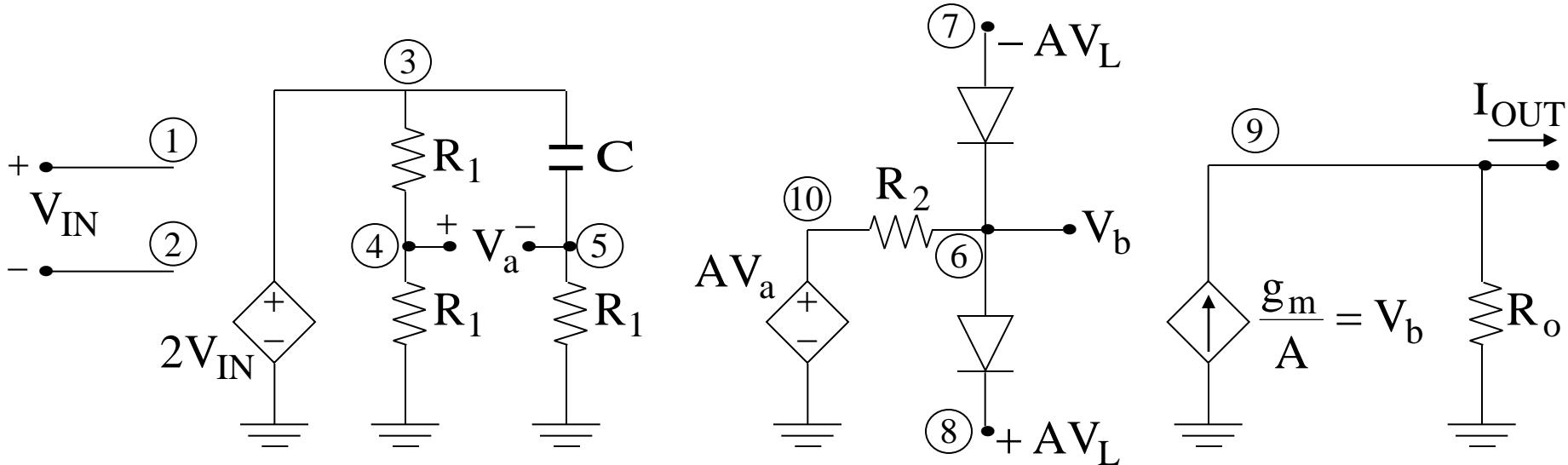
This structure is easier to tune. For a realistic design the OTA non-idealities have to be considered.





Furthermore amplitude control by external limiters. That is connect the limiters discussed before* at the output of any of the integrators.



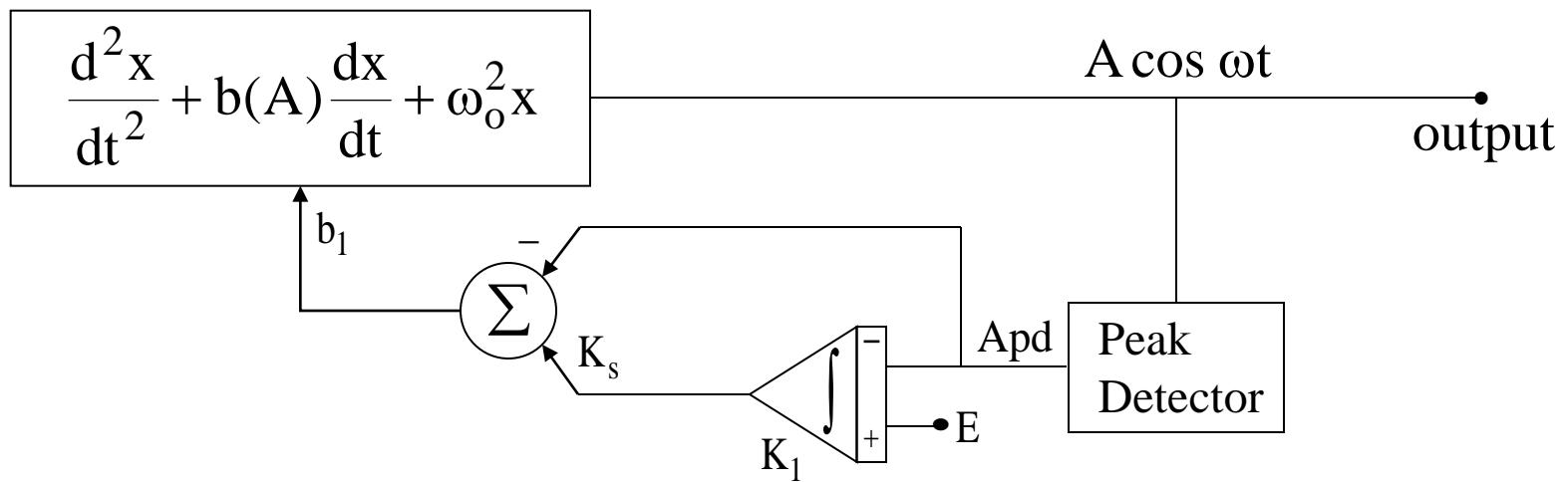
Instead of using limiters, another strategy is using an automatic gain control i.e.,




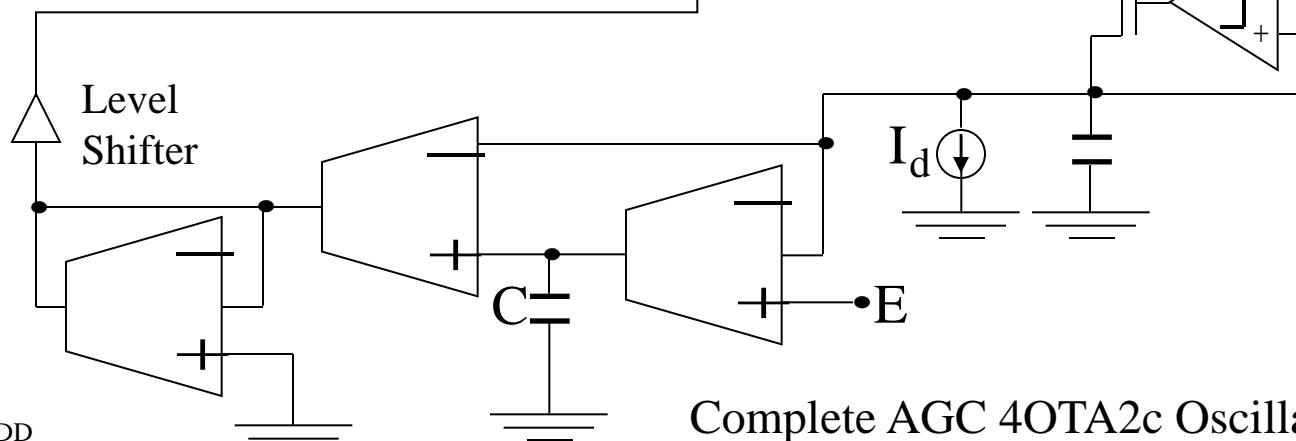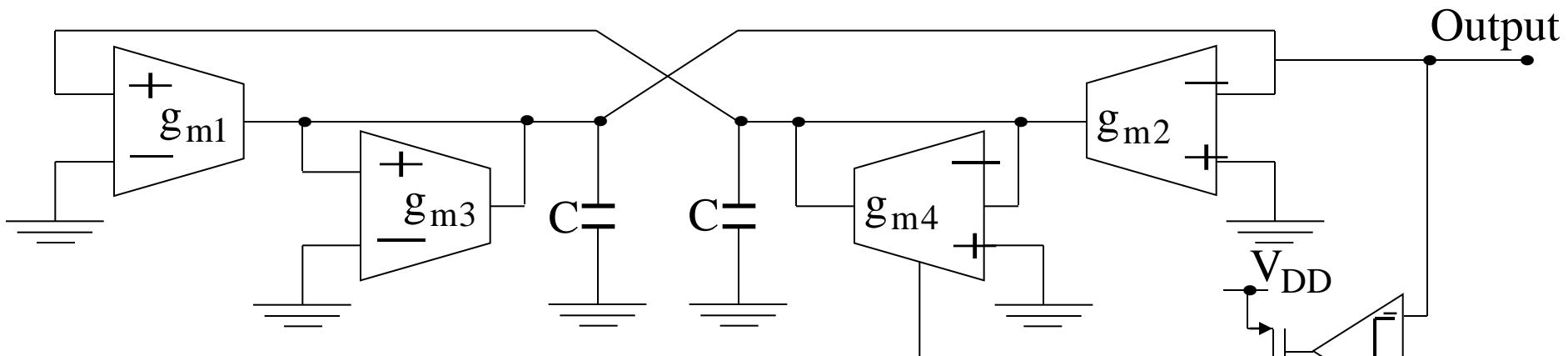Can you reformulate as an adaptive filter minimizing $(E - Apd)^2$?



Complete AGC 4OTA2c Oscillator

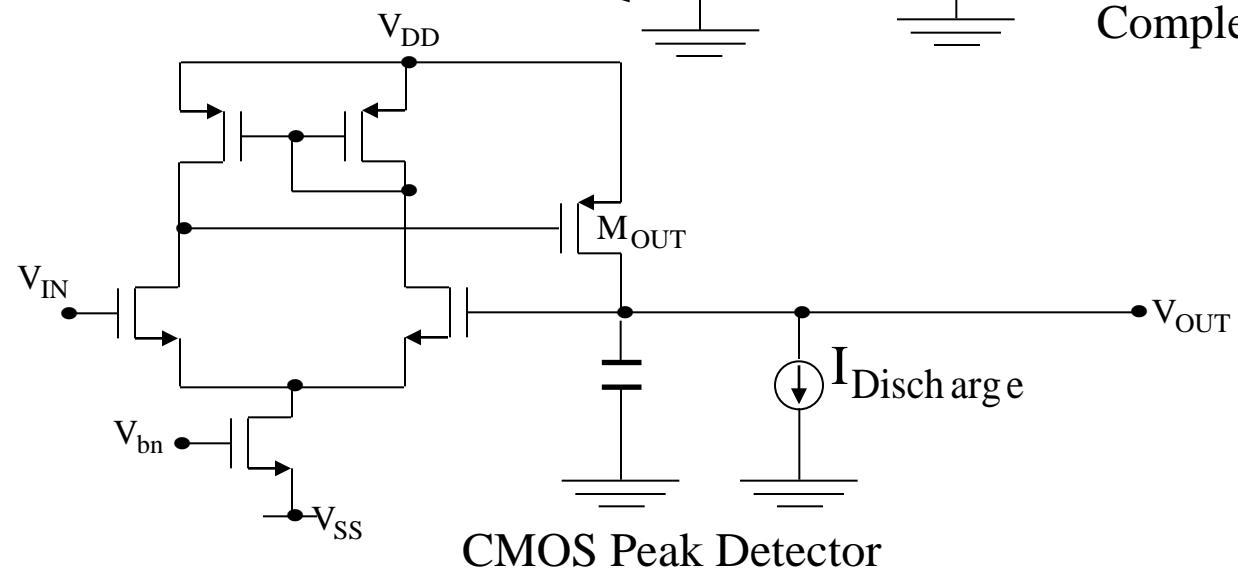

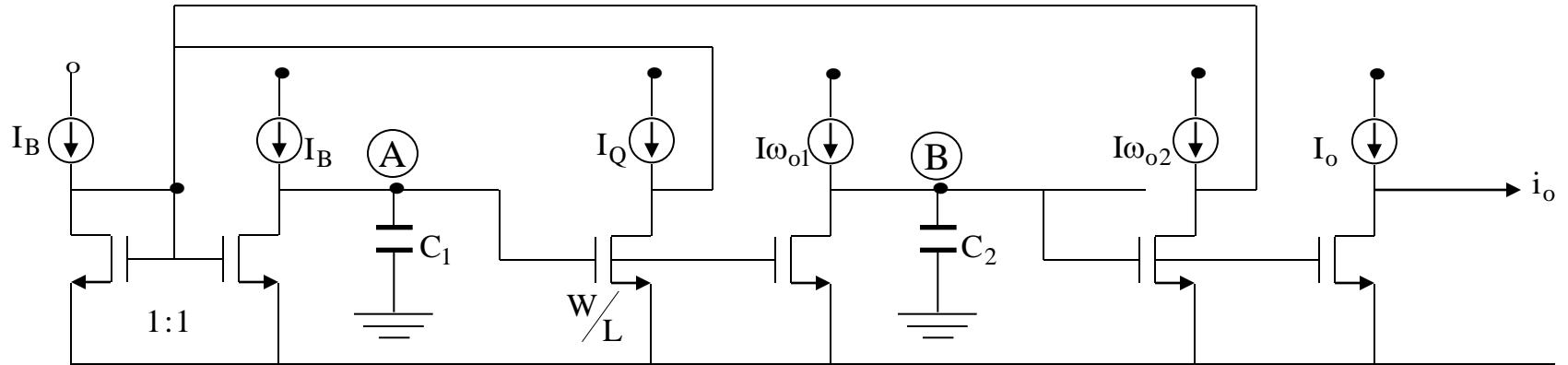

- A potential current - mode Quadrature Oscillator

Note that limiters are needed to sustain oscillators. A limiter should be placed at point (A) or (B).

References

- [1] B. Linares-Barranco, A. Rodríguez-Vázquez, E. Sánchez-Sinencio and J. L. Huertas,
“A 10 MHz CMOS OTA-C Voltage Controlled Quadrature Oscillator,” *Electronics Letters*,
Vol. 25, pp. 765-767, 8 June 1989.
- [2] B. Linares-Barranco, E. Sánchez-Sinencio, A. Rodríguez-Vázquez and J. L. Huertas,
“A Programmable Neural Oscillator Cell,” *IEEE Trans. Circuits and Systems
(Special Issue on Neural Networks)*, Vol. 36, pp. 756-761, May 1989.
- [3] A. Rodríguez-Vázquez, B. Linares-Barranco, J. L. Huertas and E. Sánchez-Sinencio,
“On the Design of Voltage Controlled Sinusoidal Oscillators Using OTA's,”
IEEE Trans. on Circuits and Systems, Vol. 37, pp. 198-211, February, 1990.
- [4] B. Linares-Barranco, A. Rodríguez-Vázquez, E. Sánchez-Sinencio and J. L. Huertas,
“CMOS OTA-C High-Frequency Sinusoidal Oscillators,” *IEEE J. Solid-State Circuits*,
Vol. 26, pp. 160-165, February 1991.
- [5] B. Razavi, “*Design of Analog CMOS Integrated Circuits*” McGraw-Hill, Boston, 2001
- [6] N.M. Nguyen and R.G. Mayer, “ Start-up and Frequency Stability in High-Frequency
Oscillators”, *IEEE J. of Solid-State Circuits*, vol 27,pp810-820,May 1992.
- [7] D. O. Pederson and K. Mayaram, “*Analog Integrated Circuits for Communication: Principles,
Simulation and Design*” Kluwer Academic Publishers , Boston1991.

References

- [1] J.Craninckx, M.Steyaert, *Wireless CMOS Frequency Synthesizer Design*, Kluwer Academic Publishers, Dordrecht, The Netherlands, 1998.
- [2] D.A.Johns, K.Martin, *Analog Integrated Circuit Design*, John Wiley & Sons, Inc., New York, U.S.A., 1997.
- [3] M.Zanno, B.Kolb, J.Fenk, and R.Weigel, “A fully integrated VCO at 2 GHz,” *IEEE J. Solid-State Circuits*, vol.33, pp. 1987-1991, Dec. 1998.
- [4] M.Curtin and P.O’Brien, “Phase-Locked Loops for High-Frequency Receivers and Transmitters-Part 2,” *Analog Dialogue*, 33-5, Analog Devices, 1999.
- [5] R.W.Rhea, *Oscillator Design and Computer Simulation*, Noble Publishing Corporation, Georgia, U.S.A., 2nd edition, 1995.
- [6] J.Craninckx and M.Steyaert, “A 1.8-GHz low-phase noise CMOS VCO using optimized hollow inductors,” *IEEE J. Solid-State Circuits*, vol.32,pp.736-744, May 1997.
- [7] A.Hajimiri and T.H.Lee, “A General theory of phase noise in electrical oscillators,” *IEEE J. Solid-State Circuits*, vol.33, pp.179-194, Feb. 1998.
- [8] A.Hajimiri and T.H.Lee, “Design issues in CMOS differential LC oscillators,” *IEEE J. Solid-State Circuits*, vol.34, pp.717-724, May 1999.

References



- [9] A.Hajimiri, S.Limotyrakis, and T.H.Lee, "Jitter and phase noise in ring oscillators," *IEEE J. Solid-State Circuits*, vol.34, pp.790-804, June 1999.
- [10] C.H.Park, and B.Kim, "A low-noise, 900-MHz VCO in 0.6- μ m CMOS," *IEEE J. Solid-State Circuits*, vol.34, pp.586-591, May 1999.
- [11] C.Samori, A.L.Lacaita, F.Villa, and F.Zappa, "Spectrum folding and phase noise in LC tuned oscillators," *IEEE Trans. Circuits Syst. II*, vol.45, pp.781-789, July 1998.
- [12] B. Razavi, "A study of phase noise in CMOS oscillators," *IEEE J. Solid-State Circuits*, vol.31, pp.331-343, Mar. 1996.
- [13] T.C.Weigandt, B.Kim, and P.R.Gray, "Analysis of timing jitter in CMOS ring oscillators," in *Proc. ISCAS*, June 1994.
- [14] P.Kinget, "A fully integrated 2.7V 0.35 μ m CMOS VCO for 5GHz wireless applications," *ISSCC Digest of Technical Papers*, pp. 226-227, Feb. 1998.
- [15] M.A.Margarit, J.L.Tham, R.G.Meyer, and M.J.Deen "A low-noise, low-power VCO with automatic amplitude control for wireless applications," *IEEE J. Solid-State Circuits*, vol.34, pp.761-771, June 1999.
- [16] B. Linares-Barranco, A. Rodríguez-Vázquez, E. Sánchez-Sinencio and J. Huertas, "On the Generation, Design and Tuning of OTA-C High-Frequency Sinusoidal Oscillators," *IEE Proceedings-G Electronic Circuits and Systems*, Vol. 39, pp. 557-568, October 1992.
- [17] B. Linares-Barranco, A. Rodríguez-Vázquez, E. Sánchez-Sinencio and J. L. Huertas, "CMOS OTA-C High-Frequency Sinusoidal Oscillators," *IEEE J. Solid-State Circuits*, Vol. 26, pp. 160-165, February 1991.

A Low THD Bandpass-Based Oscillator Using Multilevel Hard Limiter

Faramarz Bahmani
Edgar Sanchez-Sinencio

Bandpass Based Oscillator

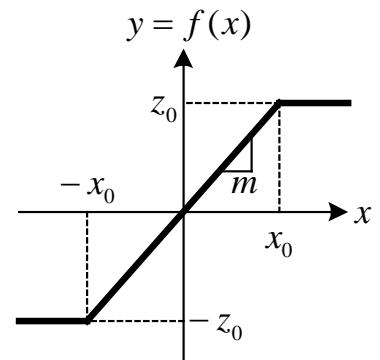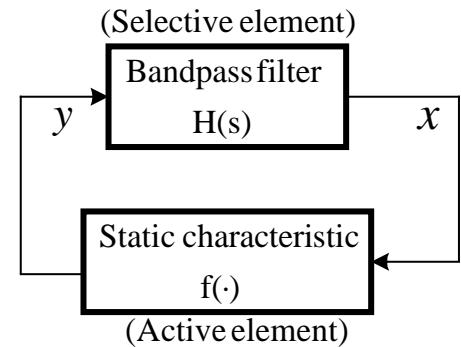- Theory
- Filter and comparator are in positive feedback
- Amplitude and frequency of oscillation in decoupled
- Oscillation amplitude is indirectly controlled by the clamping levels $\pm z_0$



Bandpass Based Oscillator

- To analyze this kind of oscillators the nonlinear block needs to be linearized.
 - Describing Function: Assume the input to the nonlinear block is a pure sinusoidal, DF is defined as the ratio of the amplitude of the first harmonic at the output to the input amplitude A_0 .

$$N(A_0) = \frac{a}{A_0} = \begin{cases} \frac{2m}{\pi} \left[\sin^{-1}\left(\frac{x_0}{A_0}\right) + \frac{x_0}{A_0} \sqrt{1 - \left(\frac{x_0}{A_0}\right)^2} \right] & A_0 > x_0 \\ m & A_0 < x_0 \end{cases}$$

Bandpass Based Oscillator

$$H(s) = \frac{k_0 s}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2} = \frac{X(s)}{Y(s)} = \frac{1}{N(A_0)}$$

$$\frac{d^2 x(t)}{dt^2} + \frac{dx(t)}{dt} \left[\frac{\omega_0}{Q} - k_0 N(A_0) \right] + \omega_0^2 x(t) = 0$$

$$A_0 \cong N^{-1} \left(\frac{\omega_0}{k_0 Q} \right)$$

- Thus, oscillation amplitude A_0 is a function of the nonlinearity...

Linearity

- Due to the nature of the nonlinear block, the output signal is rich in harmonic.
- To increase the linearity of the output signal the most obvious way is to increase the Q of the bandpass filter. However, this solution is power hungry and expensive.
- Question: Does the nonlinear block have any effect on linearity?

General Case


- N-slope nonlinearity

– It can be proved:

$$N(A_0) = \frac{1}{2\pi} \sum_{i=1}^{N-1} (m_i - m_{i+1}) r(\rho_i)$$

$$r(\rho_i) = \frac{2}{\pi} \left[\sin^{-1}(\rho_i) + \rho_i \sqrt{1 - \rho_i^2} \right] ; \rho_i < 1$$


$$\rho_i = x_i / A_0$$

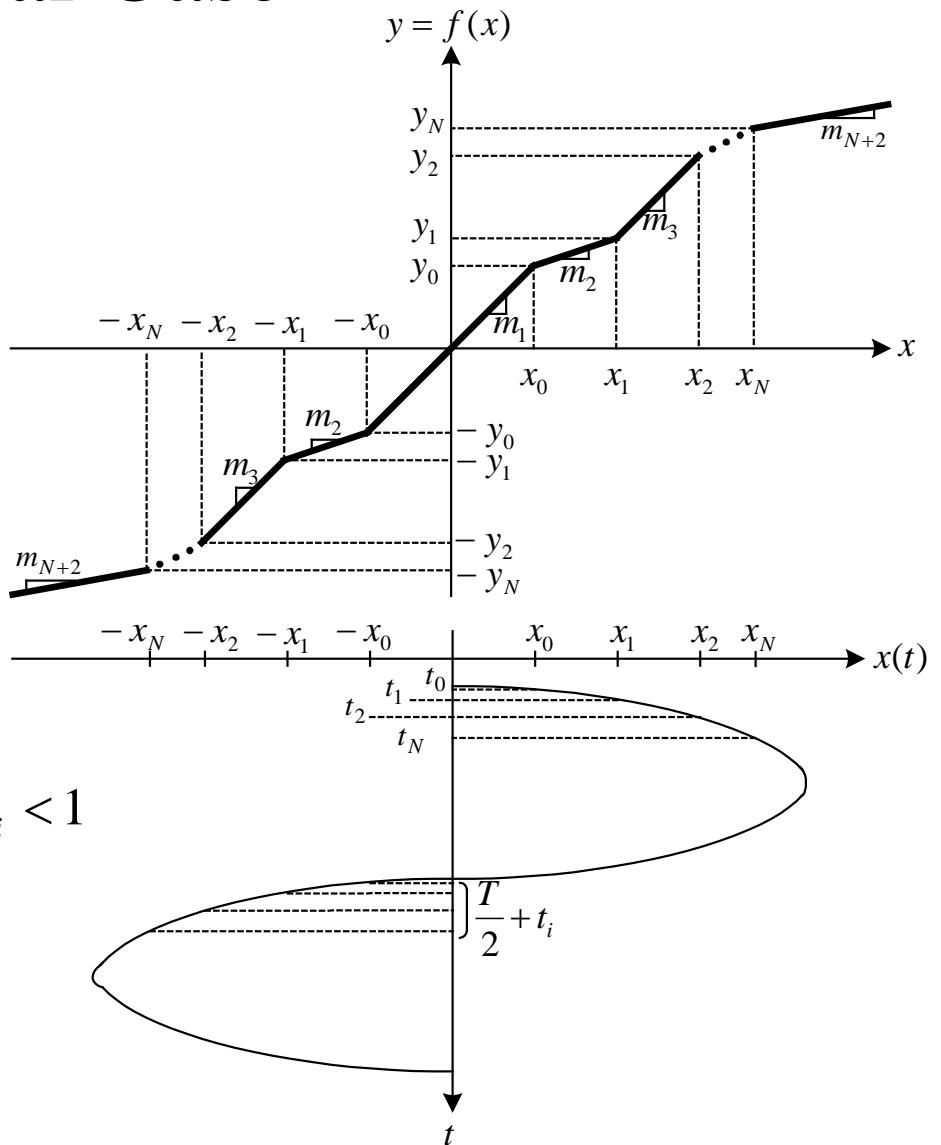

General Case: An Example

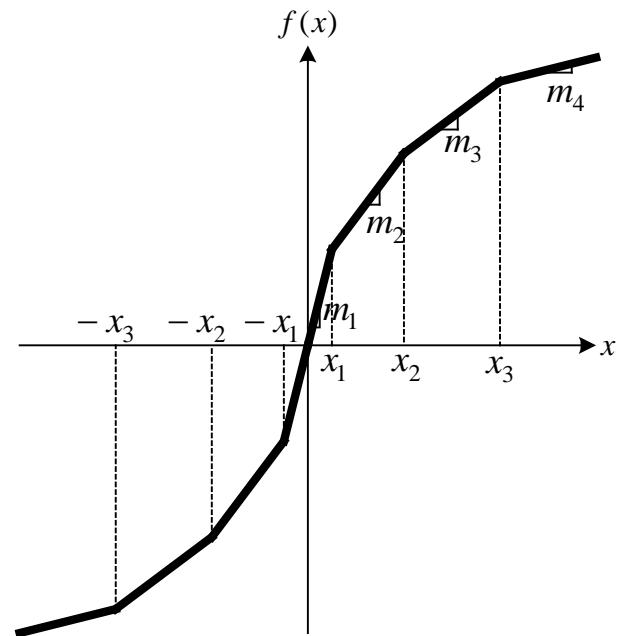- Example: 4-level nonlinearity

$$N(A_0) = \frac{1}{2\pi} \left(m_3 r(\rho_3) + (m_2 - m_3) r(\rho_2) + (m_1 - m_2) r(\rho_1) \right)$$




- Assuming $A_0=x_3$, it can be shown that to have a perfect nonlinear function:


$$m_1 = \infty, m_2 = 0, m_3 = \infty \text{ and } m_4 = 0$$

General Case: An Example

- Thus optimum nonlinearity functions look like the following figures

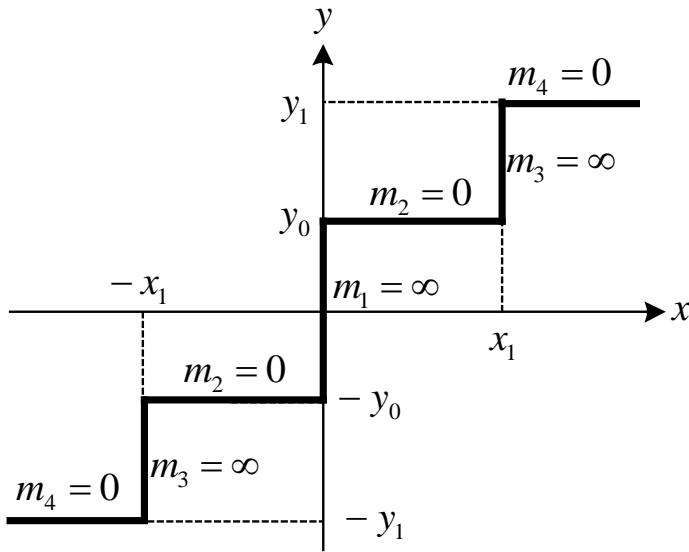

Our 4-level example

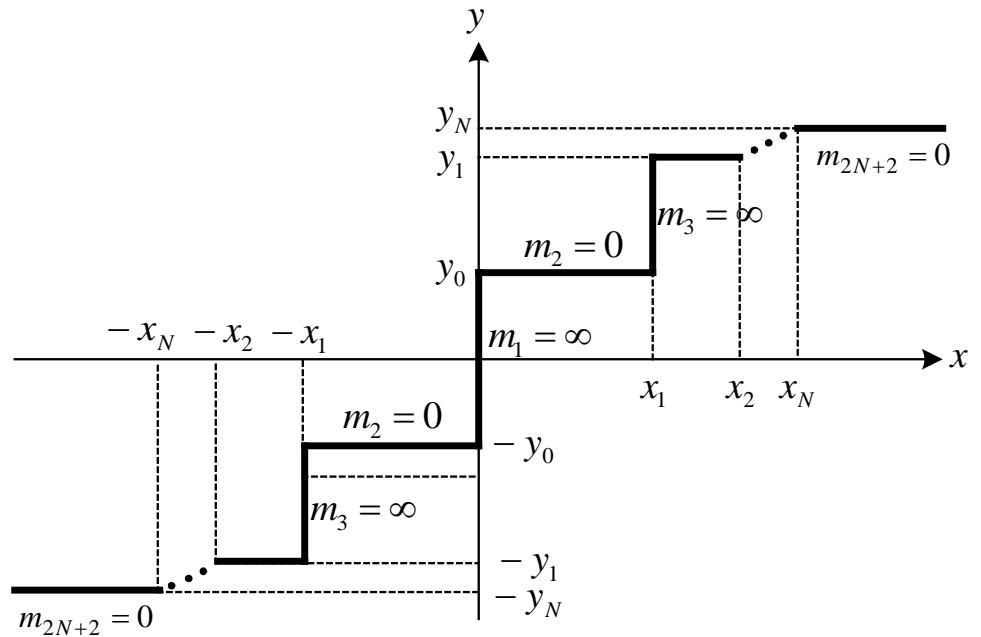

General N -level

Harmonic Distortion

- Next question: what is the best values of x_i 's and y_i 's to minimize the THD at the output the nonlinear block?
- Answer: Assuming the input is a sinusoidal the n^{th} Fourier harmonic can be found as

$$a_c(n\omega_0) = a_0(n\omega_0) \left\{ 1 + \sum_{i=1}^{N-1} \left[y_i \left(1 - (-1)^n \right) \cdot \cos(\omega_0 t_i) \right] \right\}, n = 3, 5, 7, \dots$$

- Note that due to symmetry the even order harmonics are zero.

Harmonic Distortion



- It can be demonstrated that for specific values of k and n , the following expressions of t_i and y_i make $a_c(n\omega_0)$ zero

$$t_i = \frac{T}{2^{K+2}} i, \quad i = 1, 2, 3, \dots$$

$$y_i = \cos\left(\frac{\pi}{2^{K+1}} i\right), \quad i = 1, 2, 3, \dots$$

Harmonic Distortion: 4-Level Case

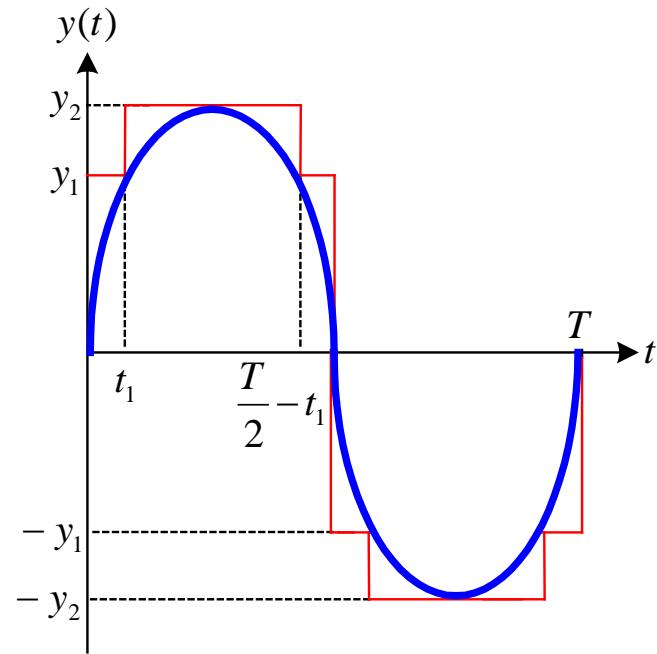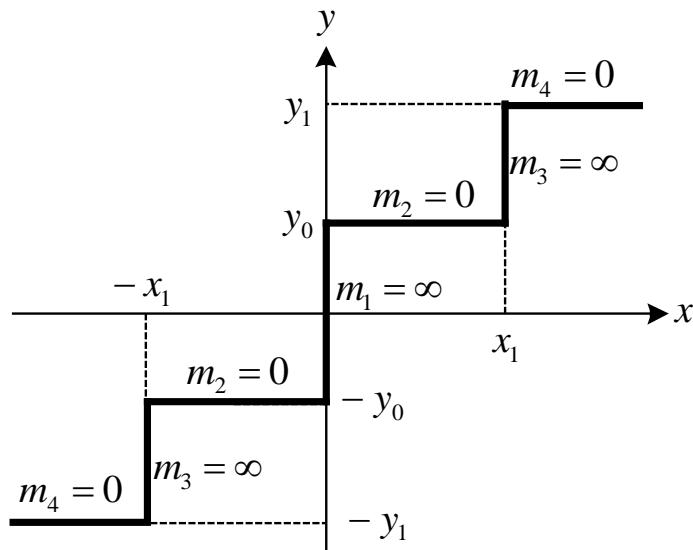- Back to our 4-level example:
 - By applying a sinusoidal to the previously found optimum nonlinear block the following output (Red) can be obtained



Harmonic Distortion: 4-Level Case

- The first three odd harmonic of the **output** can be expressed as

$$a_c(\omega_0) = y_2 \left\{ \frac{y_1}{y_2} + \cos\left(\frac{2\pi}{T_1}\right) \right\} a_0(\omega_0)$$

$$a_c(3\omega_0) = y_2 \left\{ \frac{y_1}{y_2} + \cos\left(\frac{6\pi}{T_1}\right) \right\} a_0(3\omega_0)$$

$$a_c(5\omega_0) = y_2 \left\{ \frac{y_1}{y_2} + \cos\left(\frac{10\pi}{T_1}\right) \right\} a_0(5\omega_0)$$

Where $a_0(n\omega_0)$ are the nth harmonic of a rectangular wave at f_0 and amplitude of 1.

Harmonic Distortion: 4-Level Case


- It can be proven that for the following parameters the $a_c(3\omega_0)$ and $a_c(5\omega_0)$ become zero:

$$\frac{y_2}{y_1} = \sqrt{2}$$

$$t_1 = \frac{T}{8}$$


Harmonic Distortion: N-Level Case

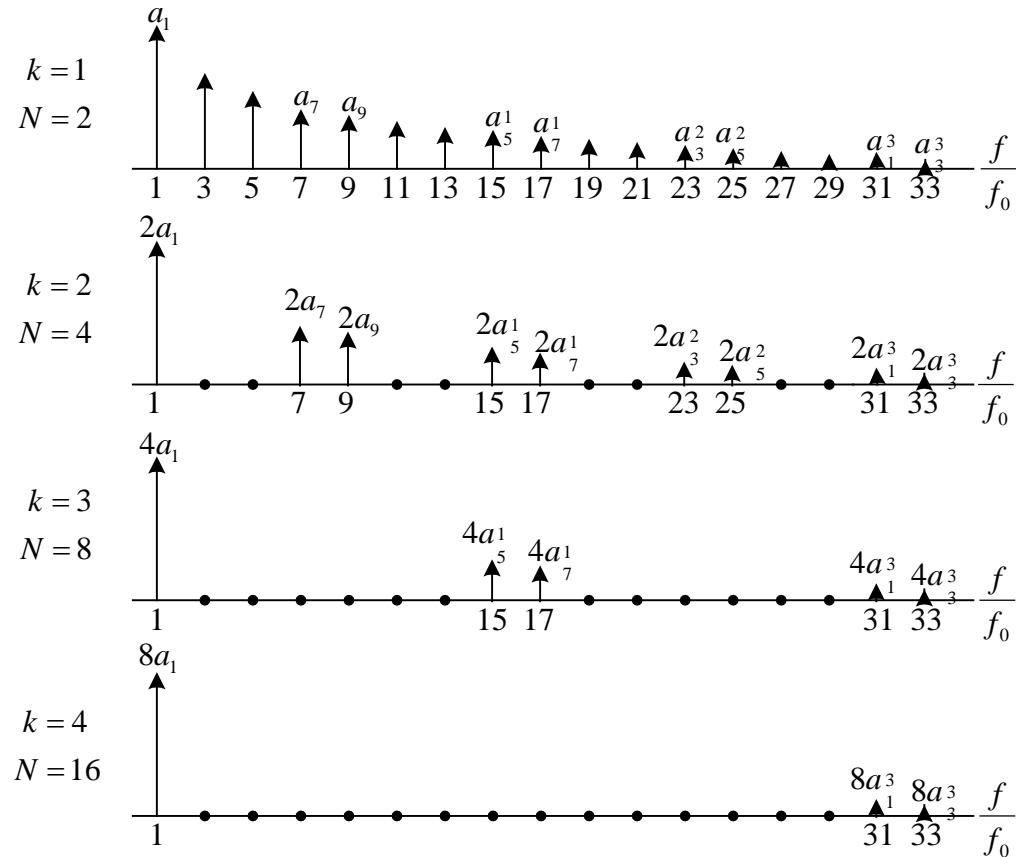- For the general N-level nonlinearity function and for specific values of N and K it can be shown that the first odd harmonics, based on the following figure, become zero.




Nonidealities

- Non-idealities:

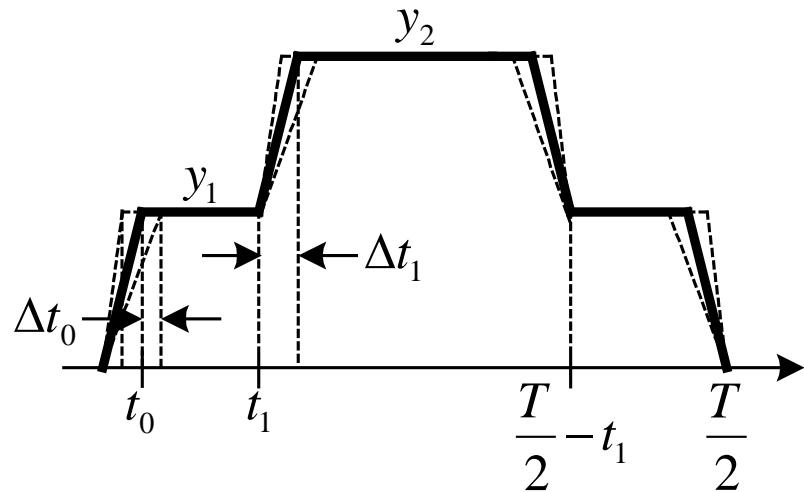

$$\hat{a}_c(n\omega_0) = \frac{\left(1 - (-1)^n\right) \text{sinc}\left(\frac{n\omega_0 t_0}{2}\right)}{n\pi} \left[y_1 \cos\left(\frac{n\omega_0 t_0}{2}\right) + (y_2 - y_1) \cos\left(n\omega_0(t_1 + \frac{\Delta t_1}{2})\right) \right]$$

Nonidealities


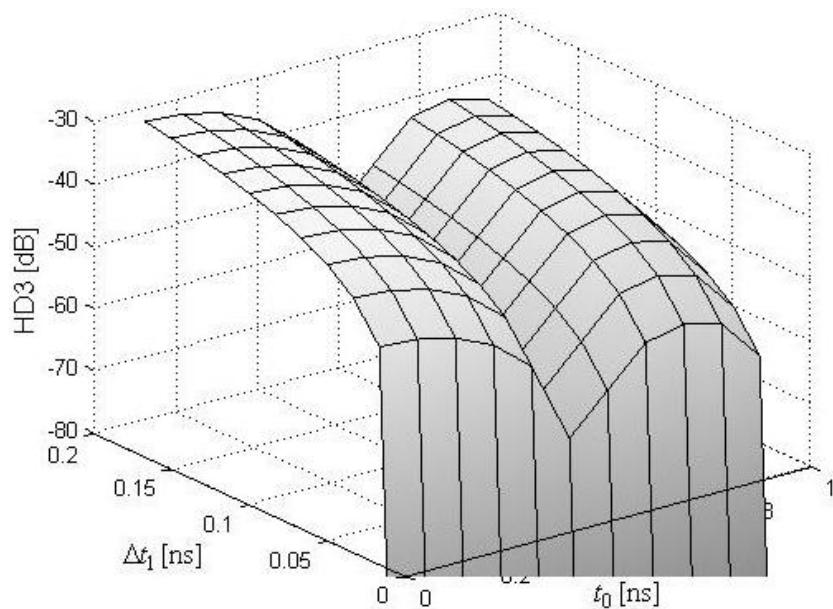


To be added

- HD3 and HD5 of the 4-level nonlinearity. Note that at $t_0=\Delta t_1=0$, $HD3=HD5=-\infty$


Nonidealities

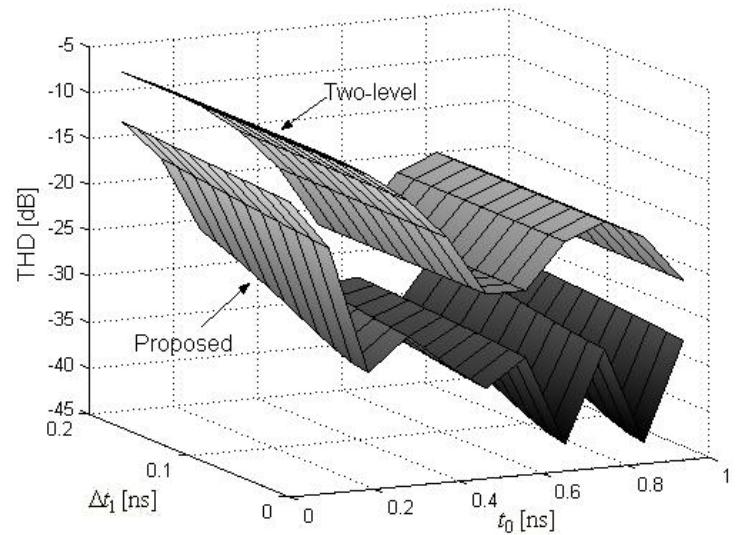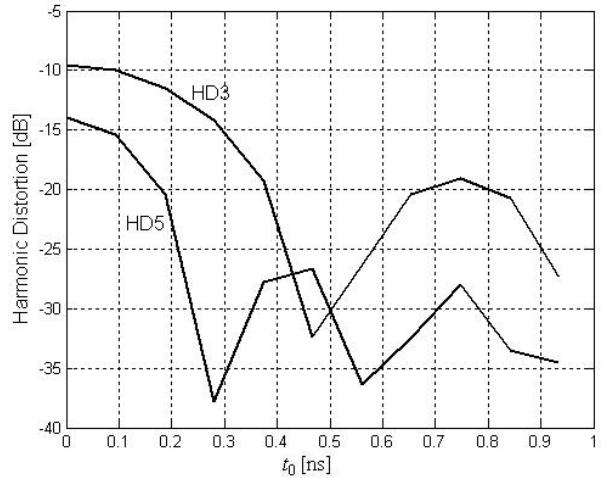- HD3 and HD5 for a 2-level (comparator)
- Total THD:
 - At least 20dB improvement in 4-level nonlinearity




Implementation

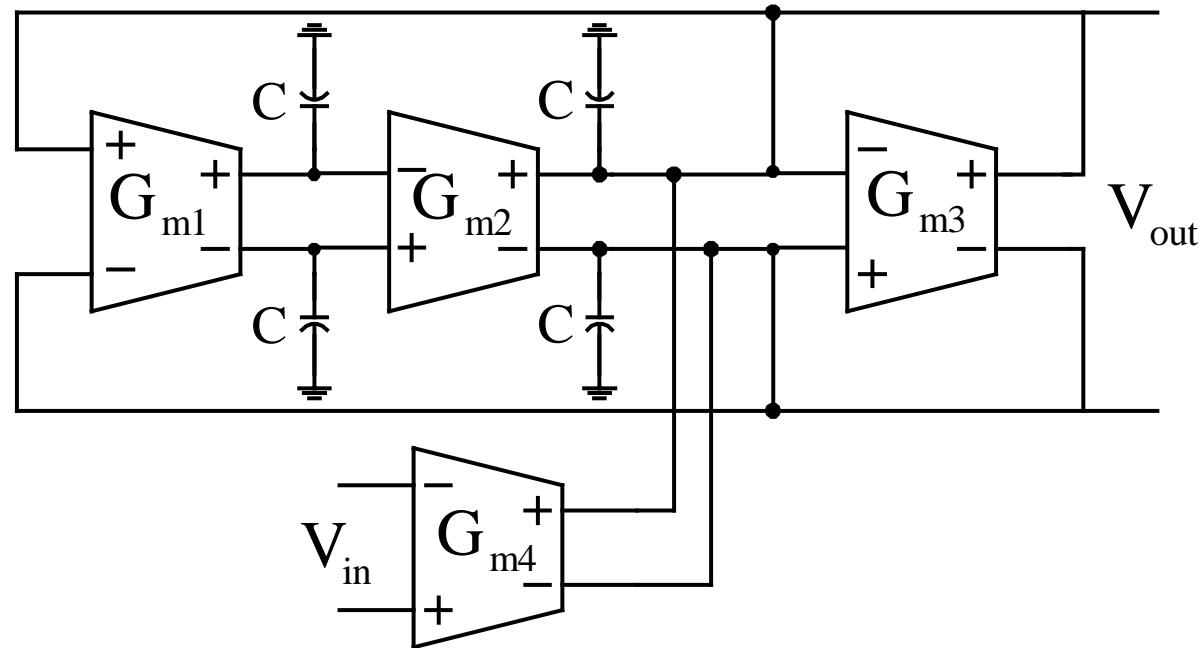- Bandpass filter: A simple Gm-C biquad with a Q of 15





Implementation

- Implementation of the nonlinear block

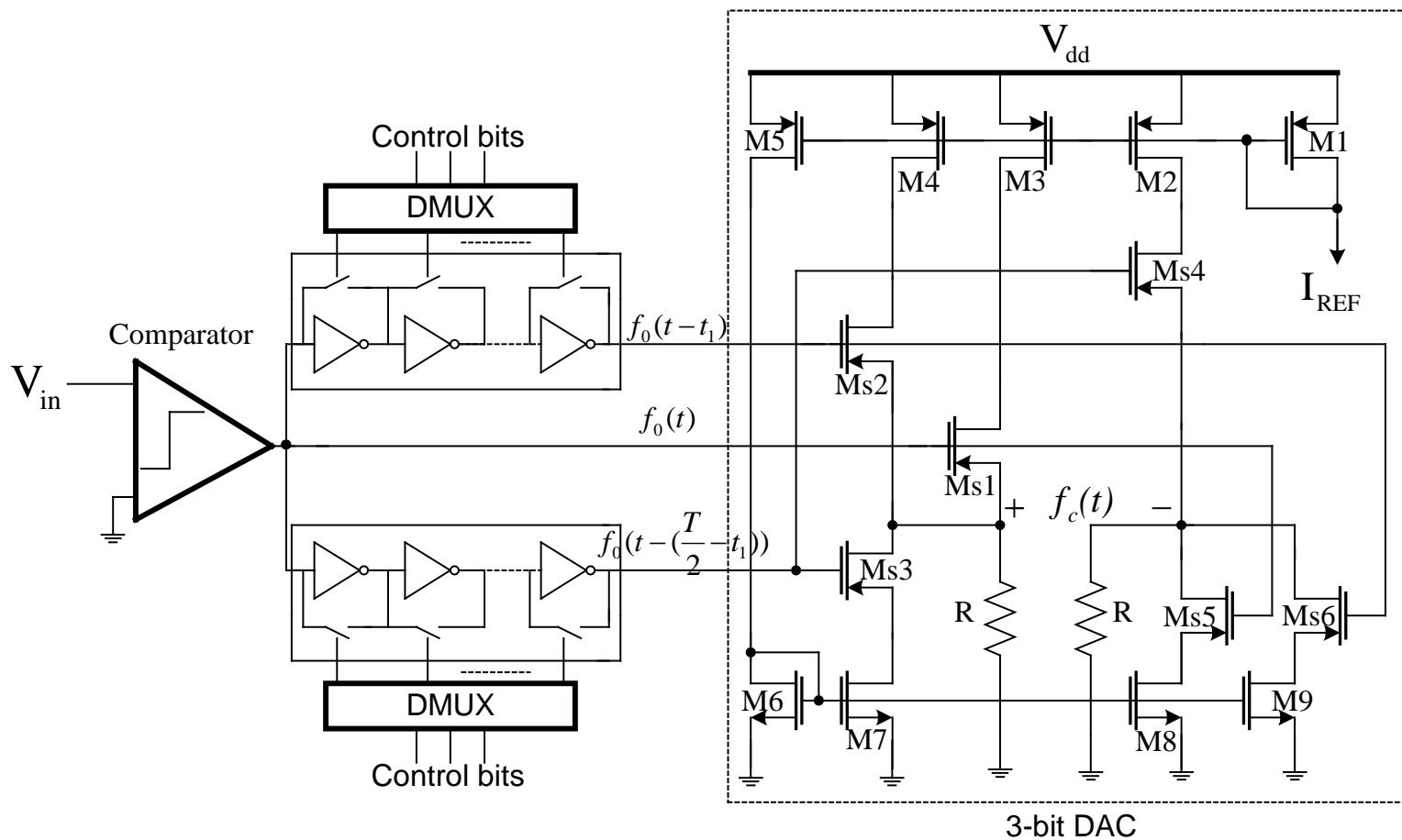


Implementation

- Silicon

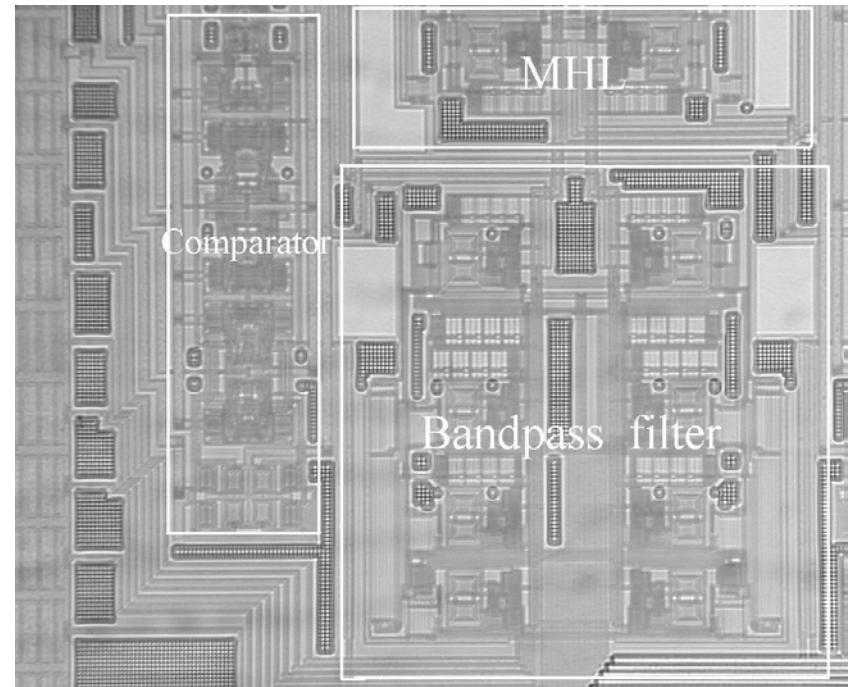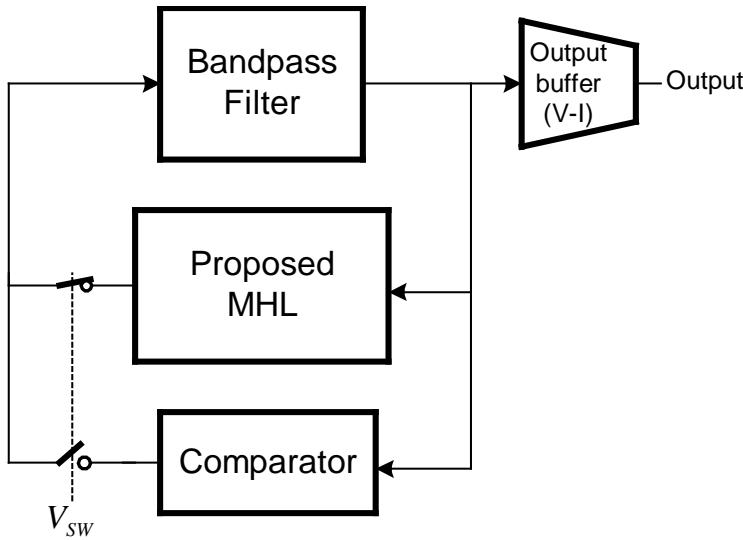


Measurement

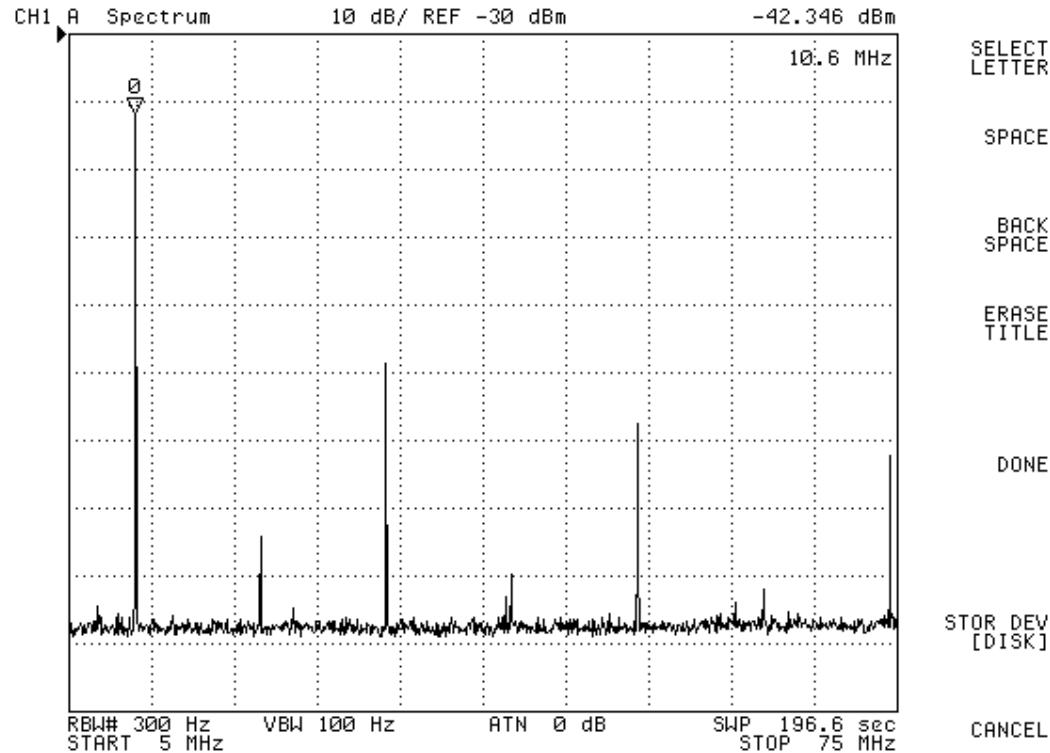- Oscillator with a 2-level (comparator) nonlinearity block



Measurement

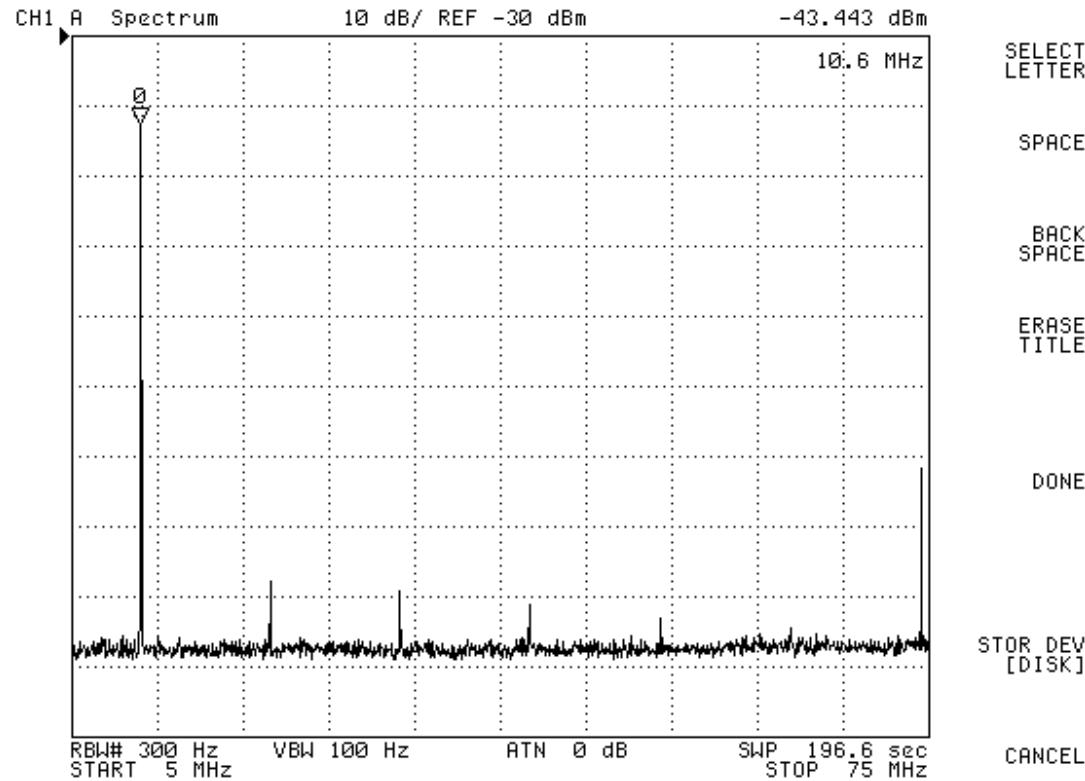- Oscillator with the proposed 4-level nonlinearity block



Measurement

- THD: Theory and measurement

