


HIGHER-ORDER FILTERS

- Cascade of Biquad Filters
- Follow the Leader
Feedback Filters (FLF)



CASCADE FILTER DESIGN
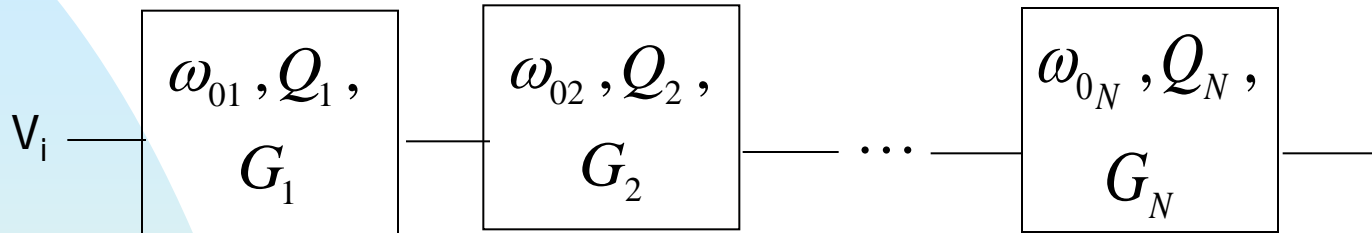
$$H(s) = \prod_{i=1}^N H_i(s) = H_1(s) H_2(s) \cdots H_N(s)$$



Is the order in which sections are connected important?

- Mathematically is irrelevant
- On one hand, to avoid loss of dynamic and to avoid signal clipping in the high-Q sections use:

$$Q_1 < Q_2 < \cdots Q_N$$

- On the other to minimize noise, use

$$Q_1 > Q_2 > \cdots Q_N$$

- What is the optimal ordering to yield the best S/N?



$$H_i(s) = k_i \frac{a_{2i}s^2 + a_{1i}s + a_{0i}}{s^2 + s^{\omega_{oi}} / Q_i + \omega_{oi}^2}$$

$$H(s) = \prod_{i=1}^{n/2} k_i t_i(s)$$

n is even

How do we assign pole-zero pairs?

Proposition 1. Minimize the maximum value of d_i where

$$d_i = \log \frac{G_i}{m_i}$$

, G_i and m_i are the maximum and minimum gain in the

frequency range of interest, $\omega_L \leq \omega \leq \omega_H$. Then determine the optimal

sequence of the biquad sections, such that again the maximum number d_i is minimized. The final step is to assign the gain constants (k_i) of the biquads. To yield optimal dynamic range i.e. ,

$$\max |V_{oi}(j\omega)| = \max |V_{o,n/2}(j\omega)| = \max |V_{out}(j\omega)|$$

Proposition 2. To jointly optimize signal gain and noise gain. Noise by itself is minimized by assigning the largest possible gain to the first-stage, then the second with the largest gain among the other stages and so on.




Realization of High Order Transfer Functions ($N > 2$)

- Cascade of 2nd order sections (one 1st order section if N is odd)
- Leapfrog
- Follow-The-Leader

	Cascade	FLF	Leap-Frog
Sensitivity	High	Medium	Low
Easy to Tune	Medium	Easy	Difficult




Primary Resonator Block

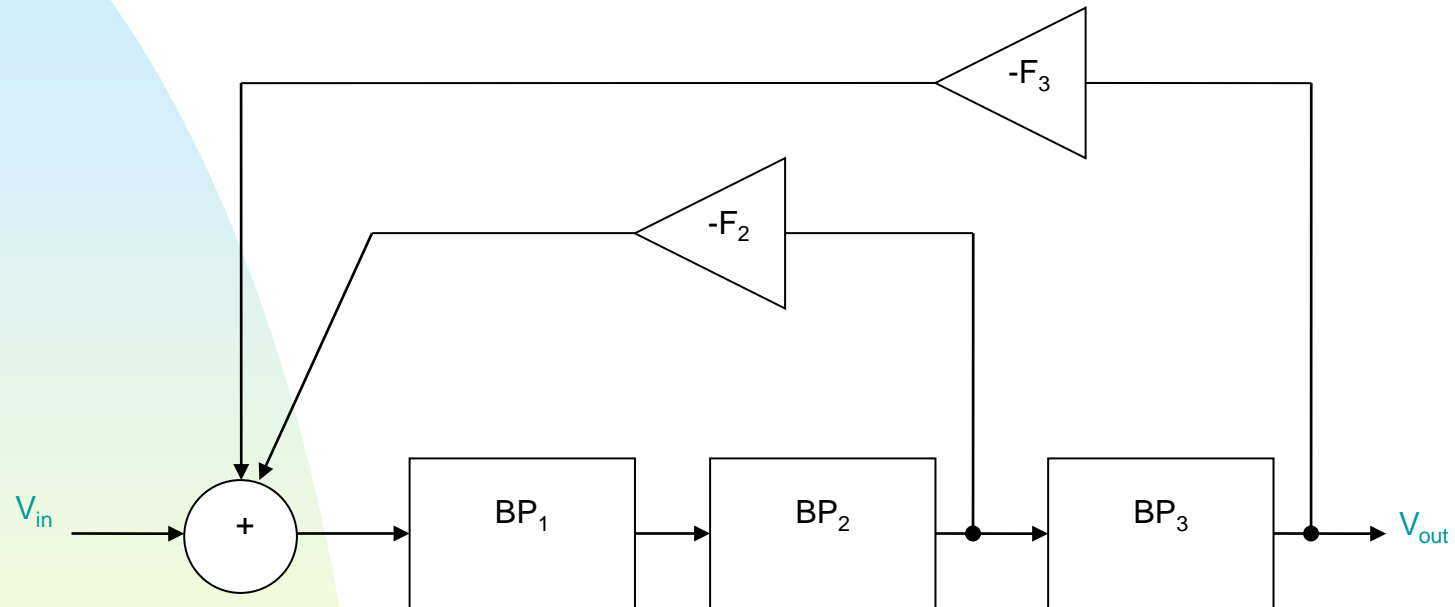

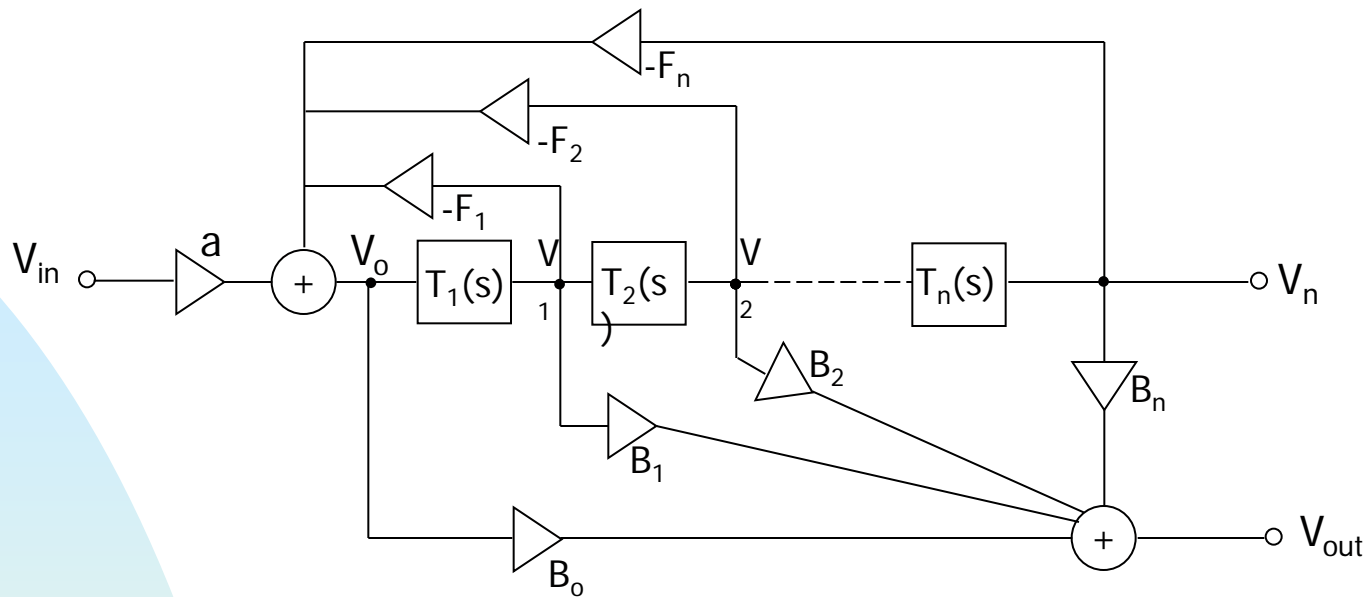- It provides compensatory internal interactions between the different filter sections through coupling the biquad building blocks.
- F_1 is incorporated in BP₁.





Follow-the-Leader Feedback Filter Topology

$$H_n(s) = \frac{V_n}{V_{in}} = \frac{a \prod_{j=1}^n T_j(s)}{1 + \sum_{k=1}^n \left[F_k \prod_{j=1}^k T_j(s) \right]}$$

$$H(s) = \frac{V_{out}}{V_{in}} = a \frac{B_o + \sum_{k=1}^n \left[B_k \prod_{j=1}^k T_j(s) \right]}{1 + \sum_{k=1}^n \left[F_k \prod_{j=1}^k T_j(s) \right]}$$



Design Questions:



- How do we obtain the feedback coefficients F_2 and F_3 ?
- How do we determine the specifications for each biquadratic section?

→ Q


→ ω_0

→ Gain



Design Procedure

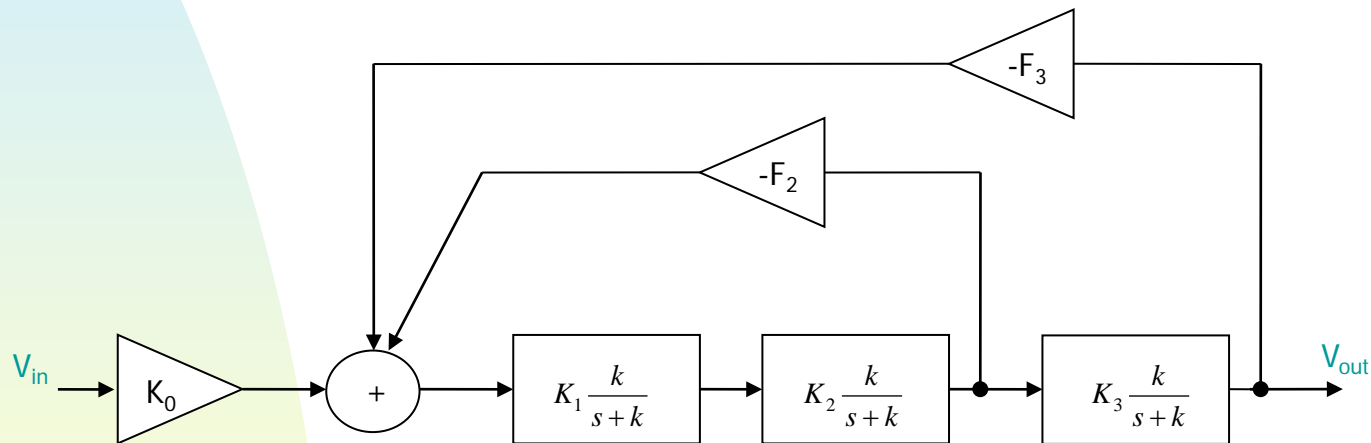
- Start with the Lowpass equivalent system.



However Elliptic Filters need finite zeros in their lowpass equivalent transfer function.



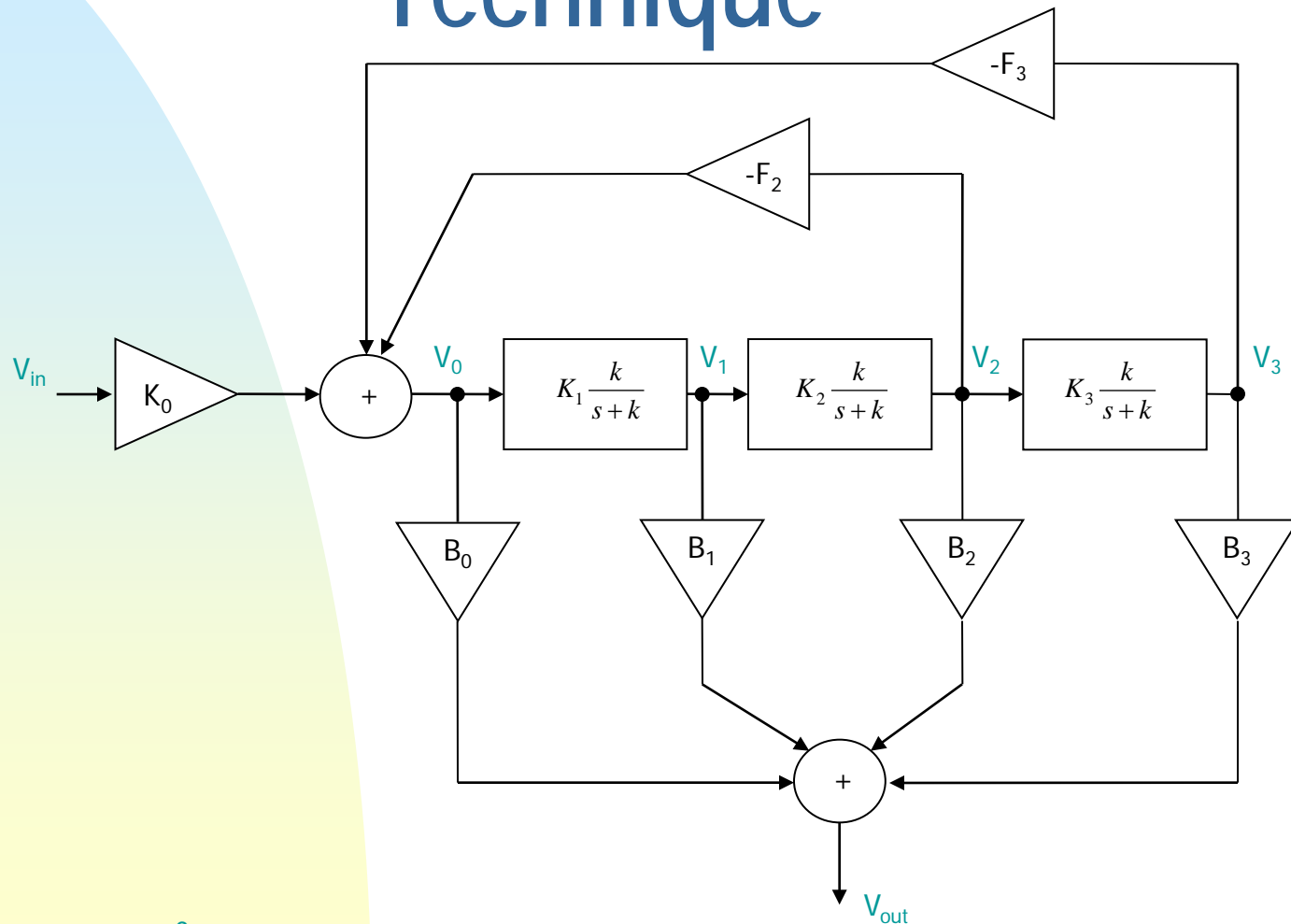Implementation of Finite Zeros by the Summation Technique



EXAMPLE

- To design a 6th order bandpass elliptic filter using the Follow-the-Leader (FLF) architecture. The specifications are:

Specification	Value
Order	6
Passband	1.9MHz to 2.1MHz
Passband Ripple	0.1dB
Attenuation	≥ 30 dB at 0.6MHz



Design Procedure

Let for now $K_1=K_2=K_3=1$

and

$$T(s) = \frac{k}{s+k} \quad (1)$$

Applying Mason's rule, the complete transfer function is given by:

$$\begin{aligned} H(s) &= \frac{V_{out}(s)}{V_{in}(s)} = K_0 \frac{B_0 + B_1T(s) + B_2T^2(s) + B_3T^3(s)}{1 + F_2T^2(s) + F_3T^3(s)} \\ &= K_0 \frac{B_0(s+k)^3 + B_1k(s+k)^2 + B_2k^2(s+k) + B_3k^3}{(s+k)^3 + F_2k^2(s+k) + F_3k^3} \quad (2) \end{aligned}$$



Design Procedure

- From Matlab or Fiesta, we can obtain the lowpass prototype transfer function of the desired 6th Order Elliptic Filter:

$$H(s) = m \frac{a_0 b_3 s^3 + b_2 s^2 + b_1 s + b_0}{b_0 s^3 + a_2 s^2 + a_1 s + a_0} \quad (3)$$

- Equating the denominators of equations (2) and (3), we obtain the following set of equations from which we can solve for k , F_2 , and F_3 .

$$3k = a_2 \quad (4)$$

$$3k^2 + F_2 k^2 = a_1$$

$$(1 + F_2 + F_3)k^3 = a_0$$

- Also from equations (2) and (3)

(5)

$$K_0 = m \frac{a_0}{b_0}$$



Design Procedure

- To obtain the summation coefficients, we equate the numerators of equations (2) and (3). If $H(s)$ is a bandpass: $B_0=b_3=0$. Then, we obtain the following set of equations from which we can determine B_1 , B_2 and B_3 .

$$B_0 = b_3 = 0$$

$$B_1 k = b_2 \tag{6}$$

$$2B_1 k + B_2 k^2 = b_1$$

$$(B_1 + B_2 + B_3)k^3 = b_0$$



Designing for Maximum Dynamic Range

- We need to distribute the gains of each section $T(s)$, i.e. K_1 , K_2 and K_3 such that we maximize the Dynamic Range.
- The maximum dynamic range will be obtained if the signal spectra at the output of all sections have equal maxima, i.e.

$$V_{\text{out,max}} = V_{3,\text{max}} = V_{2,\text{max}} = V_{1,\text{max}} = V_{0,\text{max}}$$



Maximizing Dynamic Range

- To make $V_{3,\max} = V_{out,\max}$

$$K_0 \rightarrow K'_0 = K_0 q \quad (7)$$

where

$$q = \frac{V_{out,\max} \leftarrow \text{prior to scaling}}{V_{3,\max} \leftarrow \text{prior to scaling}} \quad (8)$$

- We also need to adjust the summation coefficients to keep the overall gain:

(9)

If we assume a flat spectrum for the $B_i \rightarrow B'_i = \frac{B_i}{q}$ input, i.e. $V_{in}(\omega) = 1$

(10)

$$V_{out,\max} = \text{Max}|H(\omega)|$$

$$V_{3,\max} = \text{Max}|H_3(\omega)|$$



Gain Values Determination

Where

$$H_3(s) = \frac{V_3(s)}{V_{in}(s)} = K_0 \frac{k^3}{s^3 + a_2s^2 + a_1s + a_0} \quad (11)$$

- To obtain K_1 , K_2 and K_3 :

$$K_i = \frac{\text{Max} \left\{ \left| H_3(\omega) \left(\frac{k^2 + \omega^2}{\omega^2} \right)^{\frac{4-i}{2}} \right| \right\}}{\text{Max} \left\{ \left| H_3(\omega) \left(\frac{k^2 + \omega^2}{\omega^2} \right)^{\frac{3-i}{2}} \right| \right\}} \quad \text{for } i=1,2,3. \quad (12)$$



Feedback Coefficients

- The feedback coefficients need to be readjusted to keep the same loop gains:

$$F_2 \rightarrow F'_2 = \frac{F_2}{K_1 K_2} \quad (13)$$

$$F_3 \rightarrow F'_3 = \frac{F_3}{K_1 K_2 K_3}$$

- The summation coefficients also need to be readjusted again:

$$B_1 \rightarrow B'_1 = B_1 \frac{K_2 K_3}{q} \quad (14)$$

$$B_2 \rightarrow B'_2 = B_2 \frac{K_3}{q}$$

$$B_3 \rightarrow B'_3 = B_3 \frac{1}{q}$$



Summary of Design Procedure

- Obtain from Matlab or Fiesta the lowpass prototype for the desired filter.
- From equations (4), (5) and (6), obtain K_0 , the feedback and the summation coefficients.
- To maximize dynamic range, obtain q using equation (8). Recalculate K_0 using equation (7).
- Calculate the gain of each section, i.e. K_1 , K_2 and K_3 using equation (12).
- Recalculate the feedback and summation coefficients using equations (13) and (14).
- Finally, apply a lowpass-to-bandpass transformation to obtain the desired bandpass filter specifications:

$$\omega_0 = 2\pi\sqrt{f_L f_U}$$

$$Q_0 = \frac{Q}{k}$$

where Q is the quality factor of the overall filter and Q_0 is that required for each biquad section.

- Note: A Matlab program was written to automate the design procedure for an arbitrary filter specification of order N .



Summary of Results


- For the required specifications, the following values were obtained:

Feedback Coefficients	F2 = 0.657640 F3 = 0.227545
Feedforward Coefficients	B0 = 0 B1 = 0.169792 B2 = -0.216571 B3 = 1.129814
Gain for the input and each biquad stage	K0 = 0.604488 K1 = 2.349 K2 = 2.165 K3 = 2
Center frequency and Q_0 of each biquad stage	$f_0 = 1.9975\text{MHz}$ $Q_0 = 15.7$





Simulation Results System Level

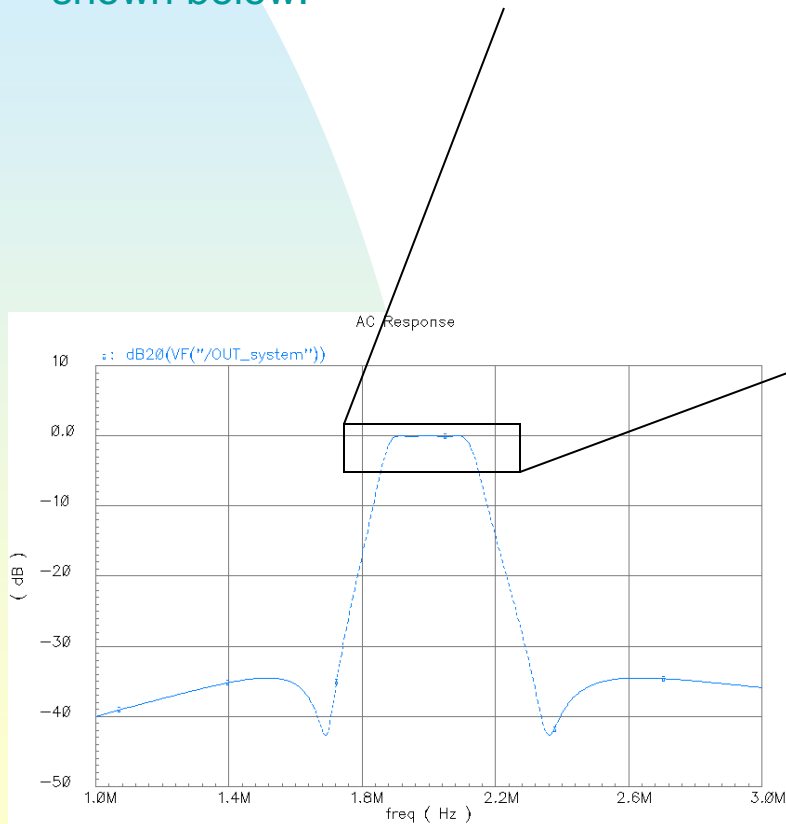- The complete filter was simulated in Cadence at a system-level. The results are shown below:



20
Magnitude Response

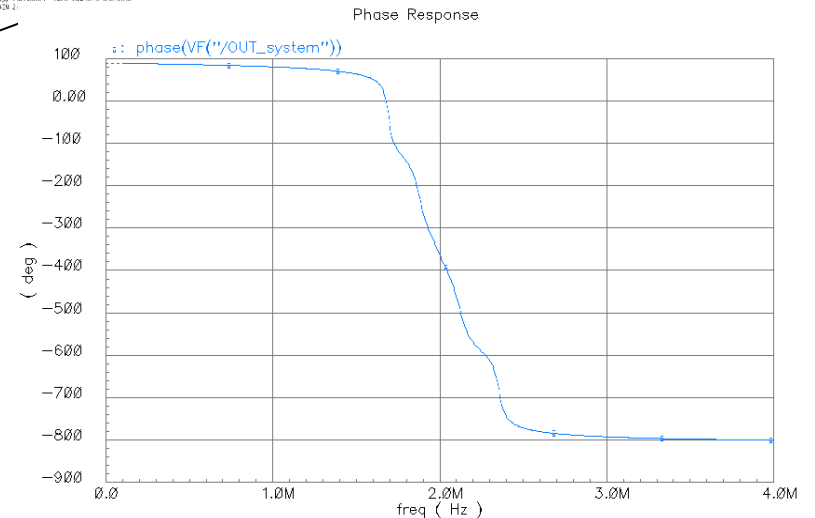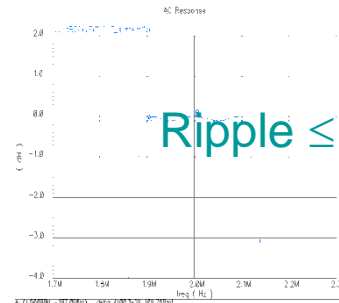

Phase Response

[Jump to first page](#)




Transistor Level Implementation

- To implement each biquadratic section, a two-integrator loop biquad OTA-C filter was used.
- Advantages with respect to Active-RC:
 - ◆ Easy Tunability by changing the bias currents of the OTAs. (Active-RC needs the use of varactors).
 - ◆ Lower Power Consumption and Smaller Area.
- Disadvantages with respect to Active-RC:
 - ◆ Smaller Dynamic Range
 - ◆ Poorer Linearity



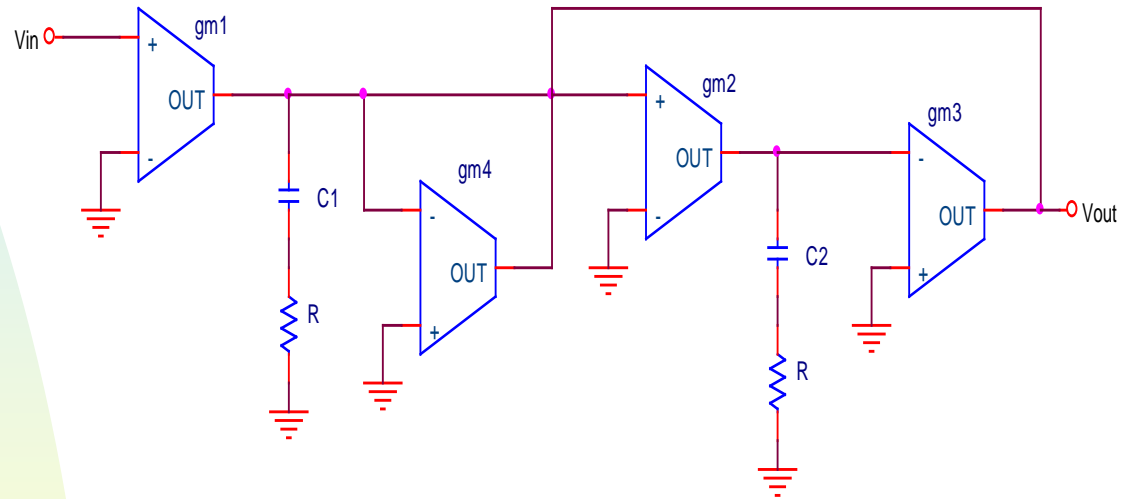Transistor Level Implementation of each Biquad Section



$$H(s) = \frac{s \frac{g_{m1}}{C_1}}{s^2 + s \frac{g_{m4}}{C_1} + \frac{g_{m2} g_{m3}}{C_2 C_1}}$$



Design of Lossless Integrator

- The lossless integrator was designed to have unity gain at $f_0=1.9975\text{MHz}$.

$$|H(\omega)| = \frac{g_{m2}}{\omega C_2} = 1$$

$$g_{m3} = 376.52 \mu\text{A/V}$$

$$C_2 = 30 \text{ pF}$$

- The following specifications are needed if a 5% variation in Q is allowed:


$$\text{Excess Phase: } \phi_E \leq \frac{1}{2Q} \left(1 - \frac{Q}{Q_a} \right) = 1.5 \times 10^{-3} \text{ rad} = 0.086^\circ$$

$$\text{DC Gain: } A_V \geq \frac{2Q}{\frac{Q}{Q_a} - 1} = 602 = 55.58 \text{ dB}$$



Design of Lossless Integrator

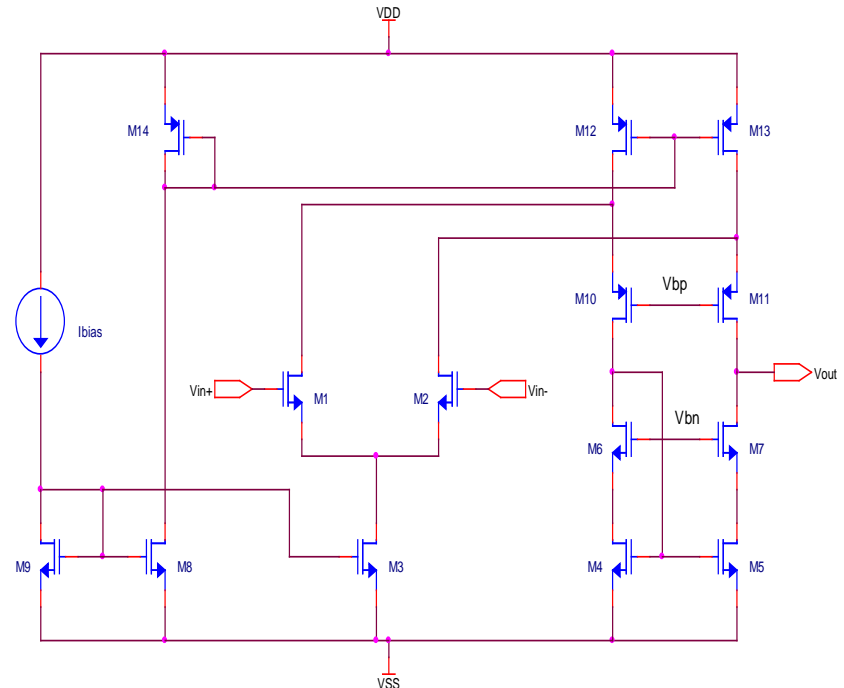- Due to the relatively high DC gain required for the OTA, a folded-cascode topology was used:




Transconductance	DC Gain	GBW	Bias Current	Power Consumption	Active Area
$376.52\mu\text{A/V}$	64.1dB	263MHz	$40\mu\text{A}$	$792\mu\text{W}$	$727\mu\text{m}^2$




Simulation Results of the Lossless Integrator

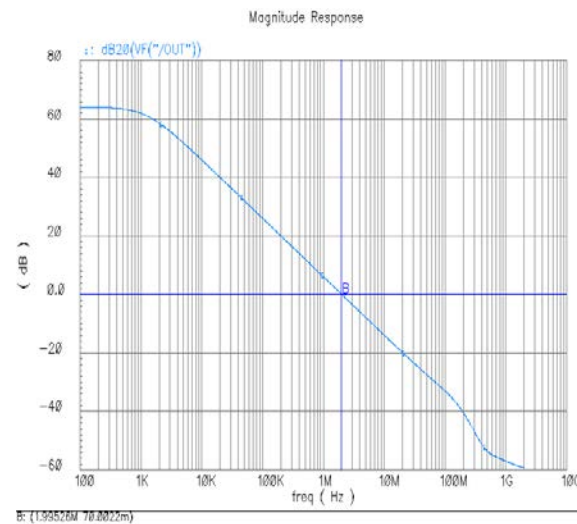- The excess phase without any compensation was 1.17° .
- Passive excess phase compensation was used $\rightarrow R=55\Omega$.



Magnitude Response

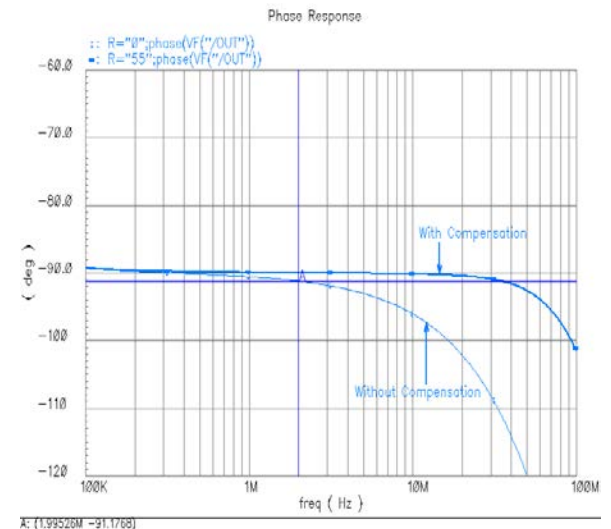

Phase Response



Design of Biquadratic Bandpass Filter

- To reuse the designed OTA:

$$g_{m3} = g_{m2} = 376.52 \mu\text{A}/\text{V}$$

$$C_1 = C_2 = 30 \text{ pF}$$

$$g_{m4} = \frac{C_1}{Q_0} \omega_0 = 23.827 \mu\text{A}/\text{V}$$

- Transconductance g_{m1} depends on K_i


$$g_{m1} = K_i g_{m4}$$

- For demonstrations purposes, $g_{m1} = g_{m4}$, i.e. $K=1$



Design of Biquadratic Bandpass Filter


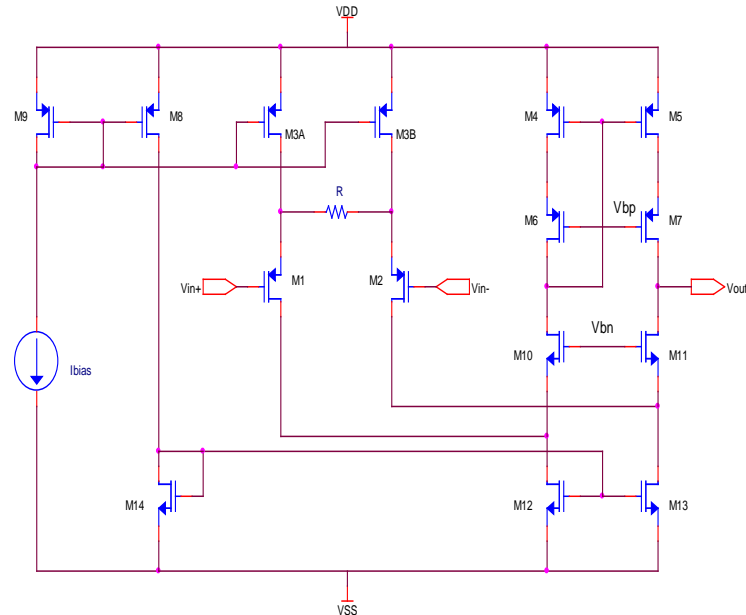
- Due to the relatively small transconductance required, source degeneration was used. Also, a PMOS differential pair was more suitable.



Transconductance	DC Gain	GBW	Bias Current	Power Consumption	Active Area
23.827 μ A/V	61.15dB	62.3MHz	14 μ A	277.2 μ W	820 μ m ²



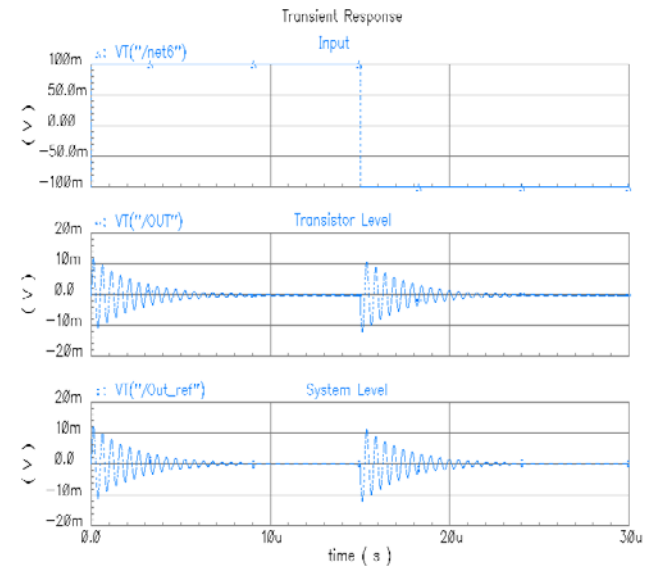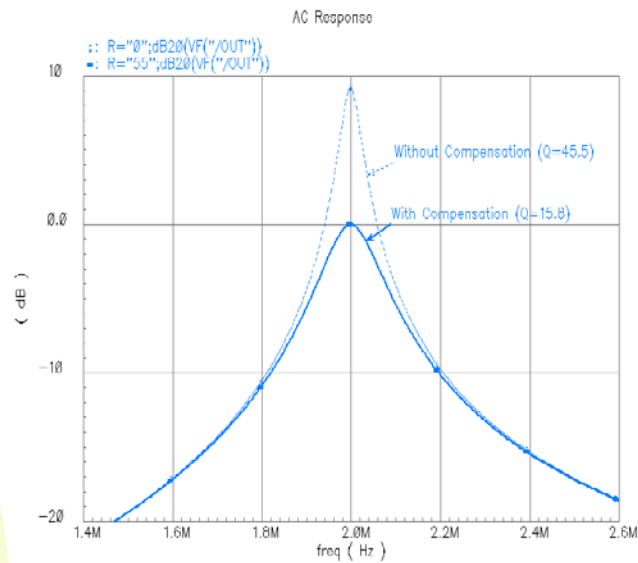Simulation Results of the Biquadratic Bandpass Filter




Frequency Response

Step Response




Summation Nodes

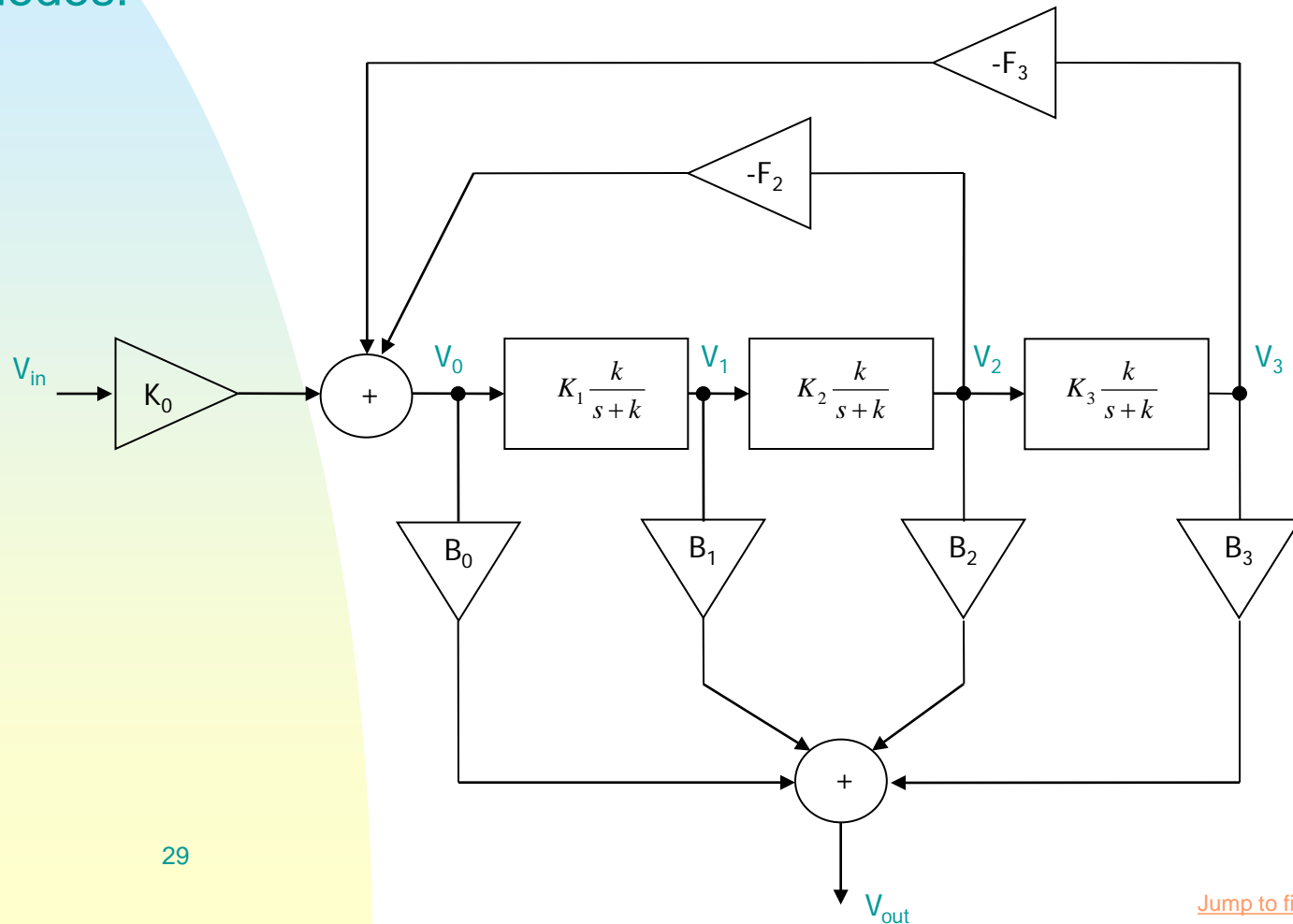- To complete the transistor-level design, we need two summation nodes:




Summation Nodes

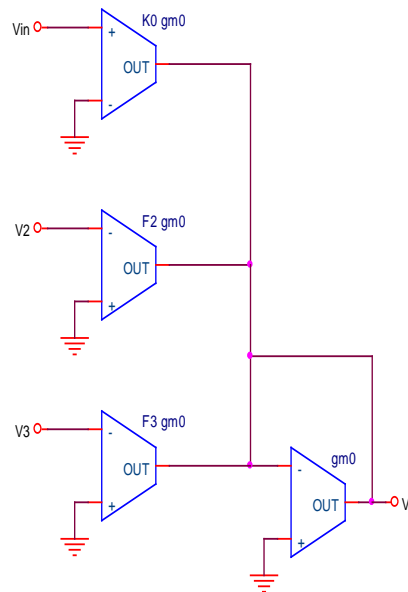The summation nodes can be implemented with OTAs in the following configurations:



Summation Node for the Feedback Paths

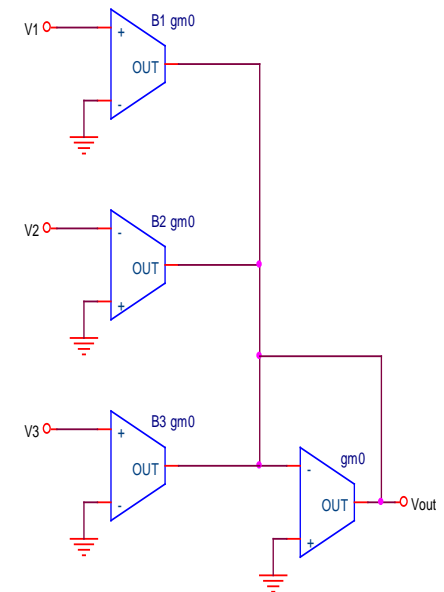


Summation Node at the Output

If g_{m0} is chosen large enough, the output resistance of each OTA does not need to be very high. Excess Phase of OTAs can be a concern.



Summation Nodes


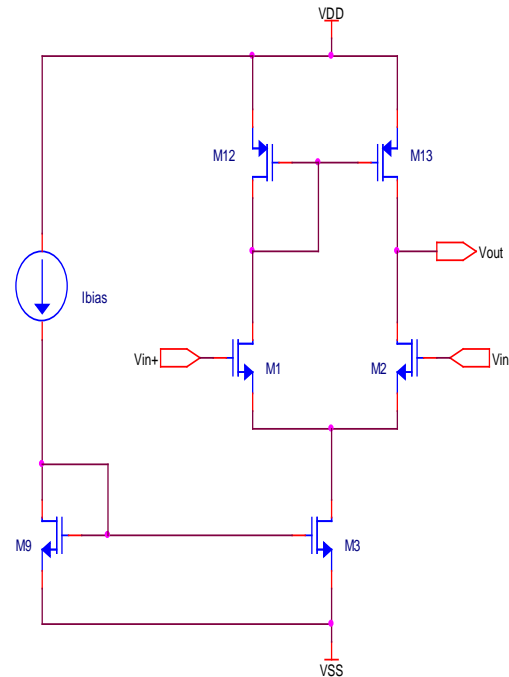
- Due to the desired low excess phase introduced by the OTAs, it is more convenient to use a simple differential pair.




Transconductance	Bias Current	Power Consumption	Active Area
300 $\mu\text{A/V}$	40 μA	264 μW	269 μm^2



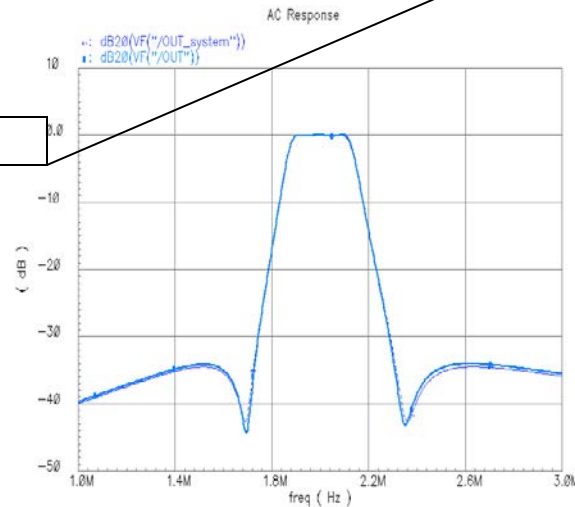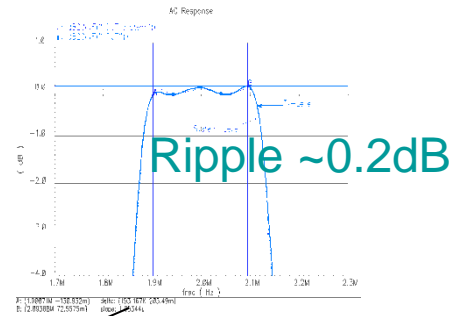Simulation Results of the Complete FLF Filter (Transistor vs. System Level)




Magnitude Response

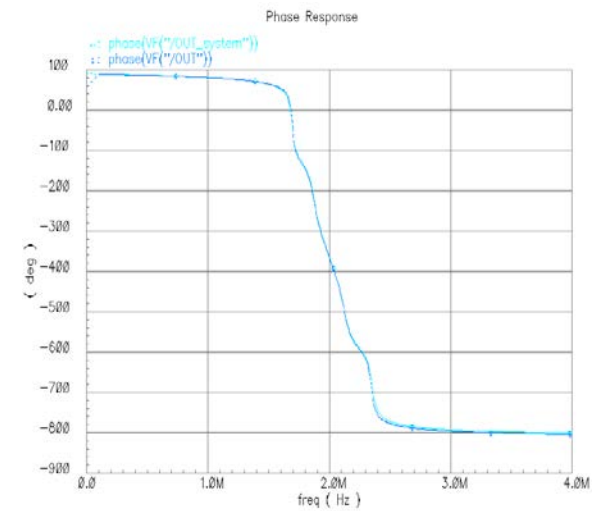


Phase Response



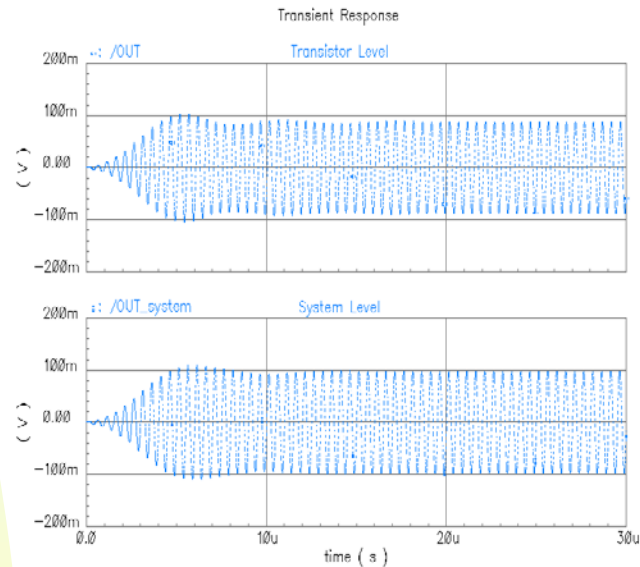Simulation Results of the Complete FLF Filter (Transistor vs. System Level)



Transient Response to a Sinewave

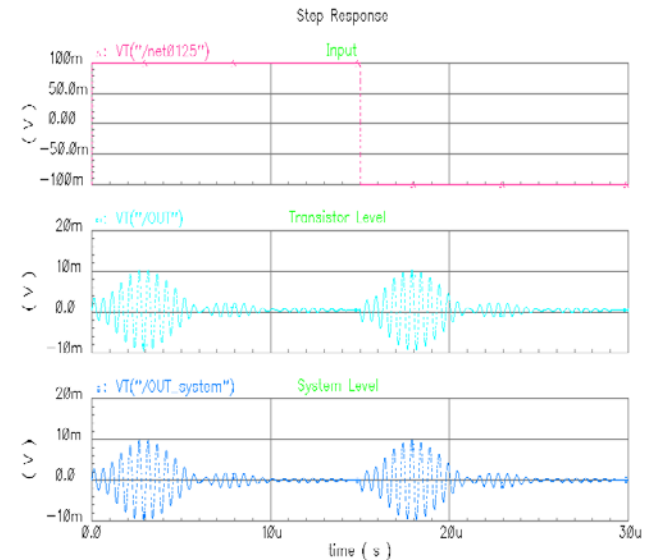

Step Response



Summary of Results

Specification	Value
Passband	1.9MHz to 2.1MHz
Passband Ripple	~0.2dB
Attenuation	≥ 40 dB at 0.6MHz
Power Consumption	8.53mW
Active Area	11,434 μm^2
Total Area	~ 211,549 μm^2




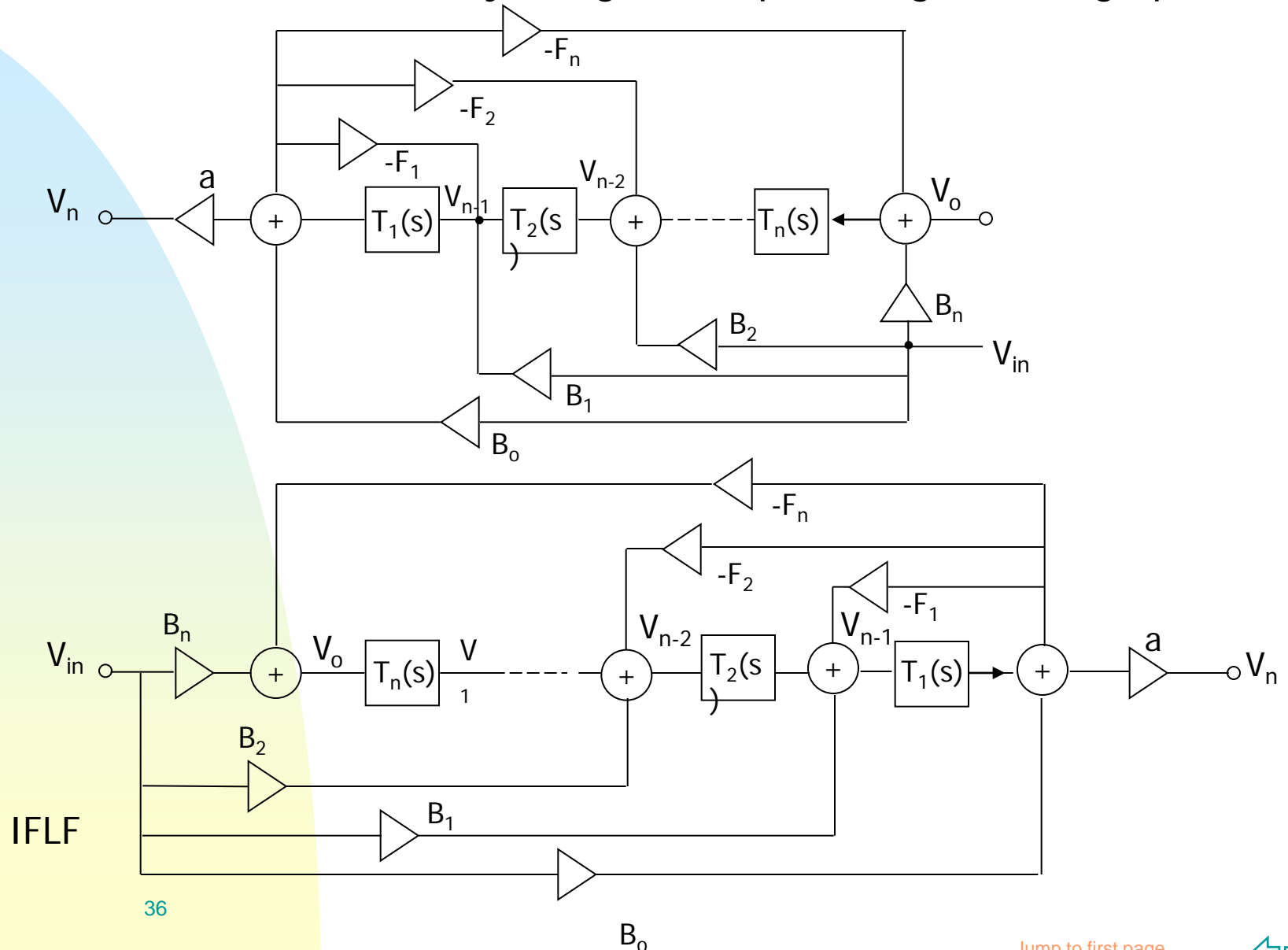Problems to be considered

- **Voltage Swing:** The allowable input voltage swing is only 100mV. A small voltage swing is expected, since the OTAs have a small linear range limited by $\pm V_{DSAT}$ of the input transistors (in case no linearization technique is used, such as source degeneration or others). Nevertheless, 100mV is too small and is basically because the OTAs with $g_m=376.52\mu A/V$ use input transistors with a small V_{DSAT} and no linearization technique is being used. I need to redesign these OTAs to increase the linear range.
- **Bias Network:** To design the bias network for the folded-cascode OTAs capable of effectively tracking changes of V_T due to process variations.
- **Sensitivity and Tunability:** To characterize the complete filter in terms of sensitivity and tunability.
- **Layout**



Another structure for higher-order filters that can be obtained from the FLF is the inverse FLF by using a transposed signal-flow graph.



References

- [1] Sedra, Brackett. Filter Theory and Design: Active and Passive. Matrix Series in Circuits and Systems. pp. 589-659.
- [2] Deliyannis, Sun, Fidler. Continuous-Time Active Filter Design. CRC Press 1999. pp. 151-180.
- [3] G. Hurtig, III. The Primary Resonator Block Technique of Filter Synthesis Proc. Int. Filter Symposium, p.84, 1972.
- [4] Barbargires. Explicit Design of General High-Order FLF OTA-C Filters. Electronics Letters. 5th August 1999, Vol. 35, No. 16, pp. 1289-1290.
- [5] Jie Wu, Ezz I. El-Masry. Synthesis of Follow-the-Leader Feedback Log-Domain Filters. IEEE 1998. 0-7803-5008-1/98. pp. 381-384.



References (cont.)

- [6] G. S. Moschytz, “Linear Integrated Networks-Design”, Van Nostrand, Reinhold, New York 1975
- [7] R. Schaumann, M.S. Ghaussi, and K.R. Laker, “Design of Analog Filters: Passive, Active RC and Switched Capacitor”, Prentice Hall, Englewood Cliffs, 1990.
- [8] A.S. Sedra, and P.O. Brackett, “Filter Theory and Design: Active and Passive”, Matrix, Portland 1978.
- [9] W.M. Snelgrove, and A.S. Sedra, “Optimization of Dynamic Range in Cascade Active Filters”, Proc. IEEE ISCAS, pp. 151-155, 1978.

