

# Follow The Leader Architecture

## 6<sup>th</sup> Order Elliptic Bandpass Filter

A numerical example

# Objective

- To design a 6th order bandpass elliptic filter using the Follow-the-Leader (FLF) architecture. The specifications are:


<b>Specification</b>	<b>Value</b>
Order	6
Passband	1.9MHz to 2.1MHz
Passband Ripple	0.1dB
Attenuation	$\geq 30$ dB at 0.6MHz

# Realization of High Order Transfer Functions ( $N > 2$ )

- Cascade of 2<sup>nd</sup> order sections (one 1<sup>st</sup> order section if  $N$  is odd)
- Leapfrog
- Follow-The-Leader

	Cascade	FLF	Leap-Frog
Sensitivity	High	Medium	Low
Easy to Tune	Medium	Easy	Difficult

# Primary Resonator Block

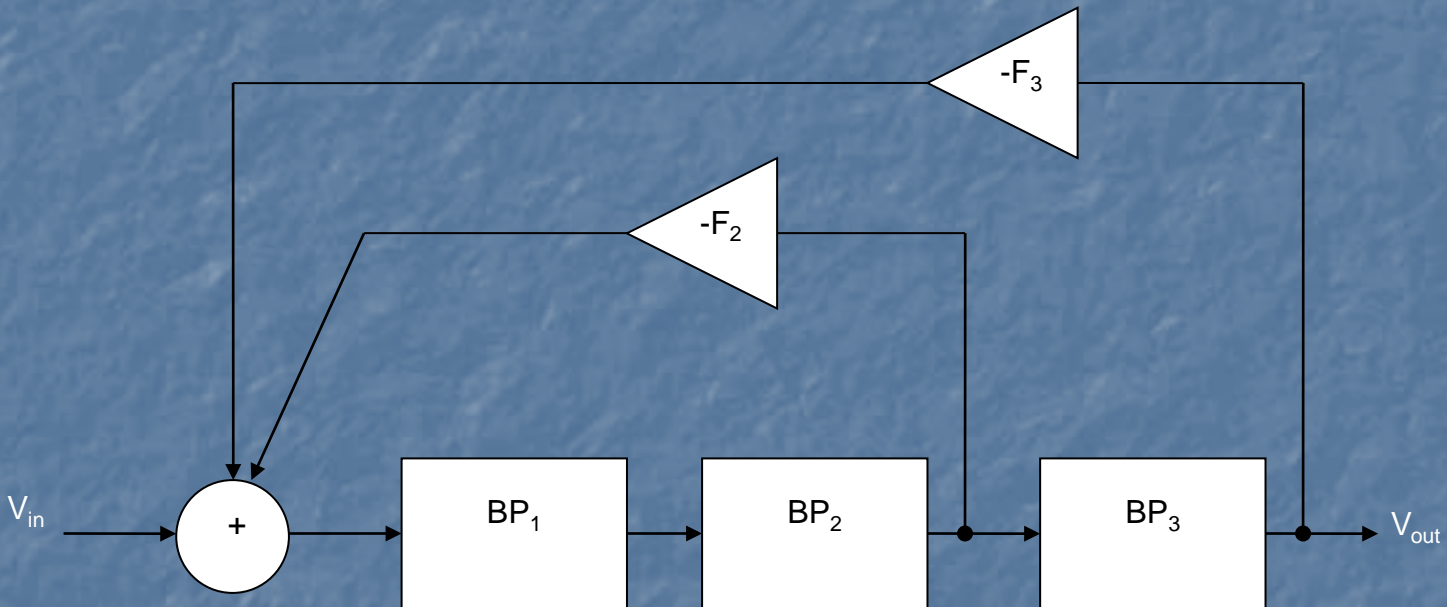

- It provides compensatory internal interactions between the different filter sections through coupling the biquad building blocks.


# Design Questions:



- How do we obtain the feedback coefficients  $F_2$  and  $F_3$ ?
- How do we determine the specifications for each biquadratic section?
  - $Q$
  - $\omega_0$
  - Gain

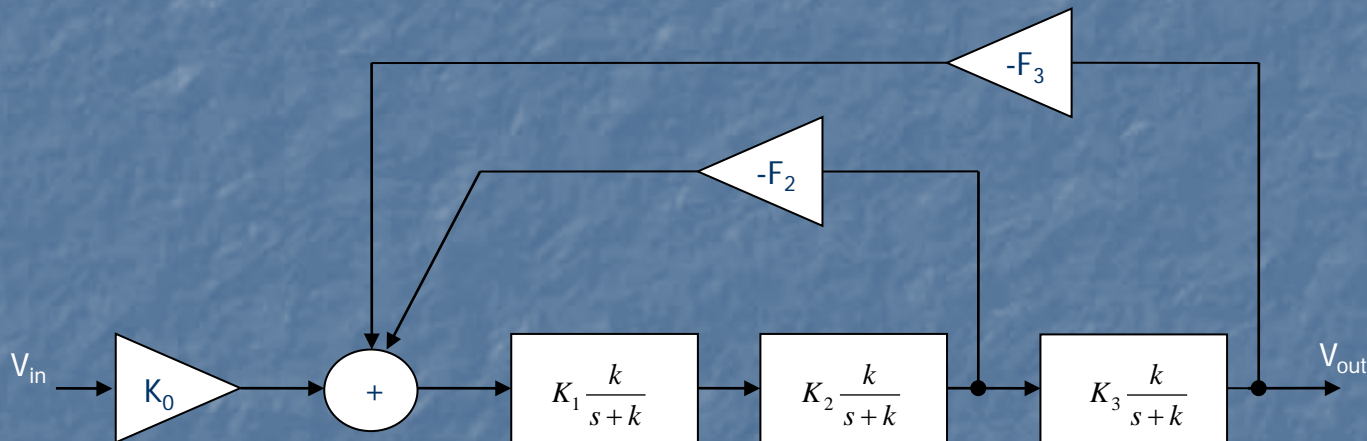
# Design Procedure

- Start with the Lowpass equivalent system.



- Bad News: Elliptic Filters need finite zeros in their lowpass equivalent transfer function.
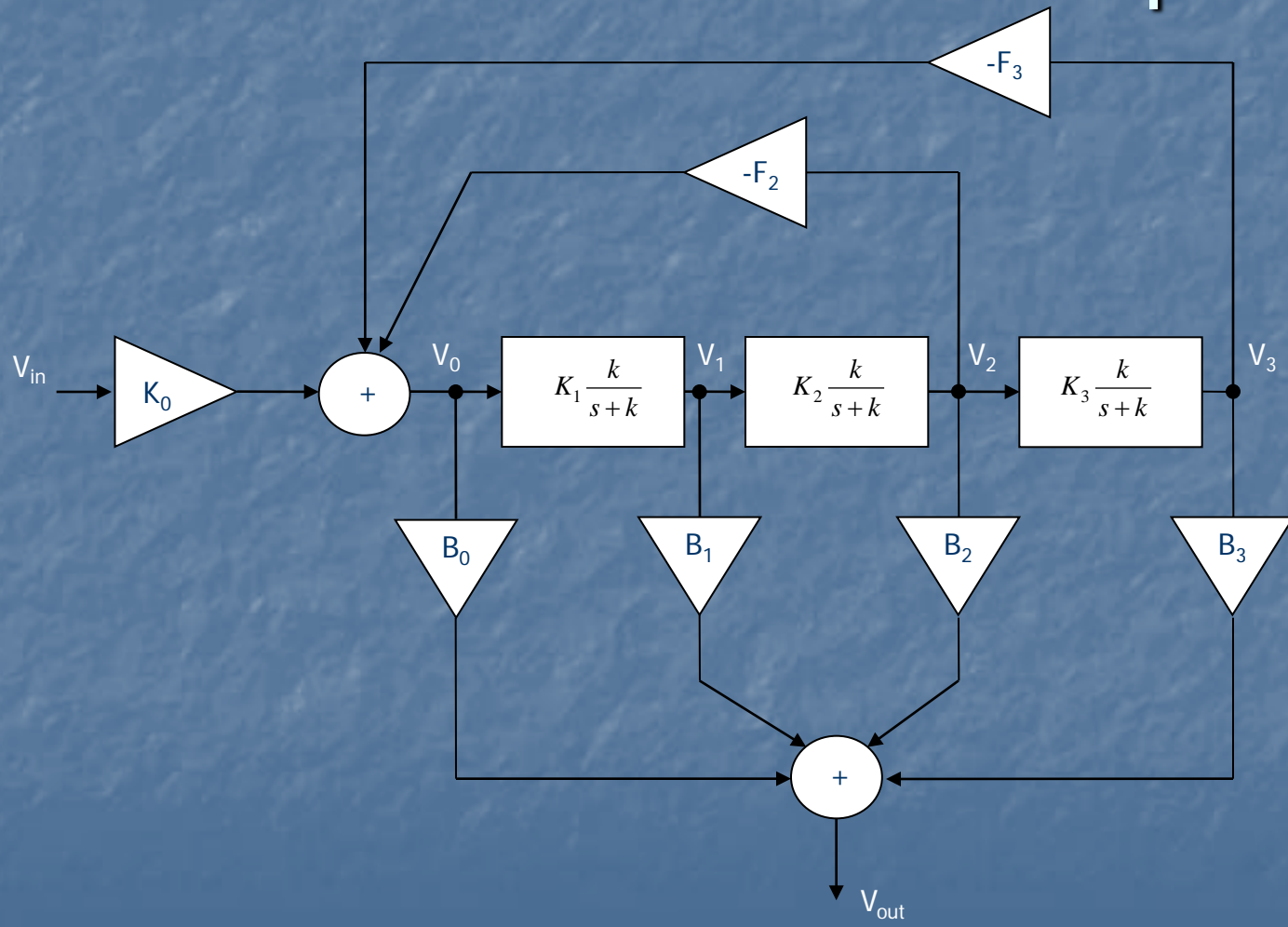
# Implementation of Finite Zeros by the Summation Technique



# Design Procedure

Let for now  $K_1=K_2=K_3=1$

and

$$T(s) = \frac{k}{s+k} \quad (1)$$

Applying Mason's rule, the complete transfer function is given by:

$$\begin{aligned} H(s) &= \frac{V_{out}(s)}{V_{in}(s)} = K_0 \frac{B_0 + B_1T(s) + B_2T^2(s) + B_3T^3(s)}{1 + F_2T^2(s) + F_3T^3(s)} \\ &= K_0 \frac{B_0(s+k)^3 + B_1k(s+k)^2 + B_2k^2(s+k) + B_3k^3}{(s+k)^3 + F_2k^2(s+k) + F_3k^3} \end{aligned} \quad (2)$$



# Design Procedure

- From Matlab or Fiesta, we can obtain the lowpass prototype transfer function of the desired 6<sup>th</sup> Order Elliptic Filter:

$$H(s) = m \frac{a_0 b_3 s^3 + b_2 s^2 + b_1 s + b_0}{b_0 s^3 + a_2 s^2 + a_1 s + a_0} \quad (3)$$

- Equating the denominators of equations (2) and (3), we obtain the following set of equations from which we can solve for  $k$ ,  $F_2$ , and  $F_3$ .

$$\begin{aligned} 3k &= a_2 \\ 3k^2 + F_2 k^2 &= a_1 \\ (1 + F_2 + F_3) k^3 &= a_0 \end{aligned} \quad (4)$$

- Also from equations (2) and (3)

$$K_0 = m \frac{a_0}{b_0} \quad (5)$$

# Design Procedure

- To obtain the summation coefficients, we equate the numerators of equations (2) and (3). If  $H(s)$  is a bandpass:  $B_0=b_3=0$ . Then, we obtain the following set of equations from which we can determine  $B_1$ ,  $B_2$  and  $B_3$ .

$$B_0 = b_3 = 0$$

$$B_1 k = b_2 \tag{6}$$

$$2B_1 k + B_2 k^2 = b_1$$

$$(B_1 + B_2 + B_3)k^3 = b_0$$

# Designing for Maximum Dynamic Range

- We need to distribute the gains of each section  $T(s)$ , i.e.  $K_1$ ,  $K_2$  and  $K_3$  such that we maximize the Dynamic Range.
- The maximum dynamic range will be obtained if the signal spectra at the output of all sections have equal maxima, i.e.

$$V_{\text{out,max}} = V_{3,\text{max}} = V_{2,\text{max}} = V_{1,\text{max}} = V_{0,\text{max}}$$

# Maximizing Dynamic Range

- To make  $V_{3,\max} = V_{out,\max}$

$$K_0 \rightarrow K'_0 = K_0 q \quad (7)$$

where

$$q = \frac{V_{out,\max} \leftarrow \text{prior to scaling}}{V_{3,\max} \leftarrow \text{prior to scaling}} \quad (8)$$

- We also need to adjust the summation coefficients to keep the overall gain:

$$B_i \rightarrow B'_i = \frac{B_i}{q} \quad (9)$$

If we assume a flat spectrum for the input, i.e.  $V_{in}(\omega) = 1$

$$V_{out,\max} = \text{Max}|H(\omega)| \quad (10)$$

$$V_{3,\max} = \text{Max}|H_3(\omega)|$$

# Maximizing Dynamic Range

Where

$$H_3(s) = \frac{V_3(s)}{V_{in}(s)} = K_0 \frac{k^3}{s^3 + a_2s^2 + a_1s + a_0} \quad (11)$$

- To obtain  $K_1$ ,  $K_2$  and  $K_3$  :

$$K_i = \frac{\text{Max} \left\{ \left| H_3(\omega) \left( \frac{k^2 + \omega^2}{\omega^2} \right)^{\frac{4-i}{2}} \right\}}{\text{Max} \left\{ \left| H_3(\omega) \left( \frac{k^2 + \omega^2}{\omega^2} \right)^{\frac{3-i}{2}} \right\}} \quad \text{for } i = 1, 2, 3. \quad (12)$$

# Design Procedure

- The feedback coefficients need to be readjusted to keep the same loop gains:

$$F_2 \rightarrow F'_2 = \frac{F_2}{K_1 K_2} \quad (13)$$

$$F_3 \rightarrow F'_3 = \frac{F_3}{K_1 K_2 K_3}$$

- The summation coefficients also need to be readjusted again:

$$B_1 \rightarrow B'_1 = B_1 \frac{K_2 K_3}{q}$$

$$B_2 \rightarrow B'_2 = B_2 \frac{K_3}{q} \quad (14)$$

$$B_3 \rightarrow B'_3 = B_3 \frac{1}{q}$$

# Summary of Design Procedure

- Obtain from Matlab or Fiesta the lowpass prototype for the desired filter.
- From equations (4), (5) and (6), obtain  $K_0$ , the feedback and the summation coefficients.
- To maximize dynamic range, obtain  $q$  using equation (8). Recalculate  $K_0$  using equation (7).
- Calculate the gain of each section, i.e.  $K_1$ ,  $K_2$  and  $K_3$  using equation (12).
- Recalculate the feedback and summation coefficients using equations (13) and (14).
- Finally, apply a lowpass-to-bandpass transformation to obtain the desired bandpass filter specifications:

$$\omega_0 = 2\pi\sqrt{f_L f_U}$$

$$Q_0 = \frac{Q}{k}$$

where  $Q$  is the quality factor of the overall filter and  $Q_0$  is that required for each biquad section.

- Note: A Matlab program was written to automate the design procedure for an arbitrary filter specification of order  $N$ .

# Summary of Results


- For the required specifications, the following values were obtained:

Feedback Coefficients	F2 = 0.657640 F3 = 0.227545
Feedforward Coefficients	B0 = 0 B1 = 0.169792 B2 = -0.216571 B3 = 1.129814
Gain for the input and each biquad stage	K0 = 0.604488 K1 = 2.349 K2 = 2.165 K3 = 2
Center frequency and $Q_0$ of each biquad stage	$f_0 = 1.9975\text{MHz}$ $Q_0 = 15.7$



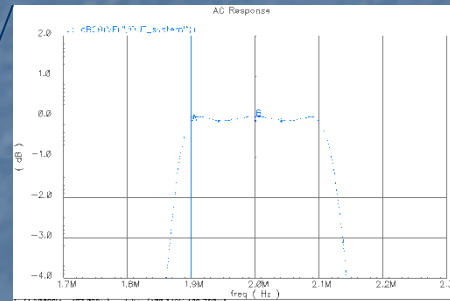
# Simulation Results System Level


- The complete filter was simulated in Cadence at a system-level. The results are shown below:



Ripple  $\leq 0.1$ dB

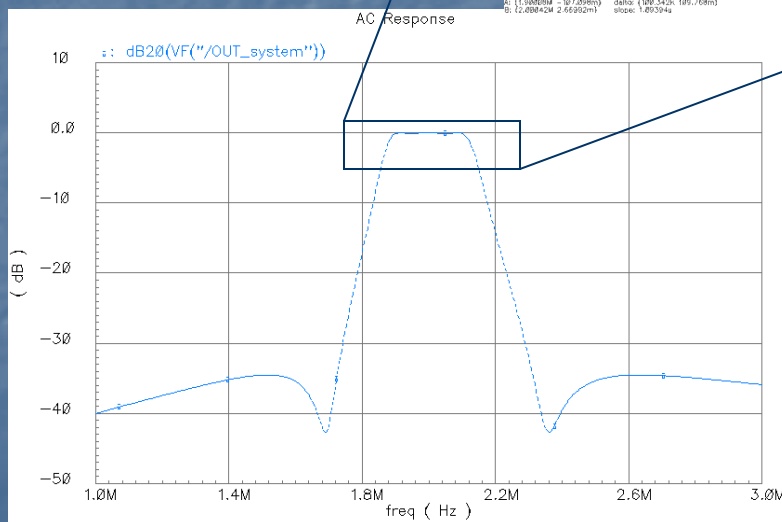

Magnitude Response

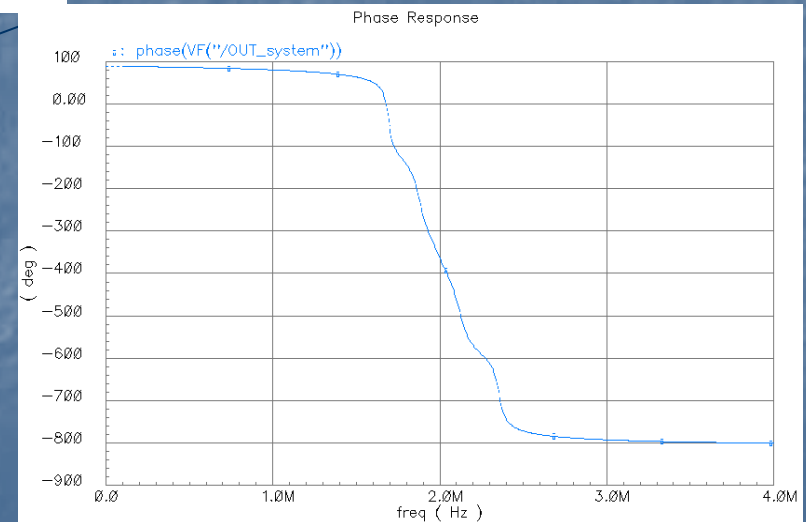


Phase Response

# Transistor Level Implementation

- To implement each biquadratic section, a two-integrator loop biquad OTA-C filter was used.
- Advantages with respect to Active-RC:
  - Easy Tunability by changing the bias currents of the OTAs. (Active-RC needs the use of varactors).
  - Lower Power Consumption and Smaller Area.
- Disadvantages with respect to Active-RC:
  - Smaller Dynamic Range
  - Poorer Linearity
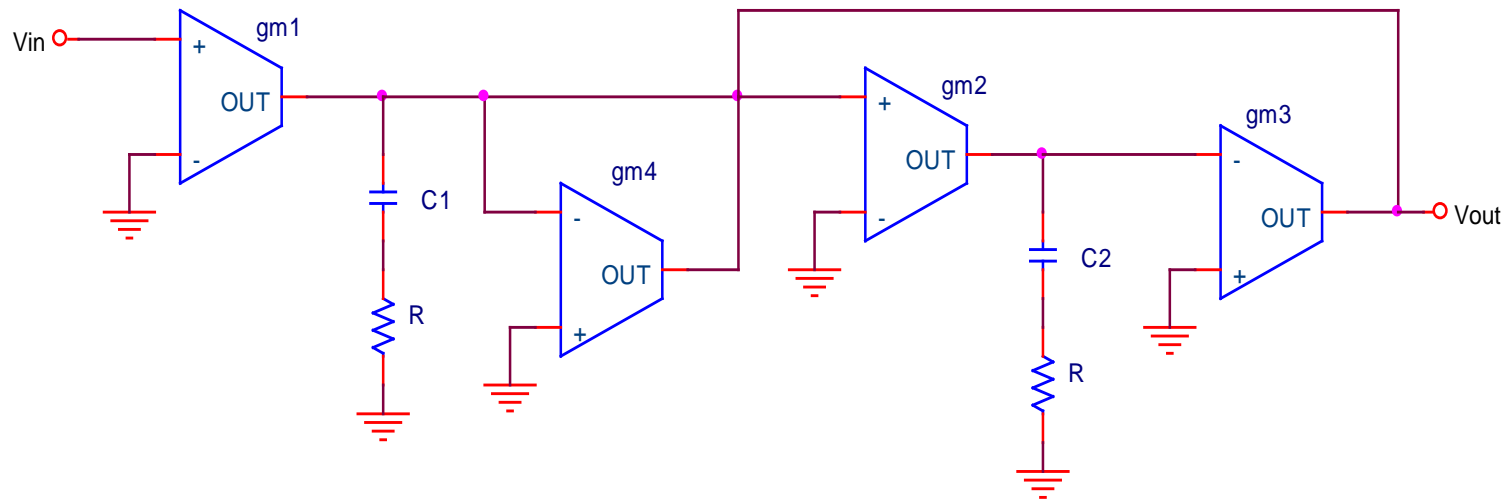
# Transistor Level Implementation of each Biquad Section



$$H(s) = \frac{s \frac{g_{m1}}{C_1}}{s^2 + s \frac{g_{m4}}{C_1} + \frac{g_{m2} g_{m3}}{C_2 C_1}}$$

# Design of Lossless Integrator

- The lossless integrator was designed to have unity gain at  $f_0=1.9975\text{MHz}$ .

$$|H(\omega)| = \frac{g_{m2}}{\omega C_2} = 1$$

$$g_{m3} = 376.52 \mu\text{A/V}$$

$$C_2 = 30 \text{ pF}$$


- The following specifications are needed if a 5% variation in  $Q$  is allowed:

$$\text{Excess Phase: } \phi_E \leq \frac{1}{2Q} \left( 1 - \frac{Q}{Q_a} \right) = 1.5 \times 10^{-3} \text{ rad} = 0.086^\circ$$

$$\text{DC Gain: } A_V \geq \frac{2Q}{\frac{Q}{Q_a} - 1} = 602 = 55.58 \text{ dB}$$
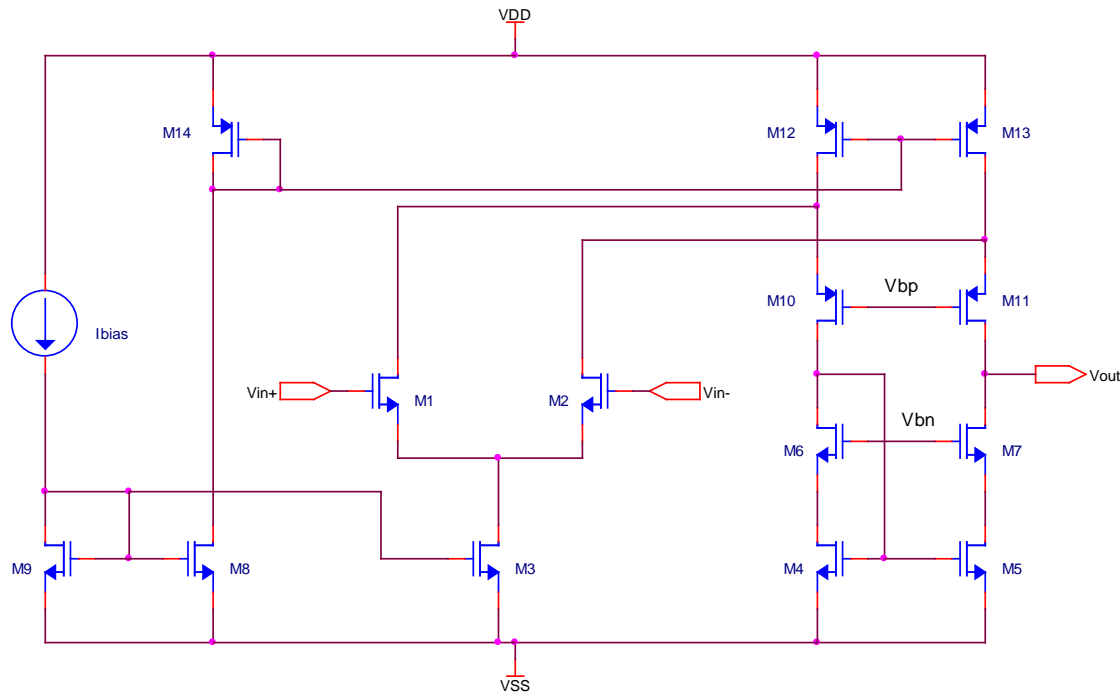
# Design of Lossless Integrator


- Due to the relatively high DC gain required for the OTA, a folded-cascode topology was used:




Transconductance	DC Gain	GBW	Bias Current	Power Consumption	Active Area
$376.52\mu\text{A/V}$	64.1dB	263MHz	$40\mu\text{A}$	$792\mu\text{W}$	$727\mu\text{m}^2$
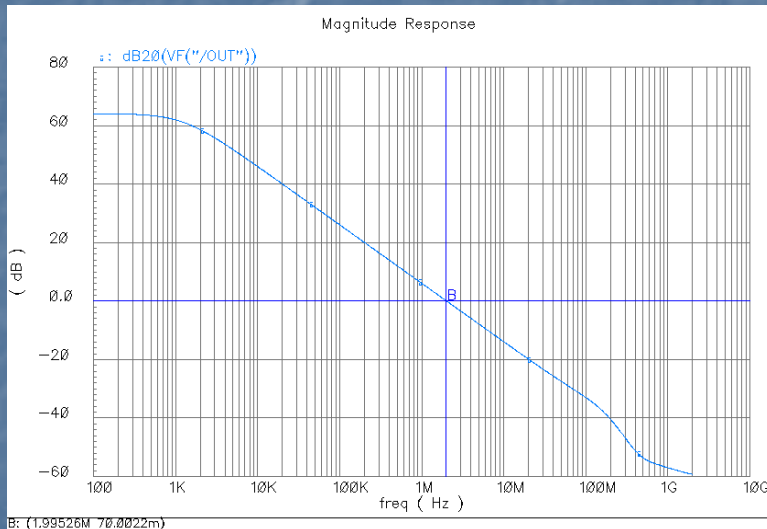
# Simulation Results of the Lossless Integrator

- The excess phase without any compensation was  $1.17^\circ$ .
- Passive excess phase compensation was used  $\rightarrow R=55\Omega$ .



Magnitude Response

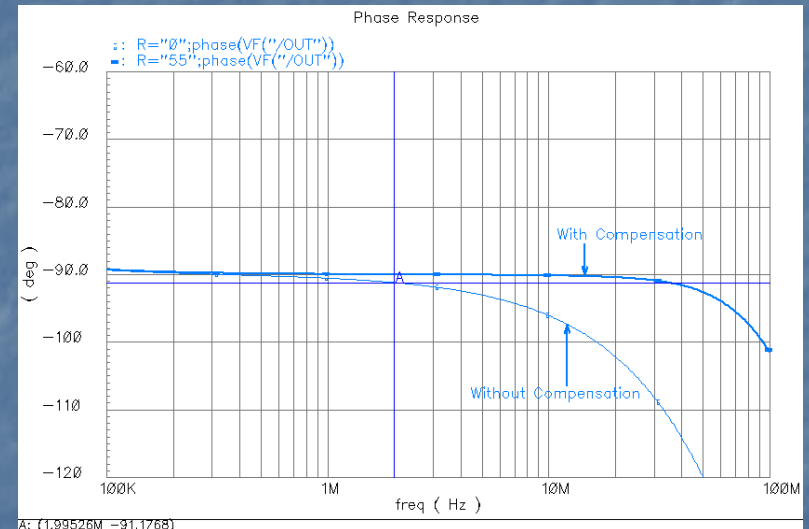

Phase Response

# Design of Biquadratic Bandpass Filter

- To reuse the designed OTA:

$$g_{m3} = g_{m2} = 376.52 \mu\text{A}/\text{V}$$

$$C_1 = C_2 = 30 \text{ pF}$$

$$g_{m4} = \frac{C_1}{Q_0} \omega_0 = 23.827 \mu\text{A}/\text{V}$$

- Transconductance  $g_{m1}$  depends on  $K_i$


$$g_{m1} = K_i g_{m4}$$

- For demonstrations purposes,  $g_{m1} = g_{m4}$ , i.e.  $K=1$





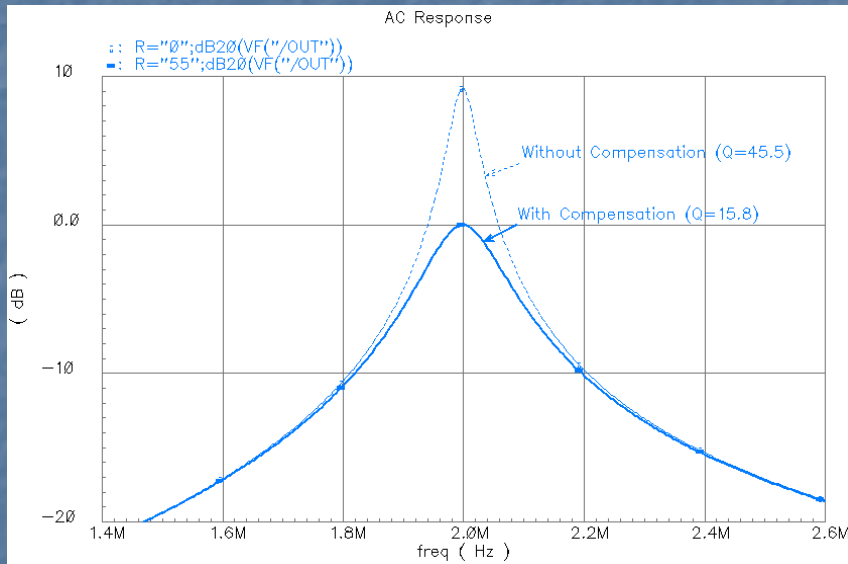
# Simulation Results of the Biquadratic Bandpass Filter




Frequency Response

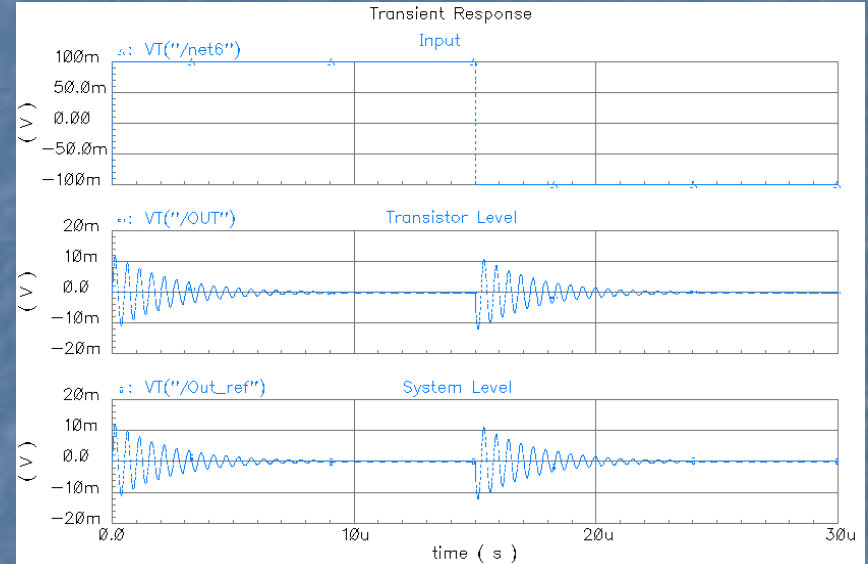

Step Response

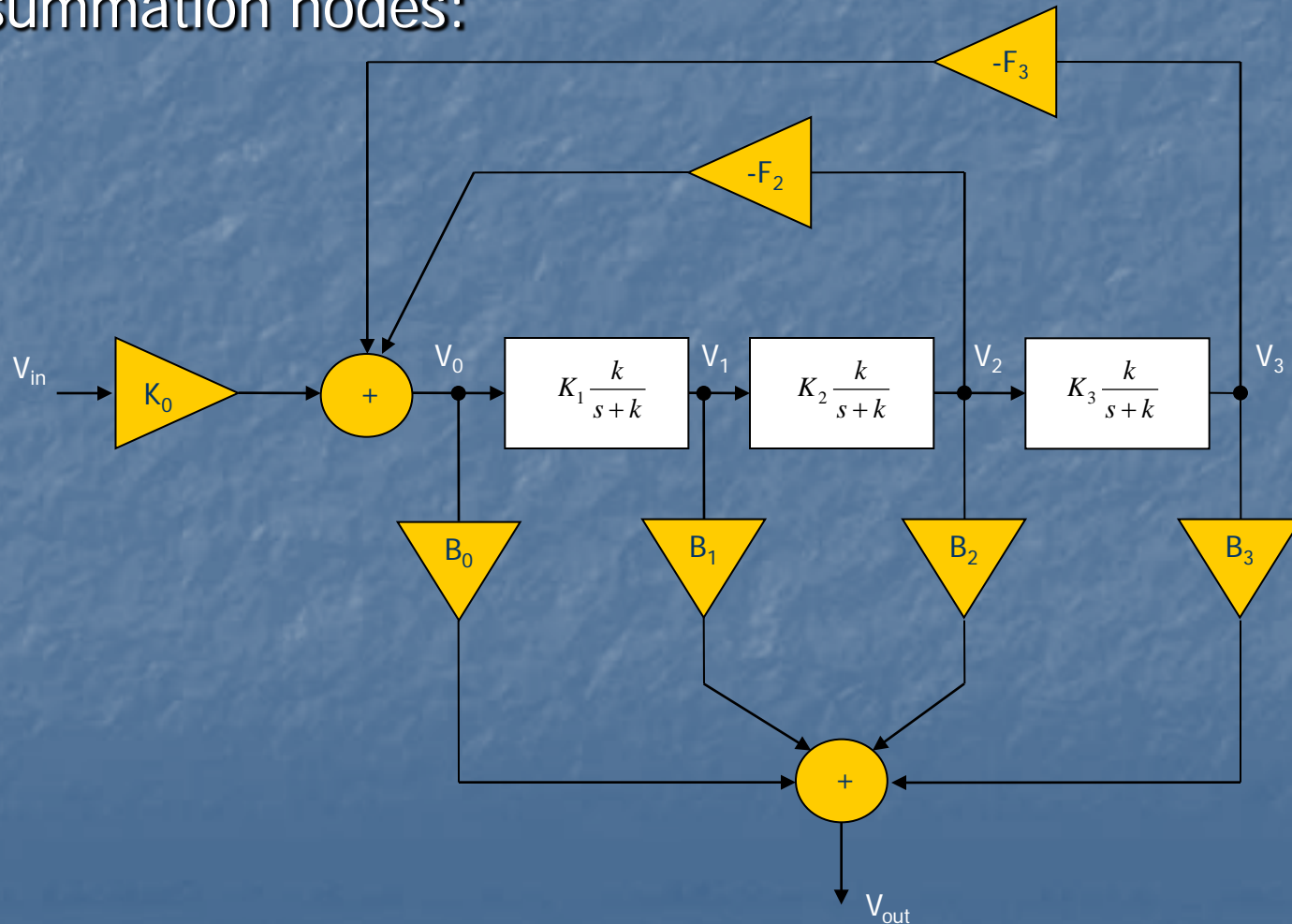
# Summation Nodes

- To complete the transistor-level design, we need two summation nodes:



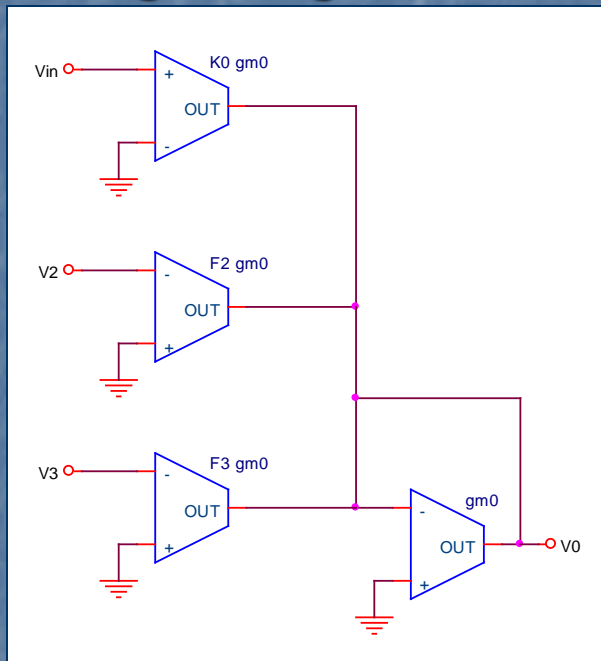
# Summation Nodes

- The summation nodes can be implemented with OTAs in the following configurations:



Summation Node for the Feedback Paths

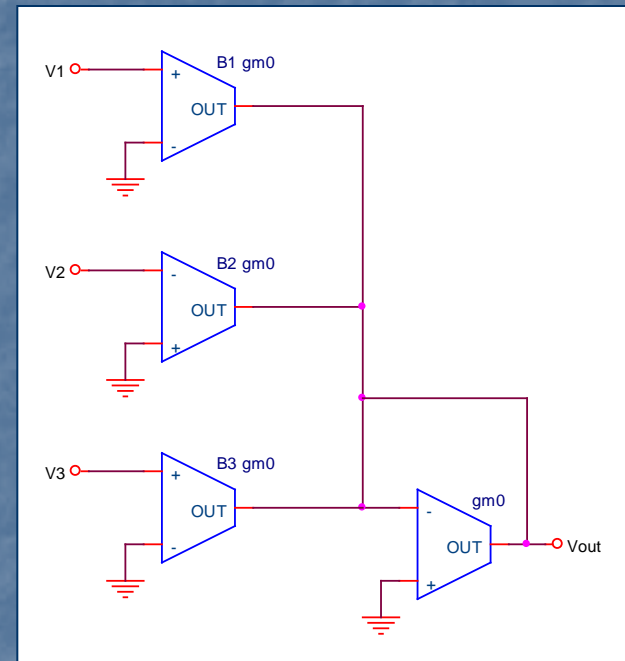


Summation Node at the Output

- If  $g_{m0}$  is chosen large enough, the output resistance of each OTA does not need to be very high. Excess Phase of OTAs can be a concern.

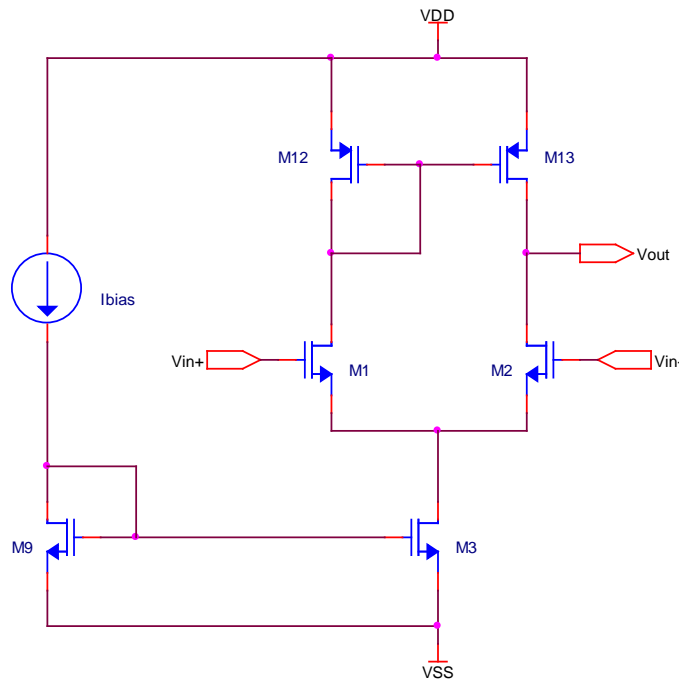
# Summation Nodes

- Due to the desired low excess phase introduced by the OTAs, it is more convenient to use a simple differential pair.




Transconductance	Bias Current	Power Consumption	Active Area
$300\mu\text{A/V}$	$40\mu\text{A}$	$264\mu\text{W}$	$269\mu\text{m}^2$

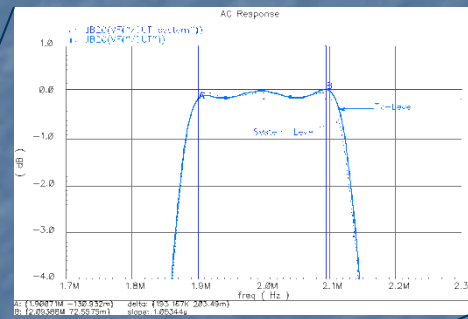
# Simulation Results of the Complete FLF Filter (Transistor vs. System Level)



Ripple  $\sim 0.2\text{dB}$

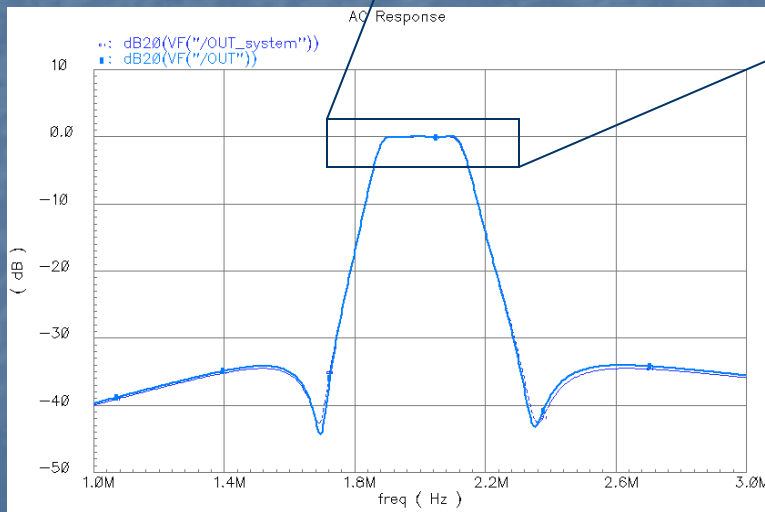


Magnitude Response

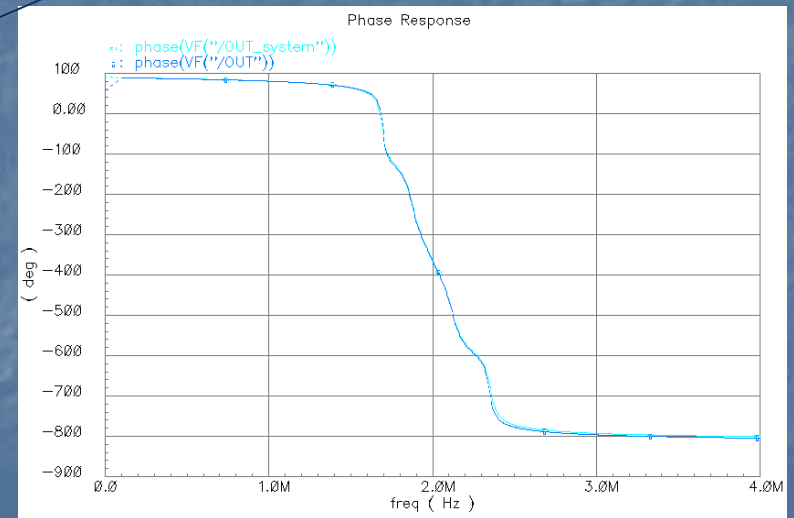


Phase Response
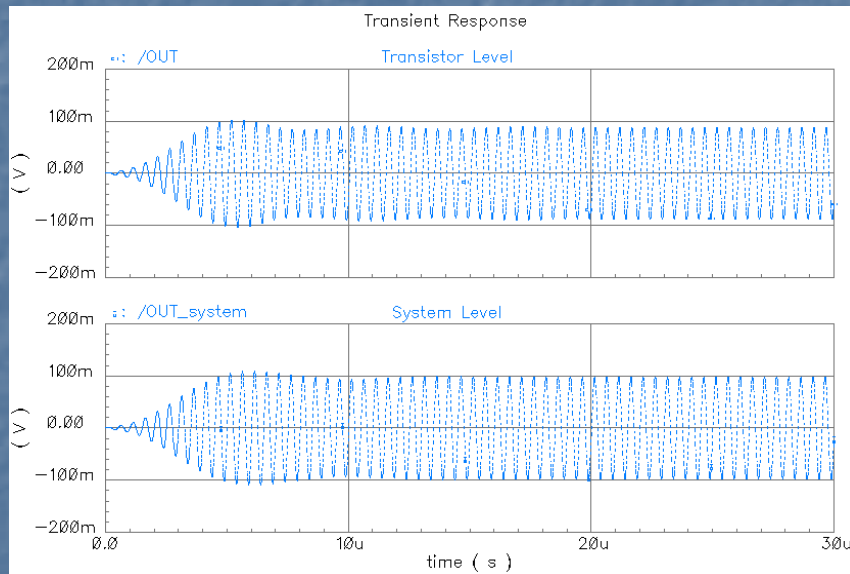
# Simulation Results of the Complete FLF Filter (Transistor vs. System Level)



Transient Response to a Sinewave

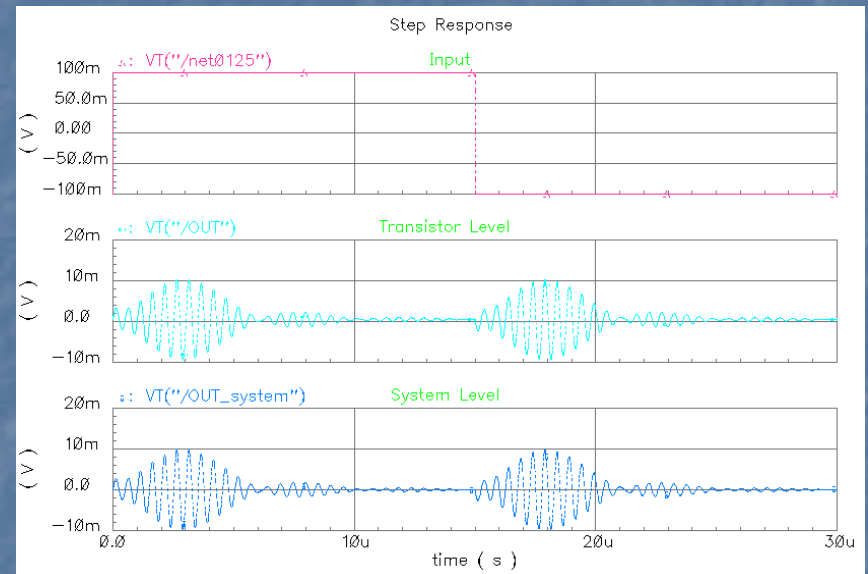

Step Response

# Summary of Results

Specification	Value
Passband	1.9MHz to 2.1MHz
Passband Ripple	~0.2dB
Attenuation	≥40dB at 0.6MHz
Power Consumption	8.53mW
Active Area	11,434 $\mu\text{m}^2$
Total Area	~ 211,549 $\mu\text{m}^2$

# Problems to be solved

- **Voltage Swing:** The allowable input voltage swing is only 100mV. A small voltage swing is expected, since the OTAs have a small linear range limited by  $\pm V_{DSAT}$  of the input transistors (in case no linearization technique is used, such as source degeneration or others). Nevertheless, 100mV is too small and is basically because the OTAs with  $g_m = 376.52 \mu\text{A/V}$  use input transistors with a small  $V_{DSAT}$  and no linearization technique is being used. I need to redesign these OTAs to increase the linear range.
- **Bias Network:** To design the bias network for the folded-cascode OTAs capable of effectively tracking changes of  $V_T$  due to process variations.
- **Sensitivity and Tunability:** To characterize the complete filter in terms of sensitivity and tunability.
- **Layout**



# References

- [1] Sedra, Brackett. Filter Theory and Design: Active and Passive. Matrix Series in Circuits and Systems. pp. 589-659.
- [2] Deliyannis, Sun, Fidler. Continuous-Time Active Filter Design. CRC Press 1999. pp. 151-180.
- [3] G. Hurtig, III. The Primary Resonator Block Technique of Filter Synthesis Proc. Int. Filter Symposium, p.84, 1972.
- [4] Barbargires. Explicit Design of General High-Order FLF OTA-C Filters. Electronics Letters. 5th August 1999, Vol. 35, No. 16, pp. 1289-1290.
- [5] Jie Wu, Ezz I. El-Masry. Synthesis of Follow-the-Leader Feedback Log-Domain Filters. IEEE 1998. 0-7803-5008-1/98. pp. 381-384.