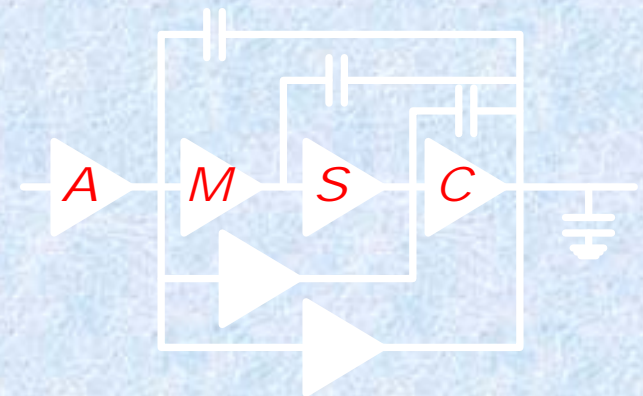




An RF Tunable LC Bandpass Filter with small Passband Ripple and transformer emulator

Department of Electrical Engineering
Analog and Mixed-Signal Center
Texas A&M University
<http://amsc.tamu.edu/>

Material Courtesy of Ahmed Mohieldin




ECEN 665 (ESS) Analog & Mixed
Signal Center, Texas A&M
University

Outline

- ❑ Introduction
- ❑ High-Order filters
- ❑ Dual resonator bandpass filter
- ❑ Design Considerations
- ❑ Measurement Results
- ❑ Conclusions

Introduction

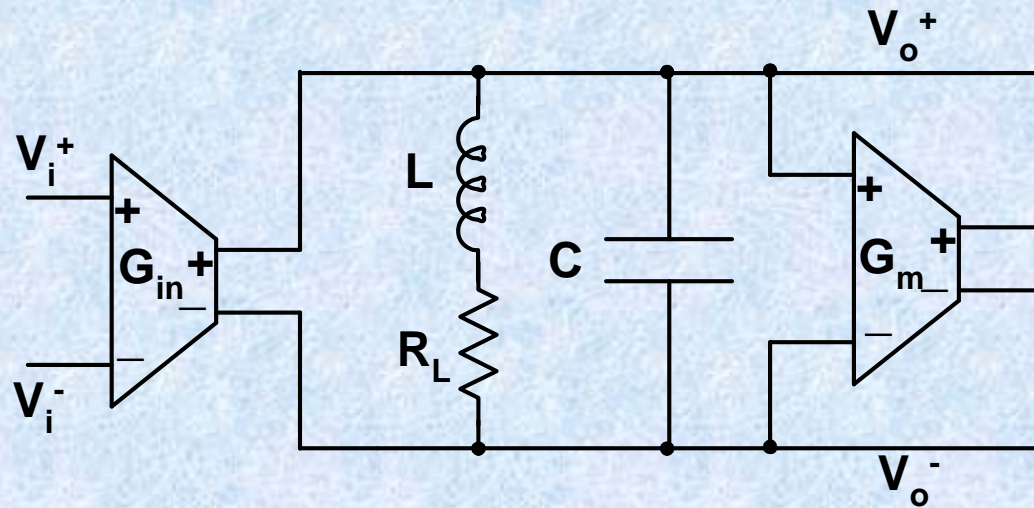

$$\omega_0 \cong \frac{1}{\sqrt{LC}} \sqrt{1 - \frac{1}{Q_0^2}}$$

$$Q \cong \frac{Q_0}{1 - (G_m / G_{loss})} \sqrt{1 - \frac{1}{Q_0^2}}$$


$$G_{loss} \cong R_L (\omega_0 C)^2$$

- ☺ Replace off-chip filters
- ☺ Eliminate need of impedance matching
- ☺ Reduce power, area, and cost
- ☹ Integrated spiral inductors are lossy
- ☹ Positive feedback is needed for Q-enhancement

High-Order Filters

- ❑ Needed to provide acceptable IR
- ❑ Classic LC filter synthesis techniques can be used with Q-enhancement
- ❑ No guarantee that the filter frequency response will be preserved
- ❑ To avoid large element value spread, especially for narrow band, coupled filters are used
- ❑ Consists of reactive tank circuits coupled by capacitors, inductors, or magnetically

Dual Resonator Bandpass Filter

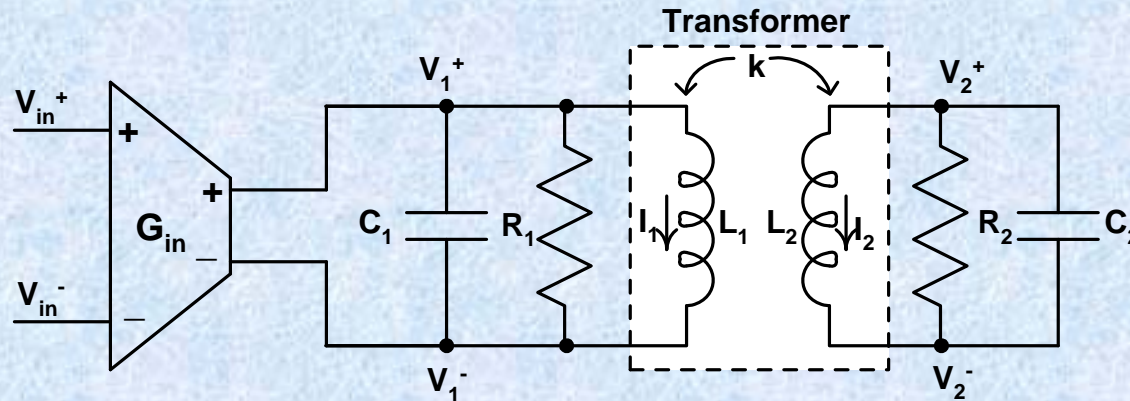

$$R = R_1 = R_2 = K_2 Q \sqrt{L/C}$$

- ❑ Two magnetically coupled resonators
- ❑ 4th order filter
- ❑ ω_0 is fixed by the LC product
- ❑ Coupling coefficient k is used to tune Q



$$LC = (1/\omega_0^2)$$

$$k = K_1 / Q$$

ECEN 665 (ESS) Analog & Mixed
Signal Center, Texas A&M

University

Effect of tuning k

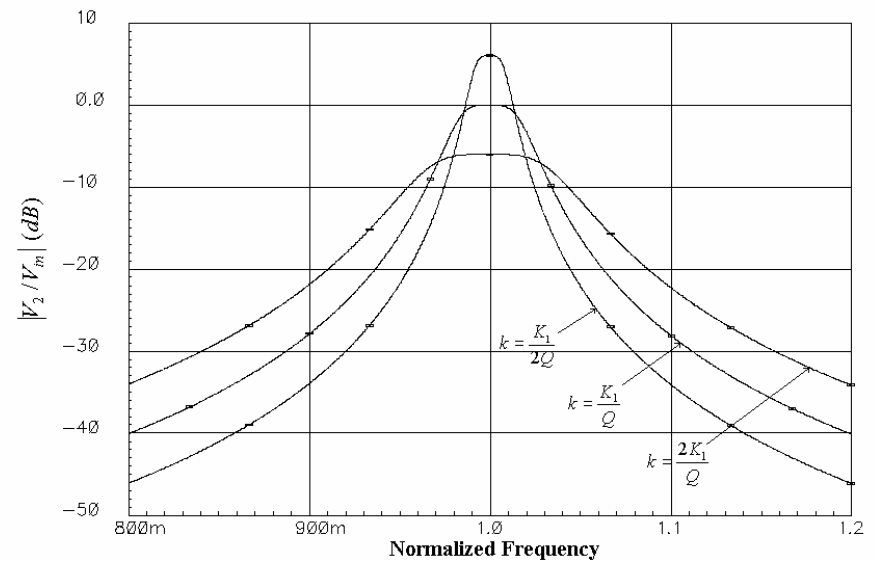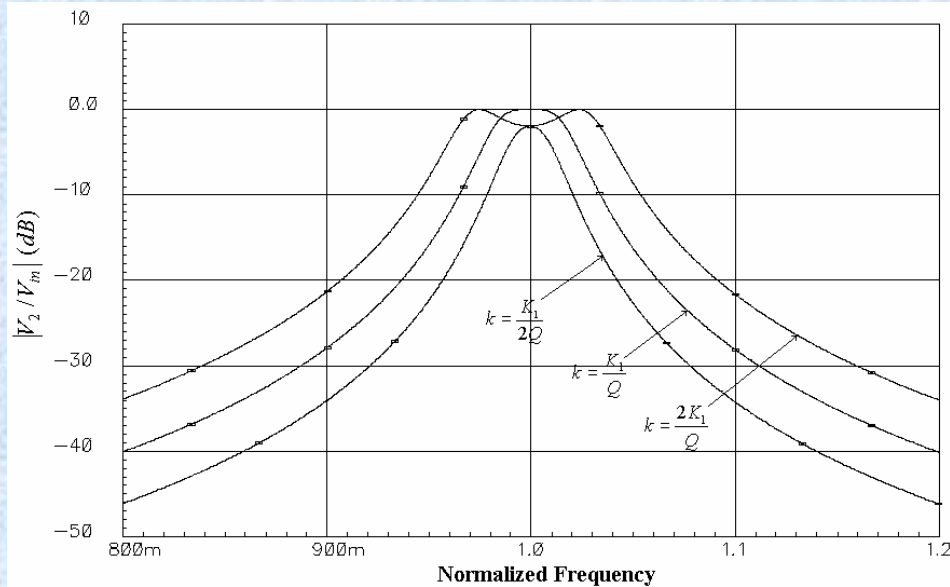


$$K = \{K_1/2Q, K_1/Q, 2K_1/Q\}$$

- ❑ Minimum passband ripple at critical coupling
- ❑ Tuning k and R simultaneously to keep $k \times R$ constant


ECEN 665 (ESS) Analog & Mixed
Signal Center, Texas A&M
University

Transformer Models

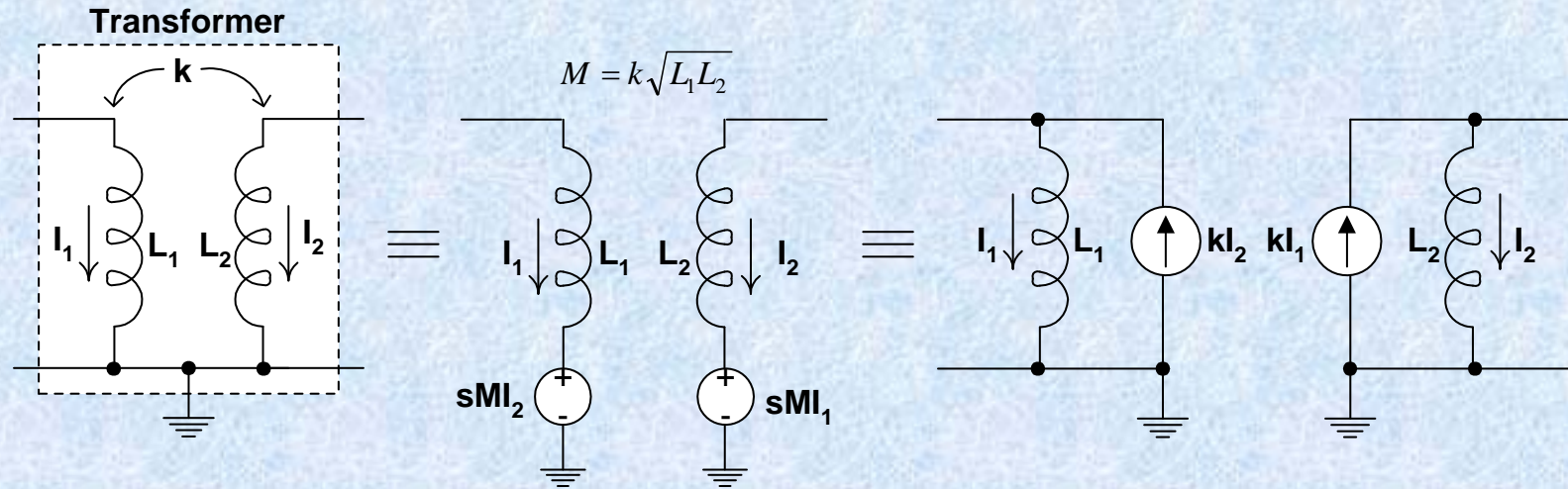


- ❑ Transformer can be replaced by induced currents
- ❑ Due to losses, induced currents are not in phase
- ❑ Severe passband ripples
- ❑ Coupling neutralization to maintain a flatband response
- ❑ Emulate the transformer action by electric coupling

Emulation of Magnetic Coupling

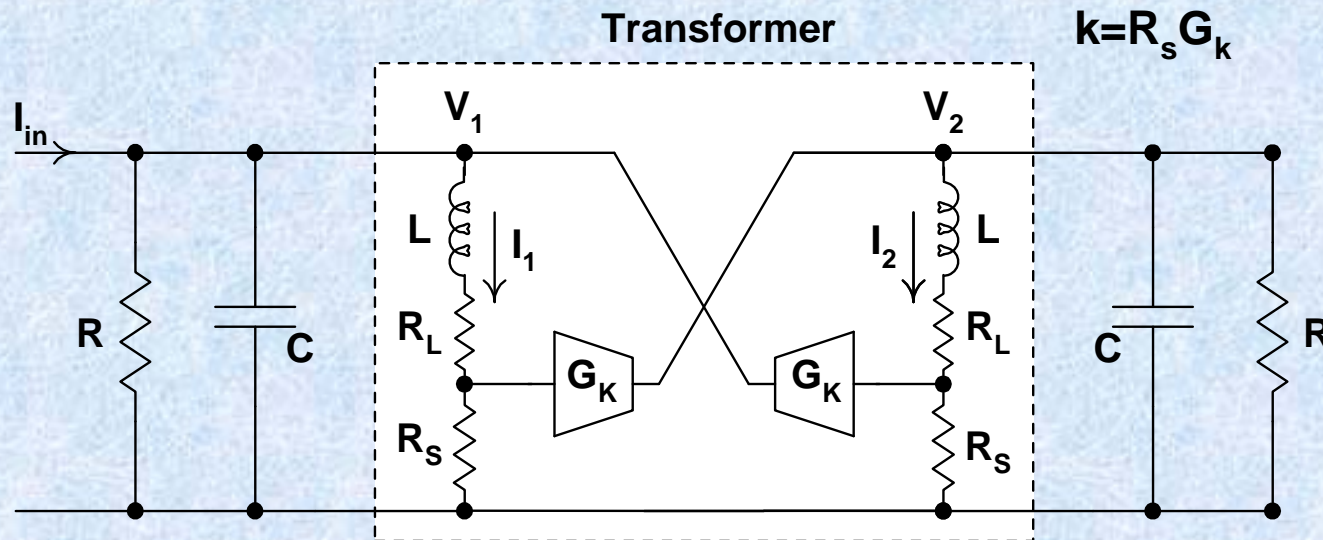

- ❑ $k = G_k R_s (\cong 0.01)$
- ❑ Provide possibility of BW tuning while maintain flatband
- ❑ Placing inductors apart to diminish magnetic coupling

Circuit Implementation

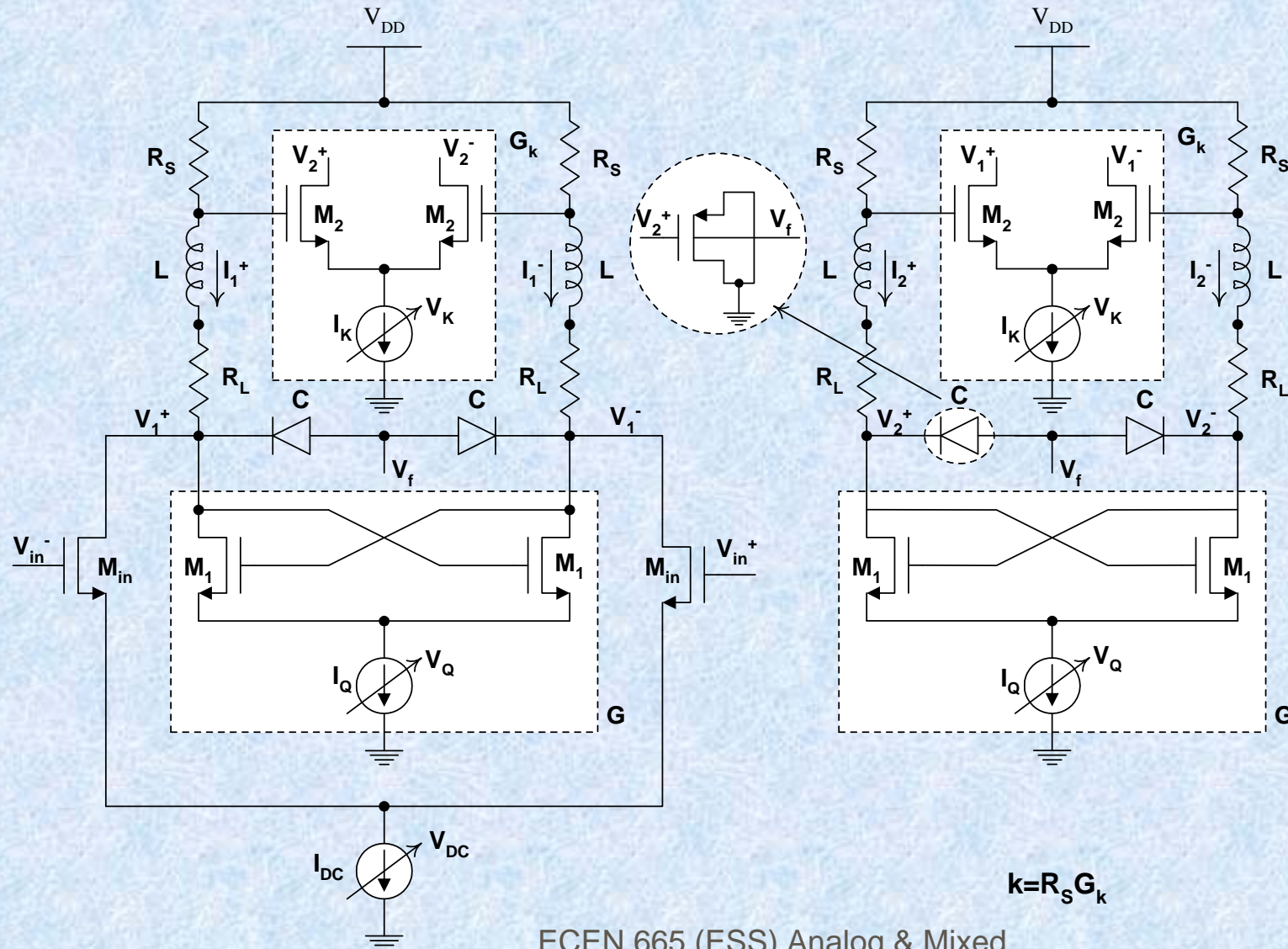

ECEN 665 (ESS) Analog & Mixed
Signal Center, Texas A&M
University

Design Considerations

□ Noise Analysis

$$v_{noise}^2 = \frac{1}{A_v^2} \left(\frac{KT}{C} \right) \left[\frac{Q}{Q_0} + \zeta \frac{Q}{Q_0} + \zeta A_v \right] = \frac{1}{A_v^2} \left(\frac{KT}{C} \right) \left(\frac{Q}{Q_0} \right) \left[1 + \zeta + \zeta \frac{G_{in}}{G_{loss}} \right]$$

ζ is a noise factor that depends on the implementation

- For low peak gain $A_v < (Q/Q_0)$, contribution of the input transconductance can be neglected

Design Considerations

Nonlinearity Analysis

- To isolate nonlinear effects, each nonlinear element is considered separately

$$V_{1-dB,in}^2 = V_{1-dB}|_{G_{in}}^2 \quad V_{1-dB}|_{G_{in}} = 1.077 \times (V_{GS} - V_T) = 1.077 \times \sqrt{\frac{2I_{SS}}{K_n(W/L)_{in}}}$$

$$V_{1-dB,Gm}^2 = \frac{V_{1-dB}|_{Gm}^2}{A_v^2} \cdot \frac{Q_0}{Q}$$


A differential pair based OTA

- For high Q narrowband or high gain applications, the negative OTA dominates linearity performance

Design Considerations

Nonlinearity Analysis

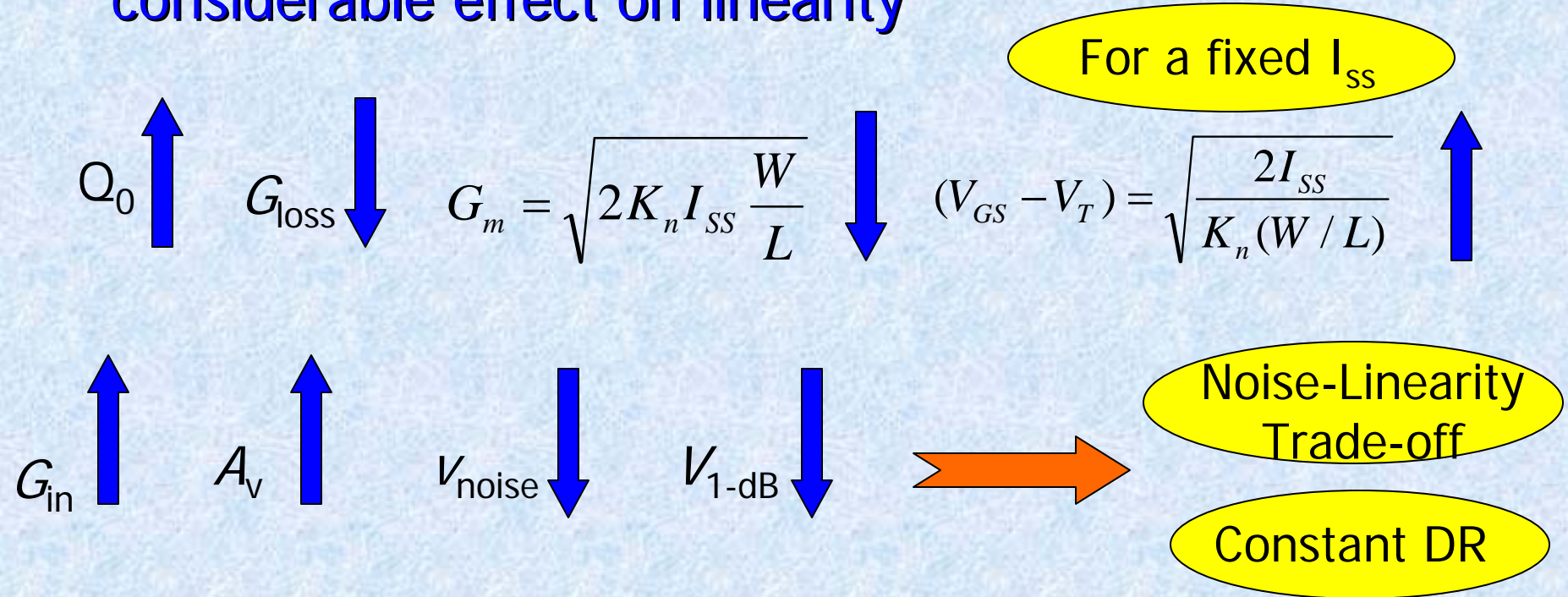- Starting inductor's quality factor Q_0 has a considerable effect on linearity



Design Considerations

Dynamic range

Factor of Q_0^2 improvement over OTA-C counterpart

$$DR = \frac{V_{1-dB}^2}{v_{noise}^2} = \frac{V_{1-dB}^2|_{G_m}}{KT \left(1 + \zeta + \zeta \frac{G_{in}}{G_{loss}} \right)} C \left(\frac{Q_0}{Q} \right)^2$$

Selectivity-DR trade-off

$$CQ_0^2 = L/R_L^2$$

$$DR$$

L and R_L scale proportionally

- DR is maximized by minimizing the losses of the inductor
- Technology issue TSMC 0.13 μ m $Q > 10$ @5GHz

ECEN 665 (LESS) Analog & Mixed
Signal Center, Texas A&M

Design Considerations

Power Consumption

L ↓ R_L ↓ DR ↑

$$G_m = G_{\text{loss}} = R_L / (\omega_0 L)^2$$

L ↓ R_L ↓ $Power$ ↑


L ↑ $Tuning\ range$ ↓

DR-Power Trade-off

How to maximize DR?
Choose minimum L to meet the power budget

Tuning-Power Trade-off

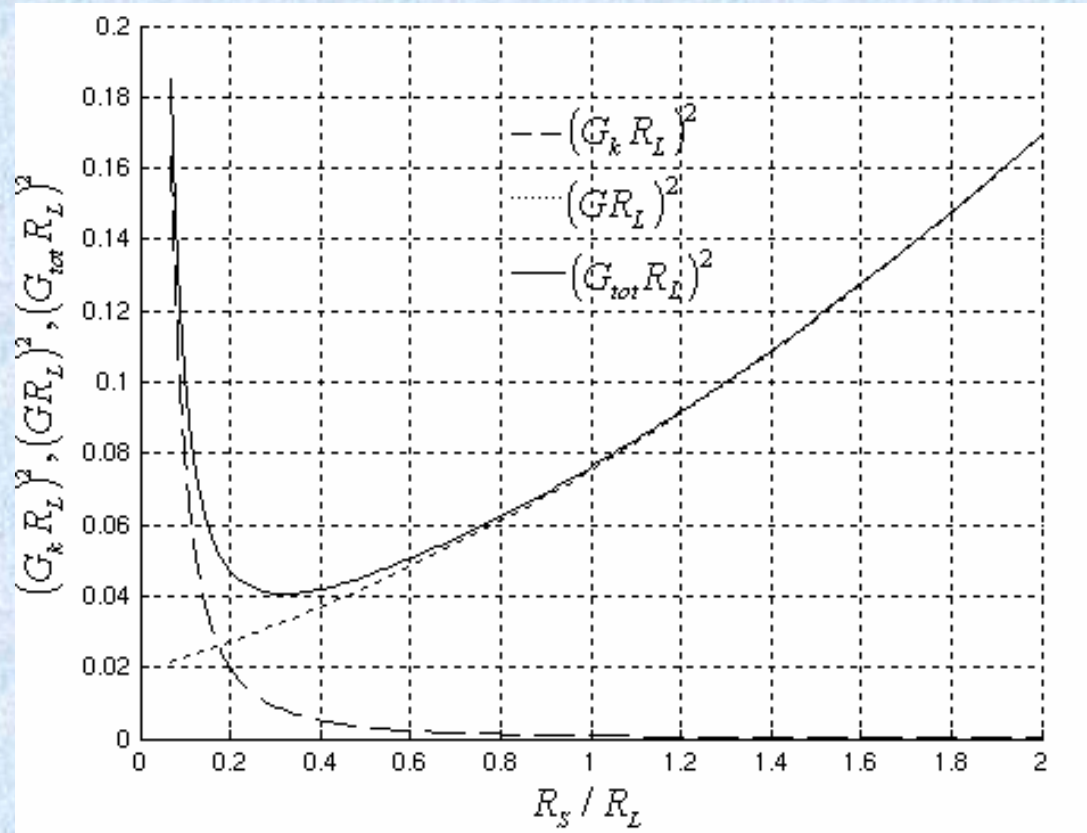Effect of R_S on filter power consumption



R_S ↑

G ↑

For a fixed R_L


R_S ↓

G_k ↑

For a fixed k

ECEN 665 (ESS) Analog & Mixed
Signal Center, Texas A&M
University

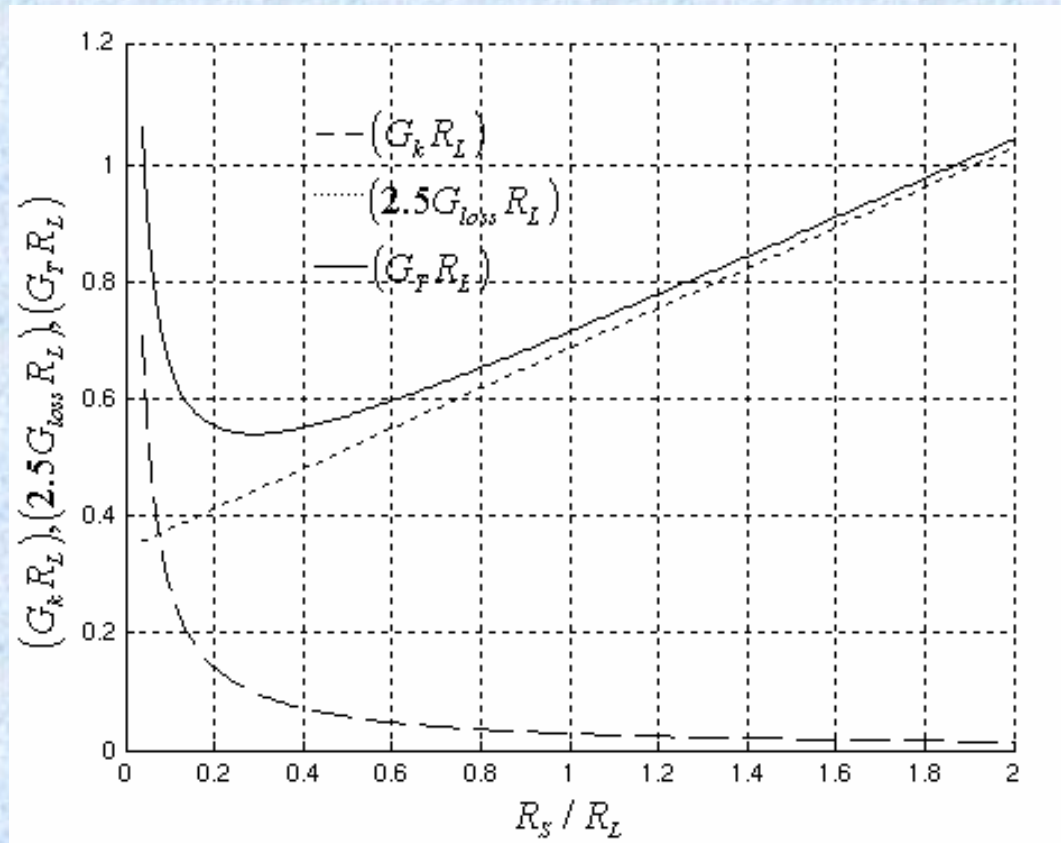Effect of R_S on filter noise performance



$R_S \uparrow$ $G_{loss} \uparrow$


For a fixed R_L

$R_S \downarrow$ $G_k \uparrow$

For a fixed k

ECEN 665 (ESS) Analog & Mixed
Signal Center, Texas A&M
University

Power and Noise optimization

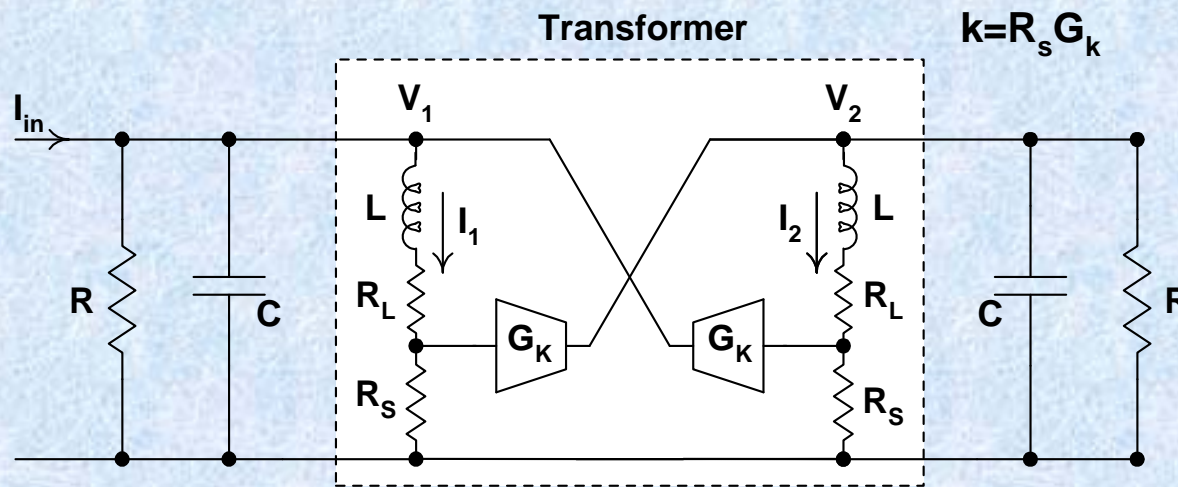

$$Q_0 = 3, Q = 100$$


$$R_S \cong R_L \left(\frac{Q_0^2}{2.5\sqrt{2}Q} \right)^{1/2}$$



Optimize Noise

NF + 1.76dB

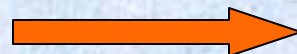
$$R_S \cong R_L \left(\frac{Q_0^4}{2Q^2} \right)^{1/3}$$



Optimize Power

P*1.15


Filter Tuning

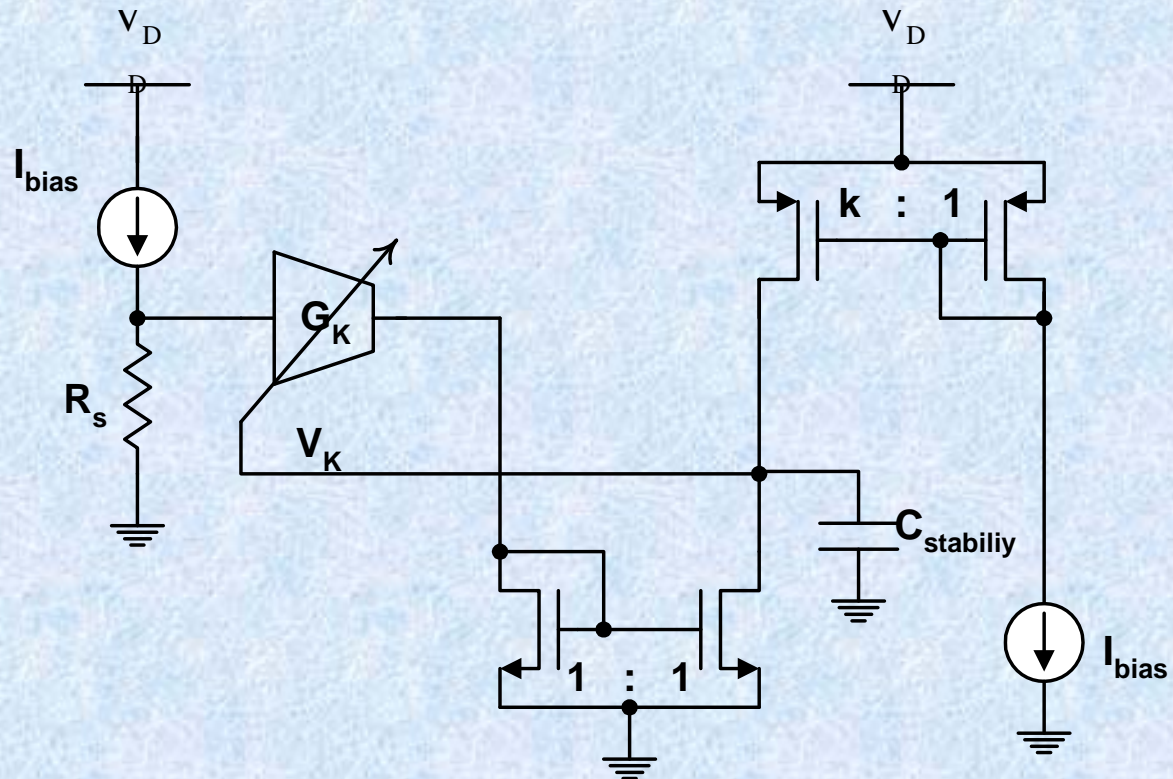

Tuning the coupling coefficient

ECEN 665 (ESS) Analog & Mixed
Signal Center, Texas A&M
University

Filter Tuning

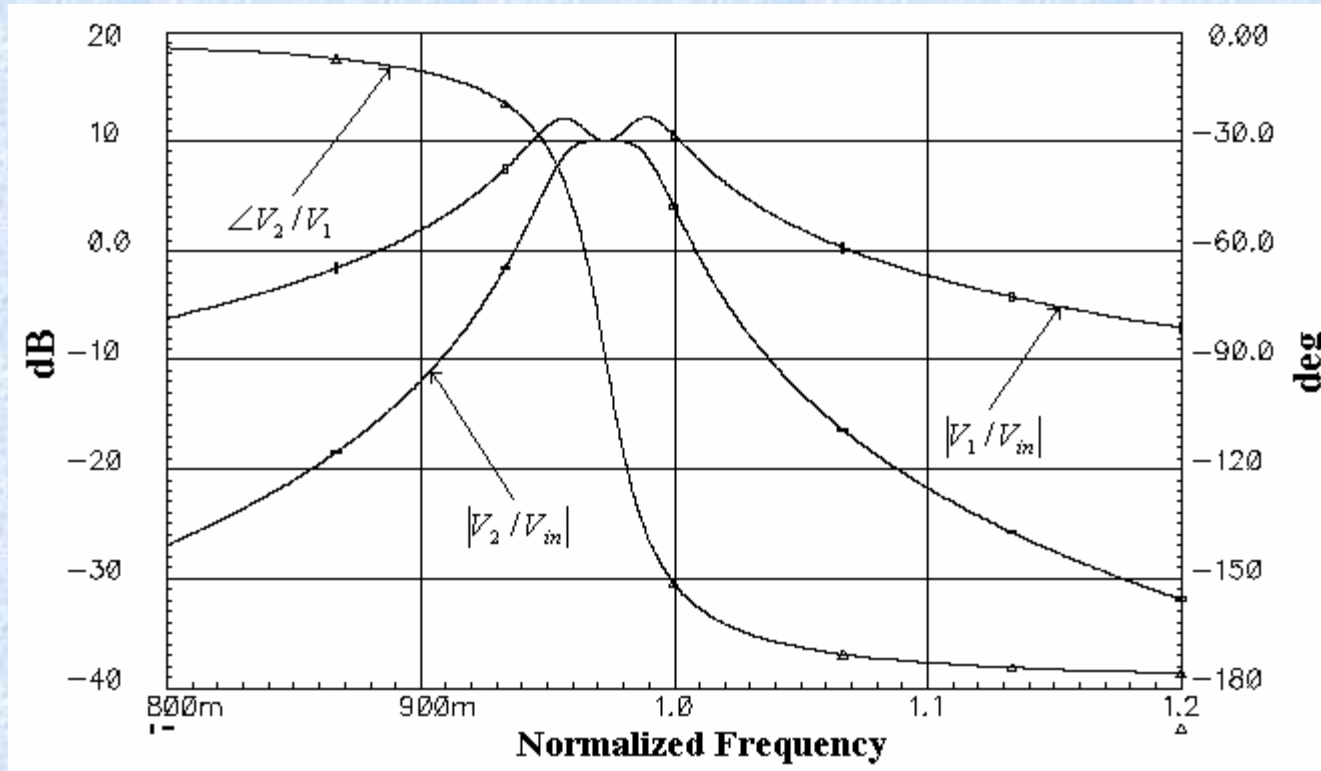


$$\frac{V_2}{V_1}(j\omega_0) = j \frac{1}{\sqrt{1 - (1/Q_0^2)}} \cong j$$

Frequency and Q tuning

ECEN 665 (ESS) Analog & Mixed
Signal Center, Texas A&M
University



Chip Micrograph

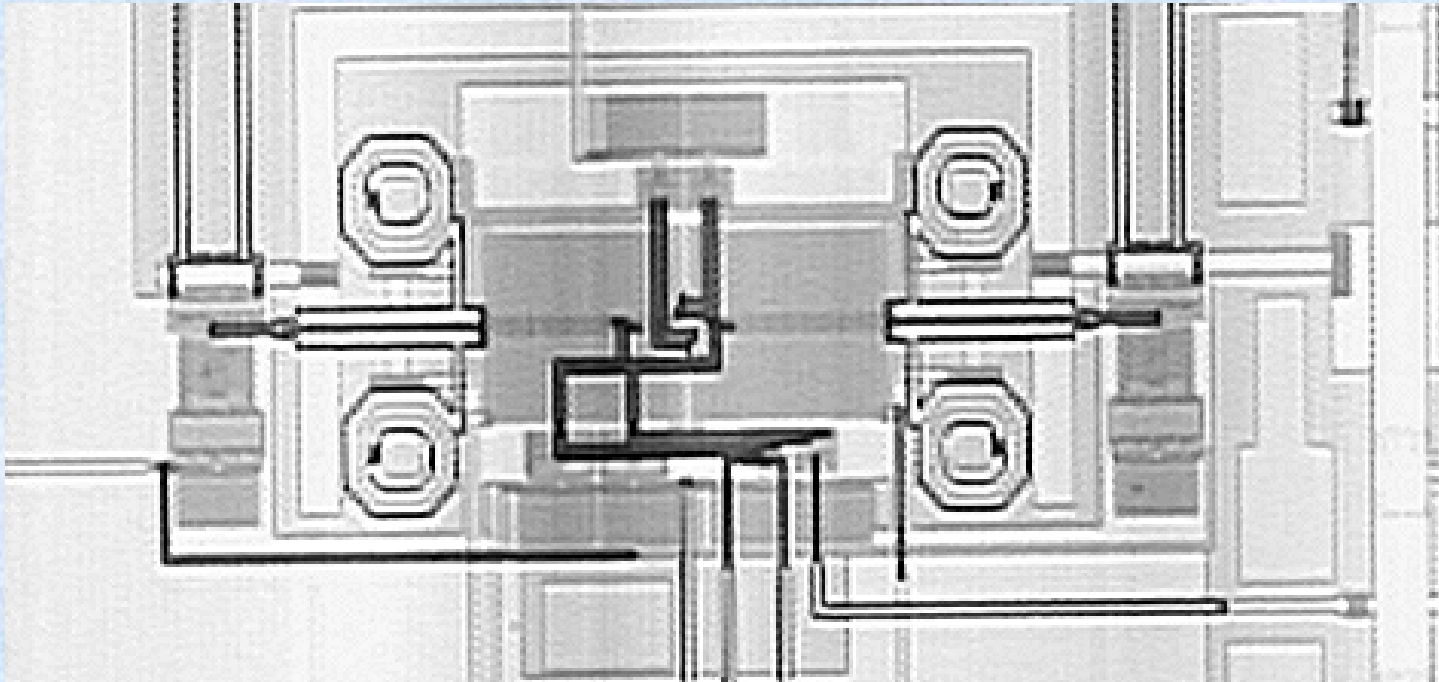

$X=500\mu\text{m}$, $Y=300\mu\text{m}$

ECEN 665 (ESS) Analog & Mixed
Signal Center, Texas A&M
University

Measurement Results

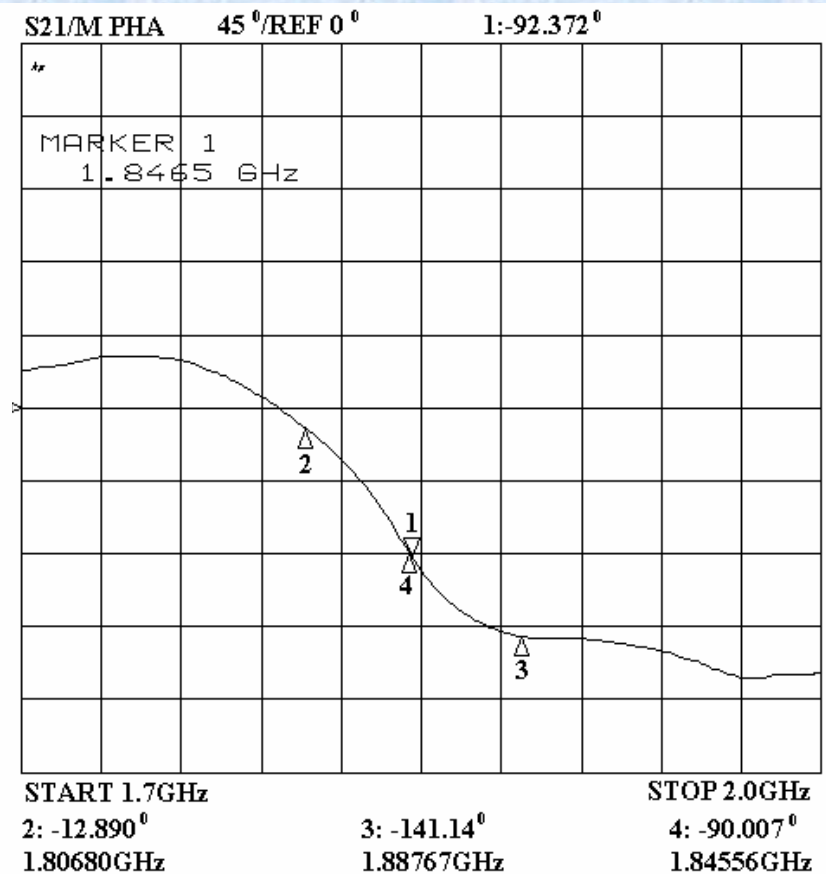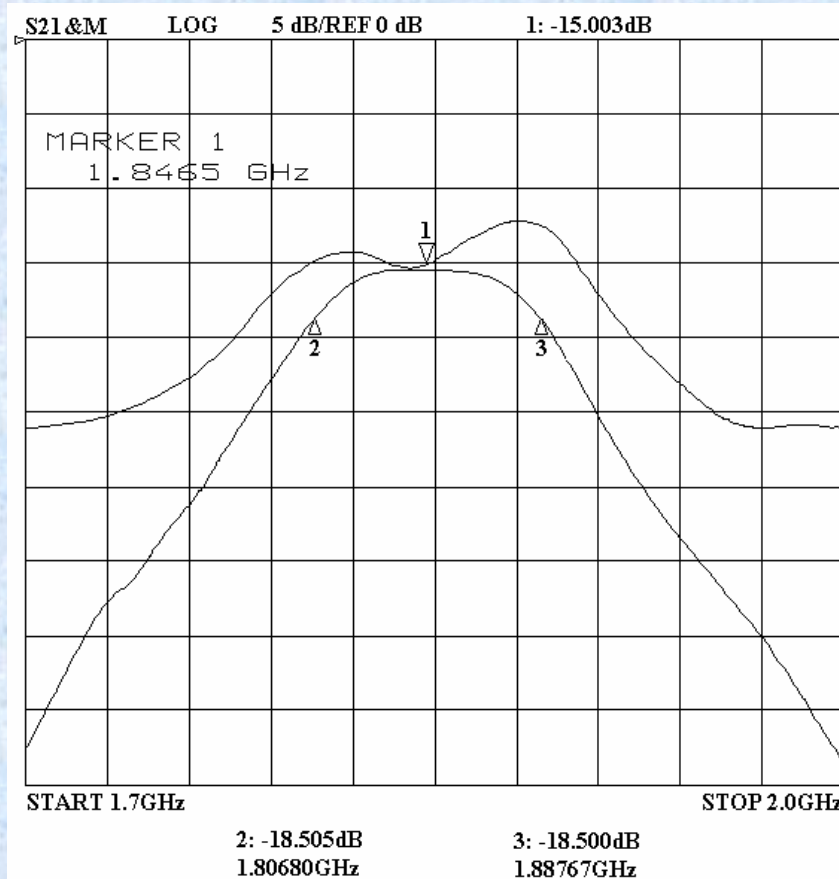


Upper trace $|V_1/V_{in}|$ (dB)

Lower trace $|V_2/V_{in}|$ (dB)

Phase Response


EN 665 (ESS) Analog & Mixed
Signal Center, Texas A&M

Measurement Results

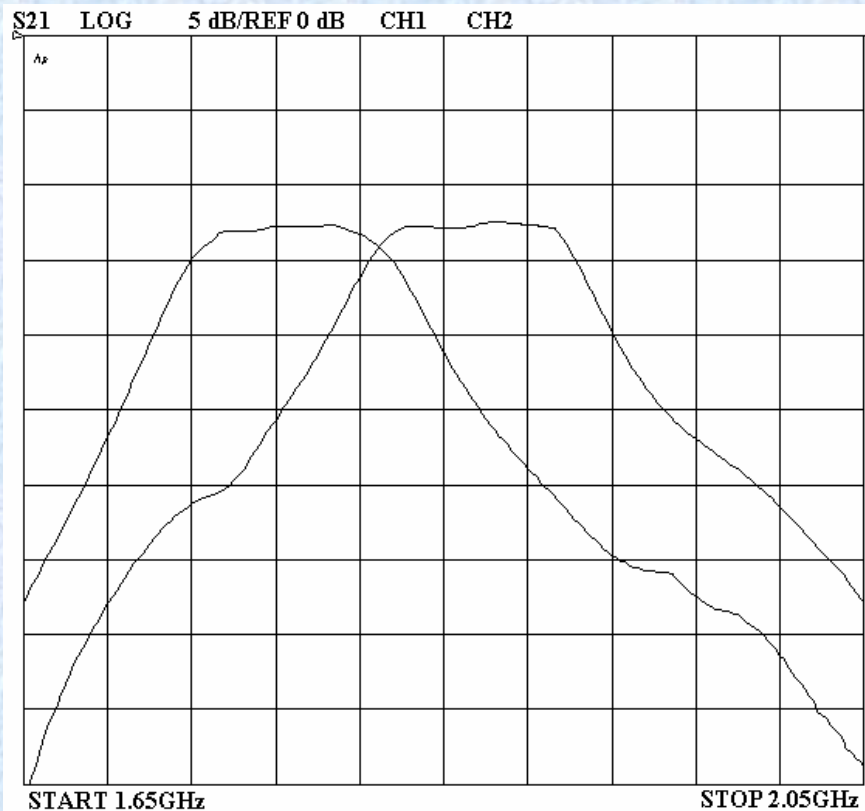

Frequency tuning
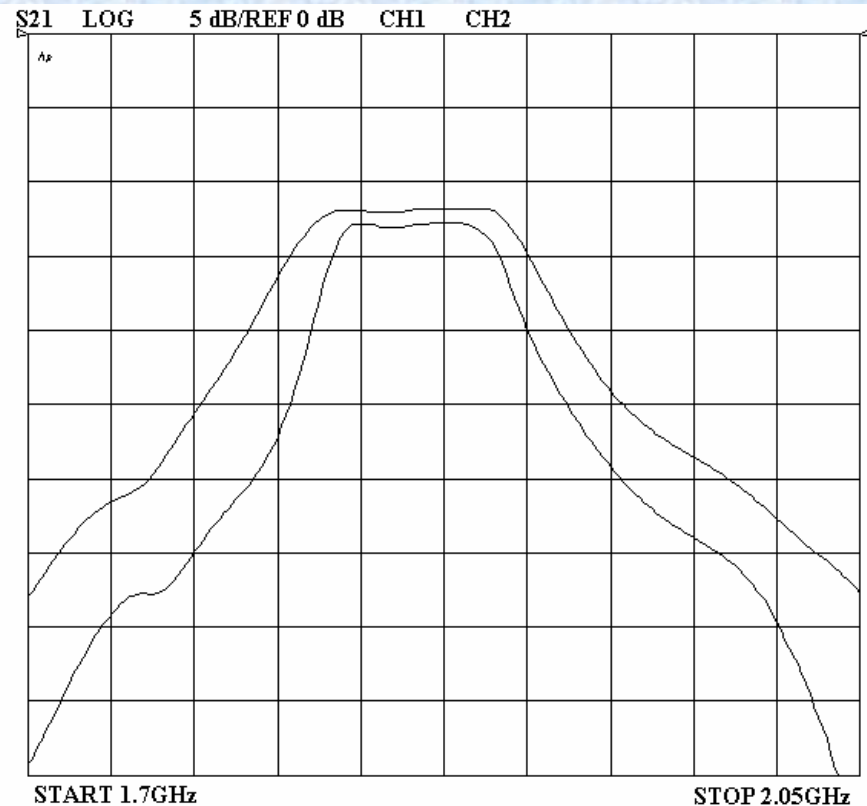
$$f_0 = \{1.77\text{GHz}, 1.86\text{GHz}\}$$




Bandwidth tuning

$$\text{BW} = \{70\text{MHz}, 100\text{MHz}\}$$

ECEN 665 (ESS) Analog & Mixed
Signal Center, Texas A&M
University

Measurement Results

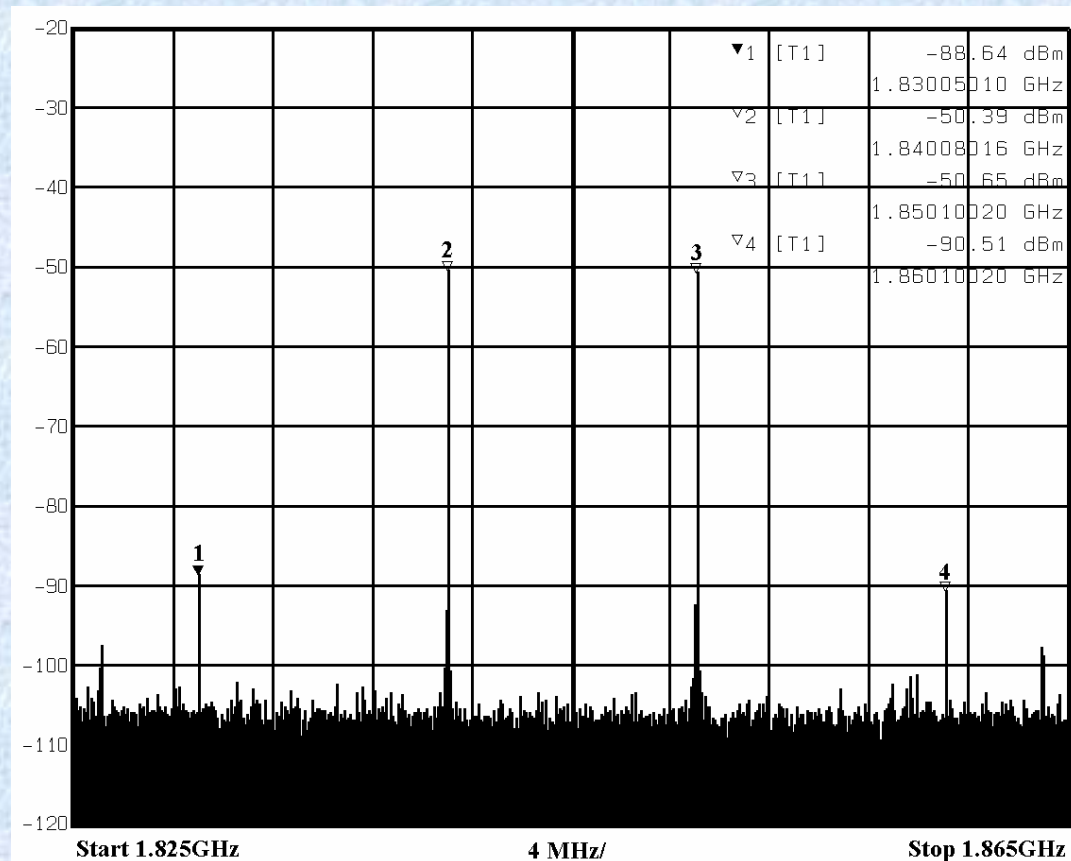


Two Tone intermodulation distortion -34dBm each

ECEN 665 (ESS) Analog & Mixed

Signal Center, Texas A&M

University

Measurement Results

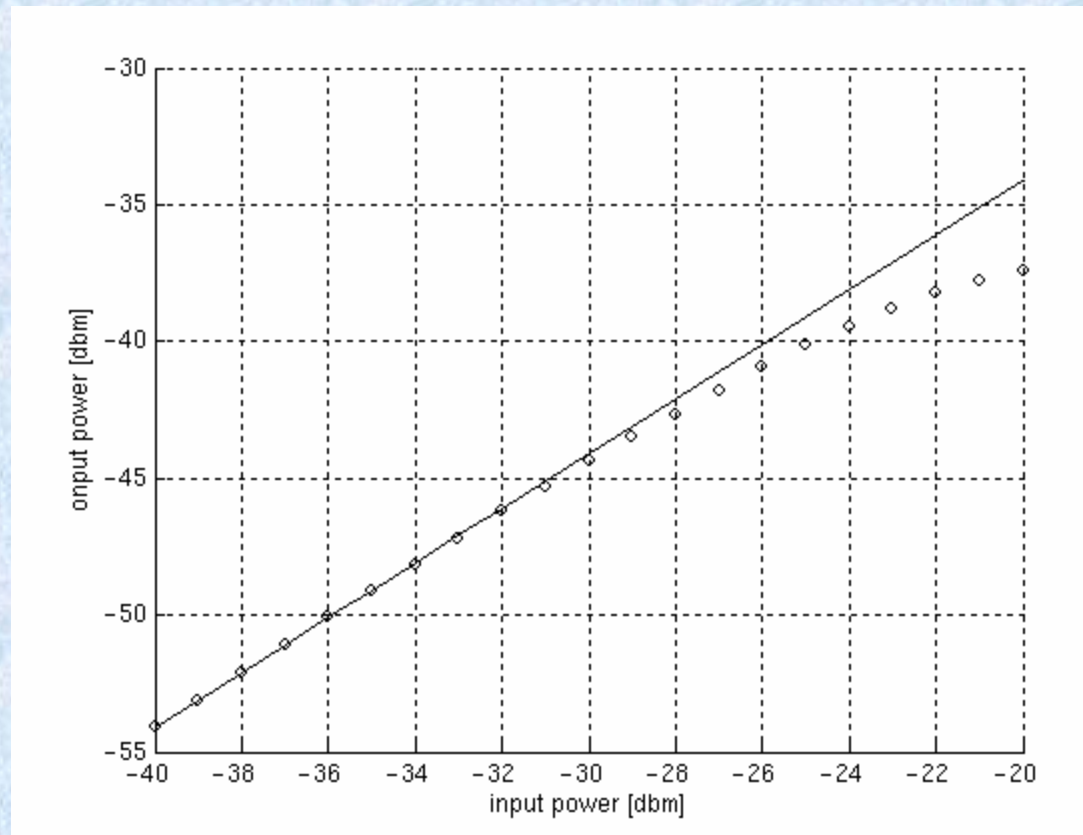

1 dB Compression Dynamic Range

ECEN 665 (ESS) Analog & Mixed
Signal Center, Texas A&M
University

Comparison with previously published work

	[4]	[5]	[6] [*]	This Work
Filter order	4	4	6	4
f_0 (GHz)	0.85	1.9	2.1	1.8
BW (MHz)	18	150	60	80
Passband gain (dB)	0	0	0	9
Ripple in passband (dB)	$< \pm 1$	+1.6	± 0.35	$< \pm 0.25$
Q_{ind}	< 3	?	?	2.7
1dB compression DR	61	63	63	42
Current drain/pole (mA)	19.25	4.5	1.17 ⁺	4
Technology	0.8 μ m CMOS	0.25 μ m BiCMOS	0.25 μ m ⁺ CMOS	0.5 μ m CMOS
Area/pole (mm ²)	0.5	0.25	0.585	0.0375
Supply voltage (V)	2.7	2.7	2.5	2.7

Remarks

- ❑ A 4th Order tunable LC filter is presented in 0.5 μ m CMOS process
- ❑ The architecture uses electric emulation of the magnetic coupling
- ❑ Electric coupling provide the capability of BW tuning with small passband ripple
- ❑ Design trade-offs have been demonstrated
- ❑ The filter achieves 42dB of DR with ± 0.25 dB passband ripple and consumes 16mA

Reference.-

Mohieldin, A.N.; Sanchez-Sinencio, E.; Silva-Martinez, J., "[A 2.7-V 1.8-GHz fourth-order tunable LC bandpass filter based on emulation of magnetically coupled resonators](#)," *IEEE Journal of Solid-State Circuits*, Volume :38 Issue:7, pp 1172-1181 July 2003