

AMSC

Analog and Mixed Signal Center  
Department of Electrical & Computer Engineering



---

# Highly Linear Low Noise Amplifier

Sivakumar Ganesan  
Texas A&M University  
sivakumar@tamu.edu

**Advisors: Dr. Edgar Sánchez-Sinencio  
Dr. Jose Silva-Martinez**



- 
- Motivation
  - Background
  - Proposed Solution
  - Testing Strategy
  - Experimental Results
  - Conclusion




- Numerous co-existing wireless standards and wireless equipment




Palm Powered devices support LAN, WAN, and PAN




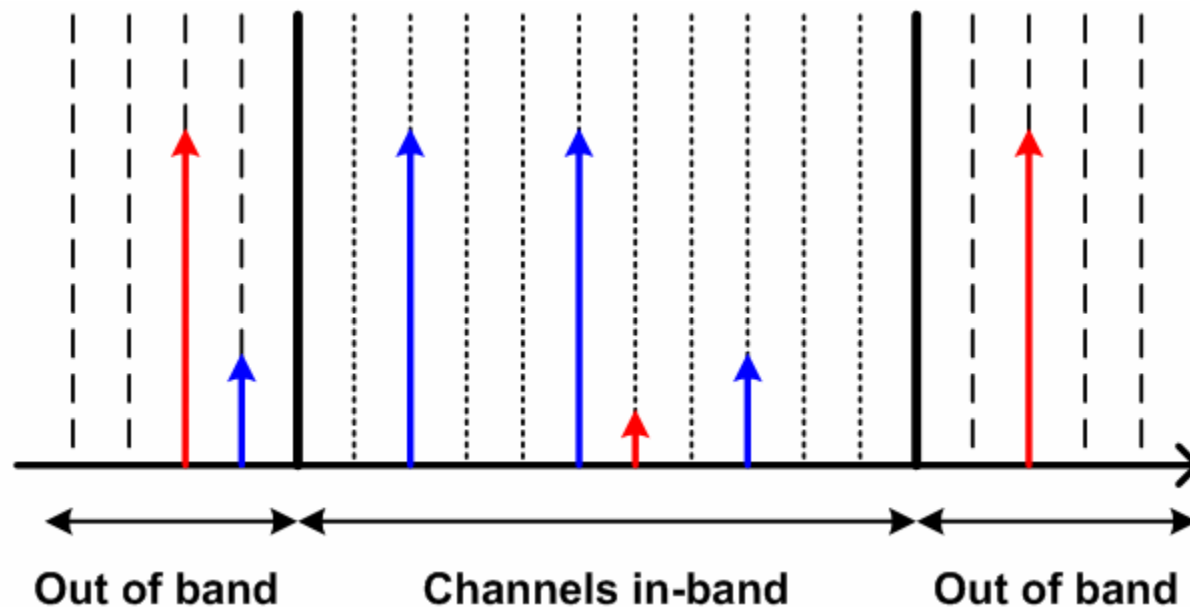- Limited spectrum allotted to each user
- Possible large interferers from other channels in-band and out of band



 

 - Antenna receives the entire band of signals
- Stringent requirements on the receiver front-end
- BPF filters the out of band channels
- LNA receives the entire in-band signals
- In-band channel interference problems in LNA
  - Blocking
  - Intermodulation



$$y(t) = \alpha_1 x(t) + \alpha_2 x^2(t) + \alpha_3 x^3(t)$$


$$x(t) = A_1 \cos \omega_1 t + A_2 \cos \omega_2 t$$

$$y(t) \cong \left( \alpha_1 + \frac{3}{2} \alpha_3 A_2^2 \right) A_1 \cos \omega_1 t + \dots$$

- If  $\alpha_3 < 0$ , a large interferer results in signal being “blocked”

**Desired**

**Interferer**

 

$$x(t) = A_1 \cos \omega_1 t + A_2 \cos \omega_2 t$$


$$y_{IM3}(t) = \frac{3}{4} \alpha_3 A_1^2 A_2 \cos(2\omega_1 - \omega_2) + \frac{3}{4} \alpha_3 A_2^2 A_1 \cos(2\omega_2 - \omega_1)$$

- Third order intermodulation (IM3) components corrupt the signal resulting in distortion
 
# AMSC Linearity Measurement



- Third order Input Intercept Point (IIP3) is a measure of circuit non-linearity
- Fundamental =  $\alpha_1 A$  , IM3 =  $\frac{3}{4} \alpha_3 A^3$









- Low Noise Amplifier
  - First amplifying block in a receiver
  - High gain, Low Noise Figure
  - Presents amplified signals (desired + IM3) to mixer
- Highly linear LNA with high gain and low NF required



- 
- Existing Linearization Techniques
    - Optimum Biasing
    - Negative Feedback
    - Input Impedance Frequency Termination
    - Feedforward Cancellation



- Current =  $i_d = g_{m1}v_{gs} + g_{m2}v_{gs}^2 + g_{m3}v_{gs}^3 + \dots$
- IIP3 =  $\sqrt{\frac{4}{3} \left| \frac{g_{m1}}{g_{m3}} \right|}$
- $g_{m3}=0$  results in very high IIP3

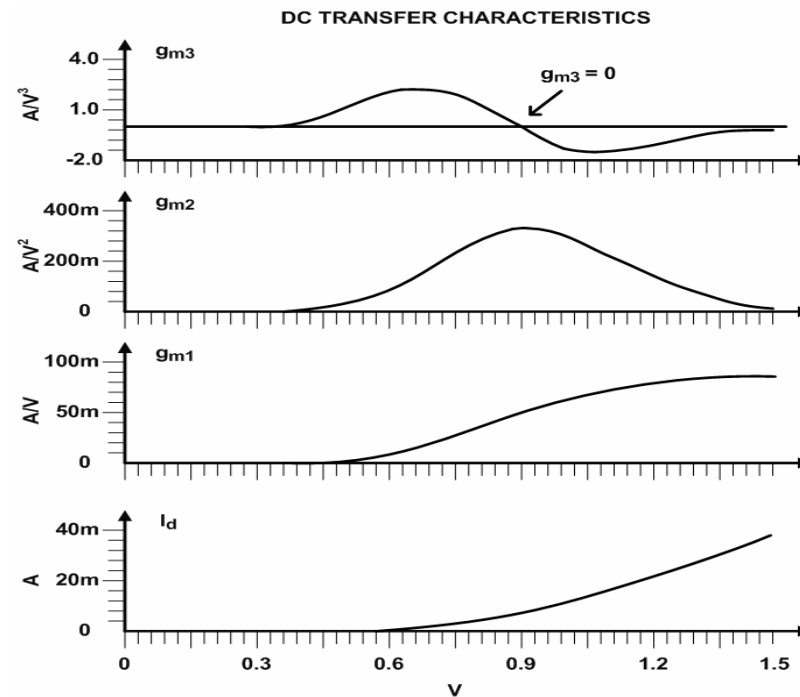 




- Drawbacks
  - High IIP3 obtained over a narrow region
  - Process variations degrade IIP3
  - Limited voltage gain due to restricted input transconductance ( $g_{m1}$ )
  - Poor NF



 - Popular in baseband circuits to improve linearity




- $$IIP3 = \sqrt{\frac{4}{3} \left| \frac{g_{m1}}{g_{m3}} \right| \frac{(1+T_o)^3}{\left( 1 - \frac{2g_{m2}^2 T_o}{g_{m1}g_{m3}(1+T_o)} \right)}}, T_o = g_{m1}\beta$$



- Linearity improvement at the expense of circuit gain
- Second order non-linearity effect on IIP3
- $g_{m3} < 0$ , leads to further deterioration
- Feedback techniques not suitable at RF frequencies




 - Inductor  $L_S$  acts as a feedback network
- Provides best gain and noise performance
- Poor linearity performance due to second order non-linearity feedback


 
# Input Impedance Termination

- Feedback network is frequency dependent
- Different effect on different harmonics



$$|IIP3| \approx \left| \frac{A_1(s)}{I_Q} \right|^3 \left| \frac{V_T}{4} [1 + sC_{je}Z(s)] \left\{ -1 + \frac{A_1(\Delta s)}{g_m} [1 + \Delta s C_{je}Z(\Delta s)] + \frac{A_1(2s)}{2g_m} [1 + 2sC_{je}Z(2s)] \right\} \right| |V_s|^2$$

where


$$\Delta s = (s_a - s_b) \ll s, \quad s_a = j2\pi f_a, \quad s_b = j2\pi f_b$$

$$A_1(s) = \frac{g_m}{sC_{je}Z(s) + s\tau_F g_m Z(s) + g_m \frac{Z(s)}{\beta_o} + 1 + g_m Z_e(s)}, \quad Z(s) = Z_b(s) + Z_e(s)$$



 
# Input Impedance Termination

- The input and output impedances selectively tuned for second harmonic frequencies
- Requires huge passive elements





 - Scaled versions of the input signal are fed to two different amplifiers



$$y_{main}(t) = A.x.(1 + \alpha_2 x^2), \quad y_{aux}(t) = A.\beta.x.(1 + \alpha_2 \beta^2 x^2) * \frac{1}{\beta^3}$$

$$y(t) = y_{main}(t) - y_{aux}(t)$$

$$= A \left( 1 - \frac{1}{\beta^2} \right) .x$$





- Drawbacks
  - Linearity improvement at the expense of gain
  - Reduced NF due to additional active components
  - Mismatch and errors in signal scaling leads to reduced improvement
- Derivative Superposition (DS) method addresses the above problems
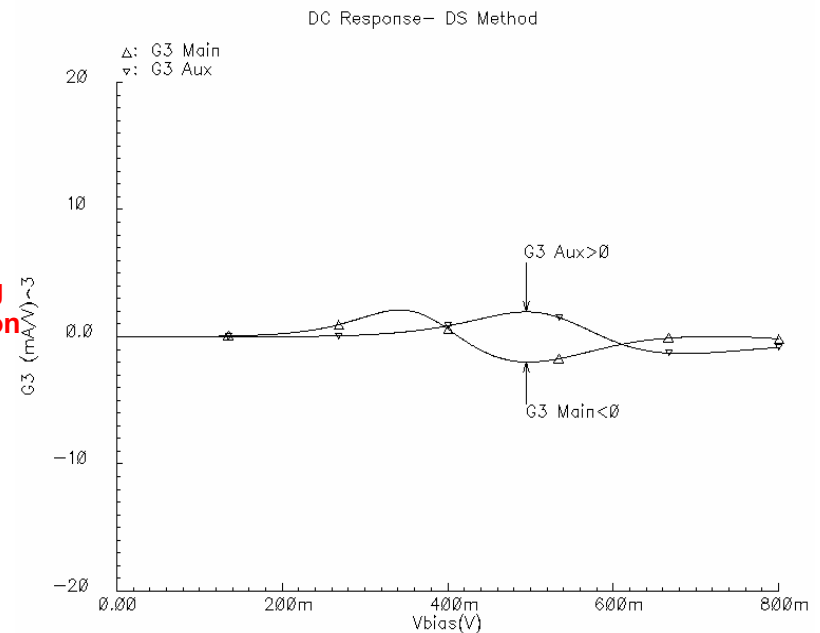 
# AMSC Derivative Superposition (DS) Method




- DS method also addresses the problem of narrow range with optimum biasing technique.
- $g_{m3}$  negative in strong inversion and positive in weak inversion





 - Wide range of bias values with very small  $g_{m3}$  and hence IIP3 improvement obtained
- Drawbacks
  - Second order harmonics ( $2\omega_a, 2\omega_b, \pm\omega_b \pm \omega_a$ ) converted to voltage at the source
  - Control parameter  $V_{gs}$  has both fundamental and second harmonics





$$IIP3 = \frac{4g_{m1}^2 \omega^2 LC_{gs}}{3|\varepsilon|}, \text{ Where}$$

$$\varepsilon = g_{m3} - \frac{2g_{m2}^2/3}{g_{m1} + \frac{1}{2j\omega L} + 2j\omega C_{gs} + Z_s(2\omega) \frac{C_{gs}}{L}}$$



 - Addresses the effect of second order non-linearity feedback
- Magnitude and phase of second order non-linearity contribution to IM3 is tuned to cancel the third order non-linearity contribution to IM3



 

$$IIP_3 = \frac{4g_{1A}^2 \omega^2 [L_1(C_A + C_B) + L_2 C_A]}{3|\varepsilon|}, \text{ Where}$$

$$\varepsilon = g_{3B} n(s) |n(s)|^2 \left[ 1 + \frac{L_2 C_A}{L_1(C_A + C_B) + L_2 C_A} \right] + g_{3A} - \frac{2g_{2A}^2}{3g_{1A}} \frac{1}{1 + \frac{1}{j2\omega(L_1 + L_2)g_{1A}}}$$

$$n(s) = 1 + j\omega L_2 g_{1A}$$



- Weak inversion transistor connected in parallel degrades NF

$$i_{nd}^2 = 4kT\Delta f\gamma g_{d0}$$

$$i_{ng}^2 = 4kT\Delta f\delta \frac{\omega^2 C_{gs}^2}{5g_{d0}}$$

$$g_{d0} = I_{Dsat} / \phi_t$$

- Auxiliary transistor loads the input affecting the frequency of operation
- Auxiliary transistor affects both linearity and input match leading to increased design steps








---
 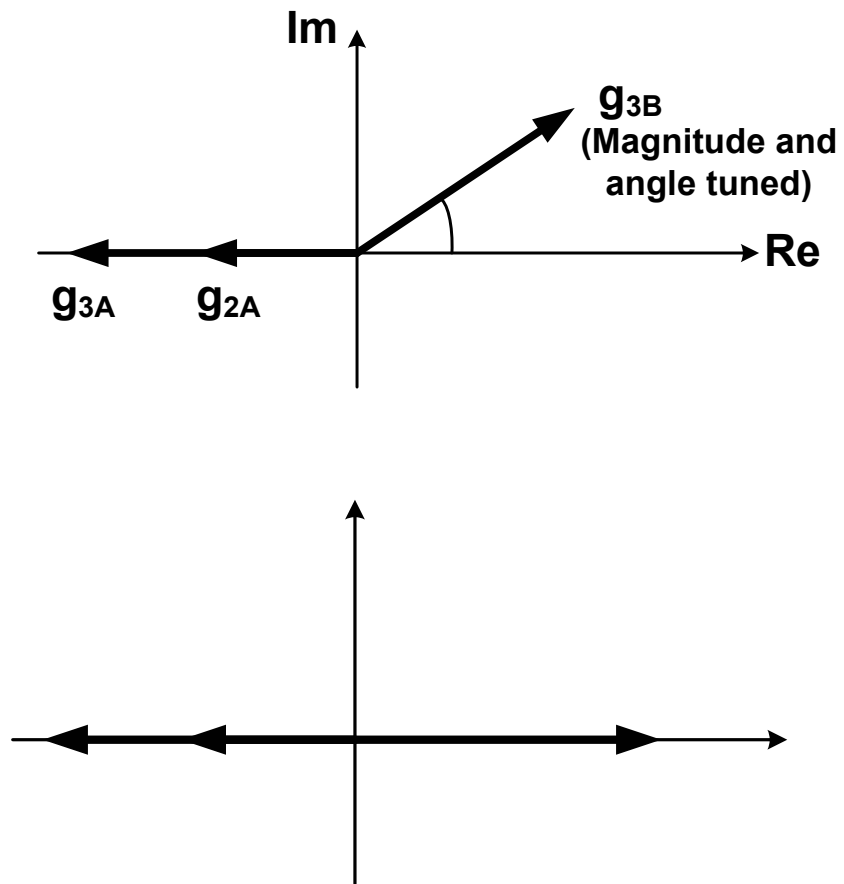
# Proposed Solution




- 
- An auxiliary circuit is unavoidable to achieve high linearity
  - IM3 components in the drain current of the main transistor has the required information of its non-linearity
  - Auxiliary circuit is used to tune the magnitude and phase of IM3 components
  - Addition of main and auxiliary transistor currents results in negligible IM3 components at output



 



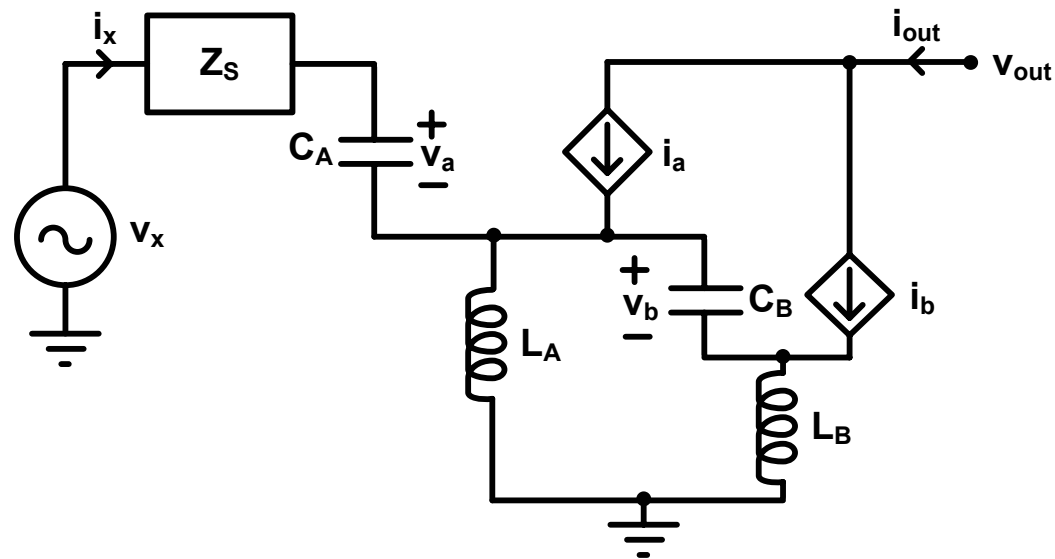- IIP3 derived using the harmonic input method of Volterra series analysis



$$i_a = g_{1a}v_a + g_{2a}v_a^2 + g_{3a}v_a^3$$

$$i_b = g_{3b}v_b^3$$

$$i_{out} = i_a + i_b = C_1(s_1) * v_x + C_2(s_1, s_2) * v_x^2 + C_3(s_1, s_2, s_3) * v_x^3$$



$$IIP3 = \frac{1}{6 \operatorname{Re}(Z_s(s)) |A_1(s)|^2} \left\{ \frac{g_{1a}}{\varepsilon} \right\}$$


$$\text{where, } \varepsilon = g_{3a} - \frac{g_{2a}^2}{3g_{1a}} + g_{3b} n(s) |n(s)|^2 \frac{2 + s^2 L_B C_B}{2(1 + s^2 L_B C_B)}$$

$$n(s) = \frac{sL_A (g_{1a} + sC_A)}{1 + sC_B (sL_A + sL_B)}$$

- The effect of second order non-linearity can be seen in the above equation
- The value of  $g_{3b}$  can be tuned to obtain high IIP3 by choosing appropriate values for the inductors  $L_A$  and  $L_B$  and the aspect ratios of the transistors.




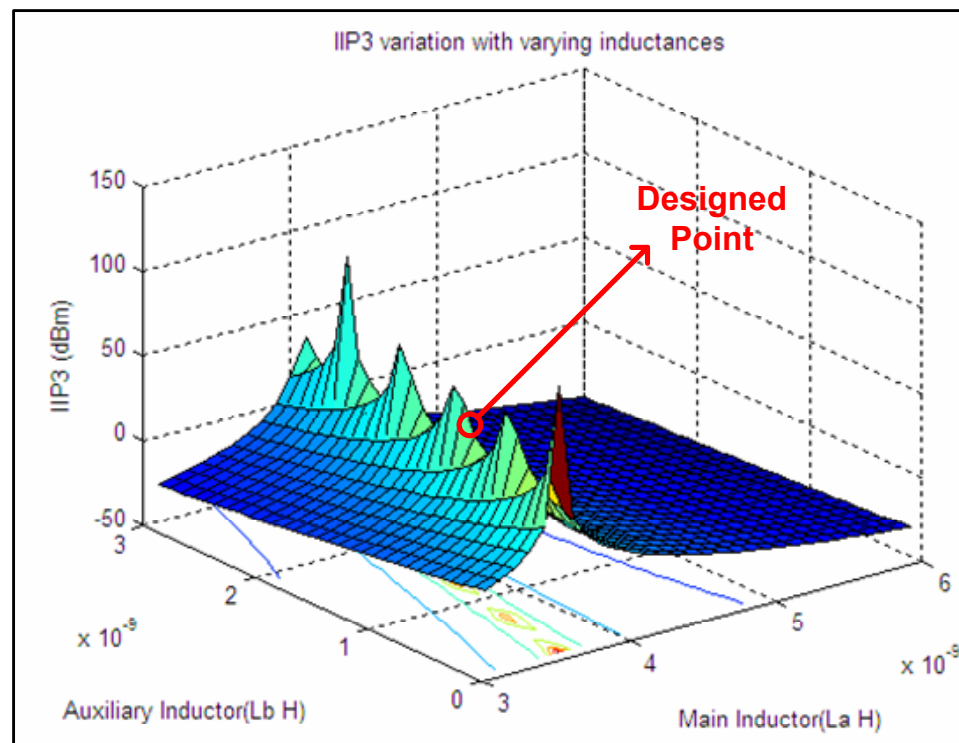- MATLAB plots for different values of  $L_A$  and  $L_B$  is plotted
- The result corroborates the idea of IIP3 improvement by cancellation of IM3 components






### Variation with $L_a$

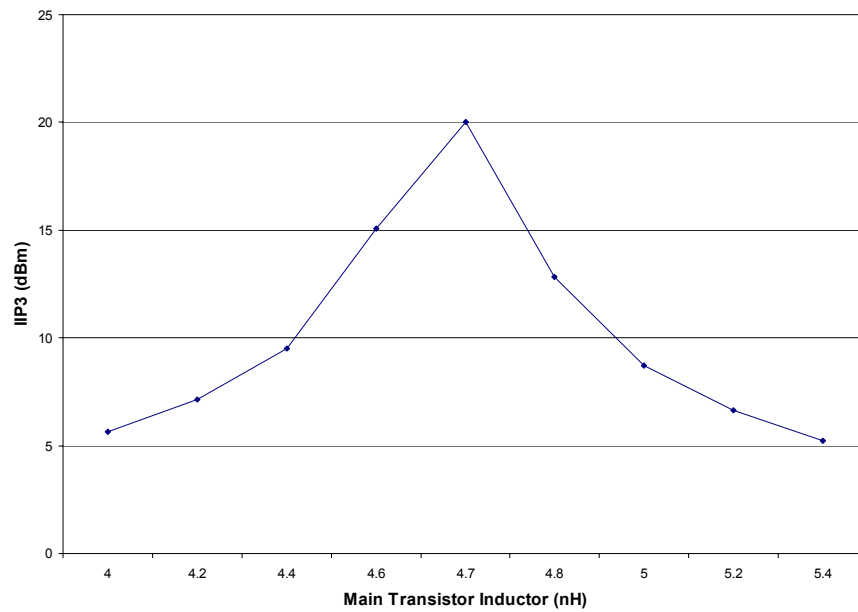

### Variation with $L_b$

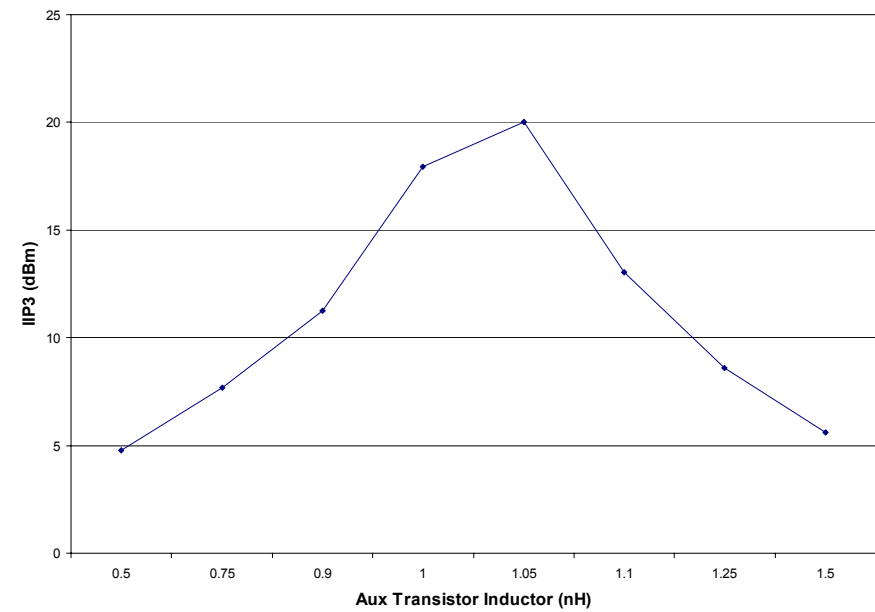






- If  $|s^2 L_A C_B| \ll 1$ , the input impedance can be simplified to that of a cascode LNA

$$Z_{in} = sL_G + \frac{1}{sC_A} + sL_A + \frac{g_{1a}L_A}{C_A}$$


- The input matching is unaffected by the auxiliary transistor




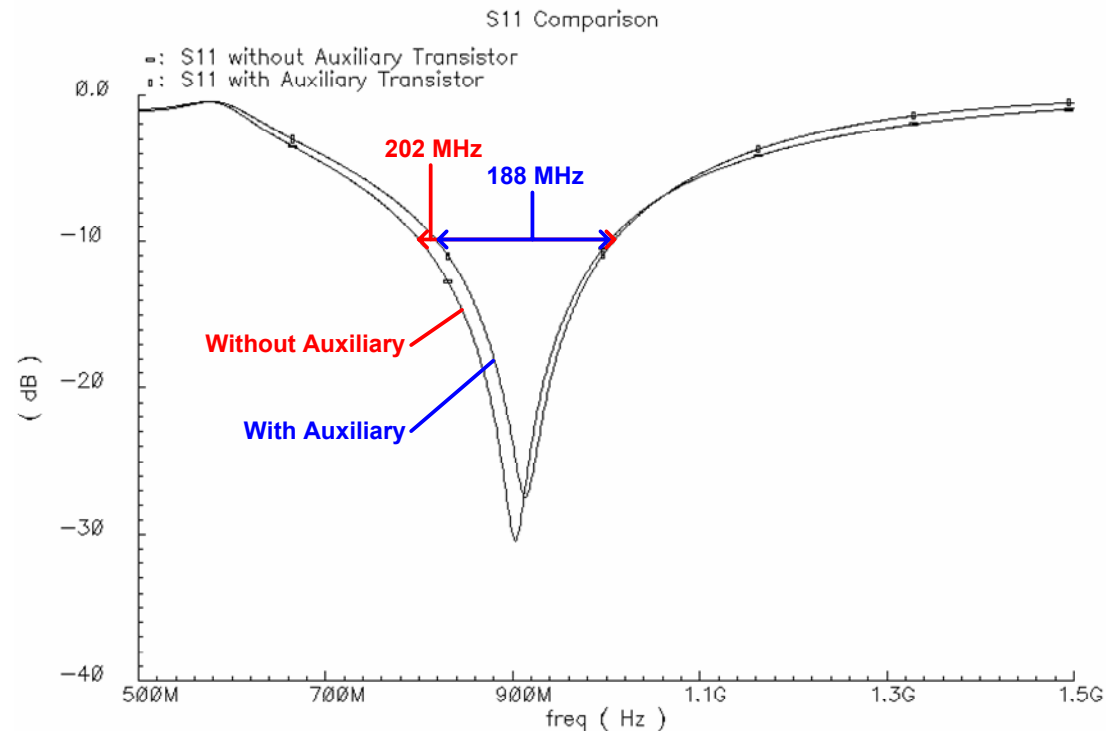- Effect on input match ( $S_{11}$ ) with and without auxiliary transistor



 - The gate noise current of the auxiliary transistor gets added with the drain noise current of main transistor and is attenuated by the gain of LNA



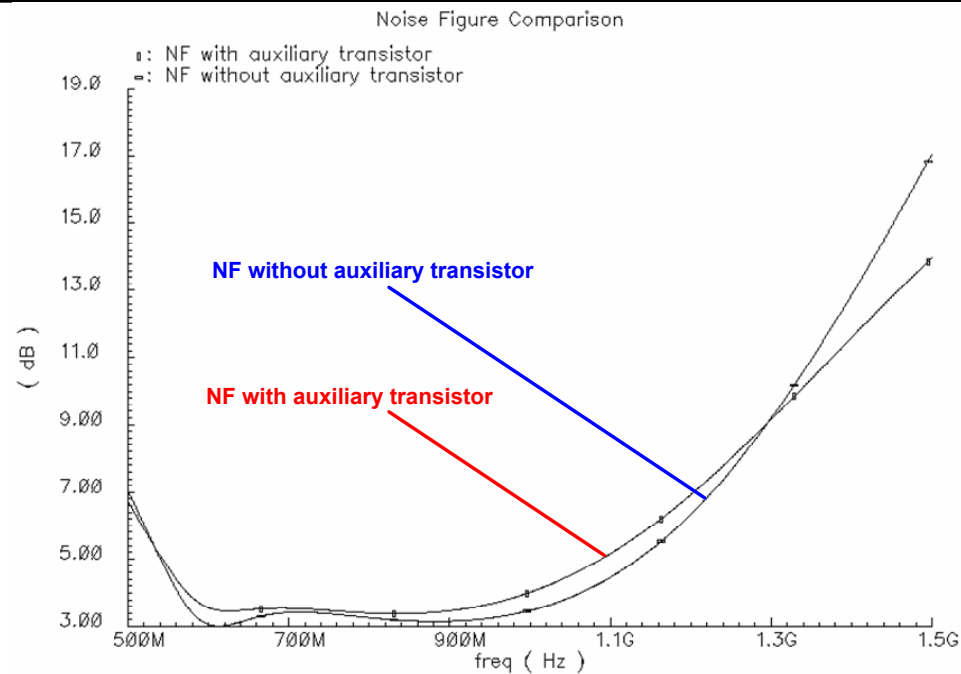

- 0.3dB degradation in NF observed
- Lossy inductor in the auxiliary branch contributes to increased NF




- Linear LNA was designed and fabricated in TSMC 0.35 $\mu\text{m}$  CMOS technology
- The inductors were designed using ASITIC and a Q of 2.5 was obtained
- The LNA was designed to have maximum gain at 900MHz
- The LNA fabricated was a stand alone LNA terminated by the 50 $\Omega$  port impedance


# Component Values



Component	Value
$M_A$	24 $\mu\text{m}$ /0.4 $\mu\text{m}$ , $m=16$
$M_C$	24 $\mu\text{m}$ /0.4 $\mu\text{m}$ , $m=16$
$M_B$	24 $\mu\text{m}$ /0.4 $\mu\text{m}$ , $m=36$
$L_G$	30 nH
$L_A$	5 nH
$L_B$	1.05 nH
$L_D$	10 nH

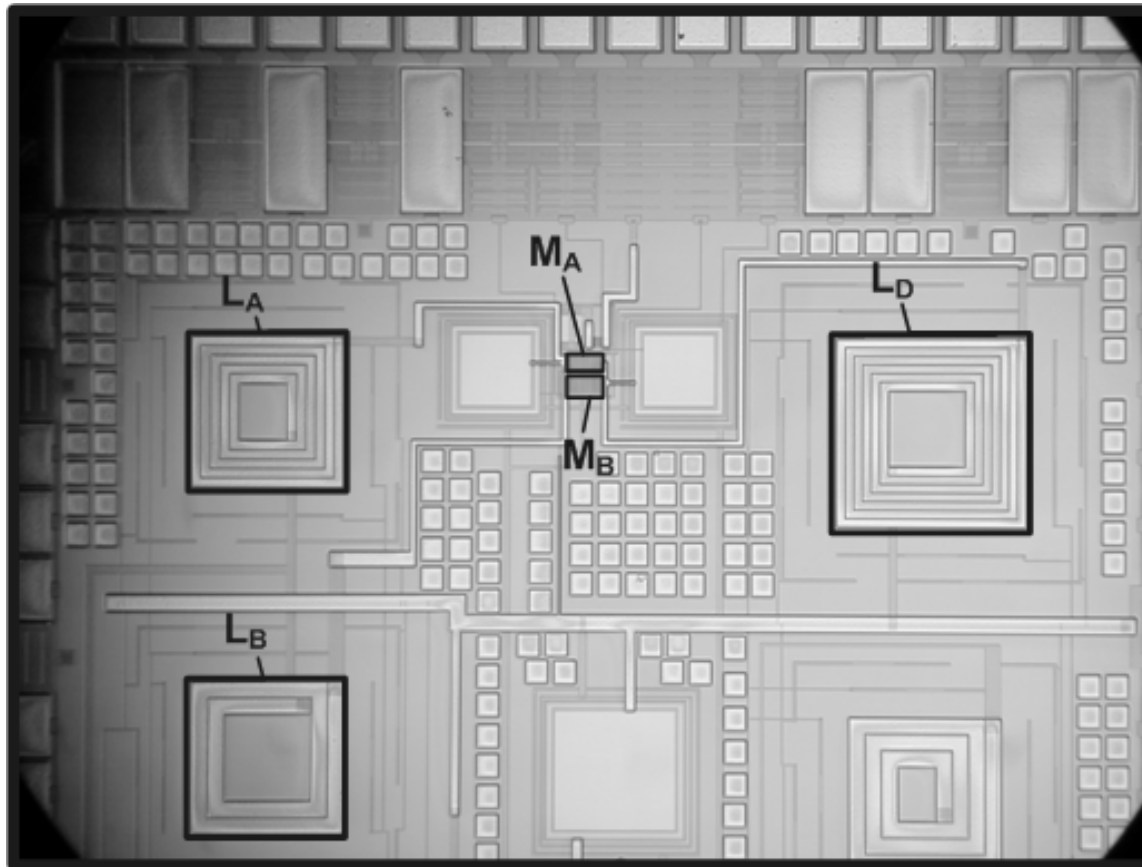

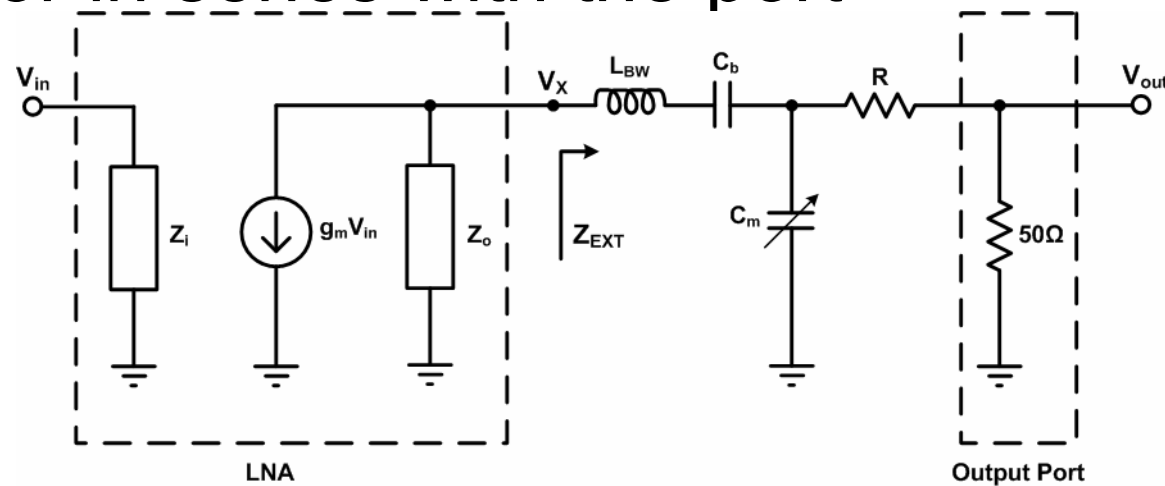- The gain obtained in LNA is less as it sees a  $50\Omega$  load impedance
- Gain can be improved by connecting a resistor in series with the port



• LNA Gain =  $\frac{V_x}{V_{in}} = \frac{V_{out}}{V_{in}} * \frac{R + 50}{50}$






- 
- Increased gain results in larger signal swings
  - LNA subject to large signal swings is an ideal test for linearity
  - Linearity of LNA unaffected due to linear resistive element




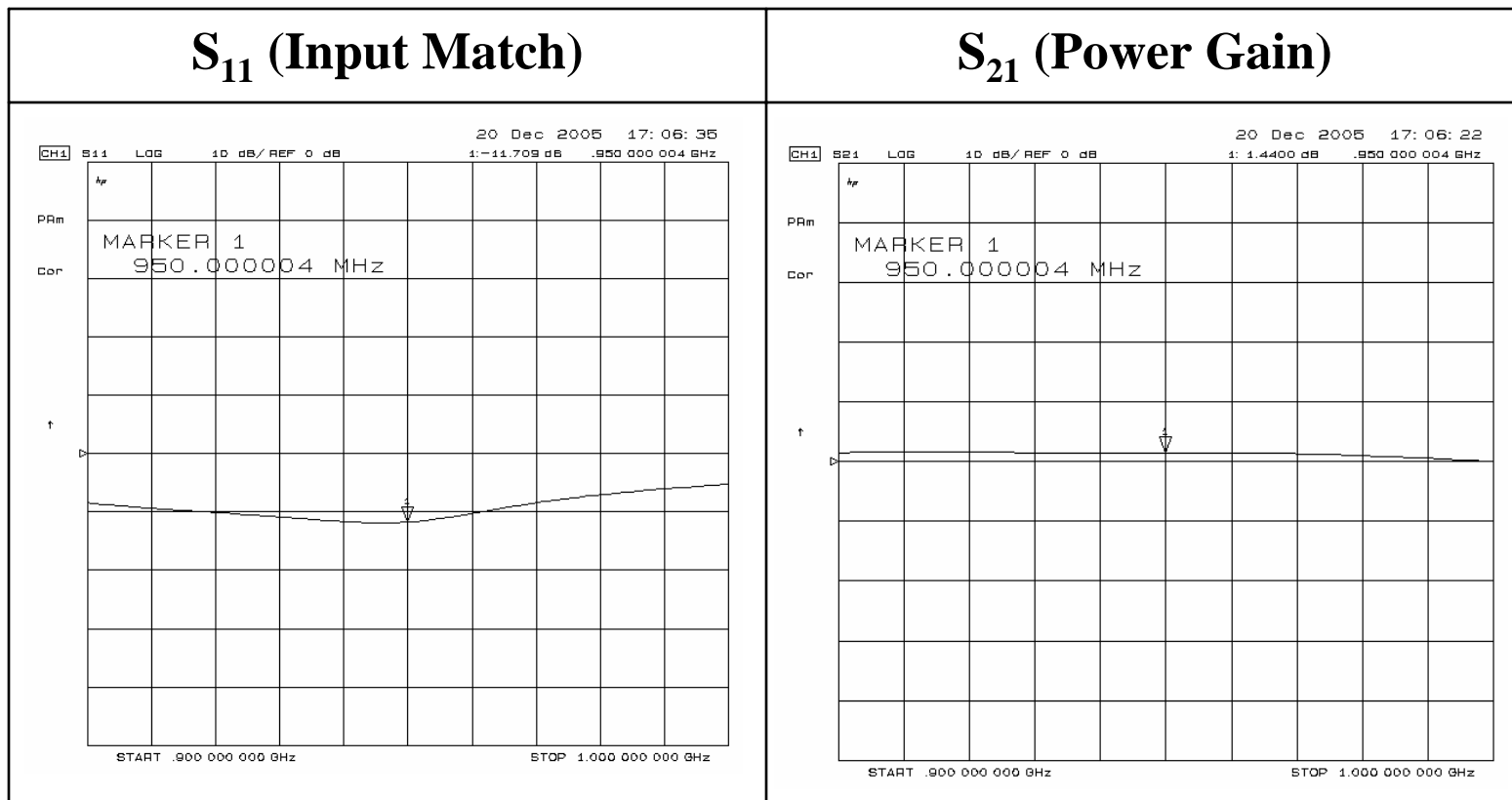
- $R=0\Omega$ ,  $S_{11}=-15.85$  dB,  $S_{21}=4.4$  dB, Gain= 4.4 dB





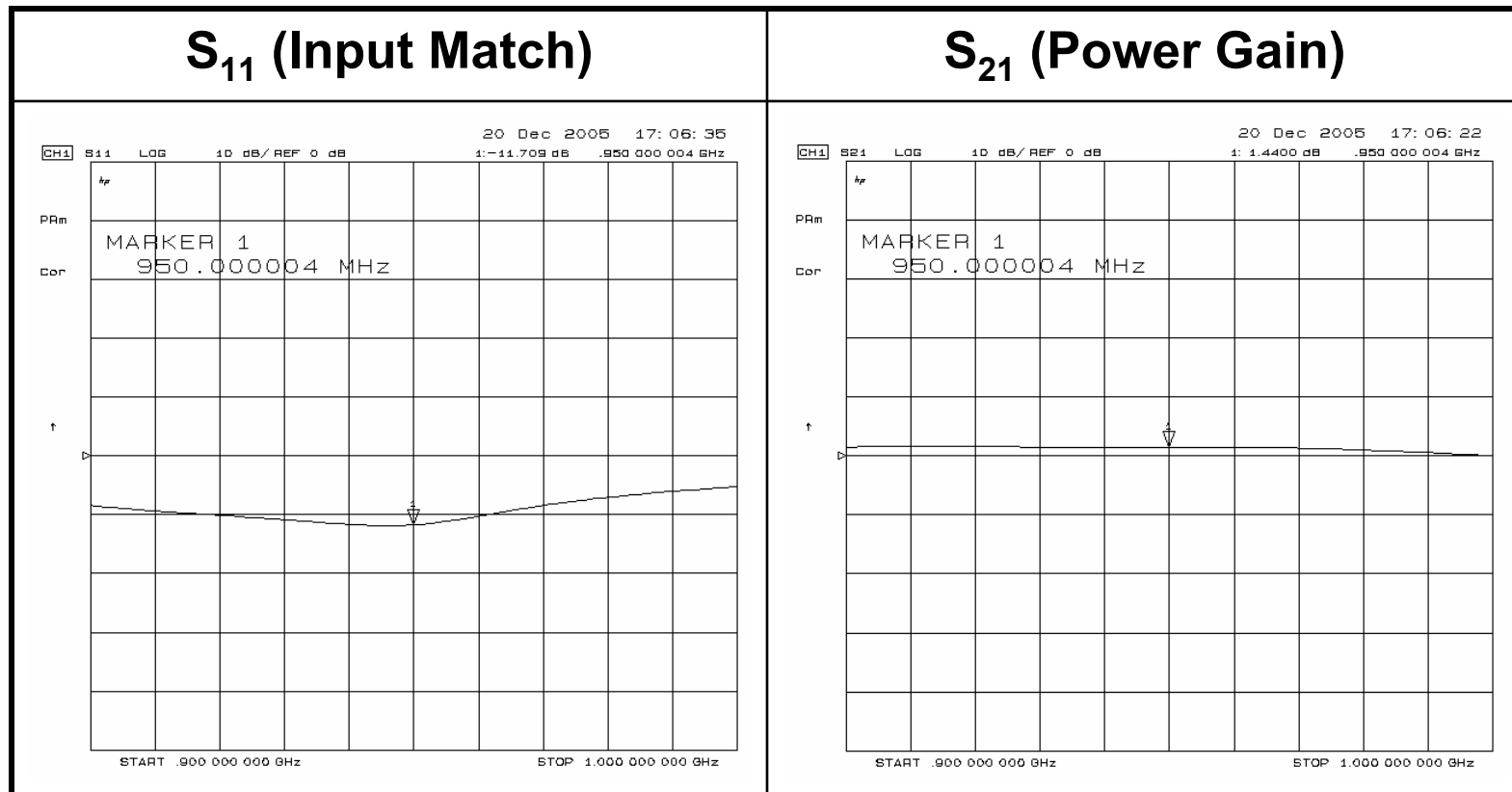- $R=75 \Omega$ ,  $S_{11}=-11.7$  dB,  $S_{21}=1.5$  dB, Gain= 9.5 dB



 



- $R=75 \Omega$


$$IIP3(dBm) = P_{in} + \frac{P_f - P_{IM3}}{2}$$


where  $P_{in}$  = Total Signal Input Power

$P_f$  = Total Signal Output Power

$P_{IM3}$  = Total IM3 tone Output Power

 
- $P_{in} = -10dBm$ ,  $P_f = -13.2dBm$
- $P_{IM3} = -75.07dBm$
- $IIP3 = +20.93 dBm$




 



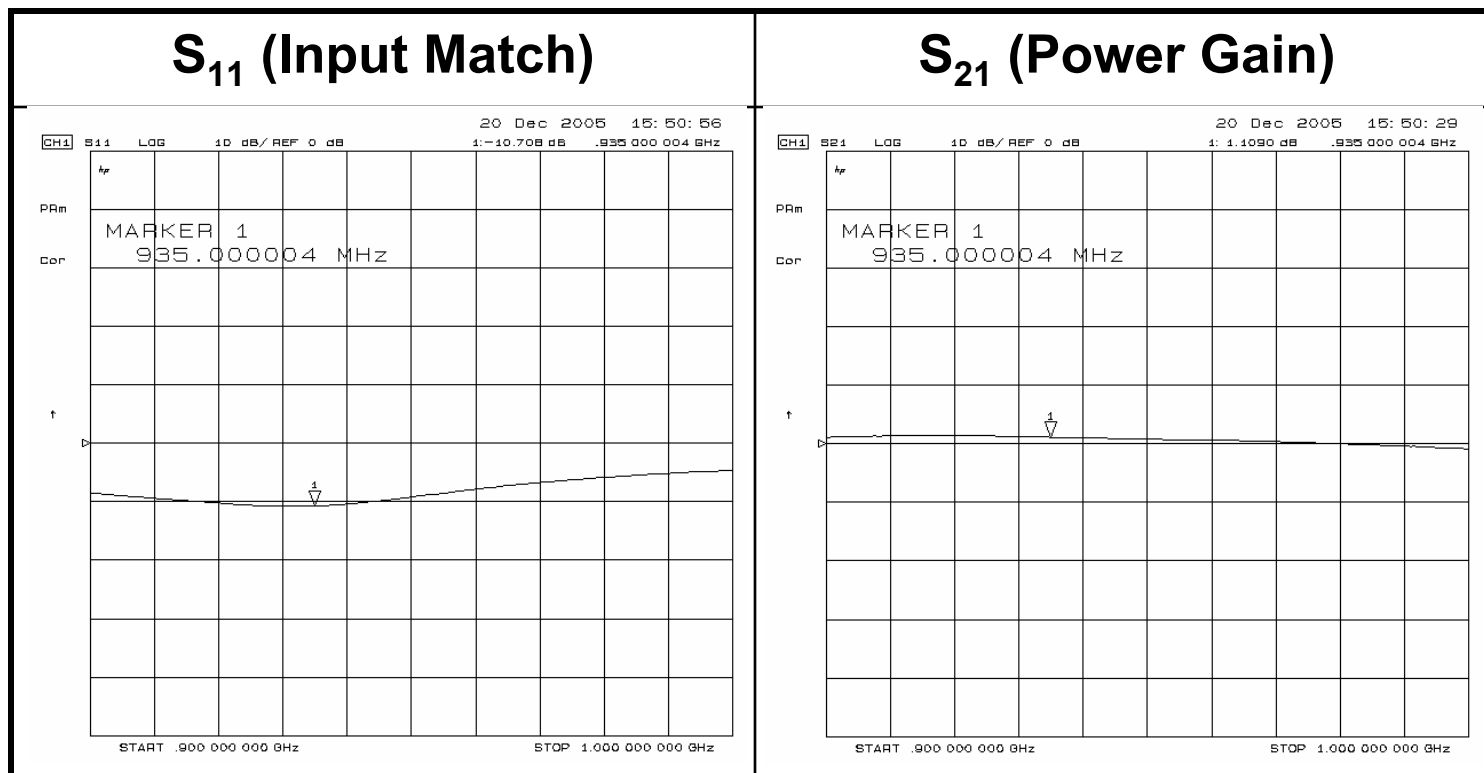- $R=100\ \Omega$ ,  $S_{11}=-10.7\ \text{dB}$ ,  $S_{21}=1.1\ \text{dB}$ , Gain= 10.6 dB




 





R ( $\Omega$ )	$S_{11}$ (dB)	$S_{21}$ (dB)	LNA Gain (dB)	IIP3 (dBm)
0	-15.85	4.4	4.4	20
75	-11.7	1.5	9.5	20.9
100	-10.7	1.1	10.6	21
150	-9.5	-0.5	11.5	20.5

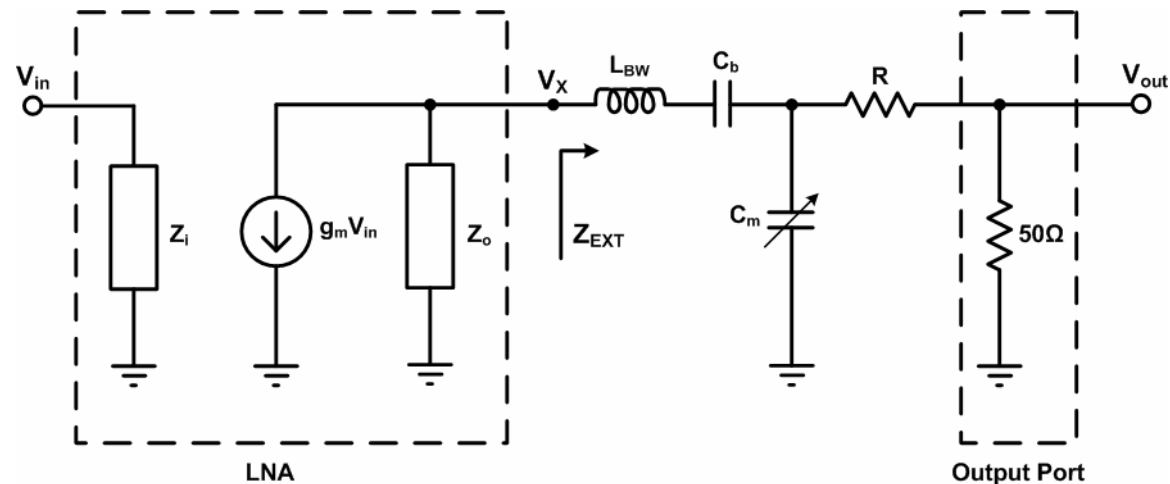

- 6dB increment in gain when 'R' is changed from  $0\Omega$  to  $100\Omega$  and hence on-chip load resistance can be computed to be  $150\Omega$
- Gain of LNA with  $Z_{ext}=\infty$  is 6dB more than gain with  $R=100\Omega$
- Gain of LNA adding other losses is estimated to be 18.5dB
- The NF of the LNA after de-embedding the noise contribution of termination resistors ( $R=100\Omega$  and  $50\Omega$  port) is calculated to be 1.76dB



Work	Technology	Freq (GHz)	Gain (dB)	NF (dB)	IIP3 (dBm)	$P_{dc}$ (mW)	FOM
This Work	0.35 $\mu$ m CMOS	0.95	18.5	1.76	21	22.5	793
JSSC '04	0.35 $\mu$ m CMOS	0.9	10	2.8	15.6	21.1	19
ISSCC '01	0.35 $\mu$ m CMOS	0.9	2.5	2.8	18	45	3
MTT '05	0.25 $\mu$ m CMOS	0.9	15.5	1.65	22	24.2	503
ISCAS '04	0.25 $\mu$ m CMOS	0.9	14.6	1.8	10.5	5.4	117
ESSCC '05	0.5 $\mu$ m SiGe BiCMOS	0.88	15.7	1.4	11.7	11.7	124
ISCAS '04	0.18 $\mu$ m CMOS	3	6.5	1.9	15	8.9	29
ISSCC '03	0.25 $\mu$ m CMOS	2.2	14.9	3	16.1	23.5	54



Fig 1 shows the simplified small signal model of LNA.  $R_L$  is the load impedance of LNA presented by the LC resonant circuit at the output,  $R$  is the external resistor connected to improve the gain and  $50\Omega$  is the resistance of the port.


 


Fig 1: Small Signal Model

For numerical analysis a value of  $R_L=150\Omega$  and  $R=75\Omega$  are used below.

From Table 3 in the paper, the measured gain at the point VLNA shown in Fig 1 is 10.5dB for  $R=75\Omega$  and NF is 2.95dB. Hence

$$NF = 1 + \frac{V_{measured-in}^2}{V_{50\Omega}^2} = 10^{2.95/10} = 1.972 \quad (1)$$

 

**Fig 2: Noise Analysis**

Fig 2 shows the model used for noise analysis.  $i_{LNA}^2$  and  $i_{RL}^2$  are the noise currents due to input transistor and the load resistance ( $R_L$ ) respectively.

$i_{LNA}^2 + i_{RL}^2$  is reflected to the output port to generate  $v_{LNA\_out}^2$

The resistors  $R$  and  $50\Omega$  generate an output noise voltage at the node 'OUT' given by

$$\begin{aligned} V_{add}^2 &= 4KT \left[ \frac{1}{50} \left( \frac{R + R_L}{R + R_L + 50} \right)^2 50^2 + R \left( \frac{50}{R + R_L + 50} \right)^2 \right] \\ &= 4KT * 50 \left[ \left( \frac{R + R_L}{R + R_L + 50} \right)^2 + \frac{R * 50}{(R + R_L + 50)^2} \right] \\ &= 4KT * 50 * (0.72) \end{aligned} \quad (2)$$

The output noise measured at the node 'OUT' is the sum of noise contributed by the LNA and the output resistive network formed by  $R$  and  $50\Omega$  and is given as follows.

$$\begin{aligned}
 V_{measured-out}^2 &= V_{LNA\_out}^2 * \left( \frac{50}{R+50} \right)^2 + V_{add}^2 \\
 &= V_{LNA\_out}^2 * \left( \frac{50}{R+50} \right)^2 + 4KT * 50 * 0.72 \quad (from (2))
 \end{aligned}
 \tag{3}$$

The overall gain of LNA for R=75Ω is given as follows.

$$Overall\ Gain = \frac{V_{out}}{V_{in}} = \frac{V_{LNA\_out}}{V_{in}} * \frac{V_{out}}{V_{LNA\_out}}$$

$$\frac{V_{LNA\_out}}{V_{in}} = 10.5\ dB = 3.35$$

$$\frac{V_{out}}{V_{LNA\_out}} = \frac{50}{50+75} = 0.4$$

$$Overall\ Gain(A_v) = 3.35 * 0.4 = 1.34$$



Total input measured noise is given as follows.

$$\begin{aligned}
 V_{measured-in}^2 &= \frac{V_{measured-out}^2}{A_v^2} \\
 &= V_{LNA-in}^2 + \frac{4KT * 50 * 0.72}{A_v^2} \quad (\text{from (3)})
 \end{aligned}$$

Where  $V_{LNA-in}^2$  is the total input referred noise contribution of LNA and  $R_L$  alone.

Let  $V_{n50}^2 = 4KT * 50$  Hence total input referred noise contribution of LNA and the load resistor alone is given by

$$\begin{aligned}
 V_{LNA-in}^2 &= V_{n50}^2 \left[ 10^{2.95/10} - 1 \right] - \frac{V_{n50}^2 * 0.72}{A_v^2} \quad (\text{from (1)}) \\
 &= V_{n50}^2 (0.9 - 0.4) \\
 &= V_{n50}^2 (0.5)
 \end{aligned}$$

De-embedded NF = 1+0.5=1.76dB



- 
- A highly Linear LNA using a non-linearity cancellation technique has been proposed
  - Theoretical analysis using Volterra series has been done to corroborate the idea
  - The LNA has been designed and fabricated in TSMC 0.35 $\mu$ m technology
  - An IIP3 of +21dBm has been experimentally achieved