
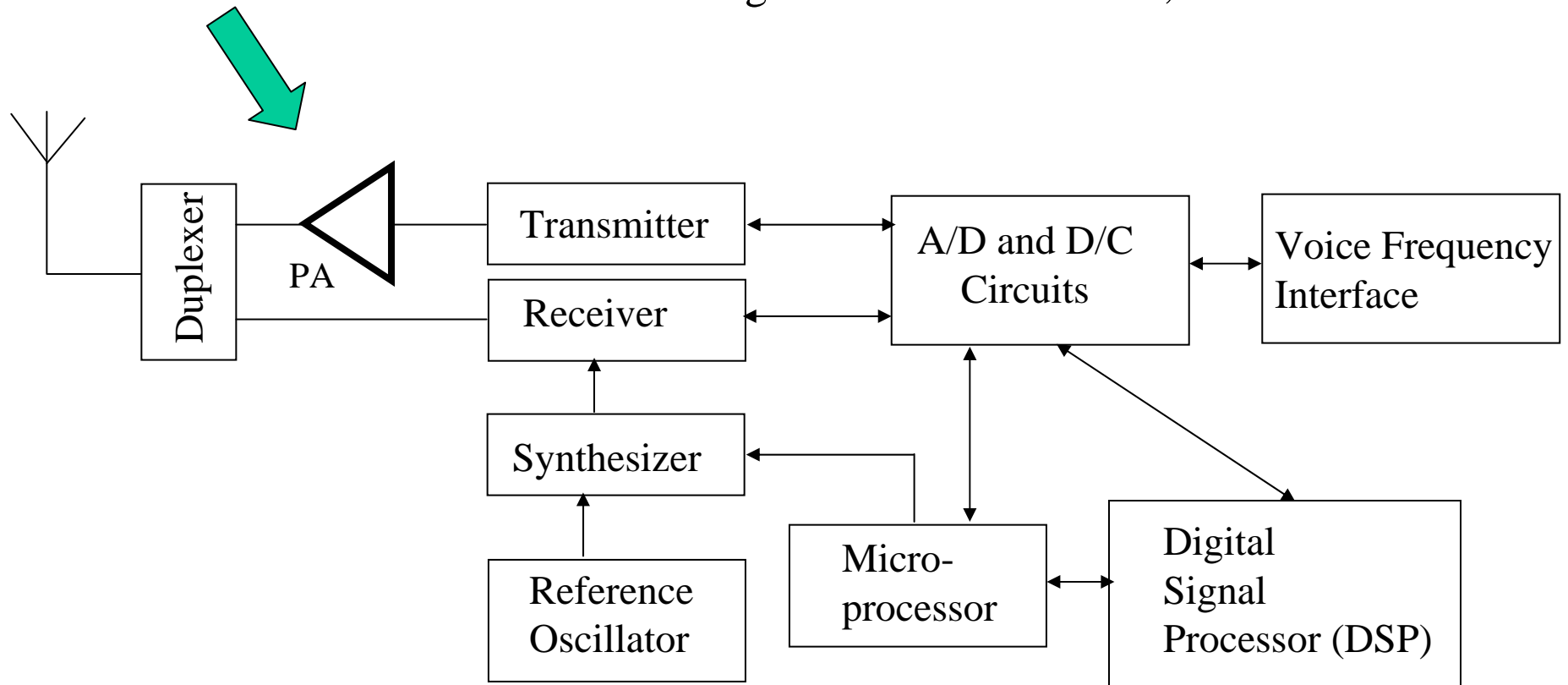

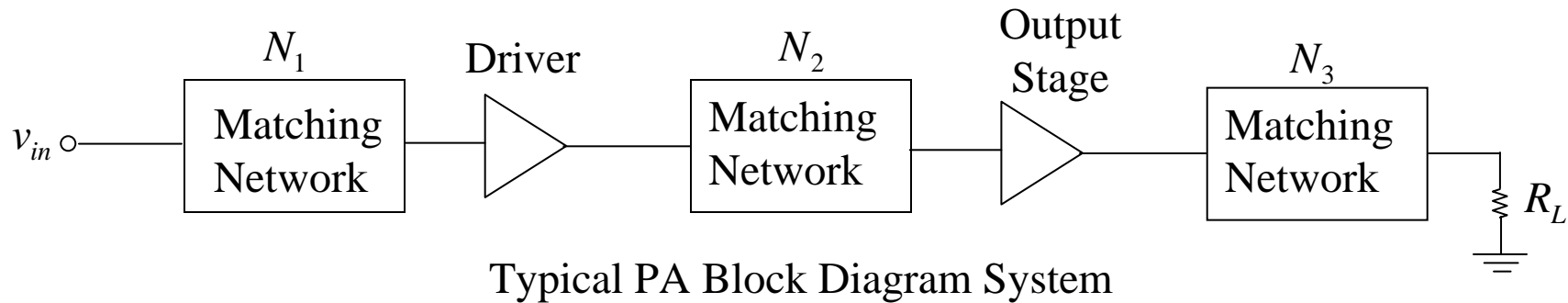
# POWER AMPLIFIERS


General Block Diagram of Cellular Radio; **where is the PA?**


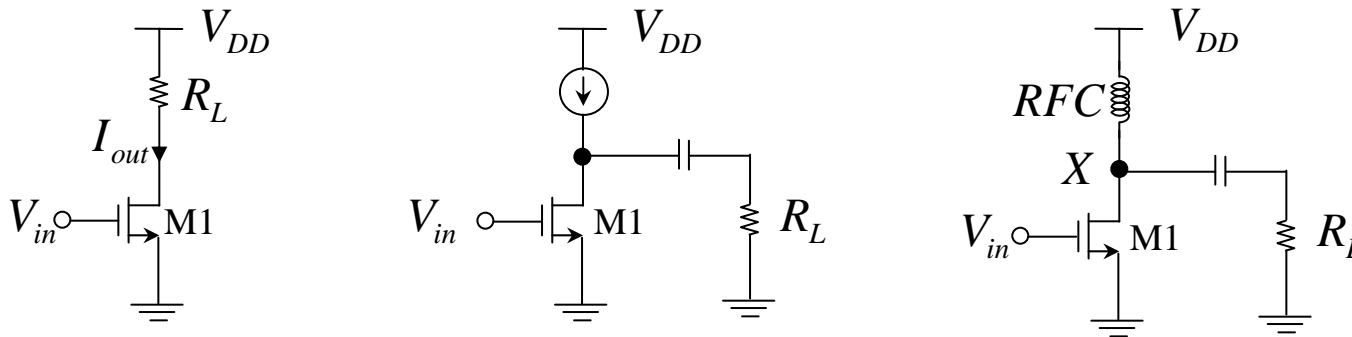
## Power Amplifier System Level Considerations



- Why can designers use only an amplifier? like this:



Common-Source Stages

To deliver for instance a 1W of power to a 50  $\Omega$  antenna with common-source is not feasible.

- Power-Amplifier Metrics

- Power Efficiency  $\eta_{PA}$

$$\eta_{PA} = \frac{P_{load}}{P_{sup ply}} = \frac{P_{RF-out}}{P_{DC-in}}$$

Ideal  $\eta_{PA} = 100\%$

- Power-Added Efficiency ( Linear concept)

$$PAE = \frac{P_{load} - P_{input}}{P_{sup ply}} = \frac{P_{load}}{P_{sup ply}} - \frac{P_{input}}{P_{sup ply}}$$

$$PAE = \frac{P_{load}}{P_{sup ply}} \left( 1 - \frac{P_{input}}{P_{load}} \right) = \eta_{PA} \left( 1 - \frac{1}{G} \right)$$

where  $G = \frac{P_{RF-out}}{P_{RF-in}}$

- Output-Referred Compression  $P_{o-1dB}$  ( **non-linear concept**)

$$P_{o-1dB} \triangleq G P_{in-1dB}$$

$$P_{o-1dB} = 10 \log G + P_{in-1dB}$$

## Power Amplifier for GSM Handset


### Typical Requirements of Power Amplifier:

- Positive supply only
  - 890 to 915 MHz transmit frequency (GSM 900)
  - $\approx 3$  Watts power out of amplifier ( $\approx 1.2$  W allowed but not popular)
  - Efficiency  $> 40\%$  (Market place issue)
  - $< 4$  dB compression (Affects efficiency, limited by spurious signal accentuation)
  - Gain Control capability  $> 34$  dB (Allows for variation in other parts of transmit path)
  - Supply voltage: 5 V (min.) to 8.5 V (during battery charge, in operation)
- Because of inductive loads, output device breakdown requirement may be  $> 17$  V.

### System Control Requirements:

- Strict turn-on time template with limits on spurious outputs during turn-on
- Control Range; 28 dB in 2 dB steps
- Absolute tolerance;  $\pm 2.5$  dB for highest power and  $\pm 6$  dB for lowest power
- Flatness control of output pulse ( $\pm 1.0$  dB)

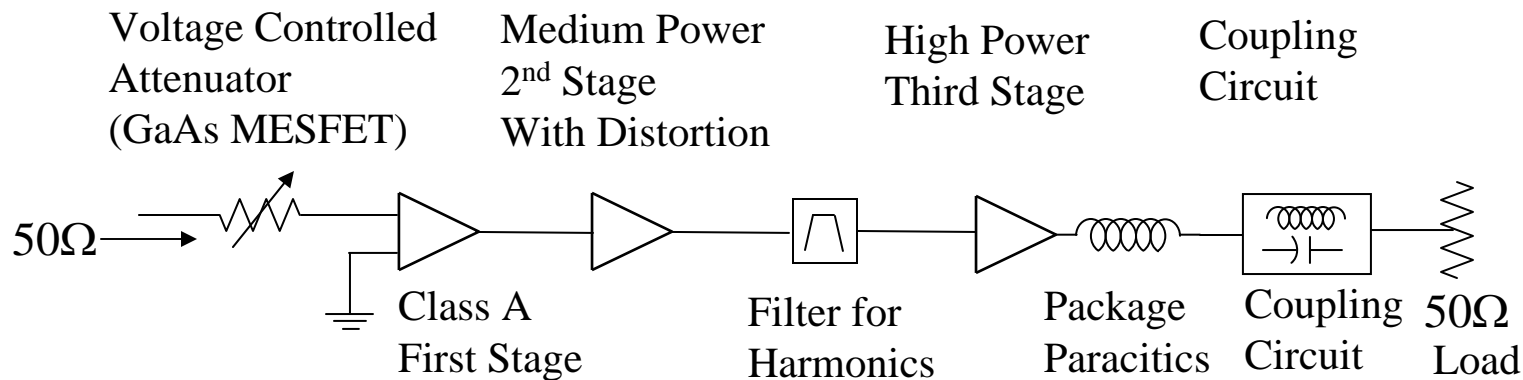
## Power Amplifier for GSM Handset, Three Stages with Power Control




### Key Questions:

- Q. Is the inter-stage band-pass filter necessary?  
A. Yes. The distortion requirements are severe. Desired efficiency cannot be met without some compression, even on the second stage.
- Q. Why not include output coupling circuit inside package?  
A. Only low Q inductors are obtainable on-chip, which affects efficiency.
- Q. Why not a 2 or 3 Volt supply?  
A. Impedance level is so low ( $< 3 \Omega$ ) that package inductance and Q still present problems.


## Effect of PA Clipping on Phase Error

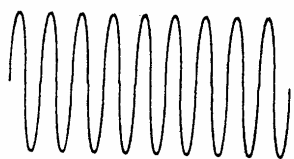


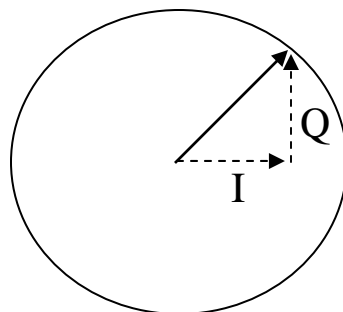
Ideal GSM (GFSK) Signal  
Has No AM (Flat Envelope)




Signal Vector Only

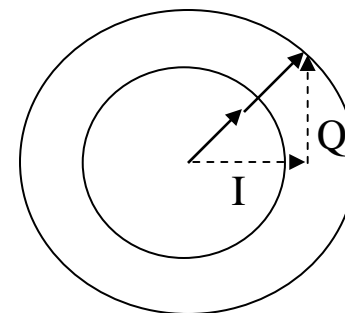

Clipping Causes No  
Change in Phase

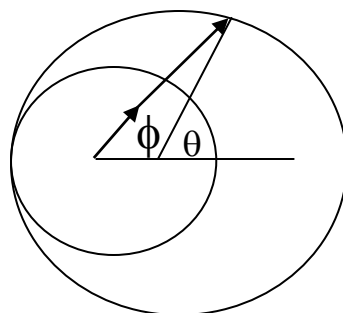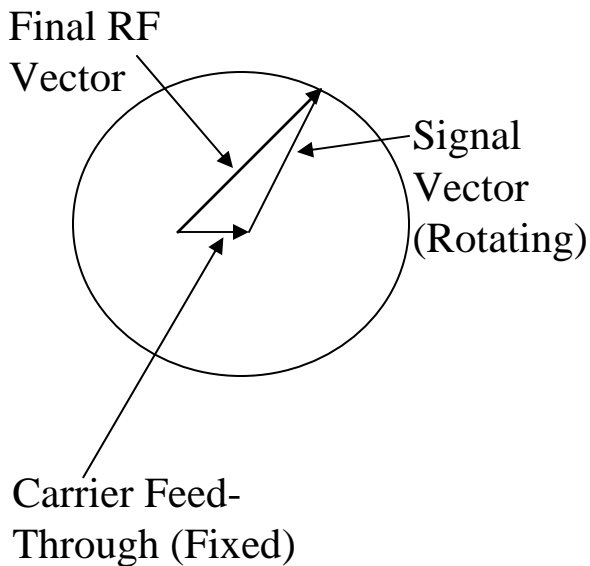

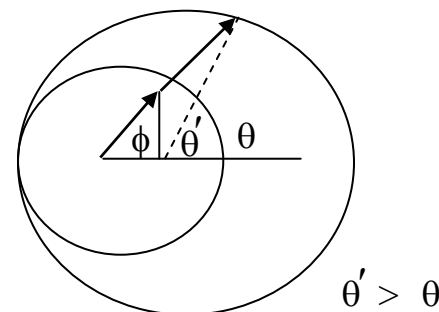
Clipping Cuts the  
Final RF Vector to a  
Constant Amplitude




Crossover Phase ( $\phi$ ) is Unaffected  
But Signal Phase ( $\theta$ ) is Modified

How to relax power dissipation across the transistor?

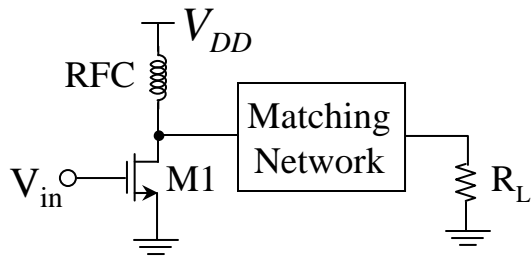One solution to alleviate this situation follows:



(i)

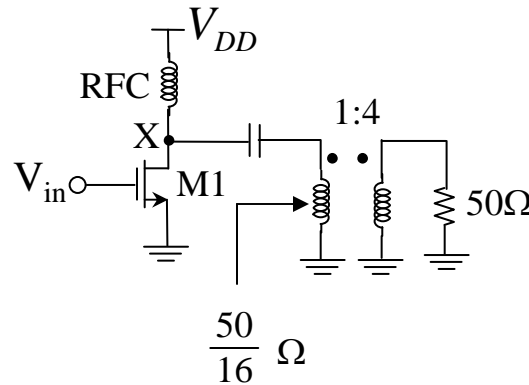

(ii)

(i) Matching network as voltage amplifier, (ii) use of a transformer as a matching network.

In general, for practical PA designs it is required matching networks to increase (and distribute) power gain.

## CLASS A AMPLIFIERS

$$i_D = I_{DC} + i_{RF} \sin \omega_o t$$

$$v_{o,RF} = -i_{RF} R \sin_o t$$

$$P_{RF} = \frac{i_{RF}^2 R}{2}$$

$$P_{RF} = \frac{v_{o,RF}^2}{2R}$$

$$P_{sup ply} = \frac{v_{oi,RF} V_{DD}}{R}$$

Thus, the power efficiency for a class A amplifier yields:

$$\eta_A = \frac{v_{o,RF}}{2V_{DD}}$$

Observe that in order to keep the transistor in saturation,  $v_{DS} > V_{DSAT} = V_{GS} - V_T$  which becomes

$$V_{DST} = \frac{I_D + \sqrt{I_D^2 + 2kI_D L^2 E_{SAT}^2}}{kLE_{SAT}} \quad ; \quad |v_{o,RF}| \leq |V_{DD} - V_{DSAT}|$$

where

$$k = \mu_o C_{ox} \frac{W}{L}, \quad I_D = \frac{k}{2} \frac{(V_{GS} - V_T)^2}{1 + \theta} \quad ; \quad \theta = \frac{V_{GS} - V_t}{LE_{SAT}}$$

$E_{SAT}$  is the field strength in V/m at which the carrier has reached velocity saturation. Furthermore, remember that:

$$f_T \cong \frac{g_m}{2\pi C_{gs}} = \begin{cases} \frac{3}{4} \frac{\mu(V_{GS} - V_T)}{L^2} & \text{for long channel} \\ \frac{1}{4\pi} \frac{\mu E_{SAT}}{L} & \text{for short channel} \end{cases}$$



Similarly for the BJT

$$f_{T,BIP} \cong \frac{1}{2\pi\tau_F} = \begin{cases} \frac{\mu kT}{\pi q \omega_B^2} & , \text{ low - level injection} \\ \frac{\mu E_{SAT}}{4\pi\omega_B} & , \text{ velocity saturation} \end{cases}$$

Typical values are

$$E_{SAT} \cong 4 \times 10^6 \text{ v/m} , \mu_{channel} = 1.5 \times 10^{-2} \text{ m}^2 / \text{V}_S , \mu_{BULK} = 5.5 \times 10^{-2} \text{ m}^2 / \text{V}_S$$

$$f_{T,NMOS} \sim 20 - 25 \text{ GHz} , 0.25\mu_m , V_{GS} - V_t = 0.8V$$

$$f_{T,BJT} \sim 30 \text{ GHz} , \omega_B = 0.05\mu_m , V_{be} = 0.8V$$

Example. Assume  $V_{DD}=3.V$  and  $V_{DSAT}=0.42$

$$\eta_A = \frac{v_{o,RF}}{2V_{DD}} = \frac{3.3 - 0.5}{2 \times 3.3} = 0.42$$

$$A_V = -g_m R_{eq}$$

$$G_A = g_m^2 R_{eg} R_s$$

$R_s$  is the source resistance, and  $R_{eg} = \frac{v_{o,RF}^2}{2P_{LOAD}}$ . Typically  $G \sim 10\text{dB}$ , then the PAE is at least 90% of the power efficiency.

Let us now explore the output 1-dB compression point.

Recall that

$$g_m = \frac{\mu C_{ox} W}{L} (V_{GS} - V_T) \frac{1 + 0.5\theta}{(1 + \theta)^2}$$

Then

$$\frac{G_A}{R_{eq}^2} P_{1-dB} = |g_m|^2 R_s P_{1-dB} / R_{eq}$$

$$P_{1-dB} = \frac{2}{9} \frac{|a_1|}{|a_3|} \frac{10^{0.05} - 1}{R_s}$$

$a_1$  and  $a_3$  are the coefficients of the non-linear polynomial of  $g_m$ .

Then the output compression point becomes:

$$|a_1|^2 \frac{R_s P_{1-dB}}{R_{eq}} = 10 \log \left[ 4.3384 \times 10^2 \frac{(1 + 0.5\theta)^3}{\theta} P_{load} \right]$$

Example.-  $V_{DD} = 3.3V$ ,  $V_{DSAT} = 0.5$  (in a  $0.25\mu_m$  CMOS technology), and a transmit power of 600 mW. (27.8dBm).

Then

$$10 \log \left[ 4.3384 \times 10^2 \frac{(1 + 0.5\theta)^3}{\theta} P_{load} \right]_{\substack{P_{load}=0.6 \\ \theta=0.5}} = 30.1dBm$$

Note that 30.1dBm is about 2.3dB higher than the  $P_{o-1dB}$

$$\eta_A = \frac{v_{o,RF}}{2V_{DD}} = \frac{V_{DD} - V_{DSAT}}{2V_{DD}} = \frac{3.3 - 0.5}{2 \times 3.3} = 42\%$$

$$R_{eq} = \frac{(V_{DD} - V_{DSAT})^2}{2P_{load}} = \frac{(3.3 - 0.5)^2}{2 \times 0.6} = 6.5\Omega$$

The corresponding bias current is

$$I_D = \frac{V_{DD} - V_{DSAT}}{R_{eq}} = \frac{3.3 - 0.5}{6.5} = 4.30.8mA$$

From the expression of  $I_D$  one can determine  $W$

$$W = \frac{2LI(1 + \theta)}{\mu C_{ox} (V_{GS} - V_t)^2} = 2I_D \frac{LE_{SAT} + V_{DSAT}}{\mu C_{ox} V_{DSAT}^2 E_{SAT}}$$

$$W = 2 \times 0.4308 \frac{0.25 \times 10^{-6} \cdot 4 \times 10^6 + 0.5}{0.015 \cdot 0.0035 (0.5)^2 4 \times 10^6} = 24.6mm$$

Its corresponding transconductance becomes:


$$g_m = \sqrt{\frac{2\mu C_{ox} W I_D}{L}} \frac{1 + 0.5\theta}{(1 + \theta)^{1.5}} = \sqrt{\frac{2 \times 0.015 \times 0.0035 \times 0.0246 \times 0.4308}{0.25 \times 10^{-6}}} \frac{1 + 0.5^2}{(1 + 0.5)^{3/2}}$$

$$g_m = 1.44 \text{ } \bar{U}$$






$$G = g_m^2 R_{eq} R_s \Big|_{R_s=50} = 1.44 \times 6.5 \times 50 = 2.8.3dB \Rightarrow P_{in,2dB} = 1.8dB$$

The efficiency for class-A power amplifier is rather modest, thus other efficient amplifier are investigated.

45% <

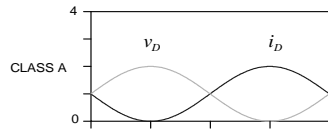

78% <

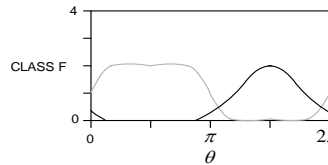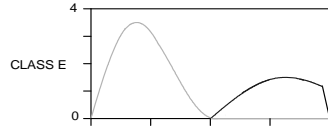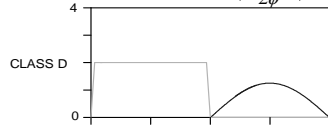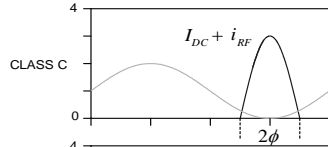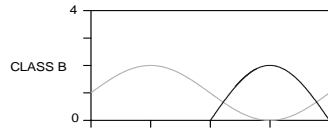

Waveforms for Ideal PAs.

$$\eta_A = \frac{v_{o,RF}}{2V_{DD}}$$

$$\eta_B = \frac{\pi v_{o,RF}}{4V_{DD}} = 0.5\pi\eta_A \quad , \quad G_B = \frac{G_A}{4} \quad \text{Distortion } \uparrow$$

$$\eta_C = \frac{2\phi - \sin 2\phi}{4(\sin \phi - \phi \cos \phi)} \quad \text{Efficiency } \uparrow$$


$$\eta_{D, IDEAL} = 100\% \quad \text{with ideal switches}$$

$$\eta_{E, IDEAL} = 100\% \quad , \quad \max P_{LOAD} = \frac{2}{1 + \pi^2/4} \frac{V_{DD}^2}{R} \cong 0.577 \frac{V_{DD}^2}{R}$$


$$\eta_{F, IDEAL} = 100\%$$

Observe that class C, D, E and F amplifiers are essentially constant-envelope amplifiers.


# CLASS-B POWER AMPLIFIER

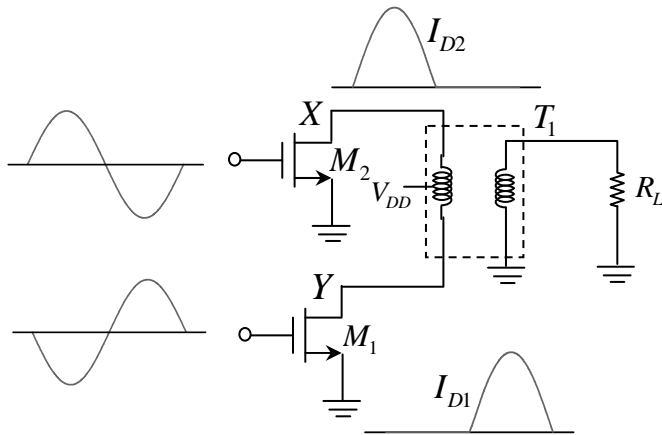

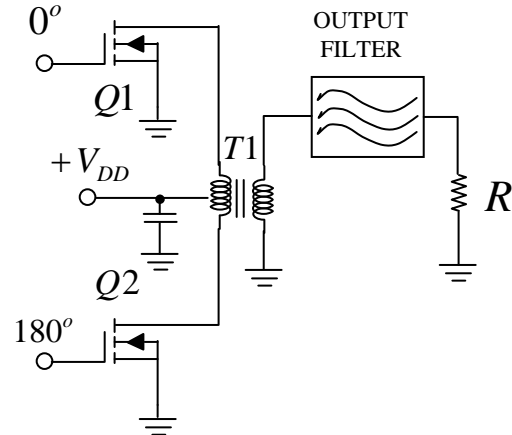Class B stage using a transformer  
For Broadband Operations.



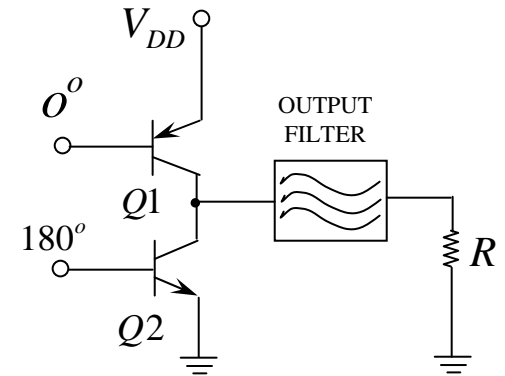Transformer-coupled push-pull  
PA. For audio applications.



Complementary PA.

- 50% duty cycle

$$i = \frac{2}{T} \int_0^{T/2} i_{RF} \sin \omega_o t \times \sin \omega_o t dt = \frac{i_{RF}}{2}; \max i_{RF} = \frac{2V_{DD}}{R}$$

$$v_{o,RF} \cong \frac{i_{RF}}{2} R \sin \omega_o t$$

$$P_o = \frac{v_{o,RF}^2}{2R}; P_{o,max} = \frac{V_{DD}^2}{2R}$$

$$i_{D,average} = \frac{1}{T} \int_0^{T/2} \frac{2V_{DD}}{R} \sin \omega_o t dt = \frac{2V_{DD}}{\pi R}$$

$$P_{DC} = \frac{2V_{DD}^2}{\pi R}$$


thus

$$\max \eta_B = \frac{P_{o,max}}{P_{DC}} = \frac{\pi}{4} \cong 0.785$$


- Class B sacrifices linearity but gains in terms of efficiency.
- For practical implementations

$$I_D \cong \frac{i_{peak}}{10}$$


# CLASS E AMPLIFIER

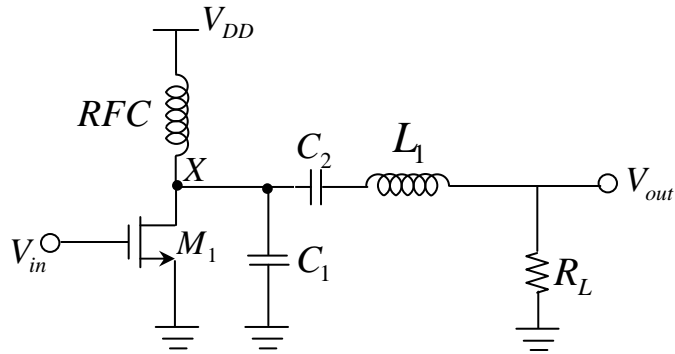

Class E stage.

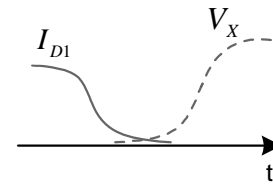


(a)

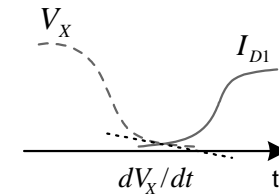


(b)

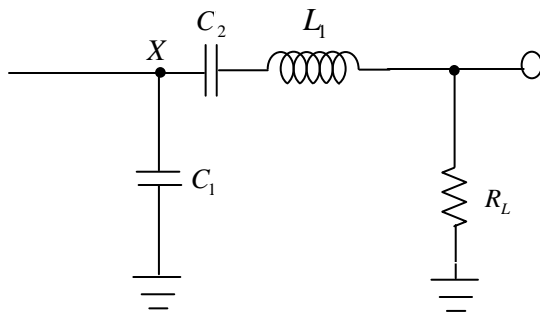Voltage and current waveforms in a class E stage.





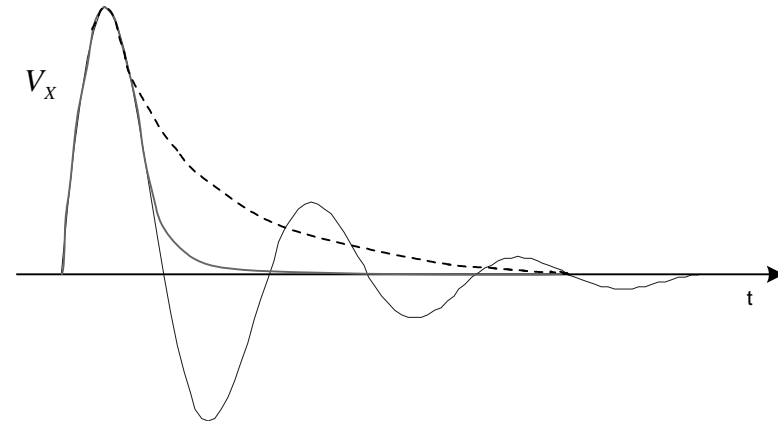Response of class E stage when the transistor turns off.





# BASIC RF SWITCHING AMPLIFIER

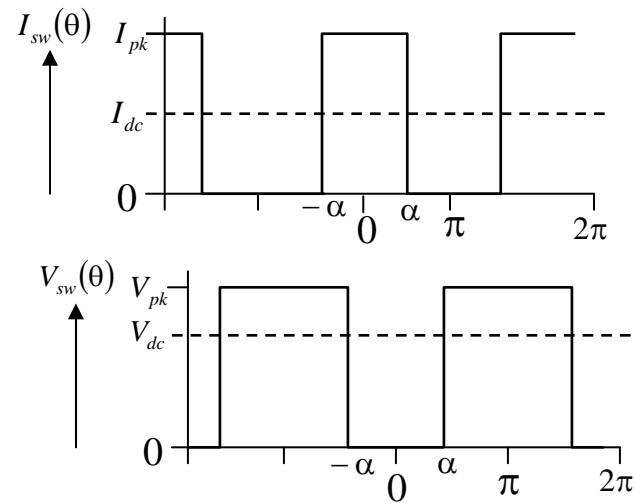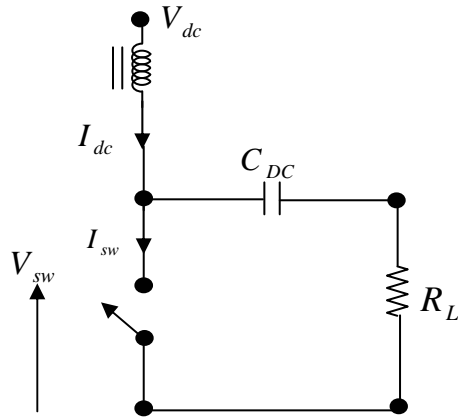

Basic RF switching amplifier.

Basic RF switch waveforms.

$$V_{dc} = \frac{1}{2\pi} \int_{-\pi}^{\pi} v_{sw}(\theta) d\theta$$

$$= \frac{1}{\pi} \int_{\alpha}^{\pi} V_{pk} d\theta \quad (1)$$

$$\frac{V_{dc}}{V_{pk}} = \frac{(\pi - \alpha)}{\pi}$$

The voltage waveform can be considered to be an alternating voltage with zero mean value if it is offset by  $V_{dc}$ . So the peak-to-peak current swing will be  $V_{pk}/R_L$  and

$$I_{pk} = V_{pk} / R_L \quad (2)$$

$$I_{dc} = \frac{\alpha}{\pi} I_{pk} \quad (3)$$

The fundamental even Fourier coefficient of current,  $I_p$  is given by

$$I_1 = \frac{1}{\pi} \int_{-\pi}^{\pi} i_{sw}(\theta) \cos(\theta) d\theta \quad (4)$$

where

$$\begin{aligned} i_{sw}(\theta) &= I_{pk}, -\alpha < \theta < \alpha \\ &= 0, -\pi < \theta < -\alpha, \alpha < \theta < \pi \\ &= \frac{2}{\pi} \int_0^{\alpha} I_{pk} \cos(\theta) d\theta \\ \frac{I_1}{I_{pk}} &= \frac{2 \sin(\alpha)}{\pi} \end{aligned} \quad (5)$$

Similarly, the fundamental Fourier coefficient for the voltage waveform is


$$\frac{V_1}{V_{pk}} = \frac{2 \sin(\alpha)}{\pi} \quad (6)$$

Combining (6.1) through (6.6), the RF power,  $P_{rf}$  can be expressed in terms of the dc supply terms,  $V_{dc}$  and  $I_{dc}$ .

$$\begin{aligned} \frac{V_1}{V_{dc}} &= \frac{2 \sin \alpha}{\pi - \alpha} \\ \frac{I_1}{I_{dc}} &= \frac{2 \sin \alpha}{\alpha} \\ P_{rf} &= V_{dc} I_{dc} \frac{2 \sin^2 \alpha}{\alpha(\pi - \alpha)} \end{aligned} \quad (7)$$

So that the output efficiency,  $\eta$ , is given by
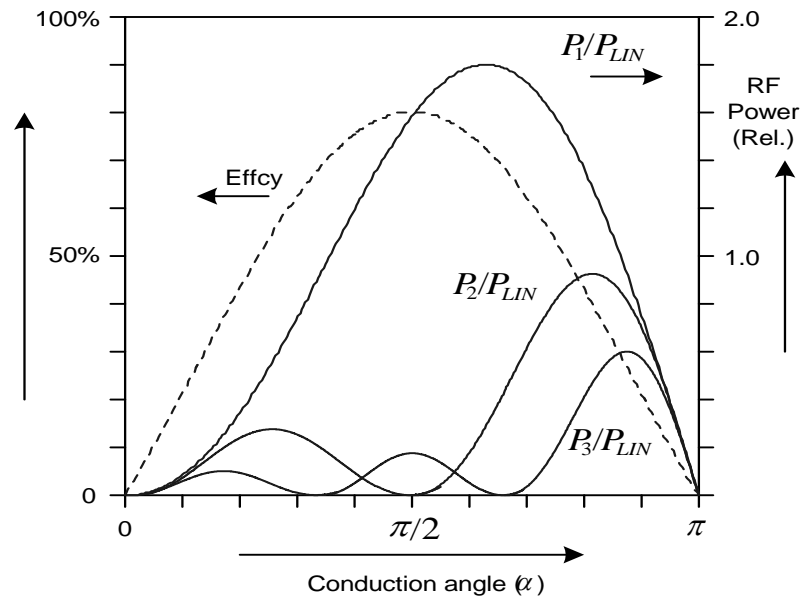
$$\eta = \frac{2 \sin^2 \alpha}{\alpha(\pi - \alpha)} \quad (8)$$



RF output power and efficiency of basic RF switch. Fundamental and harmonic power are expressed relative to  $P_{lin}$  the class A RF power having the same peak RF current at the same dc supply voltage.

and defining the linear power,  $P_{lin}$  as

$$P_{lin} = \frac{V_{dc} I_{pk}}{4} \quad (9)$$

the relative power is

$$\frac{P_1}{P_{lin}} = \frac{8 \sin^2 \alpha}{\pi(\pi - \alpha)} \quad (10)$$


# TUNED RF SWITCHING

$$\frac{I_1}{I_{pk}} = \frac{2 \sin(\alpha)}{\pi}$$


$$\frac{I_{dc}}{I_{pk}} = \frac{\alpha}{\pi}$$

The sinusoidal voltage gives the simple relationship


$$V_1 = V_{dc}$$

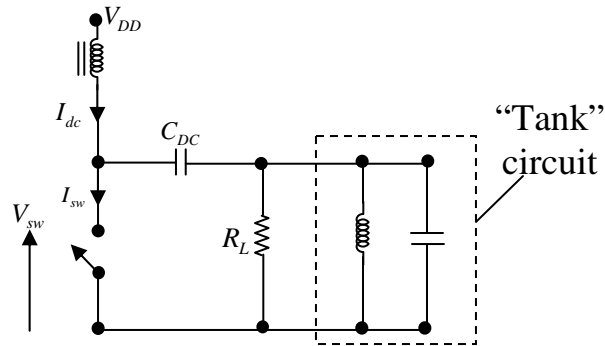

Tuned RF switching amplifier.

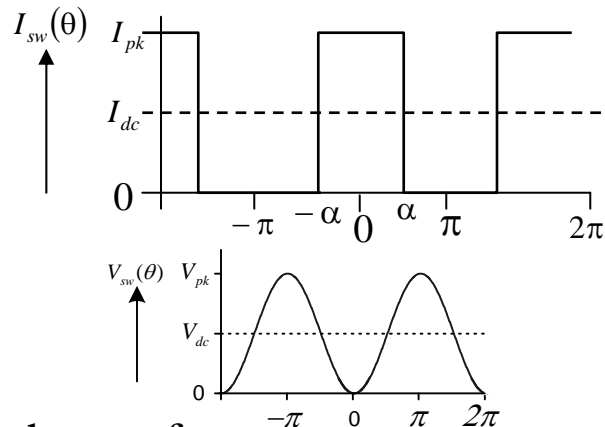

Tuned switch waveforms.

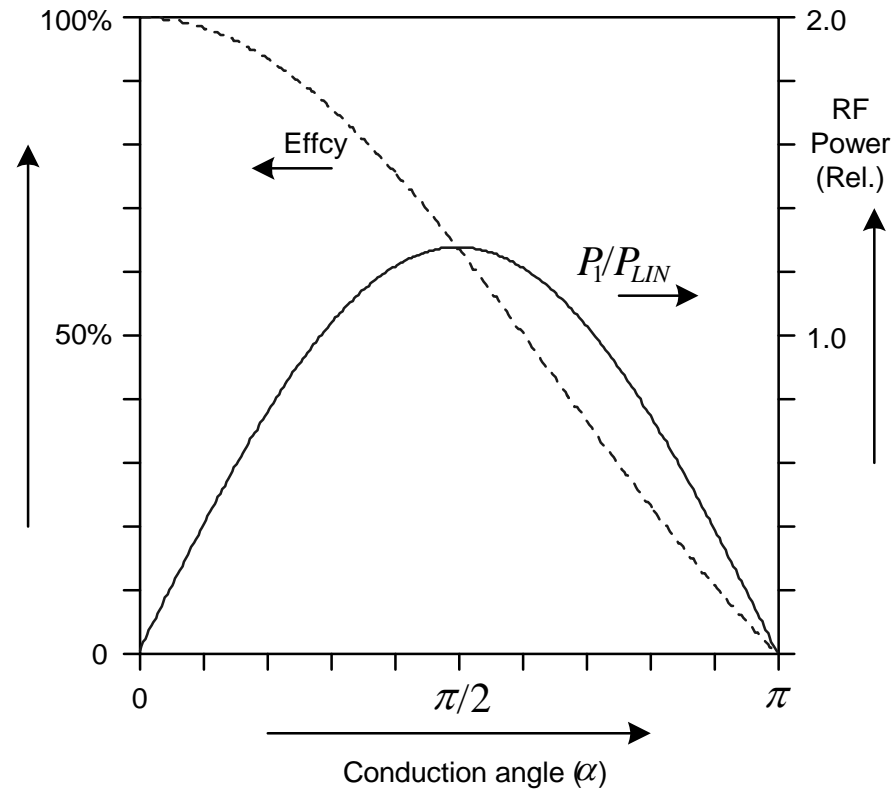

RF output power and efficiency of basic RF switch with harmonic short.

Thus the fundamental RF power is

$$P_1 = I_{dc} V_{dc} \frac{\sin(\alpha)}{\alpha} \quad (11)$$

Yielding this output efficiency:

$$\eta = \frac{\sin(\alpha)}{\alpha} \quad (12)$$

The relative power can be determined as before, by expressing  $P_1$  (in 11), in terms of the peak current  $I_{pk}$  using the relationship of (3):

$$P_1 = I_{pk} V_{dc} \frac{\sin(\alpha)}{\pi}$$

So the ratio of fundamental RF power to  $P_{lin}$  is becomes

$$\frac{P_1}{P_{lin}} = I_{pk} V_{dc} \frac{4 \sin(\alpha)}{\pi} \left( P_{lin} = \frac{I_{pk} V_{dc}}{4} \right) \quad (13)$$