



---

# Introduction to RF VCO Design

---

Sung Tae Moon

Nov. 2004

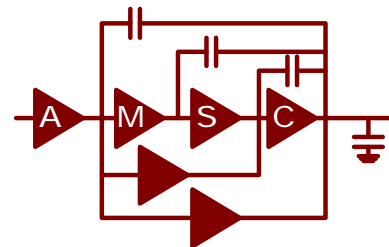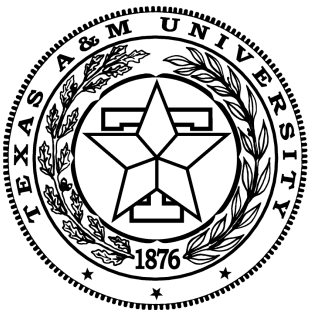

*Analog and Mixed-Signal Center*


---

# Contents

- Introduction
- VCO design procedure
- Quadrature generators
- Measurement
- Inductor measurement using microprobe
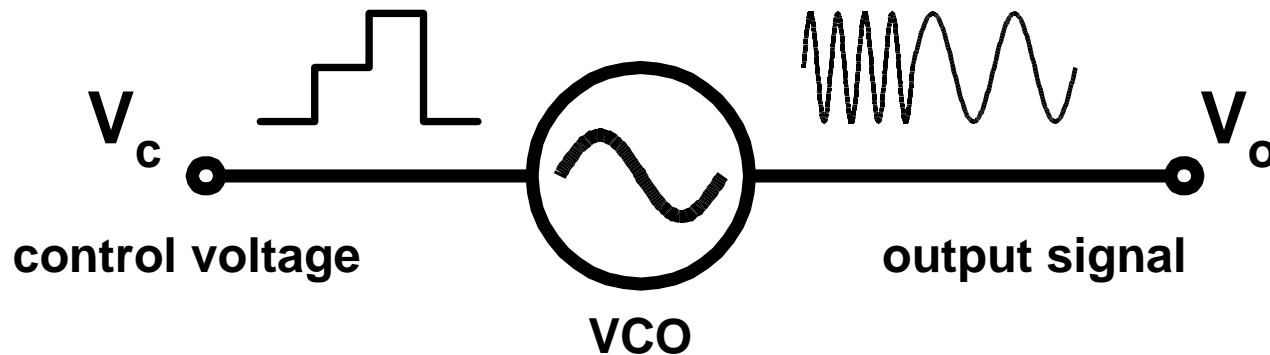
# Introduction to VCO

- VCO stands for **V**oltage **C**ontrolled **O**scillator.
- VCO is an **O**scillator of which frequency can be **C**ontrolled by external **V**oltage stimulus.




---

# VCO in Frequency Synthesizer

- One of major applications for VCO is a frequency synthesizer.
- Frequency synthesizer provides sinusoidal/pulse signals at **predetermined frequencies that is precisely controllable** by digital words.
- Frequency synthesizer is a core building block of any system that has to work at multiple frequencies such as wireless communication transceivers.
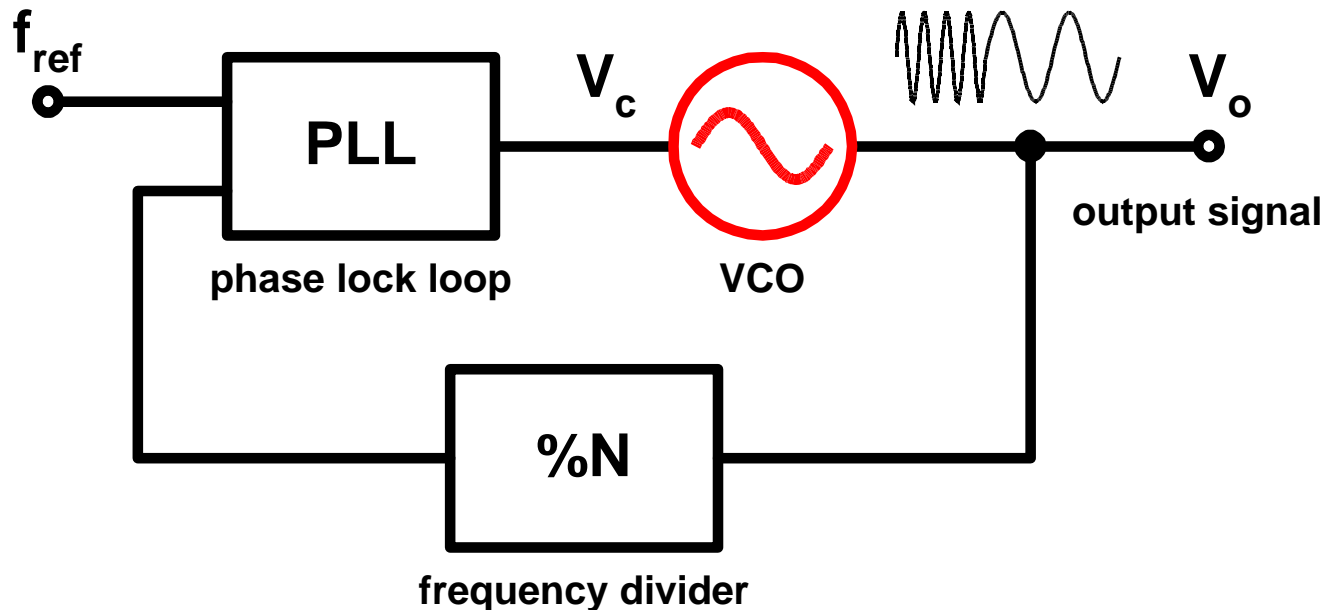
# VCO in Frequency Synthesizer cont.

- Frequency synthesizer usually consists of a VCO, a PLL and a frequency divider.



---

# Requirements for VCO Design

- Frequency tuning range
  - Tuning range must cover the entire band of operation.
- Phase noise
  - Close to the oscillation frequency due to spontaneous jitter.
- Harmonic distortion
  - Spectral impurity of the signal
- Signal power
  - Must be high enough to drive the load.
- Power consumption

---

# VCO for Bluetooth transceiver

- Frequency tuning range : 2.402 ~ 2.479GHz
- Phase noise : -128dBc/Hz@3MHz
- Harmonic distortion : less than 20dB
- Signal power : more 0dBm
- Power consumption : less than 8mA

---


# Procedure 1. Specification Study

- Relatively low tuning range : 3.3%
- High frequency of oscillation : >2.4GHz
- Very high phase noise requirement

→ LC tuned oscillator is most suitable



# Procedure 2. LC Tuned Oscillator

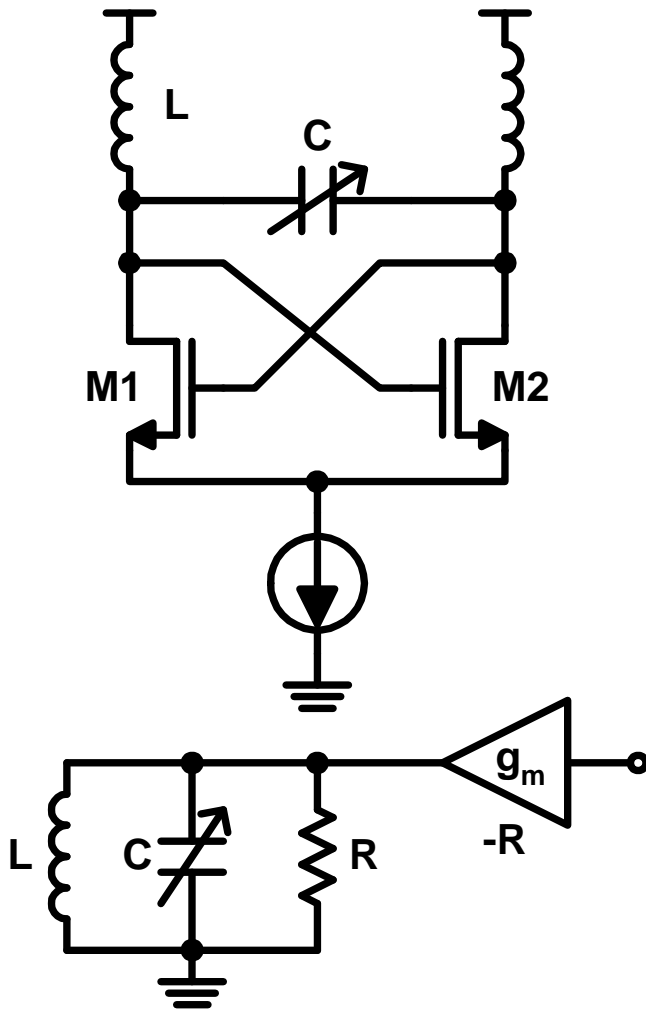


- Oscillation frequency is tuned by resonant frequency of LC tank.

$$\omega_o \approx \frac{1}{\sqrt{LC}}$$

- Cross-coupled transistors work as a negative resistance that sustains oscillation by compensating loss in the LC tank.
- Frequency is controlled by varying the capacitance of the tank.

# Procedure 3. On-chip Inductor


$$Q \approx \frac{wL}{R}$$

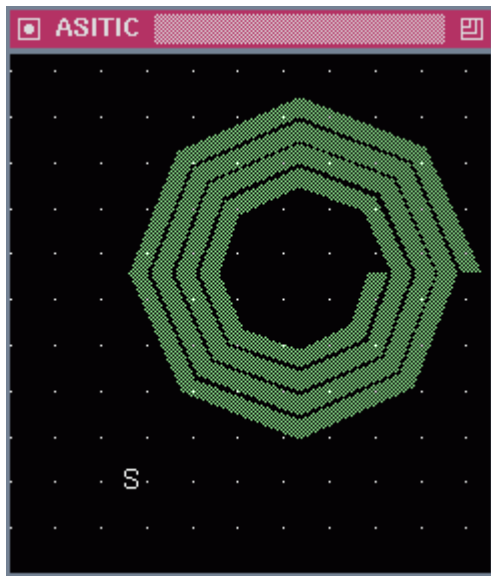

- Specifications

- $L = 2\text{nH}$

- $Q > 5$

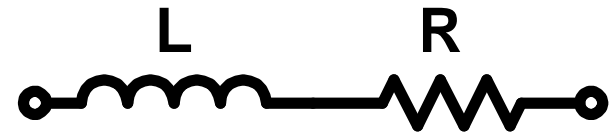

- On-chip spiral inductor must be simulated with EM(Electro-Magnetic) simulator such as ASITIC.

← ASITIC EM simulator

# Inductance and Q

$$L \propto \text{Metal area} / \text{Total area}$$


$$Q \propto \text{Metal width}$$

$$f_{self\_resonant} \propto 1 / \text{Metal area}$$


- Q can be improved by increasing metal width.
- To keep L same, total area has to be increased.
- Increased metal area reduces self resonant frequency
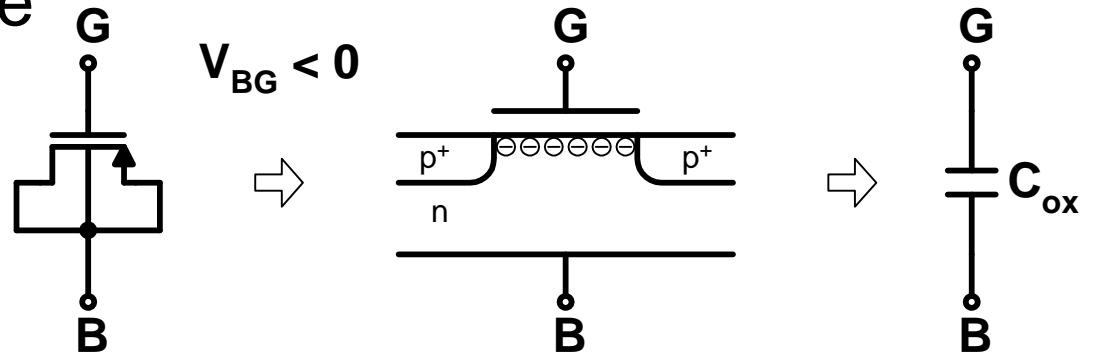
# Procedure 4. MOSFET Varactor

- Back gate controlled PMOS varactor
- Accumulation mode





- Depletion mode

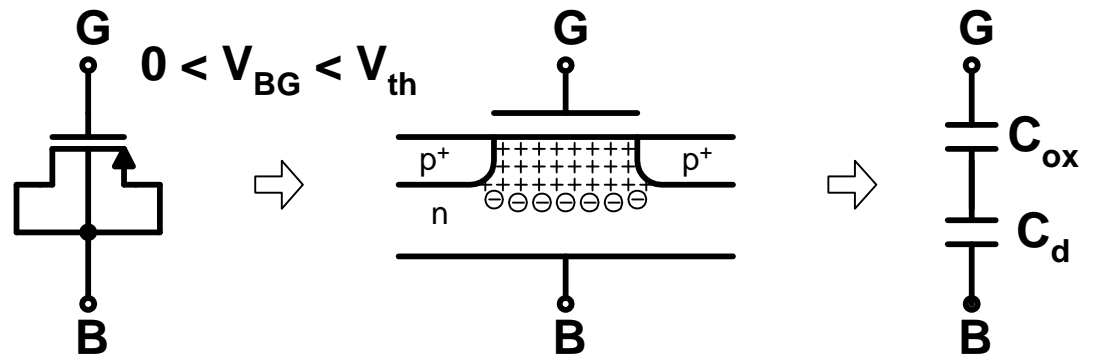


# Procedure 4. MOSFET Varactor (cont.)

## ■ Inversion mode

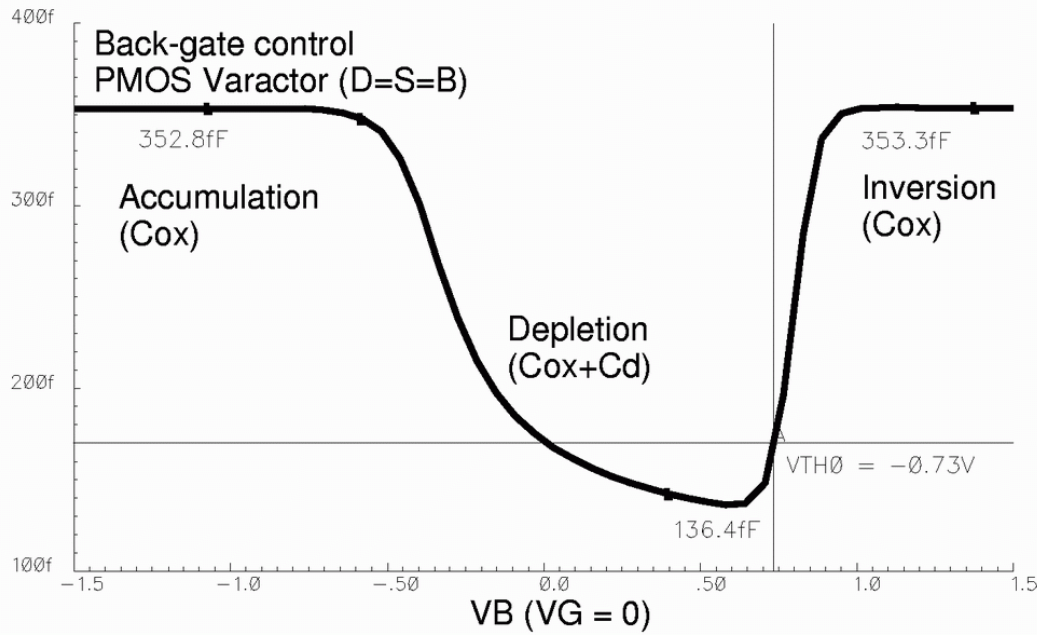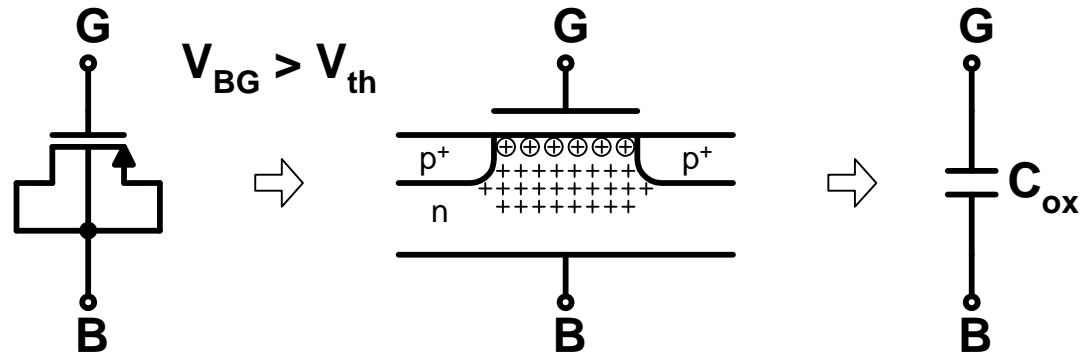


# Procedure 4. MOSFET Varactor (cont.)

- Accumulation/Depletion only varactor

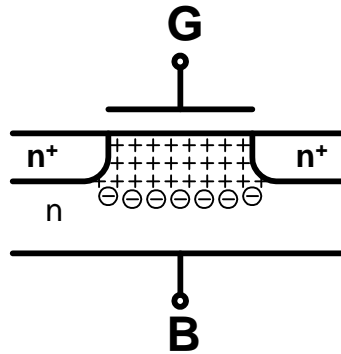

- Inversion only varactor

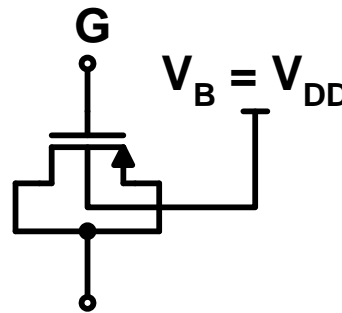


---

# Procedure 5. Active Elements

- $g_m$  of the cross-coupled MOS pairs must be high enough to compensate the loss of the tank.
- It is a good idea to have plenty of margin in design.
- The length of the transistors must be minimum in order to minimize parasitics.

# Procedure 5. Active Elements (cont.)

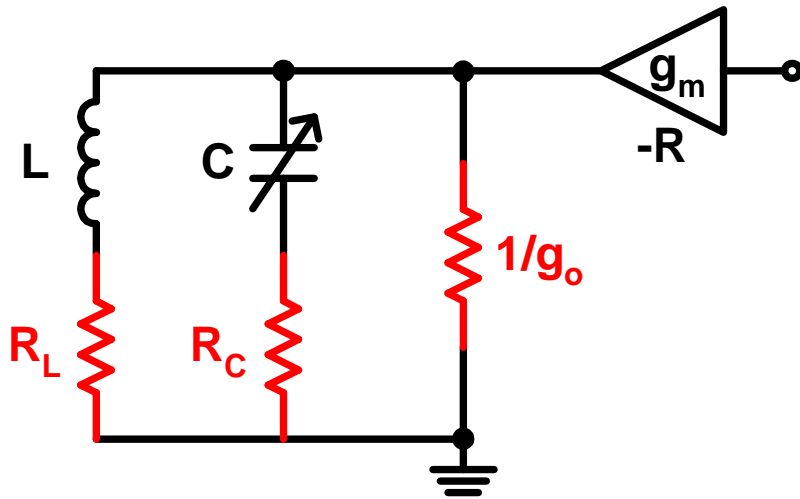

$$g_m > \alpha \left\{ g_o + \frac{1}{Q_L \omega_o L} + \frac{\omega_o C}{Q_C} \right\}$$


$$Q_L = \frac{\omega_o L}{R_L}, \quad Q_C = \frac{1}{\omega_o C R_C}$$

$$\alpha > 3$$

- Sources of the loss
  - Quality of L ( $Q_L$ )
  - Quality of C ( $Q_C$ )
  - Output impedance of the transistor. ( $g_o$ )
- Gm of the transistor must be larger than total loss.
- $\alpha$  is safety margin for starting oscillation.



# Series-parallel conversion

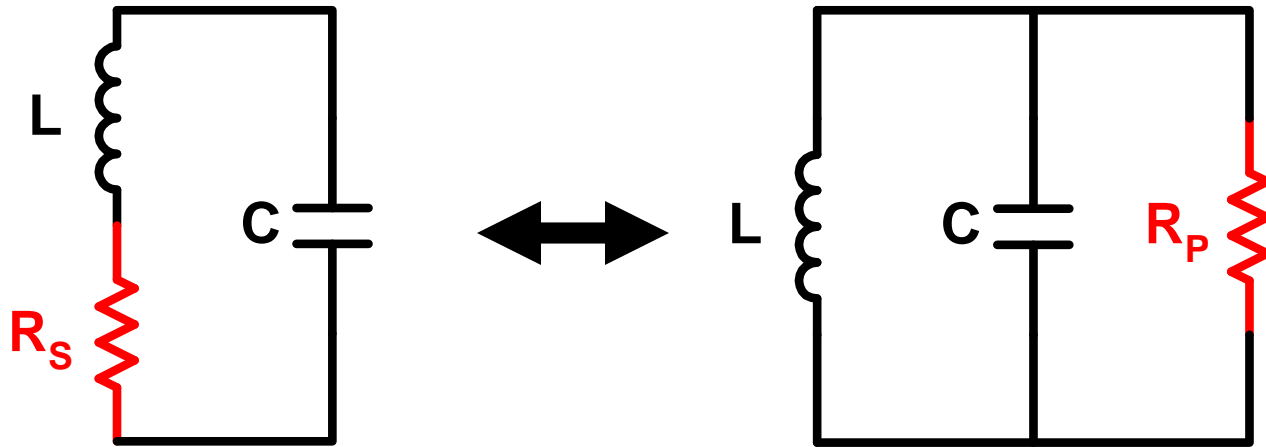

$$R_S = \frac{(\omega_o L)^2}{R_P} = \frac{R_P}{Q_L^2}$$

$$R_P = \frac{(\omega_o L)^2}{R_S} = Q_L^2 R_S$$

- Only valid close to resonant frequency

---

# Phase Noise

- Phase noise is uncertainty of center frequency of VCO output
- The spectrum looks as if it has finite power in certain frequency offset away from the center frequency
- In time domain, phase noise is also referred to as timing jitter

# Phase Noise (cont.)

- Signal amplitude

$$V_A = I_{tail} R_P = \frac{I_{tail} (\omega_o L)^2}{R_S} = I_{tail} Q_L^2 R_S$$

- Noise power

$$v_n^2 = \frac{4kT \mathbf{g} \mathbf{g}_m R_P^2}{4Q_L^2} \left( \frac{\omega_o}{\Delta \omega} \right)^2 = kT \mathbf{g} \mathbf{g}_m Q_L R_S^2 \left( \frac{\omega_o}{\Delta \omega} \right)^2$$

- Phase noise

$$PN = \frac{8v_n^2}{V_A^2} = \frac{8kT \mathbf{g} \mathbf{g}_m}{I_{tail}^2 Q_L^2} \left( \frac{\omega_o}{\Delta \omega} \right)^2$$


---

# Phase Noise (cont.)

- Signal power can be increased either by higher Q or by higher L
- Only high Q improves phase noise
- High power dissipation also improves phase noise
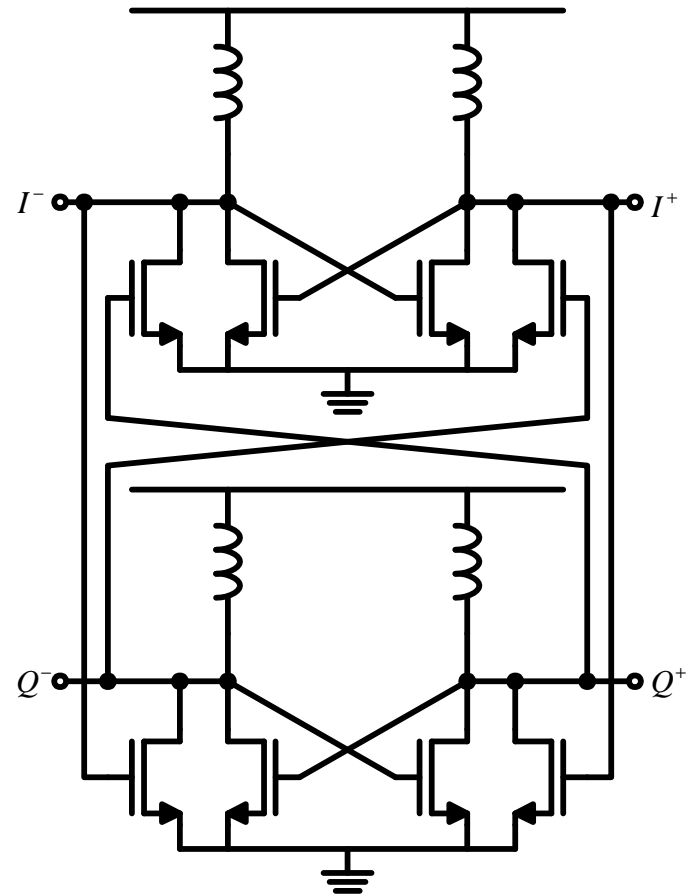
# Quadrature Signal Generation 1


- Two identical coupled oscillators
  - Immune to mismatch - the coupled oscillators synchronize to exactly the same frequency
  - Large area and power dissipation



- Lam, C.; Razavi, B. "A 2.6 GHz/5.2 GHz CMOS voltage-controlled oscillator", ISSCC, 1999, pp. 402-403
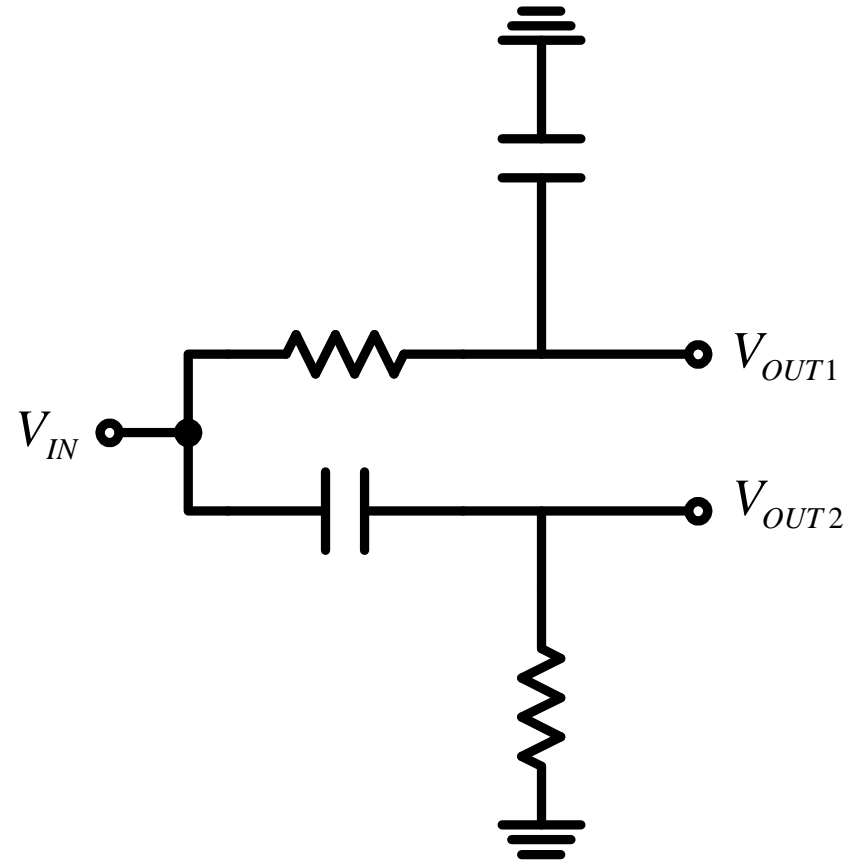
# Quadrature Signal Generation 2


- RC-CR network
  - Low power : passive element only
  - Sensitive to mismatch
  - Amplitude mismatch



- Orsatti, P.; Piazza, F.; Huang, Q., "A 20-mA-receive, 55-mA-transmit, single-chip GSM transceiver in 0.25 CMOS", JSSC, vol 34, Dec. 1999 , pp. 1869-880
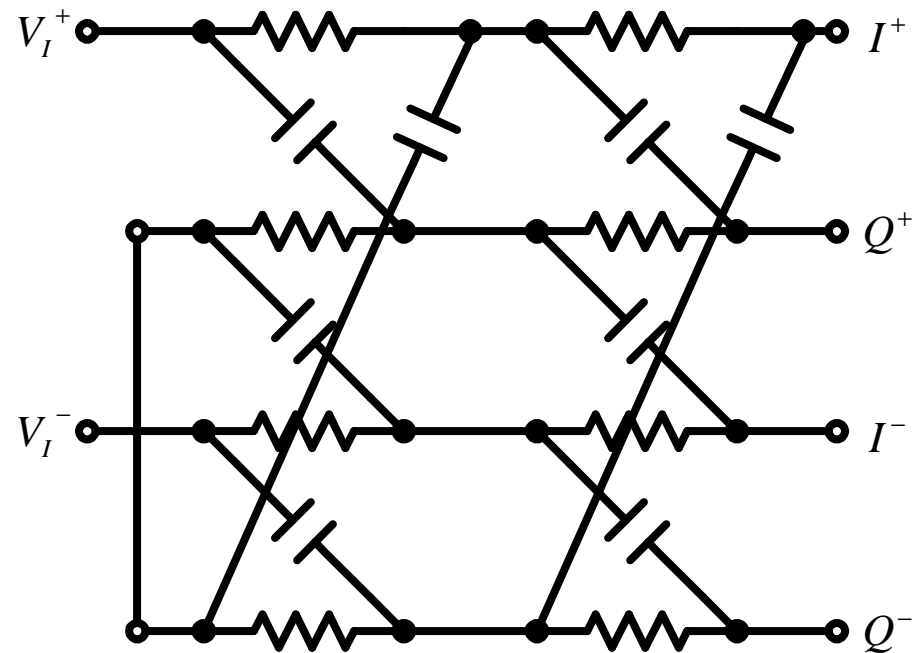
# Quadrature Signal Generation 3


- Polyphase network
  - Low power
  - Amplitude matching
  - Insertion loss



- Parssinen, A.; Jussila, J.; Ryyanen, J.; Sumanen, L.; Halonen, K.A.I., "A 2-GHz wide-band direct conversion receiver for WCDMA applications," JSSC, vol. 34, Dec. 1999, pp. 1893-903

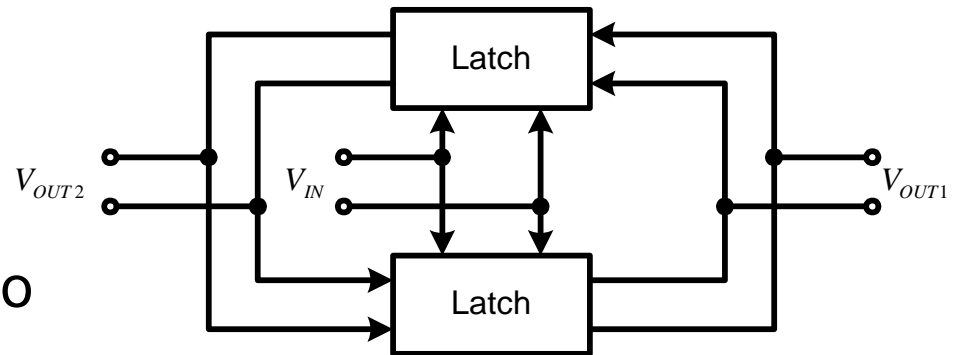
# Quadrature Signal Generation 4

- Divide-by-two circuit
  - Relatively immune to mismatch
  - Requires 2x frequency oscillation which leads to high power dissipation







# Layout of Bluetooth VCO

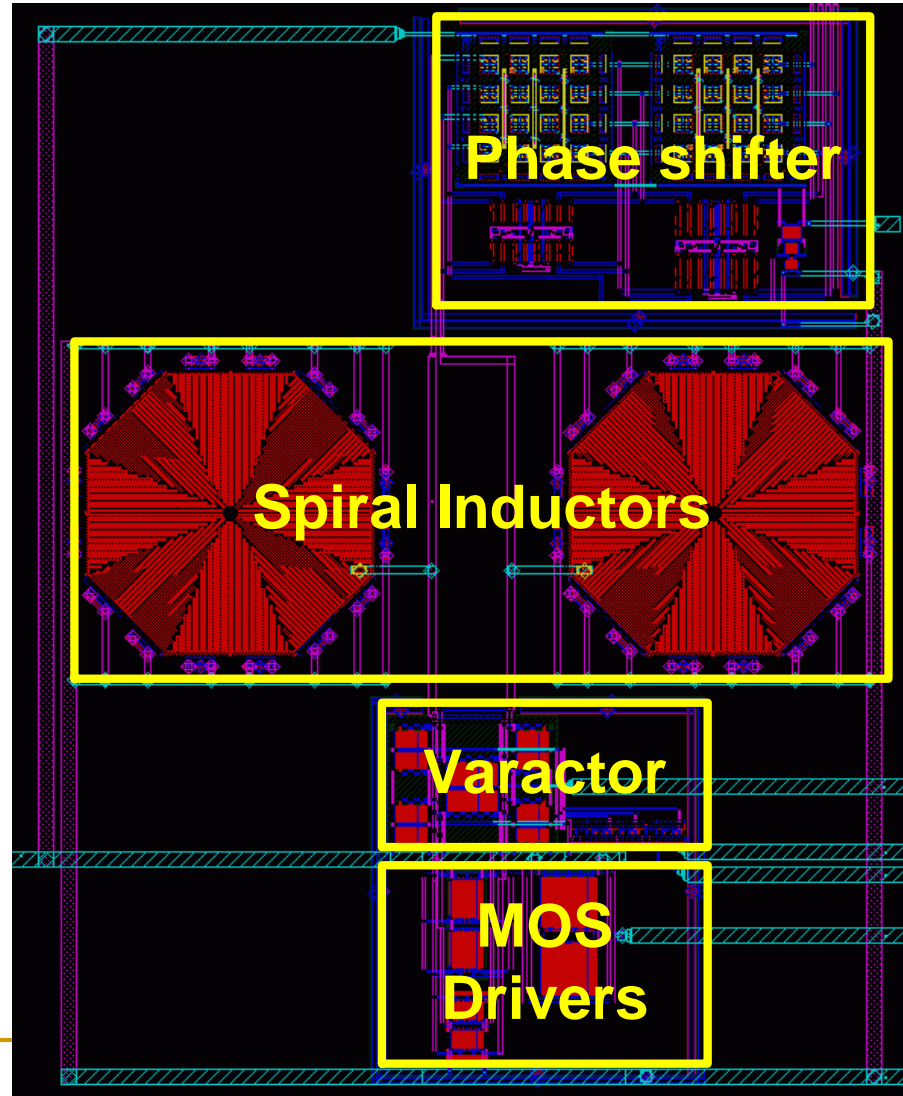


# Chip Microphotograph

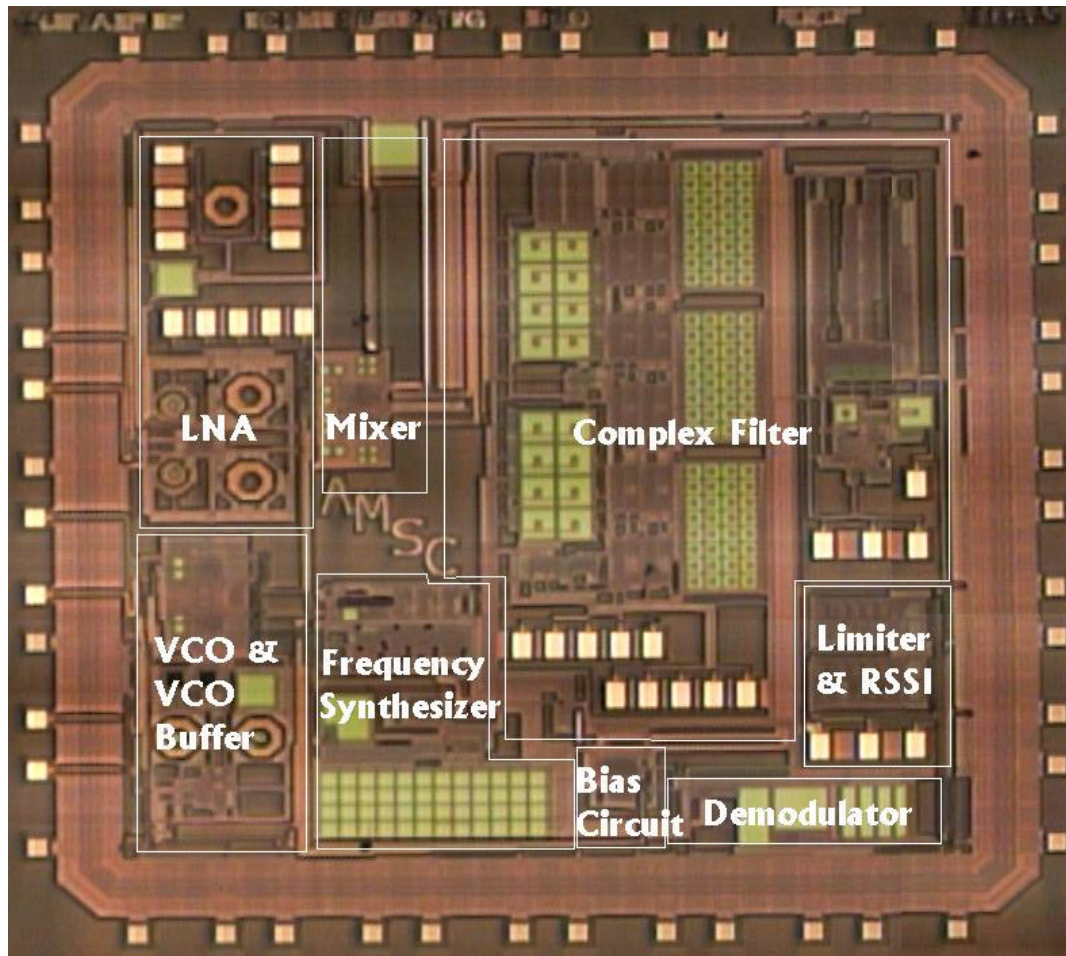


# Another Layout (for 802.11b+BT)

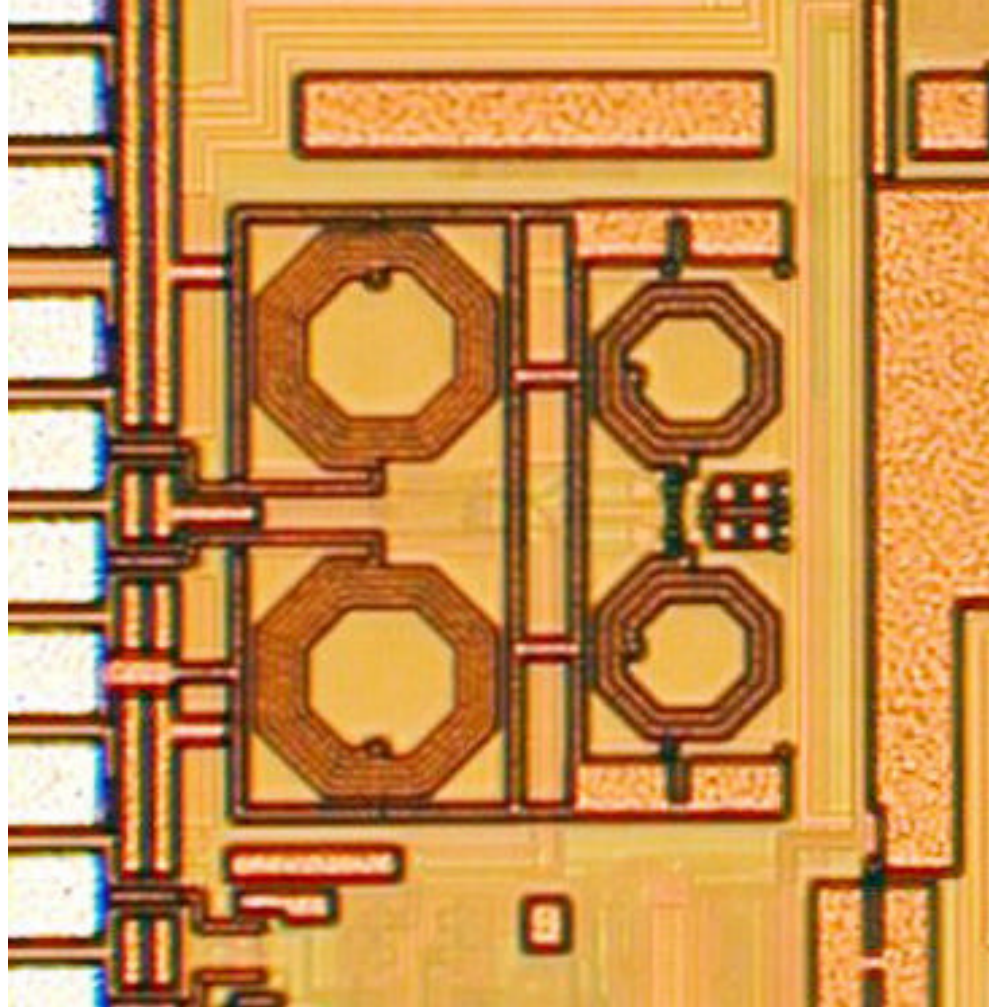

# PC Board

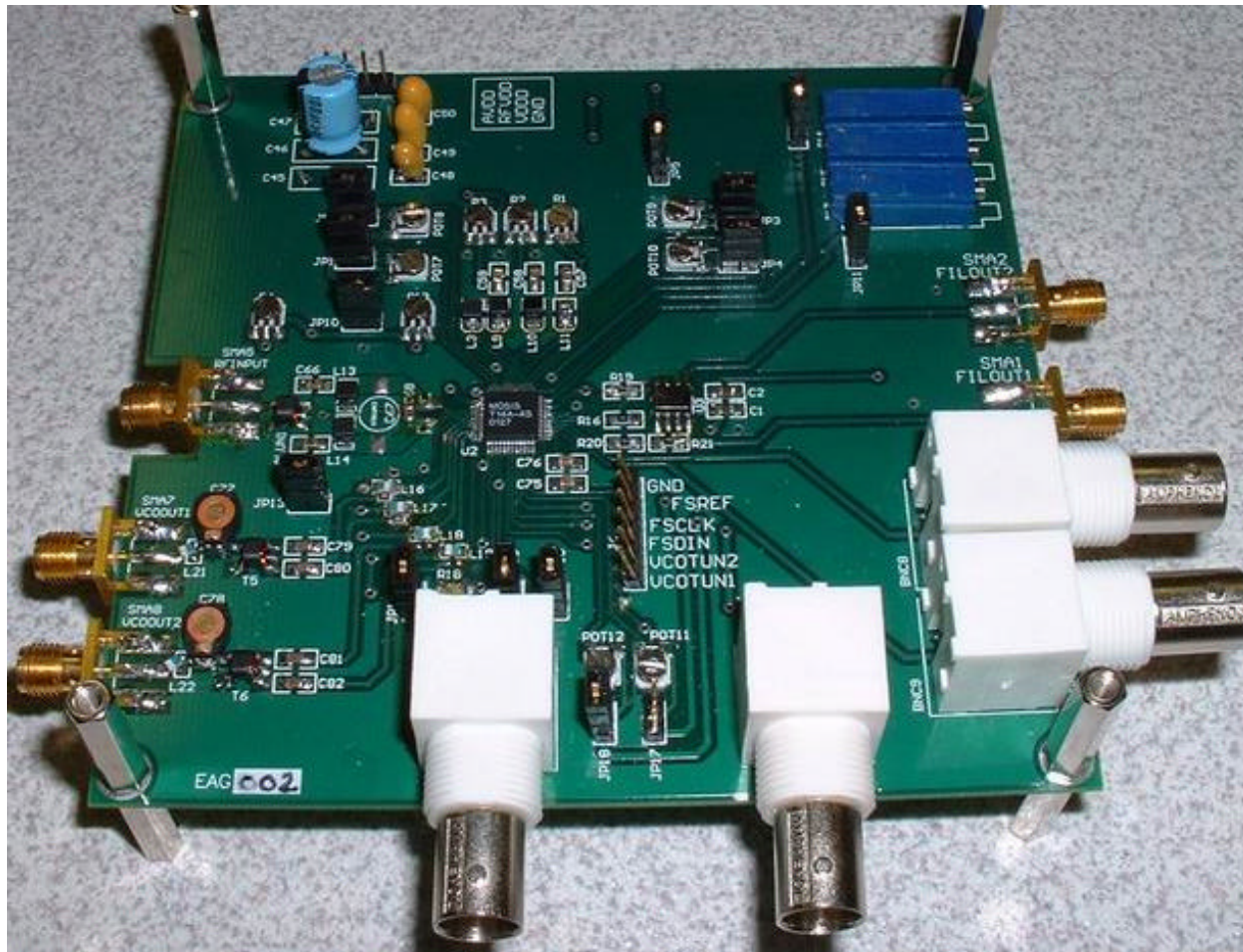

# Using Spectrum Analyzer

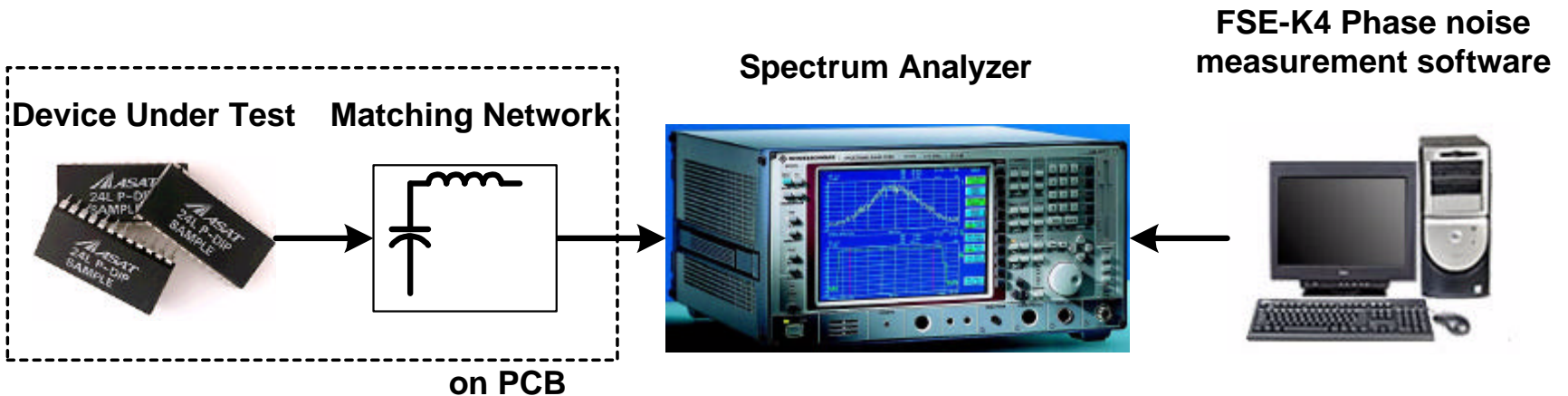

- A matching network to make the output impedance of the VCO to match  $50\Omega$  is recommended
- The phase noise measurement can be automated by using FSE-K4 software


# Testing Results

- Since the frequency of oscillation is too high for any oscilloscope available in the lab, the spectrum analyzer is the only option for testing the circuit.
- Measured parameters:
  - Frequency tuning range : 2.37 ~ 2.72GHz
  - Signal power : -12dBm
  - Phase noise : -130dBc/Hz @ 3MHz

# Testing Results


- Tuning Range

- 2.37 ~ 2.72GHz

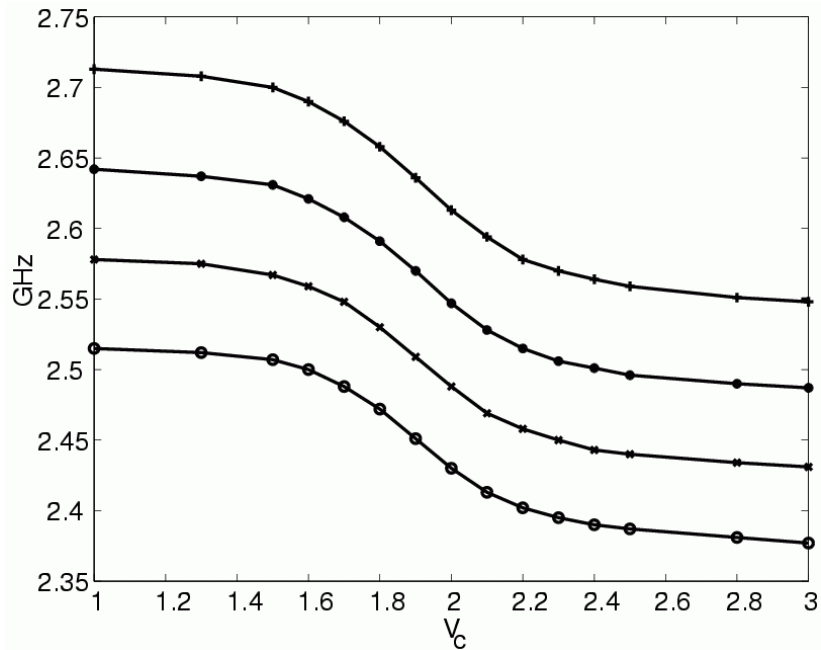


- Phase noise

- -130dBc/Hz @ 3MHz offset

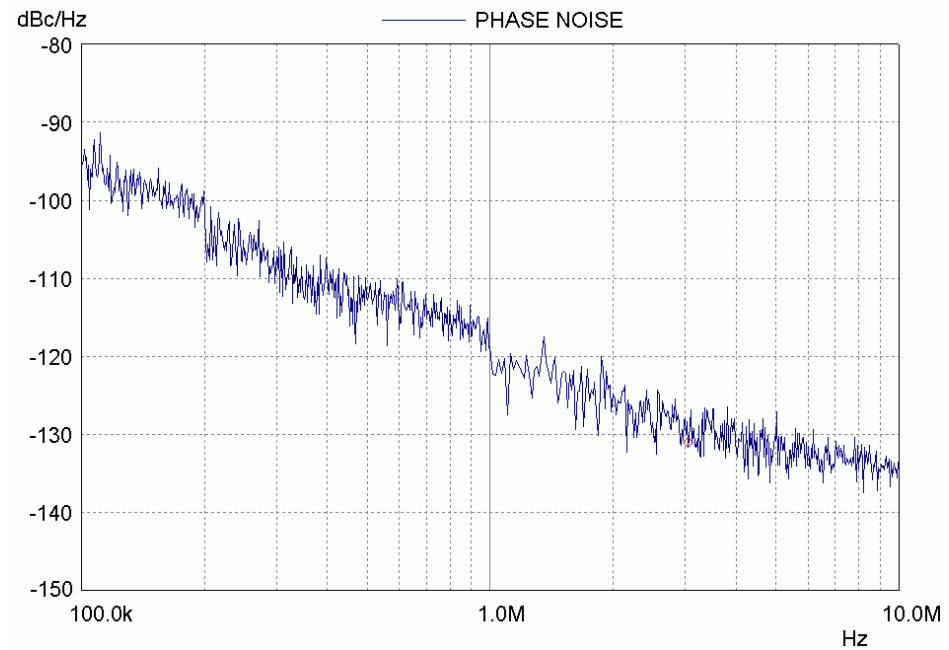


# Inductor Measurement using Microprobe

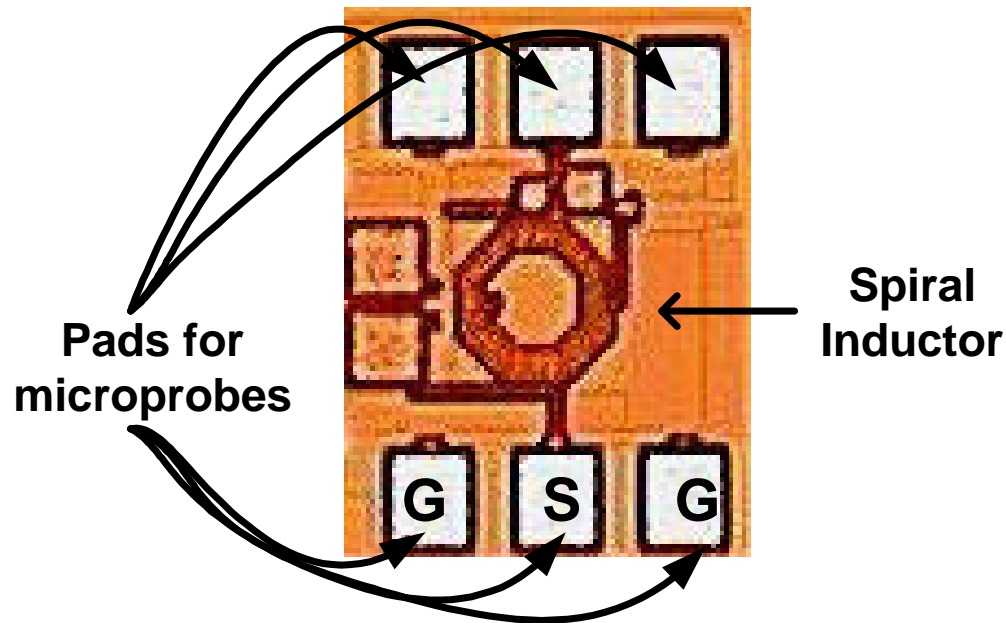

- Measurement instruments
  - Probe Mount Station
  - Microprobe ( $150\mu m$  pitch)
  - Network Analyzer (HP 8719ET)
  - SMA Coaxial cable




# Calibrating Network Analyzer

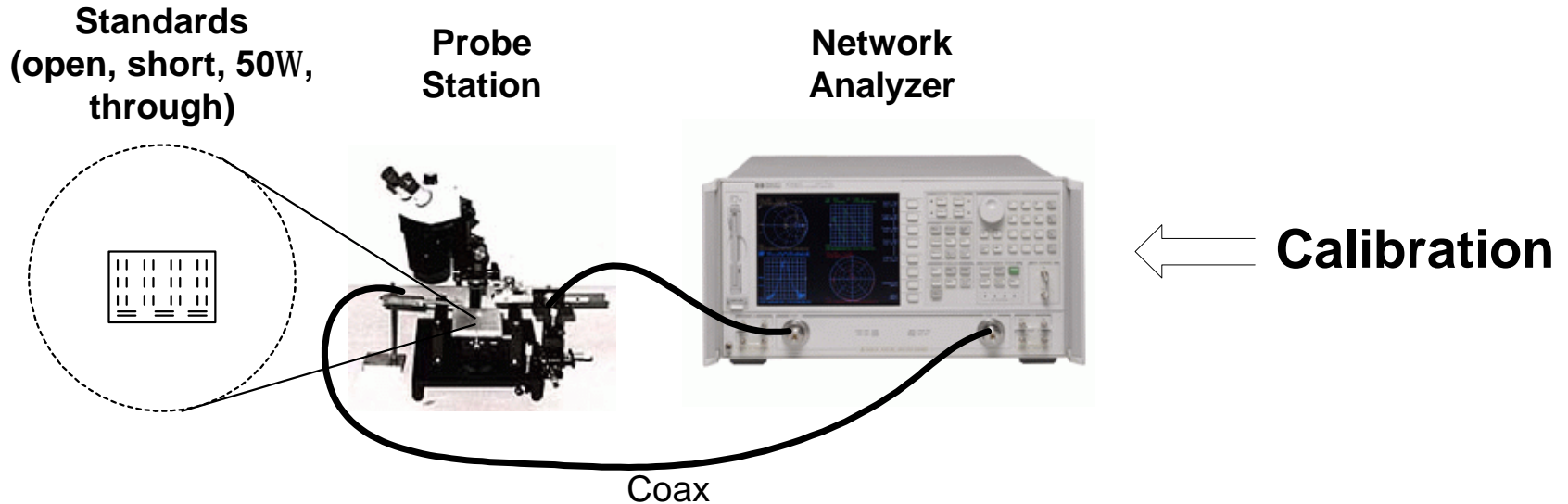

- Calibration is required to compensate the effect of microprobes, coaxial cables and network analyzer itself.
- The effect of pads for microprobe landing *cannot* be calibrated out. De-embedding after measurement is required.

# Measurement Setup

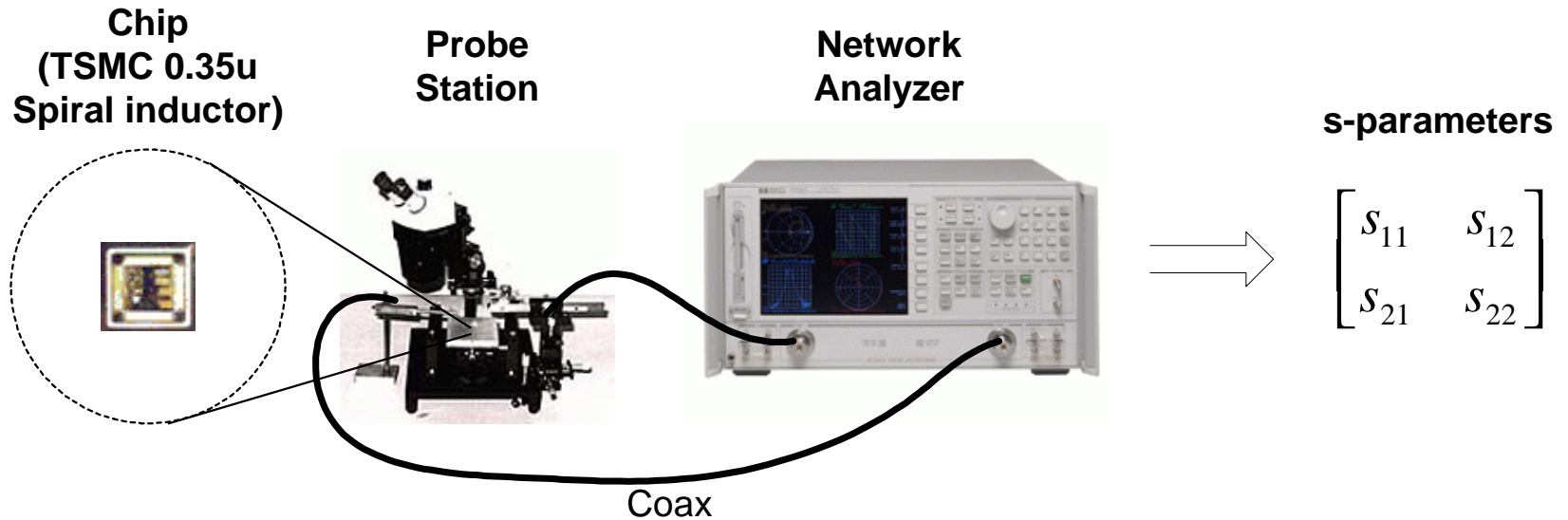

- The device under test is measured after calibration
- Network analyzer extracts the s-parameters

# s-parameter to y-parameter Conversion

$$y_{11} = \frac{(1 - s_{11})(1 + s_{22}) + s_{12}s_{21}}{Z_o \Delta}$$



$$y_{12} = \frac{-2s_{12}}{Z_o \Delta}$$

$$y_{21} = \frac{-2s_{21}}{Z_o \Delta}$$

$$y_{22} = \frac{(1 + s_{11})(1 - s_{22}) + s_{12}s_{21}}{Z_o \Delta}$$

$$\Delta = (1 + s_{11})(1 + s_{22}) - s_{12}s_{21}$$

# Modeling Inductor from y-parameter

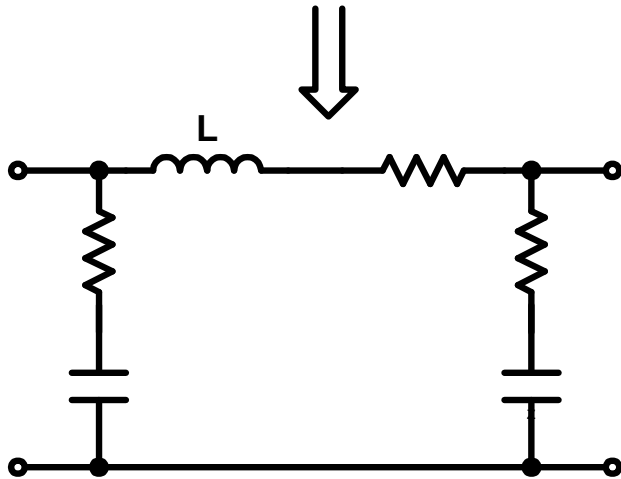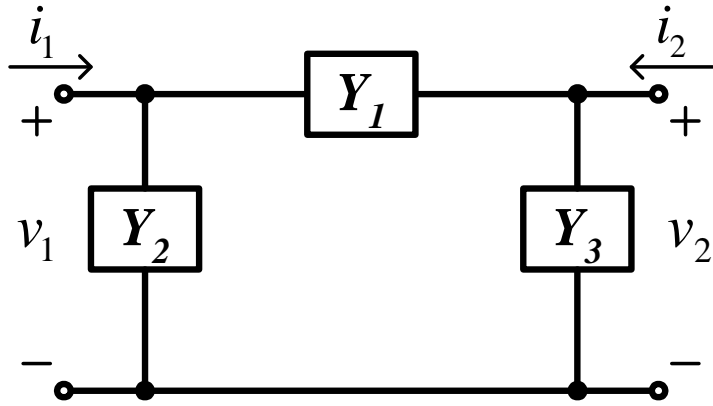

$$y_{11} = \left. \frac{i_1}{v_1} \right|_{v_2=0} = Y_1 + Y_2$$

$$y_{12} = \left. \frac{i_1}{v_2} \right|_{v_1=0} = -Y_1$$

$$y_{21} = \left. \frac{i_2}{v_1} \right|_{v_2=0} = -Y_1$$

$$y_{22} = \left. \frac{i_2}{v_2} \right|_{v_1=0} = Y_1 + Y_3$$

---

# Conclusion

- Basic concept of VCO is discussed.
- Design procedure of a 2.4GHz VCO for Bluetooth application is presented.
- Testing result of the circuit is provided.