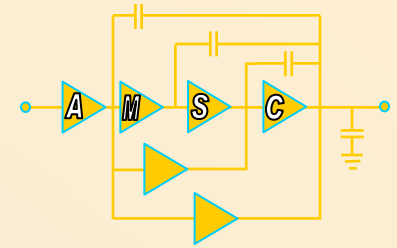




ECEN 665 (ESS)




Radio Frequency Filters

Material courtesy of Fikret Dülger,


Texas A&M University
Electrical and Computer Engineering Department
Analog & Mixed-Signal Design Center

Outline




- Problem Definition, Motivations and Research Goal
- A Fully-Integrated Q-Enhancement LC Bandpass Filter
 - Noise Analysis
 - Nonlinearity Analysis
 - IC Measurements of the Filter in 0.35 μ m CMOS
- Comparison with previous reported filters and Conclusions

Problem Definition and Motivations



- Wireless Communication systems have become an important part of our daily lives.
- The demand towards lower cost makes the task of circuit designers more and more challenging.
- This translates into the circuit specifications with lower power consumption, smaller die area but without any compromise from higher performance .

Problem Definition and Motivations


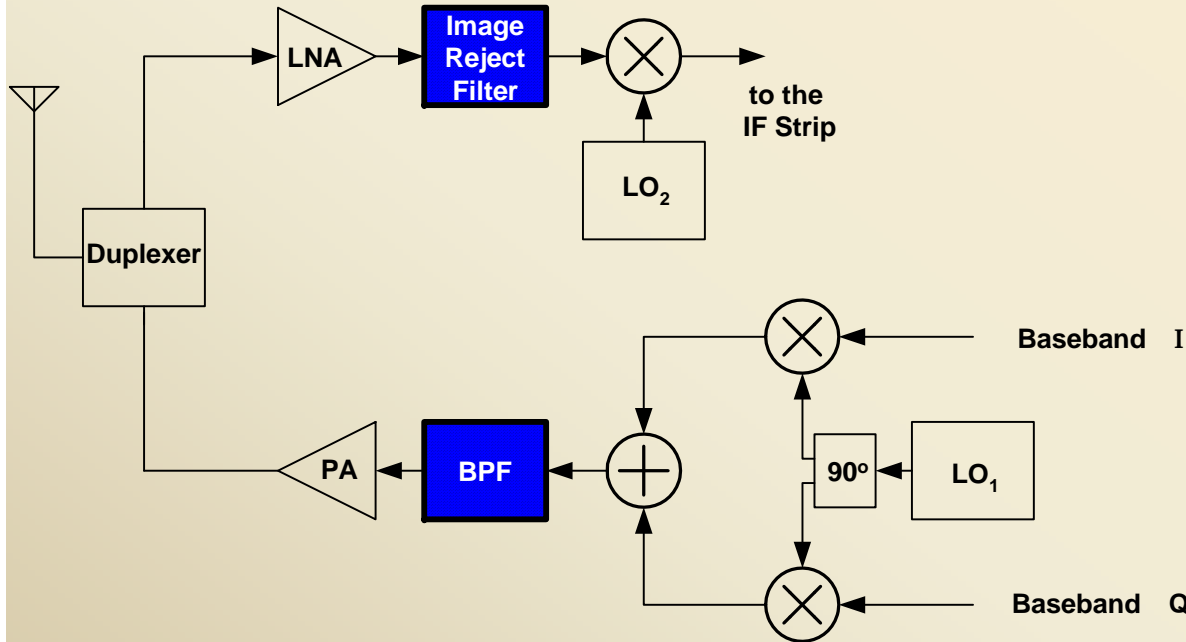


- Transceiver front-ends are the sections next to the antenna.
- Frequency range of interest is from 900 MHz to 2.4 GHz.
- In state-of-the-art solutions, the bandpass filters are off-chip.
- **MOTIVATION FOR INTEGRATION!**

Research Goal

- The feasibility of a Q-enhanced bandpass filter designed with a standard (low cost) CMOS technology at 2 GHz is investigated.
- The issue is addressed through the simulations, analyses, and the experimental verification of a prototype designed and fabricated in a 0.35 μm CMOS technology.

Q-Enhancement Bandpass Filters

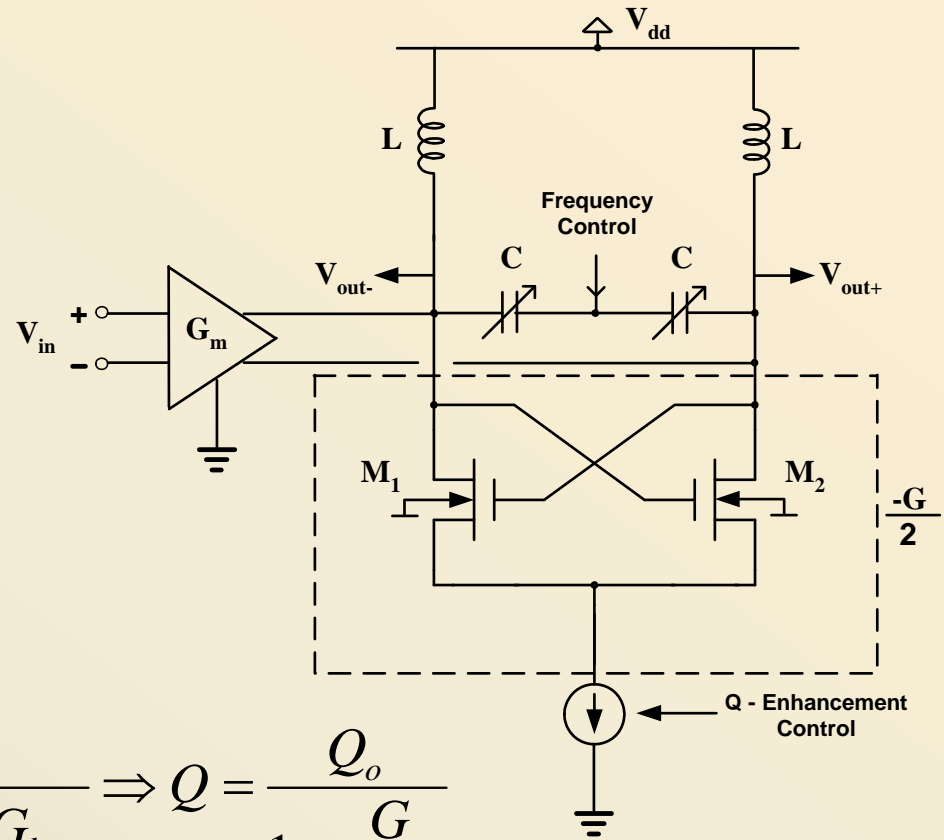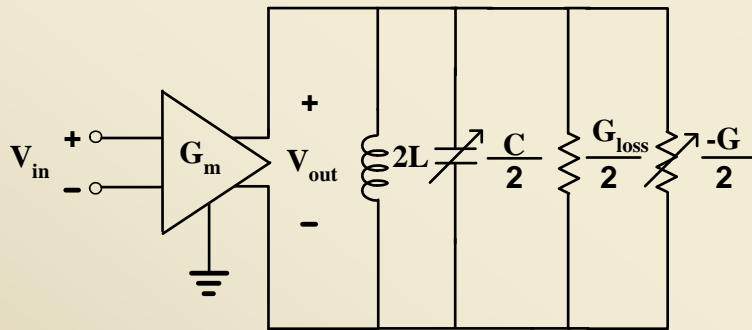

$$Q_o \equiv \frac{1}{\omega_o L G_{loss}} \Rightarrow Q = \frac{Q_o}{1 - \frac{G}{G_{loss}}}$$

(a)

(b)

$(G_{loss} > G \text{ for stability})$


A CMOS Programmable RF Bandpass Filter

Programmable in:

- Peak Gain (not exploited previously)
- Filter Q
- Center Frequency

$$|H(j\omega_o)| \cong |G_m(j\omega_o) Q \omega_o L|$$

$$\omega_o \cong \frac{1}{\sqrt{LC}}$$

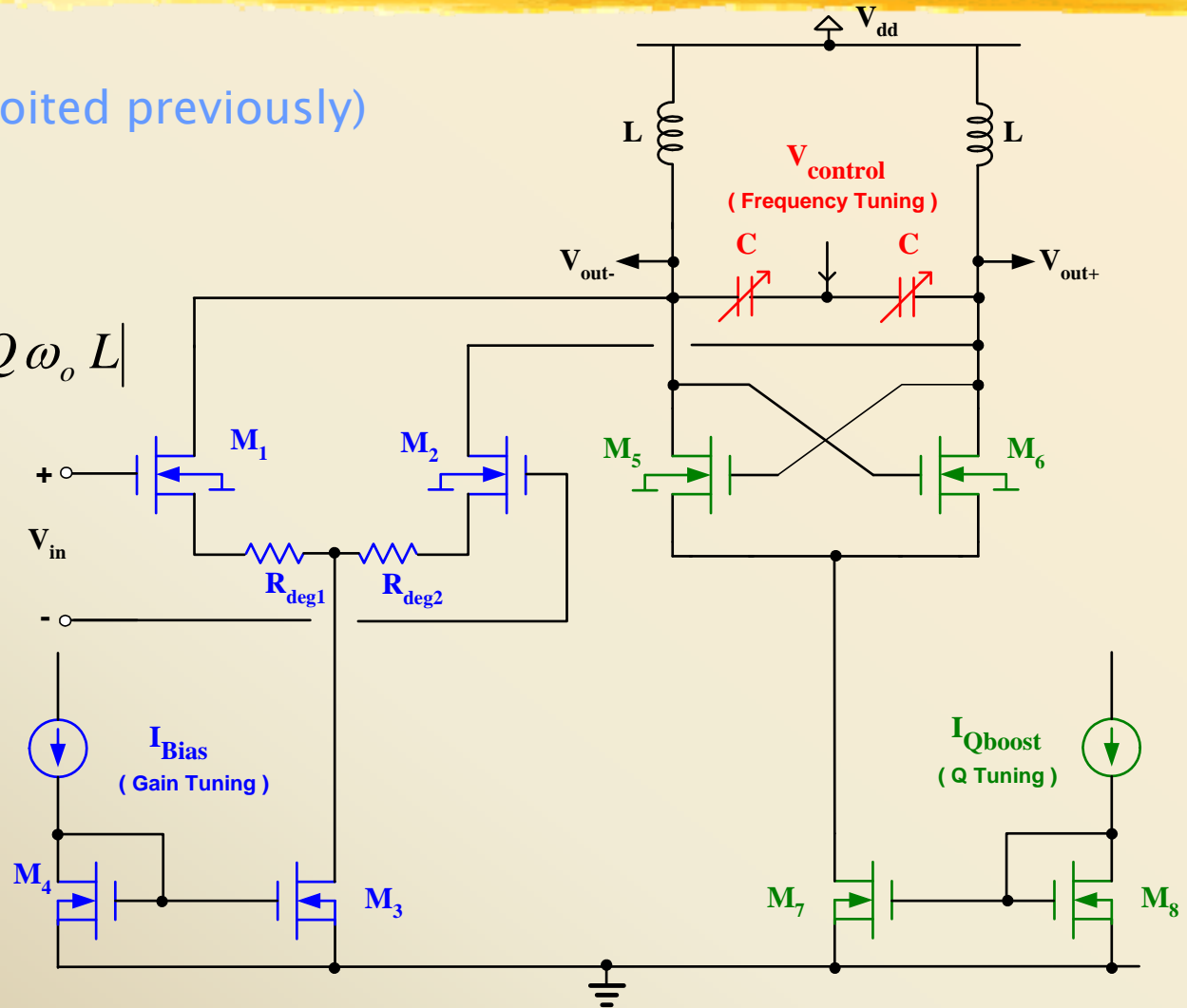


A CMOS Programmable Bandpass Filter

- The peak gain programmability through the input G_m stage.

$$|H(j\omega_o)| \cong \left| \frac{G_m(j\omega_o)}{G_{loss} - G} \right| = |G_m(j\omega_o) Q \omega_o L|$$

- Increasing Q also increases the peak gain.
- If ω_o and Q are fixed, the peak gain can be modified through G_m .

Noise Analysis

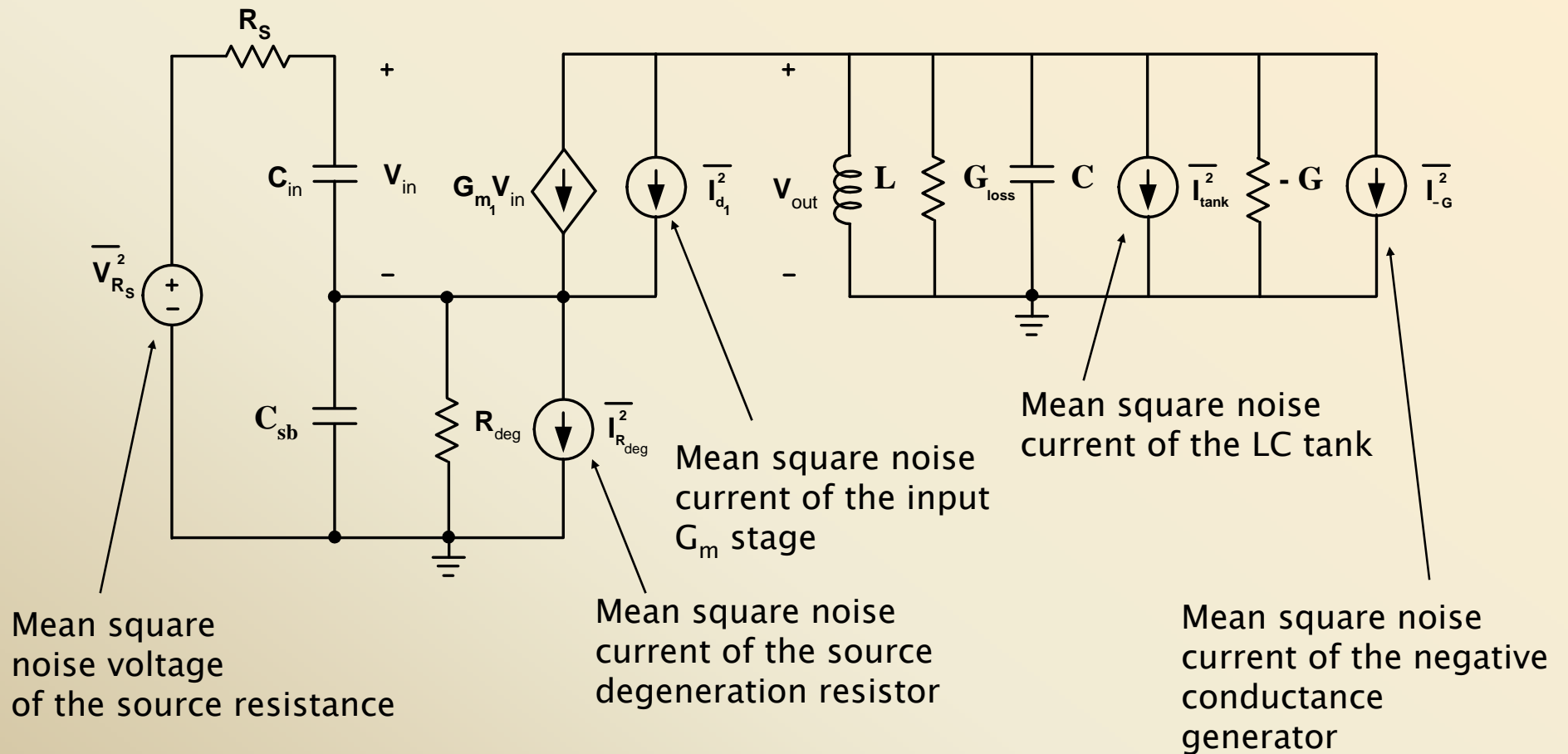

Noise Analysis (contd.)

- The noise factor at ω_o is obtained as

$$F = 1 + \frac{8kTG_{loss} + 2\overline{I_{-G}^2} + 2\overline{I_{R_{deg}}^2} G_{m1}^2 |Z_{S_{in}}(j\omega_o)|^2}{4kTR_S G_m^2} + \frac{2\overline{I_{d_{in}}^2}}{4kTR_S G_{m1}^2}$$

- The calculations yield the following percentage contributions from the components:

LC Tank: 44.5%, $-G$: 38%, Input G_m : 13.5%, R_{deg} : 2.7%


- Increasing G_m reduces the contribution of $-G$ and the LC tank

Nonlinearity Analysis

- There are three main nonlinearity contributors:
 - the negative conductance generator
 - the varactor
 - the input G_m stage
- The analyses consider each contributor separately!
- Isolating each contributor allows us to identify the design trade-offs involved.

Nonlinearity Analysis (contd.)

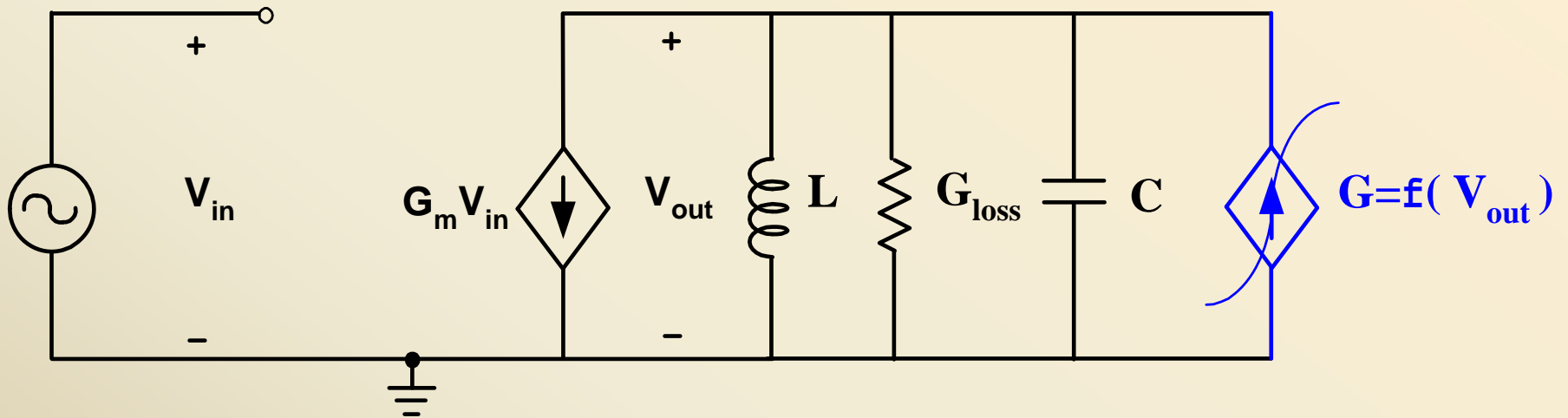Contribution of the Negative Conductance Generator



- The nonlinear behavior of the Negative Conductance is isolated first.
- We use the method proposed by Wambacq/Sansen in “Distortion Analysis of Analog Integrated Circuits”.

Noise-linearity, Q-selectivity-linearity trade-offs !

- The 1dB compression point is approximated as:

$$V_{1dB} \cong \sqrt{\frac{2.32 \times g_{m5}}{\left(2K_2^2 + \frac{K_2 \theta_5 g_{m5}}{1 + \theta_5 (V_{GS5} - V_{T5})}\right)} \left(\frac{1}{G_m^2 Q^3 \omega_o^3 L^3}\right)}$$

$$K_2 \cong \frac{\mu_o C_{OX}}{2} \left(\frac{W_5}{L_5}\right) \left(\frac{1}{(1 + \theta(V_{GS5} - V_{T5}))^3}\right)$$

- The effective bias of the negative conductance should be maximized
- With a higher Q_o , a lower g_{m5} is required: higher eff. bias with given I_{SS} .
- The higher the peak gain, $G_m Q \omega_o L$, the worse the linearity.

Nonlinearity Contribution of the Varactor

$$V_{1dB} \approx \sqrt{\frac{1.55}{G_m^2 Q^3 \omega_o^3 L^3} \times \frac{\left| \frac{1}{j2\omega_o L} + G_{loss} + j2\omega_o (C + C_{Vo}) \right|}{\left| -\frac{K_{3cv}}{L} - j\omega_o 2K_{3cv} G_{loss} + 4\omega_o^2 \left((C + C_{Vo}) K_{3cv} - 2K_{2cv}^2 \right) \right|}}$$

- Higher peak voltage gain, $G_m Q \omega_o L$, degrades linearity
- Trade-offs between noise-linearity and selectivity-linearity!


Nonlinearity Contribution of the Input G_m stage

$$V_{1dB} \cong \sqrt{2.32 \times \frac{G_{m1}^2 (1 + G_{m1} R_{deg})^3}{\left(2K_{2G_{m1}}^2 + \frac{K_{2G_{m1}} \theta_1 G_{m1}}{1 + \theta_1 (V_{GS1} - V_{T1})} \right)}}$$


- The effective bias of the transistors should be maximized!
- Increasing R_{deg} improves the linearity with a penalty in power consumption for the same input G_m .
- The same applies to adding R_{deg} to the cross-coupled pair

linearity-power trade-off

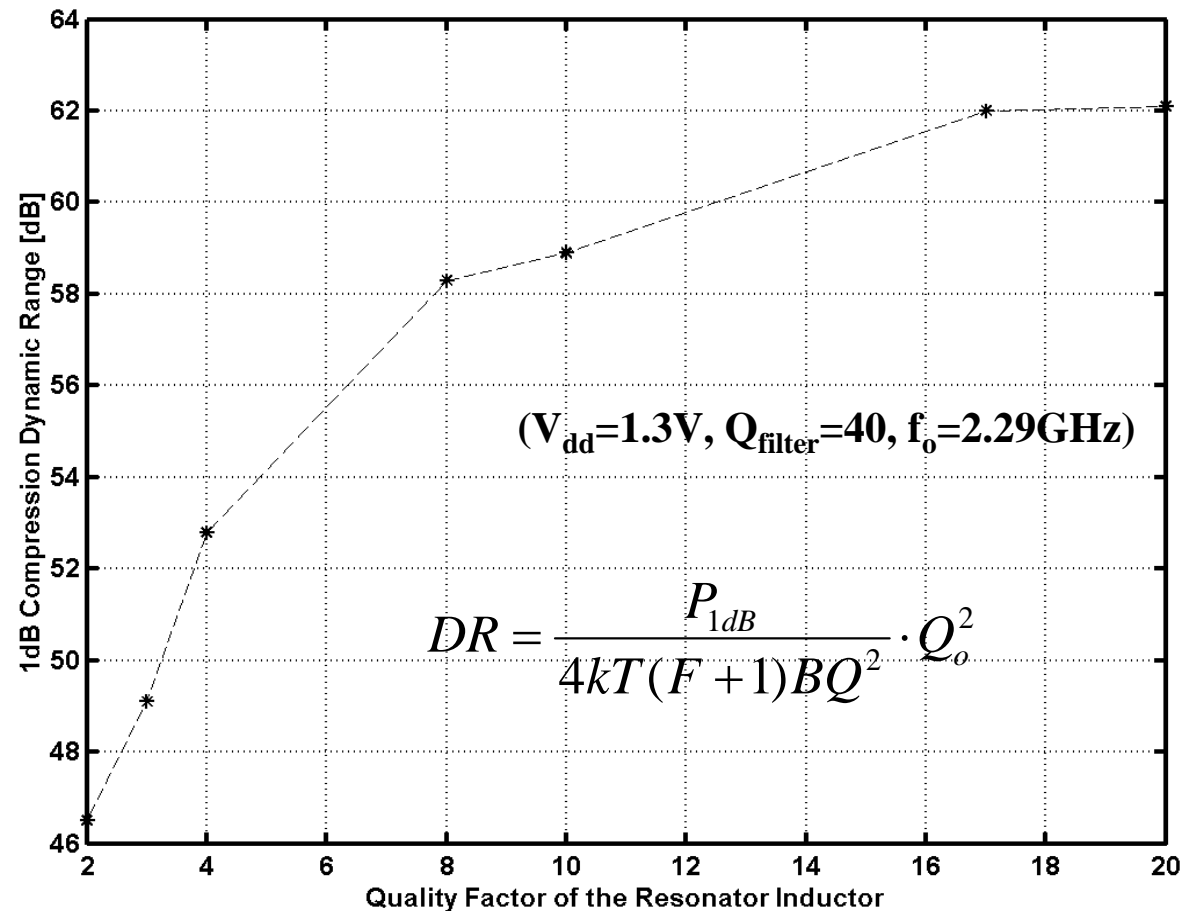
Simulated DR vs. Q of the Resonator Inductor



Dynamic Range Simulations

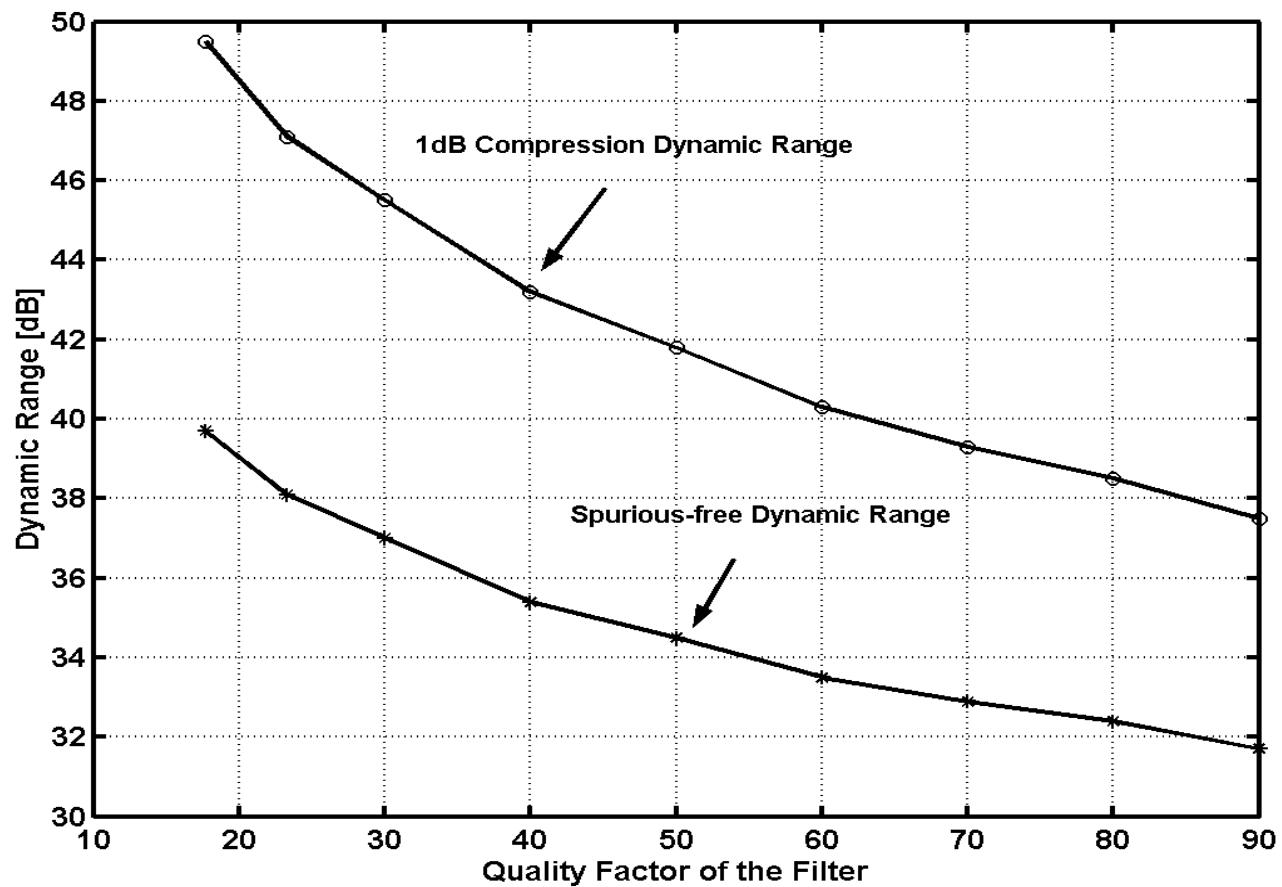


Integrated Circuit Measurements

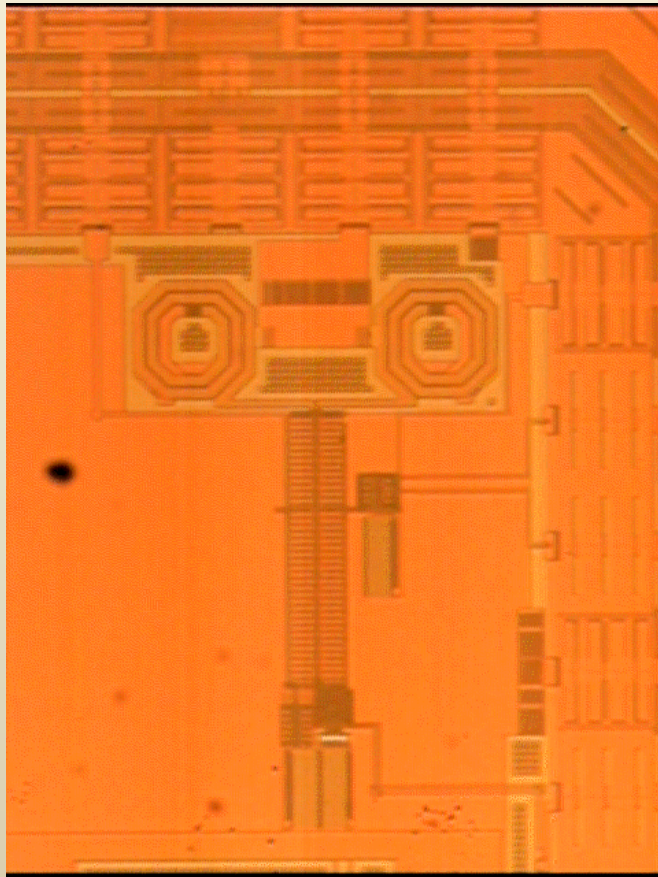

- TSMC 0.35 μm CMOS technology
- The second poly was not used. Compatibility with a standard Digital CMOS
- The filter operates with a supply voltage of 1.3V, and 4mA for a $Q= 40$ at 2.19GHz
- Chip area+buffers ~ 0.1mm².

Measured Q-Tuning

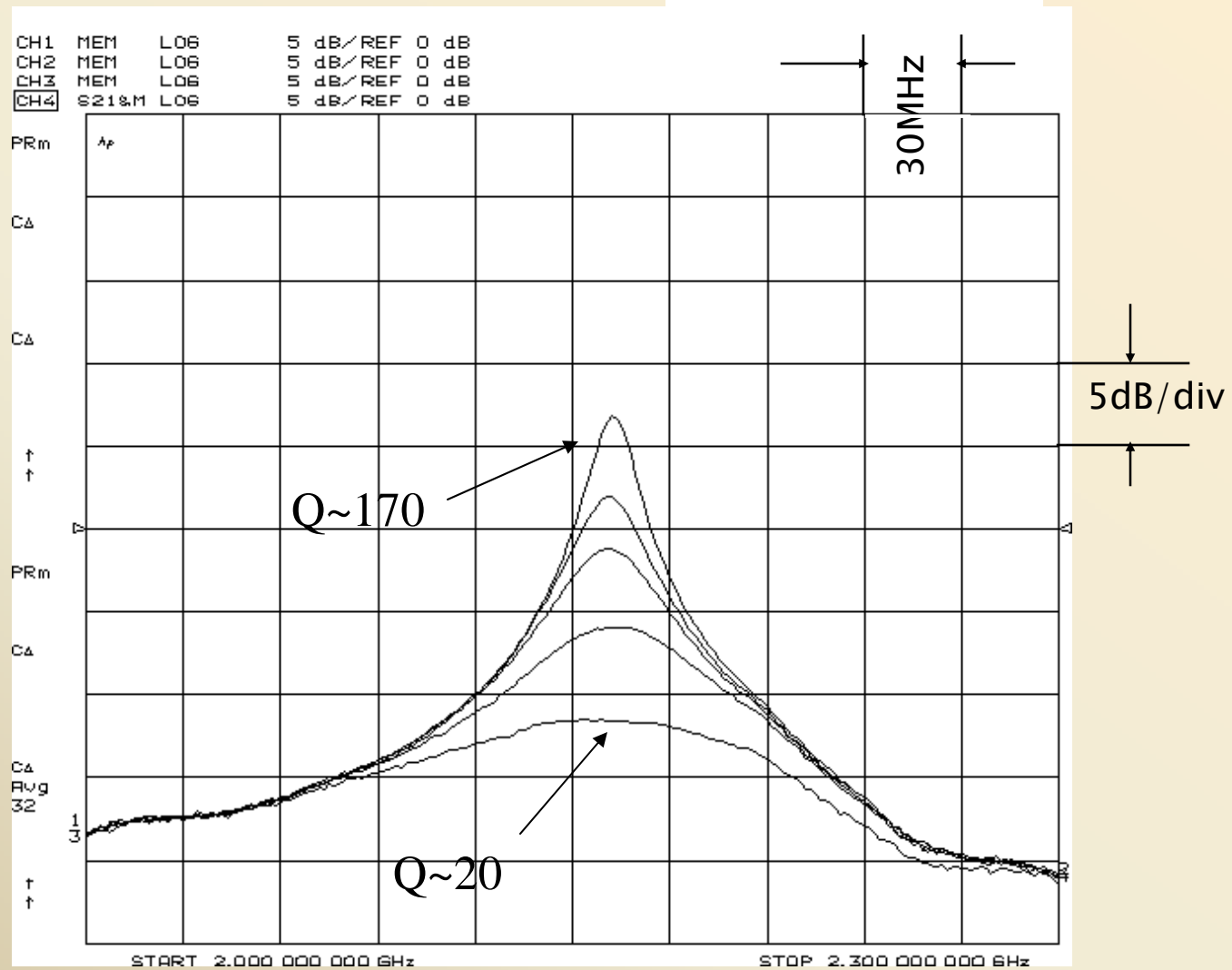
More than 3 octaves at $f_o = 2.16\text{GHz}$



Measured Frequency Tuning

22 Aug 2001 16:46:04

CH1	MEM	LOG	5 dB/REF 0 dB
CH2	S21&M	LOG	5 dB/REF 0 dB
MEM	LOG	5 dB/REF 0 dB	
MEM	LOG	5 dB/REF 0 dB	

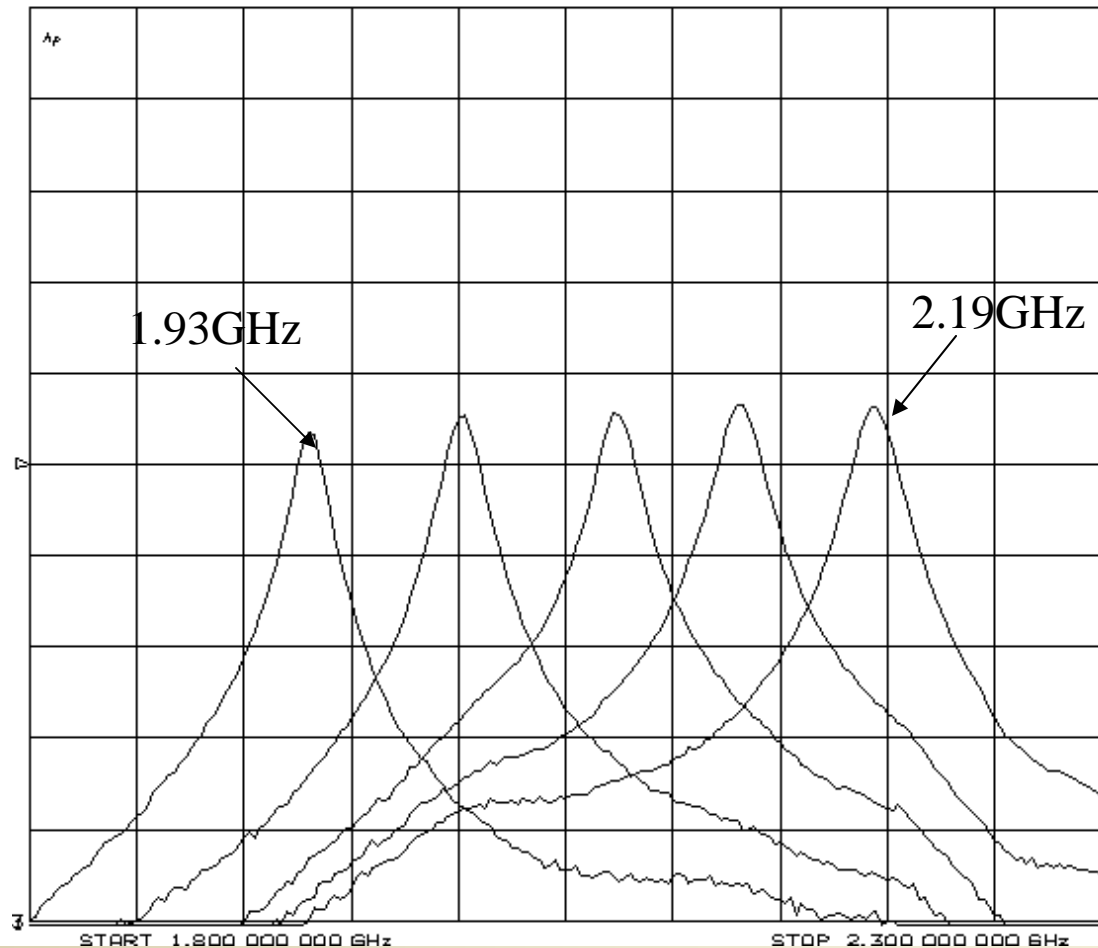


13% around
2.1GHz with
Q~100

Measured Peak Gain Tuning

27 Aug 2001 09:36:22

CH1	S21&M	LOG	5 dB/REF 0 dB
CH2	MEM	LOG	5 dB/REF 0 dB
---	MEM	LOG	5 dB/REF 0 dB
---	MEM	LOG	5 dB/REF 0 dB

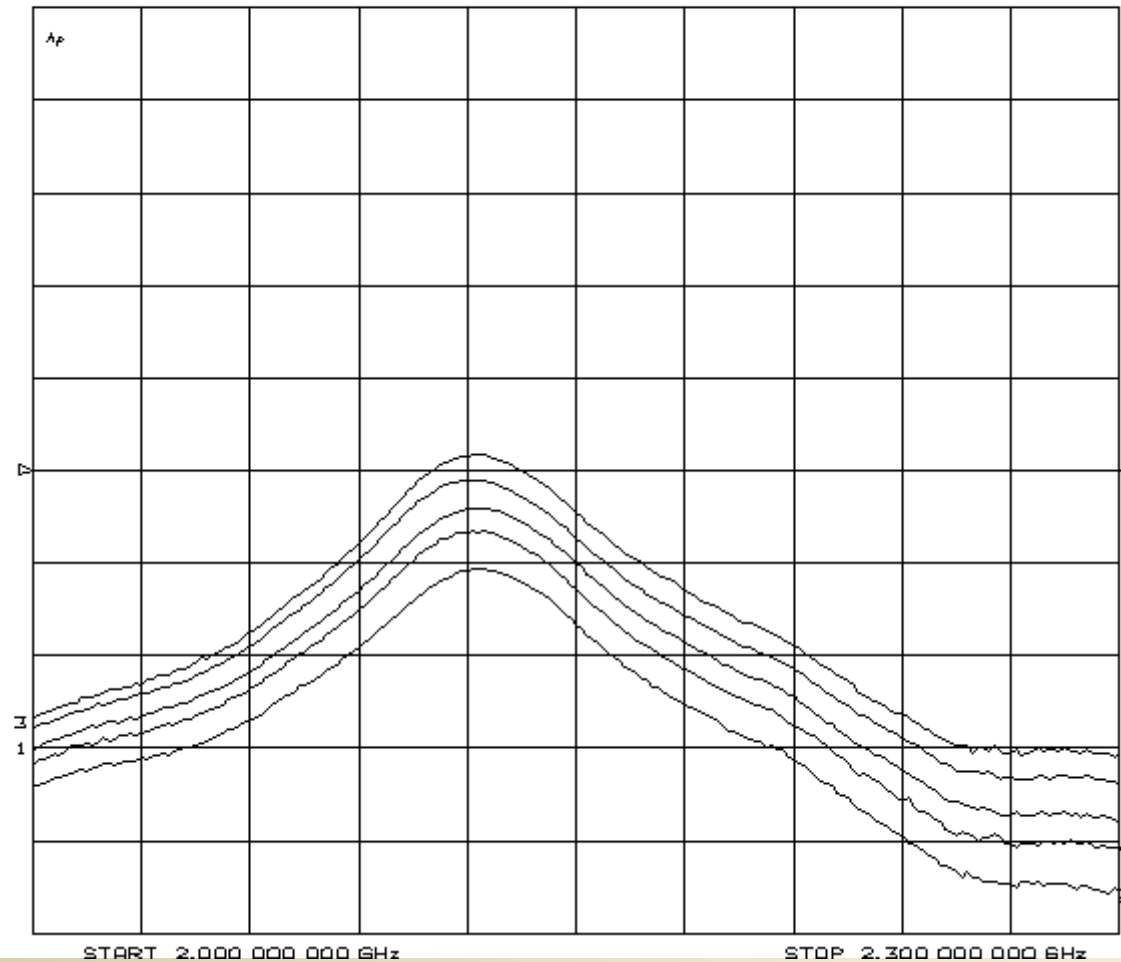


Around
2 octaves with
 $f_o=2.12\text{GHz}$
and $Q=40$

Providing gain at the ω_o of an image-reject filter is useful in a receiver front-end after the LNA, to relax the NF spec of the mixer.

Overlaid Measurements of 10 different ICs


(a)

with the same bias settings

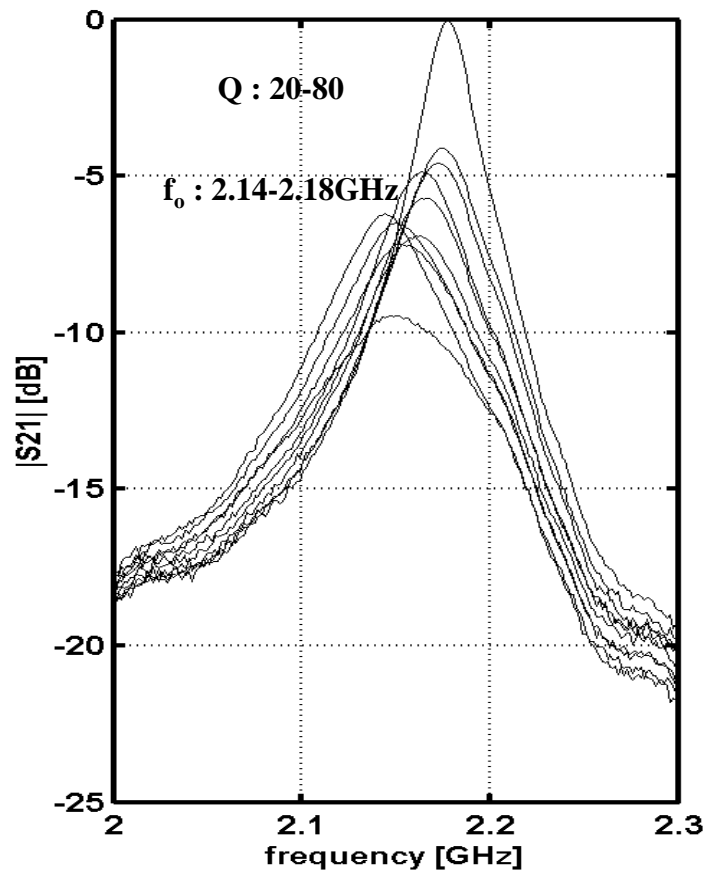

(b)

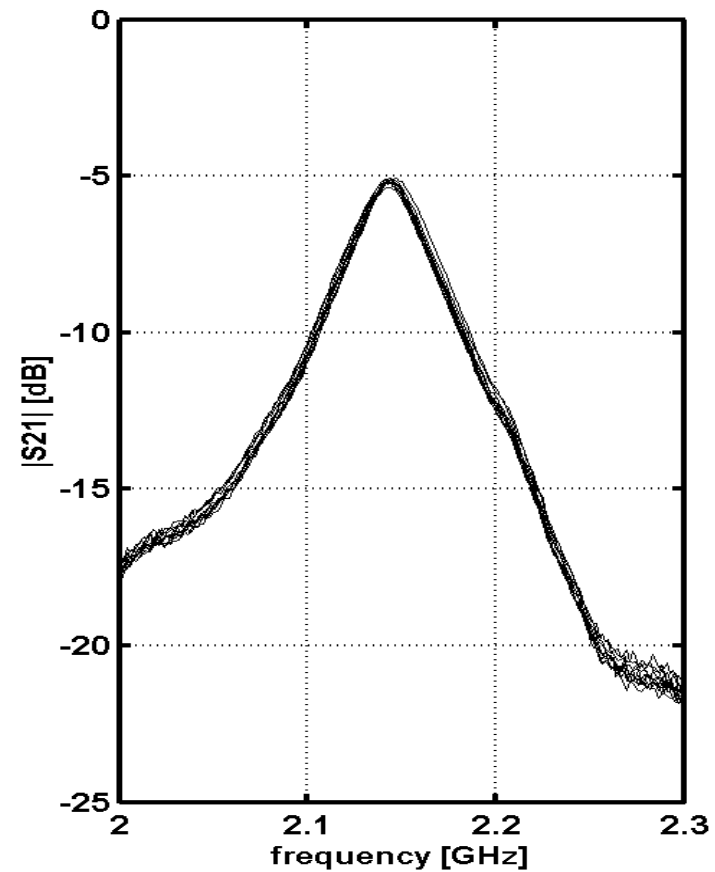
programmed for the same f_0 , gain and $Q=40$



Two-tone IM3 Measurement

* $V_{dd}=1.3V$, $f_o=2.19GHz$, $Q=40$

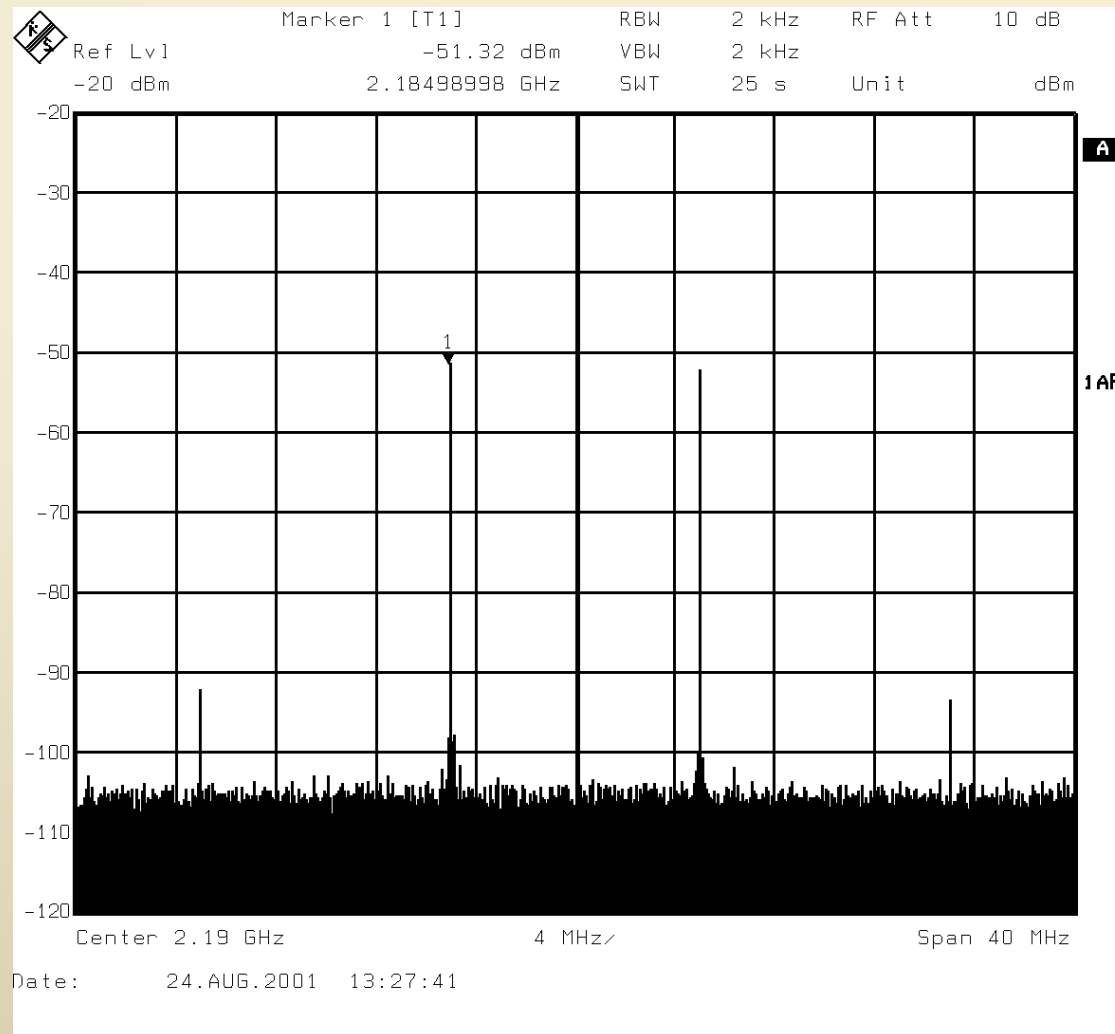
$P_{in} = -38dBm$
 $f_{in1} = 2.185GHz$
 $f_{in2} = 2.195GHz$



$P_{in,1dB} = -30dBm$
 $IIP_3 = -17.5dBm$

1 dB Compression Comparison

* $V_{dd}=1.5V$, $f_o=2.17GHz$

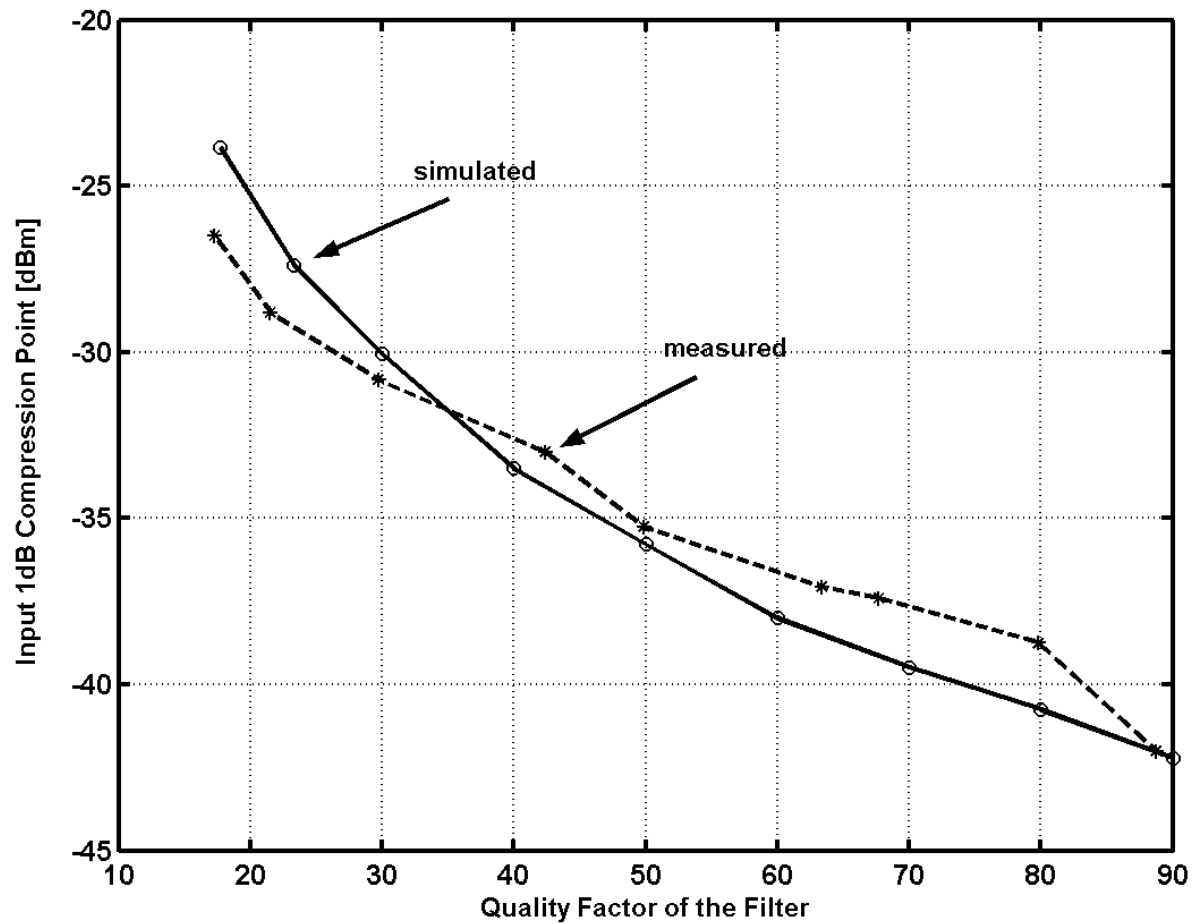

A Comparison with State-of-the-art

Reference	Tech.	f_o	Bandwidth	V_{dd}	P_D /Pole	Area/Pole	SFDR
[1]	Bipolar	1.8GHz	51.4MHz	2.8V	12.2mW	0.2mm ²	30dB
[3]	Bipolar	1GHz	25MHz	5V	34mW	0.3 mm ²	36dB
[4]	BiCMOS	750MHz	37.5MHz	5V	40mW	0.3 mm ²	25dB
[5]	BiCMOS	1.9GHz	150MHz	2.7V	12.15mW	1.79 mm ²	49dB

A Comparison with State-of-the-art (contd.)

Reference	Tech.	f_o	Bandwidth	V_{dd}	P_D /Pole	Area/Pole	SFDR
[2]	CMOS	850MHz	18MHz	2.7V	52mW	0.5mm ²	55dB
[6]	CMOS	850MHz	28.3MHz	2V	22.9mW	0.32mm ²	28dB
[7]	CMOS	2.14GHz	60MHz	2.5V	2.9mW	0.59mm ²	55dB
This work	CMOS	2.19GHz	53.8MHz	1.3V	2.6mW	0.05mm²	31dB

Remarks

- Low voltage, low power, compact fully-integrated programmable bandpass filter in mainstream CMOS at frequencies higher than 2GHz.
 - Comparison shows that the proposed RF filter uses the lowest power supply voltage, lowest power consumption per pole and occupies at least four times less silicon area per pole
 - Programmability in the peak gain
 - Noise and Nonlinearity analyses of the structure provide simplified approximate expressions to clarify design trade-offs

Reference:

- Fikret Dulger, E. Sanchez-Sinencio, J. Silva-Martinez, "[A 1.3-V 5-mW fully integrated tunable bandpass filter at 2.1 GHz in 0.35 um CMOS,](#)" *IEEE Journal of Solid-State Circuits*, Volume :38 Issue:6, June 2003, Page(s): 918– 928
- F. Dulger and E. Sanchez-Sinencio, "Integrated RF Building Blocks for Wireless Communication" book, details will follow later.