

ECEN 665 (ESS) : *RF Communication Circuits and Systems*

# Volterra Series: Introduction & Application

Prepared by: Heng Zhang

*Part of the material here provided is based on Dr. Chunyu Xin's dissertation*



# Outline

- Introduction: History, Basics
- Volterra Series in frequency domain
- Applications of Volterra Series:
  - Example1: Common Source Amplifier
  - Example2: Differential Pair
  - Example3: Current Mirror
  - Example4: Gilbert Mixer



# Volterra Series: History

- In 1887, Vito Volterra : “Volterra Series” as a model for nonlinear behavior
- In 1942, Norbert Wiener: applied Volterra Series to nonlinear circuit analysis
- In 1957, J. F. Barrett: systematically applied Volterra series to nonlinear system; Later, D.A. George: used the multidimensional Laplace transformation to study Volterra operators
- Nowadays: extensively used to calculate small, but nevertheless troublesome, distortion terms in transistor amplifiers and systems.



# Why do we need Volterra Series?

- At high enough frequency, the assumption **there's no memory effect due to capacitors and inductors** – NOT CORRECT!
- Taylor series analysis: NO memory effect, cannot calculate distortion at high frequency
- Low frequency analysis: high-frequency effect can degrade distortion performance by 100% more than predicted.

eg. Fully differential circuits without mismatch:

Low-frequency analysis predicts the  $HD_2$  to be zero

Volterra series reveals an  $HD_2$  as high as -32dB (**see the numerical example later**)



# When Volterra Series Are Good?

- Can calculate the high-frequency-low-distortion terms for weakly non-linear time-invariant (NLTI) system with memory effect
- “Weakly nonlinear” assumption:
  - Input excitation is “small” → use polynomials to model nonlinearities
  - When small inputs, the 1<sup>st</sup> term dominates



# When Volterra Series Are Bad?

- Results are a sum of infinite numbers of terms, possible to diverge
- Define: “weak enough” system ( $G_1 \gg G_3 \gg G_5$ ;  $G_1$ ,  $G_3$ ,  $G_5 = 1^{\text{st}}$  order,  $3^{\text{rd}}$  order, and  $5^{\text{th}}$  order Volterra kernels;  $G_5$  is small to be negligible), the infinite sums will converge and converge rapidly
- “Strongly nonlinear” system: sum will diverge, Volterra series becomes invalid  $\rightarrow$  Volterra series are impractical in strongly nonlinear problems

# Volterra Series: basic

- Linear system without memory :

$$y(t) = h \cdot x(t)$$

Output  $y$  at instant  $t$  only depends on input  $x$  at that instant only.

$h$ : linear gain

- Linear, discrete, causal and time-invariant system with memory (described by summing all the effects of past inputs with proper “weights”):

$$y(n) = \sum_{i=0}^n h(\tau_i) \cdot x(n - \tau_i)$$

$n$ : time index       $h(\tau)$ : impulse response

continuous time domain (the convolution sum becomes a convolution integral):

$$y(t) = \int_0^t h(\tau) x(t - \tau) d\tau$$

# Volterra Series: basic

System with 2<sup>nd</sup> order nonlinearity:

Memory-less system:  $y_2(t) = h_2 \cdot x^2(t)$

System with memory: (firstly: discrete and assume all the terms sum with equal weights)

$$\begin{aligned} y(n) &= x(n) \cdot x(n) + x(n) \cdot x(n-1) + \dots + x(n) \cdot x(0) \\ &+ x(n-1) \cdot x(n-1) + x(n-1) \cdot x(n-2) + \dots + x(n-1) \cdot x(0) \\ &+ \dots + x(0) \cdot x(0) = \sum_{i=0}^n x(n-i) \cdot x(i) + \sum_{i=0}^{n-1} x(n-1-i) \cdot x(i) + \dots = \sum_{j=0}^n \sum_{i=0}^n x(i) \cdot x(j) \end{aligned}$$

Next: Add proper weights to make it a weighed double sum:

$$y(n) = \sum_{j=0}^n \sum_{i=0}^n h_2(p_i, p_j) x(n-p_i) \cdot x(n-p_j)$$

$h_2$ : a function of time index  $p_i, p_j$  (2<sup>nd</sup> order impulse response)

Continuous time domain (the convolution sum becomes a convolution integral) :

$$y_2(t) = \int \int_0^t h_2(\tau_1, \tau_2) x(t-\tau_1) x(t-\tau_2) d\tau_1 d\tau_2$$



# Volterra Series: basic

$n^{\text{th}}$ -order nonlinear system :

Memory-less system:  $y(t) = h_1 \cdot x(t) + h_2 \cdot x^2(t) + \dots + h_n \cdot x^n(t)$

System with memory:

$$\begin{aligned} y(t) &= \int_0^t h_1(\tau_1) x(t - \tau_1) d\tau_1 \\ &+ \int \int_0^t h_2(\tau_1, \tau_2) x(t - \tau_1) x(t - \tau_2) d\tau_1 d\tau_2 \\ &+ \int \int \int_0^t h_3(\tau_1, \tau_2, \tau_3) x(t - \tau_1) x(t - \tau_2) x(t - \tau_3) d\tau_1 d\tau_2 d\tau_3 \\ &+ \dots + \int \dots \int_0^t h_n(\tau_1, \tau_2, \dots, \tau_n) x(t - \tau_1) x(t - \tau_2) \dots x(t - \tau_n) d\tau_1 d\tau_2 \dots d\tau_n \end{aligned}$$

Volterra Series expansion: an infinite sum of multidimensional convolution integrals

$h_n(\tau_1, \dots, \tau_n)$  :  $n^{\text{th}}$  order Volterra Kernels ( $n^{\text{th}}$  order impulse response of the system)



# Volterra Series vs. Taylor Series

- Nonlinear memory-less system represented using Taylor series:

$$y(t) = K_1 \cdot x(t) + K_2 \cdot x^2(t) + K_3 \cdot x^3(t) + \dots + K_n \cdot x^n(t) + \dots$$

- Nonlinear system with memory represented using Volterra series:

$$y(t) = \mathbf{H}_1[x(t)] + \mathbf{H}_2[x(t)] + \mathbf{H}_3[x(t)] + \dots + \mathbf{H}_n[x(t)] + \dots$$

in which  $H_n[x(t)] = \int \dots \int h_n(\tau_1, \tau_2, \dots, \tau_n) x(t - \tau_1) x(t - \tau_2) \dots x(t - \tau_n) d\tau_1 d\tau_2 \dots d\tau_n$

$\mathbf{H}_n[\cdot]$  : n<sup>th</sup> order Volterra operator.

$h_n(\tau_1, \dots, \tau_n)$  : n<sup>th</sup> order Volterra Kernels



# Volterra kernel

$h_n(\tau_1, \dots, \tau_n)$  :  $n^{\text{th}}$  order Volterra Kernels

$h_n(\tau_1, \dots, \tau_n) = 0$  : for any  $\tau_j < 0, j = 1, 2, \dots, n$

$h_n(\tau_1, \dots, \tau_n)$  is not necessarily symmetrical to its variables

Always possible to construct a symmetrical kernel from the asymmetrical kernel

$$h_n^{(s)}(\tau_1, \dots, \tau_n) = \frac{1}{n!} \sum_p h_n^{(a)}(\tau_1, \dots, \tau_n)$$

Summation runs through all possible permutations

# Volterra series in frequency domain

- Why study the nonlinear system in frequency domain?
- Frequency domain Volterra kernels are needed to calculate the distortion. eg. HD<sub>2</sub>, HD<sub>3</sub>, IM<sub>3</sub>,...
- Fourier transform: time domain Volterra → frequency domain Volterra

eg. the n-dimensional Fourier transform for an n<sup>th</sup> order Volterra kernel

$h_n(\tau_1, \dots, \tau_n)$  is:

$$\begin{aligned} H_n(\omega_1, \dots, \omega_n) &= F\{h_n(\tau_1, \dots, \tau_n)\} \\ &= \int \dots \int h_n(\tau_1, \dots, \tau_n) e^{-j\omega_1 \tau_1} \dots e^{-j\omega_n \tau_n} d\tau_1 \dots d\tau_n \end{aligned}$$

$H_n$  is the frequency domain Volterra kernel.

# Volterra series in frequency domain

- An input with m frequency components:

$$X = A(\cos \omega_1 t + \cos \omega_2 t + \dots + \cos \omega_m t)$$

- The output of the n<sup>th</sup> order nonlinear system can be denoted as:

$$Y = H_1(j\omega_{p1}) \circ X + H_2(j\omega_{p1}, j\omega_{p2}) \circ X^2 + \dots + H_n(j\omega_{p1}, j\omega_{p2}, \dots, j\omega_{pn}) \circ X^n$$

where  $\omega_{p1}, \omega_{p2}, \dots, \omega_{pn}$  can be chosen from  $\pm\omega_1, \pm\omega_2, \dots, \pm\omega_m$

They can be equal or different, and have both the + and – combination

For each term, the frequency components in  $H_n$  are the same as in  $X^n$

The operator  $\circ$  means:

- 1) Multiply each frequency component in  $X^n$  by:  $|H_n(j\omega_{p1}, j\omega_{p2}, \dots, j\omega_{pn})|$
- 2) Shift phase by:  $\angle H_n(j\omega_{p1}, j\omega_{p2}, \dots, j\omega_{pn})$

(analogy to filtering operation)

# Volterra series in frequency domain

eg, input with two frequency components:  $X = A(\cos w_1 t + \cos w_2 t)$

$w_{p1}, w_{p2}, \dots, w_{pn}$  can be chosen from:  $\pm w_1, \pm w_2$

$H_2(jw_{p1}, jw_{p2}) \circ X^2$  represents the following terms (eliminates all the overlap terms):

$$|H_2(jw_1, jw_1)| X^2 \angle H_2(jw_1, jw_1) = \frac{1}{2} |H_2(jw_1, jw_1)| A^2 \cos(2w_1 t + \angle H_2(j2w_1))$$

$$|H_2(jw_1, -jw_1)| X^2 \angle H_2(jw_1, -jw_1) = \frac{1}{2} |H_2(jw_1, -jw_1)| A^2$$

$$|H_2(jw_1, jw_2)| X^2 \angle H_2(jw_1, jw_2) = |H_2(jw_1, jw_2)| A^2 \cos((w_1 + w_2)t + \angle H_2(j(w_1 + w_2)))$$

$$|H_2(jw_1, -jw_2)| X^2 \angle H_2(jw_1, -jw_2) = |H_2(jw_1, -jw_2)| A^2 \cos((w_1 - w_2)t + \angle H_2(j(w_1 - w_2)))$$

$$|H_2(jw_2, jw_2)| X^2 \angle H_2(jw_2, jw_2) = \frac{1}{2} |H_2(jw_2, jw_2)| A^2 \cos(2w_2 t + \angle H_2(j2w_2))$$

# Definition of $HD_2$ , $HD_3$ and $IM_3$

Volterra Series

Taylor Series

$$HD_2 \quad \frac{1}{2} \frac{|H_2(j\omega_1, j\omega_1)|}{|H_1(j\omega_1)|} A$$

$$\frac{1}{2} \frac{a_2}{a_1} A$$

$$HD_3 \quad \frac{1}{4} \frac{|H_3(j\omega_1, j\omega_1, j\omega_1)|}{|H_1(j\omega_1)|} A^2$$

$$\frac{1}{4} \frac{a_3}{a_1} A^2$$


$$IM_3 \quad \frac{3}{4} \frac{|H_3(j\omega_1, j\omega_1, -j\omega_1)|}{|H_1(j\omega_1)|} A^2$$

$$\frac{3}{4} \frac{a_3}{a_1} A^2$$

Observation:

1. Volterra series incorporates the frequency dependent effects
2.  $H_3(j\omega_1, j\omega_1, j\omega_1) \neq H_3(j\omega_1, j\omega_1, -j\omega_1) \longrightarrow IM_3 \neq 3HD_3$

# Example 1: Common Source Amplifier

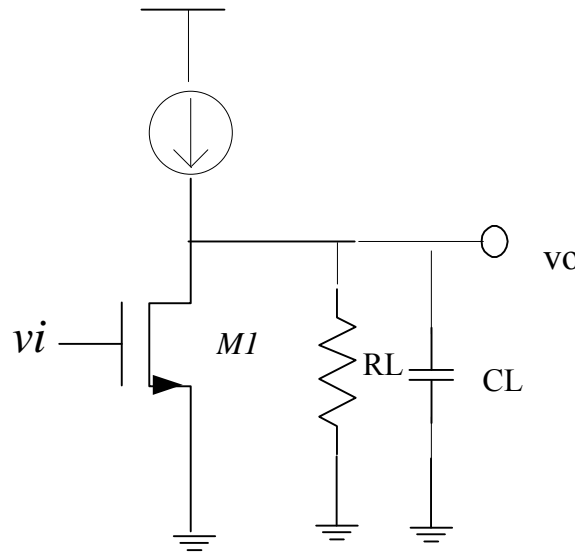

- MOS transistor: nonlinearity mainly introduced by transconductance; output impedance also contributes to distortion.
- At high frequency, load impedance dominated by  $C_L \rightarrow$  memory effect cannot be neglected, need to use Volterra series to analyze nonlinearity.



# Procedure:

1. Express output voltage  $V_{out}$  using Volterra series:

$$v_o = H_0 + H_1 \circ v_i + H_2 \circ v_i^2 + H_3 \circ v_i^3 + \dots \quad (1)$$

2. Large signal transfer function using long channel device model:

$$i_o = K (v_i + V_{od})^2 (1 + \lambda v_o) \quad (2)$$

$$v_o = -i_o Z_L = -K (v_i + V_{od})^2 (1 + \lambda v_o) Z_L \quad (3)$$

where  $V_{od} = V_{gs0} - V_{th}$ ,  $Z_L$ : impedance of R and C in parallel

3. Substitute (1) into (3):

$$\begin{aligned} H_0 + H_1 \circ v_i + H_2 \circ v_i^2 + H_3 \circ v_i^3 &= D_0 + D_1 v_i + D_2 v_i^2 \\ &+ \lambda D_0 (H_0 + H_1 \circ v_i + H_2 \circ v_i^2 + H_3 \circ v_i^3) \\ &+ \lambda D_1 (H_0 + H_1 \circ v_i + H_2 \circ v_i^2 + H_3 \circ v_i^3) v_i \\ &+ \lambda D_2 (H_0 + H_1 \circ v_i + H_2 \circ v_i^2 + H_3 \circ v_i^3) v_i^2 \end{aligned} \quad (4)$$

where  $D_0 = -KV_{od}^2 Z_L$      $D_1 = -2KV_{od} Z_L$      $D_2 = -K Z_L$

# Procedure:

4. To find the Volterra kernel  $H_k$ , equate same order terms of  $v_i$  in both sides of (4) and use the following relationships:

$$KV_{od}^2 R_L \ll \frac{1}{\lambda} \quad (5) \quad g_m = 2KV_{od} \quad (7)$$

$$\omega C_L \gg \frac{1}{R_L} \quad (6) \quad g_o = K\lambda V_{od}^2 \quad (8)$$

It can be found that:  $H_0 = \frac{D_0}{1 - \lambda D_0} \approx -KV_{od}^2 R_L (1 - g_o R_L)$  (9)

$$H_1(\omega) = \frac{1 + \lambda H_0}{1 - \lambda D_0} D_1 \approx -\frac{g_m}{j\omega C_L} (1 - g_o R_L) \quad (10)$$

$$H_2(\omega_1, \omega_2) = \frac{D_2 + \lambda(D_1 H_1 + D_2 H_0)}{1 - \lambda D_0} \approx -\frac{K(1 - g_o R_L)}{j(\omega_1 + \omega_2) C_L} \quad (11)$$

$$H_3(\omega_1, \omega_2, \omega_3) = \frac{\lambda(D_1 H_2 + D_2 H_1)}{1 - \lambda D_0} \approx -\frac{K\lambda g_m Z_3(\omega_1, \omega_2, \omega_3)}{(\omega_1 + \omega_2 + \omega_3) C_L^2} \quad (12)$$

where:  $Z_3(\omega_1, \omega_2, \omega_3) = \frac{1}{3} \left( \frac{1}{\omega_1 + \omega_2} + \frac{1}{\omega_1 + \omega_3} + \frac{1}{\omega_2 + \omega_3} + \frac{1}{\omega_1} + \frac{1}{\omega_2} + \frac{1}{\omega_3} \right)$




# Verification of Volterra Series

- M1=5um/0.6um,  $K = 130\mu\text{A}/\text{V}^2$ ,  $g_o = 100\mu\text{A}/\text{V}$ ,  $g_m = 500\mu\text{A}/\text{V}$ ,  $V_{od} = 1.92\text{V}$ . Input at 0dBm(0.316V),  $f_1 = 1\text{GHz}$ ,  $f_2 = 1.1\text{GHz}$


	Volterra Analysis	Cadence Simulation
HD <sub>2</sub>	-33.7dB	-38dB
HD <sub>3</sub>	-49dB	-58dB
IM3	-34dB	-42.9dB
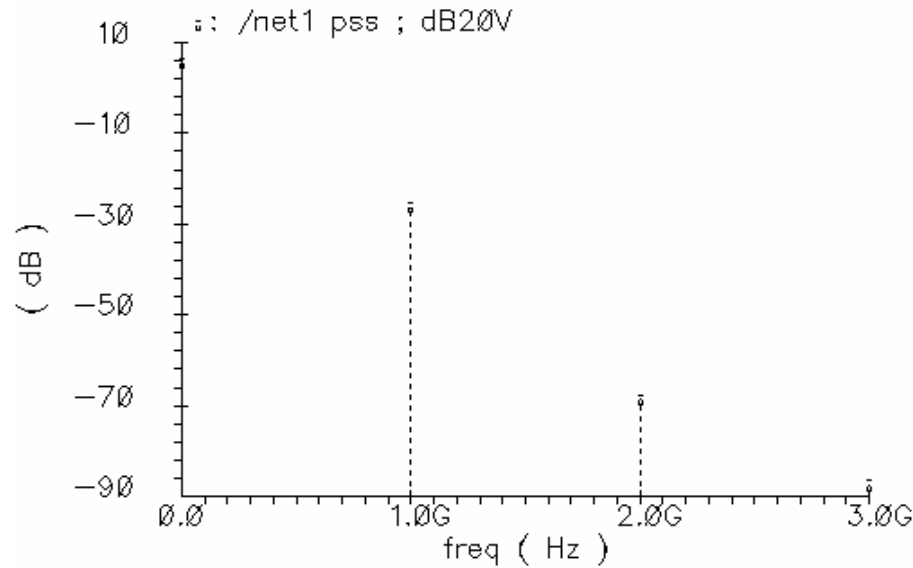
# Simulation Results


Single Point Periodic Steady State Response



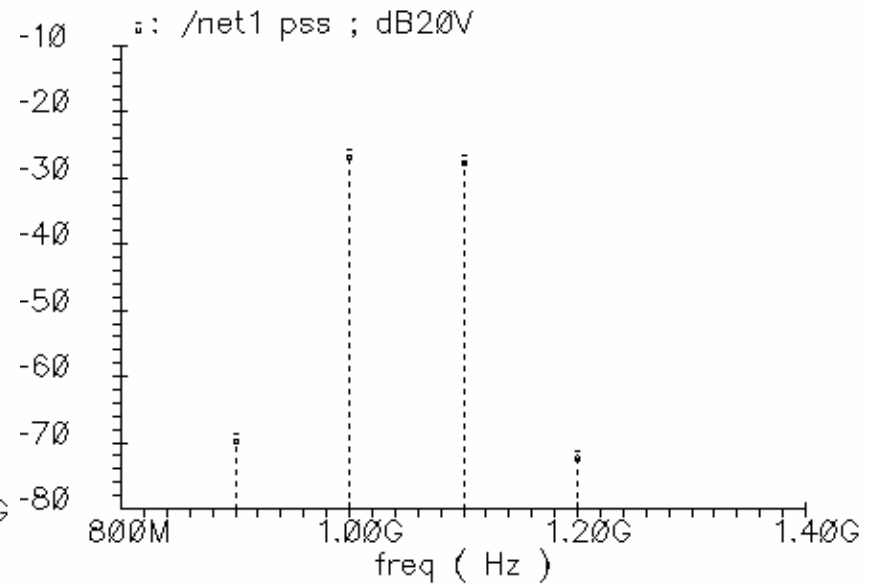Single Point Periodic Steady State Response



## Example 2: Differential Pair

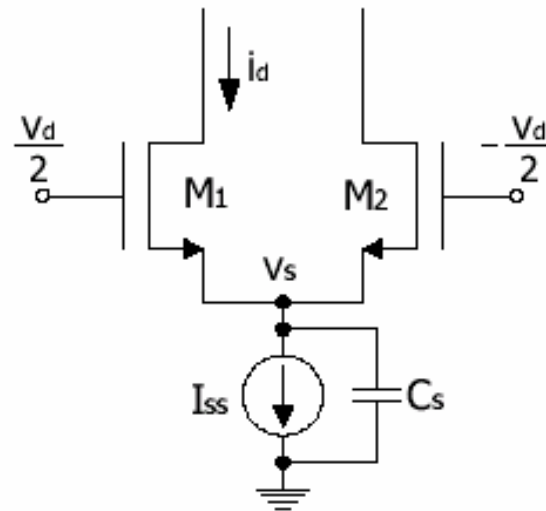

- Assume the only memory effect is introduced by the parasitic capacitance ( $C_s$ ) at node  $V_s$ , all other capacitance are ignored.
- DC bias current: 
$$I_{ss} = K (V_{GS} - V_t)^2 \quad (1a)$$
- The small signal voltages applied to the gates of M1 and M2 are  $V_d/2$  and  $-V_d/2$  respectively
- The goal is to obtain the Volterra series expansion for the small signal drain current  $i_d$  of M1 (or M2) in terms of input differential voltage  $v_d$  up to 3rd order

# Procedure:

1. Determine the Volterra series expansion of  $v_s$ :

$$\begin{aligned}v_s &= G_1 \circ v_d + G_2 \circ v_d^2 + G_3 \circ v_d^3 + \dots \\ &= v_{s1} + v_{s2} + v_{s3} + \dots\end{aligned}\tag{1b}$$

$v_{sk} = G_k \circ v_d^k$  is the k-th order term of the Volterra series of  $v_s$

2. Apply KCL law at the common source node:

$$C_s \frac{dV_s}{dt} + I_{ss} = \frac{K}{2} [(V_{gs1} - V_t)^2 + (V_{gs2} - V_t)^2]\tag{2a}$$

where  $V_s$ ,  $V_{gs1}$  and  $V_{gs2}$  can be written into DC and signal small signal terms:

$$\begin{aligned}V_s &= V_S + v_s \\ V_{gs1} &= V_{GS} + v_{gs1} & V_{gs2} &= V_{GS} + v_{gs2} \\ v_{gs1} &= \frac{v_d}{2} - v_s & v_{gs2} &= -\frac{v_d}{2} - v_s\end{aligned}\tag{2b}$$

# Procedure:

3. Combining equations (1) & (2) yields:

$$C_s \frac{dv_s}{dt} + 2g_m v_s - K v_s^2 = \frac{K}{4} v_d^2 \quad (3)$$

where  $g_m = K (V_{GS} - V_t)$

Substituting (1b) into (3) and taking phasor form of  $\frac{dv_s}{dt}$  :

$$(j\omega C_s + 2g_m) (v_{s1} + v_{s2} + v_{s3} + \dots) - K (v_{s1} + v_{s2} + v_{s3} + \dots)^2 = \frac{K}{4} v_d^2 \quad (4)$$

# Procedure:

4. Keeping only the 1<sup>st</sup> order terms of (4):

$$(j\omega C_s + 2g_m) G_1(\omega) \circ v_d = 0 \quad (5)$$

$$\longrightarrow G_1(\omega) = 0$$

$$\longrightarrow v_{s1} = 0 \quad (6)$$

5. Substituting (6) into (4), keeping only the 2<sup>nd</sup> order terms:

$$[j(\omega_1 + \omega_2) C_s + 2g_m] G_2(\omega_1, \omega_2) \circ v_d^2 = \frac{K}{4} v_d^2 \quad (7)$$

$$\longrightarrow G_2(\omega_1, \omega_2) = \frac{\frac{K}{4}}{j(\omega_1 + \omega_2) C_s + 2g_m} \quad (8)$$

Notice that  $w$  becomes  $w_1 + w_2$  because we are interested in the 2<sup>nd</sup> order terms

Because of the operator  $\circ$ , (8) consists of four equations for four different cases:

$\omega_1, \omega_2 = \pm\omega_a, \pm\omega_b$  Where  $w_1$  and  $w_2$  are symbols and  $w_a, w_b$  are the frequency components of input.



# Procedure:

6. For the 3<sup>rd</sup> order term:

$$[j(\omega_1 + \omega_2 + \omega_3) C_s + 2g_m] G_3(\omega_1, \omega_2, \omega_3) \circ v_d^3 = 0 \quad (9)$$

$$\longrightarrow G_3(\omega_1, \omega_2, \omega_3) = 0$$

Replace  $j\omega$  by  $j(\omega_1 + \omega_2 + \omega_3)$  since we are interested in the 3<sup>rd</sup> order terms

Notice that  $G_1$  always consists of one frequency component ( $\omega$ );  $G_2$  always consists of two ( $\omega_1, \omega_2$ ), and  $G_3$  consists of three ( $\omega_1, \omega_2, \omega_3$ ).

7. Higher order kernels can be calculated by repeating the above steps.

$$\begin{aligned} \text{So: } v_s &= v_{s1} + v_{s2} + v_{s3} + \dots = G_1 \circ v_d + G_2 \circ v_d^2 + G_3 \circ v_d^3 + \dots \\ &= v_{s2} + \dots = G_2(\omega_1, \omega_2) \circ v_d^2 + \dots \end{aligned}$$

# Procedure:

- 8. Our final goal is to obtain the Volterra series expansion for  $i_d$  in terms of  $v_d$ :

$$\begin{aligned}i_d &= H_1 \circ v_d + H_2 \circ v_d^2 + H_3 \circ v_d^3 + \dots \\ &= i_{d1} + i_{d2} + i_{d3} + \dots\end{aligned}$$

Using the MOS device equation containing DC and time varying components:

$$I_d + i_d = \frac{K}{2} \left( V_{GS} + \frac{v_d}{2} - v_s - V_t \right)^2 = K (V_{GS} - V_t) \cdot \left( \frac{v_d}{2} - v_s \right) + \frac{K}{2} \left( \frac{v_d}{2} - v_s \right)^2 + \frac{K}{2} (V_{GS} - V_t)^2$$

$$\rightarrow i_d = g_m \left( \frac{v_d}{2} - v_s \right) + \frac{K}{2} \left( \frac{v_d}{2} - v_s \right)^2$$

Volterra series expansion of  $i_d$  becomes:

$$i_{d1} + i_{d2} + i_{d3} + \dots = g_m \left( \frac{1}{2} v_d - v_{s2} - \dots \right) + \frac{K}{8} v_d^2 + \frac{K}{2} (v_{s2} + \dots)^2 - \frac{K}{2} v_d (v_{s2} + \dots) \quad (11)$$

# Procedure:

- 9. Keeping the 1<sup>st</sup> order term of  $v_d$  coefficients in (11):

$$i_{d1} = \frac{1}{2}g_m v_d$$

$$\rightarrow H_1(\omega) = \frac{1}{2}g_m$$

- 10. Isolating the 2<sup>nd</sup> order terms of  $v_d$  coefficients in (11):

$$i_{d2}(\omega_1, \omega_2) = \frac{K}{8}v_d^2 - g_m G_2(\omega_1, \omega_2) \circ v_d^2$$

$$\rightarrow H_2(\omega_1, \omega_2) \approx j(\omega_1 + \omega_2) \frac{K C_s}{16 g_m}$$

- 11. Separating the 3<sup>rd</sup> order terms of  $v_d$  coefficients from (11):

$$i_{d3}(\omega_1, \omega_2, \omega_3) = -\frac{K}{2}v_d v_{s2}$$

$$H_3(\omega_1, \omega_2, \omega_3) \approx -\frac{K^2}{16g_m} \left[ 1 - j(\omega_1 + \omega_2 + \omega_3) \frac{C_s}{3g_m} \right]$$

# Summary of steps to determine Volterra Series:

- **Step1.** Determine the Volterra series expansion of the intermediate variable  $v_s$  in terms of input signal  $v_d$

$$v_s = G_1 \circ v_d + G_2 \circ v_d^2 + G_3 \circ v_d^3 + \dots \quad (1)$$

- **Step2.** Using KCL and MOS device equation to express output signal  $i_d$  in terms of  $v_d$  and  $v_s$

$$i_d = \frac{K}{2} \left( \frac{v_d}{2} - v_s \right)^2 + g_m \left( \frac{v_d}{2} - v_s \right) \quad (2)$$

- **Step3.** Substitute  $v_s$  determined in(1) into (2) and derive:

$$i_d = H_1 \circ v_d + H_2 \circ v_d^2 + H_3 \circ v_d^3 + \dots$$

$H_n$  becomes a function of  $G_n$ , and  $G_n$  has been determined in step1.


# Volterra series versus Taylor series of a MOS differential pair

	Volterra Kernel	Taylor Coefficient
1st order	$\frac{1}{2}g_m$	$\frac{1}{2}g_m$
2nd order	$j(\omega_1 + \omega_2) \frac{K C_s}{16 g_m}$	0
3rd order	$-\frac{K^2}{16g_m} \left[ 1 - j(\omega_1 + \omega_2 + \omega_3) \frac{C_s}{3g_m} \right]$	$-\frac{K^2}{16g_m}$

Note that for Taylor expansion, second order distortion is 0, while Volterra series reveals the high frequency second order distortion for a differential pair.

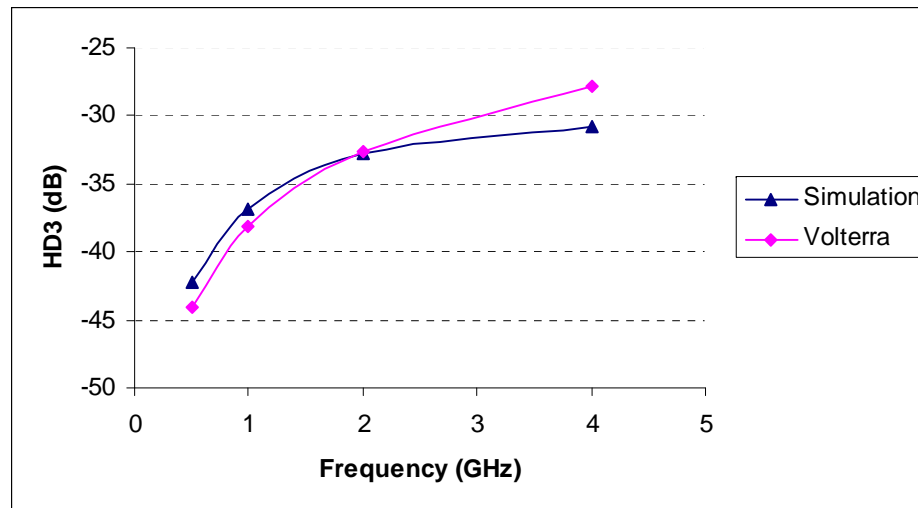
# Verification of Volterra Series

For MOS transistors with W/L=50um/0.6um, Volterra series and simulated HD3 result comparison.



$$HD3 = \frac{V_d^2 |H_3|}{4H_1}$$

# Example 3: Current Mirror

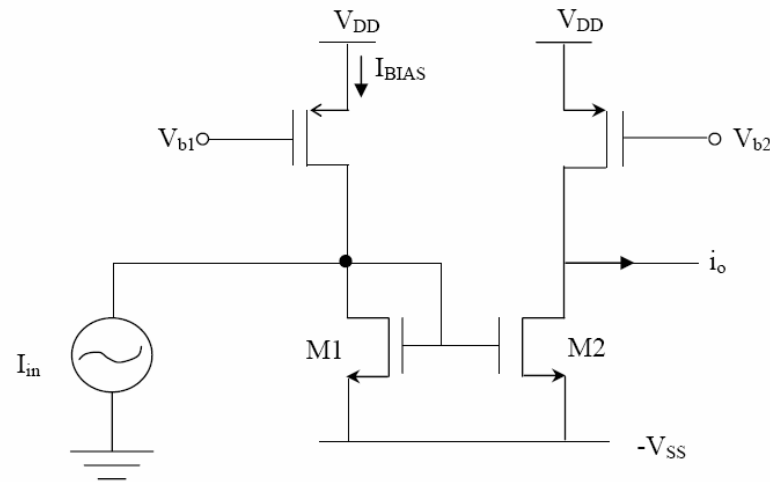

- At high frequency, the parasitic capacitance of the transistors cannot be neglected. Therefore, Volterra Series is used to model this non-linear system with memory.
- The parasitic capacitance  $C_p$  seen at the gate of M1, M2 affects the  $V_{gs}$ , which is related to the current mirror accuracy.
- The goal is to obtain the Volterra series expansion for the small signal drain current  $i_o$  of M2 in terms of input current  $i_{in}$  up to 3rd order.

# Procedure:

Follow the same steps as described in Example 1:

1. Determine the Volterra series of the gate voltage  $v_i$  first:

$$v_i = G_1 \circ I_{in} + G_2 \circ I_{2in} + G_3 \circ I_{3in} + \dots = v_{i1} + v_{i2} + v_{i3} + \dots \quad (1)$$

where  $v_{i_k} = G_k \circ I_{kin}$  is the k-th order term of the Volterra series of  $v_i$

2. Applying KCL at the gate node of M1:

$$C_p \frac{dV_i}{dt} + \frac{K}{2}(V_i - V_t)^2 = I_{in} + I_{BIAS} \quad (2)$$

where  $V_i$  can be written into DC and small signal term:

$$V_i = V_I + v_i \quad (3)$$

Also, 
$$\frac{K}{2}(V_I - V_t)^2 = I_{BIAS} \quad (4)$$



# Procedure:

3. Substituting (3) and (4) into (2) and simplifying it:

$$C_p \frac{dv_i}{dt} + g_m v_i + \frac{K}{2} v_i^2 = I_{in} \quad (5)$$

where  $g_m = K(V_I - V_t)$  is the transconductance of M1

Substituting (5) into (1) and taking the phasor form of  $\frac{dv_i}{dt}$

$$(j\omega C_p + g_m)(v_{i1} + v_{i2} + v_{i3} + \dots) + \frac{K}{2}(v_{i1} + v_{i2} + v_{i3} + \dots)^2 = I_{in} \quad (6)$$

# Procedure:

4. The Volterra kernel  $G_k$  can be obtained by equating the same order term of  $I_{in}$  at both sides of (6). Keeping only the first order terms:

$$(j\omega C_p + g_m)G_1(\omega) \circ I_{in} = I_{in} \quad (7)$$

$$\rightarrow G_1(\omega) = \frac{1}{j\omega C_p + g_m} \quad (8)$$

5. Substituting into (6), and keeping only the second order terms:

$$[j(\omega_1 + \omega_2)C_p + g_m]G_2(\omega_1, \omega_2) \circ I_{in}^2 + \frac{K}{2}G_1^2(\omega) \circ I_{in}^2 = 0 \quad (9)$$

$$\rightarrow G_2(\omega_1, \omega_2) = -\frac{\frac{K}{2}G_1^2(\omega)}{j(\omega_1 + \omega_2)C_p + g_m} = -\frac{\frac{K}{2} \frac{1}{(j\omega C_p + g_m)^2}}{j(\omega_1 + \omega_2)C_p + g_m} \quad (10)$$
$$\approx -\frac{K}{2g_m^3} \left[1 - j(\omega_1 + \omega_2) \frac{C_p}{g_m}\right] \left(1 - \frac{2j\omega_1 C_p}{g_m}\right)$$

# Procedure:

6. Factoring out the third order terms from (6):

$$[j(\omega_1 + \omega_2 + \omega_3)C_p + g_m]G_3(\omega_1, \omega_2, \omega_3) \circ I_{3in} + K G_2(\omega_1, \omega_2)G_1(\omega_1) \circ I_{3in} = 0$$

$$\begin{aligned} \rightarrow G_3(\omega_1, \omega_2, \omega_3) &= -\frac{K G_2(\omega_1, \omega_2)G_1(\omega_1)}{j(\omega_1 + \omega_2 + \omega_3)C_p + g_m} \\ &\approx \frac{K^2}{2g_m^4} \left[1 - j(\omega_1 + \omega_2)\frac{C_p}{g_m}\right] \left(1 - \frac{2j\omega_1 C_p}{g_m}\right) \left[1 - j(\omega_1 + \omega_2 + \omega_3)\frac{C_p}{g_m}\right] \end{aligned} \quad (11)$$

7. Now,  $v_i$  has been expanded into Volterra series up to the third order. Our final goal is to obtain the Volterra series expansion for  $i_o$  in terms of  $I_{in}$ :

$$i_o = H_1 \circ I_{in} + H_2 \circ I_{2in} + H_3 \circ I_{3in} + \dots = i_{o1} + i_{o2} + i_{o3} + \dots \quad (12)$$

# Procedure:

8. The small signal output current  $i_o$  can be related to  $v_i$  as:

$$i_o = g_{m2} v_i \quad (13)$$

Substituting (1) and (12) into (13):

$$i_{o1} + i_{o2} + i_{o3} = g_{m2} G_1(\omega_1) \circ I_{in} + g_{m2} G_2(\omega_1, \omega_2) \circ I_{2in} + g_{m2} G_3(\omega_1, \omega_2, \omega_3) \circ I_{3in}$$

$$\rightarrow H_1(\omega) = g_{m2} G_1(\omega_1) \approx \frac{g_{m2}}{g_{m1}} \left(1 - j\omega_1 \frac{C_p}{g_{m1}}\right)$$

$$H_2(\omega_1, \omega_2) = g_{m2} G_2(\omega_1, \omega_2) \approx -\frac{K g_{m2}}{2 g_{m1}^3} \left[1 - j(\omega_1 + \omega_2) \frac{C_p}{g_{m1}}\right] \left(1 - \frac{2 j \omega_1 C_p}{g_{m1}}\right)$$

$$H_3(\omega_1, \omega_2, \omega_3) = g_{m2} G_3(\omega_1, \omega_2, \omega_3) \\ \approx \frac{K^2 g_{m2}}{2 g_{m1}^4} \left[1 - j(\omega_1 + \omega_2) \frac{C_p}{g_{m1}}\right] \left(1 - \frac{2 j \omega_1 C_p}{g_{m1}}\right) \left[1 - j(\omega_1 + \omega_2 + \omega_3) \frac{C_p}{g_{m1}}\right]$$

# Verification of Volterra Series




Assume a current gain of 4, use long channel length to minimize channel length modulation effect. Choose  $M1 = 2\mu\text{m}/1\mu\text{m}$ ,  $M2 = 4*2\mu\text{m}/1\mu\text{m}$ ,  $I_{\text{BIAS}} = 84.4\mu\text{A}$ ,  $C_p \sim 90\text{fF}$ ,  $g_{m1} = 176 \mu\text{A/V}$ ,  $g_{m2} = 705 \mu\text{A/V}$ ,  $I_{\text{in}} = A_1 \cos w_1 t + A_2 \cos w_2 t$ , while  $w_1 = 910 * 2\pi\text{ MHz}$ ,  $w_2 = 900 * 2\pi\text{ MHz}$ ,  $A_1 = A_2 = I_{\text{BIAS}}/10 = 8.441 \mu\text{A}$ , we can get:

$$IM3 = \frac{3A_2^2}{4} \left| \frac{H_3(jw_1, -jw_2, -jw_2)}{H_1(jw_1)} \right| = 62\text{dB}$$

$$IIP3 = P_{\text{in}} + IM_3/2 = -91.5\text{dBm} + 62/2 = -60.5\text{dBm}$$

$$1\text{-dB compression point} = IIP3 - 10\text{dB} = -70.5\text{dBm}$$

# Simulation Results

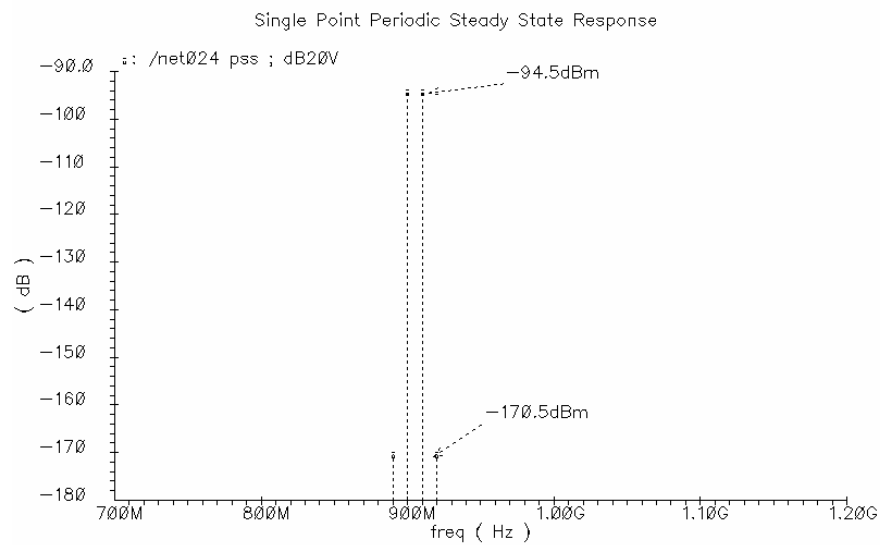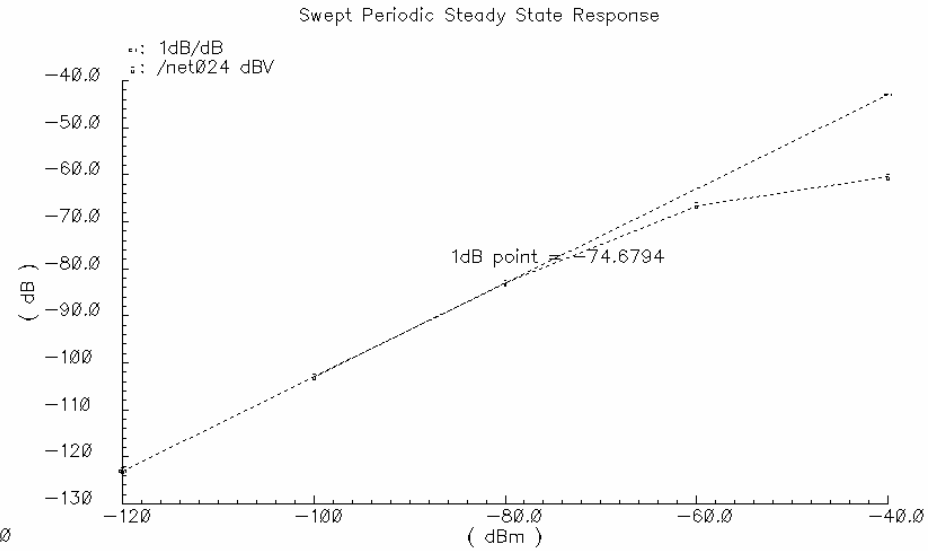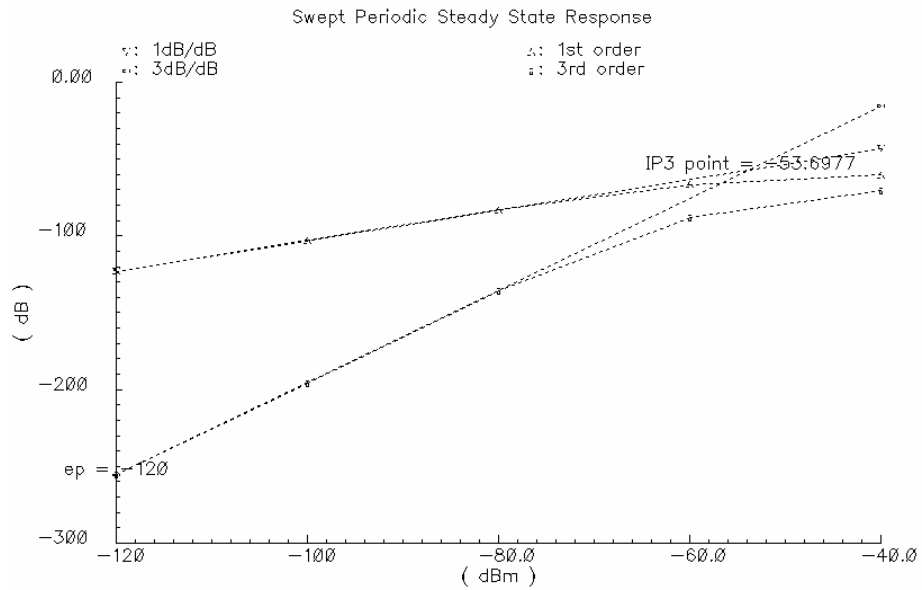



# Comparison between Volterra analytical results and Cadence simulation

	Volterra analysis	Cadence simulation
IIP3	-60.5dBm	-53.7dBm
IM3	62dB	76dB
1-dB point	-70.5dBm	-74.7dBm





# Volterra kernels:

- The Volterra series analysis of Gilbert mixer follows the Volterra series analysis of a differential pair
- The Volterra kernels for the V-I conversion transistors are:

$$H_1(\omega) = \frac{1}{2}g_m$$

$$H_2(\omega_1, \omega_2) \approx j(\omega_1 + \omega_2) \frac{K C_s}{16 g_m}$$

$$H_3(\omega_1, \omega_2, \omega_3) \approx -\frac{K^2}{16g_m} \left[ 1 - j(\omega_1 + \omega_2 + \omega_3) \frac{C_s}{3g_m} \right]$$

# Finding IM3 and HD3

- the linearity expression for Gilbert mixer cell is:

$$HD_3 = \frac{1}{4} \frac{|H_3(j\omega_1, j\omega_1, j\omega_1)|}{|H_1(j\omega_1)|} A_{rf}^2$$

$$IM_3 = \frac{3}{4} \frac{|H_3(j\omega_1, j\omega_1, j\omega_2)|}{|H_1(j\omega_1)|} A_{rf}^2$$

- IM3 is caused by adjacent channel interference
- $\omega_2$  is defined to be at  $-\omega_1 - \Delta\omega$  such that the 3<sup>rd</sup> order nonlinearity term  $2\omega_1 + \omega_2$  will generate a term at  $\omega_1 - \Delta\omega$
- $A_{rf}$  should be replaced by  $A_{interference}$

# Low frequency approximation

$$H_3(\omega_1, \omega_2, \omega_3) \approx -\frac{K^2}{16g_m} \left[ 1 - j(\omega_1 + \omega_2 + \omega_3) \frac{C_s}{3g_m} \right]$$

$$\omega_1 = \omega_2 = \omega_3 = 0 \rightarrow \frac{-K}{16(V_{GS} - V_t)}$$

$$H_1(\omega) = \frac{1}{2}g_m = \frac{K}{2}(V_{GS} - V_t)$$

$$HD_3 = \frac{1}{4} \frac{|H_3(\omega_1, \omega_1, \omega_1)|}{|H_1(j\omega_1)|} A_{rf}^2 = \frac{A_{rf}^2}{32} \frac{K}{I_{SS}}$$

- For low frequency (no memory),  $HD_3$  agrees with Taylor series expansion
- Do the same for IM3 and it would agree with Taylor series expansion

# IM3 and HD3

- For intermediate frequency:  $j(\omega_1 + \omega_2)C_s \ll 2K(V_{GS} - V_t)$

$$HD3 = \sqrt{\frac{K}{I_{SS}} \frac{A_{rf}^2}{32 \cdot (V_{GS} - V_t)}} \left| 1 - \frac{j(2\omega_1)C_s}{2K(V_{GS} - V_t)} \right|$$

$$IM3 = \frac{3A_{interference}^2}{32(V_{GS} - V_t)^2} \left[ \left| 1 - \frac{2}{3} \frac{j(\omega_1)C_s}{2K(V_{GS} - V_t)} \right| \right]$$

$$IM_3 \neq 3HD_3$$



## When $V_{LO}$ is switching...

- The mixer is no longer a time-invariant system
- The high-frequency distortion still dominated by V-I conversion
- To incorporate switching effect, multiply the output by the Fourier series representation of a square wave
- Frequency of the 1<sup>st</sup> and 3<sup>rd</sup> order products is shifted by  $f_{LO}$ , Amplitude are reduced by  $1/\pi$ .
- HD3 and IM3 remain unchanged


# Gilbert Mixer $IM_3$ Verification

Assume a Gilbert Mixer has V-I conversion transistor  $M1=M2=50\mu\text{m}/0.6\mu\text{m}$ . Let  $f_{\text{rf}}=2\text{GHz}$ , two interference signal with 0dBm power (0.316V) at  $2\text{GHz}(\omega_1)$  and  $2.001\text{GHz}(\omega_2)$ .  $C_s \approx 0.1\text{pF}$ . Make  $V_{\text{GS}}-V_t = 0.387\text{V}$ ,  $K=6250 \text{ uA/V}^2$ , thus  $g_m = 2.42\text{mA/V}$

Theoretically: 
$$IM_3 = \frac{3}{4} \frac{|H_3(\omega_1, \omega_1, \omega_2)|}{|H_1(j\omega_1)|} A_{\text{rf}}^2 = -24.0\text{dB}$$
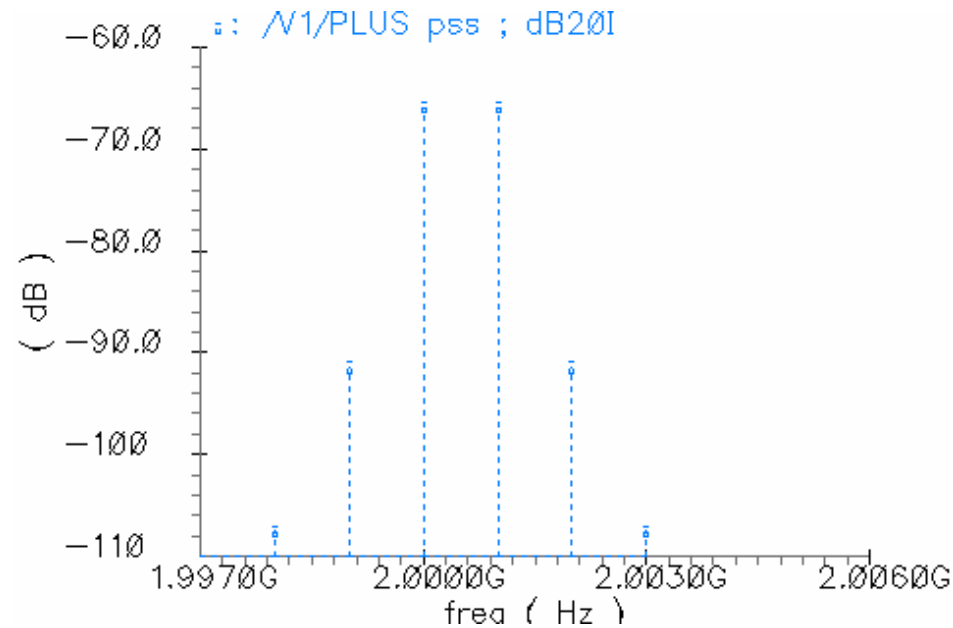
# Simulation result

- Gilbert cell simulation result: with two tones at 2GHz and 2.001GHz, the input amplitude of each tone is 0dBm.



IM3 is around -25.5 dB from simulation. The deviation error is 1.5dB(5.9%)

# HD<sub>2</sub>

Incorporating Memory:  $HD_2 = \frac{A_{rf} |H_2|}{2|H_1|} = -32dB$

Ignoring memory:  $HD_2 = \frac{A_{rf} a_2}{2a_1} = 0$

Volterra series analysis predicts that RF feedthrough will still be Present in a balance mixer with zero mismatch!





# Conclusions

- Taylor series analysis cannot calculate the distortion correctly at high frequency due to memory effect.
- Volterra series can calculate the high-frequency-low-distortion terms for any weakly non-linear time-invariant system with memory effect.
- Volterra series may diverge when nonlinearity is strong
- Volterra series are applied to four basic circuit examples and theoretical results agrees with simulation



# Reference

- W. Sansen, “Distortion in elementary transistor circuits,” IEEE Trans. On Circuits and Systems-II: Analog and Digital Signal Processing, vol. 46, pp. 315~325, March 1999.
- B. Leung, “VLSI for Wireless Communication”. Upper Saddle River, N.J.: Prentice Hall, 2002.
- B. Kim, J.-S. Ko, and K. Lee, “Highly linear CMOS RF MMIC amplifier using multiple gated transistors and its volterra series analysis,” IEEE MTT-S Int.Microwave Symp. Dig., vol. 1, pp. 515~518, May 2001.