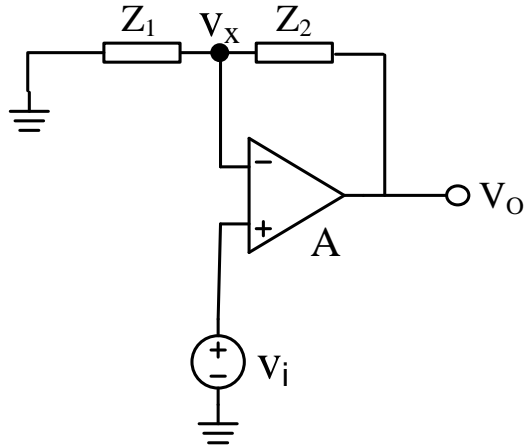


Analog and Mixed-Signal Center

FEEDBACK CONCEPTS IN OP AMPS CIRCUITS

ECEN – 457 (ESS)

FEEDBACK CONCEPTS IN OP AMPS CIRCUITS





From Circuit

$$A_{\text{Closed Loop}} = \frac{1 + \frac{Z_2}{Z_1}}{1 + \frac{1}{A} \left(1 + \frac{Z_2}{Z_1} \right)} \quad (1)$$

Where
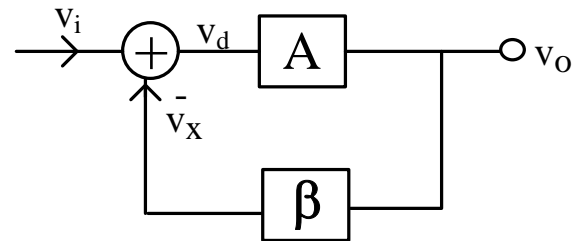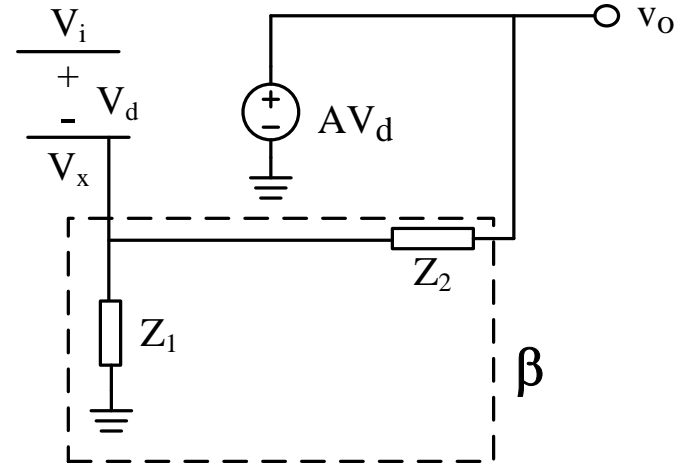
$$\beta = \left(1 + \frac{Z_2}{Z_1} \right)^{-1}$$



From Block Diagram

$$A_{\text{CL}} = \frac{v_o}{v_i} = \frac{A}{1 + \beta A} \quad (2)$$

$$\frac{v_o}{v_i} = \frac{A}{1 + T} \quad ; \quad T = \beta A$$

From (1)

$$A_{\text{Closed Loop}} = \frac{\frac{1}{\beta}}{1 + \frac{1}{A\beta}} = \frac{A}{1 + A\beta}$$

$$A_{\text{Closed Loop}} = A_{\text{CL}} = \frac{A}{1 + A\beta} \Big|_{A\beta \gg 1} \cong \frac{A}{A\beta} = \frac{1}{\beta} = 1 + \frac{Z_2}{Z_1}$$

Sensitivity Concept

$$S_x^f = \frac{\partial f}{\partial x} \frac{x}{f}$$

This will be a metric to discuss effects of process variations on closed loop gain.

Let $f = A_{CL}$ and $x = A$, thus

$$S_A^{A_{CL}} = \frac{\partial A_{CL}}{\partial A} \frac{A}{A_{CL}}$$

$$\frac{\partial A_{CL}}{\partial A} = \frac{(1 + \beta A) - A\beta}{(1 + \beta A)^2} = \frac{1}{(1 + \beta A)^2}$$

$$S_A^{A_{CL}} = \frac{1}{(1 + \beta A)^2} \frac{A}{\frac{A}{1 + \beta A}} = \frac{1}{1 + \beta A} = \frac{1}{1 + T}$$

We can write also as

$$\frac{\Delta A_{CL}}{A_{CL}} \cong S_A^{A_{CL}} \frac{\Delta A}{A}$$

EXAMPLE: We want to know how much change in the closed loop gain will occur due to changes in the feedback component or/and in the open loop gain A.

$$A = 10^5$$

$$\Delta A = \pm 10\%$$

$$\beta = 10^{-3}, T = A\beta = 10^2$$

Thus

$$\frac{\Delta A_{CL}}{A_{CL}} = \frac{1}{1+T} \left(\frac{\pm \Delta A}{A} \right) = \frac{\pm 1}{1+100} \times 10\% = \pm 0.099\%$$

Exercise. Try for $\beta = 4 \times 10^{-3}$, $A = 2 \times 10^5$ and $\Delta A = \pm 25\%$

What is

$$\frac{\Delta A_{CL}}{A_{CL}} ?$$

$$A_{CL}$$