

Op Amp Non-Idealities

What is the relation between GB and ω_u ?

Recall

$$A(s) = \frac{A_o \omega_{3dB}}{s + \omega_{3dB}} \Big|_{s=j\omega} = \frac{A_o \omega_{3dB}}{j\omega + \omega_{3dB}} = \frac{GB}{j\omega + \omega_{3dB}}$$

$$|A(j\omega_u)| = 1 \quad ; \quad \text{yields} \quad \omega_u^2 + \omega_{3dB}^2 = GB^2$$

thus


$$\omega_u = \left\{ GB^2 - \omega_{3dB}^2 \right\}^{1/2} = \left\{ A_o^2 - 1 \right\}^{1/2} \omega_{3dB}$$

In many cases $GB \gg \omega_{3dB}^2$, therefore the unity gain frequency is approximated as:

$$\omega_u \cong GB$$

Let us look now the GB for the closed loop cases (inverter and non-inverting).

Gain Bandwidth Product and Unity Gain

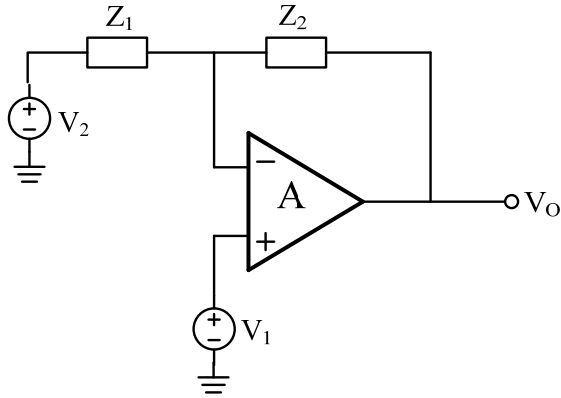

$$V_o = \frac{-\frac{Z_F}{Z_1} V_2 + \left(1 + \frac{Z_F}{Z_1}\right) V_1}{1 + \frac{1}{A} \left(1 + \frac{Z_F}{Z_1}\right)} \quad \Bigg|_{A=GB/s} = \frac{-\frac{Z_F}{Z_1} V_2 + \left(1 + \frac{Z_F}{Z_1}\right) V_1}{1 + \frac{s}{GB} \left(1 + \frac{Z_F}{Z_1}\right)}$$

For resistive components $Z_F=R_F$, $Z_1=R_1$

The 3dB cut-off frequency is given by

$$\omega_{3dB} = \frac{GB}{1 + \frac{R_2}{R_1}} = \beta GB \quad (1)$$

This can be written for the non-inverting and inverting case as

$$\omega_{3dB} = \frac{GB}{A_{NI}} = \beta GB \quad (2a)$$

$$\omega_{3dB} = \frac{GB}{1 + A_I} \quad (2b)$$

Where A_{NI} , A_I are the non-inverting and inverting ideal gains.

The corresponding closed loop gain-bandwidth product become

$$GB_{CL-non} = A_{NI} \omega_{3dB} = \frac{A_{NI}}{A_{NI}} GB = GB \quad (4)$$

$$GB_{CL-INV} = A_I \omega_{3dB} = A_I \frac{GB}{1 + A_I} = \frac{A_I}{1 + A_I} GB = (1 - \beta)GB \quad (5)$$

Observe that for equal closed loop gains, the closed loop gain-bandwidth product of the Non-inverting configuration is larger.

Let us calculate the unity gain frequency for both conguration.

Inverting

$$\left| \frac{-\frac{R_F}{R_1}}{1 + \frac{j\omega_u}{GB} \left(1 + \frac{R_F}{R_1}\right)} \right| = 1 \Rightarrow \pm \left(\frac{R_F}{R_1} \right)^2 = 1 + \left(1 + \frac{R_F}{R_1} \right)^2 \frac{\omega_u^2}{GB^2}$$

Therefore

$$\omega_u = \frac{GB \sqrt{\left(\frac{R_F}{R_1} \right)^2 - 1}}{1 + \frac{R_F}{R_1}} = GB \sqrt{1 - 2\beta}$$

Non-Inverting

$$\left| \frac{1 + \frac{R_F}{R_1}}{1 + \frac{j\omega_u}{GB} \left(1 + \frac{R_F}{R_1} \right)} \right| = 1$$

yields

$$\omega_u = \frac{GB \sqrt{\left(1 + \frac{R_F}{R_1} \right)^2 - 1}}{1 + \frac{R_F}{R_1}} = GB \sqrt{1 - \beta^2}$$

Note that for a gain of -2


$$\omega_{3dB} = \frac{GB}{3} \text{ and } \omega_u = \frac{\sqrt{3}}{3} GB = 0.577GB$$

And for a gain of +2

$$\omega_{3dB} = \frac{GB}{2} \text{ and } \omega_u = \frac{\sqrt{3}}{2} GB = 0.866GB$$

UGF versus Gain

(Inverting/Non-Inverting Amplifiers)

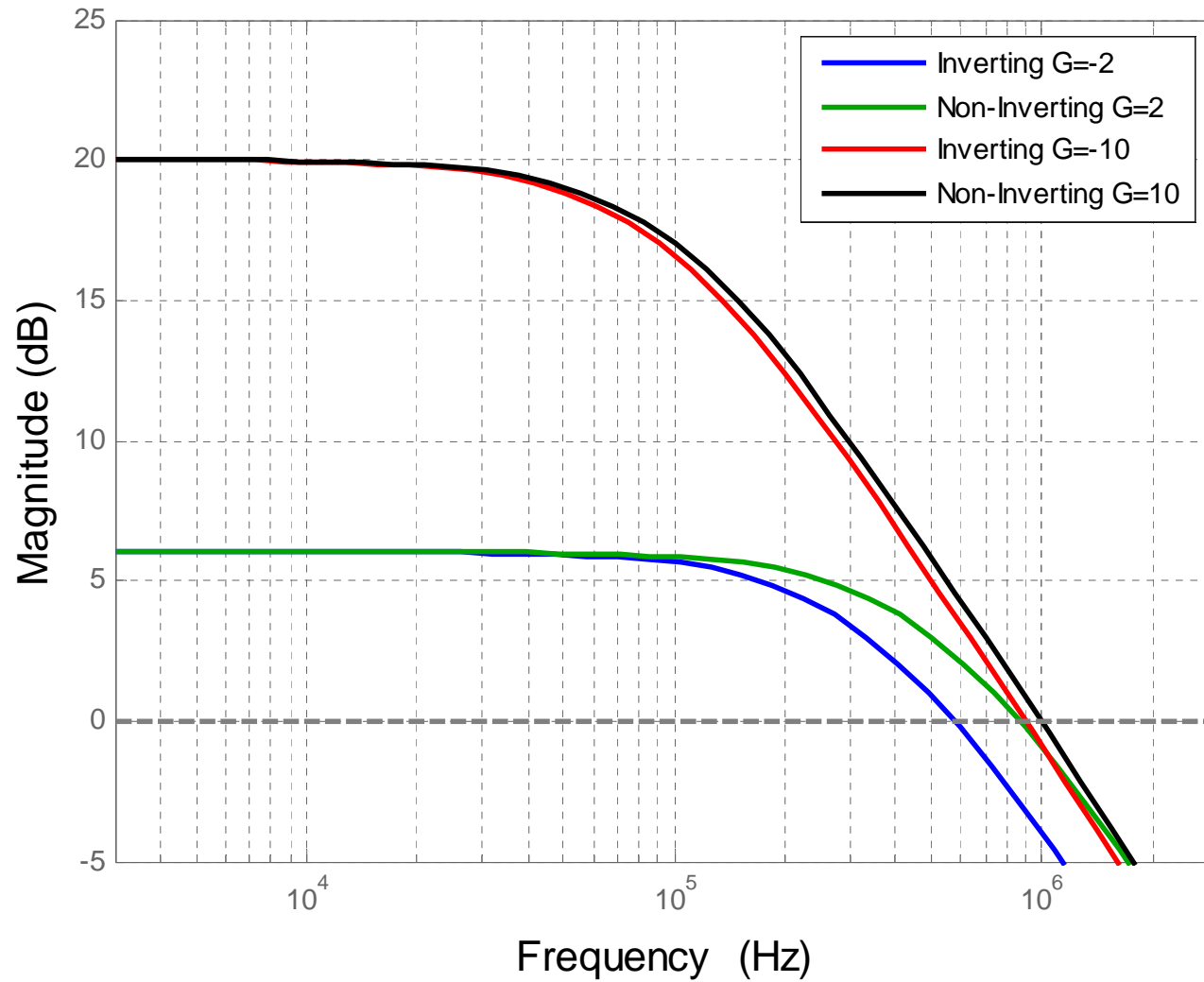

Comparison of the Results

Topology	Gain	GBW	UGF	% Error
Inverting	2	667kHz	577kHz	15.6
Non-inverting	2	1MHz	866kHz	15.5
Inverting	10	909kHz	905kHz	0.4
Non-inverting	10	1MHz	995kHz	0.5