

FALL 2013

Name _____

ECEN 457 (ESS)

FINAL EXAM


Problem	Maximum	Yours
1	4	
2	4	
3	4	
4	4	
5	4	
Extra Credit*	1	
Total	21	

***Provide the list of five fundamental concepts learned in the course**

Problem 1.


a.) Write the nodal equations in matrix form ($YV=I$) of the circuit shown below.

b.) Obtain $G_M = \frac{i_o}{V_i}$ when $V_3=0$

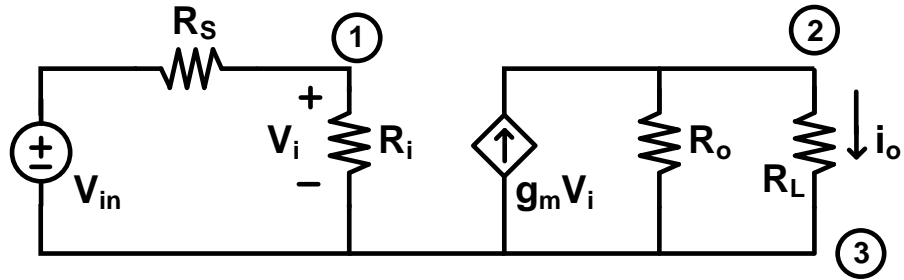

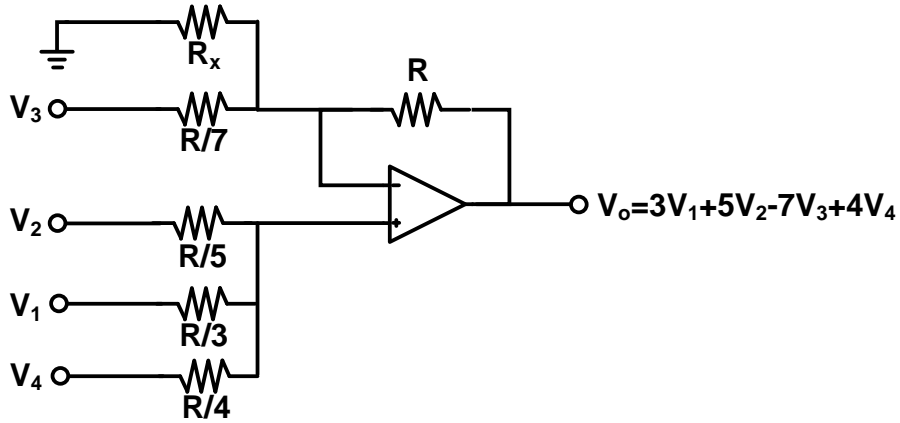Problem 2.

If the output voltage V_o must be equal to $3V_1+5V_2-7V_3+4V_4$



Determine the value of R_x to satisfy the expression of V_o .

Problem 3.

Design a low frequency non-inverting amplifier with an ideal voltage gain K . Assume the open loop gain of the Op Amp is A_o which yields a closed loop transfer function $H(s)$.

$$H(s) = \frac{V_o(s)}{V_{in}(s)} = K(1 - \varepsilon_m)$$

Determine the expression of ε_m by approximating in $H(s)$ by

$$\frac{K}{1+x} \cong K(1-x) \quad \text{when } x \ll 1$$

Also determine the minimum value (expression) of A_o that meets a given error deviation ε_m .

ε_m	
Min A_o	

Problem 4.

Propose a macromodel with passive elements and dependent sources that represent


$$H(s) = K \cdot \frac{1 - \frac{s}{\omega_z}}{\left(1 + \frac{s}{\omega_{p1}}\right)\left(1 + \frac{s}{\omega_{p2}}\right)}$$

Problem 5. Plot the open-loop gain $A(s)$ and $\left|\frac{1}{\beta}\right|$.

Determine $\frac{1}{\beta}$, ROC, and ϕ_m for the 4 cases.

Here,
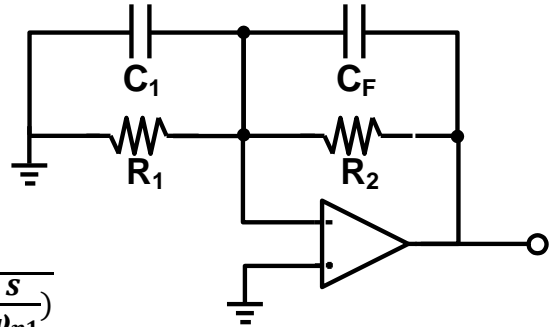
$$\frac{1}{\beta} = k \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_p}}, A(s) = \frac{A_o}{\left(1 + \frac{s}{\omega_{p1}}\right)\left(1 + \frac{s}{\omega_{p2}}\right)\left(1 + \frac{s}{\omega_{p3}}\right)}$$



$\omega_{p1} = 10\text{rad/s}$, $\omega_{p2} = 1\text{krad/s}$, and $\omega_{p3} = 100\text{krad/s}$

$A_o = 10^4$, $R_1 = 100\text{k}\Omega$, and $R_2 = 300\text{k}\Omega$

CASE	$\frac{1}{\beta}$	ROC	ϕ_m
a) $C_1=0$, $C_F=0$			
b) $C_1=0$, $C_F=10\text{nF}$			
c) $C_1=10\text{nF}$, $C_F=0$			
d) $C_1=10\text{nF}$, $C_F=10\text{nF}$			

Extra Credit

List the five most fundamental concepts you learned in this course.

1.

2.

3.

4.

5.