



Lecture 2: Voltage References/Regulators

ECEN 457(ESS): Op-Amps and Applications
Analog & Mixed-Signal Center
Texas A&M University

Agenda

- **Last lecture**
 - Motivation
 - Important Definitions
- **Today**
 - Voltage References
 - Bandgap Voltage Reference
 - Voltage Regulators
 - Shunt Regulator
 - Linear Regulators

Voltage References

- Thermal stability is very important in voltage references
 - IC components are strongly influenced by temperature
- Silicon pn junction, which forms the basis for diodes and BJTs.
 - Its forward-bias voltage V_D and current I_D are related:

$$V_D = V_T \ln(I_D / I_S)$$

where V_T is the thermal voltage and I_S is the saturation voltage.

- Their expressions are:

$$V_T = kT / q \quad I_S = BT^3 \exp(-V_{G0} / V_T)$$

where $k = 1.381 \times 10^{-23}$ is Boltzmann's constant, $q = 1.602 \times 10^{-19}$ C is the electron charge, T is the absolute temperature, B is a proportionality constant, and $V_{G0} = 1.205$ V is the bandgap voltage for silicon.

- The TC of the thermal voltage is:

$$TC(V_T) = k/q = 0.0862 \text{ mV} / \text{C}$$

- The TC of the junction voltage V_D at a given bias I_D is $TC(V_D) = \frac{\partial V_D}{\partial T}$

$$TC(V_D) = \frac{\partial V_T}{\partial T} \ln(I_D / I_S) + V_T \frac{\partial \ln(I_D / I_S)}{\partial T} = V_D / T - V_T \frac{\partial (3 \ln T - V_{G0} / V_T)}{\partial T}$$

$$TC(V_D) = - \left(\frac{V_{G0} - V_D}{T} - \frac{3k}{q} \right)$$

Assuming $V_D = 650 \text{ mV}$ at 25°C , we get $TC(V_D) \cong -2.1 \text{ mV}/^\circ\text{C}$.

Bandgap Voltage Reference

- Advantage:
 - Low voltage ($V_{DD} < 5V$)
- Based on the idea of adding the voltage drop V_{BE} of a base emitter junction, which has negative TC, to a voltage KV_T proportional to the thermal voltage V_T , which has a positive TC.

$$V_{BG} = K \cdot V_T + V_{BE}$$

$$TC(V_{BG}) = K \cdot TC(V_T) + TC(V_{BE})$$


So $TC(V_{BG}) = 0$

Thus, we need $K = -\frac{TC(V_{BE})}{TC(V_T)}$

$$K = -\frac{V_{G0} - V_{BE}}{V_T} + 3$$

$$V_{BG} = \left[\left(\frac{V_{G0} - V_{BE}}{V_T} \right) + 3 \right] \cdot V_T + V_{BE} = V_{G0} + 3V_T$$

Bandgap voltage reference

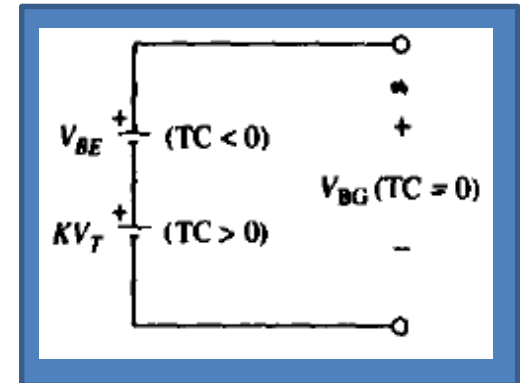

At 25°C we have $V_{BG} = 1.205V + 3 \times 25.7mV = 1.282V!$

Bandgap Voltage Reference (Brokaw)

- Based on two BJTs of different emitter areas.
- The emitter area of Q_1 is n times as large as the emitter area A_E of Q_2 .
- Thus, the saturation currents satisfy $I_{s1}/I_{s2} = n$.


$$I_{c1} = \frac{V_{BE2} - V_{BE1}}{R_3} = \frac{V_T [\ln(I_{c2}/I_{s2}) - \ln(I_{c1}/I_{s1})]}{R_3} = \frac{V_T \ln(I_{c2}I_{s1}/I_{c1}I_{s2})}{R_3} = \frac{V_T \ln(n)}{R_3}$$

$$V_{BG} = V_{BE2} + (I_{c1} + I_{c2}) \cdot R_4 = V_{BE2} + 2 \cdot I_{c1} \cdot R_4 = V_{BE2} + \left[2 \frac{R_4}{R_3} \ln(n) \right] \cdot V_T$$


$$V_{BG} = V_{BE2} + k \cdot V_T$$

where $k = 2 \frac{R_4}{R_3} \ln(n)$
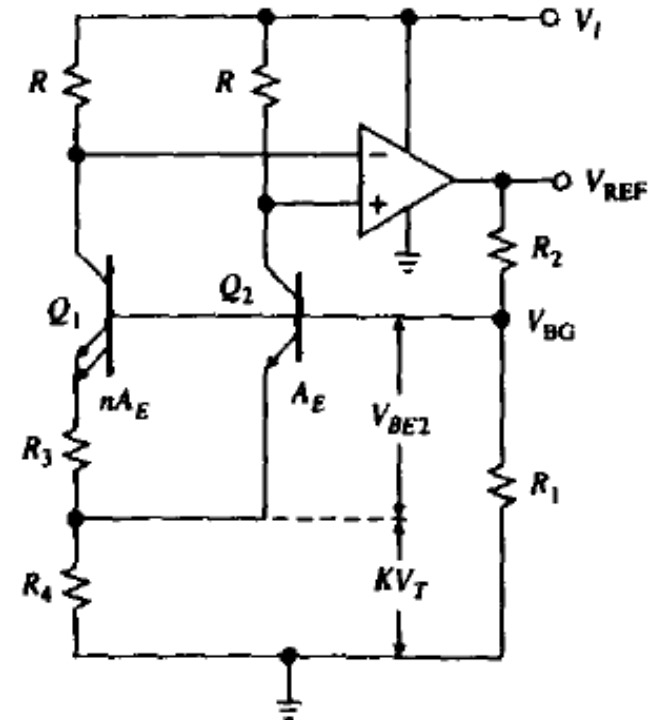
$$V_{REF} = \left(1 + R_2/R_1\right) V_{BG}$$





Shunt Voltage Regulator

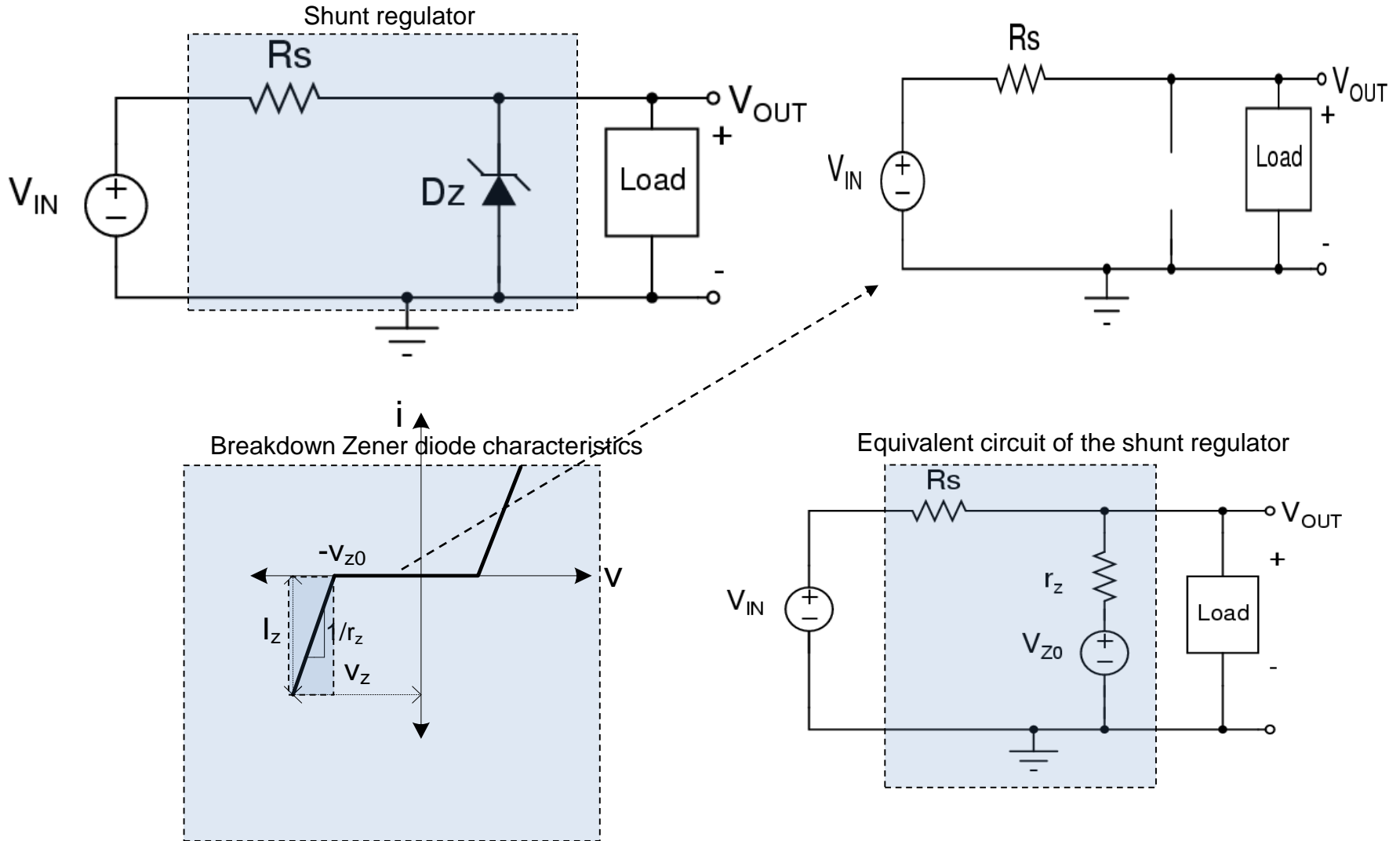

To function as a regulator, the diode must operate well within the breakdown region under all possible line and load regulation. In particular, I_z must never be allowed to drop below some safety value $I_{z(min)}$.

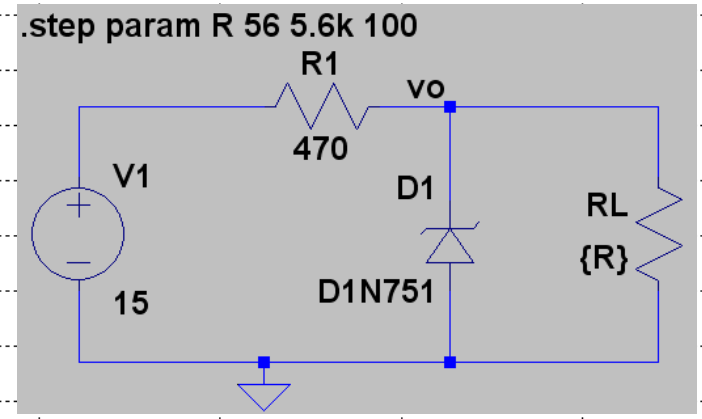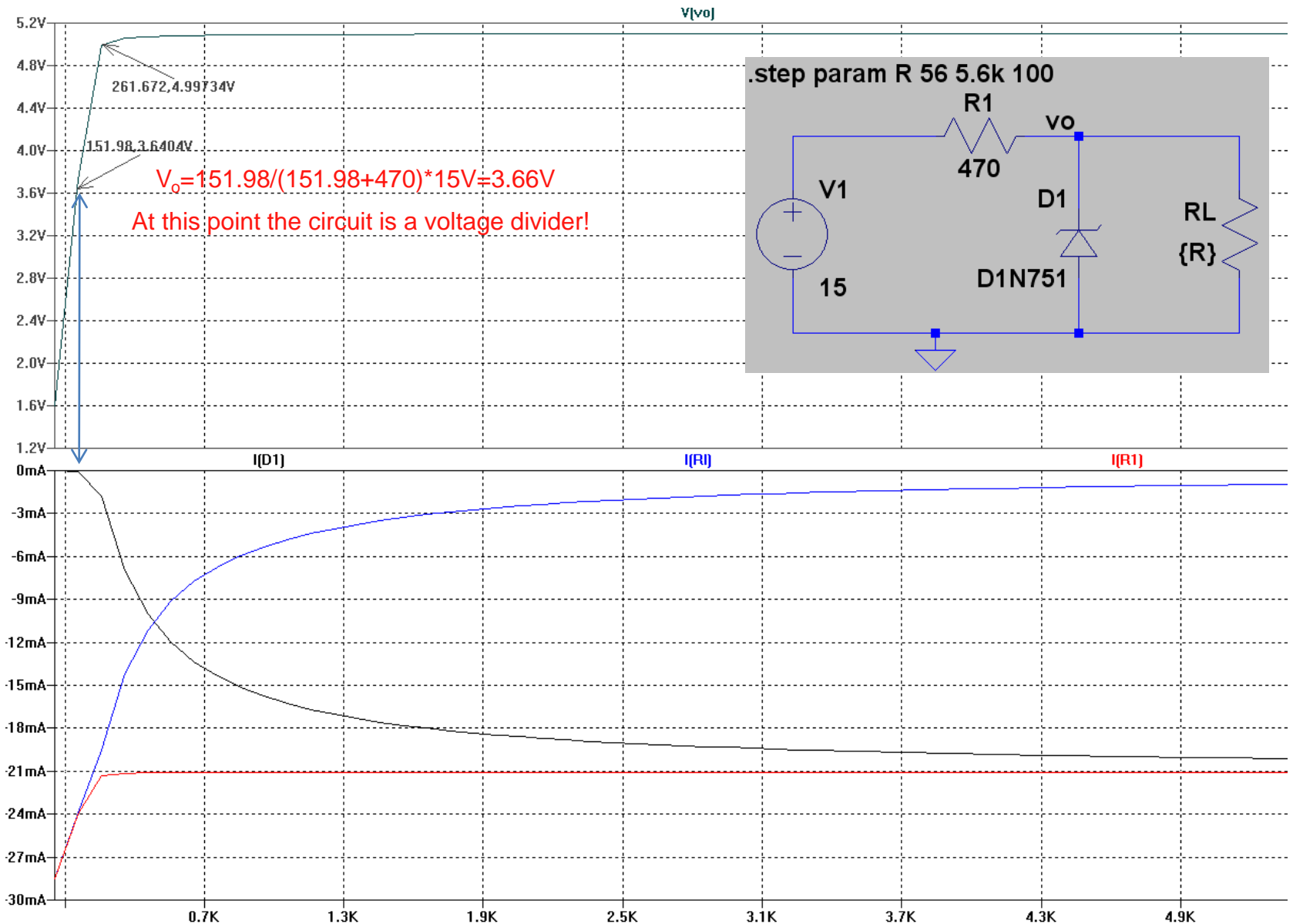Shunt Voltage Regulator (Load Regulation)




Design Approach

$$1) V_{Z0} = V_Z - r_z I_z$$

$$2) R_s (I_{z(\min)} + I_{o(\max)}) \leq V_{I(\min)} - V_{Z0} - r_z I_{z(\min)}$$
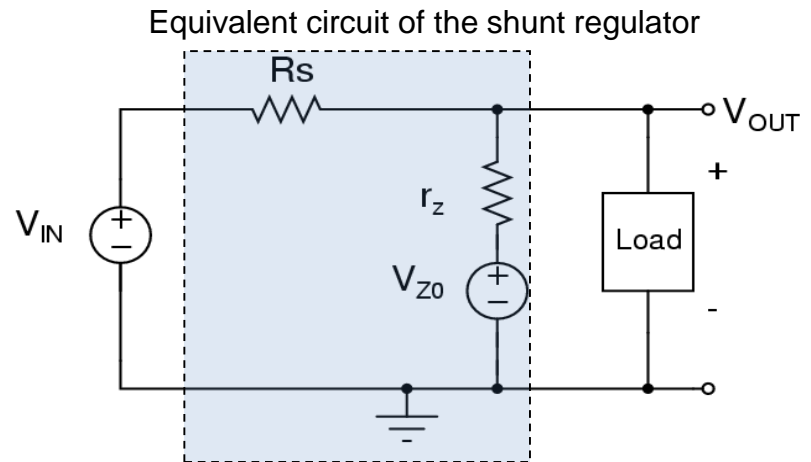
$$3) I_{Z(\min)} \cong \frac{I_{o(\max)}}{4}$$



Compromise between the need to ensure proper worst-case operation and avoid excessive power wastage.

Applying superposition principle, we find:

$$V_{OUT} = \frac{r_z}{R_s + r_z} V_{IN} - \frac{R_s}{R_s + r_z} V_{Z0} - (r_z \parallel R_s) I_{OUT}$$

$$\text{Line - regulation} = \frac{r_z}{R_s + r_z}$$

$$\text{Load - regulation} = -(r_z \parallel R_s)$$

Example 11.3

- A raw voltage $10V \leq V_{IN} \leq 20V$ is to be stabilized by a 6.8-V, 0.5-W, 10- Ω Zener diode and is to feed a load with $0 \leq I_{OUT} \leq 10mA$. (a) Find a suitable value for R_s , and estimate the line and load regulation. (b) Estimate the effect of the full-scale changes of V_{IN} and I_{OUT} on V_{OUT} .

(a) Let $I_{Z(\min)} \cong \frac{I_{OUT(\max)}}{4} = 2.5mA$

$$R_s \leq (10 - 6.43 - 10 \cdot 2.5mA) / (2.5mA + 10mA) = 0.284k\Omega$$

$$R_s = 270\Omega$$

$$\text{Line - regulation} = \frac{10}{270 + 10} = 35.7mV/V$$

$$\text{Load - regulation} = -(10 \parallel 270) = -9.64mV/mA$$

(b) Changing V_{IN} from 10V to 20V gives: $\Delta V_{OUT} = 35.7mV/V \cdot 10V = 0.357V$

Changing I_{OUT} from 0 to 10mA gives: $\Delta V_{OUT} = -9.64mV/mA \cdot 10mA = -0.096V$


Self-Regulated Voltage Reference

$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_Z$$

Shifts the burden of line and load regulation from the diode to the op amp!

V_o is adjustable, for instance, via R_2 .

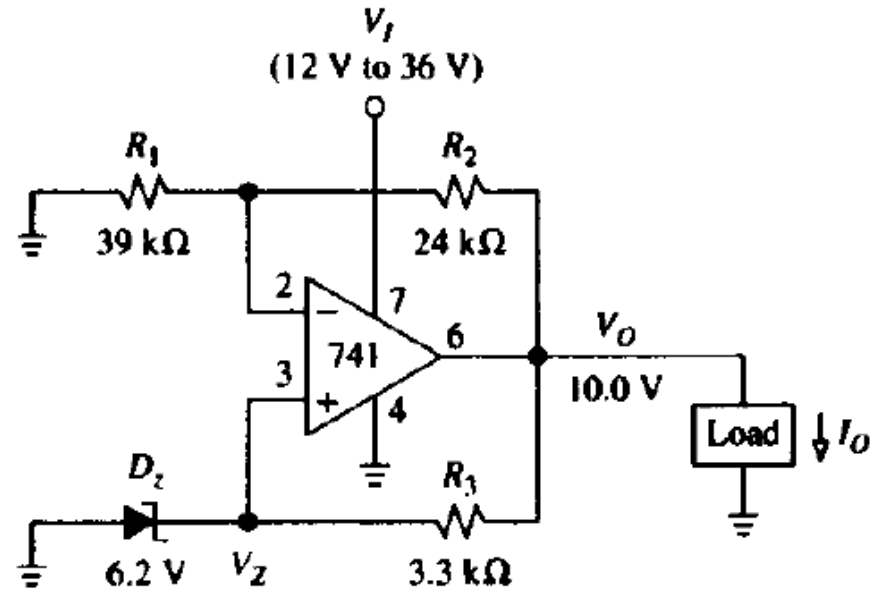R_3 can be raised to avoid unnecessary power wastage and self-heating effects.




$$\text{Load - regulation} \cong -\frac{z_o}{1 + a\beta} = -\frac{z_o}{1 + a \frac{R_1}{R_1 + R_2}}$$

where a and z_o are the open-loop gain and impedance of the op amp.

$$\Delta V_{os} = \Delta V_i \left(\frac{1}{PSRR} + \frac{0.5}{CMRR} \right) \quad \text{Appearing in series with } V_Z.$$


$$\Delta V_o = \Delta V_{os} \left(1 + \frac{R_2}{R_1} \right) \quad \longrightarrow \quad \text{Line - regulation} = \left(1 + \frac{R_2}{R_1} \right) \times \left(\frac{1}{PSRR} + \frac{0.5}{CMRR} \right)$$

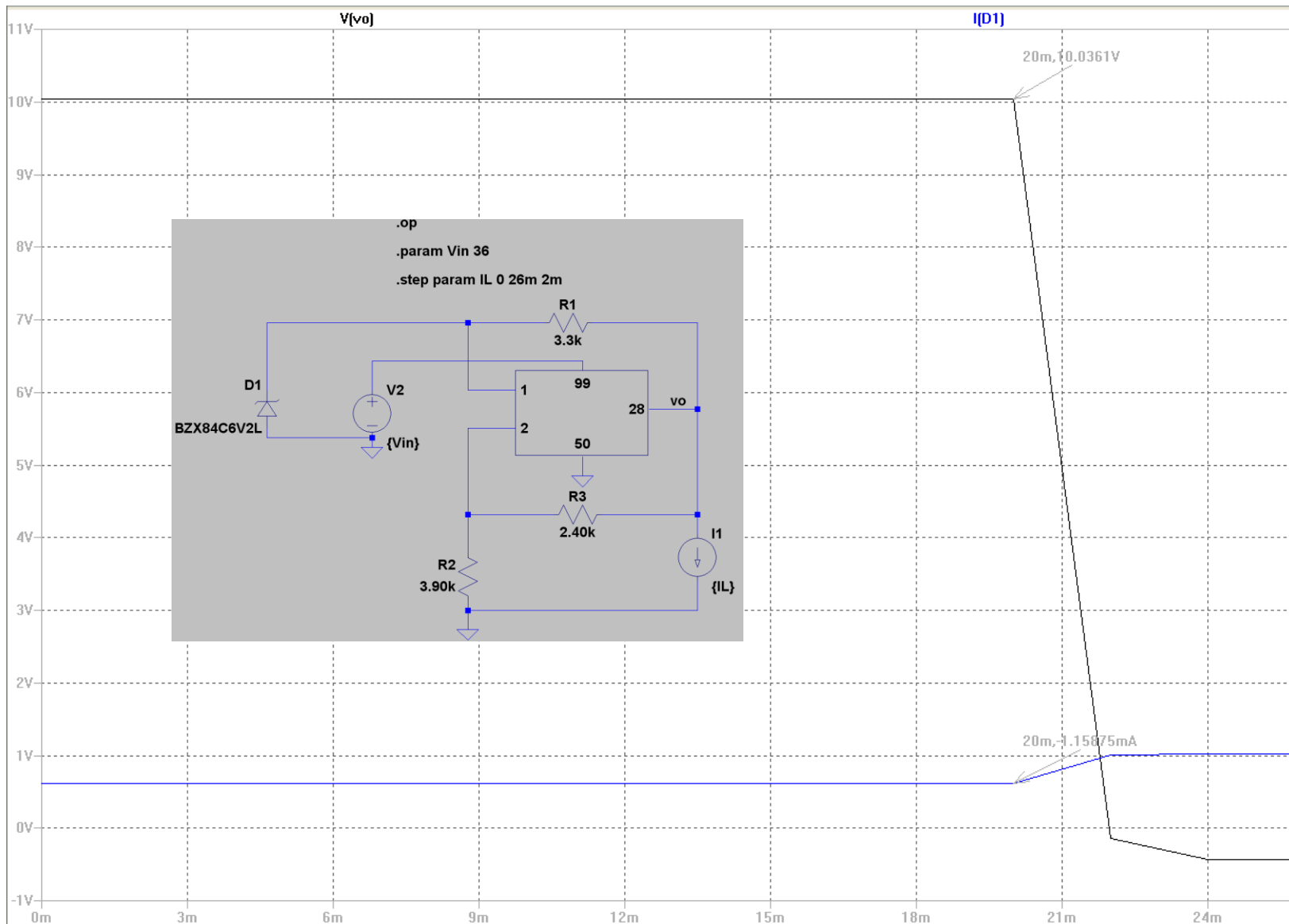Self-Regulated Voltage Reference (load regulation)



Basic Series Voltage Regulator

Darlington Pair or series pass element

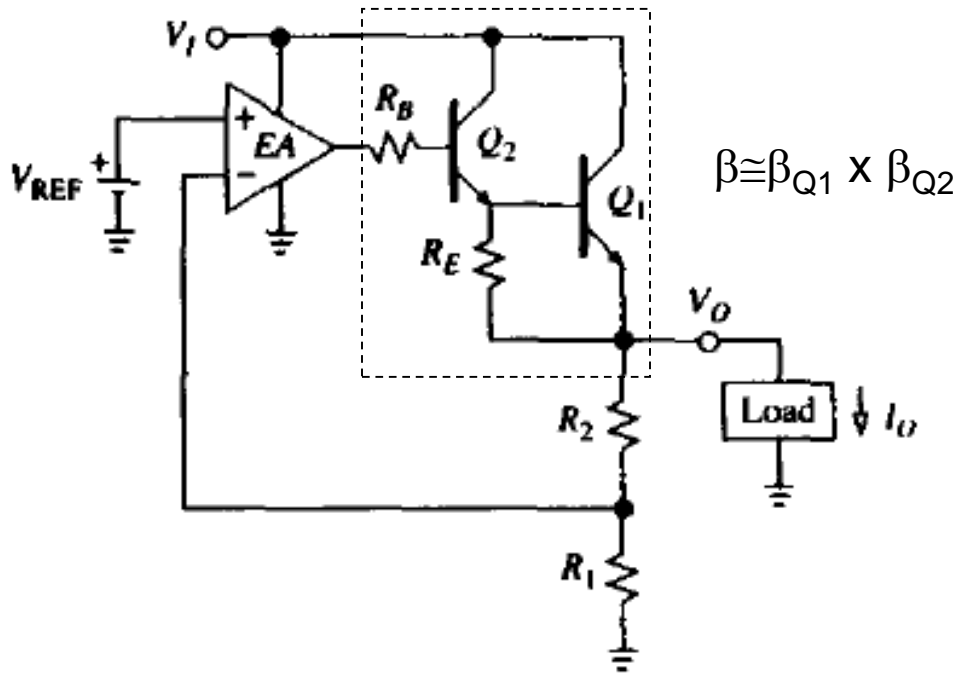

The regulator can be seen as a non-inverting amplifier with a Darlington current booster!

$$V_o = \left(1 + \frac{R_2}{R_1} \right) V_{REF}$$

Forward-active region: $I_C = \beta I_B$

$$1) V_{BE} = V_{BE(on)}$$

$$2) V_{CE} \geq V_{CE(sat)}$$

Power Transistor (Q_1):

$$\beta = 20$$

$$V_{BE(on)} \approx 1V$$

$$V_{CE(sat)} \approx 0.5V$$

Typical Transistor (Q_2):

$$\beta = 100$$

$$V_{BE(on)} \approx 0.7V$$

$$V_{CE(sat)} \approx 0.1V$$

Example 11.9

- Let $R_B = 510\Omega$ and $R_E = 3.3k\Omega$ in the regulator. Assuming a reference voltage of 1.282V and typical BJT parameters, find (a) R_2/R_1 for $V_o = 5.0V$, (b) the error amplifier output drive needed to provide, $I_o = 1A$, (c) the dropout voltage V_{DO} if the error amplifier saturates at $V_{OH} = V_i - 0.5V$, and (d) the maximum efficiency attainable for the given I_o

$$\text{a) } 5 = \left(1 + \frac{R_2}{R_1}\right) \cdot 1.282 \quad \text{gives} \quad \frac{R_2}{R_1} = 2.9.$$

$$\text{b) For } I_o = 1A \quad \text{we have } I_{B1} = I_{E1} / (\beta_1 + 1) \cong 1/21 \cong 48mA,$$

$$\text{and } I_{E2} = I_{B1} + V_{BE1(on)} / R_E \cong 48mA.$$

$$\text{The error amplifier must source: } I_{OA} = I_{B2} = I_{E2} / (\beta_2 + 1) \cong 48/101 \cong 0.47mA;$$

in addition, :

$$V_{OA} = V_{BE2(on)} + V_{BE1(on)} + V_{R_B} + V_o \cong 0.51 \times 0.47 + 0.7 + 1 + 5 \cong 7V$$

Continue Example 11.9...

- c) For this circuit to work properly we need $V_{OA} \leq V_{OH}$ and $V_{CE} \geq V_{CE(sat)}$ for both BJTs. It is readily seen that these conditions are met if $V_I \geq 7.5V$.

$$\text{Hence, } V_{DO} \geq V_I - V_o = 7.5V - 5.0V = 2.5V$$

- d) $V_I \geq 7.5V, \eta(\%) \leq (5/7.5) \times 100 \cong 67\%$