

Texas A&M University
Department of Electrical and Computer Engineering

ECEN 325 – Electronics

Fall 2025

Exam #1

Instructor: Sam Palermo

- Please write your name in the space provided below
- Please verify that there are **6** pages in your exam
- Good Luck!

Problem	Score	Max Score
1		30
2		25
3		25
4		20
Total		100

Name: _____ *SAM PALERMO*


UIN: _____

Problem 1 (30 points)

Plot the magnitude and phase response of the following transfer function. Label key points and slopes.

$$H(s) = \frac{10^6(s + 10^4)}{(s + 10^5)(s + 10^6)}$$

$$20 \log(10) |H(j\omega)| \text{ (dB)}$$

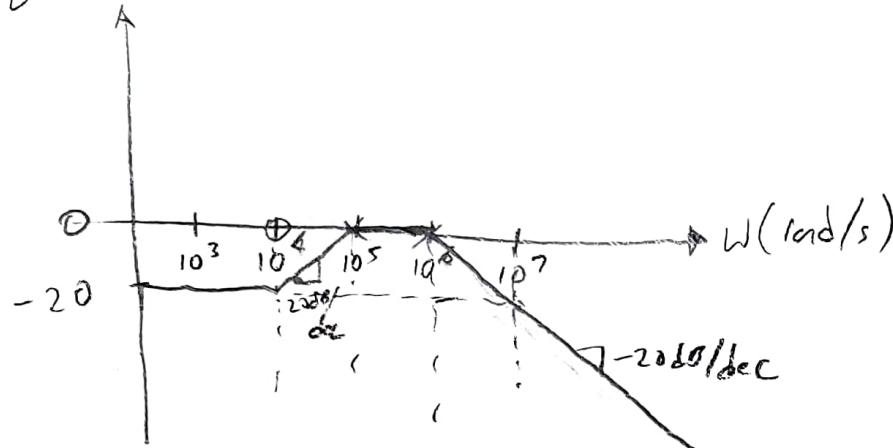

$$\text{DC gain} = \frac{10^6(10^4)}{10^5(10^6)} = 10^{-1} = -20 \text{ dB}$$


$$\text{HF gain} = \phi = -\infty \text{ dB}$$

$$z_1 = -10^4 \quad \rho_1 = -10^5 \quad \rho_2 = -10^6$$

$$\text{LP Phase} = 0^\circ$$

$$\text{HF Phase} =$$
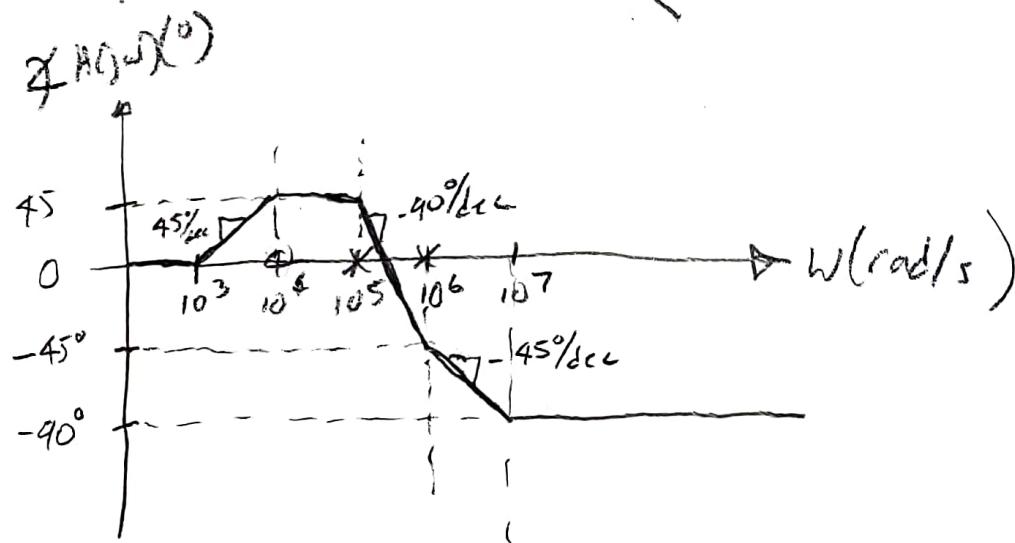
$$0^\circ + 90^\circ + 2(-40^\circ) \\ = -90^\circ$$




Problem 2 (25 points)

Assume for the Problem 2 circuit that all operational amplifiers are ideal.

For the following circuit:

- Obtain the transfer function, $v_o(s)/v_i(s)$
- Set the component values to achieve a $1k\Omega$ input resistance, 34dB low-frequency gain (magnitude), and a pole frequency of $|\omega_p| = 1\text{krad/s}$.

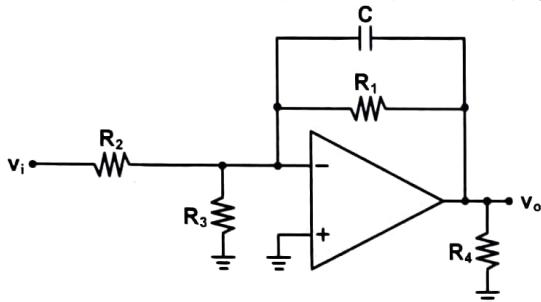

$$\frac{V_o}{V_i} = \frac{-Z_C || Z_{R1}}{Z_{R2}} = -\frac{1}{\left(sC_1 + \frac{1}{R_1}\right)R_2} = \frac{-\frac{R_1}{R_2}}{1 + sR_1C}$$

$$\frac{V_o}{V_i} = \frac{-\frac{R_1}{R_2}}{1 + sR_1C}$$

$$R_1 = R_2 = 1k\Omega$$

$$|\text{LF gain}| = 34\text{dB} = 50\% \Rightarrow R_1 = 50R_2 = 50k\Omega$$

$$|\omega_p| = 1\text{krad/s}$$

$$C = \frac{1}{R_1 |\omega_p|} = \frac{1}{(50k\Omega)(1\text{krad/s})} = 20\text{nF}$$

$$R_1 = 50k\Omega$$


$$R_2 = 1k\Omega$$

$$C = 20\text{nF}$$

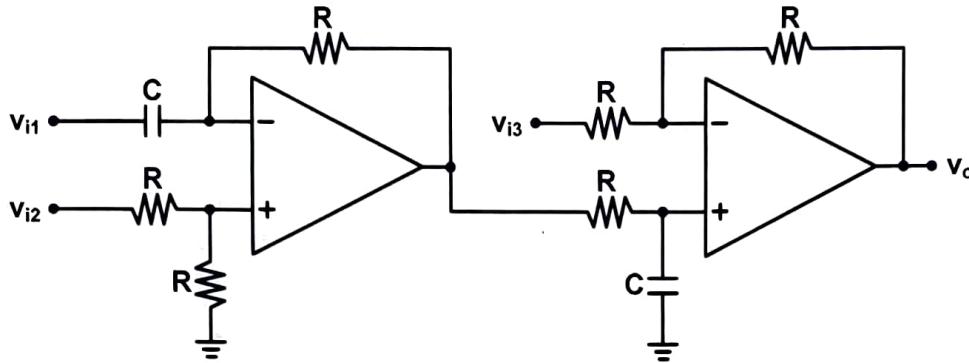Problem 3 (25 points)

Assume for the Problem 3 circuit that all operational amplifiers are ideal.

For the following circuit obtain the expression for v_o as a function of v_{i1} , v_{i2} , and v_{i3} . Assume ideal opamps. Hint: apply superposition.



$$V_o = -\left(\frac{Z_R}{Z_C}\right)\left(\frac{Z_C}{Z_R + Z_C}\right)\left(1 + \frac{Z_R}{Z_R}\right)V_{i1} + \left(\frac{Z_R}{Z_R + Z_C}\right)\left(1 + \frac{Z_R}{Z_C}\right)\left(\frac{Z_C}{Z_R + Z_C}\right)\left(1 + \frac{Z_R}{Z_R}\right)V_{i2} - \left(\frac{Z_R}{Z_R}\right)V_{i3}$$

$$V_o = -\left(\frac{Z_R}{Z_R + Z_C}\right)(2)V_{i1} + V_{i2} - V_{i3} = -\frac{2R}{R + \frac{1}{Z_C}}V_{i1} + V_{i2} - V_{i3}$$



$$V_o = -\frac{s^2 R C}{1 + s R C} V_{i1} + V_{i2} - V_{i3}$$

Problem 4 (20 points)

The operational amplifier used in the remainder of the problem has the following **open-loop** transfer function

$$A(s) = \frac{10^5}{1 + \frac{s}{10}}$$

- Sketch the **open-loop** magnitude response of the operational amplifier. **Make sure to label the unity-gain frequency.**
- The finite gain-bandwidth operational amplifier from part (a) is used in the following amplifier circuit. Find the expression for the **closed-loop** transfer function (v_o/v_i).
- What is the **closed-loop** -3dB frequency (bandwidth) of the total amplifier circuit?
- Sketch the **closed-loop** magnitude response of the amplifier circuit. **Make sure to label the unity-gain frequency.**

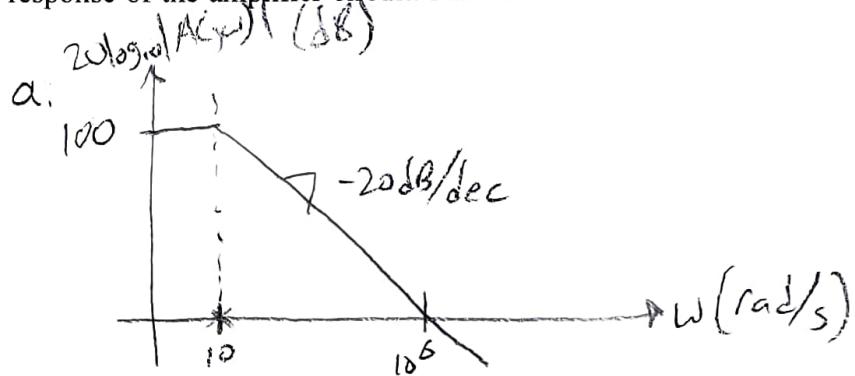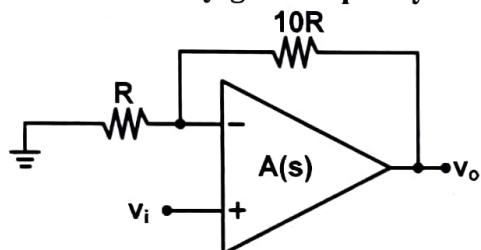

b. $\frac{V_o(s)}{V_i(s)} \approx \frac{11}{1 + \frac{s}{10^6/11}}$

c. $\omega_{CL} = \frac{10^6}{11} \text{ rad/s}$

