

**Texas A&M University**  
**Department of Electrical and Computer Engineering**

**ECEN 325 – Electronics**

**Spring 2024**

**Exam #1**

**Instructor: Sam Palermo**

- Please write your name in the space provided below
- Please verify that there are **6** pages in your exam
- Good Luck!

Problem	Score	Max Score
1		30
2		25
3		25
4		20
<b>Total</b>		<b>100</b>

Name: SAM PALERMO

UIN: \_\_\_\_\_

Problem 1 (30 points)

Plot the magnitude and phase response of the following transfer function. Label key points and slopes.

$$H(s) = \frac{(s + 10^4)(s + 10^6)}{10^5(s + 10^5)}$$

LF gain = 1 = 0dB



HF gain =  $\infty = \infty$  dB

$z_1 = -10^4, z_2 = -10^6$

$p_1 = -10^5$

LF Phase =  $0^\circ$

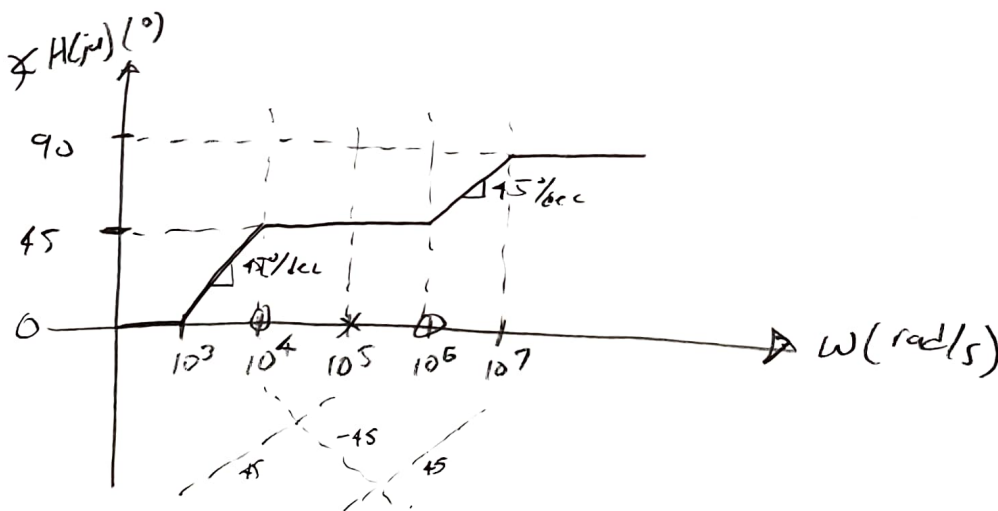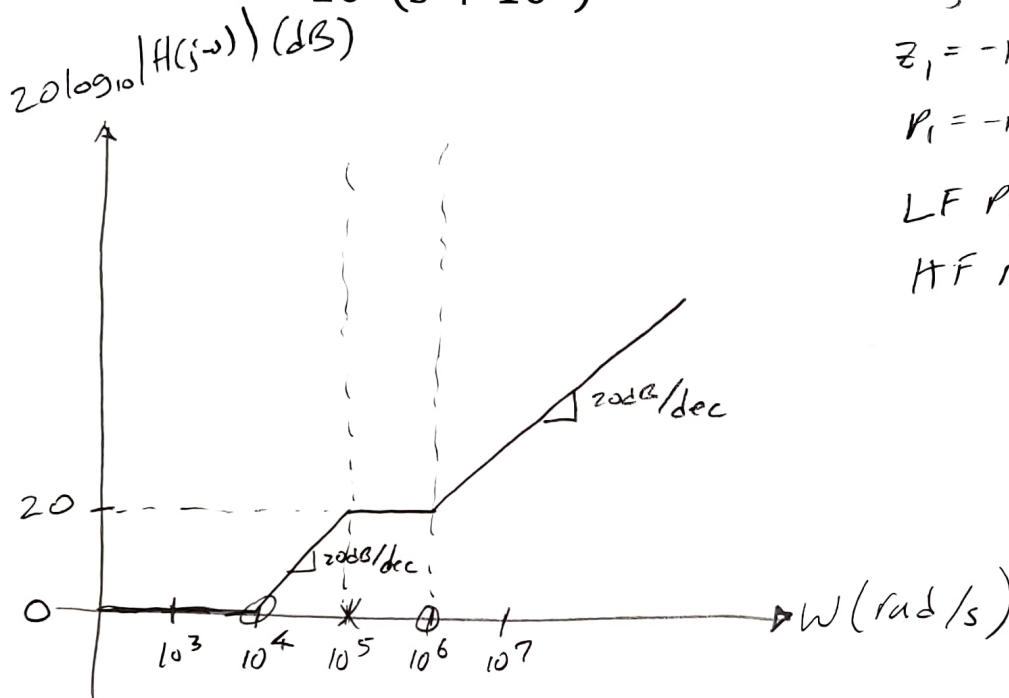
HF Phase =  $0^\circ + 2(90^\circ) + 1(-90^\circ)$   
 $= 90^\circ$



Problem 2 (25 points)

Assume for problem 2 that all operational amplifiers are ideal, unless specifically noted.

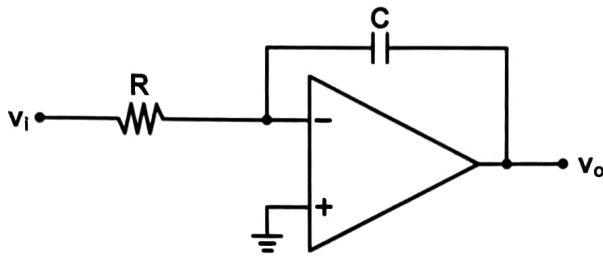- a) Design the following ideal integrator circuit to have a  $10\text{k}\Omega$  input resistance and implement the following transfer function. (15 points)



$$V_o(s) = -\frac{10^7}{s} V_i(s)$$

$$V_o(s) = -\frac{z_c}{z_R} V_i(s) = -\frac{1}{sRC} V_i(s)$$


$$R_{in} = R = 10\text{k}\Omega$$

$$R = 10\text{k}\Omega$$

$$C = 10\text{pF}$$

$$-\frac{1}{sRC} = -\frac{10^7}{s} \Rightarrow C = \frac{10^7}{R(10^7)} = \frac{1}{(10^4\Omega)(10^7)} = 10\text{pF}$$

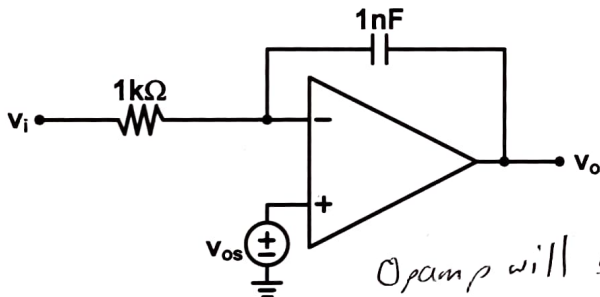- b) Now assume that  $R=1\text{k}\Omega$  and  $C=1\text{nF}$ . **Note, this is not the answer to (a).** Also, the opamp has an offset voltage  $v_{os}=5\text{mV}$  and output saturation voltages of  $V_{SAT}=\pm 7\text{V}$ . If the integrator circuit is powered up with  $v_i=0\text{V}$  and no initial capacitor voltage, how long does it take for the circuit to saturate? (10 points)



$$V_o(t) = V_{os} \left( 1 + \frac{t}{RC} \right)$$

Opamp will saturate when  $V_o(t) = 7\text{V}$


$$5\text{mV} \left( 1 + \frac{t}{(1\text{k}\Omega)(1\text{nF})} \right) = 7\text{V}$$

$$t = \left( \frac{7\text{V}}{5\text{mV}} - 1 \right) (1\text{k}\Omega)(1\text{nF}) = 1.399\text{ms}$$

$$t_{SAT} = 1.399\text{ms}$$

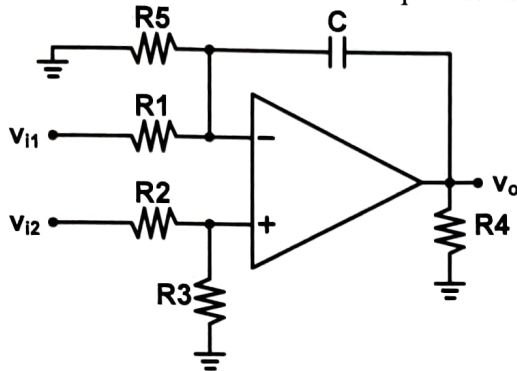Problem 3 (25 points)

Assume for problem 3 that the operational amplifiers is ideal.



- a) Find the expression for  $v_o$  as a function of  $v_{i1}$  and  $v_{i2}$ . (10 points)
- b) Find the expression for the circuit input resistance seen from  $v_{i1}$ . (5 points)
- c) Find the expression for the circuit input resistance seen from  $v_{i2}$ . (5 points)
- d) Find the expression for the circuit output resistance. (5 points)

a.


$$V_o = -\frac{Z_c}{Z_{R1}} v_{i1} + \left( \frac{Z_{R3}}{Z_{R2} + Z_{R3}} \right) \left( 1 + \frac{Z_c}{Z_{R1} \parallel Z_{R5}} \right) v_{i2}$$

$$= -\frac{1}{sR_1 C} v_{i1} + \left( \frac{R_3}{R_2 + R_3} \right) \left( 1 + \frac{1}{sC \left( \frac{R_1 R_5}{R_1 + R_5} \right)} \right) v_{i2}$$


b.  $R_{in}$  for  $v_{i1} = R_1$

c.  $R_{in}$  for  $v_{i2} = R_2 + R_3$

d.  $R_{out} = \phi$

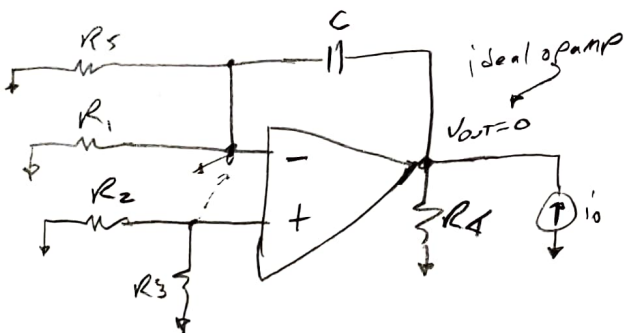

EQ circuit  $\Rightarrow$

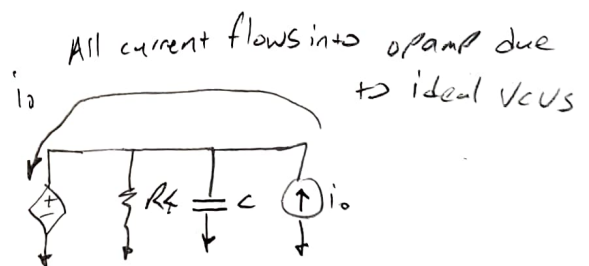

$$\phi \parallel R_4 \parallel \frac{1}{sC} \Rightarrow \phi$$

$$R_o = \frac{v_o}{i_o} = \frac{\phi}{i_o} = \phi$$

## Problem 4 (20 points)

The operational amplifier for this problem has a finite slew rate of  $1\text{V}/\mu\text{s}$ .

- a) For an output  $200\text{kHz}$  **sine** wave, what is the maximum amplitude that can be reproduced without distortion? (10 points)

$$\max \left| \frac{dV_o(t)}{dt} \right| \leq SR$$

$$V_o(t) = A \sin \omega t$$


$$\frac{dV_o(t)}{dt} = A\omega \cos \omega t$$

$$\max |A\omega \cos \omega t| = A\omega \leq SR$$

$$A \leq \frac{SR}{\omega} = \frac{1\text{V}/\mu\text{s}}{2\pi(200\text{kHz})} = 0.796\text{V}$$

$$\text{Max } A = 0.796\text{V}$$

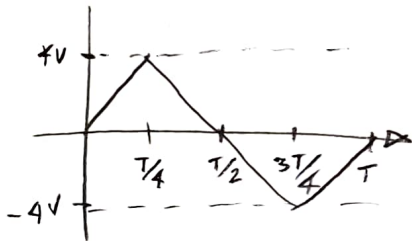- b) For an output  $4\text{V}$  amplitude **triangle** wave, what is the minimum period that can be reproduced without distortion? (10 points)



$$\max \left| \frac{dV_o(t)}{dt} \right| \leq SR$$

$$\max \left| \frac{dV_o(t)}{dt} \right| = \left| \frac{-4\text{V} - 4\text{V}}{\frac{3T}{4} - \frac{T}{4}} \right| = \frac{8\text{V}}{T/2} = \frac{16\text{V}}{T}$$

$$\frac{16\text{V}}{T} \leq SR$$

$$T \geq \frac{16\text{V}}{SR} = \frac{16\text{V}}{1\text{V}/\mu\text{s}} = 16\mu\text{s}$$

$$T \geq 16\mu\text{s}$$