

Texas A&M University
Department of Electrical and Computer Engineering

ECEN 325 – Electronics

Fall 2022

Exam #2

Instructor: Sam Palermo

- Please write your name in the space provided below
- Please verify that there are 6 pages in your exam
- Good Luck!

Problem	Score	Max Score
1		10
2		20
3		35
4		35
Total		100


Name: SAM PALERMO

UIN: _____

Problem 1 (10 points)


For all the circuits below, use the constant-voltage-drop diode model ($V_D=0.7V$), $V_{th}=25.9mV$, and $n=1$.

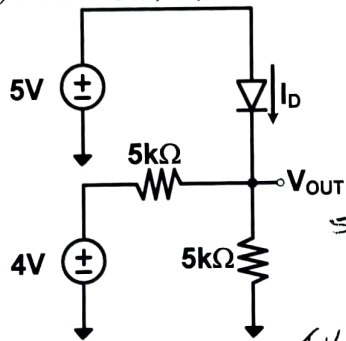a) Find V_{OUT} , I_D , and the small signal diode resistance, r_d .



If Diode is OFF $\Rightarrow V_{OUT} = 2V, V_D = 3V$, Wrong

Diode is ON

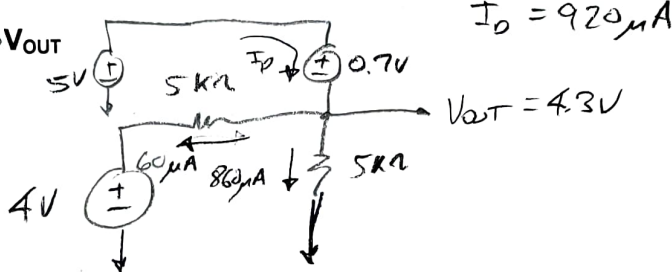

$V_{OUT} = 4.3V$

$I_D = 920 \mu A$


$r_d = 28.2 \Omega$

$$r_d = \frac{V_{th}}{I_D} = \frac{25.9mV}{920 \mu A} = 28.2 \Omega$$


Problem 2 (20 points)

Assume for the following circuit that **all diodes are forward biased**. Also assume that the capacitors act as AC shorts.

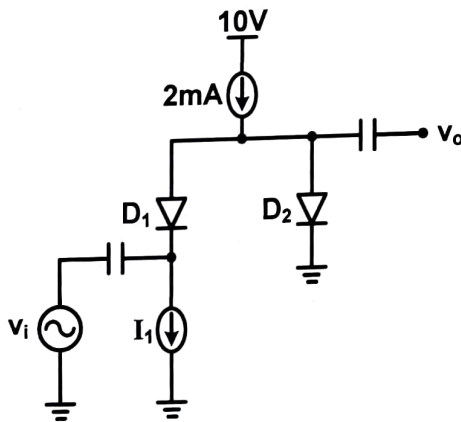- a) Derive an expression for the small-signal gain $A_v = v_o/v_i$. (10 points)
- b) Calculate the value of I_1 for $A_v=0.4$ (10 points)



AC Equivalent Circuit

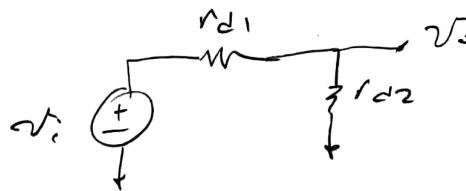

$$\frac{v_o}{v_i} = \frac{r_{d2}}{r_{d1} + r_{d2}}$$

$$\frac{r_{d2}}{r_{d1} + r_{d2}} = 0.4$$

$$r_{d2} = \frac{2}{3} r_{d1} \Rightarrow I_{D2} = \frac{3}{2} I_{D1}$$

$$I_{D1} + I_{D2} = 2mA$$

$$\frac{5}{2} I_{D1} = 2mA$$

$$I_{D1} = 0.8mA = I_1$$



A_v Expression = $\frac{r_{d2}}{r_{d1} + r_{d2}}$

$I_1 (A_v=0.4) = 0.8mA$

Problem 3 (35 points)

Assume for problem 2 that the transistor $\beta=150$, $V_{BE}=0.7V$, and $V_{th}=25.9mV$.

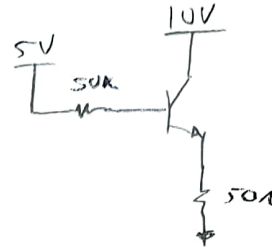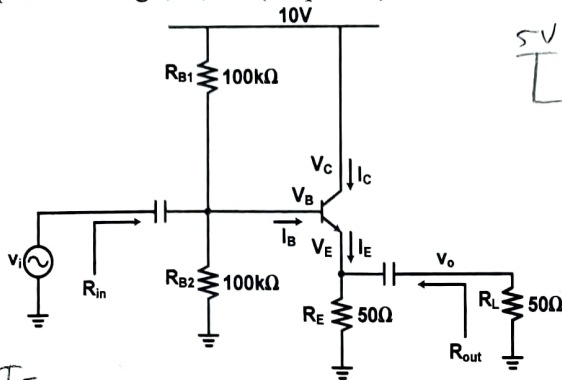a) Calculate the DC values for V_C , V_B , V_E , I_C , I_B , and I_E . Compute the AC small signal parameters g_m , r_π , r_e . (18 points)



$$I_B = \frac{I_E}{\beta + 1} = 74.7 \mu A, \quad I_C = \beta I_B = 11.2 mA$$

$$V_E = I_E R_E = 11.3 mA (50 \Omega) = 0.57 V$$

$$V_B = V_E + 0.7 = 1.27 V$$

$$V_C = 10 V$$

$$r_\pi = \frac{V_{th}}{I_B} = \frac{25.9 mV}{74.7 \mu A} = 347 \Omega$$

$$r_e = \frac{V_{th}}{I_E} = \frac{25.9 mV}{11.3 mA} = 2.29 \Omega$$


$$I_E = \frac{5V - 0.7V}{50 + \frac{50k}{151}} = 11.3 mA$$

$$g_m = \frac{I_C}{V_{th}} = \frac{11.2 mA}{25.9 mV} = 432 mA/V$$


- $I_C = 11.2 mA$
- $I_B = 74.7 \mu A$
- $I_E = 11.3 mA$
- $V_C = 10 V$
- $V_B = 1.27 V$
- $V_E = 0.57 V$
- $g_m = 432 mA/V$
- $r_\pi = 347 \Omega$
- $r_e = 2.29 \Omega$

b) Sketch the small-signal model of the circuit. Assume that the capacitors act as AC shorts and that the transistor's r_o is infinite. Only ONE version of the model (π or T) is required (11 points)

π -model

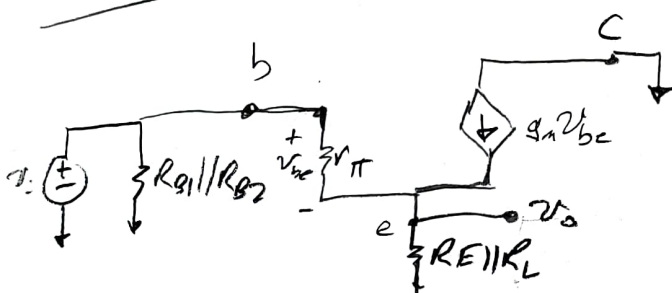

T-model

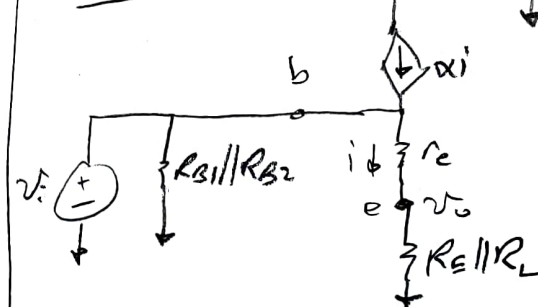

c) Calculate the small signal gain $A_v = v_o/v_i$, the input resistance R_{in} , the output resistance R_{out} . (6 points)

$$A_v = \frac{R_E \parallel R_L}{r_e + R_E \parallel R_L} = \frac{50 \parallel 50}{2.29 + 50 \parallel 50} = 0.916 V/V$$

$$R_{in} = R_B \parallel \left[r_\pi + (\beta + 1)(R_E \parallel R_L) \right] = 50k \parallel \left[347 + (151)(50 \parallel 50) \right] = 3.81 k\Omega$$

$$R_{out} = r_e \parallel R_E = 2.29 \parallel 50 = 2.19 \Omega$$


- $A_v = 0.916 V/V$
- $R_{in} = 3.81 k\Omega$
- $R_{out} = 2.19 \Omega$

4

Problem 4 (35 points)

Assume for problem 3 that **the transistors are operating in active mode** and that the capacitors act as AC shorts and that the transistor's r_o is infinite (can be neglected).

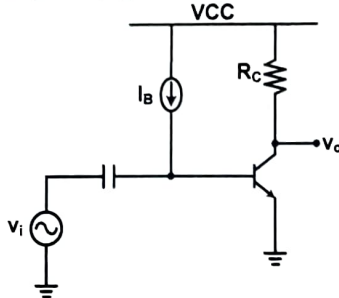a) For the amplifier below derive an expression for the small signal gain $A_v = v_o/v_i$ as a function of β . (6 points)



$$A_v = -g_m R_C = -\frac{I_C}{V_{th}} R_C = -\frac{\beta I_B}{V_{th}} R_C$$

$A_v(\beta)$ Expression : $-\frac{\beta I_B}{V_{th}} R_C$

b) Now assume that $I_B = 10\mu\text{A}$, $R_C = 270\Omega$, and $V_{th} = 25.9\text{mV}$. Calculate A_v for a β of 150 and 300. (4 points)


$$A_{v1} = -\frac{150(10\mu\text{A})}{25.9\text{mV}}(270\Omega) = -15.6 \text{ V/V}$$

$$A_v(\beta_1=150) = -15.6 \text{ V/V}$$

$$A_v(\beta_2=300) = -31.3 \text{ V/V}$$

$$A_{v2} = -\frac{300(10\mu\text{A})}{25.9\text{mV}}(270\Omega) = -31.3 \text{ V/V}$$

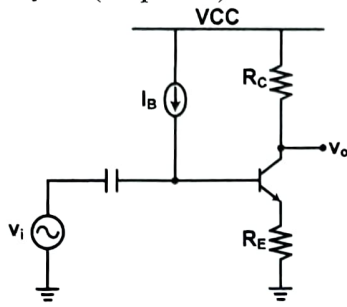c) For the amplifier below derive an expression for the small signal gain $A_v = v_o/v_i$ as a function of β . (10 points)



$$A_v = \frac{-g_m R_C}{1 + \frac{g_m R_E}{\alpha}} = \frac{-\beta I_B}{V_{th}} R_C}{1 + \frac{\beta I_B}{V_{th}} \left(\frac{R+1}{R}\right) R_E}$$

$A_v(\beta)$ Expression :

$$\frac{-\frac{\beta I_B}{V_{th}} R_C}{1 + \frac{I_B(\beta+1)}{V_{th}} R_E} = \frac{-\left(\frac{R}{R+1}\right) R_C}{R_E + \frac{V_{th}}{I_B(\beta+1)}}$$

d) Now assume that the nominal transistor $\beta_1=150$, $R_C=1.5k\Omega$, $I_B=10\mu A$, and $V_{th}=25.9mV$. If β increases, the gain will increase also. However, having an R_E lowers the amplifier sensitivity to β . What is the minimum value of R_E required to insure that if β doubles to $\beta_2=300$ the gain will change no more than 10%? (10 points)

$$A_v(\beta_2=300) = 1.1 A_v(\beta_1=150)$$

$$\frac{-\frac{300(10\mu A)}{25.9mV} (1.5k\Omega)}{1 + \frac{10\mu A(301)}{25.9mV} R_E} = \frac{-\frac{1.1(150)(10\mu A)}{25.9mV} (1.5k\Omega)}{1 + \frac{10\mu A(151)}{25.9mV} R_E}$$

$$\frac{174}{1 + 0.116 R_E} = \frac{95.6}{1 + 0.058 R_E}$$

Min. R_E for $A_v(\beta_2=300) = 1.1 * A_v(\beta_1=150)$: 83.0Ω

$R_E = 83.0\Omega$

e) Using the R_E value computed in part (d), calculate A_v for a β of 150 and 300. Again, assume $R_C=1.5k\Omega$, $I_B=10\mu A$, and $V_{th}=25.9mV$. (5 points)

$$A_v(\beta=150) = \frac{-\frac{150(10\mu A)}{25.9mV} (1.5k)}{1 + \frac{10\mu A(151)}{25.9mV} (83)} = -14.9\%$$

$A_v(\beta_1=150) = -14.9\%$

$A_v(\beta_2=300) = -16.3\%$

$$A_v(\beta=300) = \frac{-\frac{300(10\mu A)}{25.9mV} (1.5k)}{1 + \frac{10\mu A(301)}{25.9mV} (83)} = -16.3\%$$