

**Texas A&M University**  
**Department of Electrical and Computer Engineering**

**ECEN 325 – Electronics**

**Spring 2024**

**Exam #3**

**Instructor: Sam Palermo**

- Please write your name in the space provided below
- Please verify that there are **6** pages in your exam
- You may use one double-sided page of notes and equations for the exam
- Good Luck!

Problem	Score	Max Score
1		30
2		35
3		35
<b>Total</b>		<b>100</b>

Name: SAM PALERMO

UIN: \_\_\_\_\_

Problem 1 (30 points)

For all the circuits below, use the following NMOS parameters

$$K_{PN} = \mu_n C_{ox} = 100 \mu A/V^2, V_{TN} = 1V, \lambda_N = 0V^{-1}$$

and the following PMOS parameters


$$K_{PP} = \mu_p C_{ox} = 30 \mu A/V^2, V_{TP} = -1V, \lambda_P = 0V^{-1}$$

For the following two circuits calculate

i.  $I_D$  with  $W_2/L_2 = 10/1$ . (10 points)

ii. The minimum  $W_2/L_2$  such that the M1 transistor remains in saturation (10 points)

a)

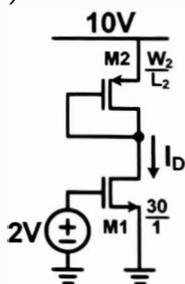

$$M1 \text{ Sat! } V_{DS1} \cong V_{GS1} - V_{TN} = 2V - 1V = 1V$$

$$I_{D1} = \frac{1}{2} (100 \mu A/V^2) \left(\frac{30}{1}\right) (2V - 1V)^2 = 1.5 \text{ mA}$$


$$V_{O1} = V_{DD} - V_{SG2} = 10V - \left( \sqrt{\frac{2(1.5 \text{ mA})}{(30 \mu)(10)}} + |-1V| \right) = 5.84 \Rightarrow M1 \text{ Sat}$$

$$\text{Min } \left(\frac{W}{L}\right)_2 = \frac{2I_D}{K_{PP} (V_{SG} - |V_{TP}|)^2} = \frac{2(1.5 \text{ mA})}{30 \mu (9V - |-1V|)^2} = 1.56$$

$$I_D (W_2/L_2 = 10/1) = 1.5 \text{ mA}$$

$$M1 \text{ Sat. Min } W_2/L_2 = 1.56$$

b)

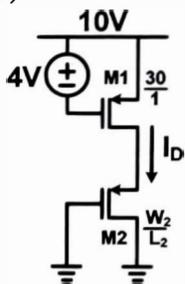

$$M1 \text{ Sat } V_{SD1} \cong V_{SG1} - |V_{TP}| = 4V - |-1V| = 3V$$

$$I_{D1} = \frac{1}{2} (30 \mu A/V^2) \left(\frac{30}{1}\right) (4V - |-1V|)^2 = 4.05 \text{ mA}$$


$$V_{O1} = V_{SG2} = \sqrt{\frac{2(4.05 \text{ mA})}{(30 \mu)(10)}} + |-1V| = 6.20V \Rightarrow V_{SD1} = 3.8V \Rightarrow M1 \text{ Sat}$$

$$\text{Min } \left(\frac{W}{L}\right)_2 = \frac{2I_D}{K_{PP} (V_{SG} - |V_{TP}|)^2} = \frac{2(4.05 \text{ mA})}{(30 \mu)(7V - |-1V|)^2} = 7.5$$

$$I_D (W_2/L_2 = 10/1) = 4.05 \text{ mA}$$

$$M1 \text{ Sat. Min } W_2/L_2 = 7.5$$

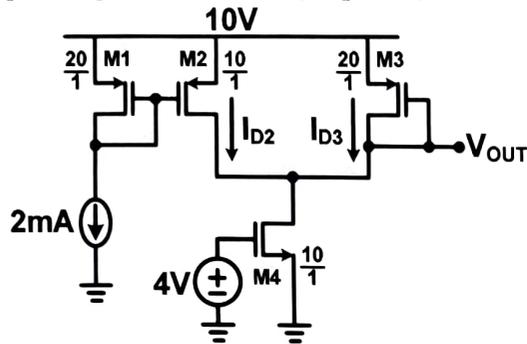c) For the following circuit find the values for  $I_{D2}$ ,  $I_{D3}$ , and  $V_{OUT}$ . Assume all transistors are operating in saturation. (10 points)



$$I_{D2} = I_{REF} \frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_1} = 2\text{mA} \frac{(10)}{(20)} = 1\text{mA}$$

$$I_{D2} = 1\text{mA}$$

$$I_{D3} = 3.5\text{mA}$$

$$I_{D4} = \frac{1}{2} (100\mu)(10) (4V - 1V)^2 = 4.5\text{mA}$$

$$V_{OUT} = 5.58V$$

$$I_{D3} = I_{D4} - I_{D2} = 4.5\text{mA} - 1\text{mA} = 3.5\text{mA}$$


$$V_{OUT} = V_{DD} - V_{SG3} = 10V - \left( \sqrt{\frac{2(3.5\text{mA})}{(30\mu)(20)}} + |-1V| \right) = 5.58V$$

Problem 2 (35 points)

Assume for problem 2 that the NMOS transistors are all operating in saturation and have

$$K_{PN} = \mu_n C_{ox} = 100 \mu A/V^2, V_{TN} = 1V, \lambda_N = 0V^{-1}$$

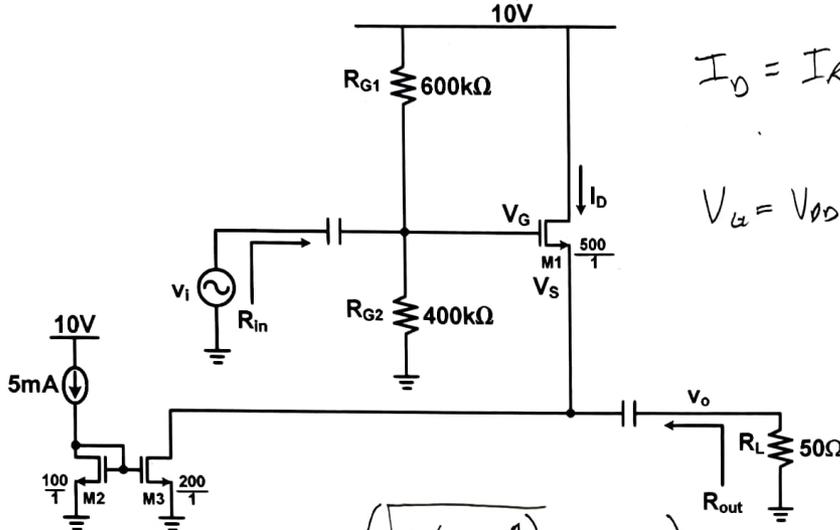a) Calculate the DC values for  $I_D$ ,  $V_G$ ,  $V_S$  and the AC small-signal  $g_{m1}$ . (10 points)



$$I_D = I_{REF} \frac{(W/L)_3}{(W/L)_2} = 5mA \frac{200}{100} = 10mA$$

$$V_G = V_{DD} \frac{R_{G2}}{R_{G1} + R_{G2}} = 10V \left( \frac{400k}{600k + 400k} \right) = 4V$$

$$V_S = V_G - V_{GS} = 4V - \left( \sqrt{\frac{2(10mA)}{100\mu(500)}} + 1V \right) = 2.37V$$

$$g_{m1} = \sqrt{K_{PN} \frac{W}{L} 2I_D} = \sqrt{(100\mu)(500)(2)(10mA)} = 31.6 mA/V$$

$$I_D = 10mA$$


$$V_G = 4V$$

$$V_S = 2.37V$$


$$g_{m1} = 31.6 mA/V$$

b) Sketch the small-signal model of the circuit. Assume that the capacitors act as AC shorts and only draw the essential transistor(s). Only ONE version of the model ( $\pi$  or T) is required. (10 points)

$\pi$ -model points)

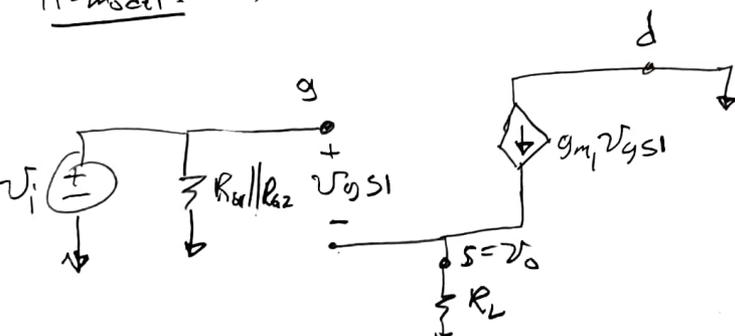

T-model

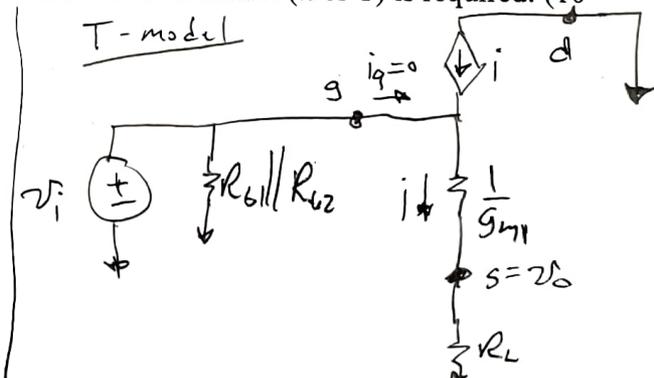

c) Calculate small signal gain  $A_v = v_o/v_i$ , input resistance  $R_{in}$ , output resistance  $R_{out}$ . (15 points)

$$v_o = v_i \left( \frac{R_L}{\frac{1}{g_m} + R_L} \right) = \frac{g_m R_L}{1 + g_m R_L} = \frac{(31.6m)(50)}{1 + (31.6m)(50)} = 0.612 V/V$$

$$A_v = 0.612 V/V$$

$$R_{in} = 240k$$

$$R_{out} = 31.6 \Omega$$


$$R_{in} = R_{G1} \parallel R_{G2} = 400k \parallel 600k = 240k$$

$$R_{out} = \frac{1}{g_m} = \frac{1}{31.6 mA/V} = 31.6 \Omega$$

Problem 3 (35 points)

This problem involves the small signal analysis of the circuit below. Assume that the transistors are all operating in saturation and have  $r_o = \infty$ .

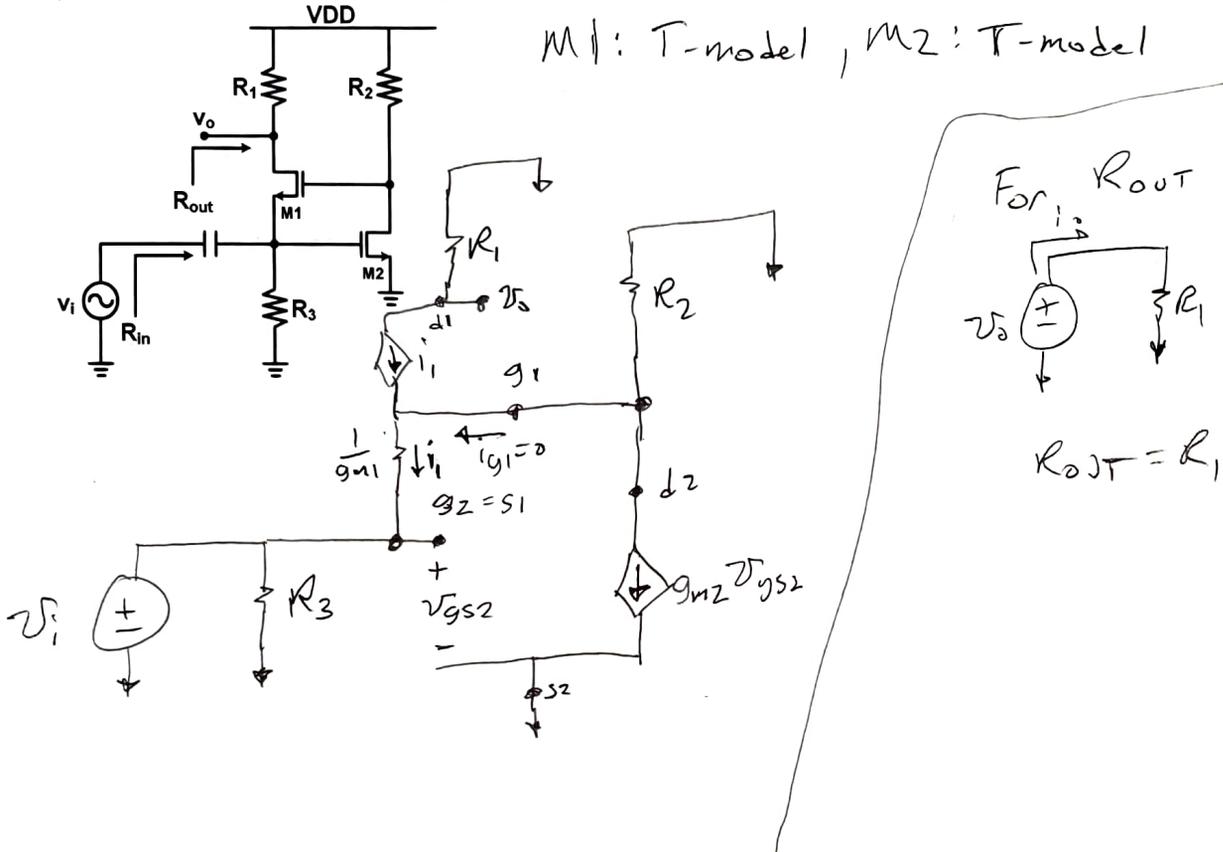a) Sketch the circuit's small-signal model. Assume the capacitors act as AC shorts. (15 points)



b) Derive expressions for the small signal gain  $A_v = v_o/v_i$ , input resistance  $R_{in}$ , and output resistance  $R_{out}$ . (20 points)


$$v_o = -i_1 R_1$$

$$i_1 = \frac{-g_{m2} v_i R_2 - v_i}{1/g_{m1}} \Rightarrow v_o = +v_i \left[ g_{m1} g_{m2} R_2 + g_{m1} \right] R_1$$

$$\frac{v_o}{v_i} = g_{m1} R_1 \left[ 1 + g_{m2} R_2 \right]$$

$$A_v = g_{m1} R_1 \left[ 1 + g_{m2} R_2 \right]$$
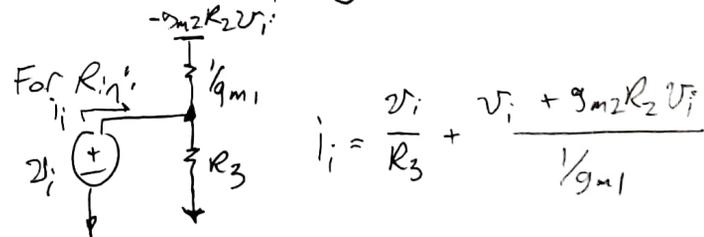
$$R_{in} = R_3 \parallel \left( \frac{1}{g_{m1} (1 + g_{m2} R_2)} \right)$$



$$R_{out} = R_1$$

$$R_{in} = \frac{v_i}{i_1} = \frac{1}{\frac{1}{R_3} + g_{m1} (1 + g_{m2} R_2)}$$

$$= R_3 \parallel \left( \frac{1}{g_{m1} (1 + g_{m2} R_2)} \right)$$