

## Complex Number Review

a.  $a + jb$

$$\text{magnitude} = \sqrt{a^2 + b^2}$$
$$\text{phase} = \tan^{-1}\left(\frac{b}{a}\right)$$

b.  $\frac{a+jb}{c+jd}$

$$\text{magnitude} = \frac{\sqrt{a^2 + b^2}}{\sqrt{c^2 + d^2}}$$

$$\text{phase} = \tan^{-1}\left(\frac{b}{a}\right) - \tan^{-1}\left(\frac{d}{c}\right)$$

c.  $(a+jb)(a-jb)$

$$\text{magnitude} = \sqrt{a^2 + b^2} \sqrt{a^2 + b^2} = a^2 + b^2$$

$$\text{phase} = \tan^{-1}\left(\frac{b}{a}\right) + \tan^{-1}\left(\frac{-b}{a}\right)$$

$$= \tan^{-1}\left(\frac{b}{a}\right) - \tan^{-1}\left(\frac{b}{a}\right) = \emptyset$$

d.  $100 + j10$

$$\text{magnitude} = \sqrt{100^2 + 10^2} = 100.5$$

$$\text{phase} = \tan^{-1}\left(\frac{10}{100}\right) = 5.71^\circ$$

e.  $\frac{100 + j10}{(1 + j10)(10 + j10)}$


$$\text{magnitude} = \frac{\sqrt{100^2 + 10^2}}{\sqrt{1^2 + 10^2} \sqrt{10^2 + 10^2}} = 0.707$$

$$\text{phase} = \tan^{-1}\left(\frac{10}{100}\right) - \tan^{-1}\left(\frac{10}{1}\right) - \tan^{-1}\left(\frac{10}{10}\right) = -123.6^\circ$$

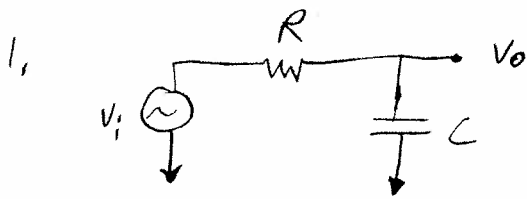f.  $\frac{(1 + j10)(10 + j10)}{100 + j10}$

$$\text{magnitude} = \frac{\sqrt{1^2 + 10^2} \sqrt{10^2 + 10^2}}{\sqrt{100^2 + 10^2}} = 1.414$$

$$\text{phase} = \tan^{-1}\left(\frac{10}{1}\right) + \tan^{-1}\left(\frac{10}{10}\right) - \tan^{-1}\left(\frac{10}{100}\right) = 123.6^\circ$$



$$V_o(s) = \frac{Z_C}{Z_R + Z_C} V_i(s)$$

$$\frac{V_o(s)}{V_i(s)} = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} = \frac{\frac{1}{RC}}{s + \frac{1}{RC}}$$

$$1/RC = 10^5, \quad C = 10 \text{ nF}$$

$$F(s) = \frac{V_o(s)}{V_i(s)} = \frac{10^5}{s + 10^5}$$

1 pole at  $\omega = -10^5 \text{ rad/s}$  or  $f = -15.9 \text{ kHz}$

$$\lim_{s \rightarrow 0} F(s) = \frac{10^5}{10^5} = 1$$

$$\lim_{s \rightarrow \infty} F(s) = \frac{10^5}{\infty + 10^5} = 0$$

DC gain = 1


High Freq. gain = 0

Low-Pass Filter


# Bode Approximate Plot

2


$20 \log_{10} |F(s)|$  (dB)

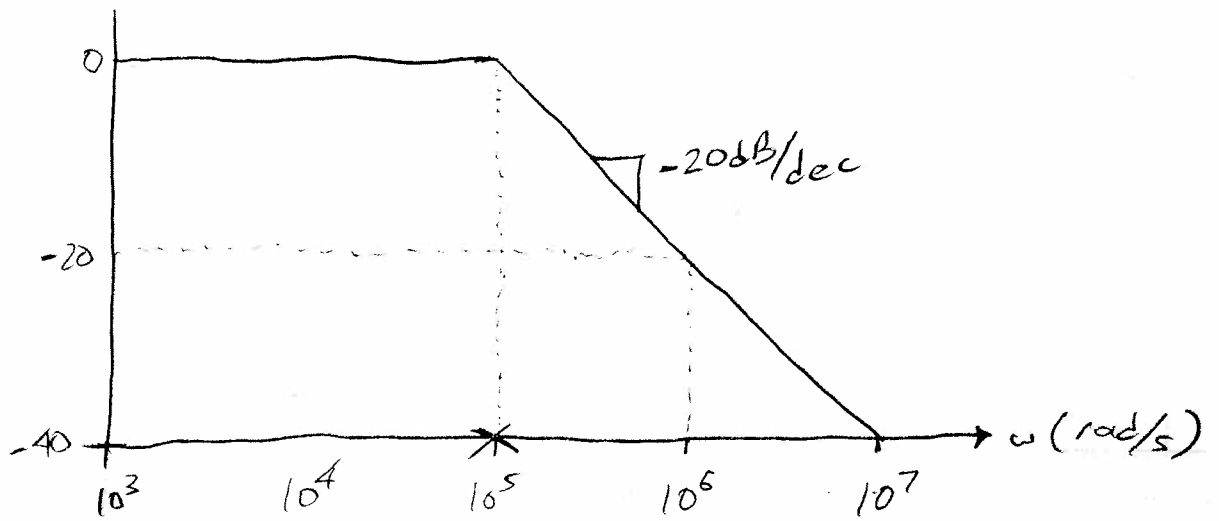


Phase( $F(s)$ ) (degrees)

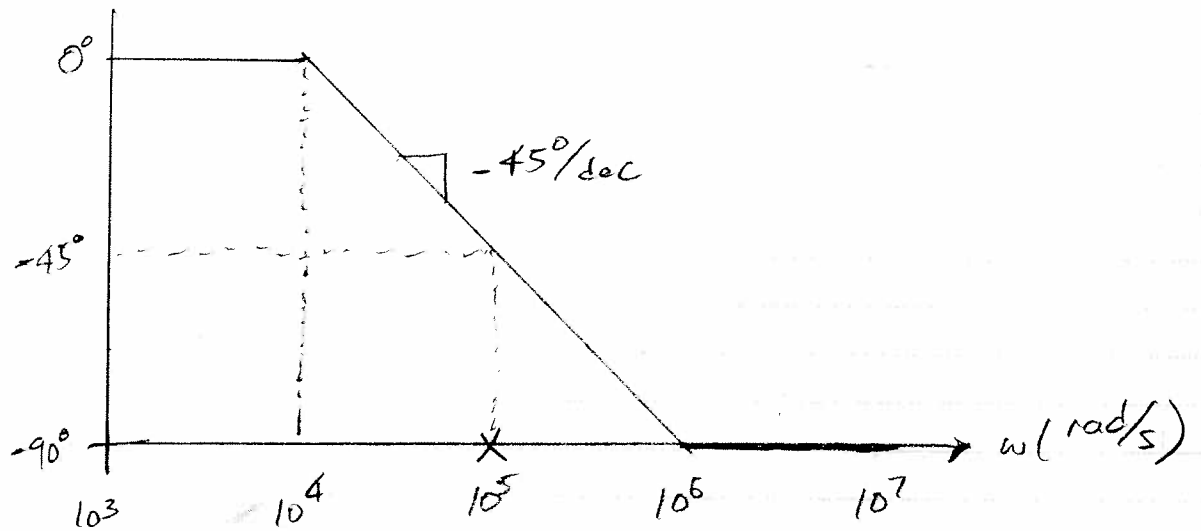


1.

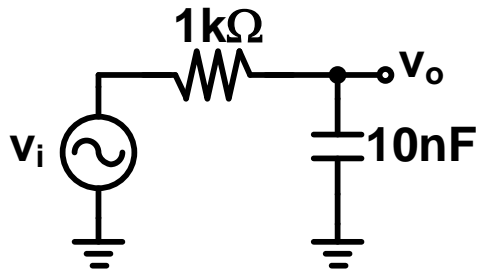

## Bode Plot

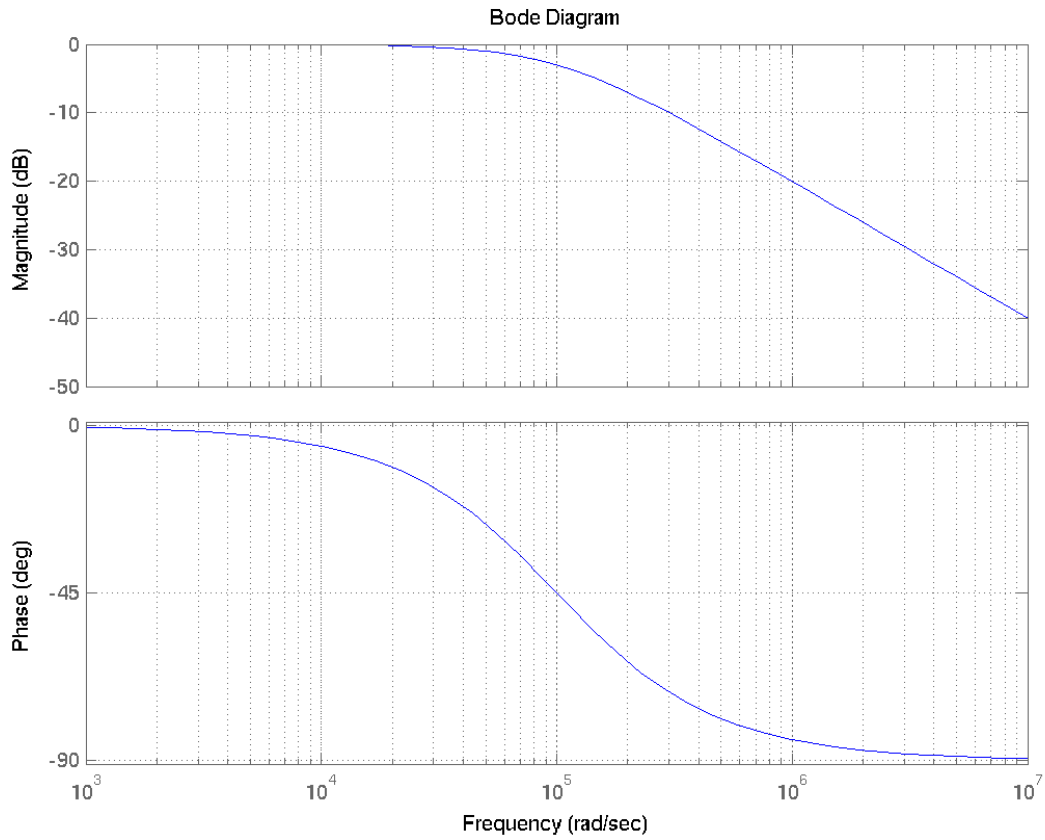

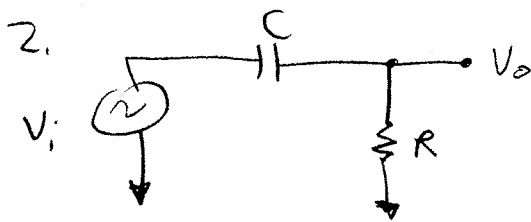

$$V_o(s) = \frac{Z_R}{Z_R + Z_C} V_i(s)$$

13

$$\frac{V_o(s)}{V_i(s)} = \frac{R}{R + \frac{1}{sC}} = \frac{s}{s + \frac{1}{RC}}$$

w/R = 1k $\Omega$ , C = 10nF

$$F(s) = \frac{V_o(s)}{V_i(s)} = \frac{s}{s + 10^5}$$

$$\lim_{s \rightarrow 0} F(s) = \frac{0}{0 + 10^5} = 0$$

$$\lim_{s \rightarrow \infty} F(s) = \frac{\infty}{\infty + 10^5} \Rightarrow 1$$

DC gain = 0

High freq gain = 1


High-Pass Filter

1 zero at 0


1 pole at  $-10^5$  rad/s

# Approximate Bode Plot


$20 \log_{10} |F(s)|$  (dB)

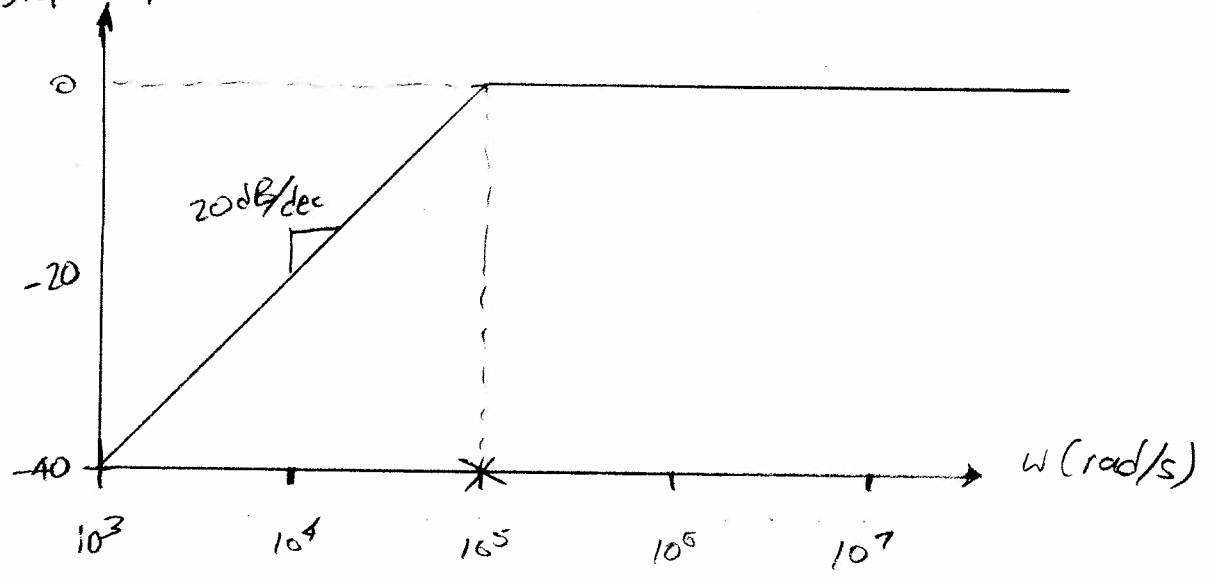


Phase  $(F(s))$  (degrees)

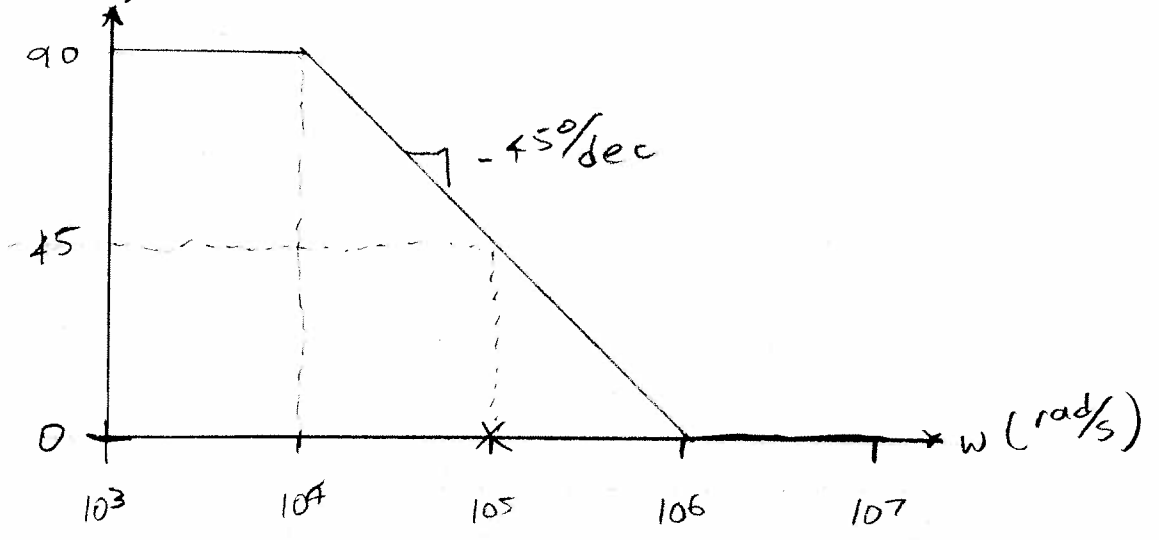


2.

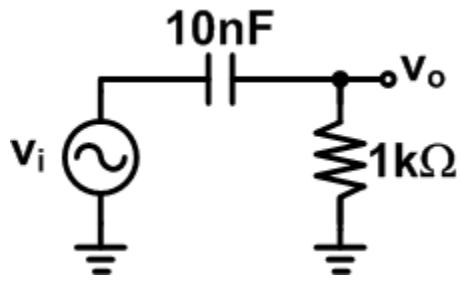

## Bode Plot

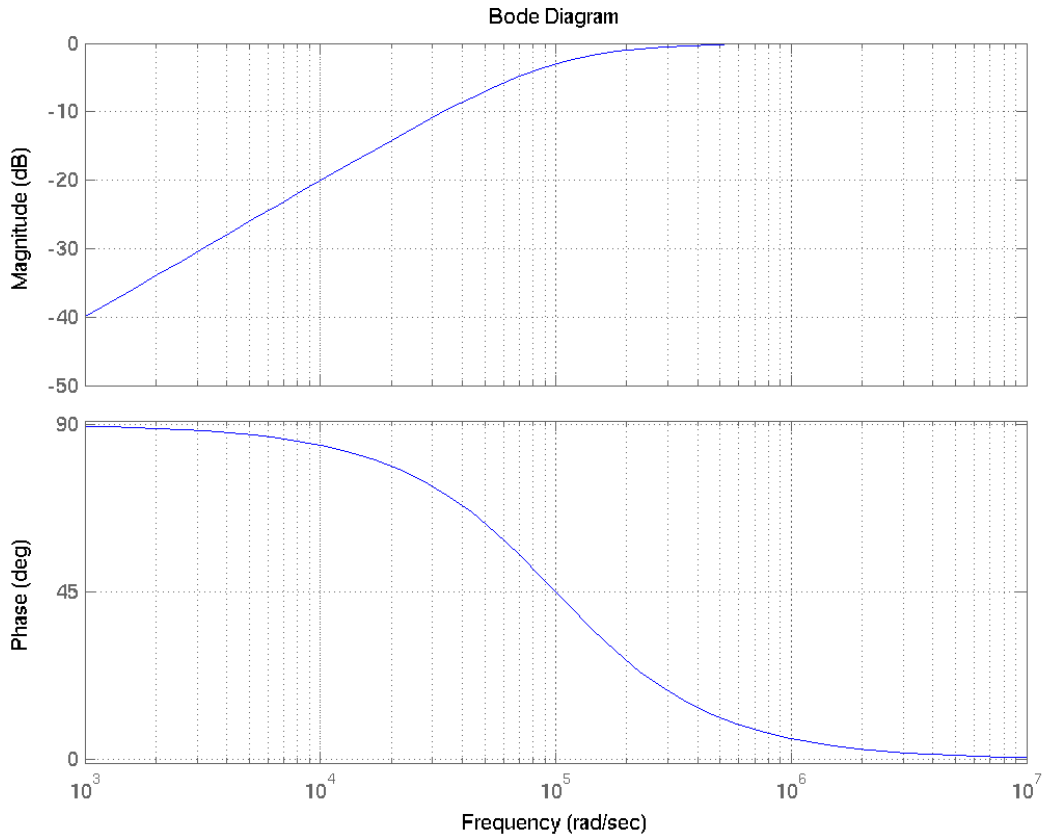



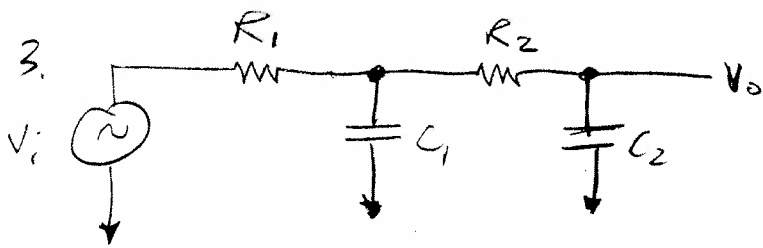

5

$$V_o(s) = \left[ \frac{Z_{C_1} \parallel (Z_{R_2} + Z_{C_2})}{Z_{R_1} + Z_{C_1} \parallel (Z_{R_2} + Z_{C_2})} \right] \left[ \frac{Z_{C_2}}{Z_{R_2} + Z_{C_2}} \right] V_i(s)$$

$$\frac{V_o(s)}{V_i(s)} = \left[ \frac{\frac{1}{sC_1 + \frac{1}{R_2 + \frac{1}{sC_2}}}}{R_1 + \frac{1}{sC_1 + \frac{1}{R_2 + \frac{1}{sC_2}}}} \right] \left[ \frac{\frac{1}{sC_2}}{R_2 + \frac{1}{sC_2}} \right]$$

$$= \left[ \frac{1}{sR_1C_1 + \frac{R_1}{R_2 + \frac{1}{sC_2}} + 1} \right] \left[ \frac{\frac{1}{sC_2}}{R_2 + \frac{1}{sC_2}} \right]$$

$$= \frac{\frac{1}{sC_2}}{sR_1R_2C_1 + R_1 \frac{C_1}{C_2} + R_1 + R_2 + \frac{1}{sC_2}}$$

$$= \frac{1}{s^2 R_1 R_2 C_1 C_2 + s R_1 C_1 + s R_1 C_2 + s R_2 C_2 + 1}$$

$$= \frac{1}{R_1 R_2 C_1 C_2}$$

$$s^2 + s \left[ \frac{R_1 C_1 + R_1 C_2 + R_2 C_2}{R_1 R_2 C_1 C_2} \right] + \frac{1}{R_1 R_2 C_1 C_2}$$

W/  $R_1 = R_2 = 1k\Omega$   $C_1 = C_2 = 10nF$

16

$$F(s) = \frac{V_o(s)}{V_i(s)} = \frac{10^{10}}{s^2 + 3 \times 10^5 s + 10^{10}}$$

$$\lim_{s \rightarrow 0} F(s) = \frac{10^{10}}{0 + 0 + 10^{10}} = 1$$

$$\lim_{s \rightarrow \infty} F(s) = \frac{10^{10}}{\infty} = 0$$

DC gain = 1

High Freq gain = 0


Low Pass Filter

2 poles at  $\frac{-3 \times 10^5 \pm \sqrt{9 \times 10^{10} - 4 \times 10^{10}}}{2}$


Poles at  $-38.2 \text{ krad/s}$   
 $-262 \text{ krad/s}$

# Approximate Bode Plot


$20 \log_{10} |F(s)|$  (dB)

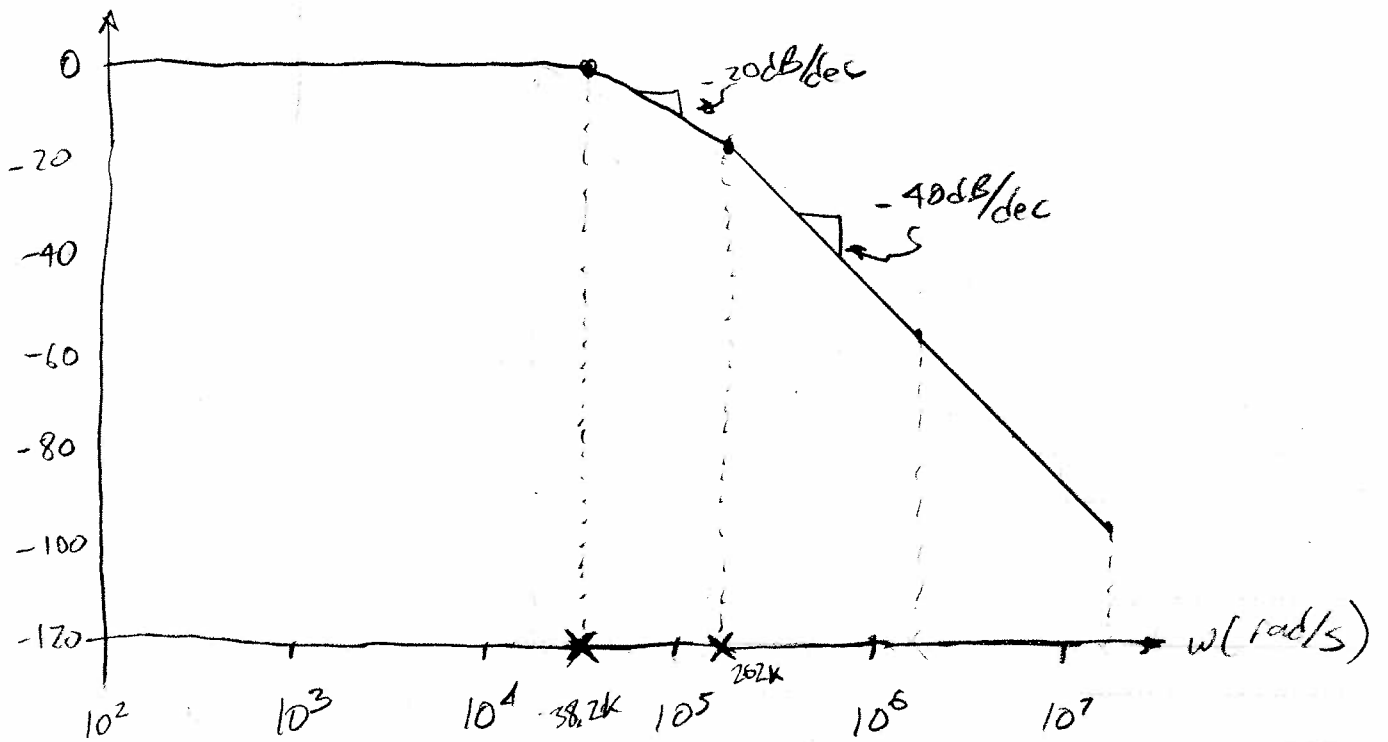


Phase (F(s)) (degrees)

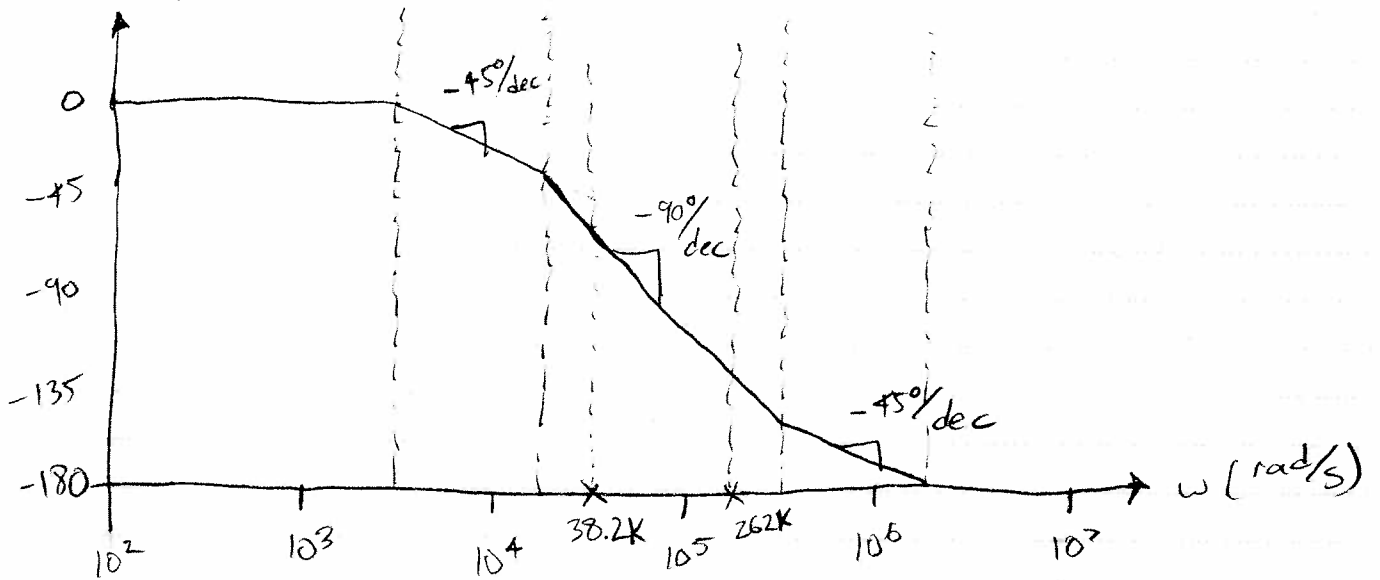


3.

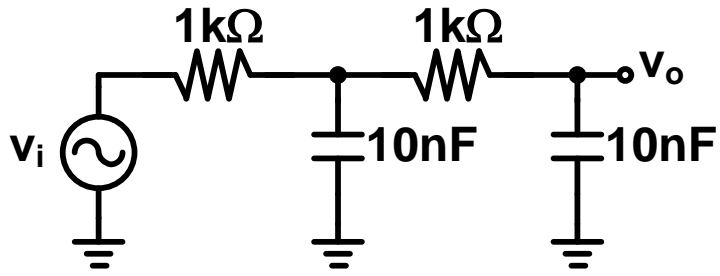

### Bode Plot

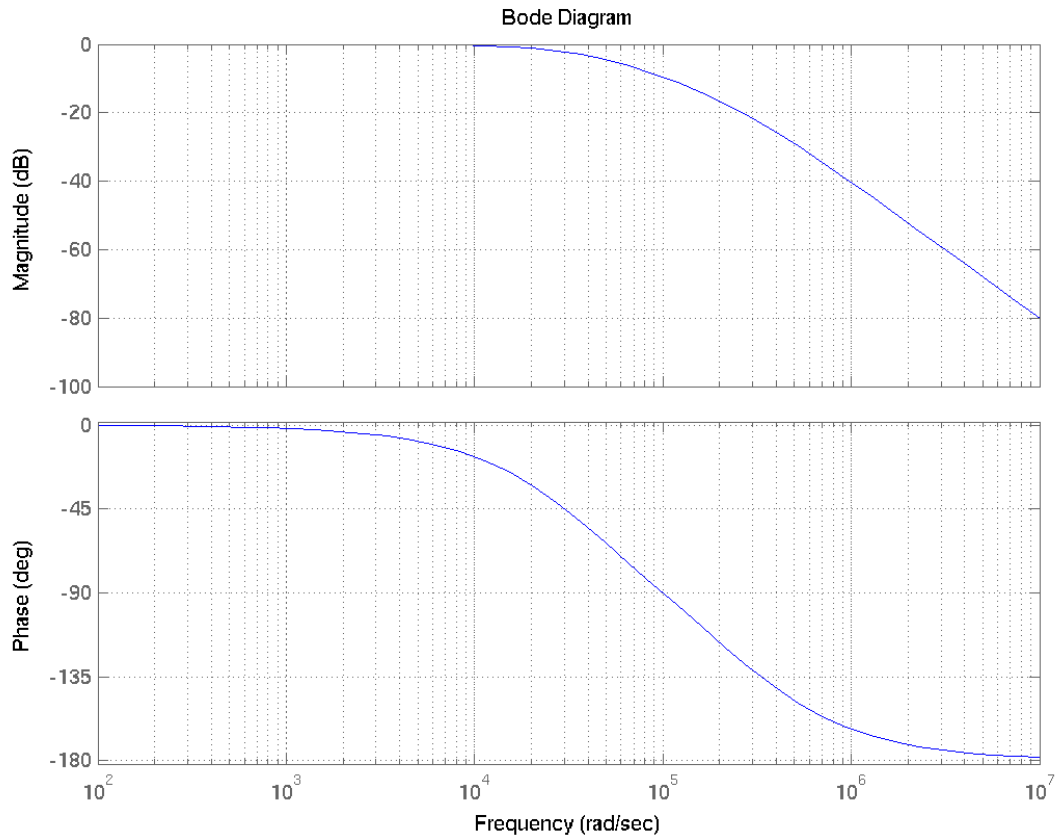

4.

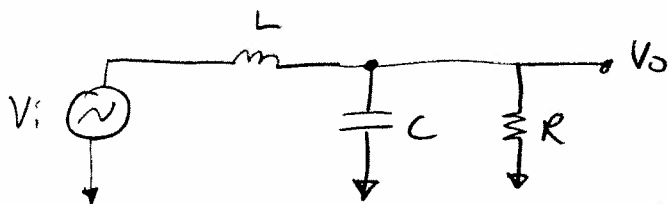

$$V_o(s) = \frac{Z_C \parallel Z_R}{Z_L + Z_C \parallel Z_R} V_i(s)$$

$$\frac{V_o(s)}{V_i(s)} = \frac{\frac{1}{sC + \frac{1}{R}}}{sL + \frac{1}{sC + \frac{1}{R}}} = \frac{1}{s^2 LC + s \frac{L}{R} + 1}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{\frac{1}{LC}}{s^2 + s \left(\frac{1}{RC}\right) + \frac{1}{LC}}$$

W/  $L = 1 \text{ nH}$ ,  $C = 1 \text{ pF}$ ,  $R = 25 \Omega$

$$F(s) = \frac{V_o(s)}{V_i(s)} = \frac{10^{21}}{s^2 + 4 \times 10^{10} s + 10^{21}}$$

$$\lim_{s \rightarrow 0} F(s) = \frac{10^{21}}{10^{21}} = 1$$

$$\lim_{s \rightarrow \infty} F(s) = \frac{10^{21}}{\infty} = 0$$

DC gain = 1

High Freq Gain = 0

Low-Pass Filter

2 poles at  $-2 \times 10^{10} \pm j 2.4 \times 10^{10} \text{ rad/s}$


From  $F(s)$  denominator...

$$s^2 + 2\zeta\omega_n s + \omega_n^2 = s^2 + 4 \times 10^{10} s + 10^{21}$$


$$\omega_n = 3.16 \times 10^{10} \text{ rad/s}, \zeta = 0.63$$

For Approximate Bode Plot, both poles at  $\approx \omega_n$


$20 \log_{10} |F(s)| \text{ (dB)}$

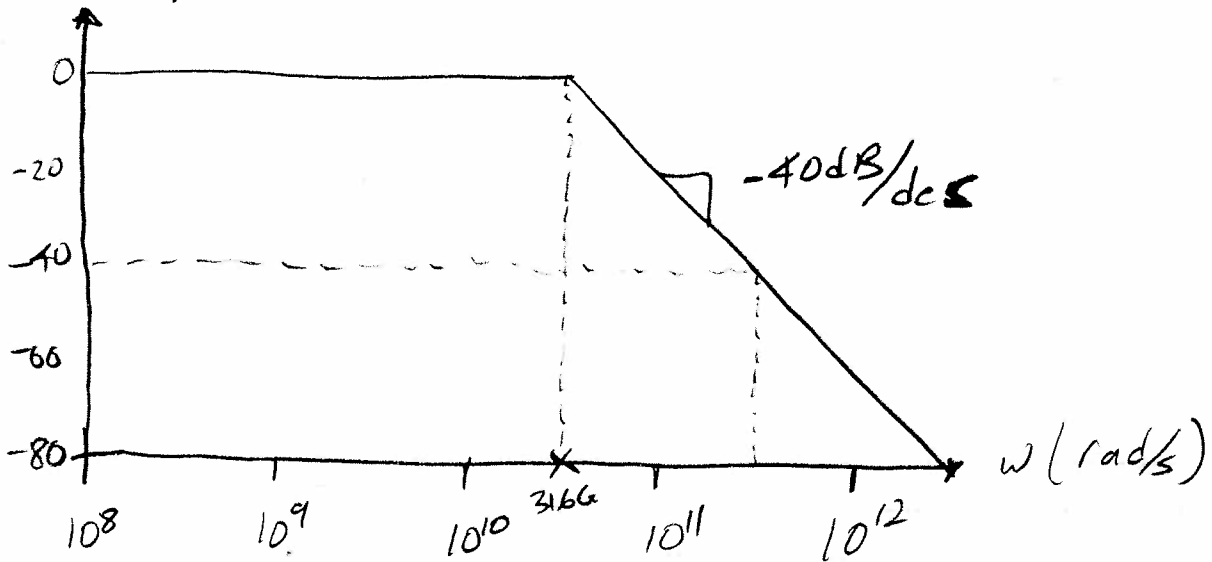

Phase  $(F(s)) \text{ (degrees)}$

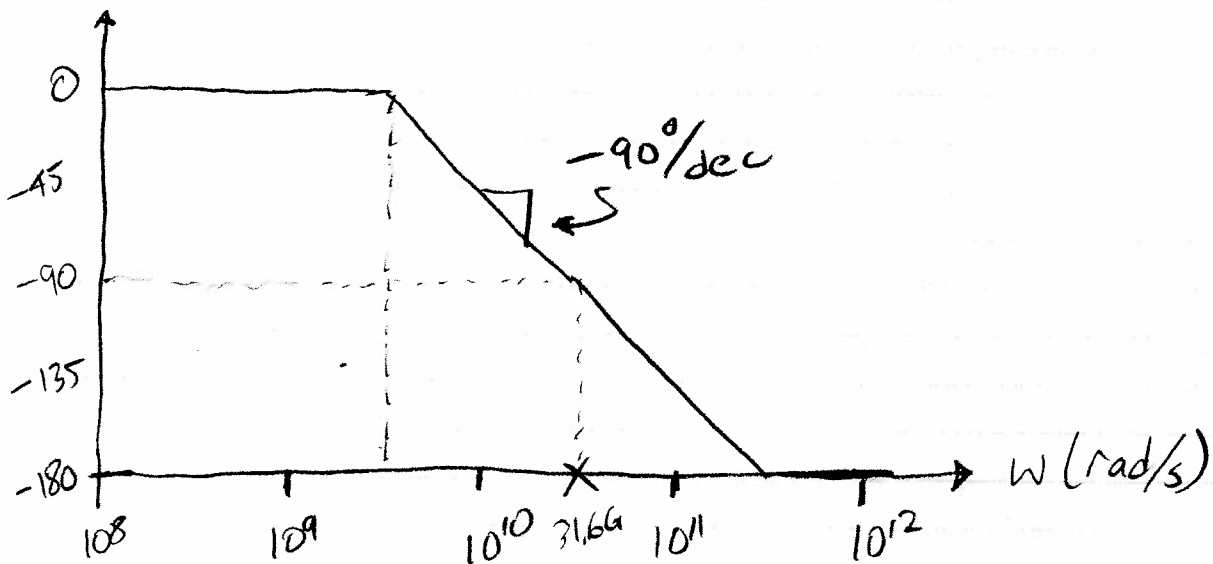

4.

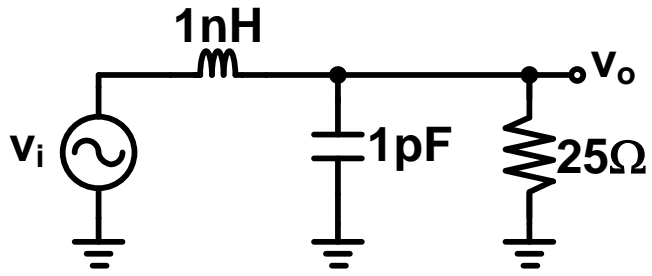

### Bode Plot

