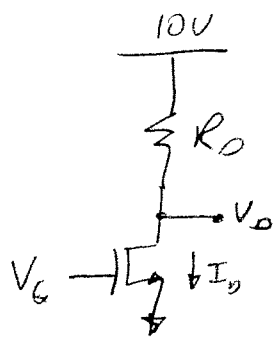


2.



$$K_{PN} = 100 \mu\text{A/V}$$

$$V_{TN} = 0.7\text{V}$$

$$W/L = 10 \mu\text{m}/1 \mu\text{m}$$

$$\text{Max } R_D \text{ for saturation} = \frac{10\text{V} - V_{DS_{\text{sat}}}}{I_{DSAT}}$$

$$\text{where } V_{DS_{\text{sat}}} = V_{GS} - V_{TN}$$

$$W/V_{GS} = 1\text{V} \Rightarrow V_{DS_{\text{sat}}} = 0.3\text{V}$$

$$V_{GS} = 2\text{V} \Rightarrow V_{DS_{\text{sat}}} = 1.3\text{V}$$

$$I_{DSAT} = \frac{1}{2} K_{PN} \frac{W}{L} (V_{GS} - V_{TN})^2$$

$$W/V_{GS} = 1\text{V} \Rightarrow I_{DSAT} = 45 \mu\text{A}$$

$$W/V_{GS} = 2\text{V} \Rightarrow I_{DSAT} = 845 \mu\text{A}$$

V_{GS}	$\text{Max } R_D$
1V	$\frac{10\text{V} - 0.3\text{V}}{45 \mu\text{A}} = 216 \text{K}\Omega$
2V	$\frac{10\text{V} - 1.3\text{V}}{845 \mu\text{A}} = 10.3 \text{K}\Omega$

$$w/ V_G = 2V \quad \therefore R_D = 5k\Omega$$

$$R_D = 5k\Omega \leq R_{MAX} = 10,3k\Omega$$

\therefore Transistor is saturated.

$$\begin{aligned} w/ R_D = 5k\Omega \quad I_D &= 845 \mu A \\ V_D &= 10V - I_D R_D = 10V - 845 \mu A (5k\Omega) = 5,78V \end{aligned}$$

$$w/ V_G = 2V \quad \therefore R_D = 15k\Omega$$

$$R_D = 15k\Omega > R_{MAX} = 10,3k\Omega$$

\therefore Transistor is in triode.

$$I_D = K'_N \frac{W}{L} \left[V_{GS} - V_{TN} - \frac{1}{2} V_{DS} \right] V_{DS}$$

$$I_D = (1m^2/V) \left[1,3V - 0,5(10V - I_D 15k\Omega) \right] (10V - I_D 15k\Omega)$$


$$\Rightarrow 112,5 \times 10^3 I_D^2 - 129,5 I_D + 37 \times 10^{-3} = 0$$

$$I_D = \underline{527 \mu A}, \quad \underline{\text{OR}} \quad 624 \mu A$$

$$V_D = 2,1V \Rightarrow \text{still in sat.} \\ \text{(not valid)}$$

$$V_D = 0,64V \Rightarrow \text{triode (valid)}$$
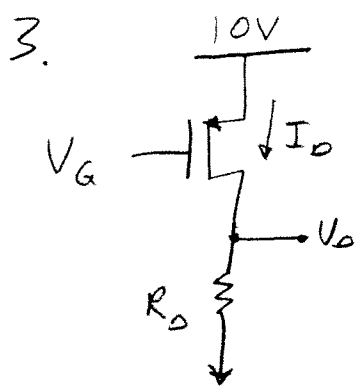
$$\begin{aligned} w/ R_D = 15k\Omega \quad I_D &= 624 \mu A \\ V_D &= 0,64V \end{aligned}$$



$$K_P = 30 \mu A/V$$

$$V_{TP} = -1V$$

$$W/L = 10$$

$$\text{Max } R_D \text{ for saturation} = \frac{10V - V_{SDSAT}}{I_{DSAT}}$$

$$\text{where } V_{SDSAT} = V_{SG} - |V_{TP}|$$

$$W/V_G = 8.5V \Rightarrow V_{SDSAT} = 0.5V$$

$$W/V_G = 7.5V \Rightarrow V_{SDSAT} = 1.5V$$

$$I_{DSAT} = \frac{1}{2} K_P \frac{W}{L} (V_{SG} - |V_{TP}|)^2$$

$$W/V_G = 8.5V \Rightarrow I_{DSAT} = 37.5 \mu A$$

$$W/V_G = 7.5V \Rightarrow I_{DSAT} = 337.5 \mu A$$

V_G	Max R_D
8.5V	$\frac{10V - 0.5V}{37.5 \mu A} = 253k\Omega$
7.5V	$\frac{10V - 1.5V}{337.5 \mu A} = 25.2k\Omega$

$$W/V_G = 7.5V \quad \frac{1}{3} R_D = 20k\Omega$$

$$R_D = 20k\Omega \leq R_{max} = 25.2k\Omega$$

\therefore Transistor is saturated

$$\frac{W}{R_D} = 20k\Omega$$

$$I_D = 337.5 \mu A$$

$$V_D = I_D R_D = 337.5 \mu A (20k\Omega) = 6.75V$$

$$W/V_G = 7.5V \quad \frac{1}{3} R_D = 40k\Omega$$

$$R_D = 40k\Omega > R_{max} = 25.2k\Omega$$

\therefore Transistor is in triode.

$$I_D = K_P \frac{W}{L} \left[V_{SG} - |V_{TP}| - \frac{1}{2} V_{SD} \right] V_{SD}$$

$$I_D = (0.3 \text{ mA/V}) \left[1.5V - 0.5(10V - I_D 40k\Omega) \right] (10V - I_D 40k\Omega)$$

$$\Rightarrow 240 \times 10^3 I_D^2 - 10 I_D + 10.5 \times 10^{-3} = 0$$

$$I_D = 187.5 \mu A \quad \underline{\text{OR}} \quad 233.3 \mu A$$


$$V_D = 7.5V \Rightarrow \text{still in sat (not valid)}$$

$$V_D = 9.33V \Rightarrow \text{triode (valid)}$$

$$\frac{W}{R_D} = 40k\Omega$$

$$I_D = 233.3 \mu A$$

$$V_D = 9.33V$$

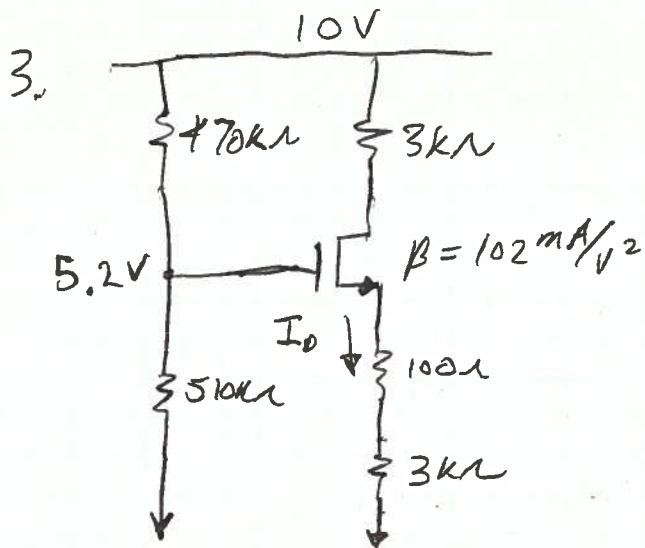

$$K_{PN} \frac{W}{L} = \beta = 102 \text{ mA/V}^2$$

$$V_{TN} = 2.0 \text{ V}$$

$$\lambda = 0.01 \text{ V}^{-1} \quad (\text{no calc only})$$

$$V_G = 10 \text{ V} \left(\frac{510 \text{ k}}{470 \text{ k} + 510 \text{ k}} \right) = 5.20 \text{ V}$$

$$I_D = \frac{1}{2} K_{PN} \frac{W}{L} \left[V_G - I_D R_S - V_{TN} \right]^2$$

$$I_D^2 R_S^2 - I_D \left[2(V_G - V_{TN}) R_S + \frac{2}{K_{PN} \frac{W}{L}} \right] + (V_G - V_{TN})^2 = 0$$

$$9.61 \times 10^6 I_D^2 - 19.86 \times 10^3 I_D + 10.24 = 0$$

$$I_D = 987 \mu\text{A} \quad \underline{\text{OR}} \quad 1.08 \text{ mA}$$

$$V_S = I_D R_S = 3.06 \text{ V} \quad \underline{\text{OR}} \quad 3.35 \text{ V} \quad (\text{inconsistent})$$

(valid)

$$V_D = 10 \text{ V} - 3 \text{ k}\Omega (987 \mu\text{A}) = 7.04 \text{ V}$$

$$g_m = K_{PN} \frac{W}{L} (V_{GS} - V_{TN}) = (102 \text{ mA/V}^2) (2.14 - 2.0) = 14.3 \text{ mA/V}$$

$$r_o = \frac{1}{\lambda I_D} = \frac{1}{(0.01 \text{ V}^{-1})(987 \mu\text{A})} = 101 \text{ k}\Omega$$

$V_D = 7.04 \text{ V}$	$I_D = 987 \mu\text{A}$	$g_m = 14.3 \text{ mA/V}$
$V_G = 5.2 \text{ V}$		$r_o = 101 \text{ k}\Omega$
$V_S = 3.06 \text{ V}$		


ECEN 325

Homework #8 Multisim

Instructor: Sam Palermo

3.

DC Operating Points

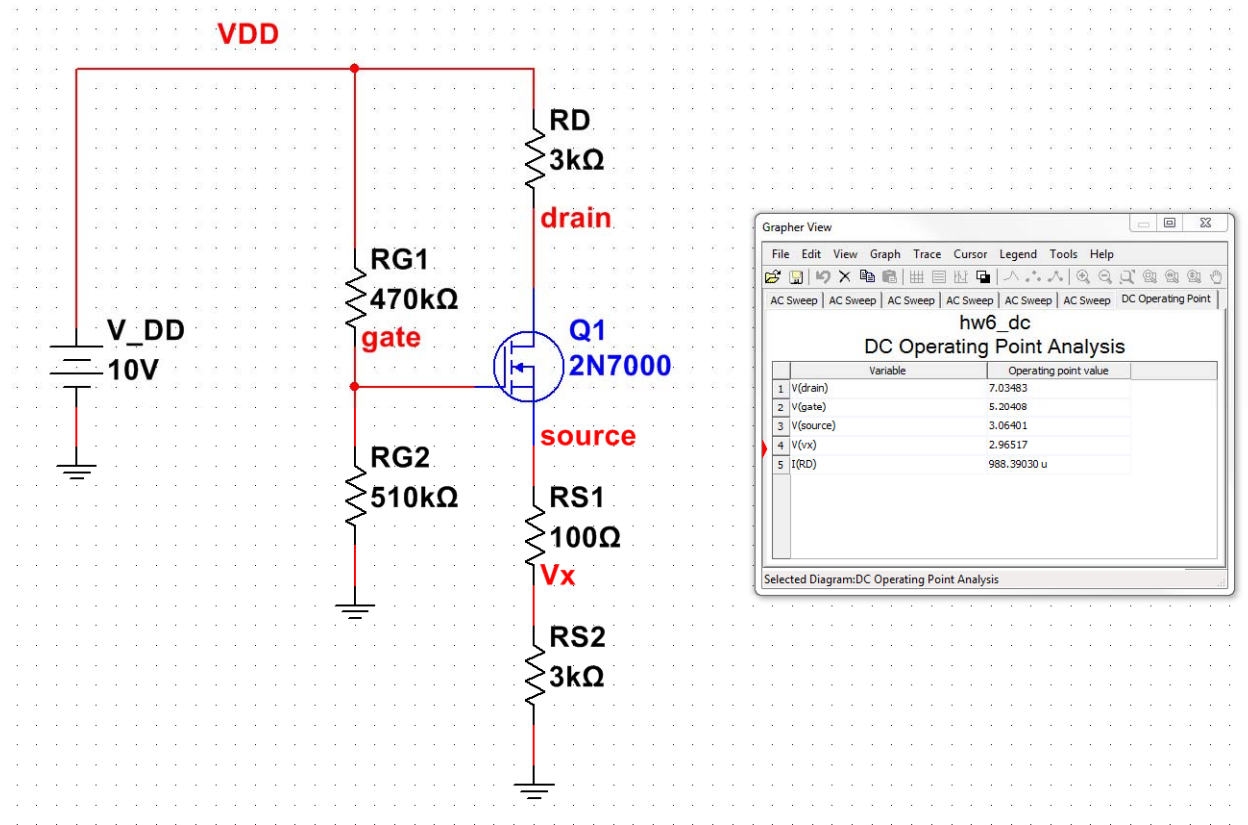

4. Common Source Amplifier

$$A_v = - \frac{g_m (R_o \parallel R_L)}{1 + g_m R_{S1}} = - \frac{(14.3 \text{ mA/V})(3 \text{ k}\Omega \parallel 120 \text{ k}\Omega)}{1 + (14.3 \text{ mA/V})(100 \text{ }\Omega)}$$

$$A_v = -15.4 \text{ V/V} = 23.7 \text{ dB}$$

$$R_{in} = R_{\theta} = 470 \text{ k}\Omega \parallel 510 \text{ k}\Omega = 245 \text{ k}\Omega$$

$$R_{in} = 245 \text{ k}\Omega = 108 \text{ dB}\Omega$$


$$R_{out} = R_o = 3 \text{ k}\Omega = 69.5 \text{ dB}\Omega$$

$$G_v = \frac{R_{in}}{R_{in} + R_{S1}} A_v = \frac{245 \text{ k}\Omega}{245 \text{ k}\Omega + 50} (-15.4)$$

$$G_v = -15.4 \text{ V/V} = 23.7 \text{ dB}$$


2. Common Source Amplifier

A_v and G_v

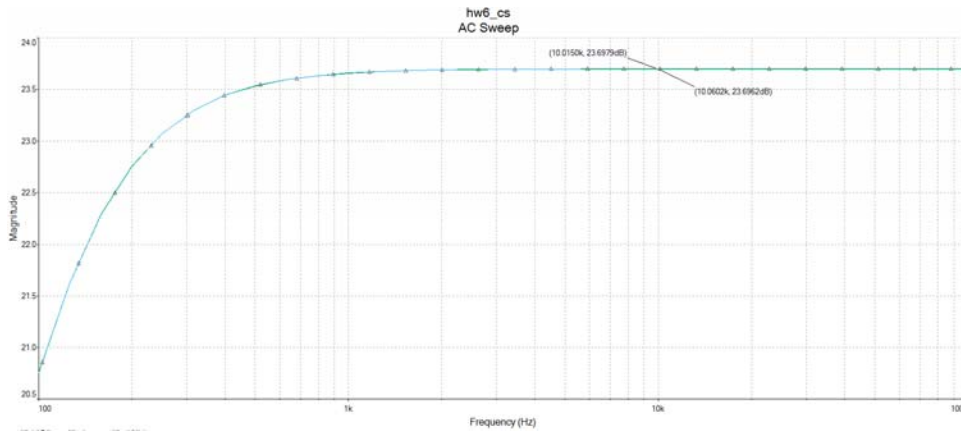


The simulated value of 23.7dB closely matches the hand calculation of 23.7dB for both A_v and G_v .

R_{in}

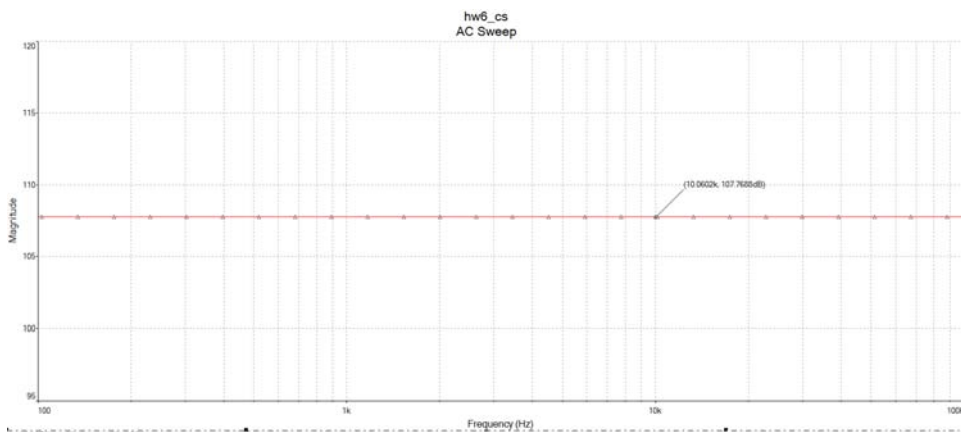

The simulated R_{in} value of 108dBΩ matches the hand calculation of 108dBΩ.

R_{out}

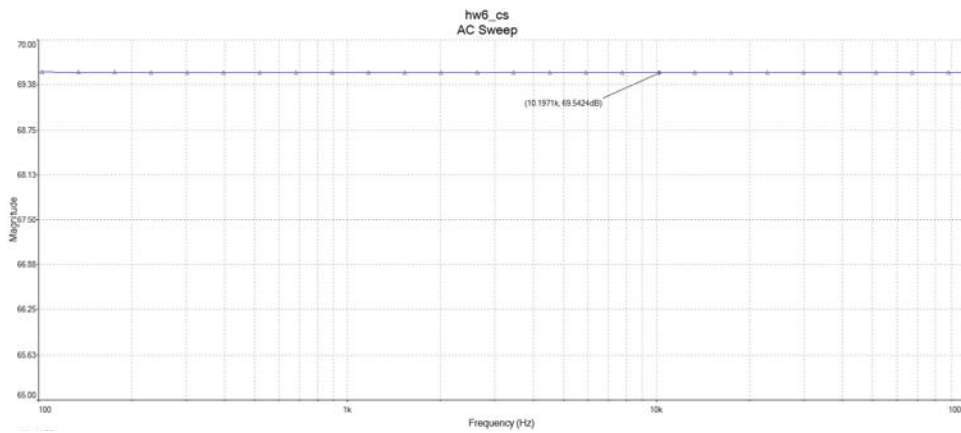

The simulated R_{out} value of 69.5dBΩ closely matches the hand calculation of 69.5dBΩ.

5. Common Drain Amplifier

$$A_v = \frac{g_m (R_s \parallel R_L)}{1 + g_m (R_s \parallel R_L)} = \frac{14.3 \text{ mA/V} (3.1 \text{ k}\Omega \parallel 20 \text{ k}\Omega)}{1 + 14.3 \text{ mA/V} (3.1 \text{ k}\Omega \parallel 20 \text{ k}\Omega)}$$

$$A_v = 0.975 \text{ V/V} = -0.22 \text{ dB}$$

$$R_{in} = R_G = 470 \text{ k}\Omega \parallel 510 \text{ k}\Omega = 245 \text{ k}\Omega$$

$$R_{in} = 245 \text{ k}\Omega = 108 \text{ dB}\Omega$$

$$R_{out} = R_s \parallel \frac{1}{g_m} = 3.1 \text{ k}\Omega \parallel \frac{1}{14.3 \text{ mA/V}}$$


$$R_{out} = 68.4 \Omega = 36.7 \text{ dB}\Omega$$

$$G_v = \frac{R_{in}}{R_{in} + R_{vs}} A_v = \frac{245 \text{ k}\Omega}{245 \text{ k}\Omega + 50} (0.975)$$

$$G_v = 0.975 \text{ V/V} = -0.22 \text{ dB}$$


3. Common Drain Amplifier

A_v and G_v

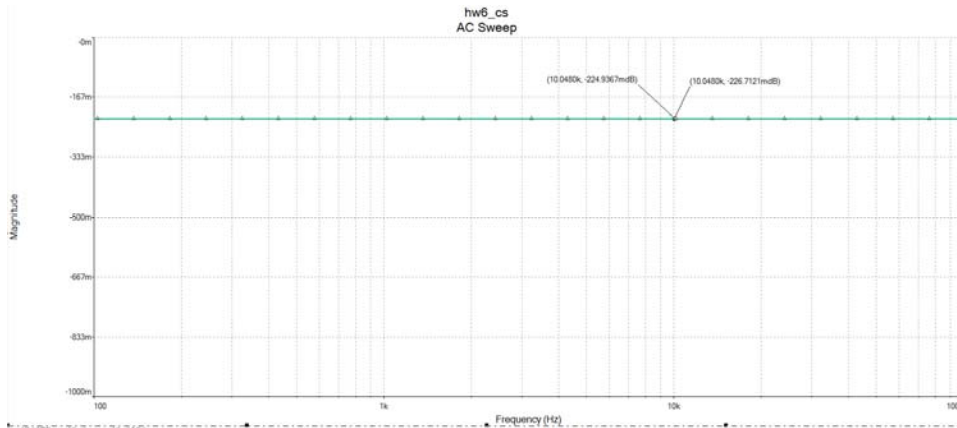


The simulated value of -0.22dB and -0.23dB closely matches the hand calculation of -0.22dB for both A_v and G_v , respectively.

R_{in}

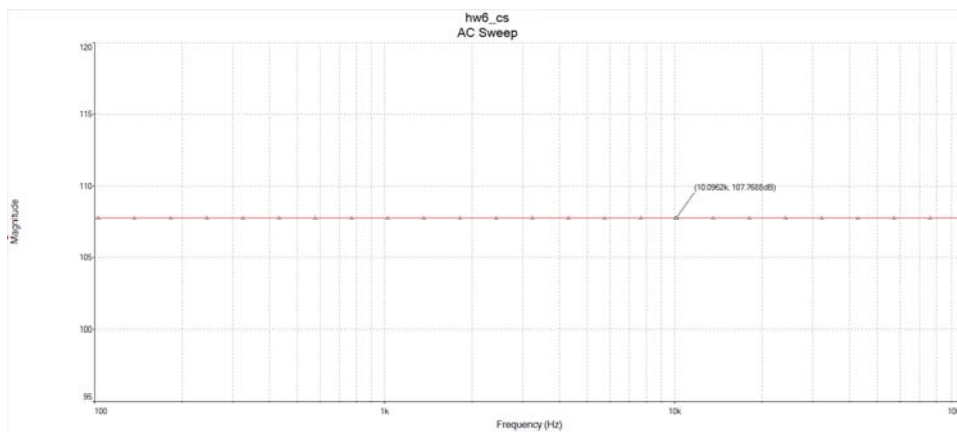

The simulated R_{in} value of 108dB Ω matches the hand calculation of 108dB Ω .

R_{out}

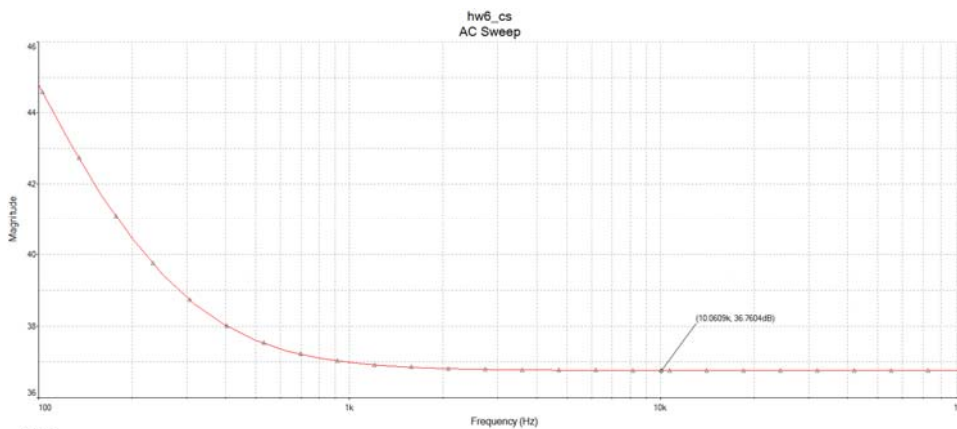

The simulated R_{out} value of 36.8dB Ω closely matches the hand calculation of 36.7dB Ω .

6. Common Gate Amplifier

$$A_v = g_m (R_o \parallel R_L) = (14.3 \text{ mA/V}) (3 \text{ k}\Omega \parallel 20 \text{ k}\Omega)$$

$$A_v = 37.3 \text{ V/V} = 31.4 \text{ dB}$$

$$R_{in} = R_s \parallel \frac{1}{g_m} = 3.1 \text{ k}\Omega \parallel \frac{1}{14.3 \text{ mA/V}}$$

$$R_{in} = 68.4 \Omega = 36.7 \text{ dB}\Omega$$


$$R_{out} = R_o = 3 \text{ k}\Omega = 69.5 \text{ dB}\Omega$$

$$G_v = \frac{R_{in}}{R_{in} + R_{us}} A_v = \frac{68.4 \Omega}{68.4 \Omega + 50 \Omega} (37.3 \text{ V/V})$$

$$G_v = 21.5 \text{ V/V} = 26.7 \text{ dB}$$


4. Common Gate Amplifier

A_v and G_v

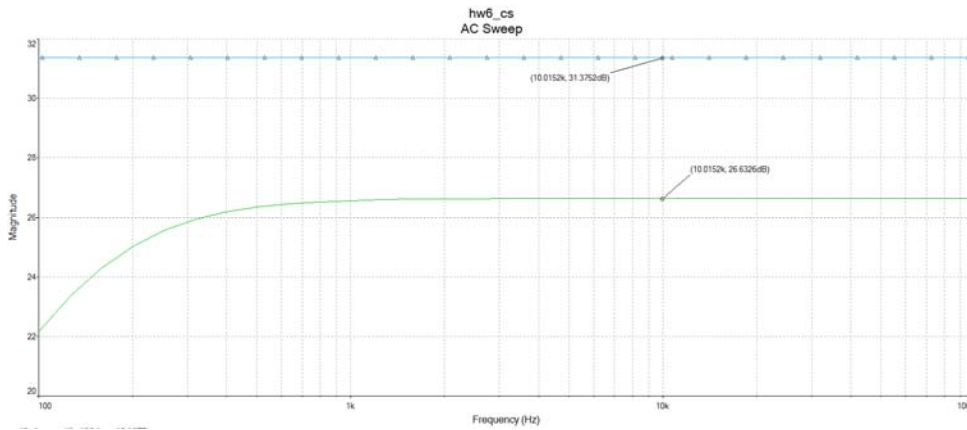


The simulated A_v value of 31.4dB matches closely the hand calculation of 31.4dB. The simulated G_v value of 26.6dB closely matches the hand calculation of 26.7dB.

R_{in}

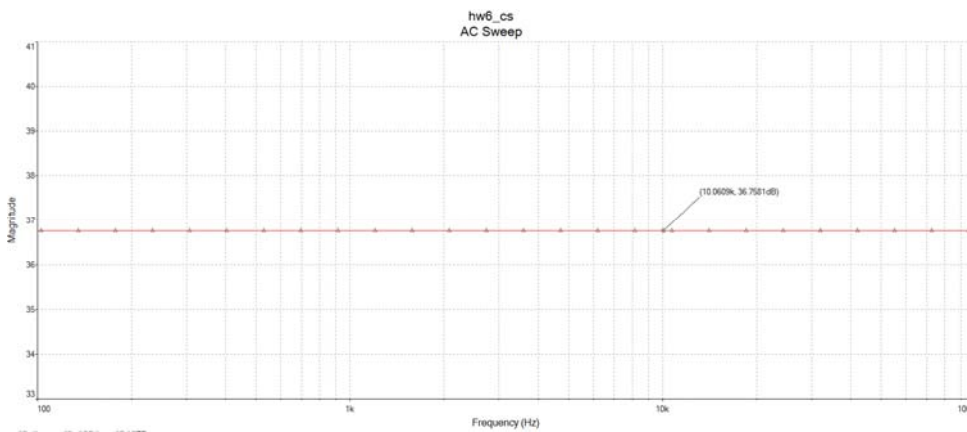

The simulated R_{in} value of 36.8dB Ω matches the hand calculation of 36.7dB Ω .

R_{out}

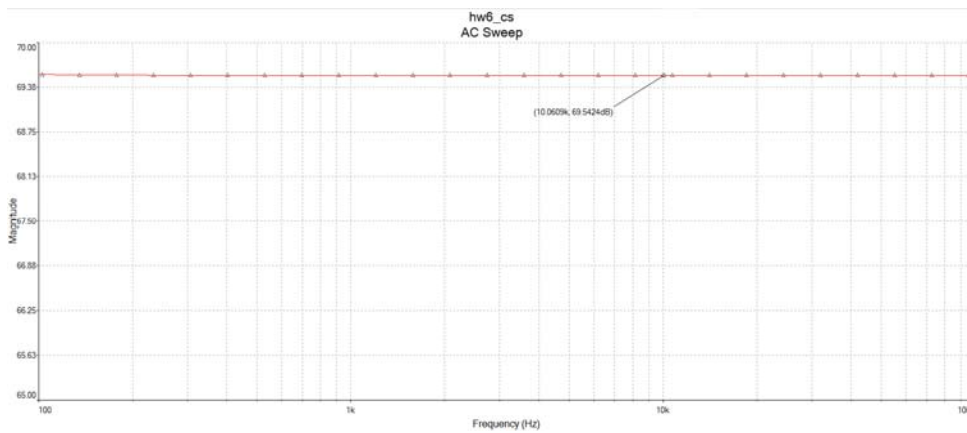

The simulated R_{out} value of 69.5dB Ω closely matches the hand calculation of 69.5dB Ω .