

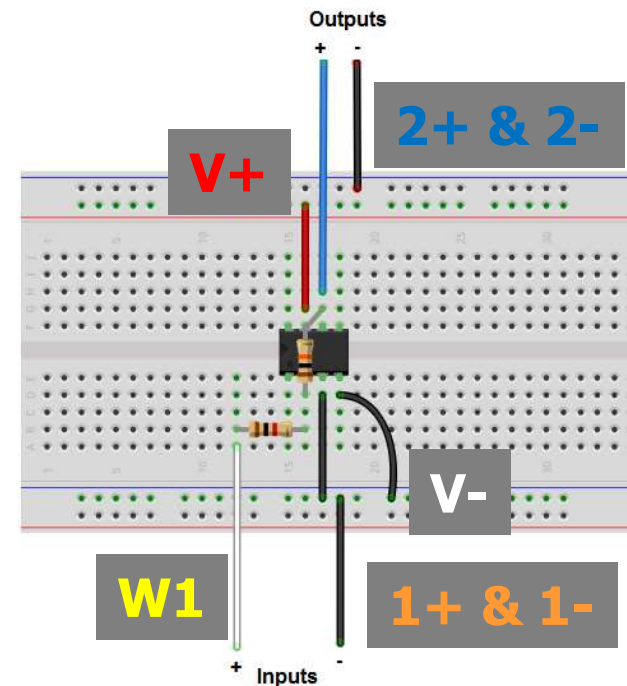
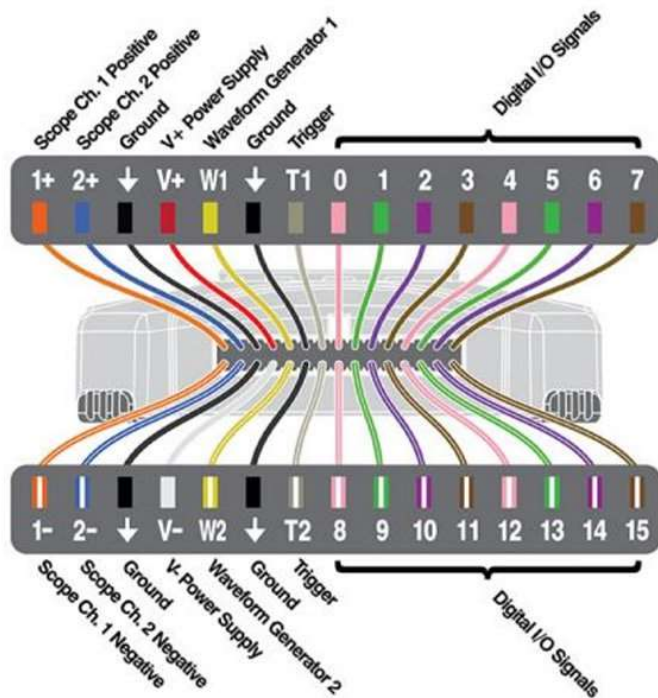


Lab 4 Review

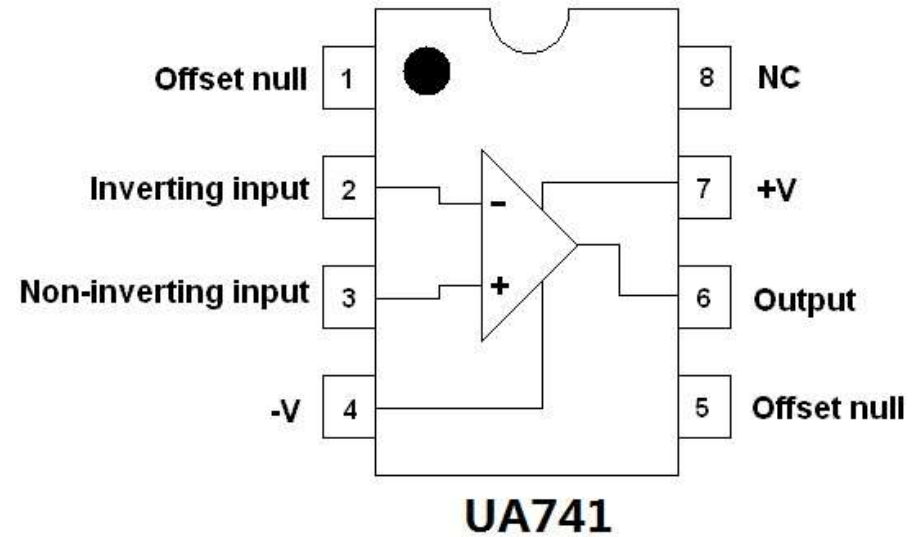


Julian Gomez
Texas A&M University


Connecting the IC

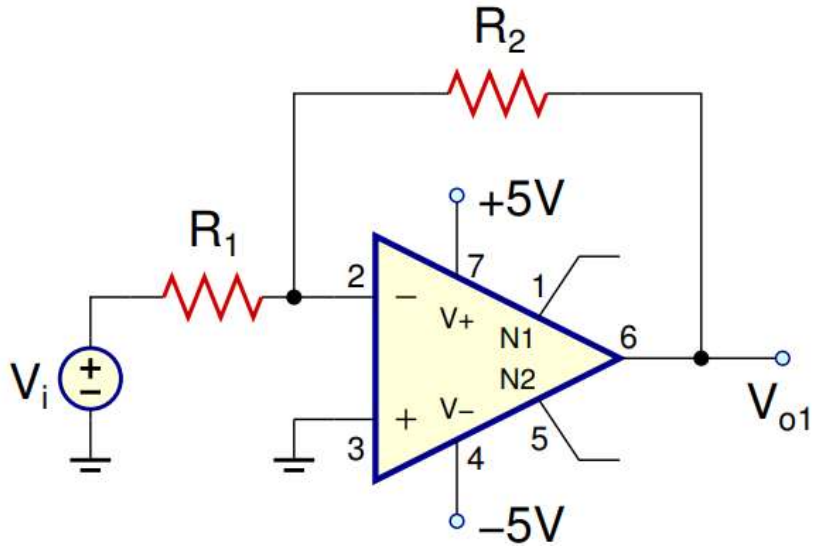

Summing Amplifier Circuit

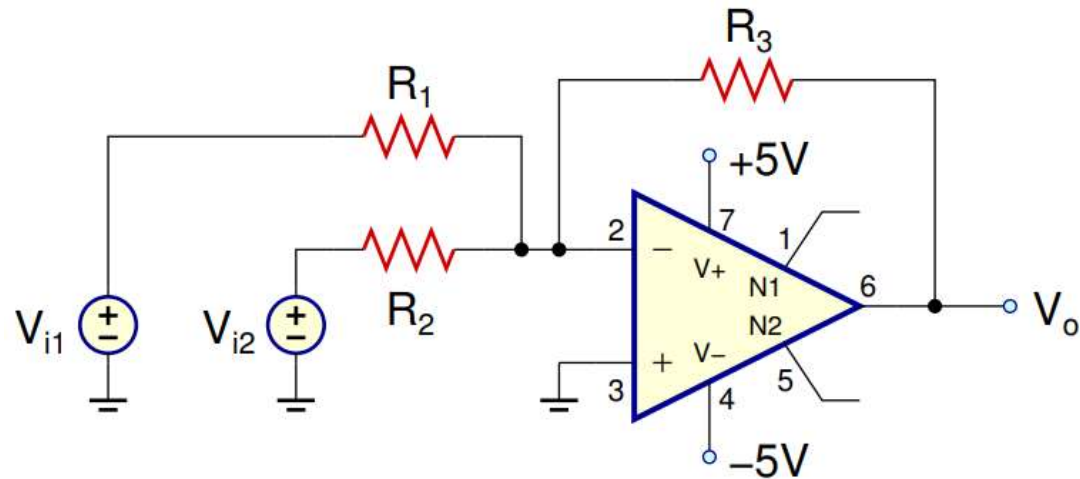


Using superposition...

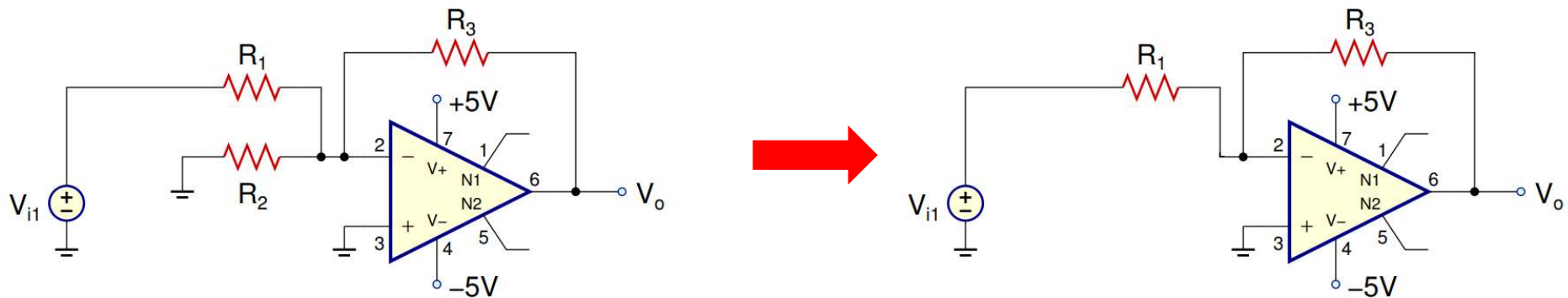

$$V_o = -\frac{R_3}{R_1} V_{i1}$$

Summing Amplifier Circuit

Similarly...

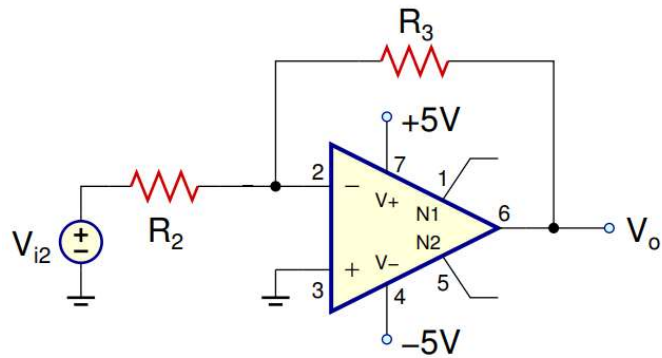

$$V_o = -\frac{R_3}{R_2} V_{i2}$$

Now, due to the superposition theorem we can add the two inputs independently


$$V_o = -\frac{R_3}{R_1} V_{i1} + \left(-\frac{R_3}{R_2} V_{i2} \right) = -\left(\frac{R_3}{R_1} V_{i1} + \frac{R_3}{R_2} V_{i2} \right)$$

For the summing amplifier in Fig. 1, find R_1 and R_2 to have $V_o = -(V_{i1} + 2V_{i2})$, if $R_3 = 15\text{k}\Omega$




$$\begin{aligned} R_1 &= 15 \text{ k}\Omega \\ R_2 &= 7.5 \text{ k}\Omega \end{aligned}$$

Differential Amplifier Circuit

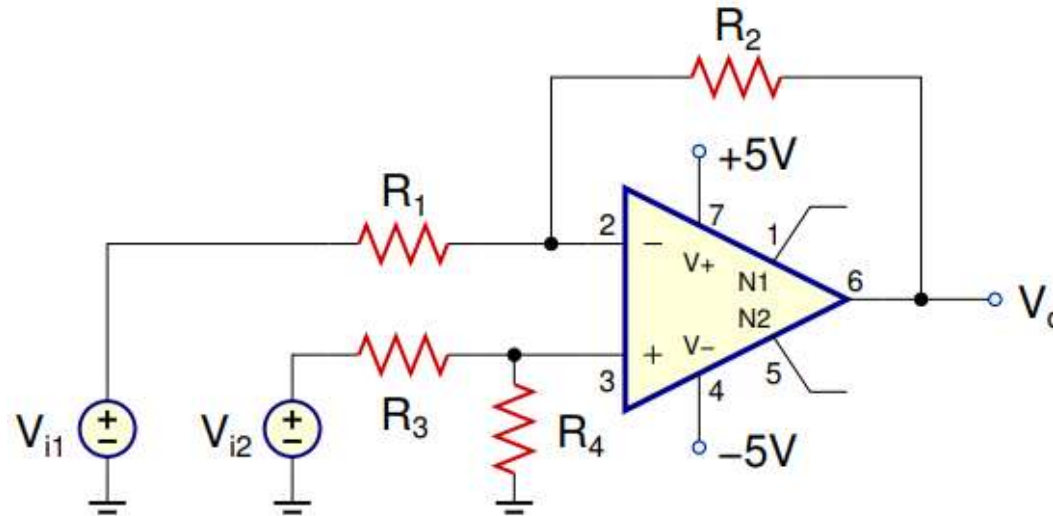


Using superposition...

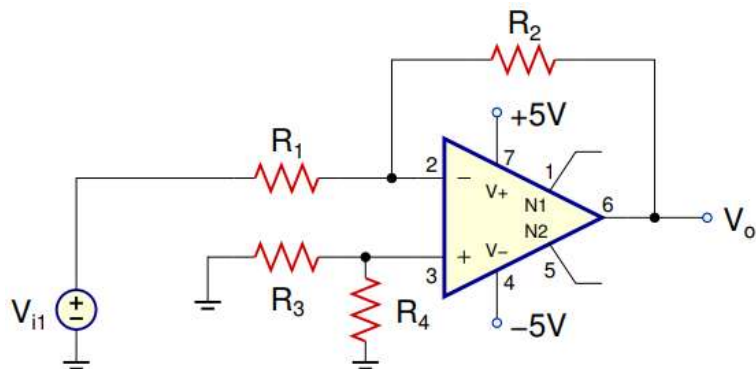

$$V_o = -\frac{R_2}{R_1} V_{i1}$$

Differential Amplifier Circuit

Similarly...

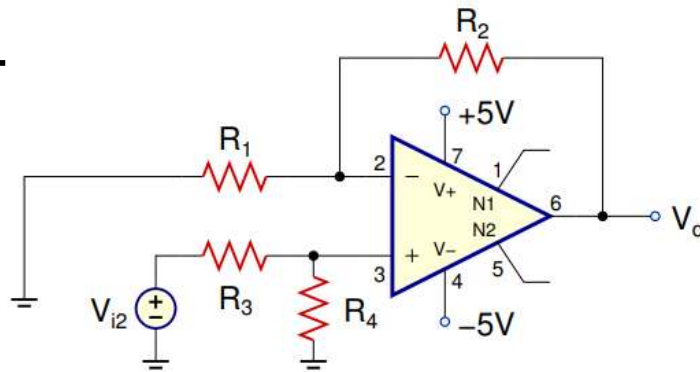

$$V_o = \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1} \right) V_{i2}$$

Now, due to the superposition theorem we can add the two inputs independently


$$V_o = -\frac{R_2}{R_1} V_{i1} + \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1} \right) V_{i2} \quad \text{or} \quad V_o = -\frac{R_2}{R_1} V_{i1} + \frac{\frac{R_4}{R_3}}{1 + \frac{R_4}{R_3}} \left(1 + \frac{R_2}{R_1} \right) V_{i2}$$

$$\text{If } R_2/R_1 = R_4/R_3 \dots \quad V_o = -\frac{R_2}{R_1} V_{i1} + \frac{\frac{R_2}{R_1}}{1 + \frac{R_2}{R_1}} \left(1 + \frac{R_2}{R_1} \right) V_{i2} \quad \rightarrow \quad V_o = \frac{R_2}{R_1} (V_{i2} - V_{i1})$$

For the differential amplifier in Fig. 2, find R_1 to have $V_o = V_{i2} - V_{i1}$, if $R_2 = R_3 = R_4 = 10\text{k}\Omega$.

→ $R_1 = 10\text{ k}\Omega$


Instrumentation Amplifier

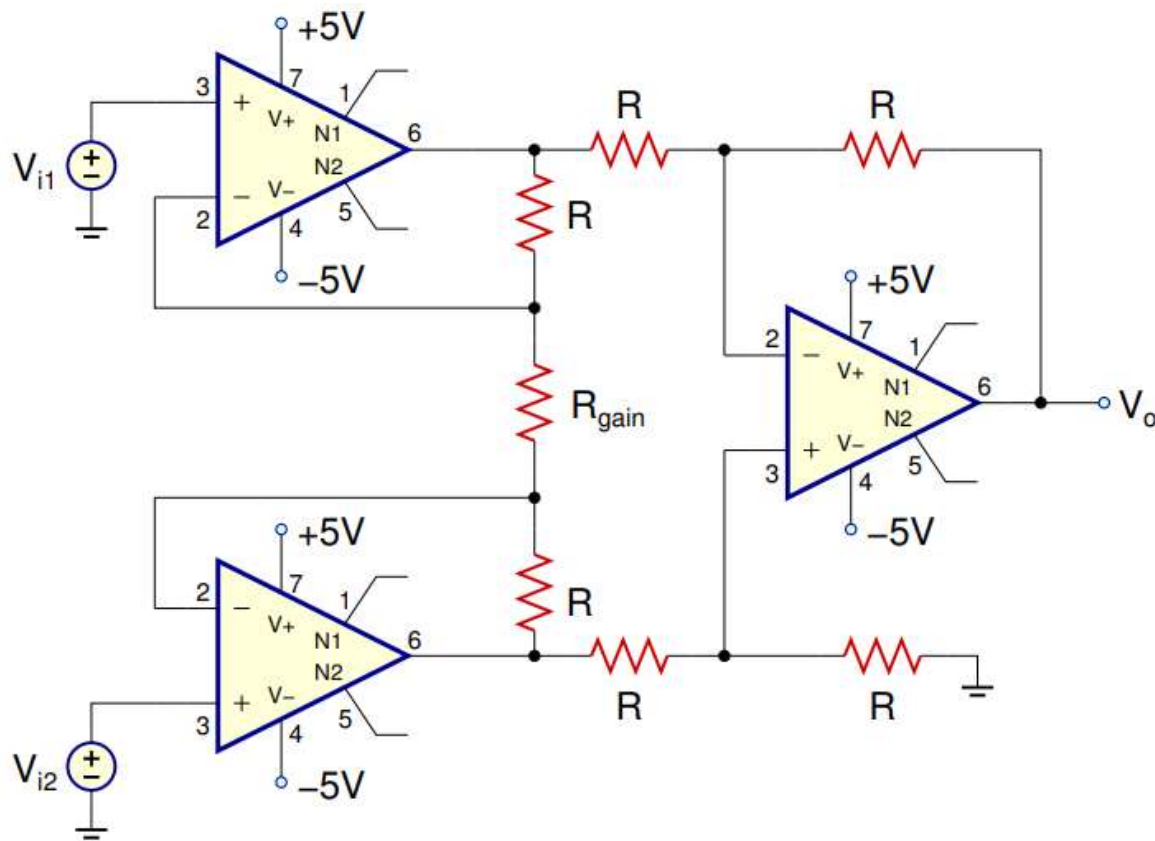

- The instrumentation amplifier offers the following advantages:
 - Very high input impedance
 - High common-mode rejection ratio
 - Low offset
 - Low noise

Instrumentation Amplifier

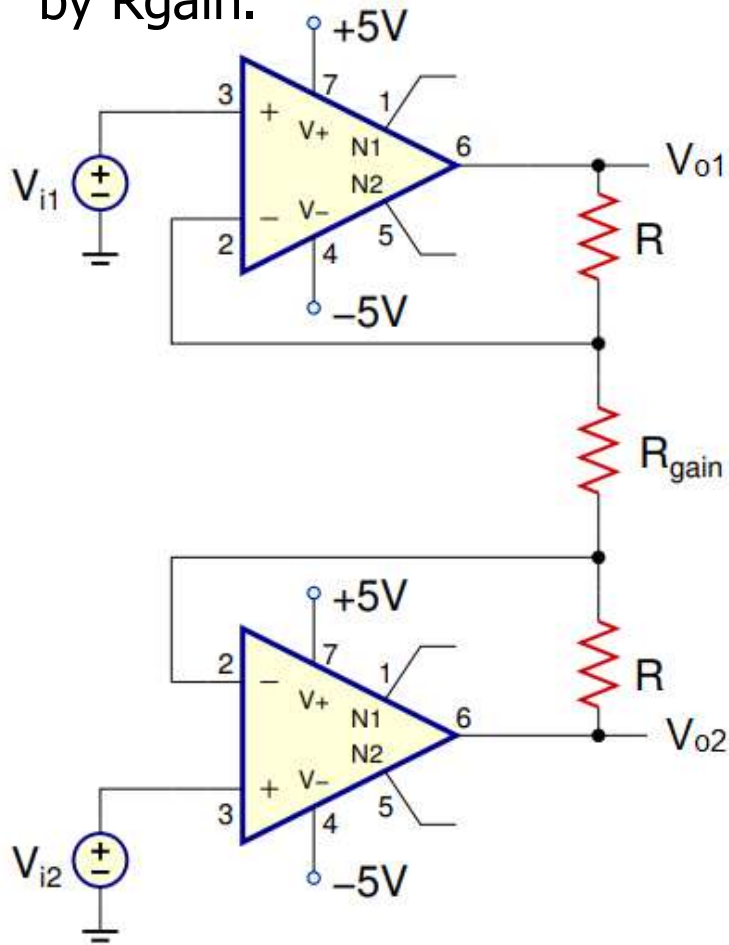The input stages operate as non-inverting amplifiers where the gain is defined by R_{gain} .



$$V_{o1,2} = \left(1 + \frac{R}{\frac{R_{gain}}{2}} \right) V_{i1,2}$$

$$V_{o2} - V_{o1} = \left(1 + \frac{2R}{R_{gain}} \right) (V_{i2} - V_{i1})$$

The third op-amp is working as the differential amplifier that we just analyzed.

$$V_o = V_{i2} - V_{i1}$$

