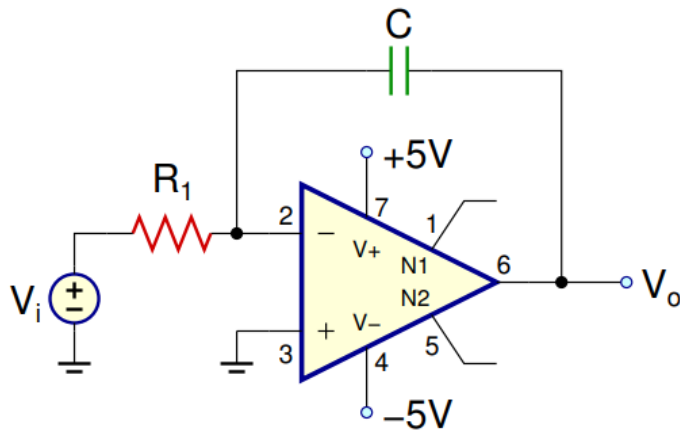


Lab 5 Review



Julian Gomez
Texas A&M University


Ideal Integrator



$$\frac{V_o}{V_i}(s) = -\frac{Z_c}{R_1} = -\frac{1}{sR_1C}$$

- The DC ($s=0$) gain is theoretically infinite
- This design is not practical since any small DC signal (like the input offset) will saturate the output over time

Lossy Integrator

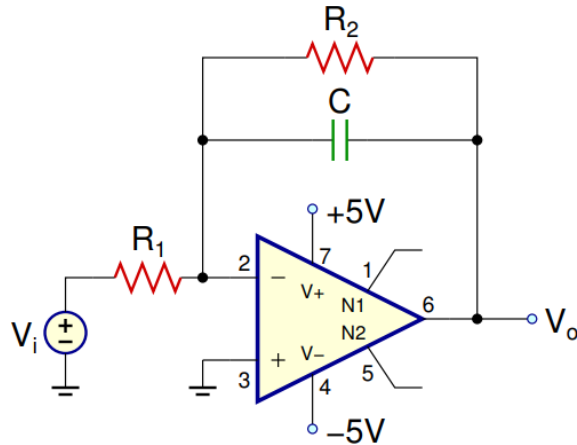



$$\frac{V_o}{V_i}(s) = -\frac{R_2 || Z_c}{R_1}$$

$$\frac{V_o}{V_i}(s) = -\frac{1}{R_1} \frac{R_2}{1 + sR_2C}$$

$$\frac{V_o}{V_i}(s) = -\frac{\frac{R_2}{R_1}}{1 + sR_2C}$$


- The lossy integrator is a practical implementation
- Includes a large parallel resistor to C to have a controlled DC gain
- It is a first-order low pass filter with low cut-off frequency

Bode Plot

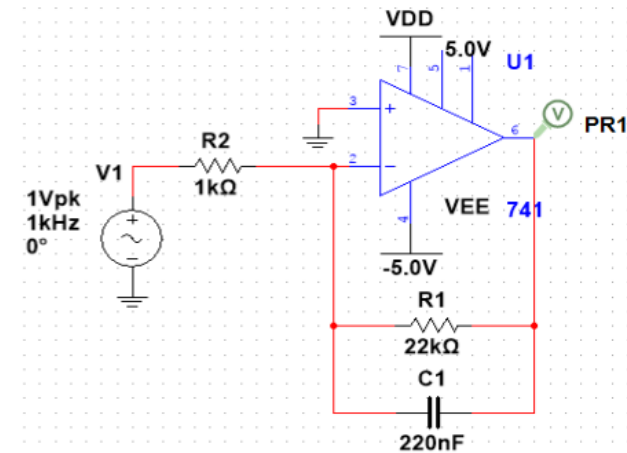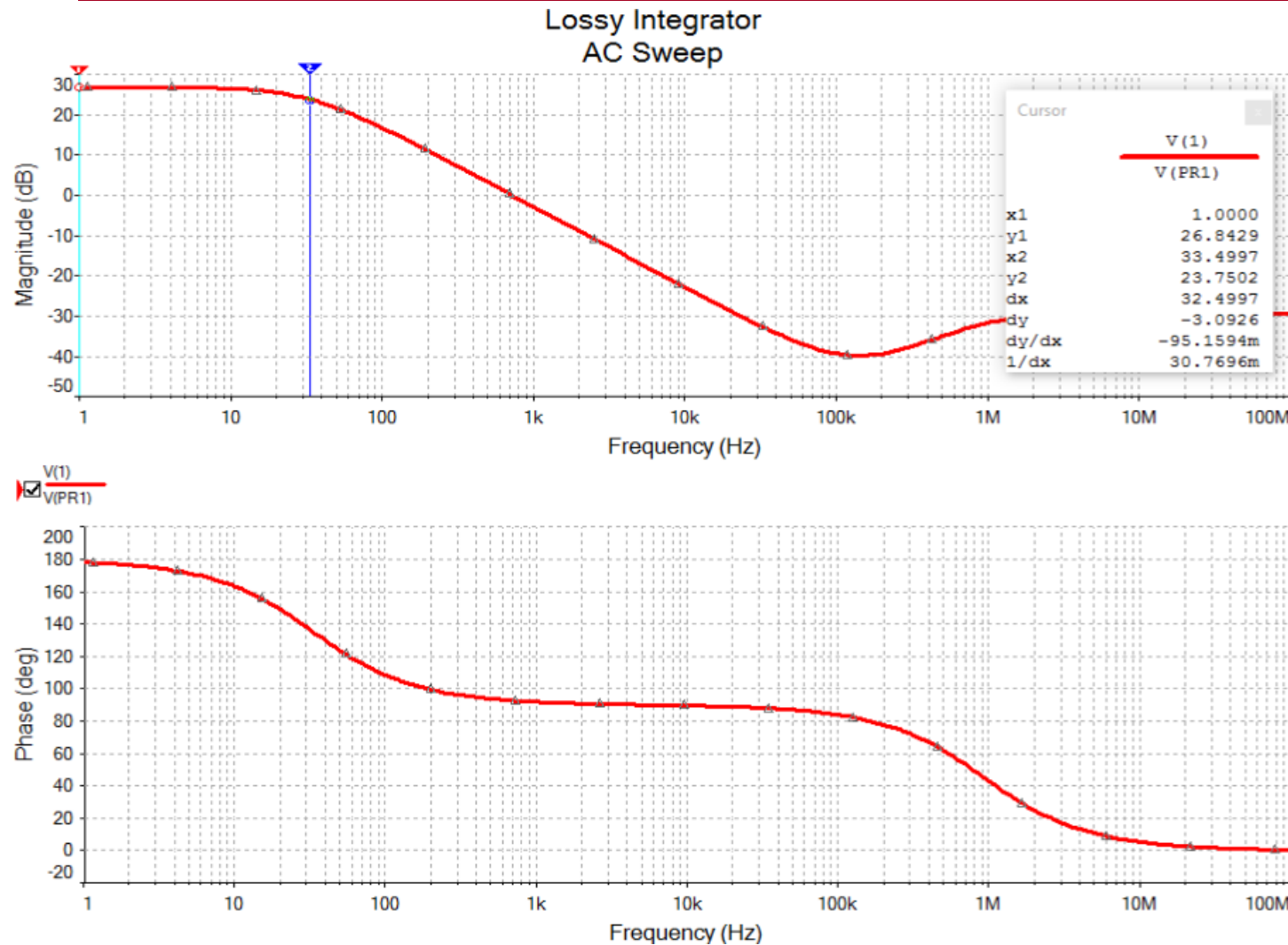



- First order LPF with f_{3dB} of 33 kHz and DC gain of -22 V/V or 26.84 dB

Transient

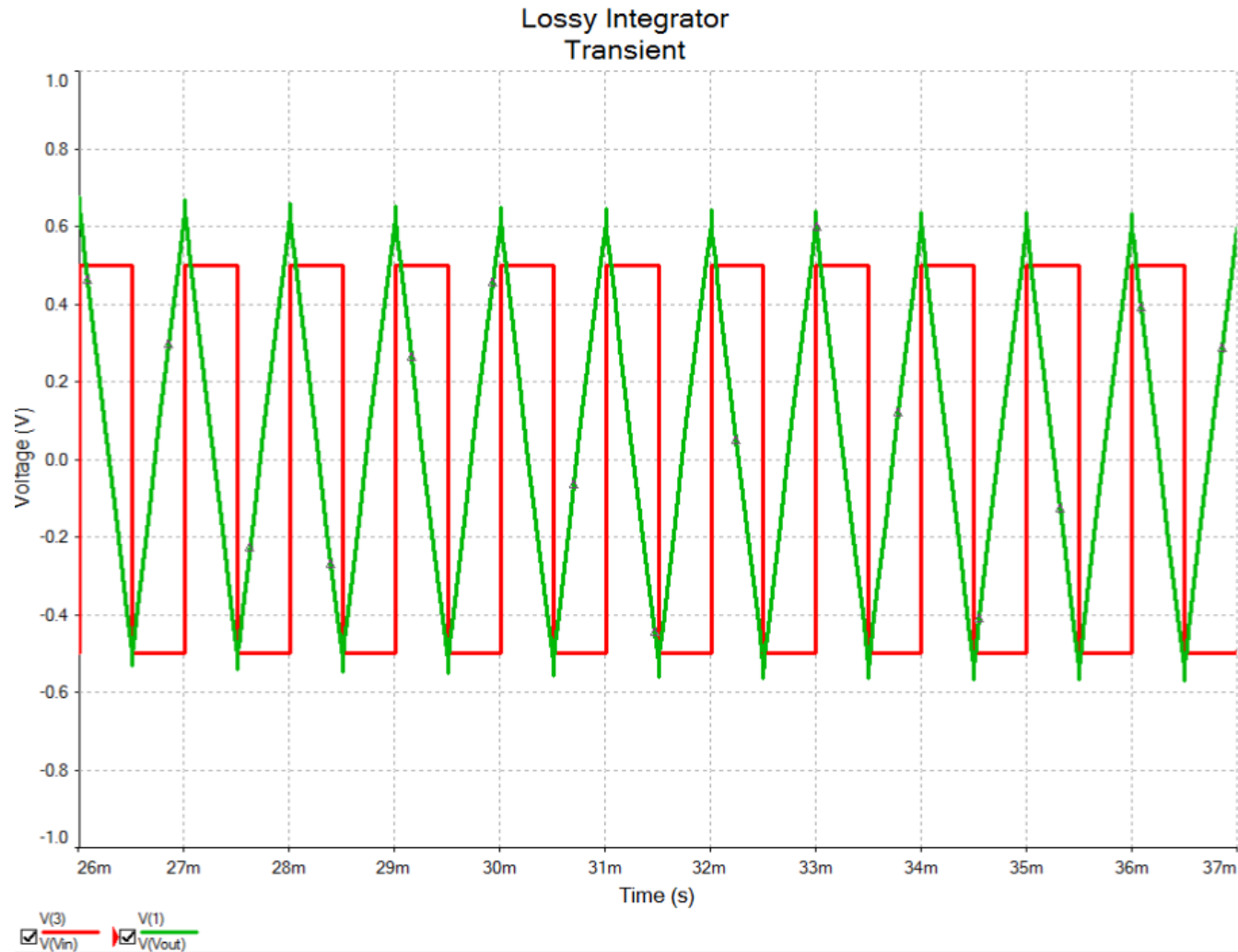

- What is the result of integrating a square wave?

Finite GBW Limitations

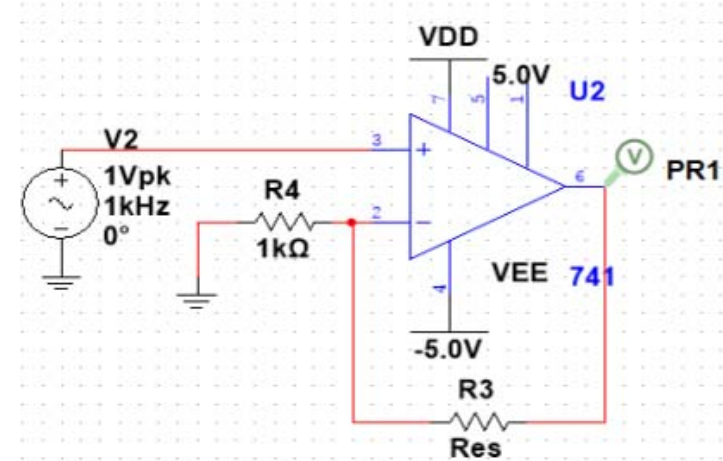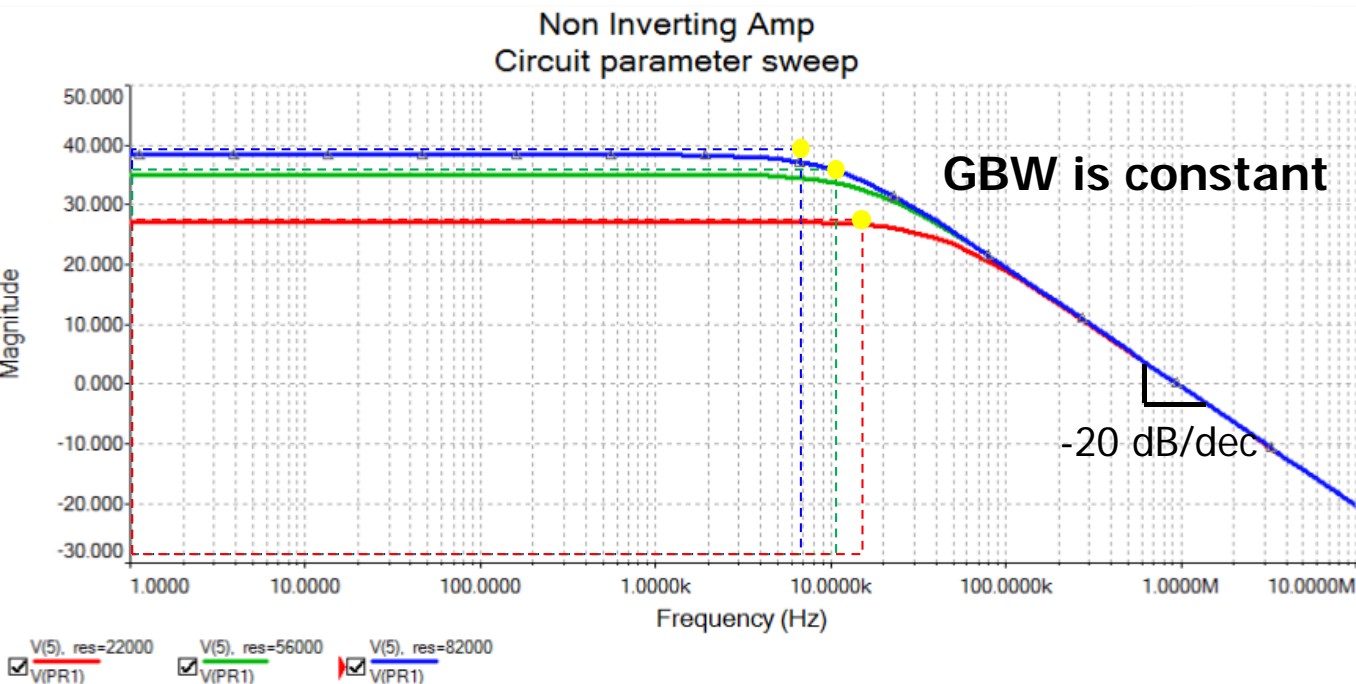


- The gain-bandwidth product is a finite constant
- There is a trade off between the gain and bandwidth of the closed-loop amplifier

Slew Rate Limitations

- The slew rate is the maximum rate of change at the output of the amplifier
- To avoid distortion:



$$\left. \frac{dV_{out}}{dt} \right|_{max} \leq SR \quad [V/s]$$

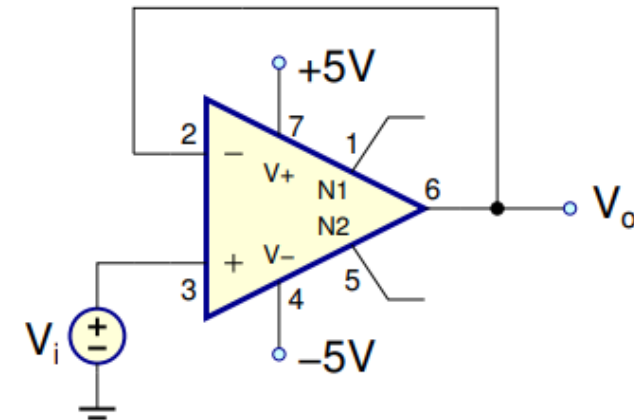

- If the output is a sinusoidal signal with amplitude A

$$\left. \frac{dV_{out}}{dt} \right|_{max} = A2\pi f \cos(2\pi ft) \Big|_{max} = A2\pi f \leq 0.5 \frac{V}{\mu s}$$

Slew Rate Limitations

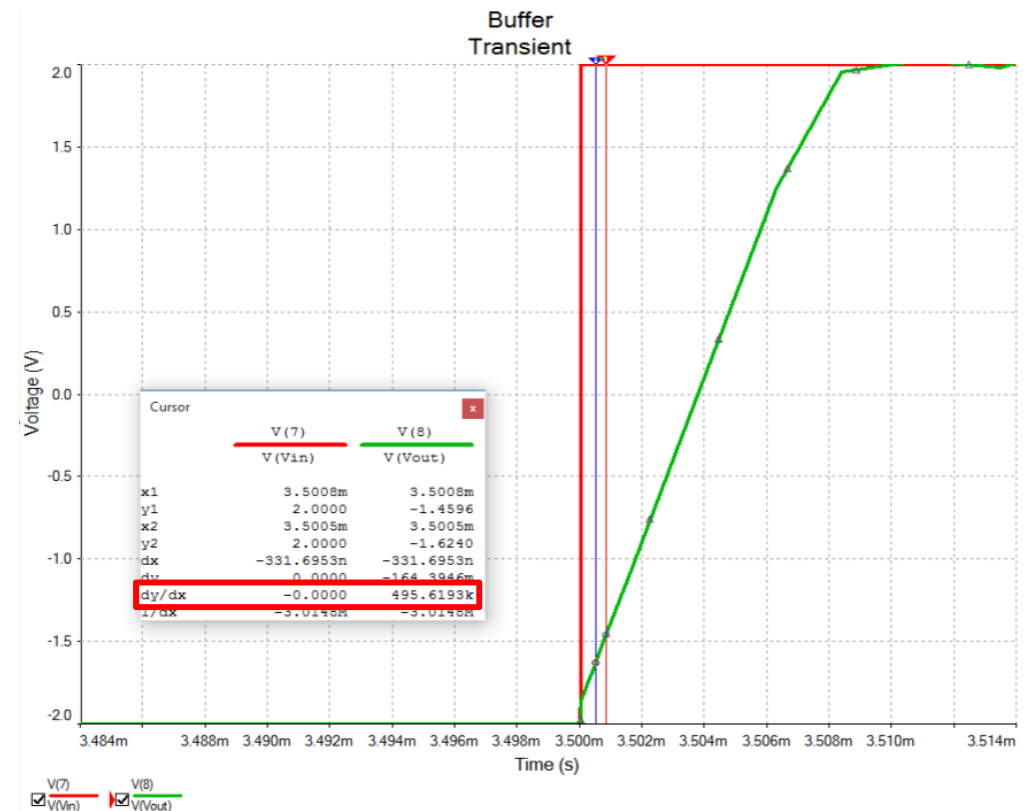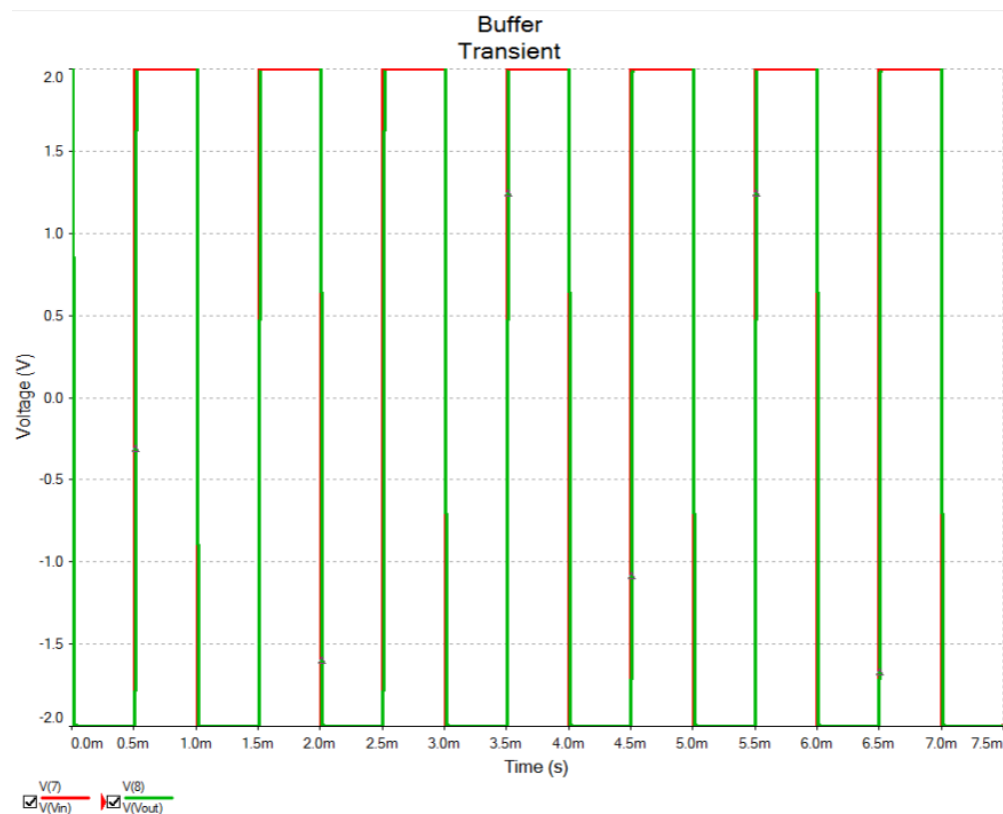

- The slew rate can be measured in the lab by feeding a large square signal to the circuit and measuring the slope at the rising edge

