


# **ECEN 325**

## **Electronics**


Operational Amplifiers

*Dr. Aydın İlker Karşılıyan*

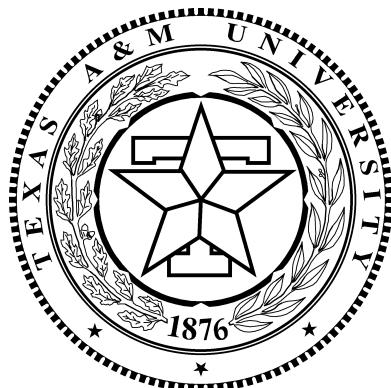
Texas A&M University  
Department of Electrical and Computer Engineering




# Opamp Terminals

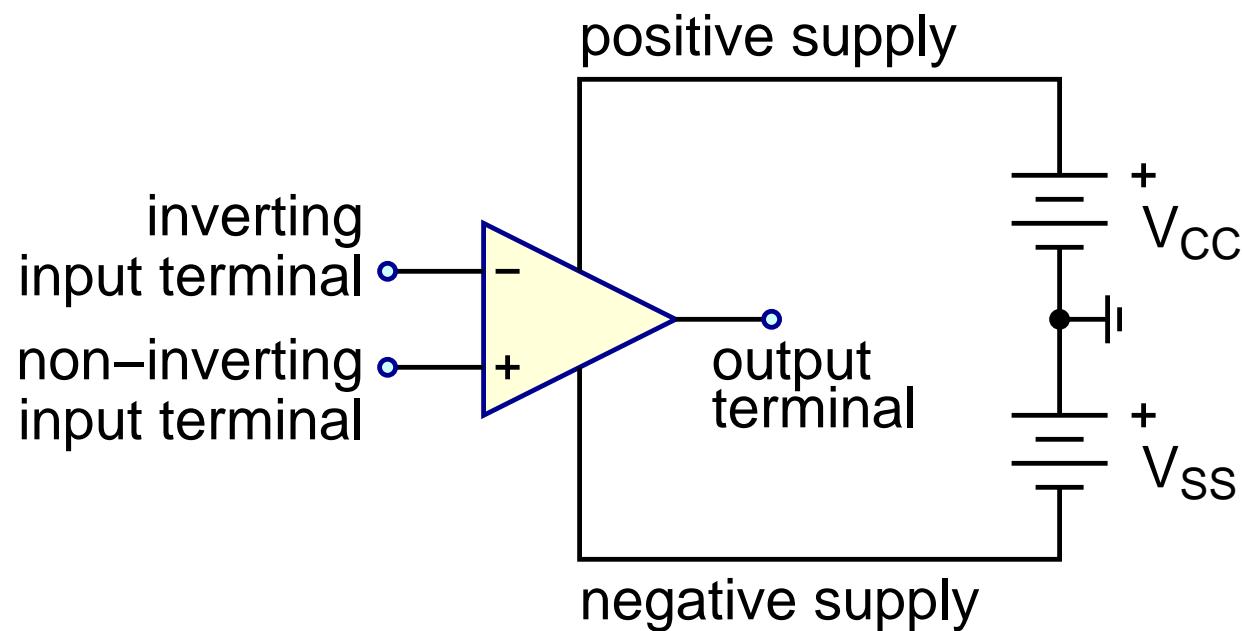


# Equivalent Circuit

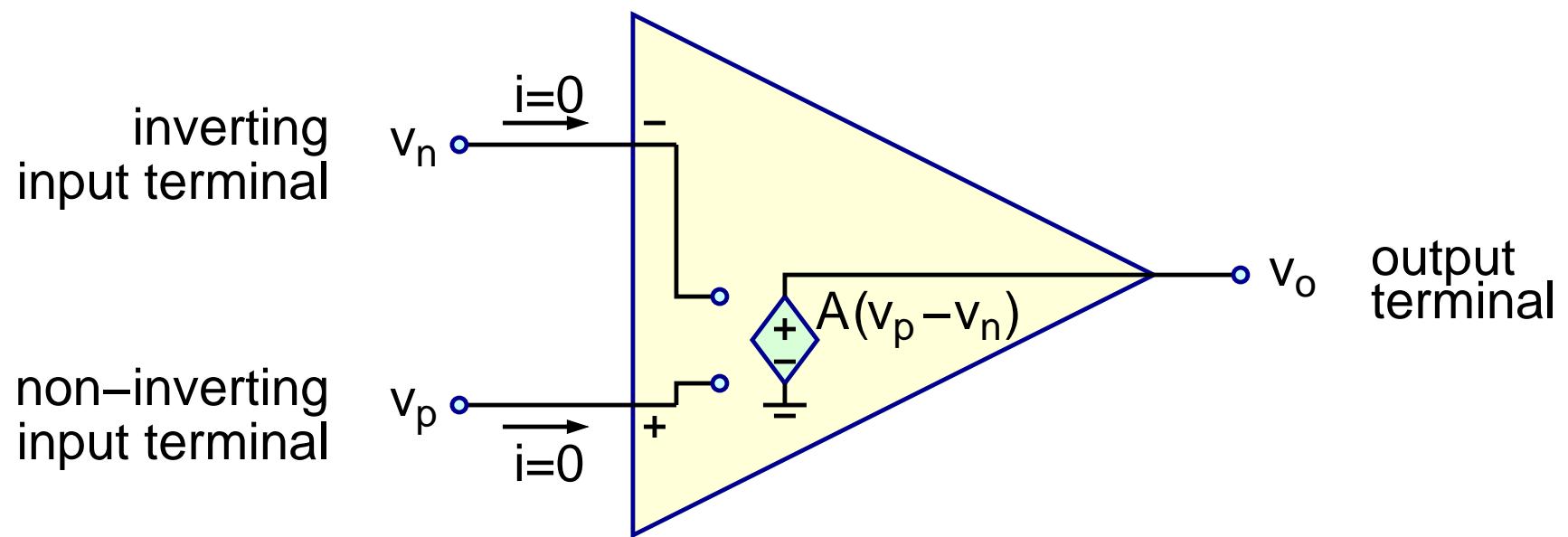

## $V_o$ VS. $V_d$

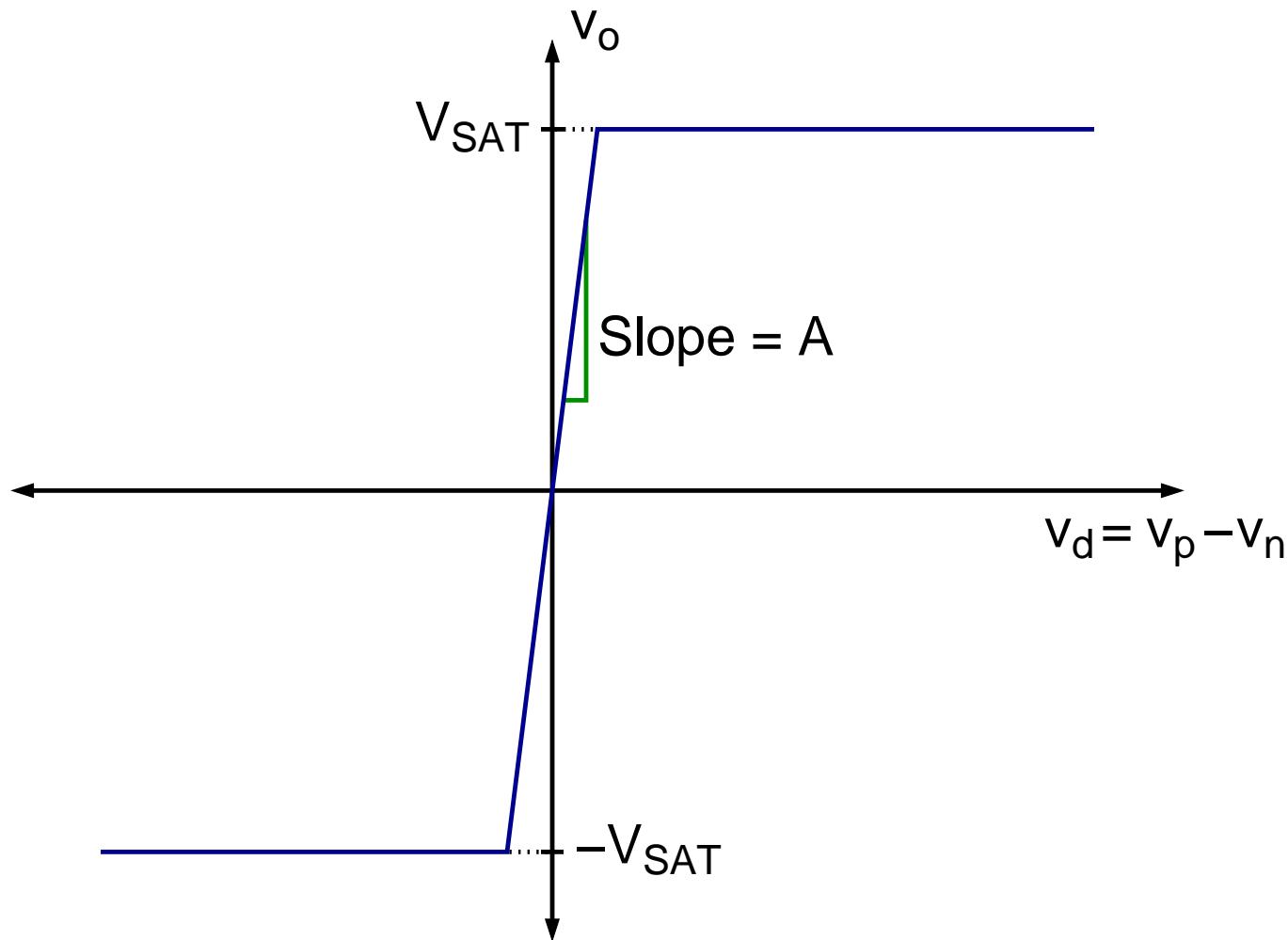


## Inverting Configuration

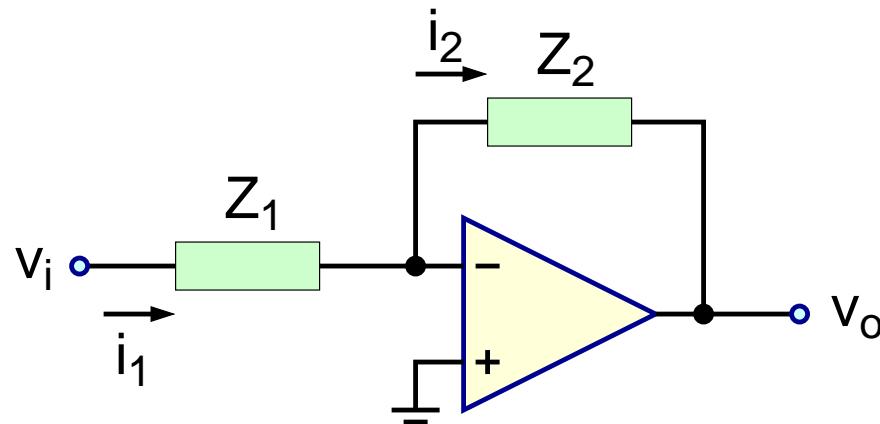

$$\frac{v_o}{v_i} = \frac{-\frac{Z_2}{Z_1}}{1 + \frac{(1 + \frac{Z_2}{Z_1})}{A}}$$


$$A \rightarrow \infty \Rightarrow \frac{v_o}{v_i} = -\frac{Z_2}{Z_1}$$

# Inverting Amplifier

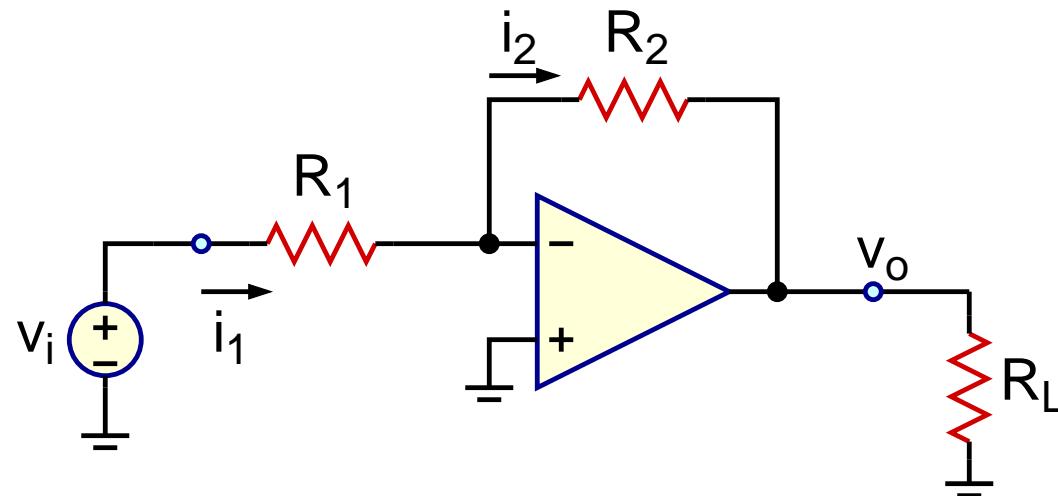


$$\frac{v_o}{v_i} = -\frac{R_2}{R_1}$$

# Inverting Integrator

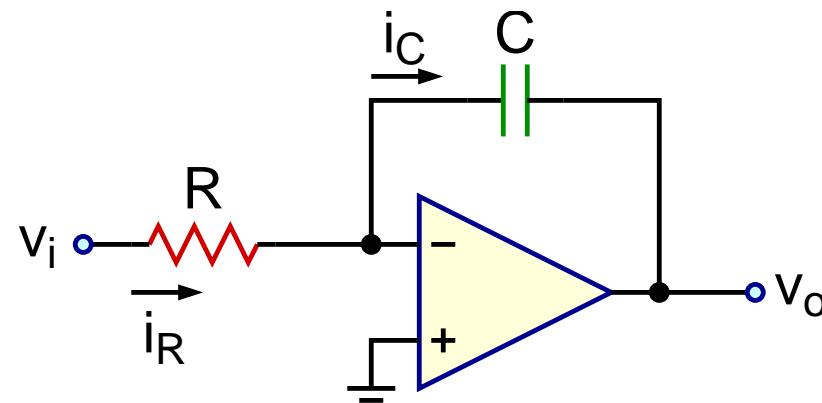


$$\frac{v_o}{v_i} = -\frac{1}{sRC}$$

## Inverting Lossy Integrator

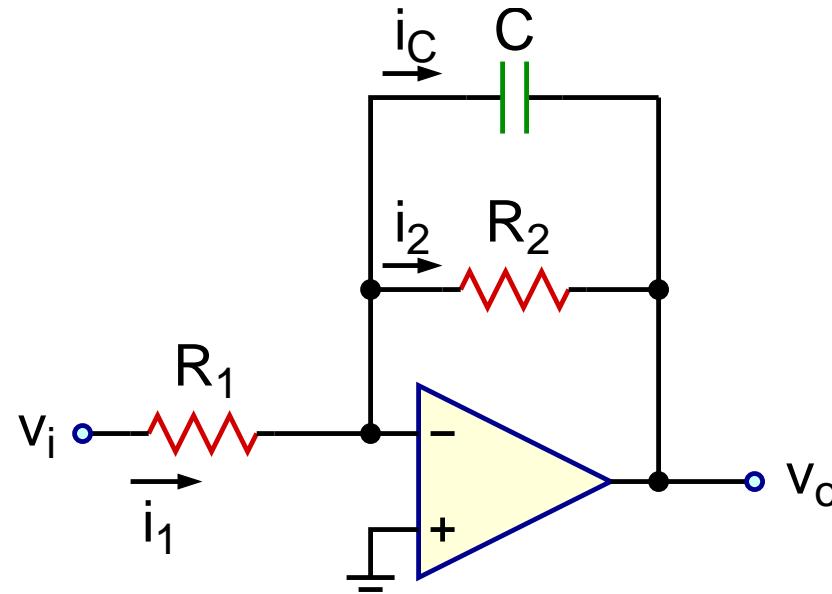


$$\frac{v_o}{v_i} = -\frac{\frac{R_2}{R_1}}{sR_2C + 1} = \frac{\kappa}{\frac{s}{\omega_o} + 1}, \quad \omega_o = \frac{1}{R_2C}, \quad \kappa = -\frac{R_2}{R_1}$$

# Inverting Differentiator

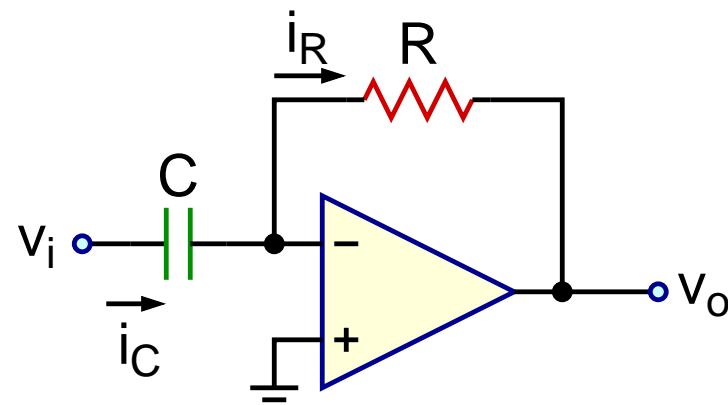


$$\frac{v_o}{v_i} = -sRC$$

## Inverting Summer

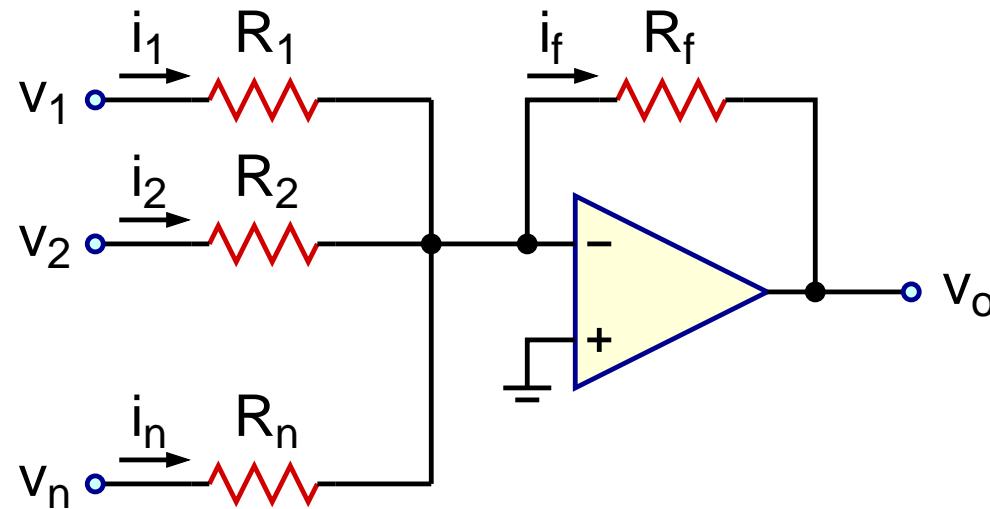

$$v_o = - \left( \frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \cdots + \frac{R_f}{R_n} v_n \right)$$


## Non-Inverting Configuration

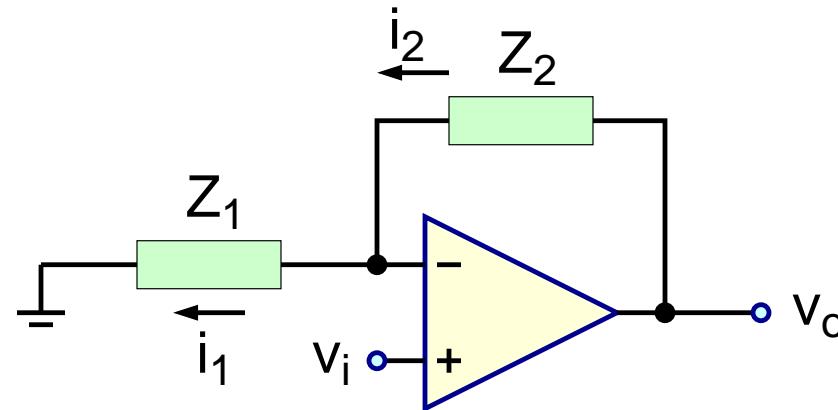

$$\frac{v_o}{v_i} = \frac{1 + \frac{Z_2}{Z_1}}{1 + \frac{Z_2}{Z_1} A}$$

$$A \rightarrow \infty \Rightarrow \frac{v_o}{v_i} = 1 + \frac{Z_2}{Z_1}$$


# Non-Inverting Amplifier

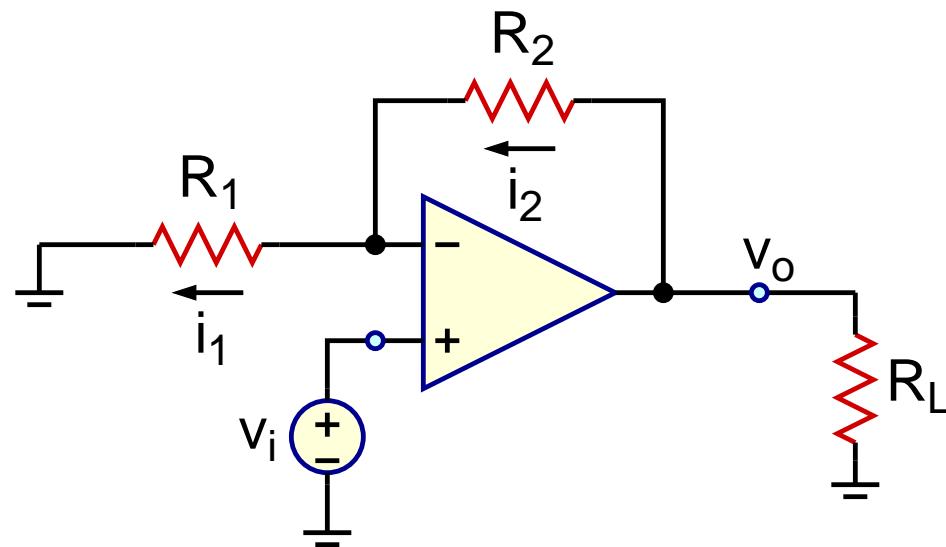

$$\frac{v_o}{v_i} = 1 + \frac{R_2}{R_1}$$


# Unity-Gain Buffer

---

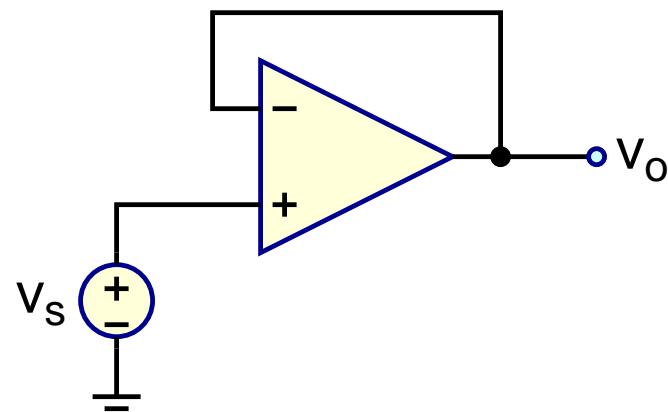


$$v_o = v_s$$

# Difference Amplifier

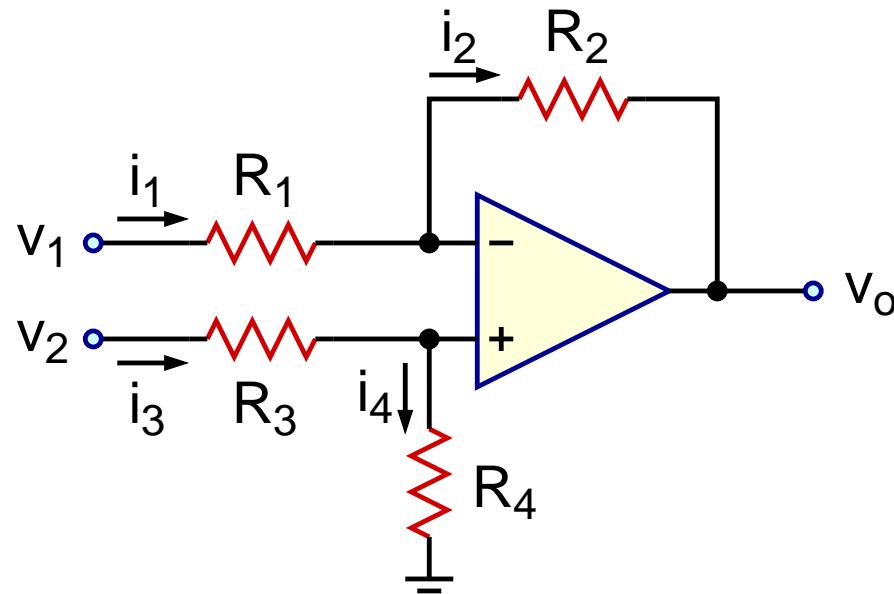


$$v_o = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{R_3}{R_4}} v_2 - \frac{R_2}{R_1} v_1$$

## Example

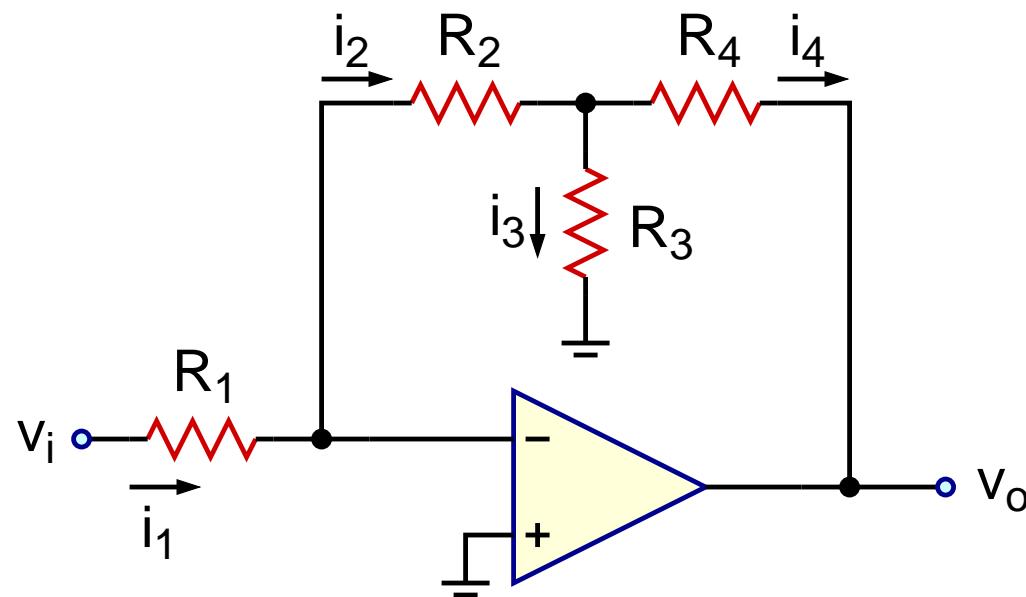

# Frequency Dependence

Open-loop gain

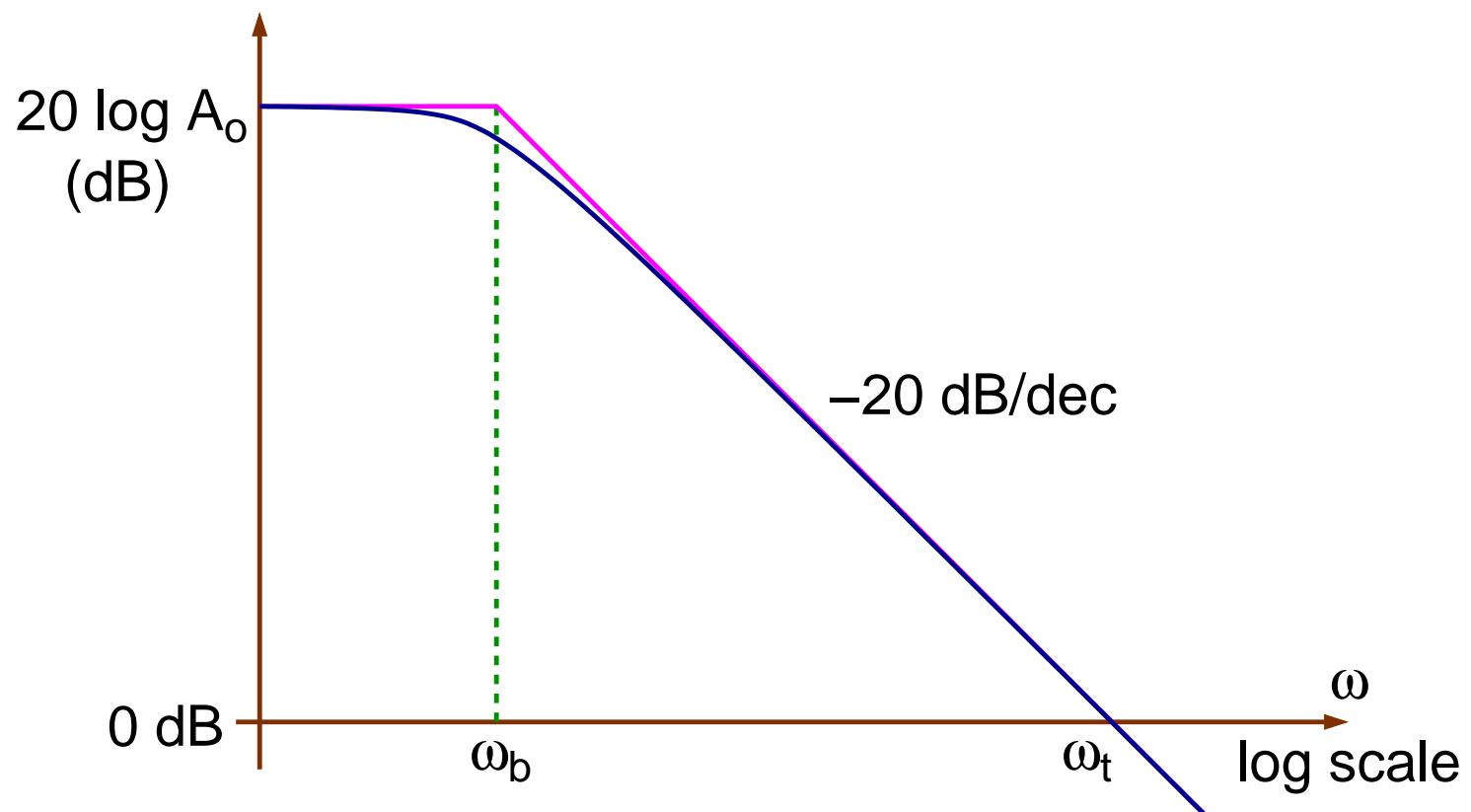

$$A(s) = \frac{A_o}{1 + \frac{s}{\omega_b}}$$

$$|A(j\omega)| = \frac{A_o}{\sqrt{1 + \frac{j\omega}{\omega_b}}}$$

# Gain-Bandwidth Product

---

$$\omega \gg \omega_b \Rightarrow |A(j\omega)| \approx \frac{A_o}{\left| \frac{j\omega}{\omega_b} \right|}$$

$$|A(j\omega)|_{\omega=\omega_t} = 1 \Rightarrow \omega_t = A_o \omega_b$$

$A_o \omega_b$  : Gain-Bandwidth (GBW) Product


$\omega_t$  : Unity-gain frequency

$\omega_b$  : Bandwidth

$A_o$  : DC gain

# Closed-Loop Gain

Inverting amplifier

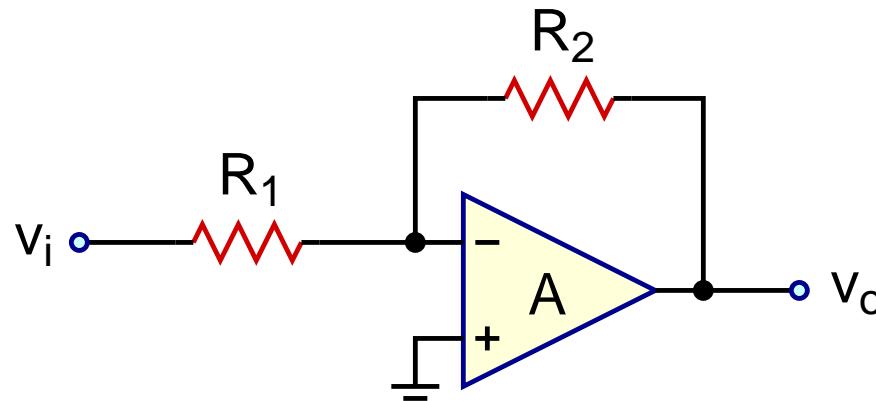

$$\frac{v_o}{v_i} = \frac{-\frac{R_2}{R_1}}{1 + \frac{R_2}{R_1}} A(s)$$
$$A(s) = \frac{A_o}{1 + \frac{s}{\omega_b}}$$

# Closed-Loop Gain

Inverting amplifier

Substitute  $\mathbf{A}(s)$  into  $v_o/v_i$ ,

$$\frac{v_o}{v_i} = \frac{-\frac{R_2}{R_1}}{1 + \frac{\left(1 + \frac{s}{\omega_b}\right)}{A_o} \left(1 + \frac{R_2}{R_1}\right)}$$

$$= \frac{-\frac{R_2}{R_1}}{1 + \underbrace{\frac{1}{A_o} \left(1 + \frac{R_2}{R_1}\right)}_{+ s \frac{1}{\omega_b A_o} \left(1 + \frac{R_2}{R_1}\right)}}$$

$\approx 0$  if  $A_o \gg \left(1 + \frac{R_2}{R_1}\right)$

# Closed-Loop Gain

Inverting amplifier


$$\frac{v_o}{v_i} \approx \frac{-\frac{R_2}{R_1}s}{1 + \frac{A_o \omega_b}{1 + \frac{R_2}{R_1}}} = \frac{-\frac{R_2}{R_1}s}{1 + \frac{\omega_o}{\omega_t}}$$

$$\omega_o = \frac{A_o \omega_b}{1 + \frac{R_2}{R_1}} = \frac{\omega_t}{1 + \frac{R_2}{R_1}}$$

$$\left(1 + \frac{R_2}{R_1}\right) \omega_o = \omega_t \quad (\text{GBW product or unity-gain freq})$$

# Closed-Loop Gain

Non-inverting amplifier

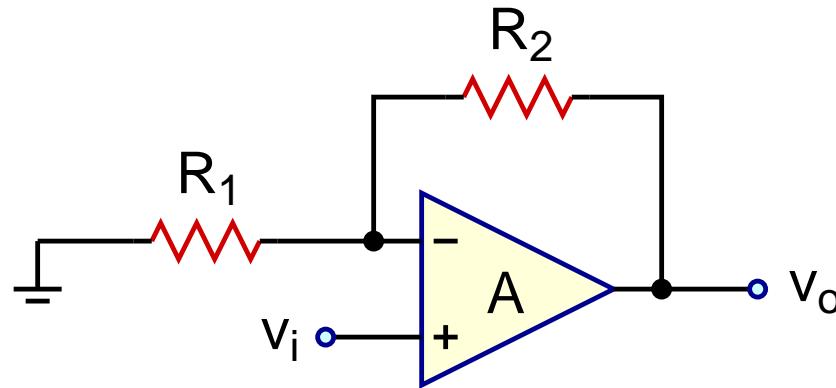

$$\frac{v_o}{v_i} = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{R_2}{R_1} A(s)}$$
$$A(s) = \frac{A_o}{1 + \frac{s}{\omega_b}}$$

## Closed-Loop Gain

Non-inverting amplifier

Substitute  $\mathbf{A}(s)$  into  $v_o/v_i$ ,

$$\frac{v_o}{v_i} = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{\left(1 + \frac{s}{\omega_b}\right)}{A_o} \left(1 + \frac{R_2}{R_1}\right)}$$

$$= \frac{1 + \frac{R_2}{R_1}}{1 + \underbrace{\frac{1}{A_o} \left(1 + \frac{R_2}{R_1}\right)}_{+ s \frac{1}{\omega_b A_o} \left(1 + \frac{R_2}{R_1}\right)}}$$

$\approx 0$  if  $A_o \gg \left(1 + \frac{R_2}{R_1}\right)$

## Closed-Loop Gain


Non-inverting amplifier

$$\frac{v_o}{v_i} \approx \frac{1 + \frac{R_2}{R_1}}{1 + \left( \frac{\frac{A_o \omega_b}{R_2}}{1 + \frac{R_2}{R_1}} \right)} = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{\omega_o}{\omega_0}} = \frac{G_o}{1 + \frac{s}{\omega_0}}$$

$$\omega_o = \frac{A_o \omega_b}{1 + \frac{R_2}{R_1}} = \frac{\omega_t}{1 + \frac{R_2}{R_1}}$$

$$\left(1 + \frac{R_2}{R_1}\right) \omega_o = \omega_t \quad (\text{GBW product or unity-gain freq})$$

## Open & Closed Loop Gain

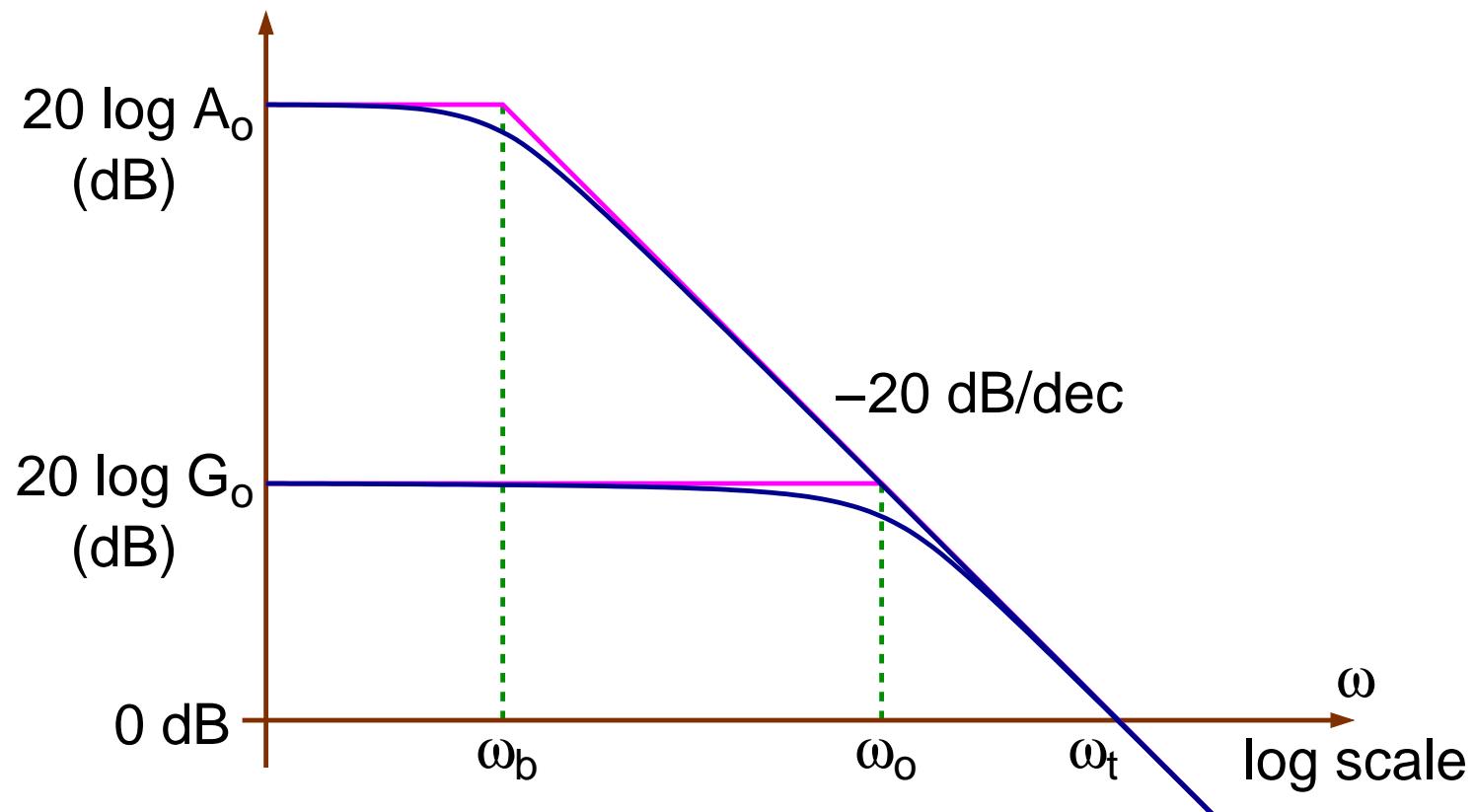

# Slew Rate

---

**Slew rate:** Maximum rate of change possible at the output of an opamp

- Find the time-domain output voltage,  $v_O(t)$
- Find the maximum value of rate of change at the output

$$\left. \frac{dv_O}{dt} \right|_{\max}$$

- To avoid distortion due to slew-rate limitation, the following should be satisfied

$$\left. \frac{dv_O}{dt} \right|_{\max} \leq SR$$

where SR is the slew rate usually specified in the opamp data sheet in units of  $V/\mu s$ .

In an amplifier circuit, the op-amp has the following slew rate and output voltage:

- SR = 100 V/ $\mu$ s
- v<sub>O</sub>(t) = A sin( $\omega$ t)

Then

- $\frac{dv_O}{dt} = A\omega \cos(\omega t) \Rightarrow \left. \frac{dv_O}{dt} \right|_{max} = A\omega \cos(\omega t)|_{max} = A\omega$
- To avoid distortion due to slew-rate limitation, the following should be satisfied

$$A\omega \leq 100 \text{ V}/\mu\text{s}$$

In an amplifier circuit,  $v_o/v_i$  is given as

$$\frac{v_o}{v_i}(s) = \frac{G_o}{1 + \frac{s}{\omega_o}}$$

where  $v_i(t) = A_i \sin(\omega_i t)$  and  $v_o$  is the output of the opamp.

$$v_o(t) = \frac{G_o}{\sqrt{1 + \left(\frac{\omega_i}{\omega_o}\right)^2}} A_i \sin(\omega_i t)$$

To avoid distortion,

$$\left. \frac{dv_o}{dt} \right|_{max} = \frac{G_o \omega_i A_i}{\sqrt{1 + \left(\frac{\omega_i}{\omega_o}\right)^2}} \leq SR$$