

ELEN 326


Current Mirrors

Dr. Aydın İlker Karşilayan

Texas A&M University
Department of Electrical Engineering

Simple Current Mirror

Bipolar

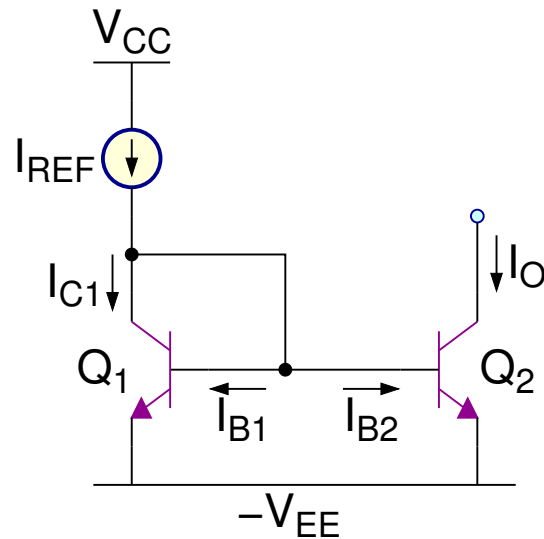

$$V_{BE1} = V_T \ln \frac{I_{C1}}{I_{S1}} = V_{BE2} = V_T \ln \frac{I_{C2}}{I_{S2}}$$

$$I_{S1} = I_{S2} \Rightarrow I_{C1} = I_{C2} = I_C$$
$$I_{B1} = I_{B2} = I_B$$

$$I_{REF} = I_C + 2I_B = I_C + \frac{2I_C}{\beta} = I_C \left(1 + \frac{2}{\beta} \right)$$

$$I_O = I_{C2} = I_C$$

$$I_O = \frac{\beta}{\beta + 2} I_{REF} = \frac{1}{1 + \frac{2}{\beta}} I_{REF}$$

$$R_o = r_{o2} = \frac{V_A}{I_{C2}}$$

$$V_{O(\min)} = V_{CE2(\text{sat})}$$

If the transistors are not identical:


$$I_O = \frac{I_{S2}}{I_{S1}} I_{REF} \frac{1}{1 + \frac{1 + (I_{S2}/I_{S1})}{\beta}}$$

Including the effect of Early voltage:

$$I_O = \frac{I_{S2}}{I_{S1}} I_{REF} \frac{1 + \frac{V_{CE2} - V_{CE1}}{V_A}}{1 + \frac{1 + (I_{S2}/I_{S1})}{\beta}}$$

Simple Current Mirror

MOS

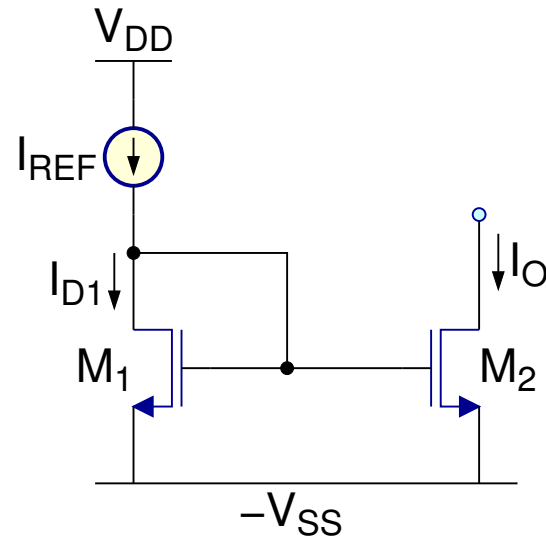

$$V_{GS1} = V_t + \sqrt{\frac{2I_{D1}}{k'(W/L)_1}} = V_{GS2} = V_t + \sqrt{\frac{2I_{D2}}{k'(W/L)_2}}$$

$$\frac{I_{D2}}{I_{D1}} = \frac{(W/L)_2}{(W/L)_1} \Rightarrow \frac{I_O}{I_{REF}} = \frac{(W/L)_2}{(W/L)_1}$$


$$R_o = r_{o2} = \frac{V_A}{I_{D2}} = \frac{1}{\lambda I_{D2}}$$

$$V_{O(\min)} = V_{ov} = \sqrt{\frac{2I_O}{k'(W/L)_2}}$$

Including the effect of Early voltage:

$$\frac{I_O}{I_{REF}} = \frac{(W/L)_2}{(W/L)_1} \left(1 + \frac{V_{DS2} - V_{DS1}}{V_A} \right)$$

Simple Current Mirror with Beta Helper

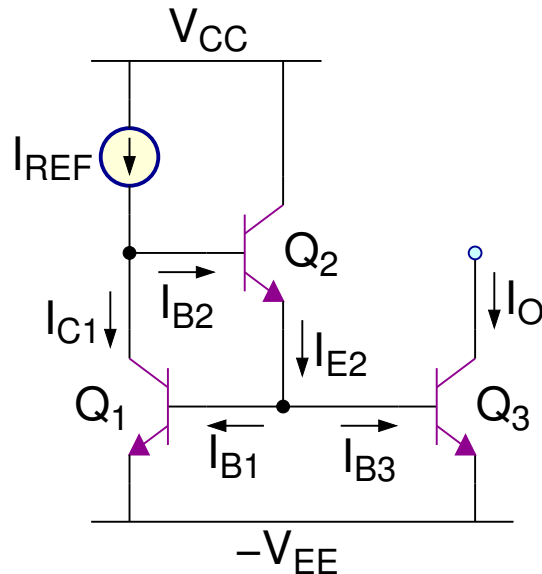

$$\begin{aligned}
 I_{REF} &= I_{C1} + I_{B2} \\
 &= I_{C1} + \frac{I_{E2}}{\beta + 1} \\
 &= I_{C1} + \frac{I_{B1} + I_{B3}}{\beta + 1}
 \end{aligned}$$

$$\begin{aligned}
 V_{BE1} = V_{BE3} &\Rightarrow I_{C1} = I_{C3} = I_C = I_O \\
 I_{B1} &= I_{B3} = I_B
 \end{aligned}$$


$$I_{REF} = I_C + \frac{2I_B}{\beta + 1} = I_C + \frac{2I_C}{\beta(\beta + 1)} = I_C \left(1 + \frac{2}{\beta(\beta + 1)} \right)$$

$$I_O = \frac{1}{1 + \frac{2}{\beta(\beta + 1)}} I_{REF}$$

$$R_O = r_{o3} = \frac{V_A}{I_{C3}}$$

$$V_{O(\min)} = V_{CE3(\text{sat})}$$

Simple Current Mirror with Degeneration

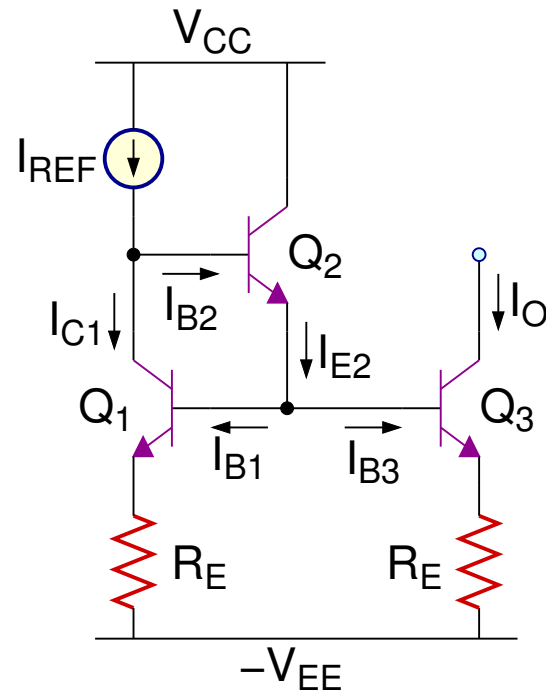


$$R_o \approx r_{o3} \left(1 + g_{m3} R_E \right) = r_{o3} \left(1 + \frac{I_{C3}}{V_T} R_E \right)$$

$$V_{O(\min)} = V_{CE3(\text{sat})} + I_{C3} R_E$$

Cascode Current Mirror

Bipolar

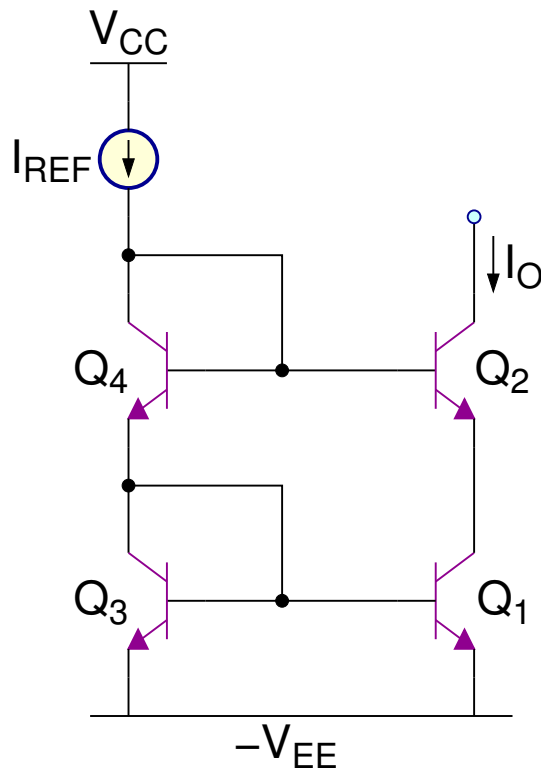


$$I_O = I_{REF} \left(1 - \frac{4\beta + 2}{\beta^2 + 4\beta + 2} \right)$$

$$R_o \approx \frac{\beta}{2} r_{o2}$$

$$V_{O(\min)} \approx V_{BE(\text{on})} + V_{CE2(\text{sat})}$$

Cascode Current Mirror

MOS

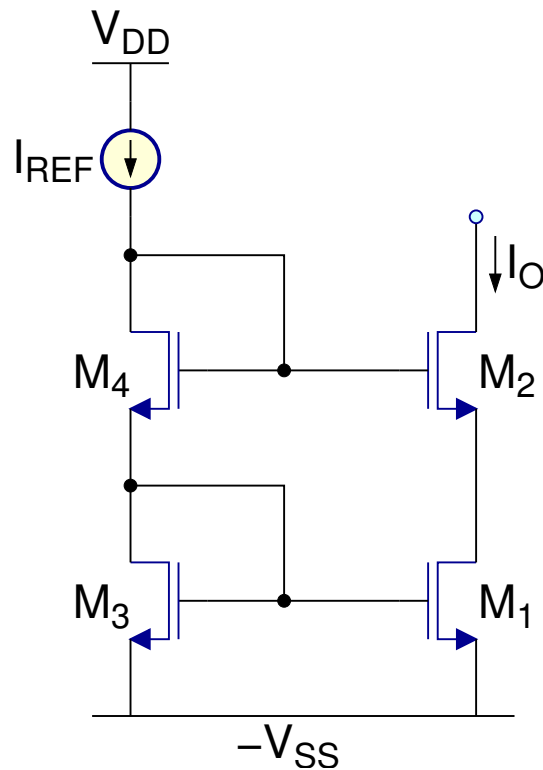

If M_1 – M_4 are identical:


$$I_O \approx I_{REF}$$

$$R_o = r_{o1} + r_{o2} + g_{m2}r_{o1}r_{o2}$$

$$V_{O(\min)} = V_t + V_{ov3} + V_{ov2}$$

Wilson Current Mirror

Bipolar

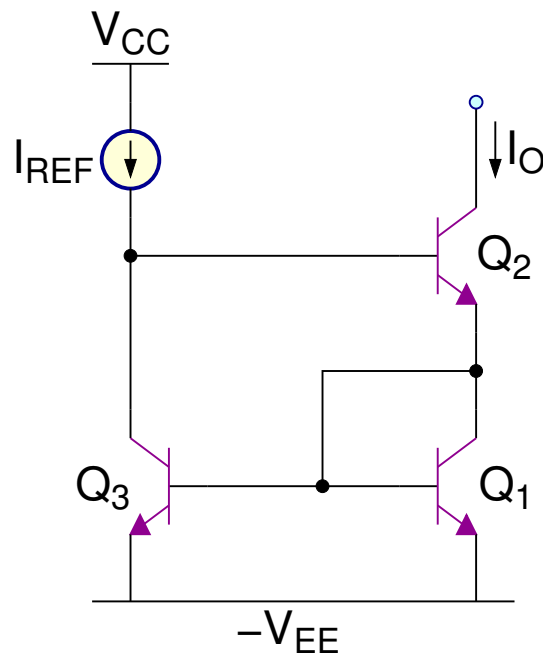


$$I_O = I_{REF} \left(1 - \frac{2}{\beta^2 + 2\beta + 2} \right)$$

$$R_o \approx \frac{\beta}{2} r_{o2}$$

$$V_{O(\min)} = V_{BE(\text{on})} + V_{CE2(\text{sat})}$$

Widlar Current Source

Bipolar

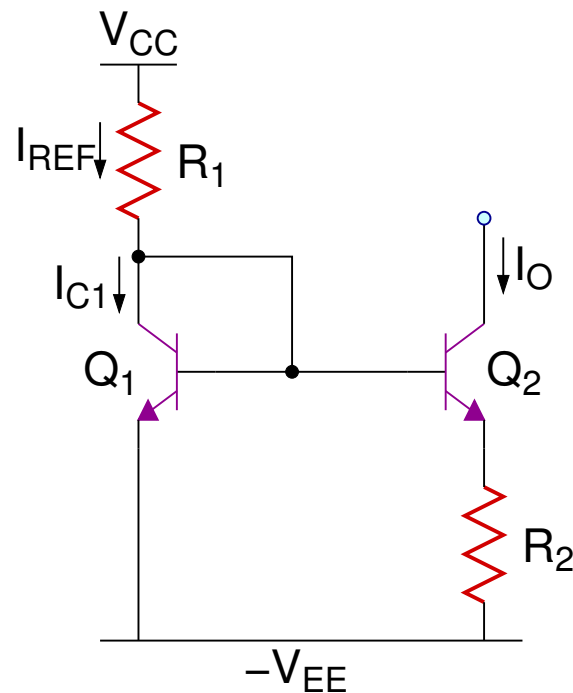

$$V_{BE1} - V_{BE2} - \frac{\beta + 1}{\beta} I_O R_2 = 0$$

$$V_T \ln \frac{I_{REF}}{I_{S1}} - V_T \ln \frac{I_O}{I_{S1}} = \frac{\beta + 1}{\beta} I_O R_2$$


If $I_{S1} = I_{S2}$ and $\beta \rightarrow \infty$:

$$V_T \ln \frac{I_{REF}}{I_O} = I_O R_2$$

$$V_{O(\min)} = V_{CE2(\text{sat})} + I_{C2} R_2$$

Widlar Current Source

MOS

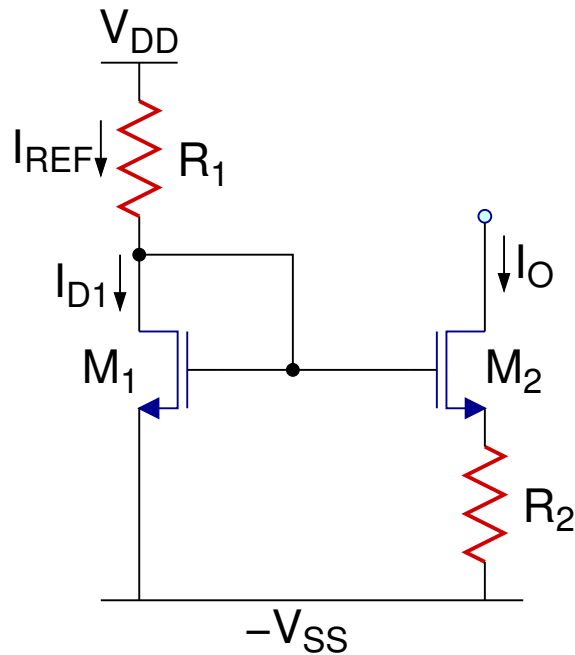

$$V_{GS1} - V_{GS2} - I_O R_2 = 0$$

$$I_O R_2 + V_{ov2} - V_{ov1} = 0$$

$$I_O = \left(\frac{-\sqrt{\frac{2}{k'(W/L)_2}} + \sqrt{\frac{2}{k'(W/L)_2} + 4R_2 V_{ov1}}}{2R_2} \right)^2$$