

Texas A&M University
Department of Electrical and Computer Engineering

ECEN 326 – Electronic Circuits

Spring 2022

Exam #1

Instructor: Sam Palermo

- Please write your name in the space provided below
- Please verify that there are 5 pages in your exam
- You may use one double-sided page of notes and equations for the exam
- Good Luck!

Problem	Score	Max Score
1		50
2		50
Total		100



Name: SAM PALERMO

UIN: _____


Problem 1 (50 points)

For the circuit shown below, assume that all transistors are operating in the active region and that $V_A = \infty$ for all transistors. Obtain expressions for the following:

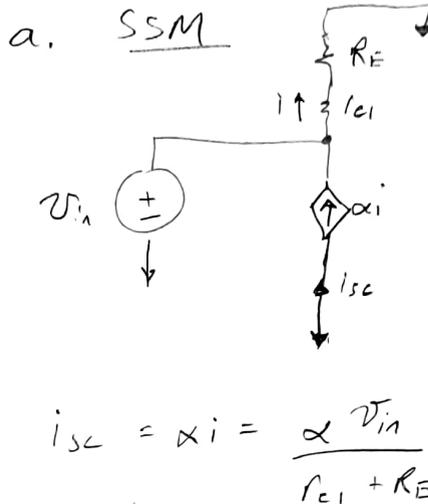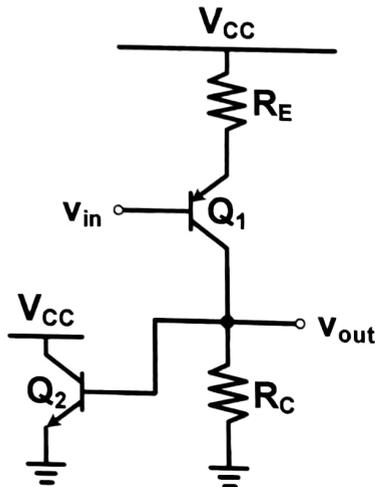- a) Short-circuit transconductance, G_m .
- b) Output resistance, R_{out}
- c) Small-signal gain, $A_v = v_{out}/v_{in}$
- d) Input resistance, R_{in}


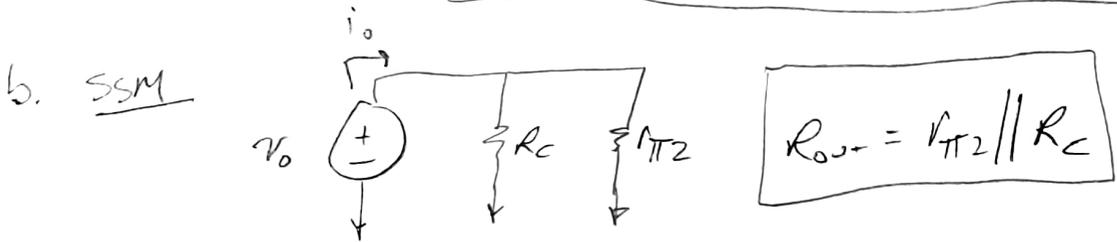
$$G_m = \frac{i_{sc}}{v_{in}} = \frac{\alpha}{r_{e1} + R_E} = \frac{g_{m1}}{1 + \frac{g_{m1} R_E}{\alpha}}$$



c.

$$A_v = -G_m R_{out} = \frac{-\alpha (R_C \parallel r_{\pi 2})}{r_{e1} + R_E} = \frac{-g_{m1} (R_C \parallel r_{\pi 2})}{1 + \frac{g_{m1} R_E}{\alpha}}$$

d.

$$R_{in} = r_{\pi 1} + (\beta + 1) R_E$$

Problem 2 (50 points)

For the circuit shown below, assume that all transistors are operating in the saturation region.


Use the following transistor parameters

$$K_{PN} = \mu_n C_{ox} = 200 \mu A/V^2, V_{TH,N} = 0.4V$$

$$K_{PP} = \mu_p C_{ox} = 100 \mu A/V^2, V_{TH,P} = -0.4V$$

$$\lambda_1 = \lambda_2 = \lambda_3 = \lambda_4 = \lambda_5 = \lambda_6 = 0$$

$$\lambda_7 = 0.1 V^{-1}$$

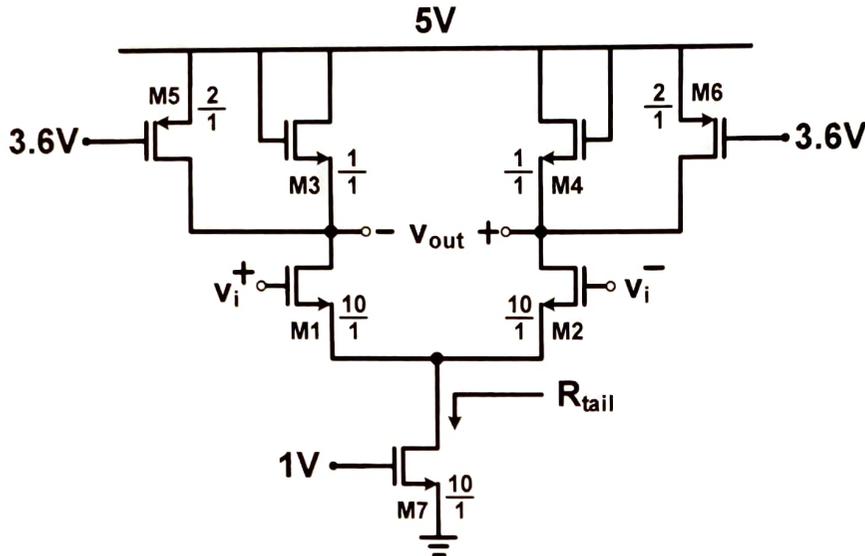

- a) Calculate (**give numbers**) the DC current flowing through the transistors requested below. Here assume that the input common-mode is sufficient to keep all the transistors operating in the saturation region. **Also, you can neglect λ effects for this part.**

$$I_{D1} = 180 \mu A$$

$$I_{D3} = 80 \mu A$$

$$I_{D5} = 100 \mu A$$

$$I_{D7} = 360 \mu A$$

$$I_{D7} = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{G1} - V_{TH,N})^2 = \frac{200 \mu}{2} (10) (1V - 0.4V)^2 = 360 \mu A$$

$$I_{D1} = \frac{I_{D7}}{2} = 180 \mu A$$

$$I_{D5} = \frac{\mu_p C_{ox}}{2} \frac{W}{L} (V_{S5} - |V_{TH,P}|)^2 = \frac{100 \mu}{2} (2) (1.4V - |-0.4V|)^2 = 100 \mu A$$


$$I_{D3} = I_{D1} - I_{D5} = 80 \mu A$$

Calculate (give numbers) the following. Include λ effects, if necessary.

b) Small-signal differential mode gain, $A_{DM} = v_{out}/(v_i^+ - v_i^-)$.

c) Tail current source impedance, R_{tail}

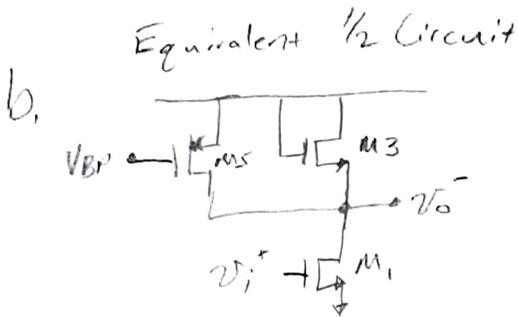d) Common-mode gain, $A_{CM} = V_{out,CM}/V_{in,CM}$



$\omega/\lambda_1 = \lambda_3 = \lambda_5 = 0$

$$G_m = g_{m1} \quad R_{out} = \frac{1}{g_{m3}}$$


$$A_v = \frac{v_o^-}{v_i^+} = - \frac{v_o^-}{v_i^+} = -(-G_m R_{out}) = \frac{g_{m1}}{g_{m3}}$$

$$g_{m1} = \sqrt{\mu_n \left(\frac{W}{L} \right) 2I_{D1}} = \sqrt{(200\mu)(10)(2)(180\mu)} = 849 \mu A/V$$

$$g_{m3} = \sqrt{\mu_n \left(\frac{W}{L} \right) 2I_{D3}} = \sqrt{200\mu(1)(2)(80\mu)} = 179 \mu A/V$$

$$A_v = \frac{g_{m1}}{g_{m3}} = \frac{849 \mu A/V}{179 \mu A/V} = 4.74 V/V$$
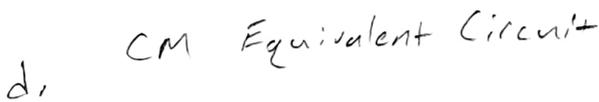
$$c. \quad R_{tail} = r_{o7} = \frac{1}{\lambda I_{D7}} = \frac{1}{(0.1V^{-1})(360\mu A)} = 27.8 k\Omega$$



$$G_m = \frac{2g_{m1}}{1 + 2g_{m1} R_{TAIL}} \quad R_{out} = \frac{1}{2g_{m3}}$$

$$A_{cm} = -G_m R_{out} = \frac{-g_{m1}}{1 + 2g_{m1} R_{TAIL}}$$

$$A_{cm} = \frac{-4.74 V/V}{1 + 2(849 \mu A/V)(27.8 k\Omega)} = -98.3 \times 10^{-3} V/V$$

Scratch Paper