

Texas A&M University
Department of Electrical and Computer Engineering

ECEN 326 – Electronic Circuits

Fall 2017

Exam #2

Instructor: Sam Palermo

- Please write your name in the space provided below
- Please verify that there are 4 pages in your exam
- You may use one double-sided page of notes and equations for the exam
- Good Luck!

Problem	Score	Max Score
1		50
2		50
Total		100


Name: SAM PALERMO

UIN: _____

Problem 1 (50 points)

For the circuit shown below, assume that all transistors are operating in the active region.

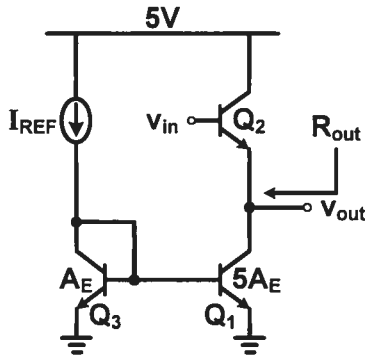a) Give an expression for the output resistance, R_{out} , as a function of I_{E2} . Assume that $V_A = \infty$.



$$R_{out} = r_{e2} = \frac{V_T}{I_{E2}}$$

b) Give the value of I_{REF} to achieve $R_{out} = 25\Omega$. Make sure to include the impact of mirroring error due to the relevant transistor base currents. Use the following transistor parameters.

$\beta = 100$, $V_{BE} = 0.7V$, $V_T = 25.9mV$, $V_A = \infty$

$$I_{E2} = \frac{V_T}{R_{out}}$$

$$I_{E2} = I_{C1} = \frac{n I_{REF}}{1 + \frac{n+1}{\beta}} = \frac{V_T}{R_{out}}$$

$$I_{REF} = \frac{V_T \left(1 + \frac{n+1}{\beta}\right)}{n R_{out}} = \frac{25.9mV \left(1 + \frac{5+1}{100}\right)}{5 (25\Omega)}$$


$$= 219.6\mu A$$

$$I_{REF} (R_{out} = 25\Omega) = 219.6\mu A$$

Problem 2 (50 points)

For the circuit shown below, assume that all transistors are operating in the saturation region and that $\lambda > 0$. Obtain expressions for the following

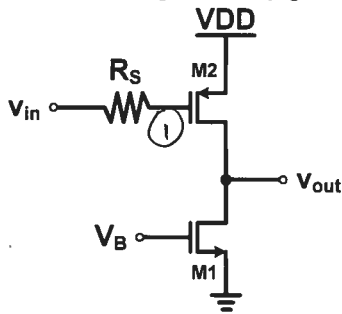- a) Low-frequency gain, $A_v = V_{out}/V_{in}$
- b) The circuit's poles, including the appropriate transistor capacitors. Where relevant, **use the Miller approximation to estimate the poles.**
- c) Using the answers from part (a) and (b), the circuit's transfer function $V_{out}(s)/V_{in}(s)$. Note, you can ignore any potential zeros in the transfer function.



a. Low frequency gain = $-g_{m2}(r_{o2} || r_{o1})$

b. 2 poles at node ① and V_{out}

Node 1: $|\omega_{p1}| = \frac{1}{R_s C_1}$ where $C_1 = C_{GD2} + C_{GD2}(1 + g_{m2}(r_{o2} || r_{o1}))$

Node V_{out} : $|\omega_{pout}| = \frac{1}{(r_{o2} || r_{o1}) C_{out}}$ where $C_{out} = C_{DB2} + C_{GD2}(1 + \frac{1}{g_{m2}(r_{o2} || r_{o1})}) + C_{DB1} + C_{GD1}$

c. $\frac{V_{out}(s)}{V_{in}(s)} = \frac{A_v}{(1 + \frac{s}{\omega_{p1}})(1 + \frac{s}{\omega_{pout}})} = \frac{-g_{m2}(r_{o2} || r_{o1})}{(1 + s R_s C_1)(1 + s (r_{o2} || r_{o1}) C_{out})}$

Scratch Paper