

$$\textcircled{4} \text{ a) } \therefore V_{RS} = 200 \text{ mV,}$$

$$\therefore I_{DS} R_S = 200 \text{ mV}$$

$$I_{DS} = \frac{0.2}{100}$$

$$I_{DS} = 2 \text{ mA.}$$

For M_1 to stay in saturation,

$$V_{DS} \geq V_{GS} - V_{TH}$$

$$\begin{aligned} \therefore V_{DS} &= V_D - V_S \\ &= [1.8 - (2 \times 10^{-3}) \times 500] - 0.2 \\ &= 0.6, \end{aligned}$$

$$\therefore V_{GS} - V_{TH} \leq 0.6,$$

Since $I_{DS} = \frac{1}{2} (M_n C_{ox}) \left(\frac{W}{L}\right) (V_{GS} - V_{TH})^2,$

$\left(\frac{W}{L}\right)$ is min. when $(V_{GS} - V_{TH})$ is max,

$$\therefore \text{min. } \left(\frac{W}{L}\right), \text{ is when } (V_{GS} - V_{TH}) = 0.6 \text{ V,}$$

$$2 \times 10^{-3} = \frac{1}{2} (200 \times 10^{-6}) \left(\frac{W}{L}\right) (0.6)^2$$

$$\therefore \text{min. } \left(\frac{W}{L}\right), = 56$$

b) With $(V_{GS} - V_{TH}) = 0.6$,

$$V_{GS} = 1,$$

$$\therefore V_G = 1 + V_S$$

$$V_G = 1.2V,$$

$$\text{ie. } 1.8x \frac{R_2}{R_1 + R_2} = 1.2V,$$

$$\frac{R_2}{R_1} = 2 \quad \text{--- (1)}$$

Input impedance = $R_2 // R_1$,

$$\text{ie. } R_2 // R_1 \geq 30k\Omega \quad \text{--- (2)}$$

Set $R_1 = 50k\Omega$ and $R_2 = 100k\Omega$

will satisfy both (1) & (2).

⑤

$$\begin{aligned}V_S &= V_{RS} \\ &= I_{D1} (200) = 0.1 \text{ V}\end{aligned}$$

$$I_{DS} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{TH})^2$$

$$0.5 \text{ mA} = \frac{1}{2} (200 \times 10^{-6}) \left(\frac{20}{0.18}\right) (V_{GS} - V_{TH})^2$$

$$\therefore V_{GS} = 0.612 \text{ V}$$

$$\begin{aligned}\therefore V_G &= 0.612 + 0.1 \\ &= 0.712.\end{aligned}$$

$$\therefore V_G = V_{DD} - I_{R1} \times R_1$$

$$R_1 = \underline{\underline{21.76 \text{ k}\Omega}}$$

$$\text{and } V_{GS} = I_{R2} \times R_2$$

$$\begin{aligned}\therefore R_2 &= \frac{0.712}{0.05 \times 10^{-3}} \\ &= \underline{\underline{14.24 \text{ k}\Omega}}\end{aligned}$$

⑧ With out defects,

$$V_{GS} = 1.8V,$$

$$\text{i.e. } V_{DS} = (1.8 - 0.1)V$$

$$= 1.7V$$

$$I_{DS} = \frac{(1.8 - 1.7)V}{2000 \Omega} = 0.05 \text{ mA.}$$

$$\therefore 0.05 \text{ mA} = \frac{1}{2} (200 \times 10^{-6}) \left(\frac{W}{L}\right) (1.8 - 0.4)^2$$

$$\therefore \left(\frac{W}{L}\right) = 0.255 //$$

b) With defects,

$$V_{GS} = V_{DS} + 50 \text{ mV}$$

$$\therefore V_{RP} = 50 \text{ mV}$$

$$I_{RP} = \frac{50 \text{ mV}}{R_p}$$

$$V_{GS} = 1.8V - \frac{0.05V}{R_p} \times 30 \text{ k}\Omega \quad \text{--- (1)}$$

$$\therefore V_{DD} - \left(I_{DS} - \frac{50 \text{ mV}}{R_p}\right) 2 \text{ k}\Omega = V_{DS}$$

$$V_{DD} - \left(I_{DS} - \frac{50 \text{ mV}}{R_p}\right) 2 \text{ k}\Omega = \underline{\underline{V_{GS} - 50 \text{ mV}}} \quad \text{--- (2)}$$

$$\begin{aligned}
 \therefore I_{DS} &= \frac{1}{2} \left(\frac{W}{L} \right) (M_n C_{ox}) (V_{GS} - V_{TH})^2 \\
 &= \frac{1}{2} (0.255) (200 \times 10^{-6}) (V_{GS} - 0.4)^2 \\
 &= 2.55 \times 10^{-5} (V_{GS} - 0.4)^2
 \end{aligned}$$

\therefore From ②,

$$\begin{aligned}
 1.8 - \left[2.55 \times 10^{-5} (V_{GS} - 0.4)^2 - \frac{0.2}{R_P} \right] 2000 \\
 = V_{GS} - 0.05.
 \end{aligned}$$

From ①,

$$\frac{0.05}{R_P} = \frac{1.8 - V_{GS}}{30000}$$

$$\therefore 1.8 - \left[0.051 (V_{GS} - 0.4)^2 - \frac{1.8 - V_{GS}}{15} \right] = V_{GS} - 0.3$$

$$1.85 - 0.051 V_{GS}^2 + 0.0408 V_{GS} - 0.00816 + \frac{1.8 - V_{GS}}{15} = V_{GS}$$

$$29.4276 - 15.388 V_{GS} - 0.765 V_{GS}^2 = 0$$


$$\therefore V_{GS} = 1.76 \text{ V} //$$

$$R_P = \frac{0.05 \times 30000}{1.8 - 1.76}$$

$$\approx 36.3 \text{ k}\Omega$$

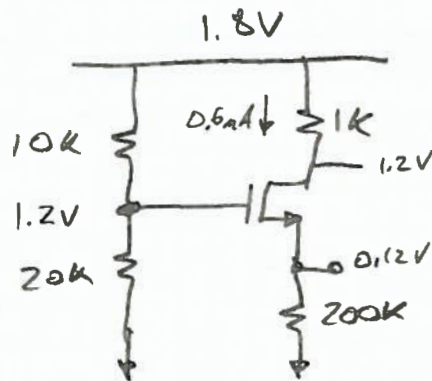7.9

w/o defect $V_{GS} = V_{DS} \Rightarrow V_G = V_D$



$$I_D = \frac{\mu C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2$$

$$\frac{W}{L} = \frac{2I_D}{\mu C_{ox} (V_{GS} - V_T)^2} = \frac{2(0.6mA)}{(200\mu)(1.2 - 0.12 - 0.4)^2}$$


$$\boxed{\frac{W}{L} = 13.0}$$

w/defect $V_{GS} = V_{DS} + V_{TH}$

$$\Rightarrow V_G = V_D + V_{TH} \Rightarrow V_D = V_G - V_{TH}$$

1.8V

$$= 1.2V - 0.4V = 0.8V$$

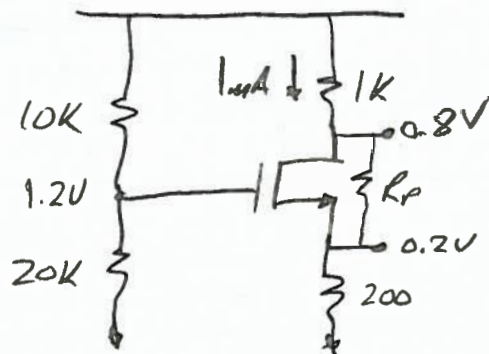


$$I_D = \frac{\mu C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2 = \frac{200\mu}{2} (13) (1.2 - 0.2 - 0.4)^2 = 468\mu A$$

$$I_{RP} = 1mA - 468\mu A = 532\mu A$$

$$\boxed{R_P = \frac{V_{RP}}{I_{RP}} = \frac{0.6V}{532\mu A} = 1.13K\Omega}$$

7.20

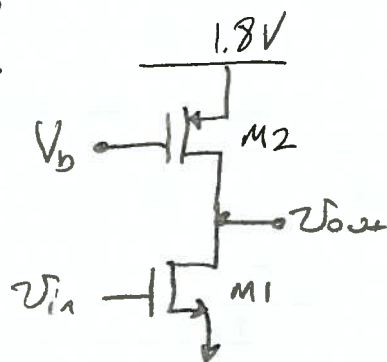

$$|A_V| = 10 \quad \mu/I_0 = 0.5 \text{ mA}$$

$$\lambda_1 = 0.1 \text{ V}^{-1}, \quad \lambda_2 = 0.15 \text{ V}^{-1}$$

a. $\frac{W}{L}_1 = ?$

$$|A_V| = g_{m1} (r_{o1} \parallel r_{o2}) = \frac{g_{m1}}{g_{o1} + g_{o2}}$$

$$= \frac{\sqrt{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 2I_0}}{\lambda_1 I_0 + \lambda_2 I_0}$$

$$\Rightarrow \left(\frac{W}{L}\right)_1 = \frac{A_V^2 I_0 (\lambda_1 + \lambda_2)}{2 \mu_n C_{ox}} = \frac{(10)^2 (0.5 \text{ mA}) (0.1 + 0.15)^2}{2 (200 \mu)}$$

$$\boxed{\left(\frac{W}{L}\right)_1 = 7.81}$$

b. $\left(\frac{W}{L}\right)_2 = \frac{20}{0.18} \Rightarrow V_b = ?$

$$I_0 = \frac{\mu_p C_{ox}}{2} \left(\frac{W}{L}\right)_2 (V_{SG} - |V_{THP}|)^2$$

$$= \frac{\mu_p C_{ox}}{2} \left(\frac{W}{L}\right)_2 (V_{DD} - V_b - |V_{THP}|)^2$$

$$V_b = V_{DD} - |V_{THP}| - \sqrt{\frac{2I_0}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2}}$$

$$\boxed{V_b = 1.1 \text{ V}}$$

$$= 1.8 \text{ V} - |-0.4 \text{ V}| - \sqrt{\frac{2 (0.5 \text{ mA})}{100 \mu \left(\frac{20}{0.18}\right)}} = 1.1 \text{ V}$$

(24). To get higher voltage gain,

(a) is preferred.

For the same dimensions of transistors
and same bias current,

(a) has a high " g_m " than (b).

$$\therefore g_{m1} > g_{m2}$$


$$(\text{since } \mu_n C_{ox} > \mu_p C_{ox})$$

while $(R_{o1} \parallel R_{o2})$ is the same
for both cases.

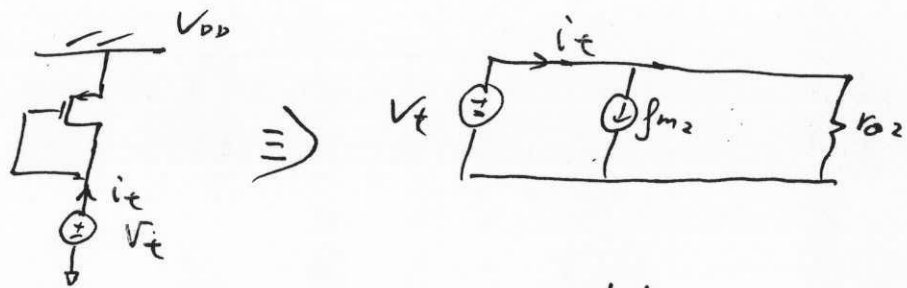(28) a) $A_v = -g_{m1} r_{o1} \parallel Z_2$,

where Z_2 is the impedance presented by M_2 .

To find Z_2 , apply a test voltage (V_t) at the drain of M_2 :



From the small-signal model,

$$i_t = g_{m2} V_t + \frac{V_t}{r_{o2}}$$

$$Z_2 = \frac{V_t}{i_t} = r_{o2} \parallel \frac{1}{g_{m2}}$$

$$\therefore A_v = -g_{m1} (r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2}})$$

b) $A_v = -g_{m1} (r_{o1} \parallel Z_2 \parallel Z_3)$

where Z_2 and Z_3 are impedances presented by M_2 and M_3 respectively.

From (a) $Z_3 = r_{o3} \parallel \frac{1}{g_{m3}}$

By inspection, $Z_2 = r_{o2}$

$$\therefore A_v = -g_{m1} (r_{o1} \parallel r_{o2} \parallel r_{o3} \parallel \frac{1}{g_{m3}})$$

$$c) \quad A_v = -\beta_{m1} r_{o1} \parallel Z_2 \parallel Z_3.$$

Similar to (b),

$$Z_2 = r_{o2},$$

$$\text{and } Z_3 = r_{o3} \parallel \frac{1}{\beta_{m3}}$$

(the small signal model of M_3 in this case is equivalent to that of M_2 in (a))

$$\therefore A_v = -\beta_{m1} (r_{o1} \parallel r_{o2} \parallel r_{o3} \parallel \frac{1}{\beta_{m3}})$$

d) M_2 is in CS arrangement. (similar to (c))

$$A_v = \beta_{m2} r_{o2} \parallel Z_1 \parallel Z_3.$$

$$Z_3 = \frac{1}{\beta_{m3}} \parallel r_{o3}$$

$$Z_1 = r_{o1}$$

$$\therefore A_v = \beta_{m2} (r_{o2} \parallel r_{o1} \parallel \frac{1}{\beta_{m3}} \parallel r_{o3})$$

$$e) \quad A_v = \beta_{m2} (r_{o2} \parallel Z_1 \parallel Z_3)$$

$$Z_1 = r_{o1}$$

$$Z_3 = \frac{1}{\beta_{m3}} \parallel r_{o3}$$


(recall: impedance looking into source = $\frac{1}{\beta_m}$)

$$\therefore A_v = \beta_{m2} (r_{o2} \parallel r_{o1} \parallel \frac{1}{\beta_{m3}} \parallel r_{o3})$$

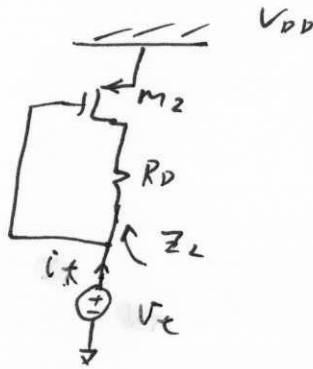
(28)

$$f) A_v = -\beta_{m_1} (r_{o1} \parallel Z_L)$$

where Z_L is the impedance depicted as follows:



The equivalent small-signal model is:

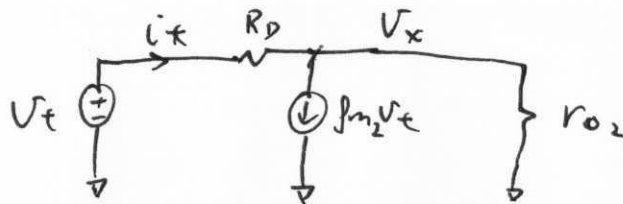

$$i_t = \beta_{m_2} V_t + \frac{V_x}{r_{o2}}$$

$$V_x = V_t - R_D i_t$$


$$\therefore i_t = \beta_{m_2} V_t + \frac{V_t - R_D i_t}{r_{o2}}$$

$$i_t \left(1 + \frac{R_D}{r_{o2}} \right) = V_t \left(\beta_{m_2} + \frac{1}{r_{o2}} \right)$$

$$\frac{V_t}{i_t} = \frac{r_{o2} + R_D}{\beta_{m_2} r_{o2} + 1}$$

$$\therefore A_v = -\beta_{m_1} \left(r_{o1} \parallel \frac{r_{o2} + R_D}{1 + \beta_{m_2} r_{o2}} \right)$$



7.32 /

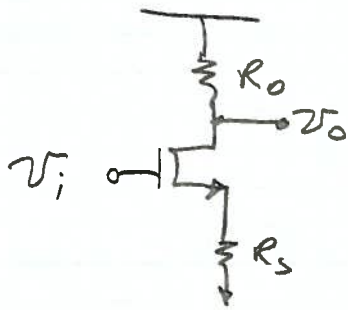

We can express the gain

$$A_v = \frac{v_o}{v_i} = G_m R_{out}$$

For G_m

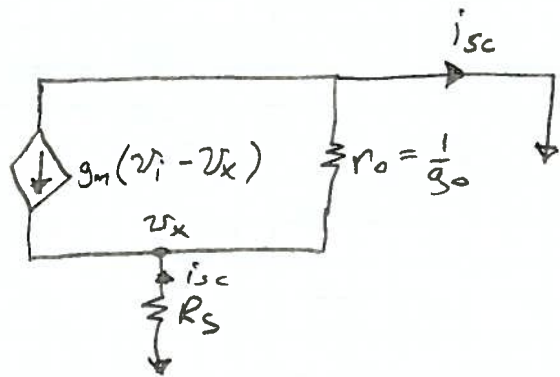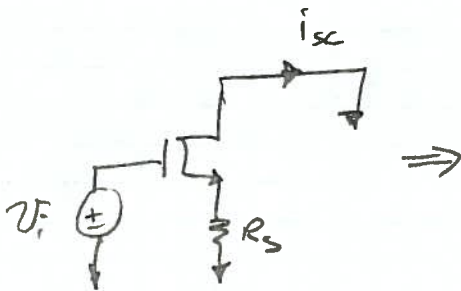

$$v_x = -i_{sc} R_s$$


KCL @ output

$$i_{sc} + g_m(v_i + i_{sc} R_s) + i_{sc} R_s g_o = 0$$

$$i_{sc} [1 + (g_m + g_o) R_s] = -g_m v_i$$

$$G_m = \frac{i_{sc}}{v_i} = -\frac{g_m}{1 + (g_m + g_o) R_s}$$

For R_{out}

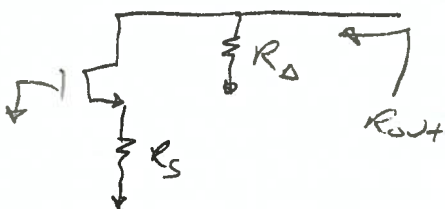

$$R_{out} = R_o \parallel [r_o + R_s + g_m r_o R_s]$$

$$A_v = G_m R_{out}$$

$$= - \left[\frac{g_m}{1 + (g_m + g_o) R_s} \right] \left[R_o \parallel [r_o + R_s + g_m r_o R_s] \right]$$

$$\frac{w}{g_m r_o} = \frac{g_m}{g_o} \gg 1$$

$$\approx - \left[\frac{g_m}{1 + g_m R_s} \right] \left[R_o \parallel [r_o + g_m r_o R_s] \right]$$

OK to just have this term, as this often dominates

37

$$a) |Voltage\ gain| = \beta_m R_D$$

$$= 5$$

$$\therefore \beta_m = \frac{5}{500}$$

$$= 10\text{ mS}$$

$$= \sqrt{2(200 \times 10^{-6}) \left(\frac{W}{L}\right) \times 10^{-3}}$$

$$\therefore \frac{W}{L} = 250 //$$

$$b) V_D = 1.8 - 500 \times 10^{-3}$$

$$= 1.3\text{ V}$$

$$\text{To obtain } V_{DS} \geq V_{GS} - V_{TH} + 0.2,$$

$$V_D \geq V_G - 0.2$$

$$\therefore V_G \leq 1.5$$

$$\text{Also, } I_{R_1+R_2} = 0.1 \times 10^{-3}\text{ A}$$

$$\therefore R_1 + R_2 = \frac{1.8}{0.1 \times 10^{-3}} \\ = 18\text{ k}\Omega$$

$$\text{choose } R_2 = 15\text{ k}\Omega \quad \& \quad R_1 = 3\text{ k}\Omega$$

c) With twice of (W/L) , M_1 will go further away from triode. As (W/L) doubles, & I_{bias} is fixed by the current source, V_{GS} is forced to decrease (so M_1 will have same I_{DS}). Thus, $(V_{GS} - V_{TH})$ decreases, and V_{DS} can be allowed to drop more before M_1 goes into triode.

Gain will be increased by $\sqrt{2}$, because $g_{ain} \propto g_m$, and $g_m \propto \sqrt{W/L}$.

44 a) Voltage gain (A_v) =
$$\left[\frac{\frac{1}{\beta_{m1}}}{R_s + \frac{1}{\beta_{m1}}} \right] \frac{\beta_{m1}}{\beta_{m2}}$$

$$= \frac{\beta_{m1} / \beta_{m2}}{1 + \beta_{m1} R_s}$$

b) Voltage gain (A_v) = $\beta_{m1} Z_L$
 (similar to prob. 32(b))

$$= \frac{\beta_{m1}}{\beta_{m2}}$$

c) Voltage gain =
$$\left[\frac{\frac{1}{\beta_{m1}} \parallel R_1}{R_s + \frac{1}{\beta_{m1}} \parallel R_1} \right] \frac{\beta_{m1}}{\beta_{m2}}$$

d) Voltage gain = $\beta_{m1} \left[R_D + r_{o3} \parallel \frac{1}{\beta_{m2}} \right]$


$\therefore r_{o3} = \infty$

gain = $\beta_{m1} \left[R_D + \frac{1}{\beta_{m2}} \right]$

e) Voltage gain = $\beta_{m1} \left[R_D + \frac{1}{\beta_{m2}} \right]$

(48)

The small-signal model is:

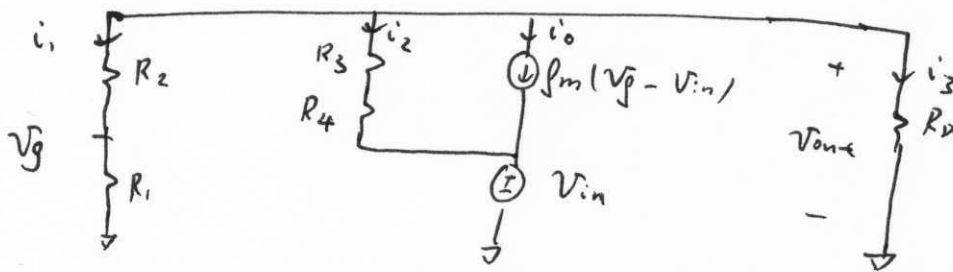

$$\therefore -i_o = i_1 + i_2 + i_3$$

$$-g_m(V_g - V_{in}) = \frac{V_{out}}{R_2 + R_1} + \frac{V_{out} - V_{in}}{R_3 + R_4} + \frac{V_{out}}{R_D}$$

$$g_m(V_{in} - \frac{R_1}{R_1 + R_2} V_{out}) = V_{out} \left(\frac{1}{R_1 + R_2} + \frac{1}{R_3 + R_4} + \frac{1}{R_D} \right) - \frac{V_{in}}{R_3 + R_4}$$


$$V_{in} \left(g_m + \frac{1}{R_3 + R_4} \right) = V_{out} \left(\frac{g_m R_1 + 1}{R_1 + R_2} + \frac{1}{R_3 + R_4} + \frac{1}{R_D} \right)$$

$$\frac{V_{out}}{V_{in}} = \frac{\left(g_m + \frac{1}{R_3 + R_4} \right)}{\frac{1}{R_D} + \frac{1}{R_3 + R_4} + \frac{g_m R_1 + 1}{R_1 + R_2}}$$

55

$$a) A_v = \frac{r_{o1} \parallel (R_s + r_{o2})}{\frac{1}{\beta_{m1}} + r_{o1} \parallel (R_s + r_{o2})}$$
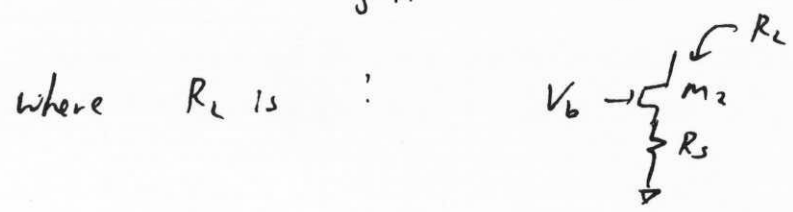
$$b) A_v = \frac{r_{o1} \parallel R_L}{\frac{1}{\beta_{m1}} + (r_{o1} \parallel R_L)}$$




$$R_L = (1 + \beta_{m2} r_{o2}) R_s + r_{o2} \quad \text{Eq. (7.110)}$$

$$\therefore A_v = \frac{r_{o1} \parallel [(1 + \beta_{m2} r_{o2}) R_s + r_{o2}]}{\frac{1}{\beta_{m1}} + r_{o1} \parallel [(1 + \beta_{m2} r_{o2}) R_s + r_{o2}]}$$

$$c) A_v = \frac{r_{o1} \parallel \frac{1}{\beta_{m2}}}{\frac{1}{\beta_{m1}} + (r_{o1} \parallel \frac{1}{\beta_{m2}})}$$


$$d) A_v = \frac{r_{o1} \parallel R_L}{\frac{1}{\beta_{m1}} + (r_{o1} \parallel R_L)}$$

where R_L is :

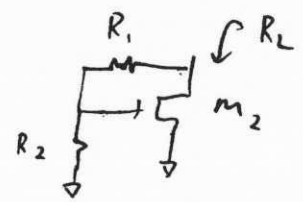

(c) Finding R_L with small-signal model:

(cont'd)

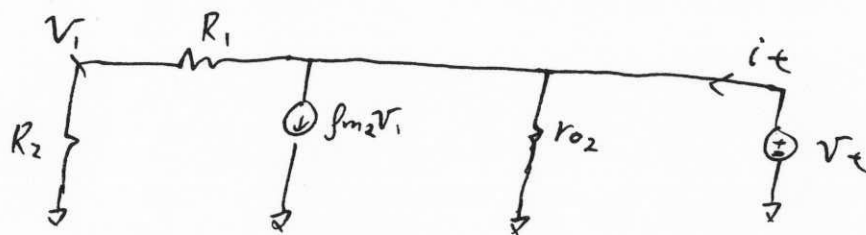

$$R_L = \frac{v_t}{i_t}$$

$$\text{where } i_t = \frac{v_t}{r_{o2}} + \beta_{m2} v_i + \frac{v_t}{R_1 + R_2}$$

$$= \frac{v_t}{r_{o2}} + \frac{\beta_{m2} R_2 v_t}{R_1 + R_2} + \frac{v_t}{R_1 + R_2}$$

$$\therefore R_L = \frac{r_{o2} (R_1 + R_2)}{R_2 + R_1 + r_{o2} + \beta_{m2} r_{o2} R_2}$$

$$\therefore A_v = \frac{r_{o1} \parallel \frac{r_{o2} (R_1 + R_2)}{R_2 + R_1 + r_{o2} + \beta_{m2} r_{o2} R_2}}{\frac{1}{\beta_{m1}} + r_{o1} \parallel \frac{r_{o2} (R_2 + R_1)}{R_2 + R_1 + r_{o2} + \beta_{m2} r_{o2} R_2}}$$

$$e) \quad A_v = \frac{r_{o2} \parallel \left(\frac{1}{\beta_{m1}} \parallel r_{o3} \right)}{\frac{1}{\beta_{m2}} + r_{o2} \left(\frac{1}{\beta_{m1}} \parallel r_{o3} \right)}$$

$$f) \quad A_v = \frac{r_{o1} \parallel \left[(1 + \beta_{m2} r_{o2}) r_{o3} + r_{o2} \right]}{\frac{1}{\beta_{m1}} + \left\{ r_{o1} \parallel \left[(1 + \beta_{m2} r_{o2}) r_{o3} + r_{o2} \right] \right\}}$$