
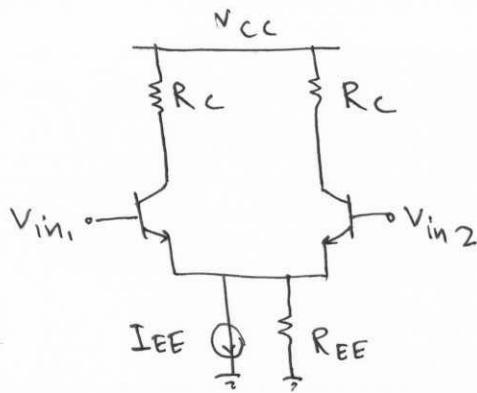


(27)

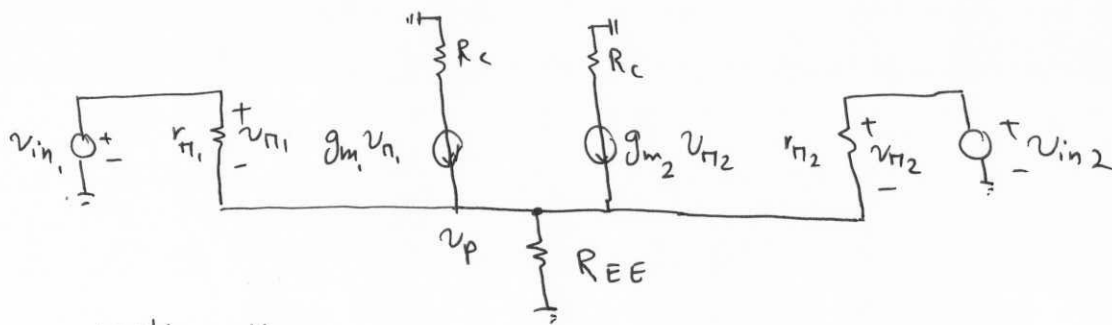

The small signal model is:




writing the node equation at P we have:

$$\frac{v_p}{R_{EE}} + \frac{v_p - v_{in1}}{r_{\pi 1}} + g_{m1}(v_p - v_{in1}) + \frac{v_p - v_{in2}}{r_{\pi 2}} + g_{m2}(v_p - v_{in2}) = 0$$


Since $v_{in1} = -v_{in2}$ and $\begin{cases} r_{\pi 1} = r_{\pi 2} \\ g_{m1} = g_{m2} \end{cases}$, the above equation simplifies to:
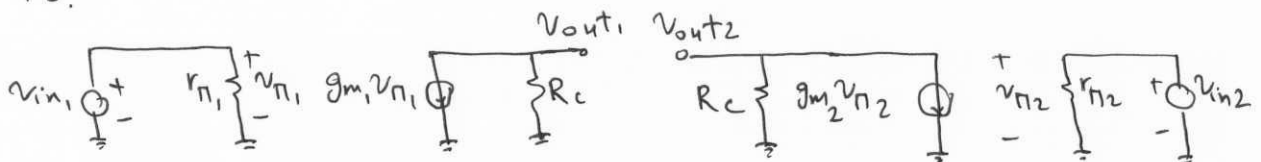
$$\frac{v_p}{R_{EE}} + \frac{2v_p}{r_{\pi 1}} + 2g_{m1}v_p = 0 \Rightarrow v_p = 0 \Rightarrow \text{the small signal model is:}$$



$$A_v = \frac{v_{out1} - v_{out2}}{v_{in1} - v_{in2}} = \frac{-g_{m1}v_{in1}R_C + g_{m2}v_{in2}R_C}{v_{in1} - v_{in2}} = -g_{m1}R_C$$


(29)

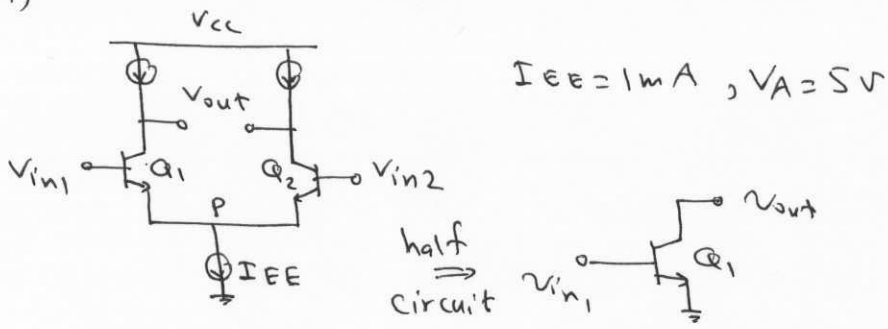


$$A_v = -g_{m1} \cdot r_{o1} = -\frac{I_{EE}}{2V_T} \frac{V_A}{\frac{I_{EE}}{2}} = -\frac{V_A}{V_T} = \frac{-5}{0.026}$$

$$\rightarrow A_v = -192.31$$


32

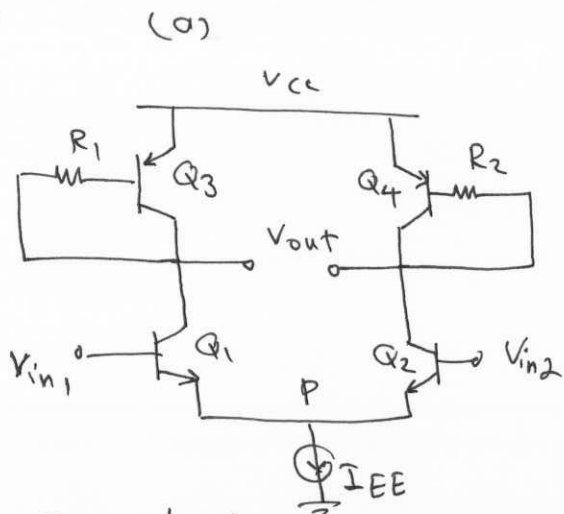

From half circuit concept we have: $A_v = -g_{m1}(r_{o1} || R_{op})$

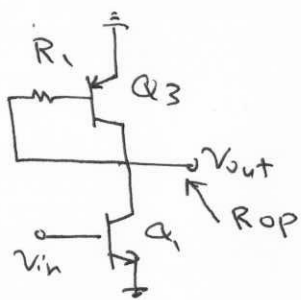

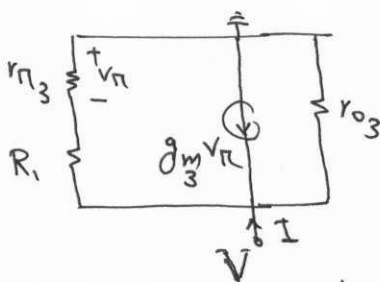To calculate R_{op} , from small signal model we have:




$$I = \frac{V}{r_{o3}} - g_{m3}V_{\pi} + \frac{V}{R_1 + r_{\pi3}} = V \left[\frac{1}{r_{o3}} + \frac{1}{R_1 + r_{\pi3}} \right] + g_{m3} \frac{r_{\pi3}}{R_1 + r_{\pi3}} V$$

$$\rightarrow R_{op} = \frac{V}{I} = r_{o3} || (R_1 + r_{\pi3}) || \left(\left(1 + \frac{R_1}{r_{\pi3}} \right) \frac{1}{g_{m3}} \right)$$


$$\rightarrow A_v = -g_{m1} \left[r_{o1} || r_{o3} || (R_1 + r_{\pi3}) || \left(\left(1 + \frac{R_1}{r_{\pi3}} \right) \frac{1}{g_{m3}} \right) \right]$$

32

b)

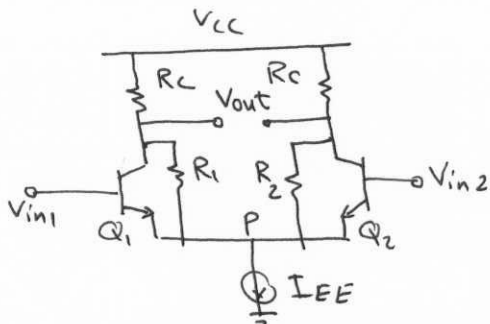


From half circuit concept:

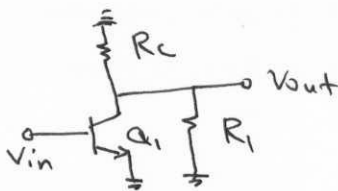


$$\rightarrow A_v = -g_{m1} (R_1 \parallel R_C \parallel r_{o1})$$


(c)

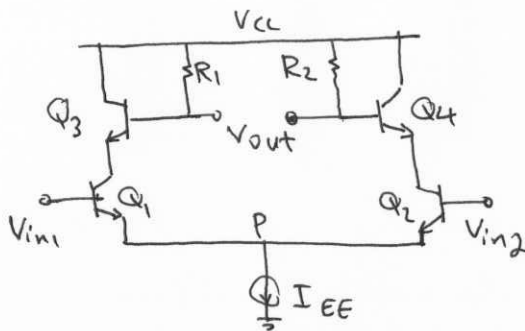

half circuit

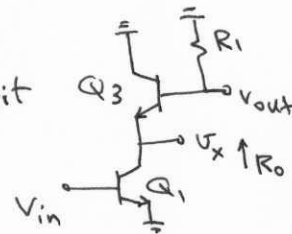

To calculate R_0 we have:

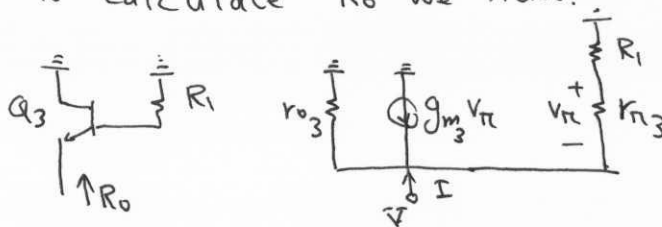

$$R_0 = \frac{V}{I}$$


$$I = \frac{V}{r_{o3}} + \frac{V}{R_1 + r_{\pi 3}} + g_{m3} \frac{r_{\pi 3} V}{r_{\pi 3} + R_1}$$

$$\Rightarrow R_0 = r_{o3} \parallel (R_1 + r_{\pi 3}) \parallel \left(1 + \frac{R_1}{r_{\pi 3}}\right) \frac{1}{g_{m3}}$$


$$A_v = \frac{v_{out}}{v_{in}} = \frac{v_x}{v_{in}} \frac{v_{out}}{v_x} = -g_{m1} (r_{o1} \parallel R_0) \frac{R_1}{R_1 + r_{\pi 3}}$$

32

(d)

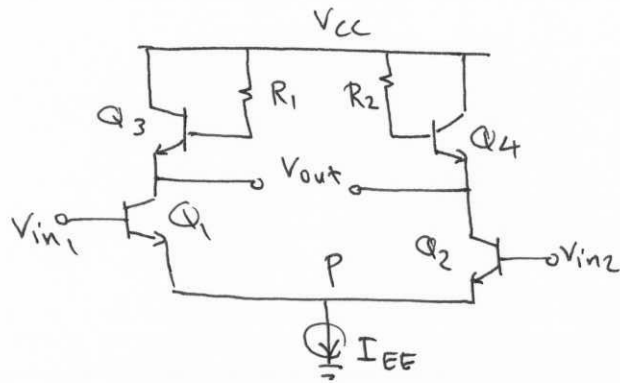

From half circuit concept :

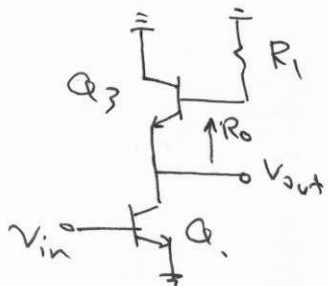


we already proved in part (c) that


$$R_o = r_{o3} \parallel (R_1 + r_{\pi 3}) \parallel \left(1 + \frac{R_1}{r_{\pi 3}}\right) \frac{1}{g_{m3}}$$

$$\rightarrow A_v = \frac{v_{out}}{v_{in}} = -g_{m1} (r_{o1} \parallel R_o)$$

33

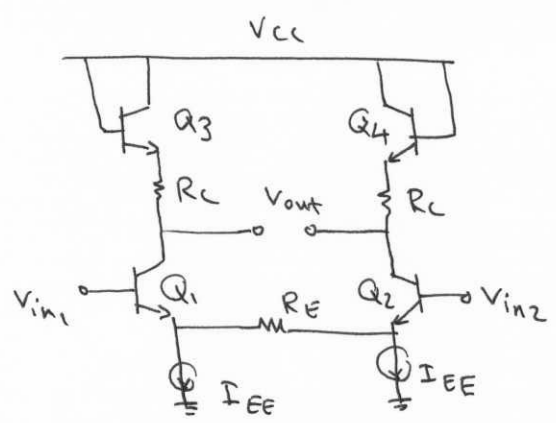

The half circuit is shown as:

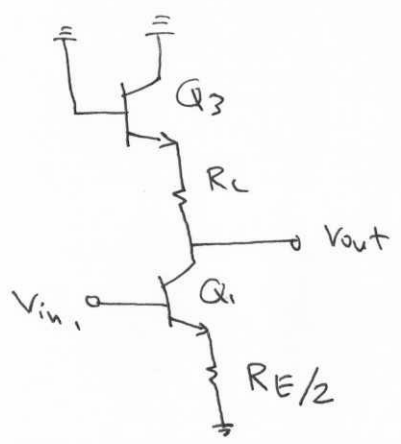


$$a) \quad A_v = \frac{v_{out}}{v_{in1}} = - \frac{R_C + 1/g_{m3}}{R_E/2 + 1/g_{m1}}$$

b) if $\frac{R_C}{R_E/2} = A$, then if $\frac{1/g_{m3}}{1/g_{m1}} = A$


we conclude $A_v = -A$ - so the circuit is very linear.

(34)

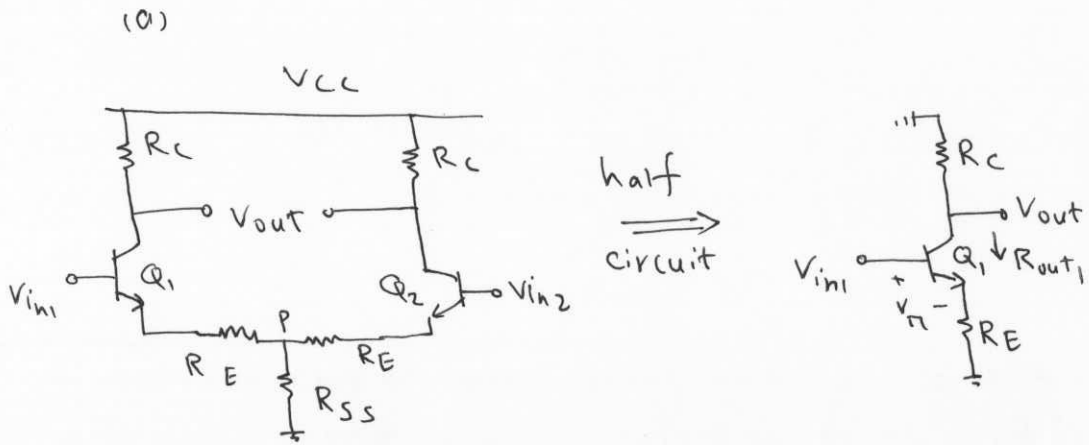

$$R_{out} = R_C \parallel R_{out1} = R_C \parallel (g_{m1} r_{o1} (R_E \parallel r_{\pi1}) + r_{o1} + R_E \parallel r_{\pi1})$$

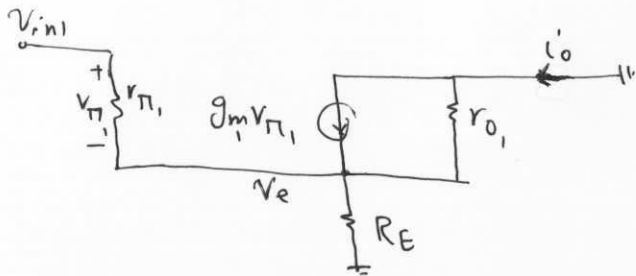To calculate G_m , the small signal model is:



writing node equation at node v_e :


$$\frac{v_e}{R_E \parallel r_{o1}} = (g_{m1} + \frac{1}{r_{\pi1}}) v_{\pi1} = \underbrace{(g_{m1} + \frac{1}{r_{\pi1}})}_{\approx g_{m1}} (V_{in1} - v_e)$$

$$\Rightarrow v_e = \frac{g_{m1}}{g_{m1} + \frac{1}{R_E \parallel r_{o1}}} V_{in1} \Rightarrow i_o = \frac{v_e}{r_{o1}} - g_{m1} v_{\pi1}$$

$$= \frac{v_e}{r_{o1}} + g_{m1} (v_e - V_{in1}) \Rightarrow G_m = \frac{i_o}{V_{in1}} = + \frac{g_{m1} r_{o1}}{g_{m1} r_{o1} R_E + r_{o1} + R_E}$$

$$\Rightarrow A_v = -G_m R_{out}$$

(34) (b)

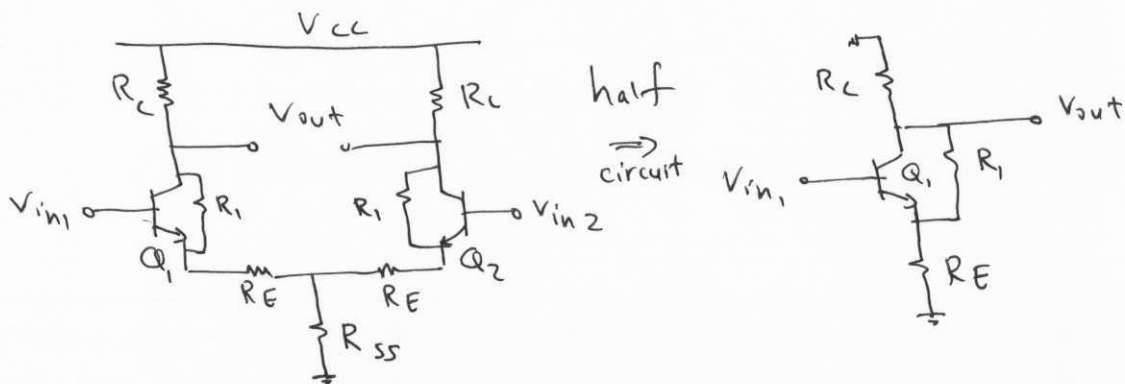


$$R_{out} = R_C \parallel \left(g_{m1} (r_{o1} \parallel R_1) (R_E \parallel r_{\pi 1}) + (r_{o1} \parallel R_1) + (R_E \parallel r_{\pi 1}) \right)$$

Similar to the approach in part (a)

$$G_m = + \frac{g_{m1} (r_{o1} \parallel R_1)}{g_{m1} (r_{o1} \parallel R_1) R_E + (r_{o1} \parallel R_1) + R_E}$$


$$\Rightarrow A_v = -G_m R_{out}$$

(51)

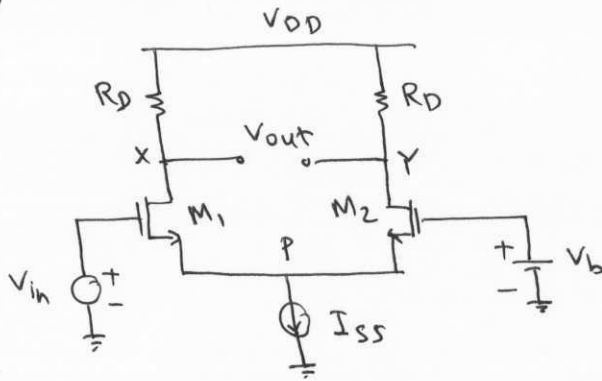

$$g_{m1} = g_{m2} = g_m$$

(a)

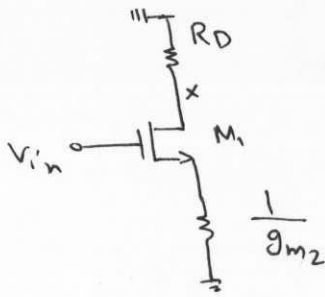


$$v_x = -g_{m1} v_{gs1} R_D =$$

$$-g_{m1} \frac{\frac{1}{g_{m1}}}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} v_{in} R_D =$$

$$-\frac{g_{m1} g_{m2}}{g_{m1} + g_{m2}} R_D v_{in} = -\frac{g_m}{2} R_D v_{in}$$

(b)

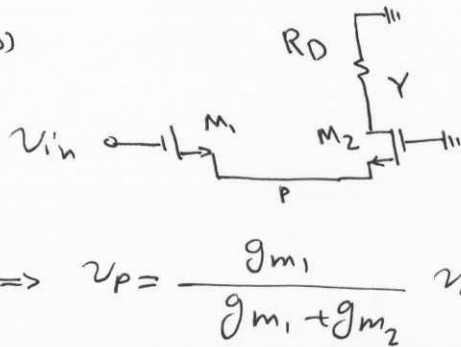

$$v_p = \frac{\frac{1}{g_{m2}}}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} v_{in}$$

$$\Rightarrow v_p = \frac{g_{m1}}{g_{m1} + g_{m2}} v_{in} \Rightarrow$$


$$v_y = -g_{m2} v_{gs2} R_D = g_{m2} v_p R_D = \frac{g_{m1} g_{m2}}{g_{m1} + g_{m2}} R_D v_{in}$$

$$\rightarrow v_y = \frac{g_m}{2} R_D v_{in}$$

$$(c) \frac{v_x - v_y}{v_{in}} = -g_m R_D$$


This value is equal to the gain of the differential amplifier.

(53)

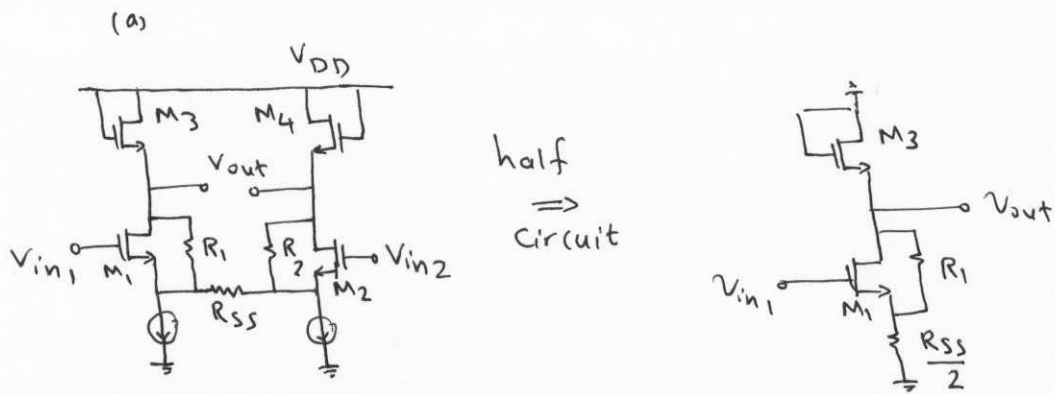

$$R_{out} = (r_{o3} \parallel \frac{1}{g_{m3}}) \parallel (g_{m1} (R_1 \parallel r_{o1}) \frac{R_{SS}}{2} + \frac{R_{SS}}{2} + R_1 \parallel r_{o1})$$

To calculate G_m :

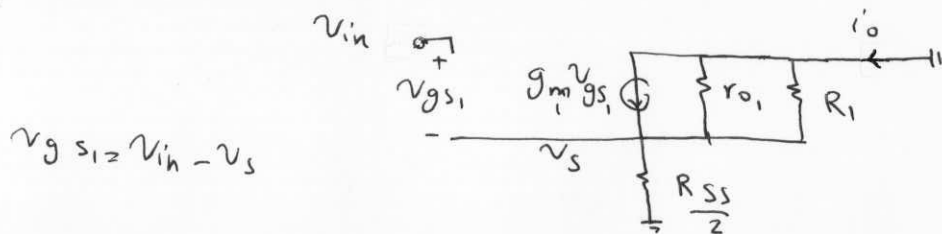

$$v_{gs1} = v_{in} - v_s$$

$$\frac{v_s}{\frac{R_{SS}}{2} \parallel R_1 \parallel r_{o1}} + g_{m1} v_s = g_{m1} v_{in} \Rightarrow v_s = \frac{g_{m1} v_{in}}{g_{m1} + \frac{1}{\frac{R_{SS}}{2} \parallel R_1 \parallel r_{o1}}}}$$


$$i_o = + \frac{v_s}{\frac{R_{SS}}{2}} = + \frac{1}{\frac{R_{SS}}{2}} \frac{g_{m1} v_{in}}{g_{m1} + \frac{1}{\frac{R_{SS}}{2} \parallel R_1 \parallel r_{o1}}} \Rightarrow$$

$$G_m = \frac{i_o}{v_{in}} = + \frac{2 g_{m1}}{R_{SS}} \frac{1}{g_{m1} + \frac{1}{\frac{R_{SS}}{2} \parallel R_1 \parallel r_{o1}}}}$$


$$A_v = -G_m R_{out}$$

53

(b)

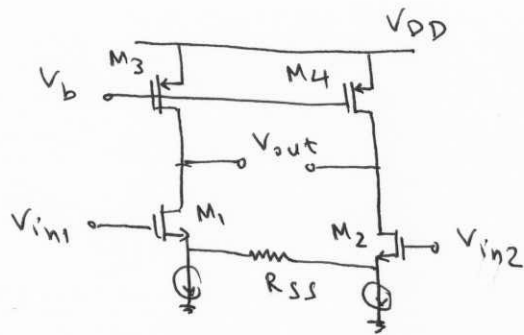


half
⇒
circuit

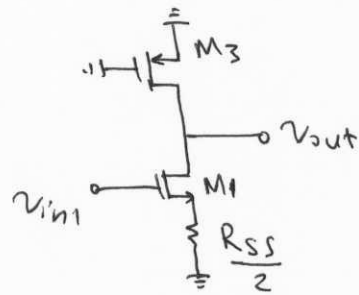

$$R_{out} = r_{o3} \parallel \left(g_{m1} r_{o1} \frac{R_{SS}}{2} + r_{o1} + \frac{R_{SS}}{2} \right)$$


To calculate G_m :

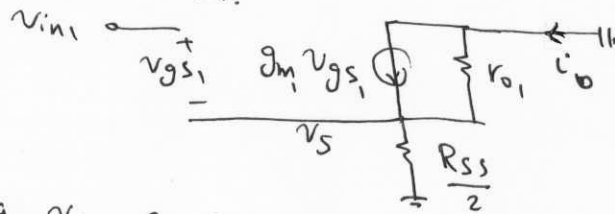


$$\frac{v_s}{r_{o1} \parallel \frac{R_{SS}}{2}} + g_{m1} v_s = g_{m1} v_{in} \Rightarrow v_s = \frac{g_{m1} v_{in}}{g_{m1} + \frac{1}{\frac{R_{SS}}{2} \parallel r_{o1}}}$$

$$G_m = \frac{i_o}{v_{in}} = + \frac{v_s}{\frac{R_{SS}}{2}} \frac{1}{v_{in}} = + \frac{2g_{m1}}{R_{SS}} \frac{1}{g_{m1} + \frac{1}{\frac{R_{SS}}{2} \parallel r_{o1}}}$$

→ $A_{v2} = -G_m R_{out}$

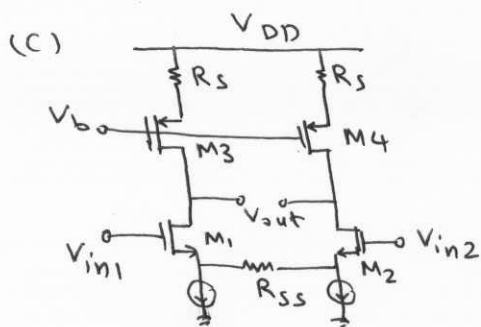

half
⇒
circuit


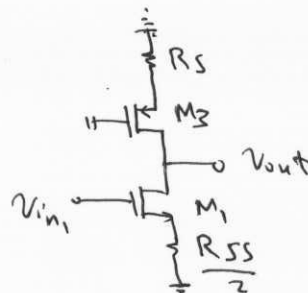


$$R_{out} = (g_{m3} r_{o3} R_s + r_{o3} + R_s) \parallel \left(g_{m1} r_{o1} \frac{R_{SS}}{2} + r_{o1} + \frac{R_{SS}}{2} \right)$$

G_m for this circuit is equal to the one for part (b) so:

$$G_m = + \frac{2g_{m1}}{R_{SS}} \frac{1}{g_{m1} + \frac{1}{\frac{R_{SS}}{2} \parallel r_{o1}}} \Rightarrow A_{v2} = -G_m R_{out}$$

(64)

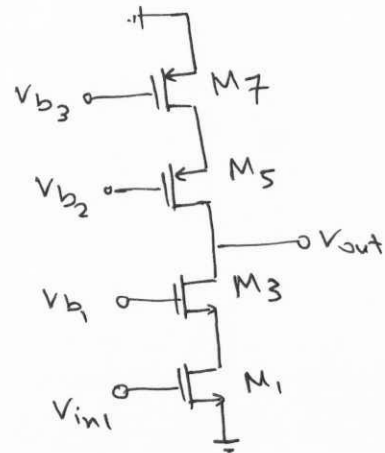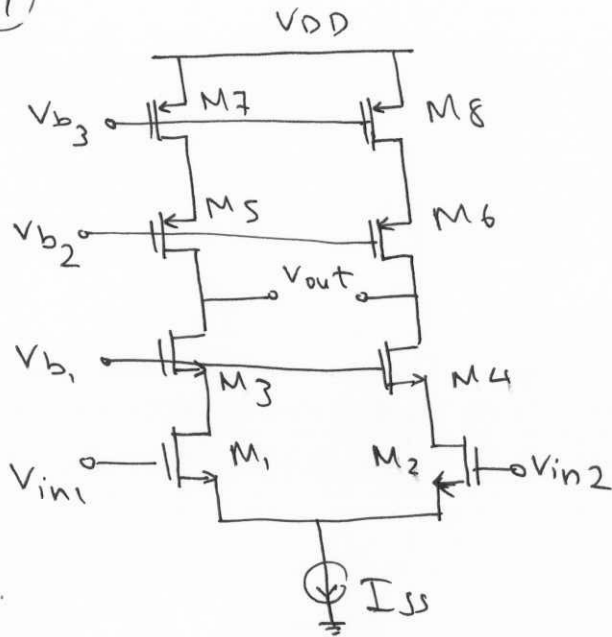

$A_v = 200$, $I_{SS} = 1\text{mA}$, $\mu_n C_{ox} = 100 \mu\text{A/V}^2$
 $\mu_p C_{ox} = 50 \mu\text{A/V}^2$, $\lambda_n = 0.1\text{V}^{-1}$, $\lambda_p = 0.2\text{V}^{-1}$

$(\frac{W}{L})_1 = \dots = (\frac{W}{L})_8 = ?$


$A_v \approx -g_{m1} \left[(g_{m3} r_{o3} r_{o1}) \parallel (g_{m5} r_{o5} r_{o7}) \right] \Rightarrow$

$200 = \sqrt{\mu_n C_{ox} (\frac{W}{L})_1 I_{SS}} \left[\left(\sqrt{\mu_n C_{ox} (\frac{W}{L})_3 I_{SS}} \left(\frac{2}{\lambda_n I_{SS}} \right)^2 \right) \parallel \left(\sqrt{\mu_p C_{ox} (\frac{W}{L})_5 I_{SS}} \left(\frac{2}{\lambda_p I_{SS}} \right)^2 \right) \right]$

$\Rightarrow 200 = \sqrt{10^{-4} (\frac{W}{L})_1 10^{-3}} \left[\left(\sqrt{10^{-4} (\frac{W}{L})_3 10^{-3}} \left(\frac{20}{10^{-3}} \right)^2 \right) \parallel \left(\sqrt{0.5 \times 10^{-4} (\frac{W}{L})_5 10^{-3}} \left(\frac{10}{10^{-3}} \right)^2 \right) \right]$

$\Rightarrow \frac{W}{L} = 33.28$

81)

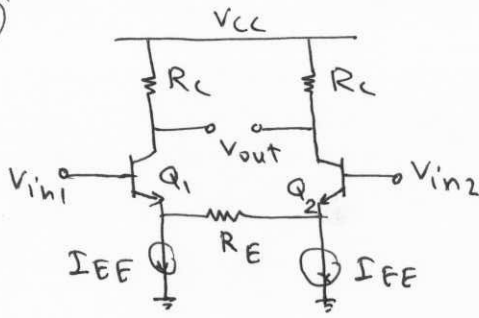


$$A_v = 5$$

$$P = 4 \text{ mW}$$

$$V_{CC} = 2.5 \text{ V}$$

$$V_A = \infty$$

The half circuit is:

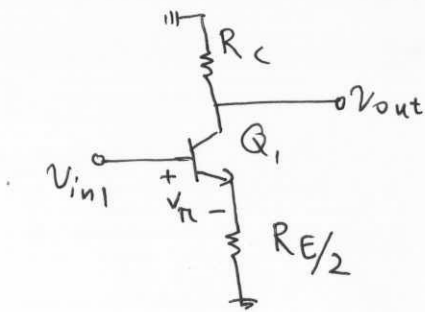

$$A_v = \frac{v_{out}}{v_{in1}} \approx \frac{-g_{m1} v_{\pi} R_c}{v_{in1}} = -\frac{g_{m1} R_c}{\frac{1}{g_{m1}} + \frac{R_E}{2}} v_{in1}$$

$$= -\frac{R_c}{\frac{R_E}{2} + \frac{1}{g_{m1}}}$$

$$P = 4 \text{ mW} = 2 I_{EE} V_{CC} = 5 I_{EE} \Rightarrow I_{EE} = 0.8 \text{ mA}$$

$$g_m = \frac{I_{EE}}{V_T} = 0.03077$$

$$A_v = 5 \Rightarrow \frac{R_c}{\frac{R_E}{2} + 32.5} = 5 \quad (1)$$

if I_{EE} increases by 10%, the gain will be:

$$A_v = \frac{R_c}{\frac{R_E}{2} + \frac{32.5}{1.1}} \Rightarrow 5 < \frac{R_c}{\frac{R_E}{2} + \frac{32.5}{1.1}} < 5 \times 1.02 \quad (2)$$

if I_{EE} decreases by 10% then:

$$5 \times 0.98 < \frac{R_c}{\frac{R_E}{2} + \frac{32.5}{0.9}} < 5 \quad (3)$$

The worse case is:

$$\left\{ \begin{array}{l} \frac{R_C}{\frac{R_E}{2} + \frac{32.5}{1.1}} = 5 \times 1.02 \quad (4) \\ \frac{R_C}{\frac{R_E}{2} + \frac{32.5}{0.9}} = 5 \times 0.98 \quad (5) \end{array} \right.$$


dividing (4) and (5) to (1) leads to:

$$\left\{ \begin{array}{l} \frac{\frac{R_E}{2} + 32.5}{\frac{R_E}{2} + \frac{32.5}{1.1}} = 1.02 \Rightarrow R_E = 236.36 \Omega \\ \frac{\frac{R_E}{2} + 32.5}{\frac{R_E}{2} + \frac{32.5}{0.9}} = 0.98 \Rightarrow R_E = 288.89 \Omega \end{array} \right.$$

To ensure less than 2% gain variation for 10% current variation $R_E = 288.89 \Omega$

$$\text{From (1)} \quad R_C = 5 \left(\frac{R_E}{2} + 32.5 \right) = 884.72 \Omega$$

(91)

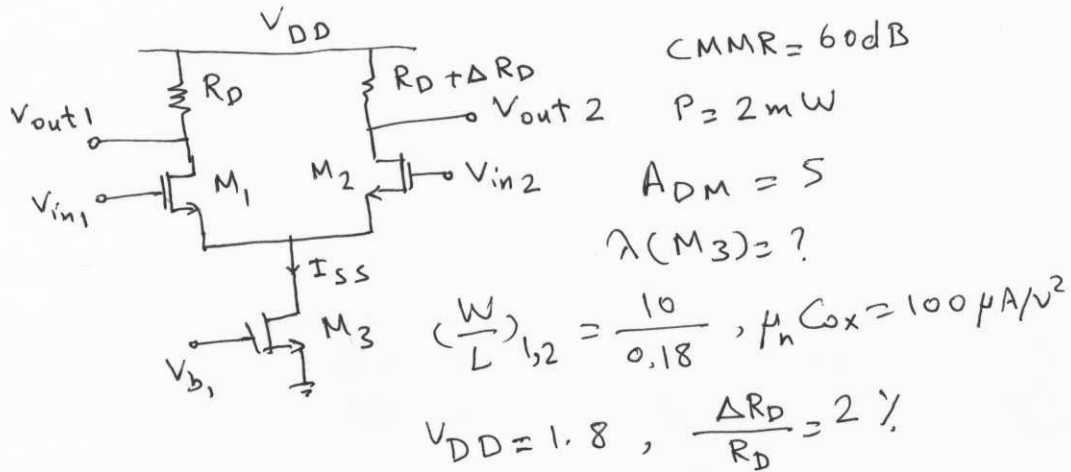


$$P = 2 \text{ mW} = I_{SS} V_{DD} \Rightarrow I_{SS} = \frac{2 \times 10^{-3}}{1.8} = 1.11 \text{ mA}$$

$$A_{DM} = -g_{m1} R_D$$

$$g_{m1} = \sqrt{\mu_n C_{ox} (\frac{W}{L})_1 I_{SS}} = \sqrt{10^{-4} \times \frac{10}{0.18} \times 1.11 \times 10^{-3}} = 2.4845 \text{ mS}$$

$$\Rightarrow R_D = \frac{|A_{DM}|}{g_{m1}} = \frac{5}{2.4845 \times 10^{-3}} = 2.012 \text{ k}\Omega$$

To calculate $A_{CM,DM}$ we have:

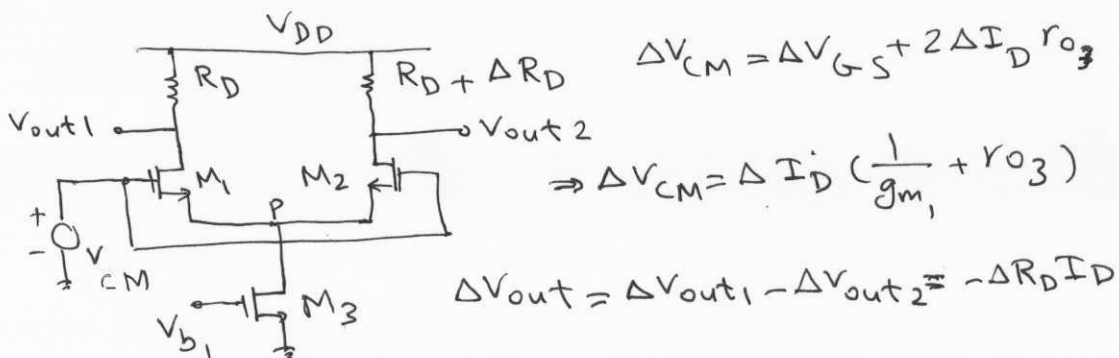

$$\Rightarrow A_{CM,DM} = \frac{\Delta V_{out}}{\Delta V_{CM}} = - \frac{\Delta R_D / 2}{\frac{1}{2g_{m1}} + r_{o3}}$$

$$\Rightarrow CMMR = \frac{A_{DM}}{A_{CM,DM}} = (1 + 2g_{m1} r_{o3}) \frac{R_D}{\Delta R_D}, \quad r_{o3} = \frac{1}{\lambda_3 I_{SS}}$$

$$\Rightarrow \text{CMRR} = 60\text{dB} = 10^3 = \left(1 + 2 \times 2.4845 \times 10^{-3} \frac{1}{\lambda_3 \times 1.11 \times 10^{-3}}\right) 50$$

$$\Rightarrow \lambda_3 = 0.2354$$