## **ECEN 326**

## Homework #5

Due: 3-29-2022, 11:59PM

Homeworks will not be received after due.

Instructor: Sam Palermo

Solve the following problems from the Razavi text:

11.3, 11.19, 11.37, 11.46(a), 11.48

## **Problem Edits**

11.48 – Just derive the output impedance transfer function. No sketch is necessary.