

# ECEN326: Electronic Circuits

## Fall 2022

---

### Lecture 5: Operational Transconductance Amplifiers (OTAs)



Sam Palermo  
Analog & Mixed-Signal Center  
Texas A&M University

# Announcements



---

- HW4 due Mar 8
- This material is related to Lab 7

# OpAmps and OTAs



---

## OpAmp

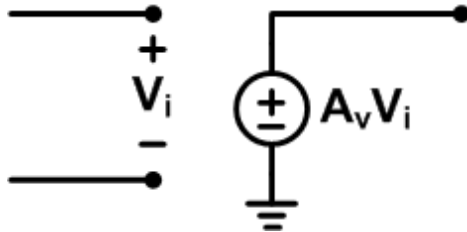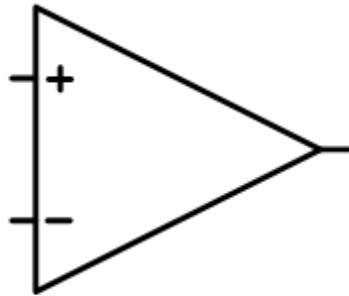

- High voltage gain
- High input impedance
- Voltage source output (low impedance)


## OTA

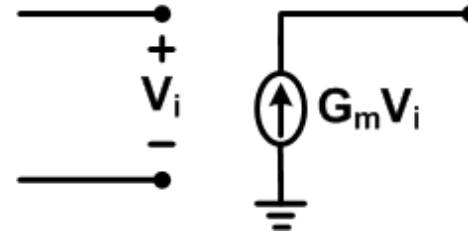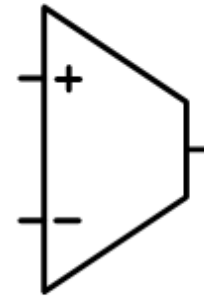

- High “voltage” gain
- High input impedance
- Current source output (high impedance)



# Simple OTA

---

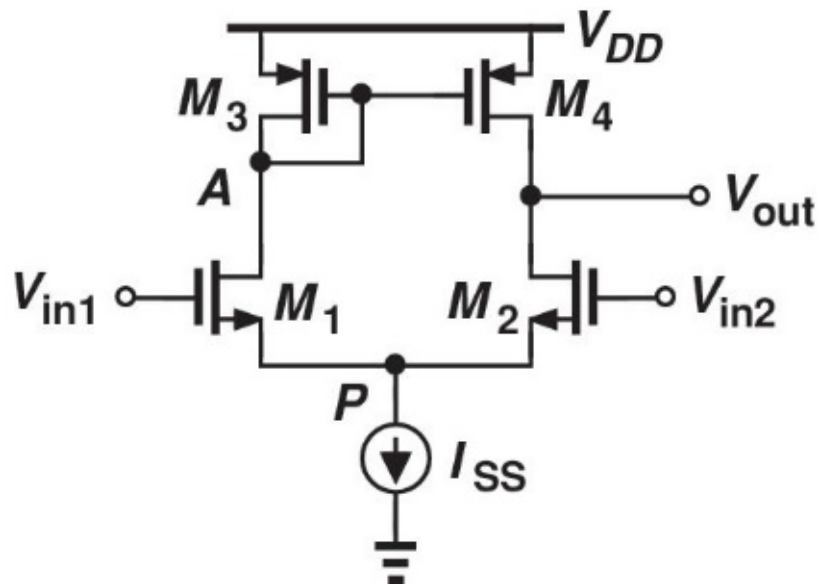

- Important Parameters
  - Transconductance
  - Output Resistance
  - Differential Gain
  - Common-Mode Input Range
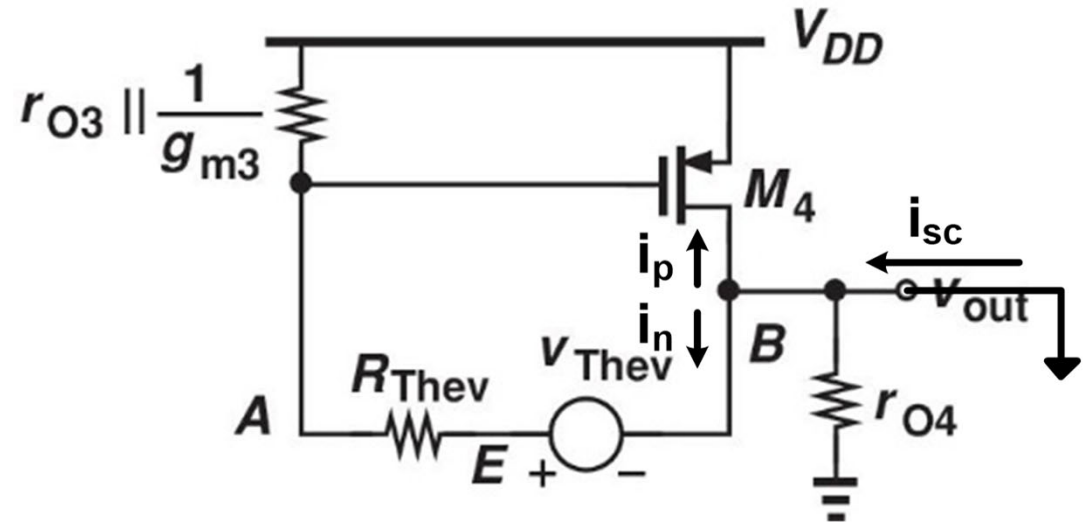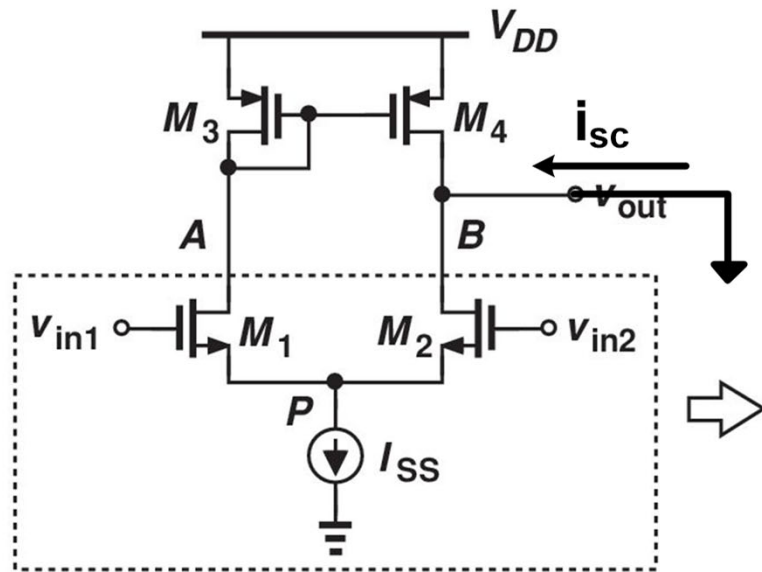
# Simple OTA Transconductance: Rigorous Analysis



From Lecture 3

$$v_{Thev} = -g_{mn}r_{ON}(v_{in1} - v_{in2}) \text{ and } R_{Thev} = 2r_{ON}$$

To find  $i_{sc}$ , we need to find  $i_p$  and  $i_n$

$$i_p = g_{m4}v_A$$

$$v_A = \frac{\frac{1}{g_{m3}} \parallel r_{O3}}{\frac{1}{g_{m3}} \parallel r_{O3} + 2r_{ON}} (-g_{mn}r_{ON}(v_{in1} - v_{in2})) \approx -\frac{g_{mn}}{2g_{m3}}(v_{in1} - v_{in2})$$

$$i_p = g_{m4}v_A = -\frac{g_{mn}}{2}(v_{in1} - v_{in2})$$


$$i_n = \frac{-g_{mn}r_{ON}(v_{in1} - v_{in2})}{2r_{ON} + \frac{1}{g_{m3}}} \approx -\frac{g_{mn}}{2}(v_{in1} - v_{in2})$$

$$i_{sc} = i_p + i_n = -g_{mn}(v_{in1} - v_{in2})$$

$$G_m = \frac{i_{sc}}{v_{in1} - v_{in2}} = -g_{mn}$$
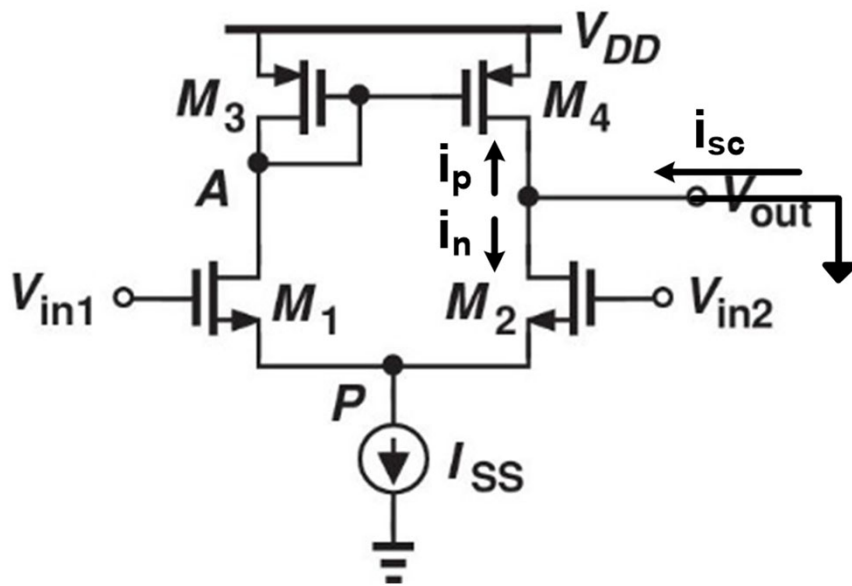
# Simple OTA Transconductance: Informal Virtual Ground Approach

- As the differential circuit is not purely symmetric, we cannot formally assume a virtual ground at node P
- However, if the differential pair transistors M1 and M2 have high output resistance, a virtual ground can be approximated at node P to simplify the analysis



$$i_n = g_{m2}v_{in2}$$


Assuming an ideal current mirror load

$$i_p = -g_{m1}v_{in1}$$

$$i_{sc} = i_p + i_n = -g_{m1}v_{in1} + g_{m2}v_{in2}$$

$$G_m = \frac{i_{sc}}{v_{in1} - v_{in2}} = \frac{-g_{m1}v_{in1} + g_{m2}v_{in2}}{v_{in1} - v_{in2}} = -g_{mn}$$

# Simple OTA Output Resistance

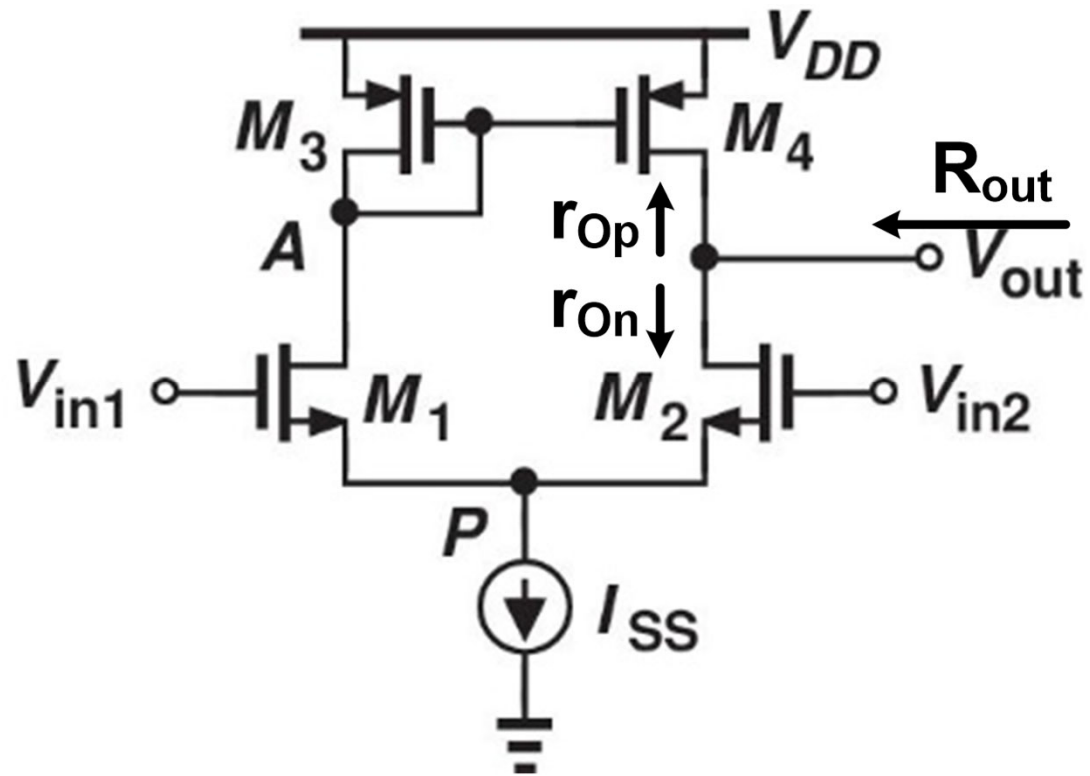


$$R_{out} = r_{Op} \parallel r_{On}$$

It is often useful to also use the output conductance

$$G_{out} = \frac{1}{R_{out}} = g_{op} + g_{on}$$

# Simple OTA Differential Gain

---

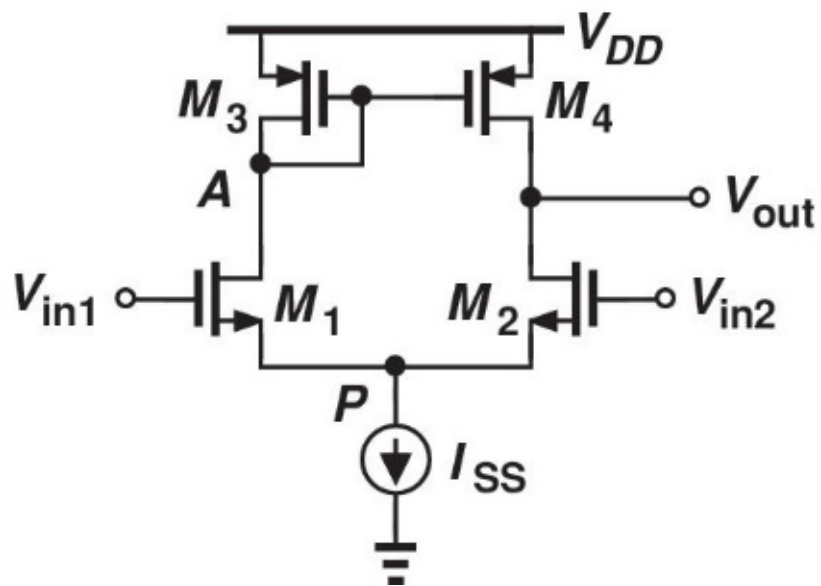


$$A_v = -G_m R_{out} = -(-g_{mn})(r_{On} \| r_{Op})$$

$$A_v = g_{mn}(r_{On} \| r_{Op}) = \frac{g_{mn}}{g_{op} + g_{on}}$$



# Simple OTA Common-Mode Input Range

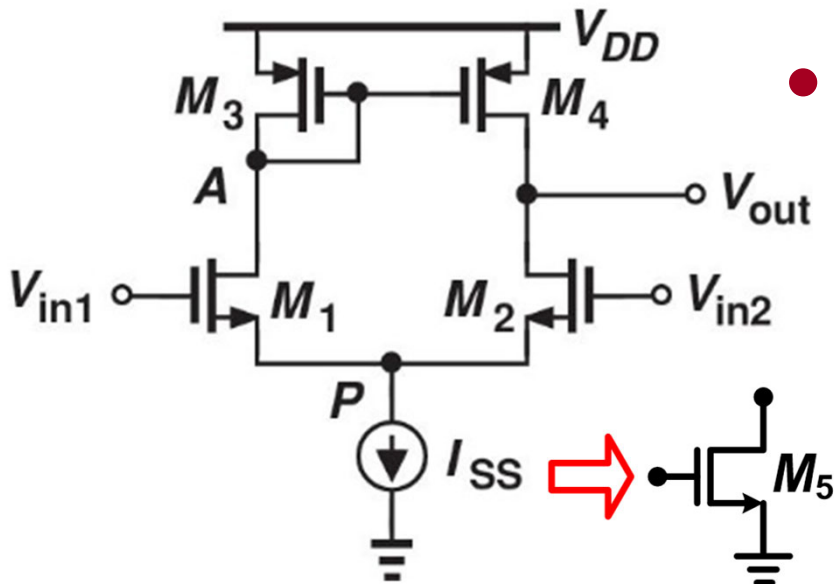

- Common-mode input range set by transistor saturation conditions

- Low-end set by tail current source saturation

$$V_{icm} \geq V_{DSAT5} + V_{GS1} = \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L_5}}} + \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L_1}}} + V_{TH,n1}$$


- High-end set by differential pair saturation

$$V_{icm} \leq V_{ocm} + V_{TH,n1} = V_{DD} - |V_{GS3}| + V_{TH,n1} = V_{DD} - \left( \sqrt{\frac{I_{SS}}{\mu_p C_{ox} \frac{W}{L_3}}} + |V_{TH,p3}| \right) + V_{TH,n1}$$

$$\sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L_5}}} + \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L_1}}} + V_{TH,n1} \leq V_{icm} \leq V_{DD} - \left( \sqrt{\frac{I_{SS}}{\mu_p C_{ox} \frac{W}{L_3}}} + |V_{TH,p5}| \right) + V_{TH,n1}$$

# Bipolar Simple OTA

- Following a similar procedure

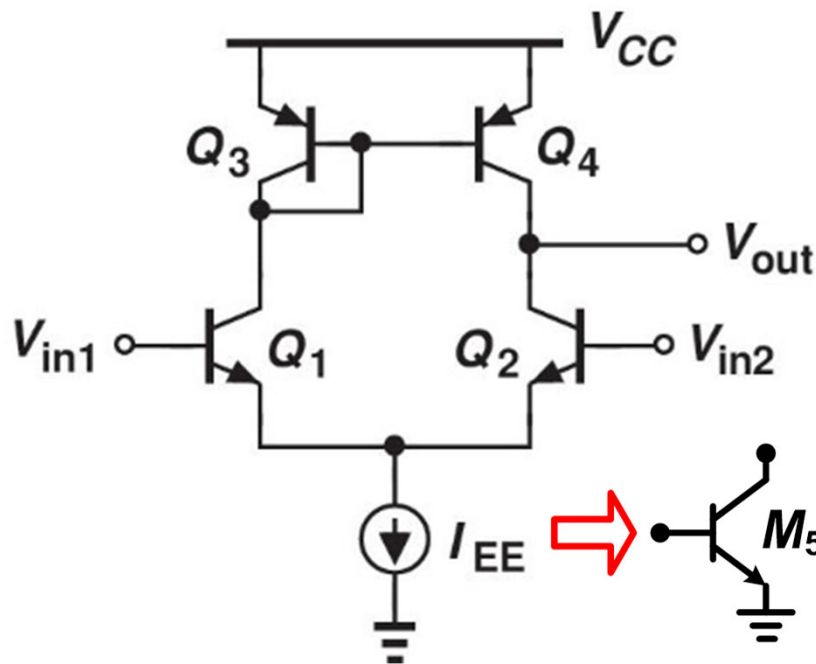

$$G_m = -g_{mn}$$

$$R_{out} = r_{On} \parallel r_{Op}$$

$$A_v = g_{mn}(r_{On} \parallel r_{Op}) = \frac{g_{mn}}{g_{on} + g_{op}}$$

- Low-end  $V_{icm}$  set by keeping tail current source in active mode


$$V_{icm} \geq V_{CE,sat} + V_{BE,on} \approx 0.3V + 0.7V = 1V$$

- High-end  $V_{icm}$  set by keeping differential pair in active mode

$$V_{CE1} = V_{CC} - V_{BE,on} - (V_{icm} - V_{BE,on}) \geq V_{CE,sat}$$

$$V_{icm} \leq V_{CC} - V_{CE,sat} \approx V_{CC} - 0.3V$$

# 3 Current Mirror OTA

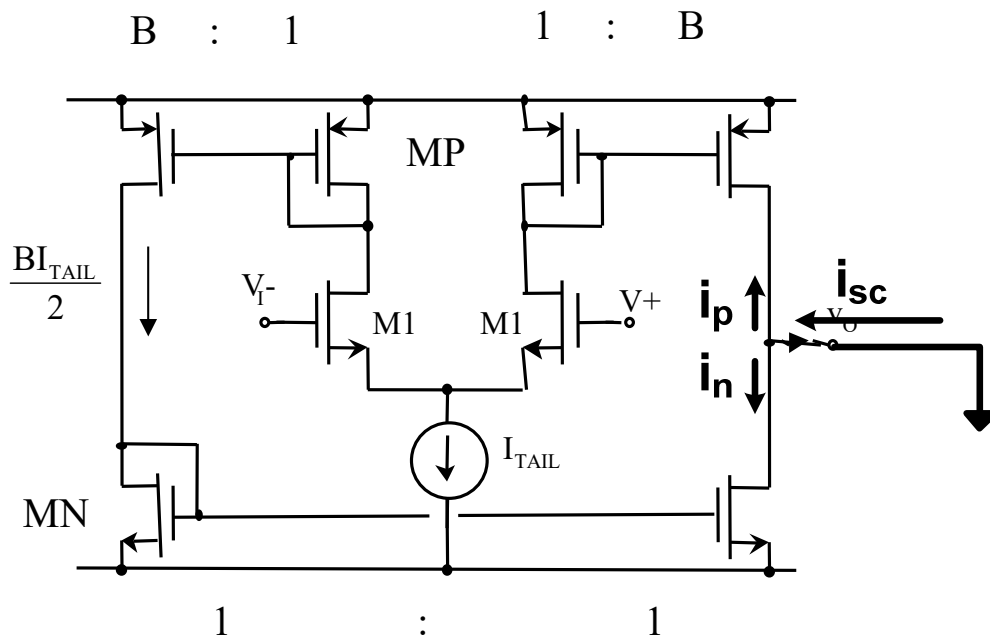

$$i_p = -Bg_{m1}v^+$$

$$i_n = Bg_{m1}v^-$$

$$i_{sc} = i_p + i_n = -Bg_{m1}v^+ + Bg_{m1}v^-$$

$$G_m = \frac{i_{sc}}{v^+ - v^-} = \frac{-Bg_{m1}v^+ + Bg_{m1}v^-}{v^+ - v^-} = -Bg_{m1}$$


$$R_{out} = \frac{r_{Op}}{B} \parallel \frac{r_{O1}}{B} = \frac{1}{B} (r_{Op} \parallel r_{O1})$$

$$G_{out} = B(g_{op} + g_{o1})$$

$$A_v = g_{m1} (r_{Op} \parallel r_{O1})$$

- While  $G_m$  has increased by the current mirror factor  $B$ , the voltage gain remains the same due to the output resistance being reduced by  $B^{-1}$
- Common-mode input range expression remains the same as the previous simple OTA
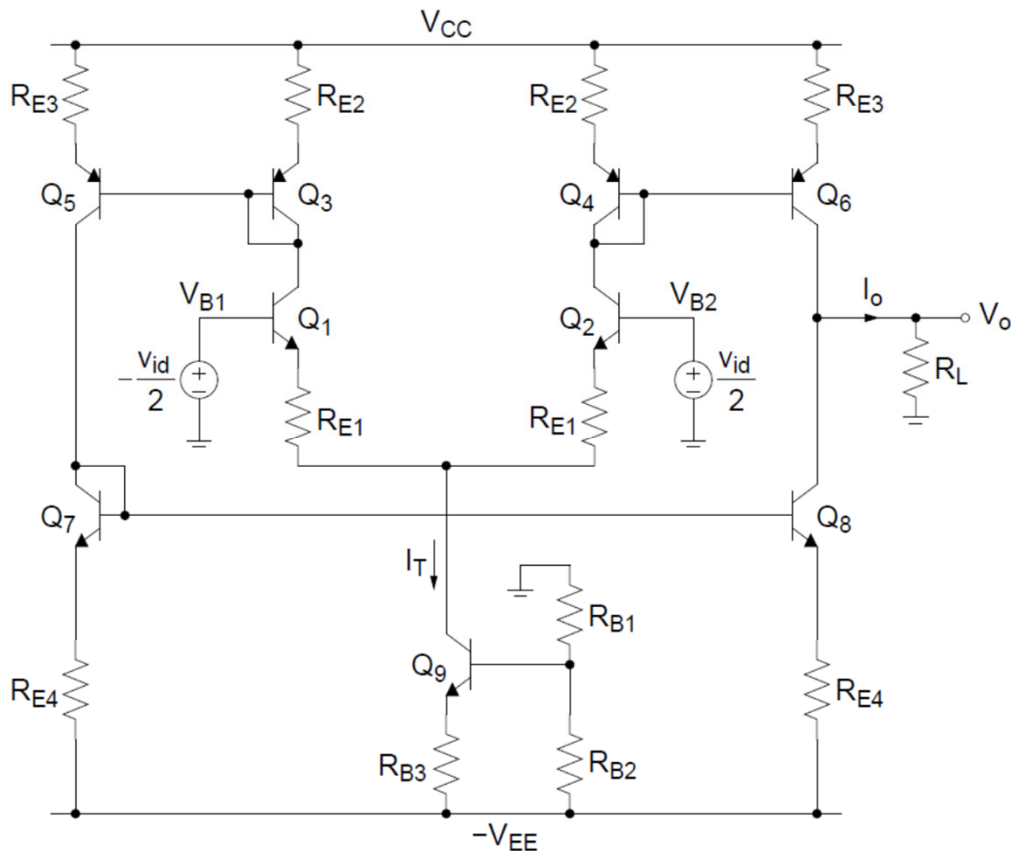
# Bipolar 3 Current Mirror OTA w/ Degenerated $G_m$ (Lab 7)




- In order to improve the distortion performance, emitter resistors have been added in the input differential pair
- In order to improve the output resistance, emitter resistance has been added to all the current mirror/source transistors

Assuming a 1 : 1 ratio for all the current mirrors,  
 $G_m$  is set by the degenerated  $G_m$  of the input transistors

$$G_m = -\frac{\alpha}{r_{e1} + R_{E1}} \approx -\frac{1}{r_{e1} + R_{E1}}$$
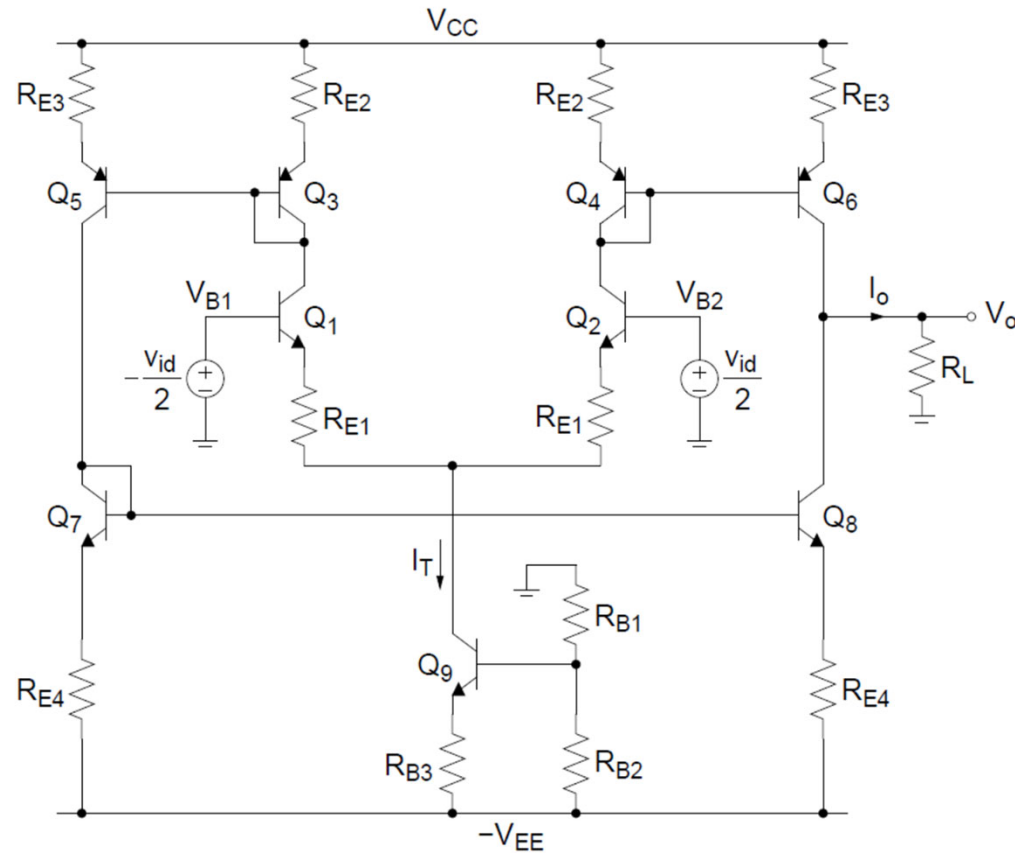
# Bipolar 3 Current Mirror OTA w/ Degenerated $G_m$ (Lab 7)




$$R_{out} \approx (g'_{m6} r_{o6} R'_{E3} + r_{o6}) \parallel (g'_{m8} r_{o8} R'_{E4} + r_{o8})$$

$$g'_{m6} = g_{m6} \frac{r_{\pi 6}}{r_{\pi 6} + r_{e4} + R_{E2}} \approx g_{m6}, \quad R'_{E3} = R_{E3} \parallel (r_{\pi 6} + r_{e4} + R_{E2}) \approx R_{E3} \parallel r_{\pi 6}$$

$$g'_{m8} = g_{m8} \frac{r_{\pi 8}}{r_{\pi 8} + r_{e7} + R_{E4}} \approx g_{m6}, \quad R'_{E4} = R_{E4} \parallel (r_{\pi 8} + r_{e7} + R_{E4}) \approx R_{E4} \parallel r_{\pi 8}$$
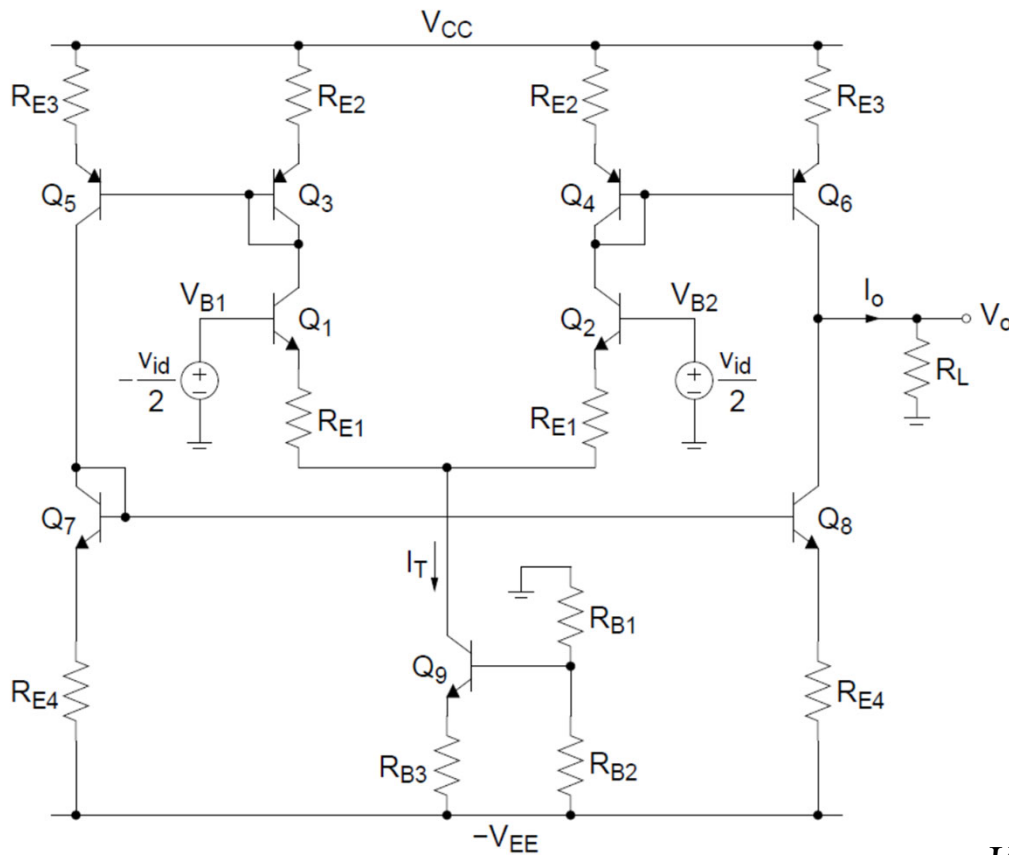
# Bipolar 3 Current Mirror OTA w/ Degenerated $G_m$ (Lab 7)



$$R_{id} = 2(\beta + 1)(r_{e1} + R_{E1})$$

- Low-end  $V_{icm}$  set by keeping tail current source in active mode

$$V_{icm} \geq -V_{EE} + I_T R_{B3} + V_{CE,sat} + \frac{I_T}{2} R_{E1} + V_{BE,on}$$

- High-end  $V_{icm}$  set by keeping differential pair in active mode

$$V_{CE1} = V_{CC} - \frac{I_T}{2} R_{E2} - V_{BE,on} - (V_{icm} - V_{BE,on}) \geq V_{CE,sat}$$

$$V_{icm} \leq V_{CC} - \frac{I_T}{2} R_{E2} - V_{CE,sat}$$

- Maximum differential input amp. for good distortion

$$|v_{id,max}| = I_T R_{E1}$$

# Simulating the 3 Current Mirror OTA

- To simulate differential amplifiers, use voltage-controlled voltage sources (VCVS or "E" elements) to generate the differential input signal and monitor the current through the load resistor


Note: This example is designed for 2X the Lab 7 Gm

Single-ended input source

DC voltage source to set input DC level

2 VCVS to generate differential inputs

Monitor  $I(RL)$

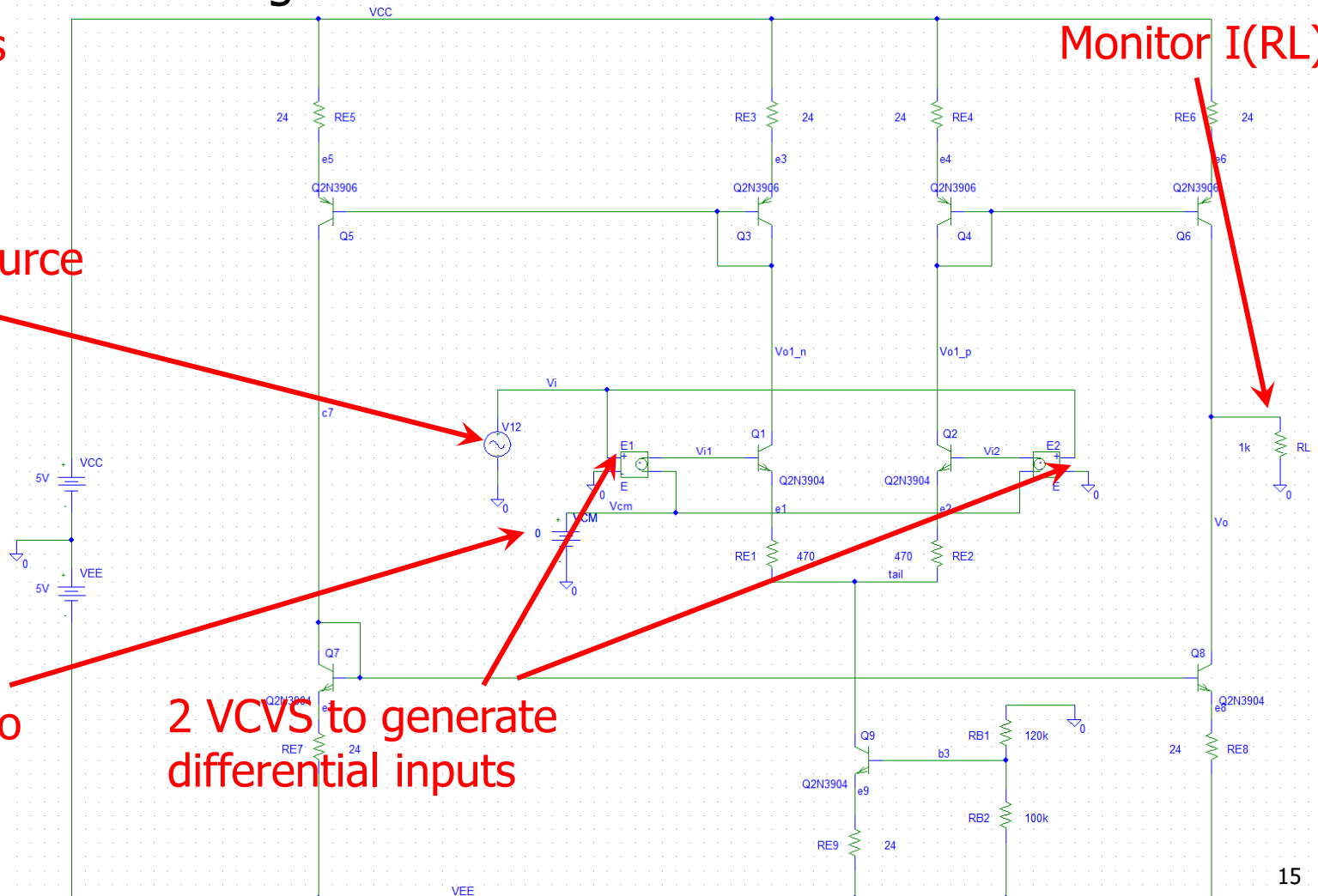






# Simulating Transconductance

- $G_m = 2.01\text{mA/V}$

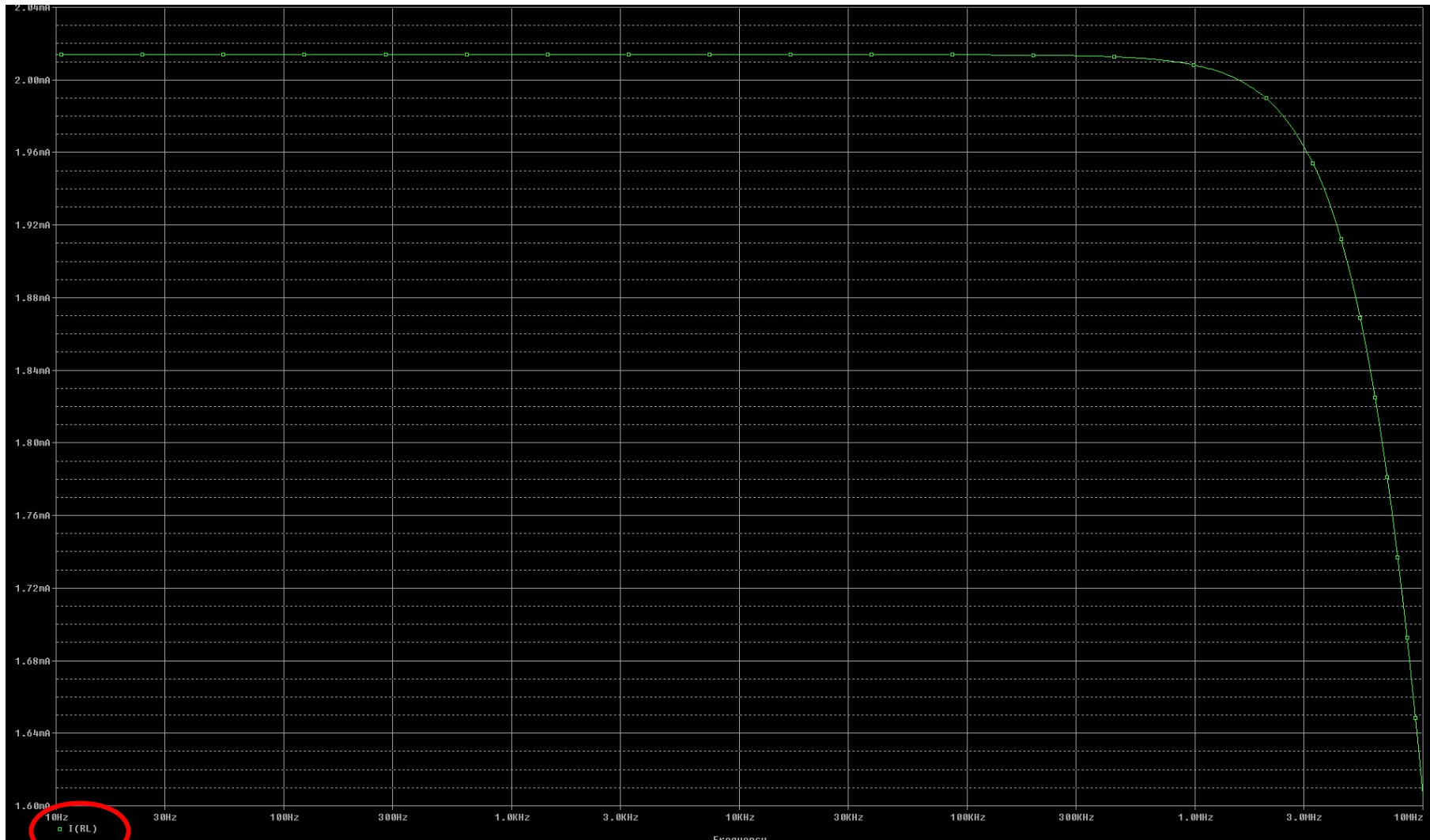





# Simulating THD

- Set input source to differential input amplitude spec
  - For Lab 7, that is 2V
- Check the THD at 3 different common-mode points
  - 0V,  $V_{CM,min}$ ,  $V_{CM,max}$


$$V_{CM} = 0V$$

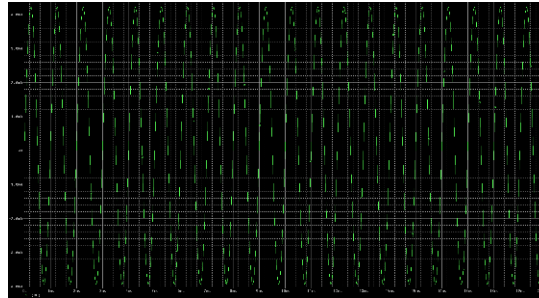

$$V_{CM} = -2V$$

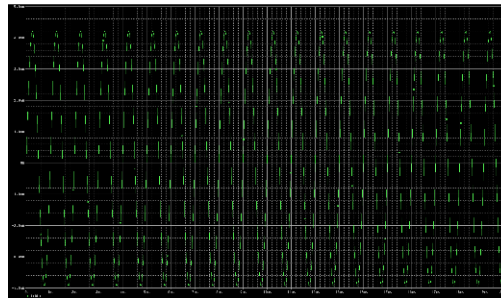

$$V_{CM} = 2V$$

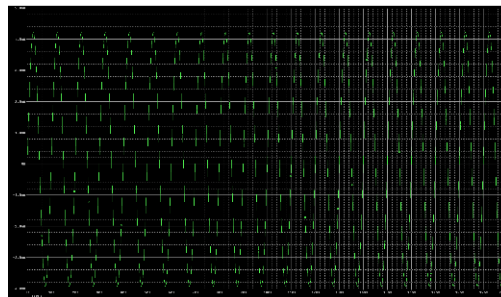

FOURIER COMPONENTS OF TRANSIENT RESPONSE I(R\_RL)

DC COMPONENT = 1.399475E-04

| HARMONIC NO | FREQUENCY (HZ) | FOURIER COMPONENT | NORMALIZED COMPONENT | PHASE (DEG) | NORMALIZED PHASE (DEG) |
|-------------|----------------|-------------------|----------------------|-------------|------------------------|
| 1           | 1.000E+03      | 4.071E-03         | 1.000E+00            | -5.660E-03  | 0.000E+00              |
| 2           | 2.000E+03      | 4.291E-06         | 1.054E-03            | -8.948E+01  | -8.947E+01             |
| 3           | 3.000E+03      | 1.216E-05         | 2.987E-03            | 1.798E+02   | 1.798E+02              |
| 4           | 4.000E+03      | 9.279E-07         | 2.279E-04            | -9.069E+01  | -9.066E+01             |
| 5           | 5.000E+03      | 2.160E-06         | 5.305E-04            | -1.797E+02  | -1.796E+02             |

TOTAL HARMONIC DISTORTION = 3.220127E-01 PERCENT

FOURIER COMPONENTS OF TRANSIENT RESPONSE I(R\_RL)

DC COMPONENT = 1.386942E-04

| HARMONIC NO | FREQUENCY (HZ) | FOURIER COMPONENT | NORMALIZED COMPONENT | PHASE (DEG) | NORMALIZED PHASE (DEG) |
|-------------|----------------|-------------------|----------------------|-------------|------------------------|
| 1           | 1.000E+03      | 4.073E-03         | 1.000E+00            | -5.699E-03  | 0.000E+00              |
| 2           | 2.000E+03      | 3.503E-06         | 8.602E-04            | -8.934E+01  | -8.933E+01             |
| 3           | 3.000E+03      | 9.537E-06         | 2.342E-03            | 1.797E+02   | 1.797E+02              |
| 4           | 4.000E+03      | 1.118E-06         | 2.745E-04            | -9.057E+01  | -9.055E+01             |
| 5           | 5.000E+03      | 4.571E-06         | 1.122E-03            | -1.798E+02  | -1.798E+02             |

TOTAL HARMONIC DISTORTION = 2.749084E-01 PERCENT

FOURIER COMPONENTS OF TRANSIENT RESPONSE I(R\_RL)

DC COMPONENT = 1.410955E-04

| HARMONIC NO | FREQUENCY (HZ) | FOURIER COMPONENT | NORMALIZED COMPONENT | PHASE (DEG) | NORMALIZED PHASE (DEG) |
|-------------|----------------|-------------------|----------------------|-------------|------------------------|
| 1           | 1.000E+03      | 4.067E-03         | 1.000E+00            | -5.759E-03  | 0.000E+00              |
| 2           | 2.000E+03      | 4.976E-06         | 1.223E-03            | -8.956E+01  | -8.954E+01             |
| 3           | 3.000E+03      | 1.330E-05         | 3.270E-03            | 1.798E+02   | 1.798E+02              |
| 4           | 4.000E+03      | 7.584E-07         | 1.865E-04            | -9.070E+01  | -9.067E+01             |
| 5           | 5.000E+03      | 8.260E-07         | 2.031E-04            | -1.791E+02  | -1.791E+02             |

TOTAL HARMONIC DISTORTION = 3.502601E-01 PERCENT

# Simulating Output Resistance

- Ground input source and apply an AC-coupled voltage stimulus at output
- With output source AC=1, plot the ratio of  $V(V_{out})$  over the current through the coupling capacitor

