

**Texas A&M University
Department of Electrical and Computer Engineering**

ECEN 474/704 – (Analog) VLSI Circuit Design

Spring 2016

Exam #1

Instructor: Sam Palermo

- Please write your name in the space provided below
- Please verify that there are 5 pages in your exam
- You may use one double-sided page of notes and equations for the exam
- Good Luck!

| Problem | Score | Max Score |
|--------------|-------|------------|
| 1 | | 40 |
| 2 | | 40 |
| 3 | | 20 |
| Total | | 100 |



Name: SAM PALERMO

UIN: _____

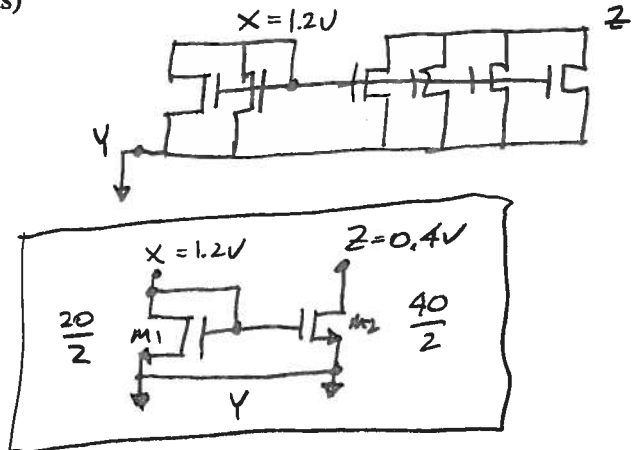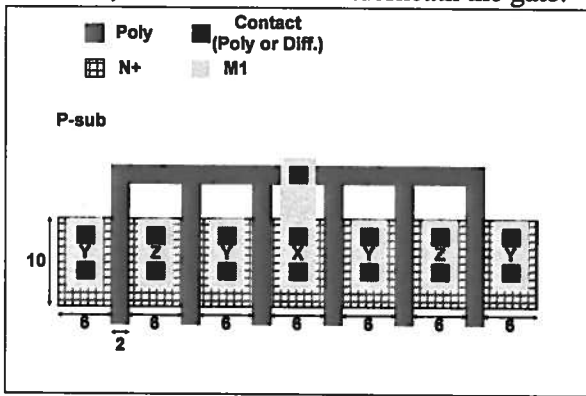
Problem 1 (40 points)

For the layout below, assume that all the commonly labeled diffusion areas are connected with the appropriate metal layers. Assume that $V_X=1.2V$, $V_Y=0V$, $V_Z=0.4V$, $V_{T0}=0.7V$, $\gamma=0$, and that all Spice parameters are given (i.e. C_j , C_{jsw} , C_{jc} , C_{ox} , C_{ov}). The dimensions are given in μm , with all the poly gates having a length of $2\mu m$ and $L_D=0.1\mu m$.

- Draw the equivalent circuit. Combine all parallel transistors and given the total width and length of the equivalent transistors. (15 points)
- What region(s) are the transistors operating in? (5 points)
- For node X only, give an expression and calculate the total gate cap. (10 points)
- For node Z only, give an expression and calculate the total junction cap. Note for the perimeter terms, include the sides underneath the gate. (10 points)



a. All unit transistors $10/2$

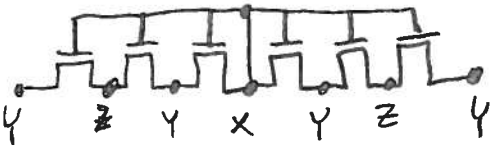

b. $M1 \Rightarrow V_{GS} = V_{OS} = 1.2V > V_T$
 $V_{OS} > V_{GS} - V_T \Rightarrow$ Saturation

$M2 \Rightarrow V_{GS} = 1.2V > V_T$
 $V_{OS} = 0.4V$ $V_{GS} - V_T = 1.2V - 0.7V = 0.5$
 $V_{OS} < V_{GS} - V_T \Rightarrow$ Triode

c. For $C_{gx} \Rightarrow M1 = Sat \Rightarrow C_{gs} + C_{gd}^{shared\ out} = \frac{2}{3}(20\mu)(1.8\mu)(C_{ox} + 20\mu C_{ov}) = 2\frac{2}{3}\mu^2 C_{ox} + 20\mu C_{ov}$
 $M2 = Triode = C_{gs} + C_{gd} = 2 \left[\frac{1}{2}(40\mu)(1.8\mu)C_{ox} + 40\mu C_{ov} \right] = 72\mu^2 C_{ox} + 80\mu C_{ov}$


Total $C_{gx} = 96\mu^2 C_{ox} + 100\mu C_{ov}$

d. $C_{jz} \Rightarrow M2 = Triode \Rightarrow C_{jz} = A_z C_j + P_z C_{jsw} + C_{jc} \frac{w_z \text{ left}}{2}$
 $C_{jz} = 2(6\mu)(10\mu)C_j + (2)(2)(6\mu + 10\mu)C_{jsw} + \frac{(40\mu)(1.8\mu)}{2}C_{jc}$

$C_{jz} = 120\mu^2 C_j + 64\mu C_{jsw} + 36\mu^2 C_{jc}$

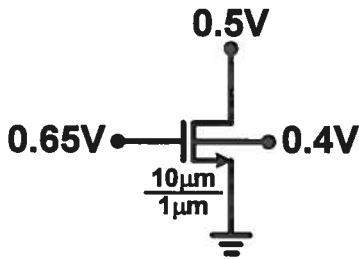Problem 2 (40 points)

For the transistor below, assume $V_{T0}=0.7V$, $\gamma=0.45V^{1/2}$, and $2\Phi_F=0.9V$.



$$I_{DS} = I_o \exp\left(\frac{(V_{GS} - V_{Tn})q}{\zeta kT}\right) \left(1 - \exp\left(-\frac{V_{DS}q}{kT}\right)\right) \quad (\text{Subthreshold})$$

$$I_{DS} = B \frac{W}{L - 2L_D} (V_{GS} - V_{Tn})^\alpha (1 + \lambda V_{DS}) \left(2 - \frac{V_{DS}}{V_{DSAT}}\right) \left(\frac{V_{DS}}{V_{DSAT}}\right) \quad (\text{Triode})$$

$$I_{DS} = B \frac{W}{L - 2L_D} (V_{GS} - V_{Tn})^\alpha (1 + \lambda V_{DS}) \quad (\text{Saturation})$$

$$V_{Tn} = V_{T0} + \gamma \left(\sqrt{|2\Phi_F| + V_{SB}} - \sqrt{|2\Phi_F|} \right)$$

$$V_{DSAT} = V_{GS} - V_{Tn}$$

a. Calculate V_T and state the transistor's operation region. (10 points)

$$V_T = 0.7V + 0.45V^{1/2} \left(\sqrt{0.9V - 0.4V} - \sqrt{0.9V} \right) = 0.591V$$

$$V_{GS} - V_T = 0.65V - 0.591V = 58.7mV$$

$$V_{DS} = 0.5V$$

$$V_T = 0.591V$$

$$V_{DS} > V_{GS} - V_T \Rightarrow \text{Saturation}$$

Operation Region = Saturation


b. Using the appropriate I_{DS} equation above, derive and sketch the small-signal model of the transistor. Include expressions for the g_m , g_o , and g_{mb} . (20 points)

$$g_m = \frac{\partial I_{DS}}{\partial V_{GS}} \bigg|_Q = B \frac{W}{L_{eff}} \alpha (V_{GS} - V_T)^{\alpha-1} (1 + \lambda V_{DS})$$

$$g_o = \frac{\partial I_{DS}}{\partial V_{DS}} \bigg|_Q = B \frac{W}{L_{eff}} (V_{GS} - V_T)^\alpha (\lambda)$$

$$g_{mb} = B \frac{W}{L_{eff}} \alpha (V_{GS} - V_T)^{\alpha-1} (-1)(-1)(1 + \lambda V_{DS}) \frac{\gamma}{2\sqrt{|2\Phi_F| + V_{SB}}}$$

$$= \frac{\gamma g_m}{2\sqrt{|2\Phi_F| + V_{SB}}}$$

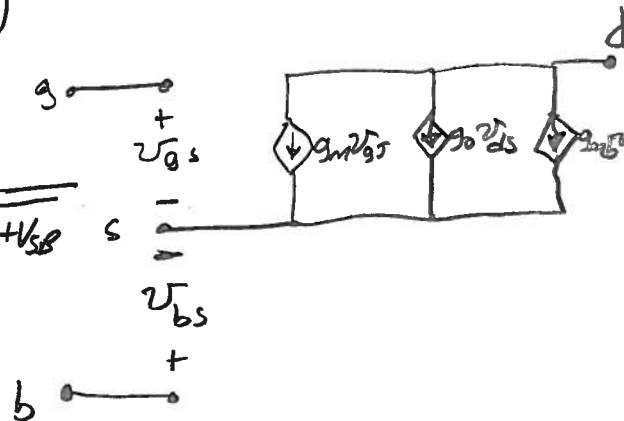

c. Assume that $B=65\mu A/V^\alpha$, $\lambda=0.1V^{-1}$, and $L_D=0.1\mu m$. Calculate the transistor's intrinsic gain (g_m/g_o) for both $\alpha=2$ and $\alpha=1$. (10 points)

$$\frac{g_m}{g_o} = \frac{B \frac{W}{L_{eff}} \alpha (V_{GS} - V_T)^{\alpha-1} (1 + \lambda V_{DS})}{B \frac{W}{L_{eff}} (V_{GS} - V_T)^\alpha (\lambda)}$$

$$\alpha=2 \text{ Intrinsic Gain } (g_m/g_o) = 358 \text{ V/V}$$

$$\alpha=1 \text{ Intrinsic Gain } (g_m/g_o) = 179 \text{ V/V}$$

$$= \left(\frac{\alpha}{V_{GS} - V_T} \right) \left(\frac{1 + \lambda V_{DS}}{\lambda} \right) \Rightarrow \left(\frac{2}{58.7mV} \right) \left(\frac{1 + (0.1V^{-1})(0.5V)}{0.1V^{-1}} \right) = 358 \text{ V/V}$$

Problem 3 (20 points)

Sketch a layout that matches **three** capacitors of unit size 2.2, 4.5, and 6.8. Assume that the unit capacitors are sized $5\mu\text{m} \times 5\mu\text{m}$. **Make sure to give the non-unit capacitor(s) dimensions.** In the sketch clearly label the critical dimensions and use at least 2 layout matching techniques. **Also, write specifically the 2 layout matching techniques that you are using.** Note, if you use a common-centroid layout technique, it doesn't have to have perfect center-of-mass matching, but it should be close.

Need to match $\frac{\text{Perimeter}}{\text{Area}}$ for all caps

"C1" for 2.2 cap \Rightarrow 1 unit cap + 1 non-unit cap
 $w/A_{nu} = 1.2 A_u \quad (K_1 = 1.2)$

"C2" for 4.5 cap \Rightarrow 3 unit caps + 1 non-unit cap
 $w/A_{nu} = 1.5 A_u \quad (K_2 = 1.5)$

"C3" for 6.8 cap \Rightarrow 5 unit caps + 1 non-unit cap
 $w/A_{nu} = 1.8 A_u \quad (K_3 = 1.8)$

$y_{nu1} = x_u (K_1 - \sqrt{K_1^2 - K_1})$

C1: $= 5\mu(1.2 - \sqrt{1.2^2 - 1.2}) = 3.55\mu$


$x_{nu1} = \frac{K_1 x_u^2}{y_{nu1}} = \frac{1.2(5\mu)^2}{3.55\mu} = 8.45\mu$

C2: $y_{nu2} = 5\mu(1.5 - \sqrt{1.5^2 - 1.5}) = 3.17\mu$

$x_{nu2} = \frac{1.5(5\mu)^2}{3.17\mu} = 11.83\mu$

C3: $y_{nu3} = 5\mu(1.8 - \sqrt{1.8^2 - 1.8}) = 3\mu$

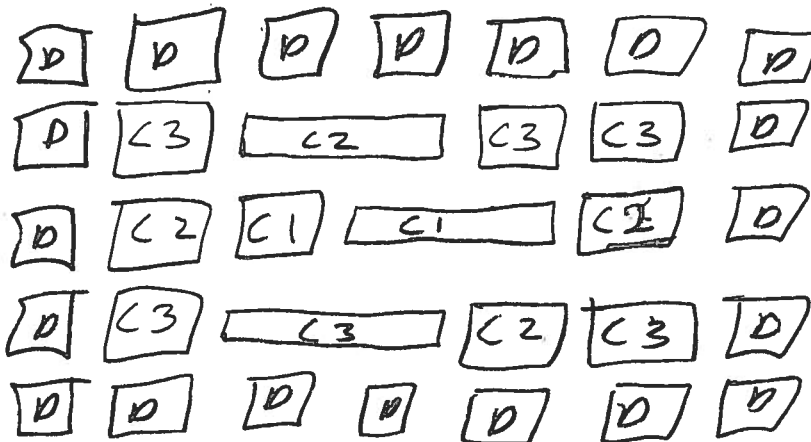$x_{nu3} = \frac{1.8(5\mu)^2}{3\mu} = 15\mu$



Layout Technique #1 = Dummies around entire perimeter

Layout Technique #2 = Common-Centroid (Approximately)

Scratch Paper