

Texas A&M University
Department of Electrical and Computer Engineering

ECEN 474/704 – (Analog) VLSI Circuit Design

Fall 2016

Exam #1

Instructor: Sam Palermo

- Please write your name in the space provided below
- Please verify that there are ⁶ pages in your exam
- You may use one double-sided page of notes and equations for the exam
- Good Luck!

Problem	Score	Max Score
1		40
2		40
3		20
Total		100





Name: SAM PALERMO

UIN: _____

  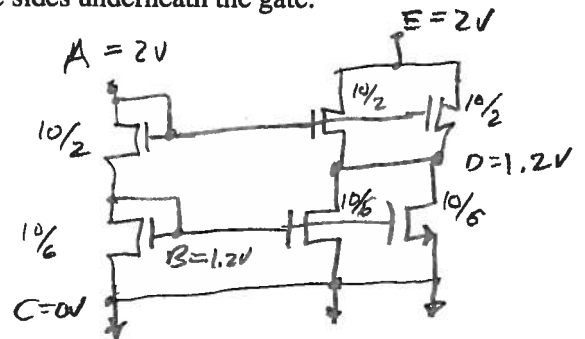 Problem 1 (40 points)

For the layout below, assume that all the commonly labeled diffusion areas are connected with the appropriate metal layers. Assume that $V_A=2V$, $V_B=1.2V$, $V_C=0V$, $V_D=1.2V$, $V_E=2V$, $V_{T0}=0.7V$, $\gamma=0$, and that all Spice parameters are given (i.e. C_j , C_{jsw} , C_{jc} , C_{ox} , C_{ov}). The dimensions are given in μm , with the poly gates having an $L_D=0.1\mu m$.

- Draw the equivalent circuit. Combine all parallel transistors and given the total width and length of the equivalent transistors.
- What region(s) are the transistors operating in?
- For node B only, give an expression and calculate the total gate cap.
- For node D only, give an expression and calculate the total junction cap, including the relevant channel-bulk cap. Note for the perimeter terms, include the sides underneath the gate.



b. $M1 \Rightarrow V_{GS} = V_{DS} = 1.2V > V_T$
 $V_{DS} > V_{GS} - V_T \Rightarrow$ Saturation
 M3 same as M1

$M2 \Rightarrow V_{GS} = V_{DS} = 0.8V > V_T$
 $V_{DS} > V_{GS} - V_T \Rightarrow$ Saturation
 M4 same as M2

d. $C_{j0} = A_0 C_j + P_j C_{jsw} + C_{CBM4}$
 $= (6\mu)(10\mu)(2)C_j + (6\mu + 10\mu)(2)(2)C_{jsw}$
 $+ \frac{2}{3}(20\mu)(1.8\mu)C_{jc}$


$C_{j0} = 120\mu^2 C_j + 64\mu C_{jsw} + 24\mu^2 C_{jc}$

c. For $C_{GB} \Rightarrow M1 = Sat \Rightarrow C_{gs} + C_{gd}$ (Shorted out)
 $= \frac{2}{3}(10\mu)(5.8\mu)C_{ox} + 10\mu C_{ov}$
 $= 38.7\mu^2 C_{ox} + 10\mu C_{ov}$
 $M3 = Sat \Rightarrow C_{gs} + C_{gd}$
 $= \frac{2}{3}(20\mu)(5.8\mu)C_{ox} + 20\mu C_{ov} + 20\mu C_{ov}$
 $= 77.3\mu^2 C_{ox} + 40\mu C_{ov}$
 Total $C_{GB} = 116\mu^2 C_{ox} + 50\mu C_{ov}$

Problem 2 (40 points)

For the circuit shown below, the transistor is operating in a fully velocity saturated region where its DC drain current is given exactly by the given equation.

 
- a. Draw the low-frequency small-signal model of the circuit (neglecting transistor capacitors) and give an expression for the small-signal voltage gain of the circuit, $A_v = v_o/v_i$, as a function of the relevant transistor conductances and the load resistor. Note, you can assume that the input AC-coupling capacitor acts as an ideal short.



Note N_0 V_{DS} dependency $\Rightarrow g_0 = \phi, r_0 = \infty$

$$I_{DS} = v_{sat} C_{ox} W (V_{GS} - V_{Th})$$

$$V_{Th} = V_{T0} + \gamma \left(\sqrt{|2\Phi_F| + V_{SB}} - \sqrt{|2\Phi_F|} \right)$$

 

$$v_o = -(g_m + g_{mb})(-v_i) R_D$$

$$A_v = \frac{v_o}{v_i} = (g_m + g_{mb}) R_D$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = v_{sat} C_{ox} W$$

$$g_{mb} = \frac{\partial I_D}{\partial V_{BS}} = v_{sat} C_{ox} W (-1)(-1) \frac{\gamma}{2\sqrt{|2\Phi_F| + V_{SB}}} = \frac{\gamma g_m}{2\sqrt{|2\Phi_F| + V_{SB}}} = \eta g_m$$

$$A_v = v_o/v_i = (g_m + g_{mb}) R_D$$

where $\eta = \frac{\gamma}{2\sqrt{|2\Phi_F| + V_{SB}}}$

- b. Assume the following DC operating points for the drain and source voltages, $V_{S,Q} = 0.2V$ and $V_{D,Q} = 1V$, and that $v_{sat} C_{ox} = 250 \mu A / (V \cdot \mu m)$, $V_{T0} = 0.7V$, $\gamma = 0.45V^{1/2}$, $2\Phi_F = 0.9V$, and $L_D = 0.1\mu m$. Calculate the necessary transistor width W for $|A_v| = 5V/V$.

$$A_v = (g_m + g_{mb}) R_D = (1 + \eta) g_m R_D = (1 + \eta) v_{sat} C_{ox} W R_D$$

$$W = \frac{A_v}{(1 + \eta) v_{sat} C_{ox} R_D} = \frac{5}{(1.269)(250 \frac{\mu A}{V \mu m}) 1k\Omega} = 15.8 \mu m$$

W for $|A_v| = 5V/V = 15.8 \mu m$

$$\eta = \frac{0.45}{2\sqrt{0.9 - 0.2}} = 0.269$$

Problem 3 (20 points)

a. Poly resistor design

Design and sketch a layout of a 500Ω poly resistor. Assume that the poly $R = 60\Omega/\square$, each ($1\mu\text{m} \times 1\mu\text{m}$) contact has resistance of 10Ω , and fabrication tolerances limit the minimum unit resistor width $W \geq 3\mu\text{m}$.

Use at least 2 fingers in the resistor design. In the sketch clearly label the critical dimensions.


$$R_{\text{total}} = \left(\frac{2R_c}{n} + R_{\square} \frac{L}{W} \right) F \quad \text{where } n = \# \text{ parallel contacts}$$

$$F = \# \text{ fingers (unit } R)$$

$$L = \left(\frac{R_{\text{total}}}{F} - \frac{2R_c}{n} \right) \frac{W}{R_{\square}}$$

$$\text{Set } W = 3\mu\text{m} \quad n = 3 \quad F = 2$$
 
$$L = \left(\frac{500}{2} - \frac{2(10)}{3} \right) \left(\frac{3\mu}{60} \right) = 12.2\mu\text{m}$$



b. Poly resistor parasitic capacitance

The poly resistor has a parallel-plate parasitic capacitance to substrate of $0.1\text{fF}/\mu\text{m}^2$. What is the total parasitic capacitance of the resistor? Include the contact area in the capacitance calculation and assume that the capacitance is only due to the parallel-plate effect, i.e. neglect any fringing capacitance.

$$\text{Resistor Area is } (12.2\mu\text{m} + 2\mu\text{m})(3\mu\text{m})(2) = 86.4\mu\text{m}^2$$

$$C_{\text{parasitic}} = (86.4\mu\text{m}^2)(0.1\text{fF}/\mu\text{m}^2) = 8.64\text{fF}$$

c. N-well resistor design


Design and sketch a layout of a 500Ω n-well resistor. Assume that the n-well $R = 2k\Omega/\square$, each ($1\mu\text{m} \times 1\mu\text{m}$) contact has resistance of 10Ω , and fabrication tolerances limit the minimum unit resistor length $L \geq 6\mu\text{m}$. Use at least 2 fingers in the resistor design. In the sketch clearly label the critical dimensions.

$$R_{\text{total}} = \left(\frac{2R_c}{n} + R_{\square} \frac{L}{W} \right) F$$

$$L = \left(\frac{R_{\text{total}}}{F} - \frac{2R_c}{n} \right) \frac{W}{R_{\square}}$$

$$\text{Set } F=2, W=50\mu\text{m}, n=50$$
 
$$L = \left(\frac{500}{2} - \frac{2(10)}{50} \right) \left(\frac{50\mu\text{m}}{2k} \right) = 6.24\mu\text{m}$$



d. N-well resistor parasitic capacitance

The n-well resistor has a parallel-plate parasitic capacitance to substrate of $1\text{fF}/\mu\text{m}^2$. What is the total parasitic capacitance of the resistor? Include the contact area in the capacitance calculation and assume that the capacitance is only due to the parallel-plate effect, i.e. neglect any fringing capacitance.

$$\text{Resistor Area is } (6.24\mu\text{m} + 3\mu\text{m}) (50\mu\text{m}) (2) = 824\mu\text{m}^2$$

$$C_{\text{parasitic}} = (824\mu\text{m}^2) (1\text{fF}/\mu\text{m}^2) = 824\text{fF}$$

e. If we have to use the 500Ω resistor for a high-frequency application, which design should we choose, the poly or n-well design? Why?

Poly R \Rightarrow Less capacitance

Scratch Paper