

**Texas A&M University**  
**Department of Electrical and Computer Engineering**

**ECEN 474/704 – (Analog) VLSI Circuit Design**

**Spring 2018**

**Exam #2**

**Instructor: Sam Palermo**

- Please write your name in the space provided below
- Please verify that there are 6 pages in your exam
- You may use one double-sided page of notes and equations for the exam
- Good Luck!

Problem	Score	Max Score
1		30
2		30
3		40
<b>Total</b>		<b>100</b>

Name: \_\_\_\_\_


SAM PALERMO

UIN: \_\_\_\_\_


Problem 1 (30 points)

For the following current source obtain the following:

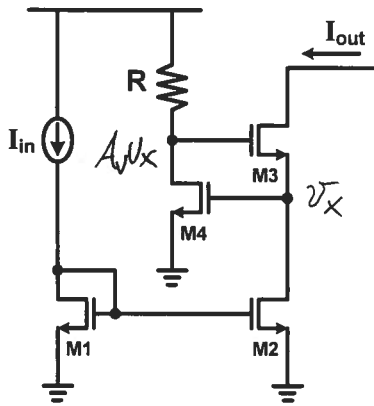- a) Give an expression for the output resistance. You can assume that all transistors are operating in saturation and that you can neglect body effect.
- b) Give an expression for the minimum compliance voltage at the output necessary to keep all transistors in saturation. Assume that all the transistors have the same  $V_{DSAT}$  value.



$\alpha$  SSM

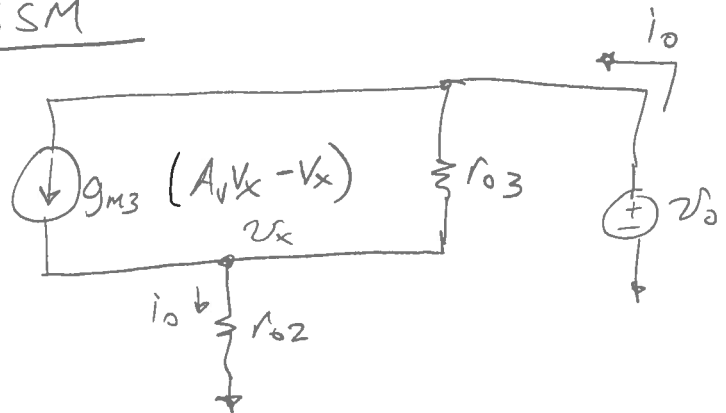

Here  $A_V = -g_{m4} (R || r_{o4})$   
 $= \frac{-g_{m4}}{G + g_{o4}}$

$v_x = i_o r_{o2}$

KCL @  $v_0$ :  $-g_{m3} v_x (1 - A_V) + (v_0 - v_x) g_{o3} - i_o = 0$

$-g_{m3} i_o r_{o2} (1 - A_V) + v_0 g_{o3} - i_o r_{o2} g_{o3} - i_o = 0$

$v_0 g_{o3} = i_o (g_{m3} r_{o2} (1 - A_V) + r_{o2} g_{o3} + 1)$

$R_{out} = g_{m3} r_{o3} (1 - A_V) r_{o2} + r_{o2} + r_{o3} \approx g_{m3} r_{o3} (1 - A_V) r_{o2}$   
 where  $A_V = -g_{m4} (R || r_{o4})$

b. Compliance Voltage:  $V_{out} \geq V_{GS4} + V_{DSAT3}$


$V_{out} \geq V_T + V_{DSAT4} + V_{DSAT3}$

$V_{out} \geq V_T + 2V_{DSAT}$

Problem 2 (30 points)

For the fully differential amplifier below obtain the following:

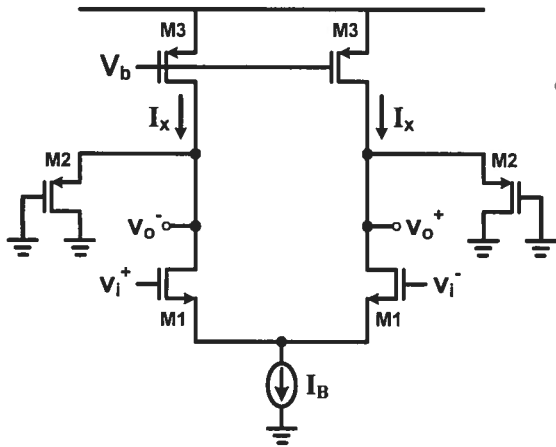- a) Give an expression for the differential gain,  $A_{vd} = (v_o^+ - v_o^-) / (v_i^+ - v_i^-)$ . **Do NOT neglect the transistors'  $r_o$ .** Assume all transistors are operating in saturation and that you can neglect body effect.
- b) Give an expression for the dominant pole of the amplifier. This expression should include all the appropriate transistor capacitances and include the Miller effect when appropriate.



a. 
$$A_{vd} = \frac{g_{m1}}{g_{o1} + g_{o3} + g_{m2} + g_{o2}}$$

b. 
$$\omega_p = \frac{g_{o1} + g_{o3} + g_{m2} + g_{o1}}{C_{DB1} + C_{GD1} + C_{SB2} + C_{GS2} + C_{DB3} + C_{GD3}}$$

Not neglecting Miller in  $C_{GD1}$  because  $1 - (A_{DG}) = 1 - \left( -\frac{1}{A_{vd}} \right)$   
 this generally very small

- c) Now simplify the differential gain expression by letting the transistors'  $r_o = \infty$ . Assume that all the transistors have equal  $W/L$  and that  $\mu_n = 4\mu_p$ . What should the DC current  $I_x$  be as a function of  $I_B$  to achieve a differential gain of 6?

$$\text{With } r_o = \infty \Rightarrow g_o = \phi$$

$$A_{vd} = \frac{g_{m1}}{g_{m2}} = \frac{\sqrt{\mu_n \left( \text{ox} \frac{W}{L} \right) 2 \left( \frac{I_B}{2} \right)}}{\sqrt{\mu_p \left( \text{ox} \frac{W}{L} \right) 2 \left( I_x - \frac{I_B}{2} \right)}} = \sqrt{4 \left( \frac{I_B/2}{I_x - I_B/2} \right)} = 6$$

$$\frac{I_B/2}{I_x - I_B/2} = 9$$


$$\frac{I_B}{18} = I_x - \frac{I_B}{2}$$

$$I_x = \frac{5}{9} I_B$$

Problem 3 (40 points)

For the amplifier below, assume all transistors are operating in saturation and that you can neglect body effect. Obtain expressions for the following:

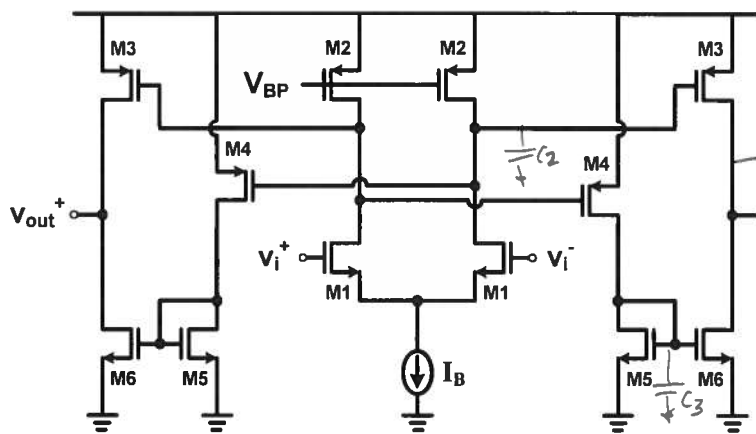- a) Small-signal transconductance.
- b) Output resistance.
- c) DC gain.
- d) The amplifier's three poles. Note, it's OK here to state this as a function of an effective capacitance at a certain node, but make sure to appropriately label the nodes.
- e) Output referred noise current power spectral density. Consider only thermal noise and include all important noise sources.
- f) Input referred noise voltage power spectral density. Consider only thermal noise and include all important noise sources.



a.  $G_m = \frac{g_{m1}}{g_{o1} + g_{o2}} \left( g_{m3} + \frac{g_{m4} g_{m6}}{g_{o4} + g_{m5} + g_{o5}} \right)$

b.  $R_{out} = r_{o3} \parallel r_{o6}$

c.  $A_v = G_m R_{out} = \frac{g_{m1}}{g_{o1} + g_{o2}} \left( g_{m3} + \frac{g_{m4} g_{m6}}{g_{o4} + g_{m5} + g_{o5}} \right) (r_{o3} \parallel r_{o6})$

d.  $\omega_{p1} = \frac{1}{R_{out} C_{out}}, \omega_{p2} = \frac{g_{o1} + g_{o2}}{C_2}, \omega_{p3} = \frac{g_{o4} + g_{m5} + g_{o5}}{C_3}$

e.  $\frac{i_{o,n}^2}{\Delta f} = \frac{16}{3} kT \left[ \left( (g_{m1} + g_{m2}) \left( \frac{1}{g_{o1} + g_{o2}} \right)^2 \left( g_{m3} + \frac{g_{m4} g_{m6}}{g_{o4} + g_{m5} + g_{o5}} \right) \right)^2 + (g_{m4} + g_{m5}) \left( \frac{g_{m6}}{g_{o4} + g_{m5} + g_{o5}} \right)^2 + g_{m3} + g_{m6} \right]$

f.  $\frac{v_{i,n}^2}{\Delta f} = \frac{i_{o,n}^2}{\Delta f} \left( \frac{1}{G_m} \right)^2$

## Scratch Paper